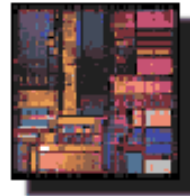


ECE 595Z

Digital VLSI Design Automation

Module 6 (Lectures 21-24): Timing Analysis and Optimization
Lecture 21



Anand Raghunathan

MSEE 318

raghunathan@purdue.edu

Technology mapping: Re-cap

- Technology mapping is a DAG covering problem
 - Convert circuit to be mapped into subject graph, cells from library into pattern graphs
- Two solution approaches discussed
 - Binate covering formulation – considers arbitrary DAGs, but not very scalable in practice
 - Tree covering using dynamic programming – divide DAG into trees, utilize optimal and efficient algorithm to map each tree
 - Inverter heuristic creates additional opportunities for matches, improves solution quality

Technology mapping: Remaining questions


- How to map for minimum delay?
 - Not an additive cost function
 - Delay of a cell depends on its drivers and loads
- How to partition a DAG into trees

Technology Mapping for Delay


- Delay of a gate

$$d(g,i) = \alpha(g,i) + \beta(g) \cdot \gamma(g)$$

 - $\alpha(g,i)$: intrinsic delay of g from input i
 - $\beta(g)$: delay per unit load
 - $\gamma(g)$: capacitive load being driven
- Problem: In tree mapping, γ is NOT known when finding the best match at a vertex
 - γ is determined by matches at fanout



What is the value of γ ?

 

Technology Mapping for Delay : Constant Delay Model

- **Simplification:** Constant delay model
 - Delay of gate is independent of load it drives
- In this case, dynamic programming still works!

```
int min_delay_const_load(v, P){
/* v is a vertex in the tree, P is the set of pattern graphs */
    best_cost = infinity;
    foreach(m = match(v, P)) {
        cost(m) = maxvi ∈ inputs(m) ( α(m,i) + β(m) γ0 +
                                         min_delay_constant_load(vi, P) );
        if(cost(m) < best_cost){
            match(v) = m;
            best_cost = cost(m);
        }
    }
    return best_cost;
}
```

Technology Mapping for Delay : Load-dependent Delay Model



- Consider a set of discrete loads $\Gamma(v) = \{\gamma_1, \gamma_2, \dots, \gamma_k\}$ for vertex v .
 - can be obtained by dividing useful range into bins
- Find best solution for each load at each vertex

```
int min_delay(v,  $\Gamma(v)$ , P){  
    foreach( $\gamma \in \Gamma(v)$ ) {  
        best_cost(v,  $\gamma$ ) = infinity;  
    }  
  
    foreach(m = match(v, P),  $\gamma \in \Gamma(v)$ ){  
        cost(m,  $\gamma$ ) =  $\max_{v_i \in \text{inputs}(m)} (\alpha(m,i) + \beta(m) \gamma +$   
            min_delay( $v_i, \gamma(m,i), P$  ));  
        /*  $\gamma(m,i)$  is input capacitance of match m at input i */  
        if(cost(m,  $\gamma$ ) < best_cost(v,  $\gamma$ )){  
            match(v,  $\gamma$ ) = m;  
            best_cost(v,  $\gamma$ ) = cost(m,  $\gamma$ );  
        }  
    }  
    return best_cost(v,  $\gamma_0$ );  
}
```

- Final step: Given a load at the root of the tree, a backward traversal from the root to the leaves is needed at the end to pick the appropriate matches.



Partitioning a DAG into Trees

  - Trivial Partition: Break the DAG at all multiple fanout points.
 - Guarantees no overlap among trees (no logic replication).
 - Sometimes leads to lots of small trees.



Partitioning a DAG into Trees

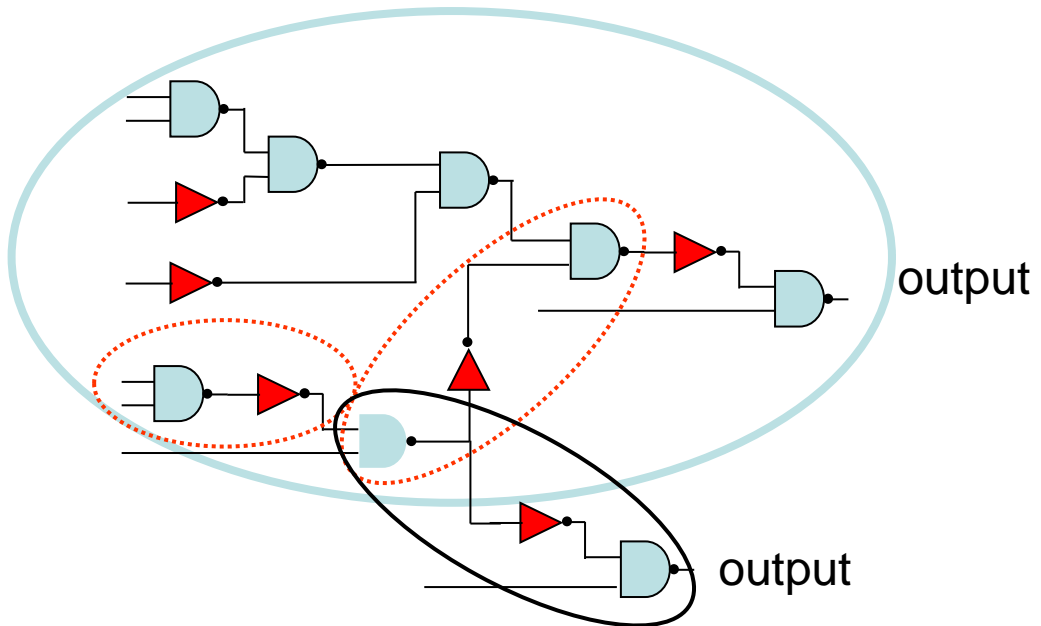 - Single-cone partition
 - From a single output, form a large tree back to the primary inputs;
 - Map successive outputs until they hit match output formed from mapping previous primary outputs.
 - Duplicates some logic (where trees overlap)
 - Produces larger trees, better area results in practice



Summary: Technology Mapping

- Three different approaches
 - Rule-based
 - Structural matching
 - Graph covering problem (subject DAG, pattern DAGs)
 - Binate covering formulation
 - » Too slow in practice
 - Tree covering
 - » Dynamic programming, very efficient and scalable
 - Boolean matching

General Principles

- Look for problems from a different domain that are equivalent to the problem you are trying to solve
 - Technology mapping in logic synthesis \Leftrightarrow code generation in compilers
- Combining exact solutions for sub-problems may give an exact (or a good approximate) solution for the complete problem




Suggested Reading

- Hachtel & Somenzi, Chapter 13
- De Micheli, Chapter 10.1,10.2,10.3.1-10.3.3
- Key Papers
 - K. Keutzer, "DAGON: Technology binding and local optimization by DAG matching," in Proc. 24th ACM/IEEE Conf. on Design Automation, pp. 341-347, 1987
 - "MIS: A Multiple-Level Logic Optimization System", R. K. Brayton, R. Rudell, A. Sangiovanni-Vincentelli, A. R. Wang, IEEE Transactions on Computer-Aided Design of Integrated Circuits and Systems, vol. 6, no. 6, Nov. 1987, pp. 1062 - 1081
 - "Logic synthesis for VLSI design", R. Rudell, Ph.D. thesis, U. C. Berkeley, 1989.
 - Performance-Oriented Technology Mapping, (H.J. Touati, Ch.W. Moon and R. K. Brayton), Proceedings of MIT VLSI Conference, 1990.
 - "Technology mapping for low power", V. Tiwari, P. Ashar, and S. Malik, Design Automation Conference, pp. 74-79, 1993.

Acknowledgments


- Prof. Sharad Malik, Princeton
- Prof. Rob Rutenbar, CMU

 

ECE 595Z

Digital VLSI Design Automation

 Module 6 (Lectures 21-24): Timing Analysis and Optimization
Lecture 21



Anand Raghunathan

MSEE 318


raghunathan@purdue.edu

Timing Optimization

- We have learnt thus far how to synthesize (small) circuits fast
- But, we also want to synthesize FAST circuits!
- Until recently, performance (clock frequency) was undisputed king for most ICs
 - Still is important, except power also matters in most applications and can be the primary metric in some

Timing Analysis

 - Given a (sequential) circuit, how fast can I clock it while maintaining correct operation?




Outline

- Timing Analysis
 - Clocking criteria for sequential circuits
 - Timing graph
 - Delay models for gates
 - Topological timing analysis
 - Functional timing analysis
- Timing Optimization
 - Collapsing and re-structuring
 - Generalized Bypass Transform
 - Generalized Select Transform
 - Eliminating false paths

Timing Analysis


Clocking Criteria for Sequential Circuits

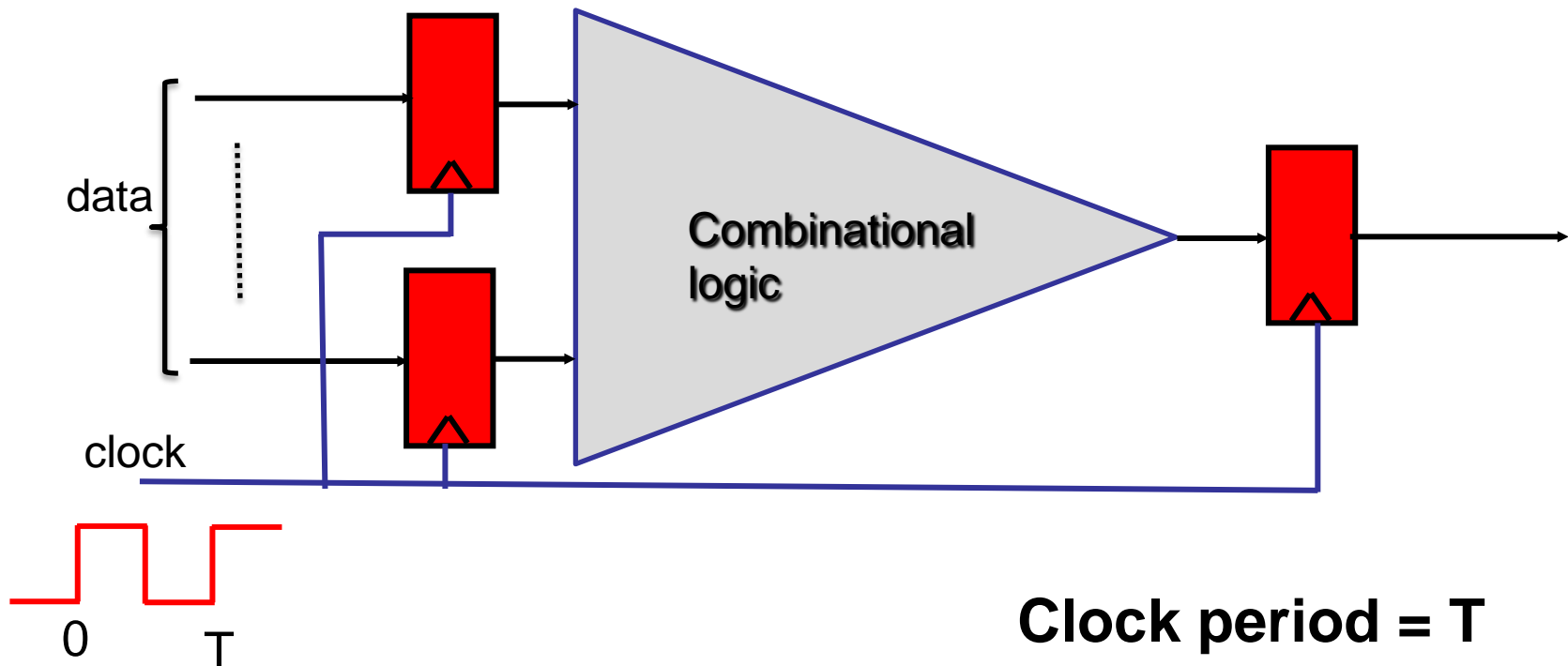- Consider circuits with edge-triggered storage elements (Flip-Flops)
- What timing properties should be satisfied for correct operation?




Setup Condition

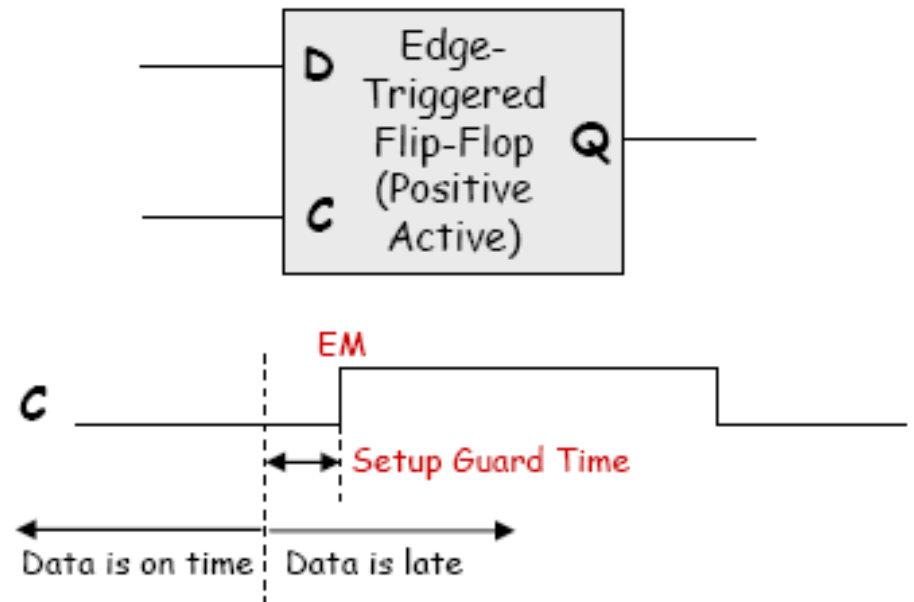- Data that we intend to capture at a Flip-Flop must arrive before the clock edge by at least the setup time




Setup Criterion for Sequential Circuits

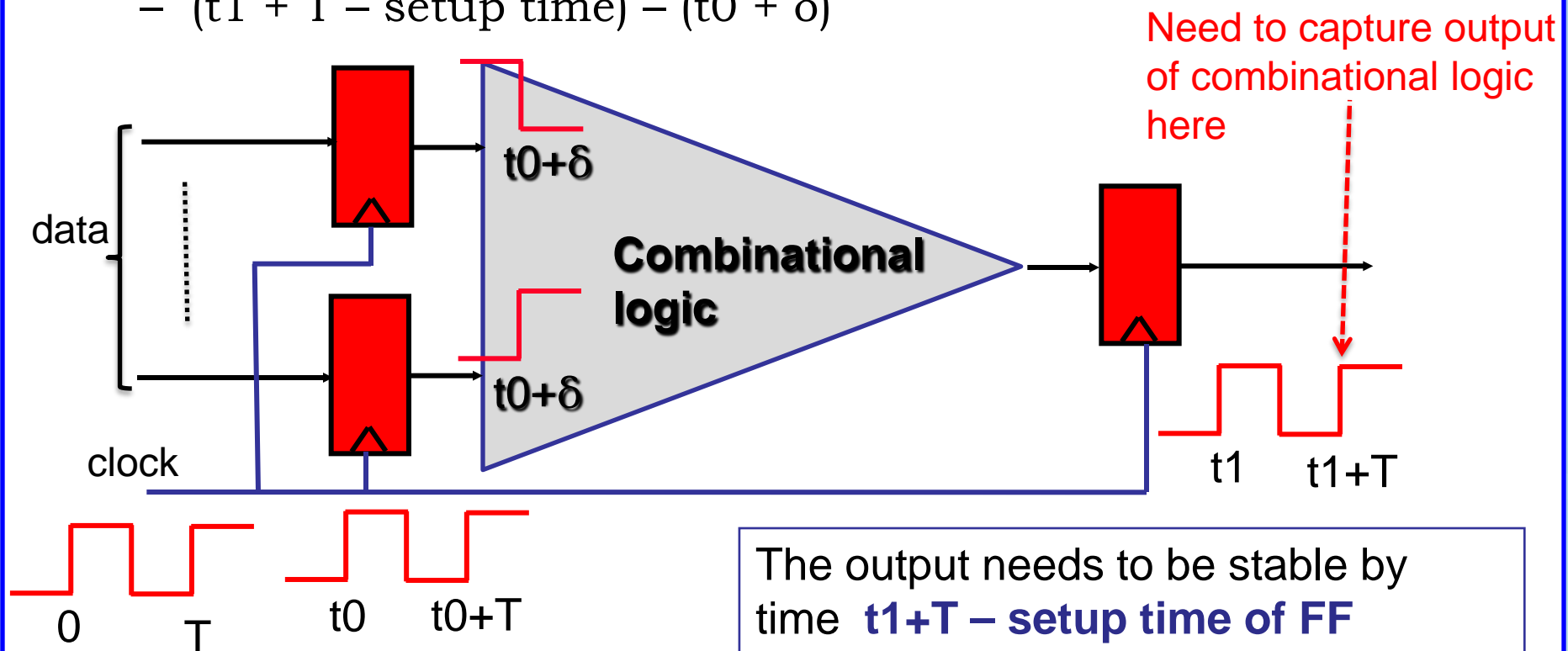- **Setup condition:** The outputs of the combinational logic should settle in time to be captured
- Translates to an upper bound on the longest delay through the combinational logic
 - $(t_1 + T - \text{setup time}) - (t_0 + \delta)$




Hold Condition

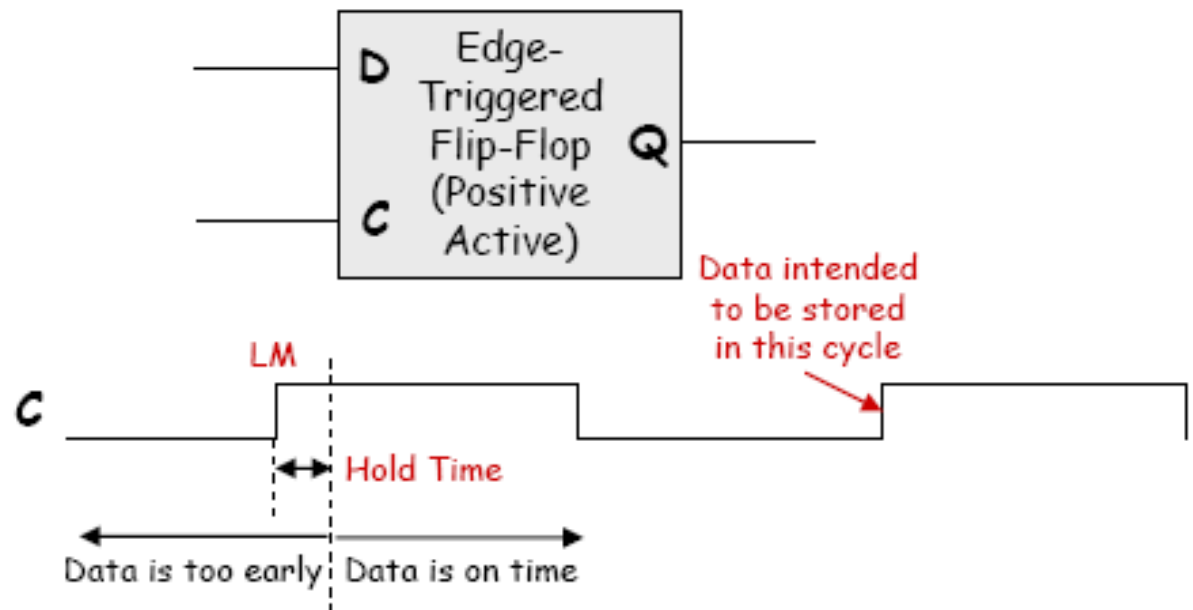- Data that we intend to capture at a Flip-Flop must not change after the clock edge until at least the hold time



Hold Criterion for Sequential Circuits

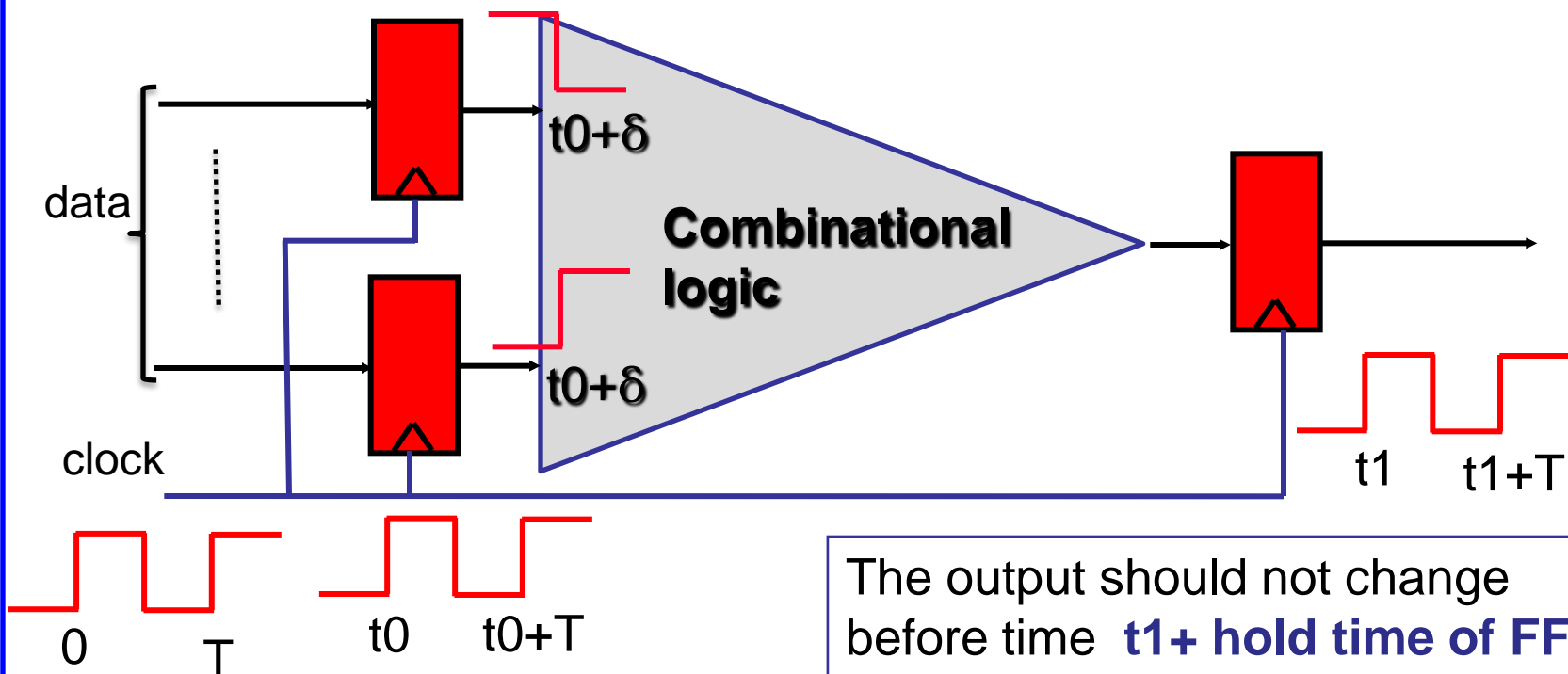- **Hold condition:** The outputs of the combinational logic should not change too early
- Translates to a lower bound on the shortest delay through the combinational logic
 - $(t_1 + \text{hold time}) - (t_0 + \delta)$





Delay Models for Gates

- Unit delay
- Constant delay
- Pin-to-pin delay
- State and Transition dependent delay
- Load and slew rate dependent delay
- PVT corners
- Statistical delay models

Accuracy vs. computation time tradeoff



Unit Delay Model

 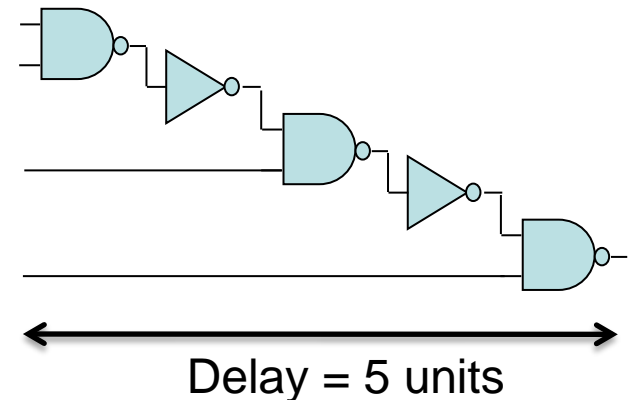- Simplest model: Assume each gate has a fixed delay of 1 unit
- Usually applied to a network of 2-input gates and inverters
- Typically used in technology-independent optimizations
- Still useful for coarse-grained comparisons between alternative circuit structures






Constant Delay Model

  - Different but fixed delay for each gate type
- Simplest technology-dependent delay model




Pin-to-Pin Delay Model

   - Not all pins are created equal!
- Accounts for the fact that different paths through a gate can have different delays
- Input to output delay depends on transistor-level implementation of gate/cell




State / Transition Dependent Delay Model

 - The values on inputs of the gate actually matter in determining its delay
 - Example: Not all transitions are equal! Rising and falling transition at output have different delays
- Note: Gate delay can be dependent on history



 
Delay(o/p rising) = 1.2
Delay(o/p falling) = 1



Delay(i/p falling, o/p falling) = 3.1
Delay(i/p falling, o/p rising) = 3.4
Delay(i/p rising, o/p falling) = 3.6
Delay(i/p rising, o/p rising) = 3.8

Load and Slew Rate Dependent Model

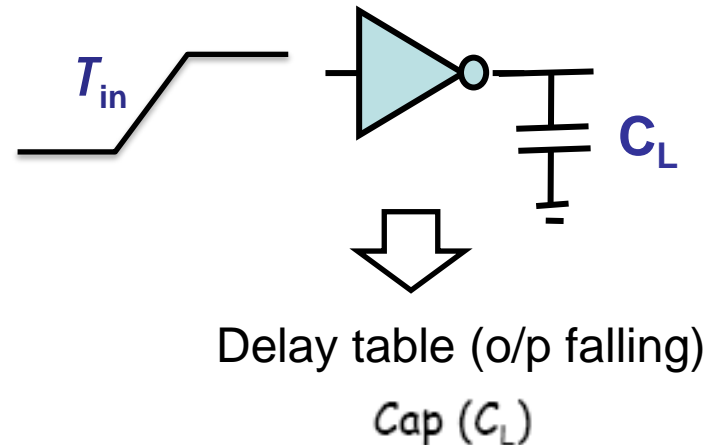- Considers dependency of delay on output load and input slew rate
 - Lookup table with interpolation
 - Discretize useful range of input slew rates and output loads
 - Equation
 - Fit simulated / measured data
- Need similar model for computing slew rate at output



Input Slew (τ_{in})		Delay		

Delay equation (o/p falling)

$$\text{Delay} = \alpha \cdot \tau_{in} + \beta \cdot C_L + \gamma \cdot \tau_{in} \cdot C_L + \delta$$

PVT Corners

- Delay is impacted by Process, Voltage, and Temperature variations
- Conventional approach: Consider “corners”
 - Slow, Typical (or Nominal), Fast
- Problem: Increasing spread leads to very conservative estimates

– Possible solution: Statistical models (active area of research)

Propagation Delays						
Path (I-O)	Perf. Level	Parameter	Delay			
			$V_{DD}=1.7V$ $T_j=125^\circ C$ Process=Slow	$V_{DD}=1.8V$ $T_j=25^\circ C$ Process=Nom.	$V_{DD}=1.9V$ $T_j=0^\circ C$ Process=Fast	
A-Z	A	t_{PLH}	0.10+0.20N	0.09+0.19N	0.08+0.18N	
		t_{PHL}	0.11+0.21N	0.10+0.18N	0.09+0.17N	
B-Z	A	t_{PLH}	0.09+0.19N	0.07+0.15N	0.06+0.14N	
		t_{PHL}	0.08+0.17N	0.05+0.15N	0.04+0.12N	
A-Z	B	t_{PLH}			

Summary

- Basic questions in timing analysis
 - Do the outputs of the combinational logic always reach the (final) stable value in time to be correctly captured?
 - Setup condition
 - Do the outputs of the combinational logic stay stable long enough to be correctly captured?
 - Hold condition
- Various delay models possible for gates
- Need delay models for wires too, but we will not talk about them in this class