

Spring 2019 Purdue University

ECE 255: L12

BJT Bias Circuits

(Sedra and Smith, 7th Ed., Sec. 6.3)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA

Lundstrom: 2019

PURDUE
UNIVERSITY

Announcements

Exam 1: Thursday, Feb. 7, 6:30 PM, LILY 1105.

(Weeks -1- 4 topics, semiconductors, diodes, BJTs. i.e. HW1-HW4)

Two practice exams are posted on BlackBoard

Graded HW can be picked up in EE 326B (Mary Ann Satterfield)


Professor Janes will conduct a help session for Exam 1 on Thursday, 2/7 at 1:30 PM in ME 1061.


Spice 1 project postponed until Monday, Feb. 11


There will be class on Friday, Feb. 8.

DC bias circuits

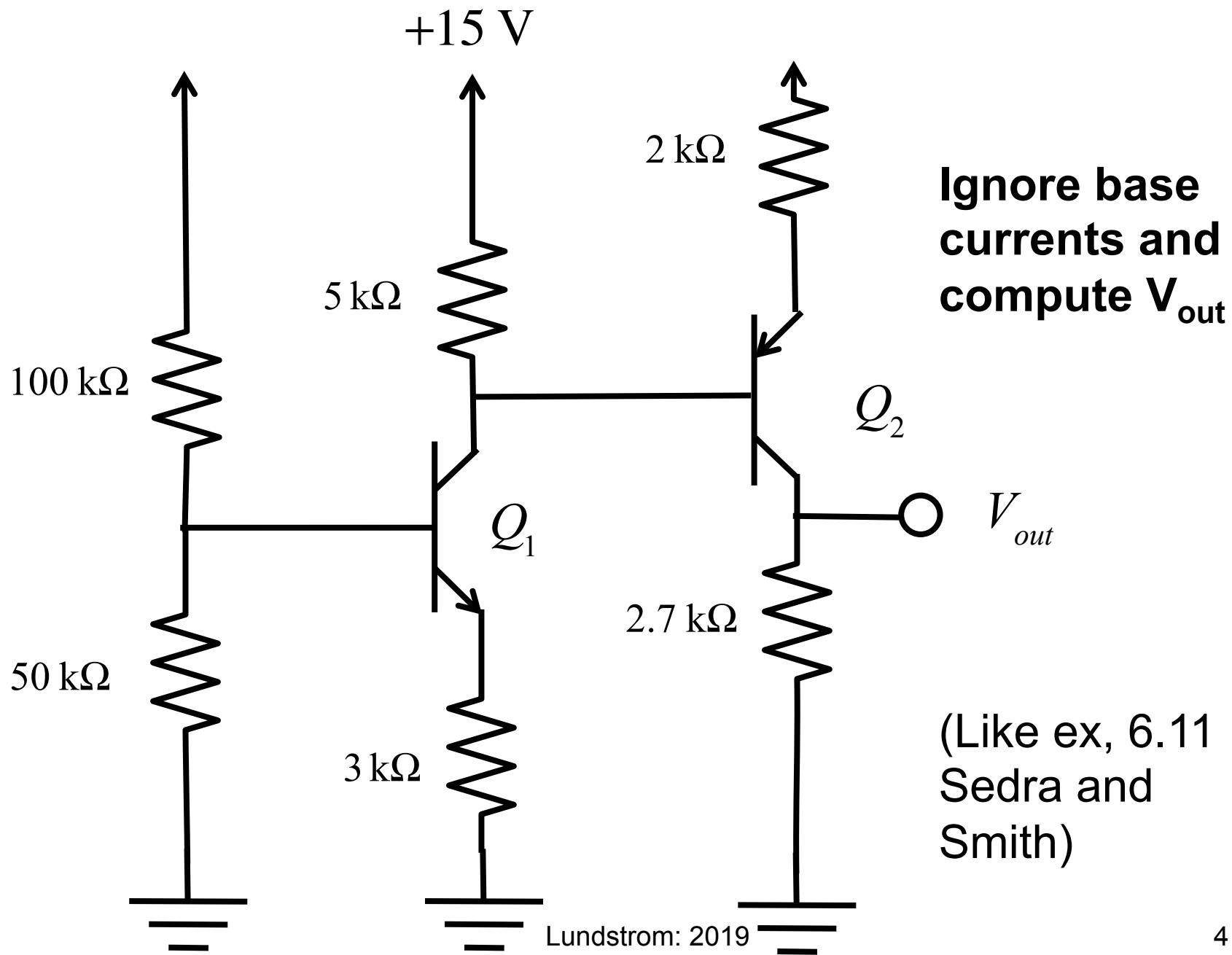- 1) NPN and PNP circuits
- 2) Bias circuits (discrete)



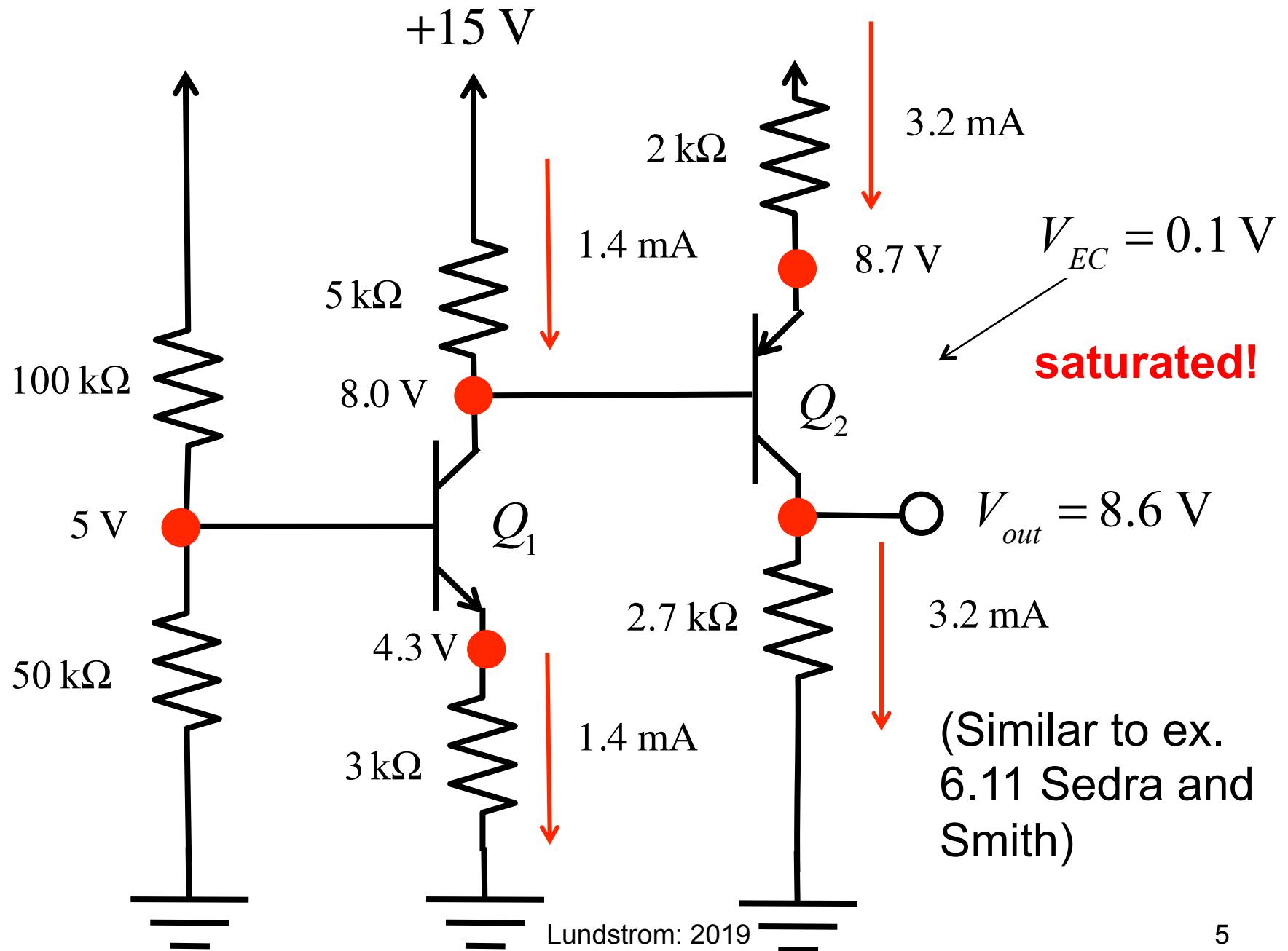

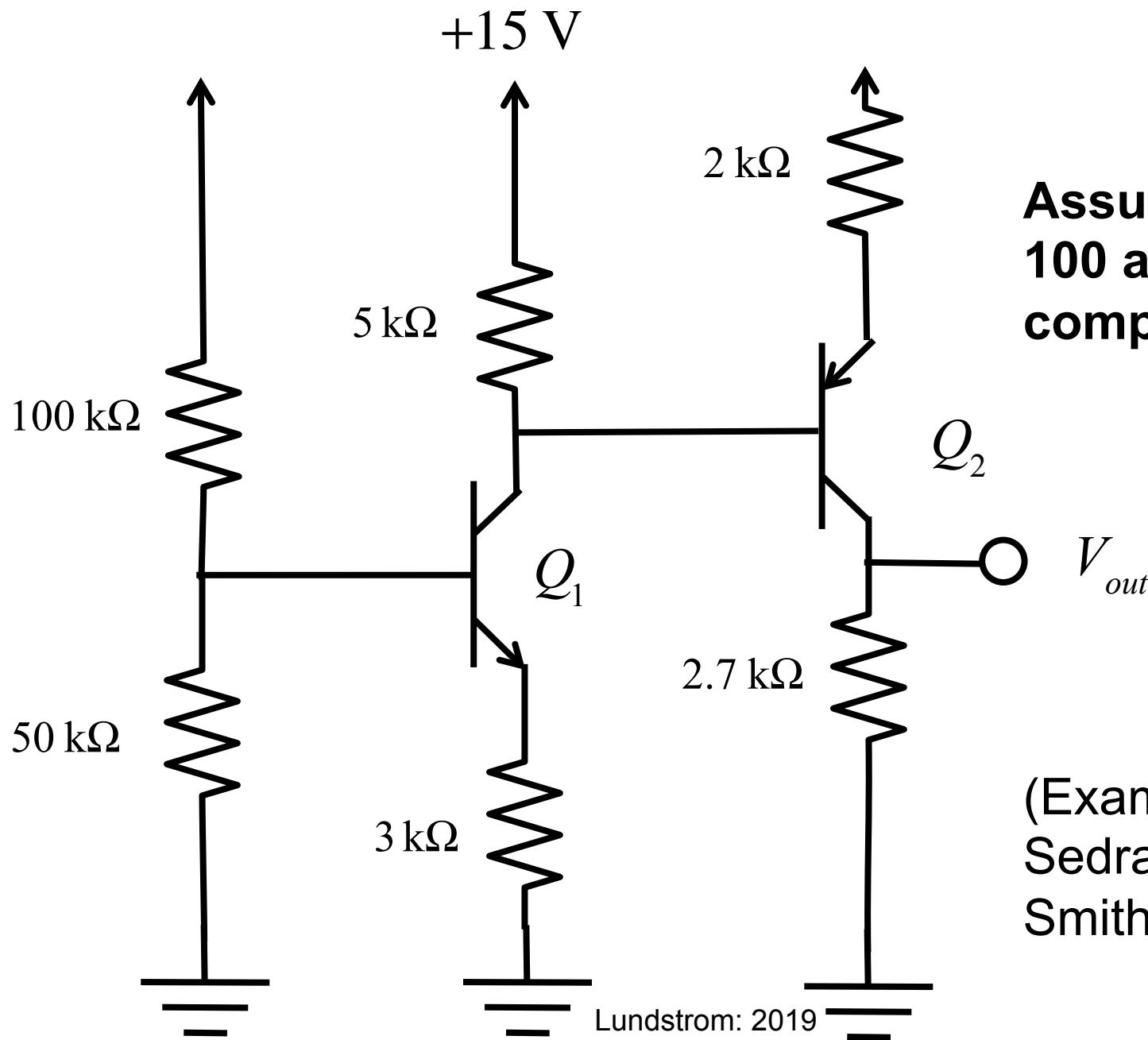

**Assume beta =
100 and
compute V_{out}**


V_{out}

(Example 6.11
Sedra and
Smith)

BJT bias circuits


- 1) NPN and PNP circuits
- 2) **Bias circuits (discrete)**

Diode bias circuits

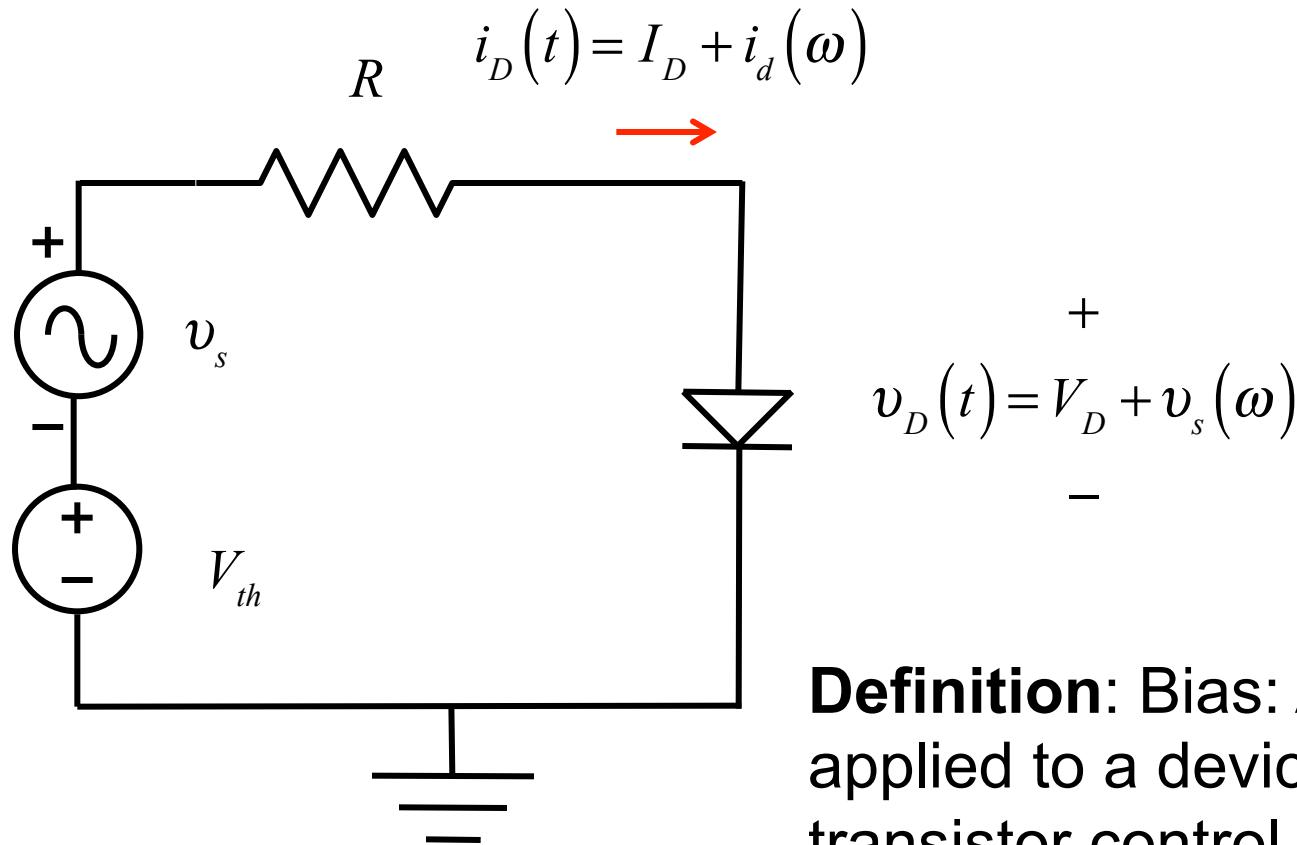


Definition: Bias: A voltage applied to a device (such as a transistor control electrode) to establish a reference level for operation.

Diode bias circuits

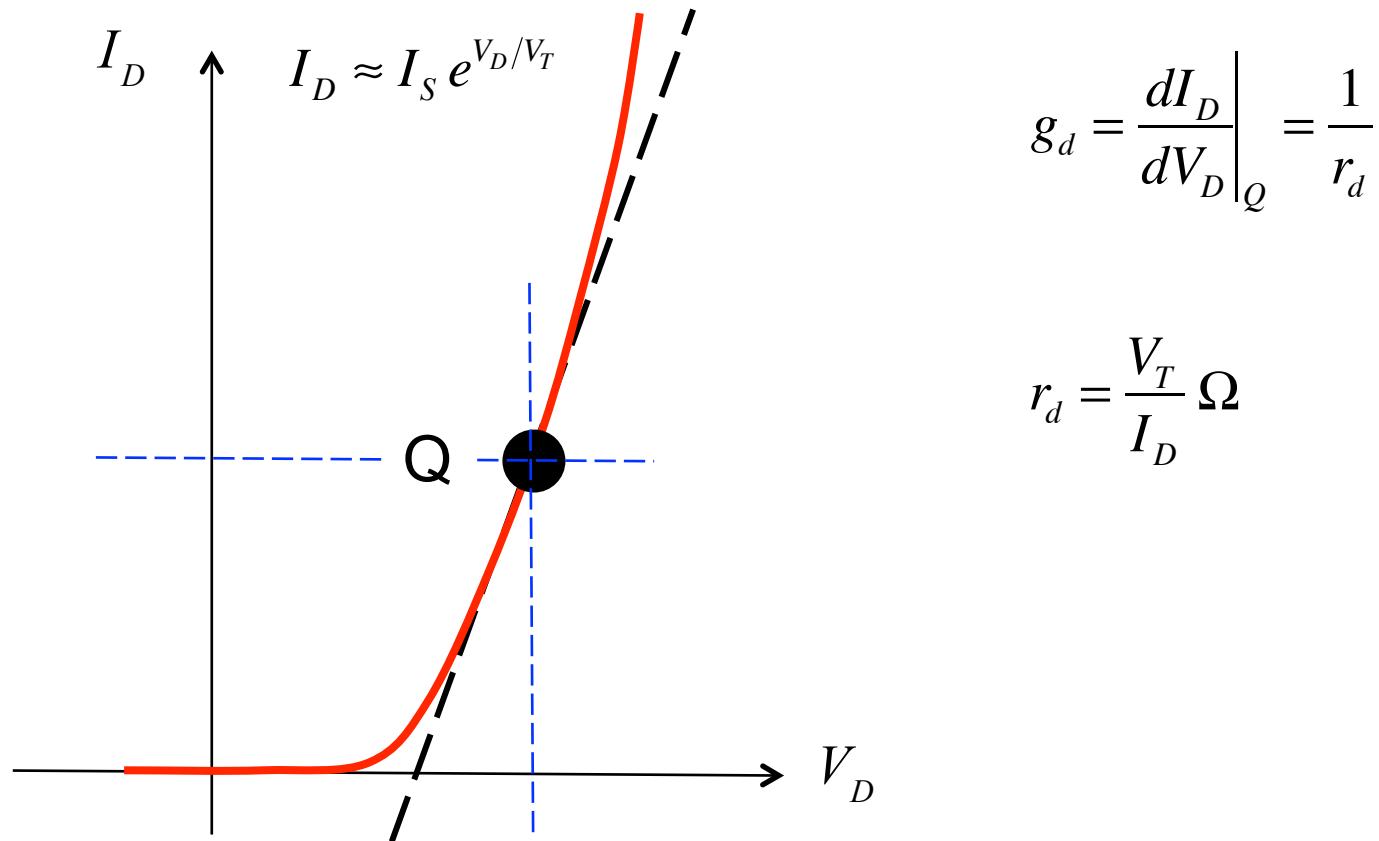


Transistor bias circuit **design**

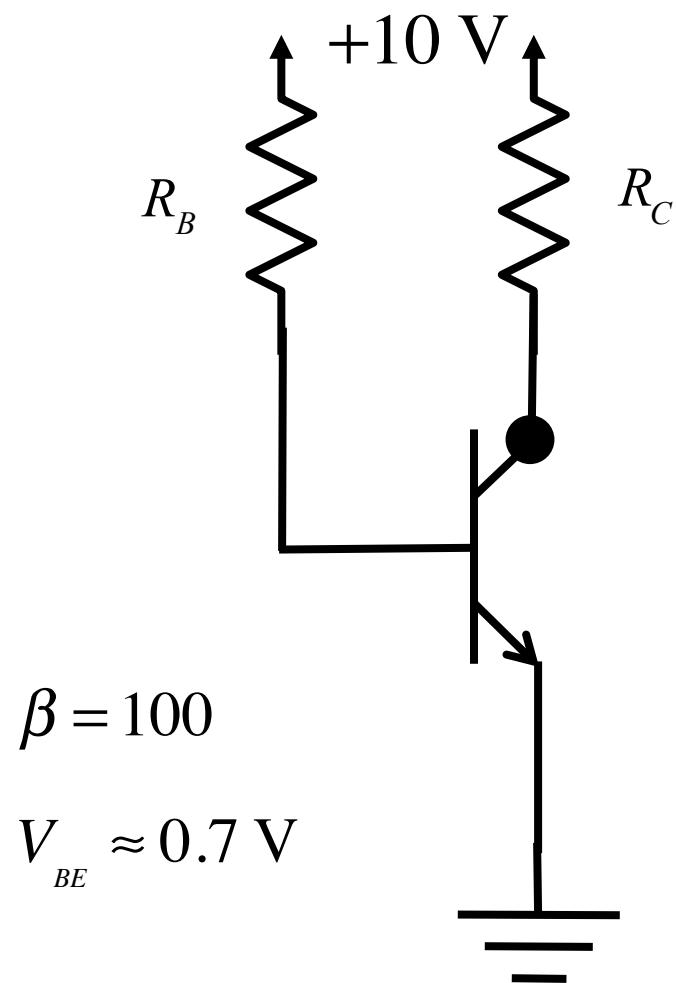

Design for


$$V_{CE} = 3.0 \text{ V}$$
$$I_C = 1.0 \text{ mA}$$

Bias circuit design

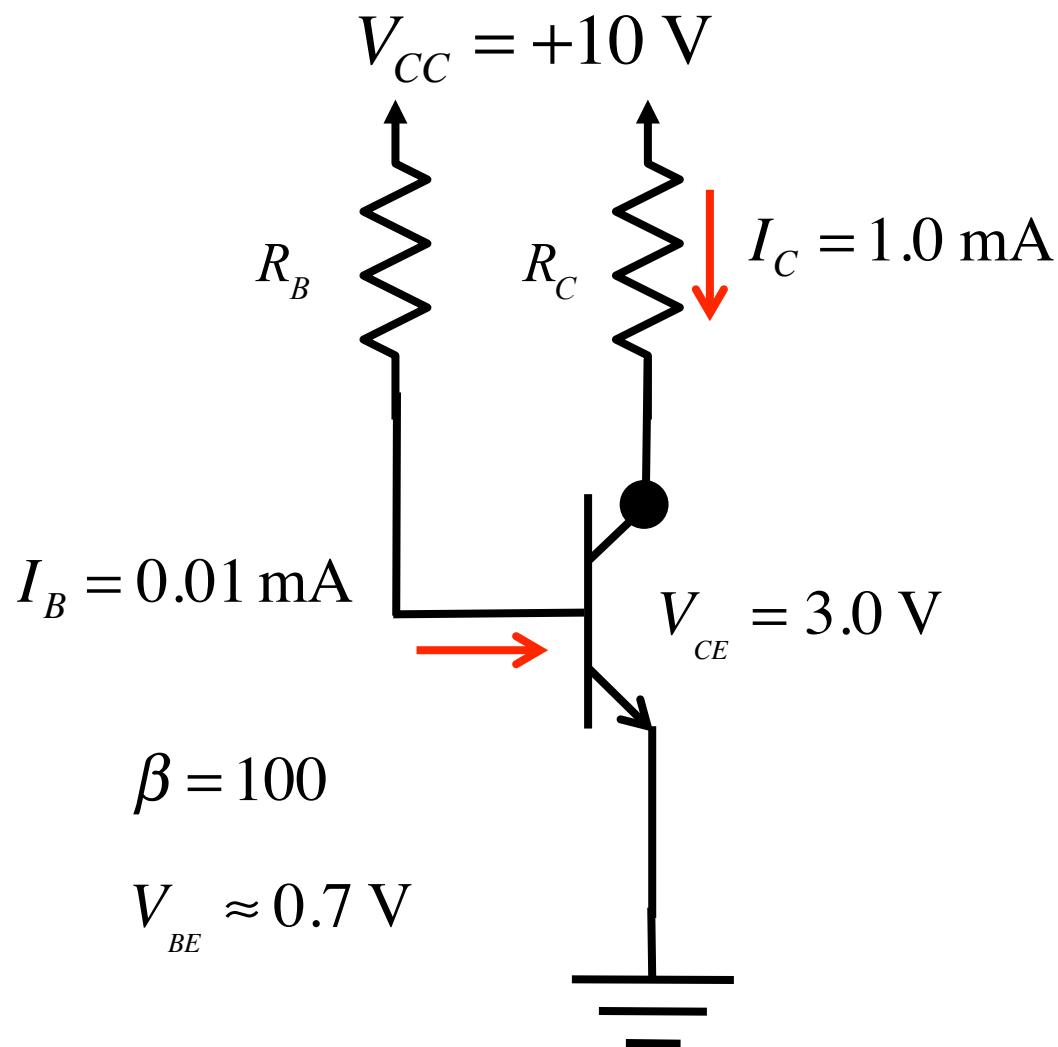


Lundstrom: 2019

Bias circuit design

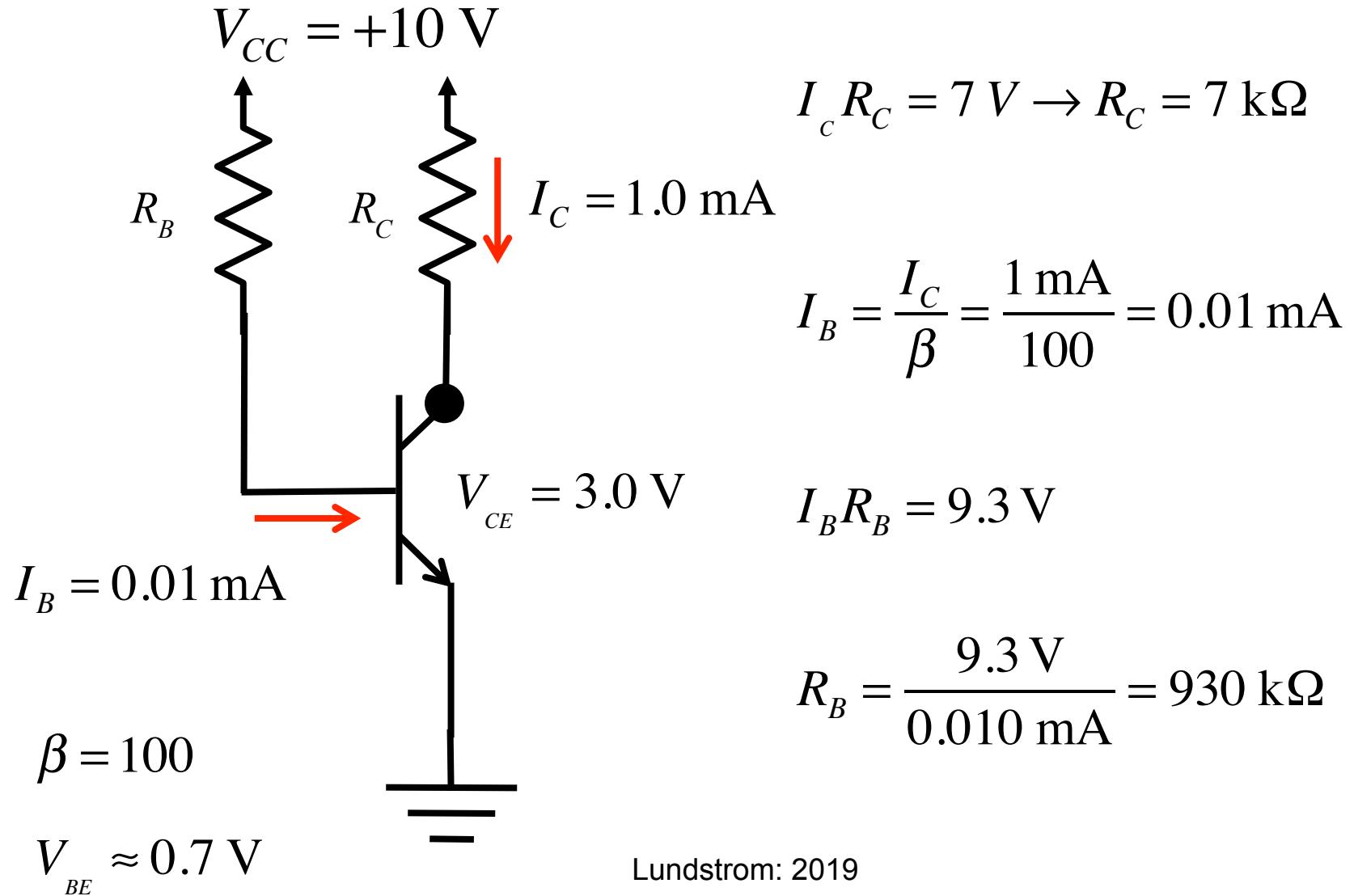


741 Op amp

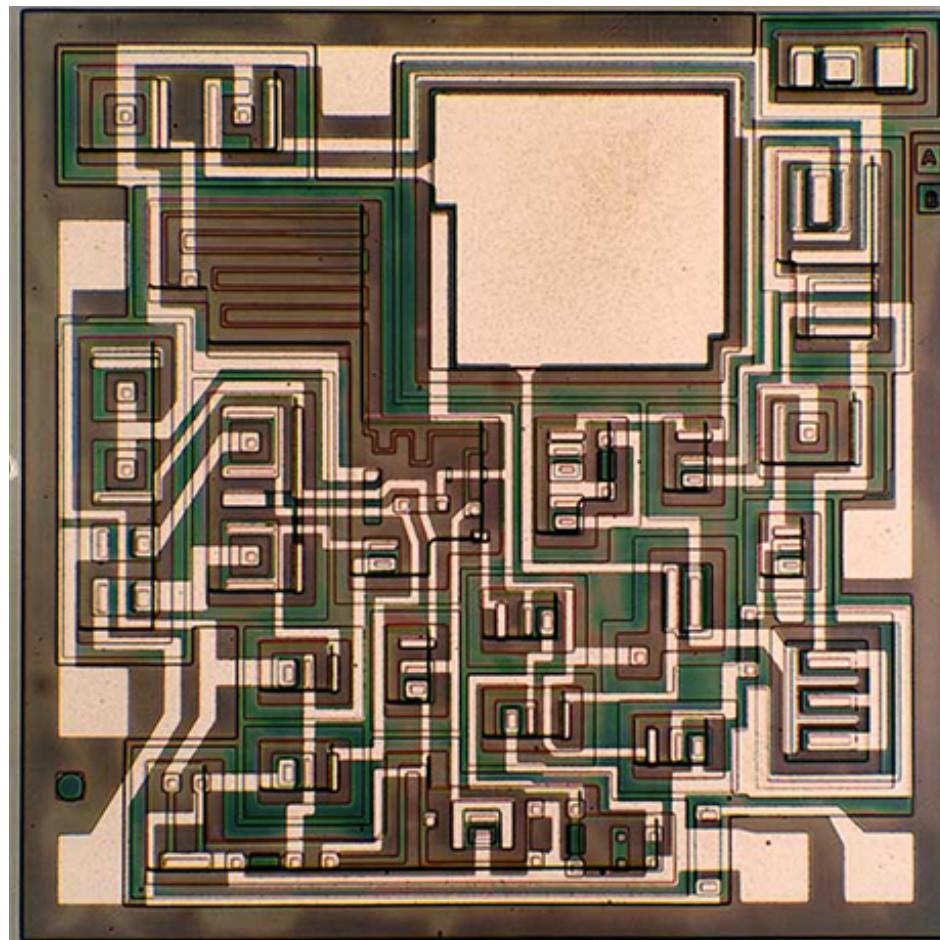

David Fullagar

IEEE Spectrum, “Chip Hall of Fame: Fairchild Semiconductor μA741 Op-Amp,” June 30, 2017

Bad Bias circuit design

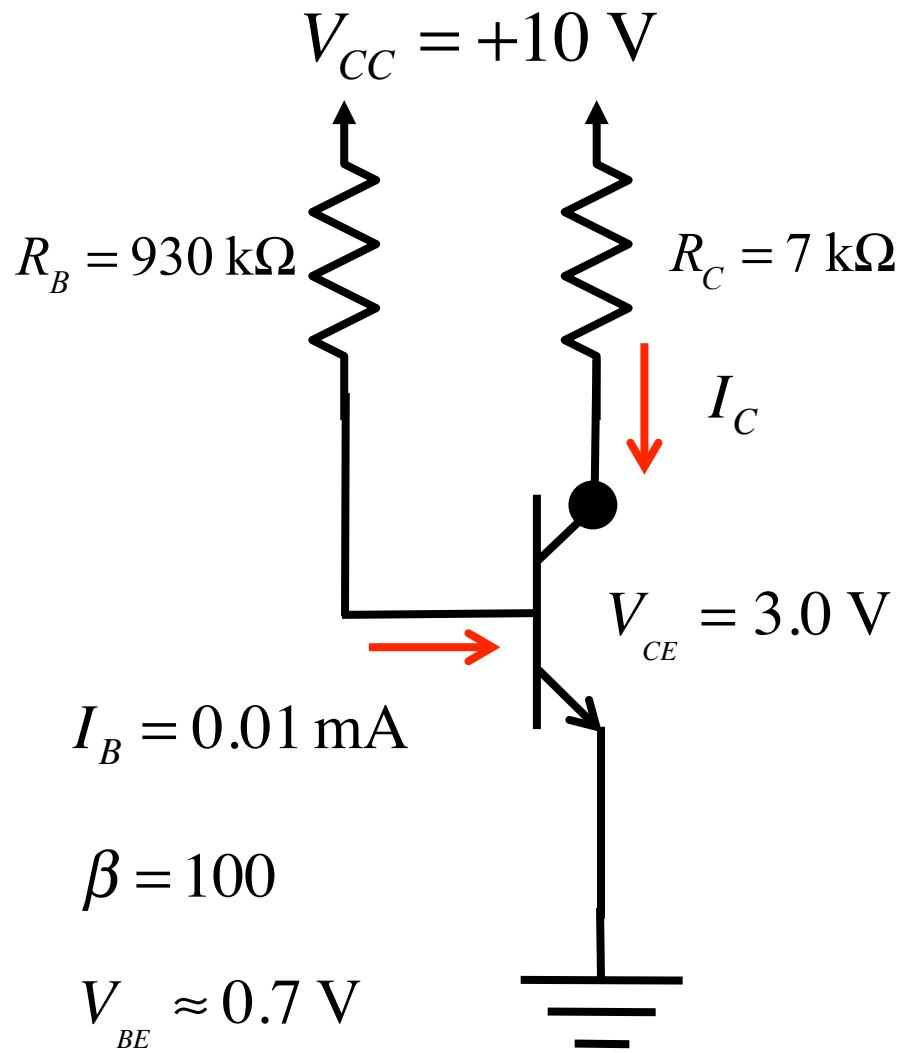

$$I_C = \beta I_B = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$


What if beta doubles?

$$I_C \rightarrow 2.0 \text{ mA}$$

$$V_C = 10 \text{ V} - I_C R_C = -4 \text{ V}!$$

Saturation!

A better bias circuit

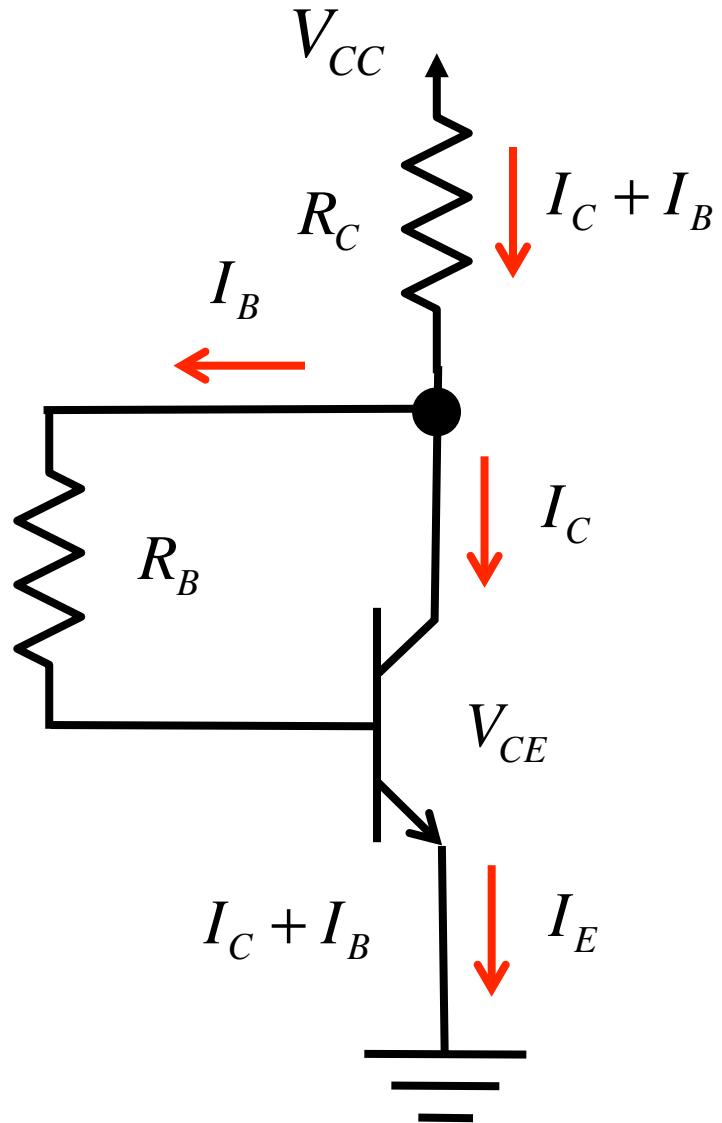


$$V_{CC} = R_C (I_C + I_C/\beta) I_C + R_B I_C / \beta + V_{BE}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C \left(1 + \frac{1}{\beta} \right) + R_B \frac{1}{\beta}}$$

$$\beta \rightarrow \infty$$


$$I_C \rightarrow \frac{V_{CC} - V_{BE}}{R_C}$$

Design

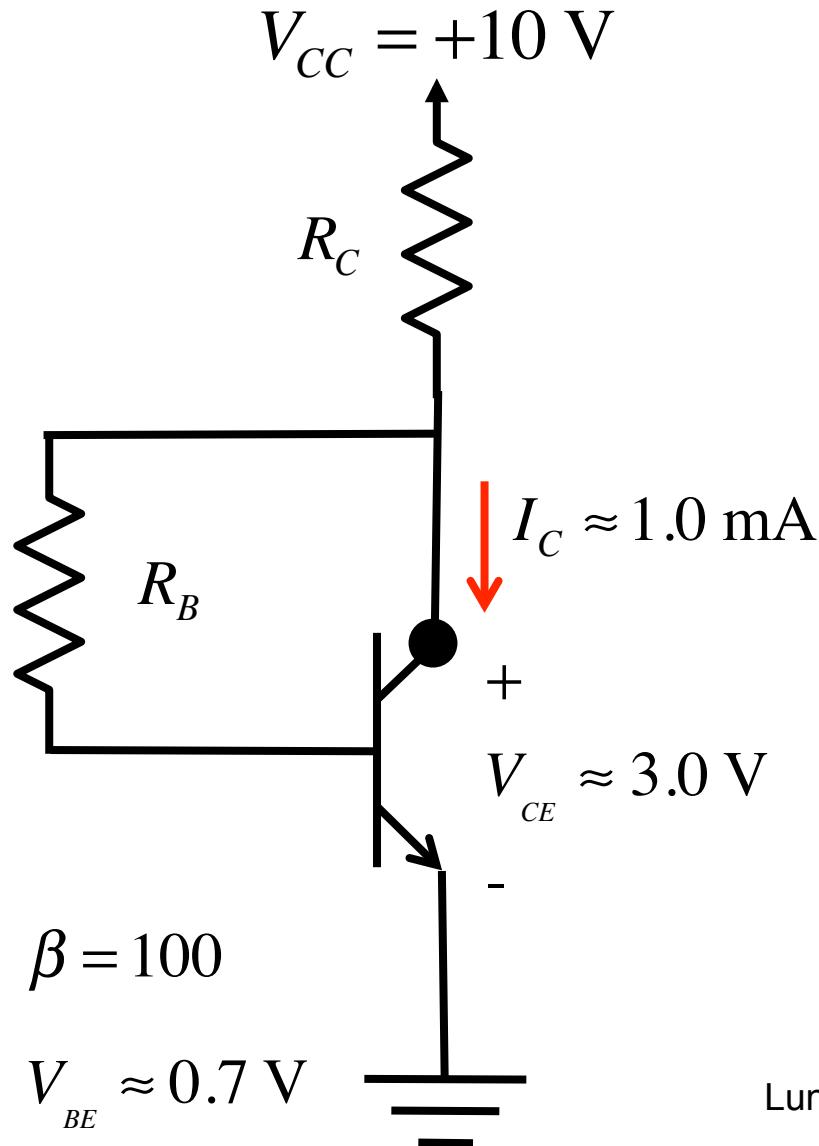

Lundstrom: 2019

Design (Results)

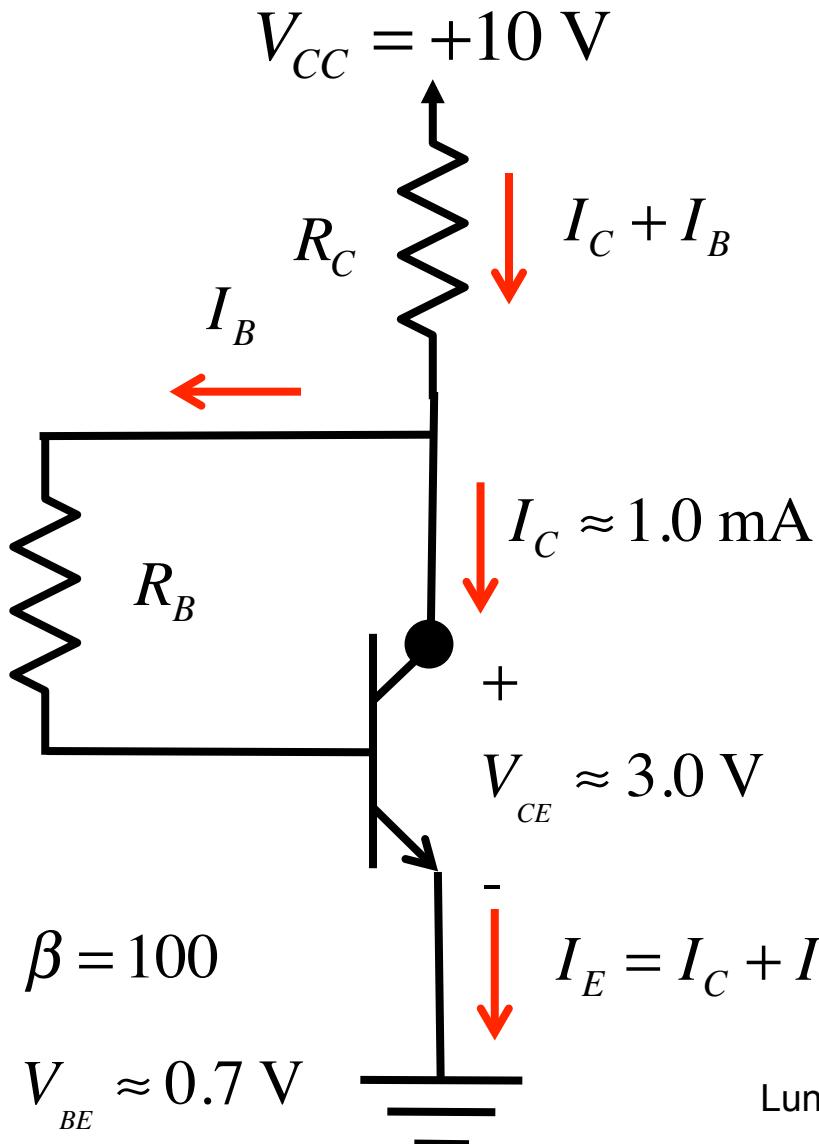


$$I_C R_C \approx 7 \text{ V} \quad R_C = 7 \text{ k}\Omega$$

$$I_B = 0.01 \text{ mA}$$

$$R_B = \frac{V_{CE} - V_{BE}}{I_B} = \frac{2.3}{0.01} = 230 \text{ k}\Omega$$

Analysis

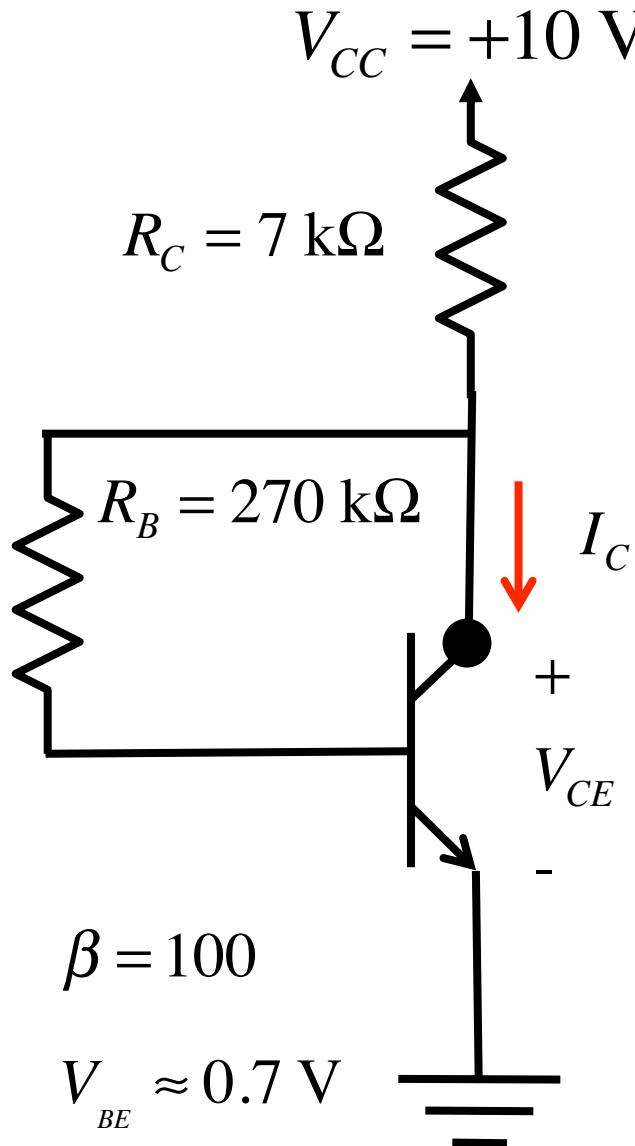

$$I_C = \frac{V_{CC} - V_{BE}}{R_C \left(1 + \frac{1}{\beta} \right) + R_B \frac{1}{\beta}}$$


$$I_C = \frac{10 - 0.7}{7 \left(1 + \frac{1}{100} \right) + \frac{230}{100}}$$

$$I_C = 1.0 \text{ mA}$$

$$V_{CE} = V_{CC} - \left(\frac{\beta + 1}{\beta} \right) I_C R_C$$

$$V_{CE} = 2.9 \text{ V} \quad (\text{close})$$

Analysis for beta = 200

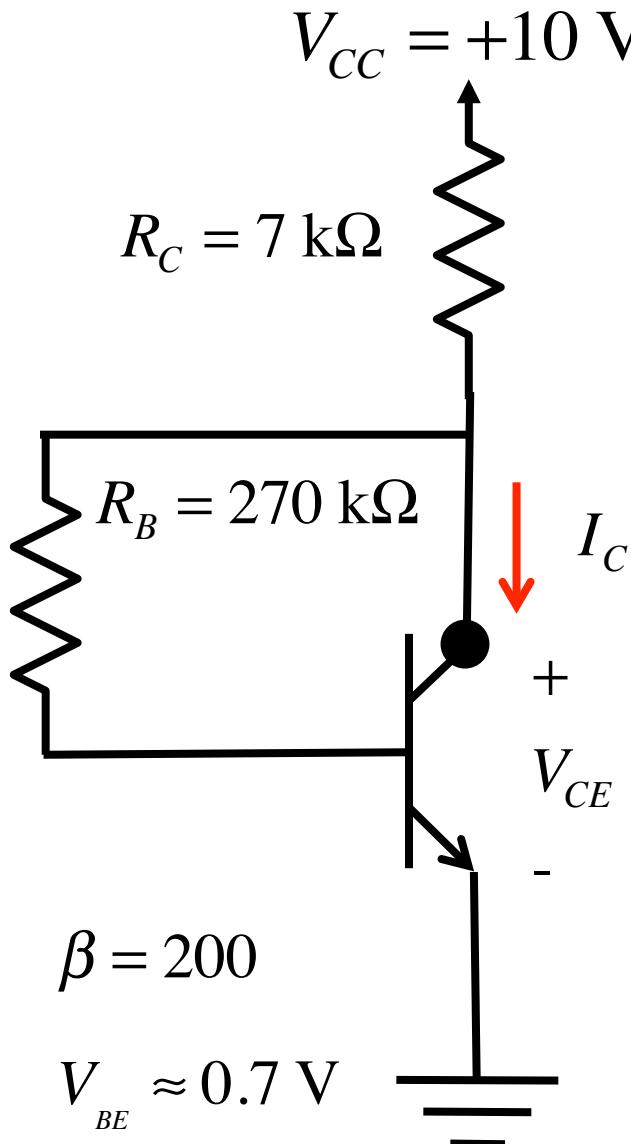

$$I_C = \frac{V_{CC} - V_{BE}}{R_C \left(1 + \frac{1}{\beta} \right) + R_B \frac{1}{\beta}}$$


$$I_C = 1.1 \text{ mA}$$

$$(I_C = 1.0 \text{ mA})$$

$$V_{CE} = 2.3 \text{ V}$$

$$(V_{CE} = 2.9 \text{ V})$$


Why does it work?

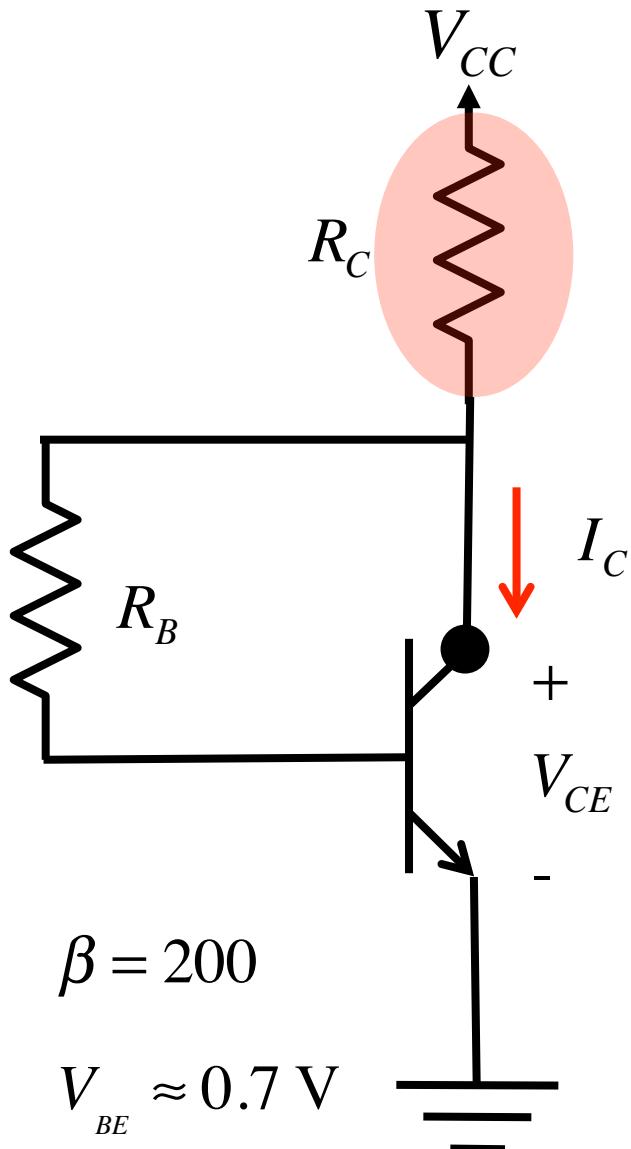

Negative feedback

$I_C \uparrow$	$V_{R_C} \uparrow$	$V_C \downarrow$	$I_B \downarrow$	$I_C \downarrow$
$I_C \downarrow$	$V_{R_C} \downarrow$	$V_C \uparrow$	$I_B \uparrow$	$I_C \uparrow$

Classic 4-resistor Bias circuit design

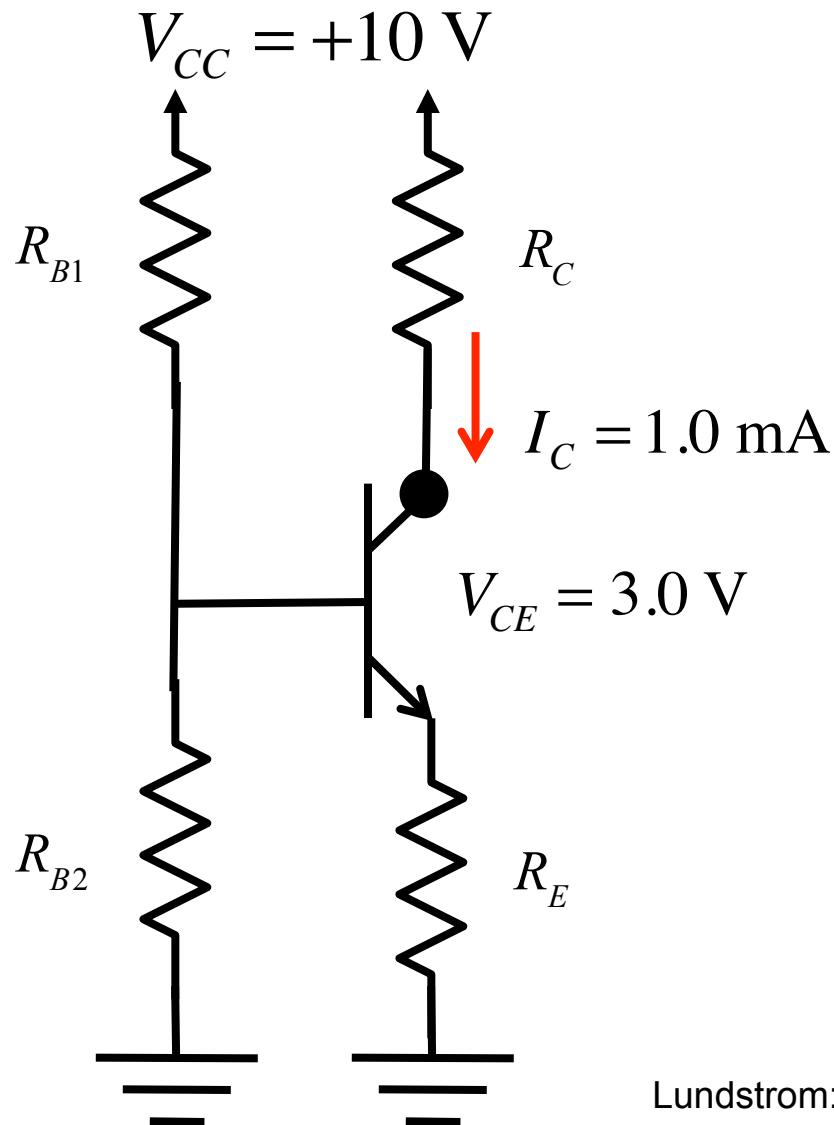

Design for


$$V_{CE} = 3.0 \text{ V}$$

$$I_c = 1.0 \text{ mA}$$

$$\beta = 100$$

$$V_{BE} \approx 0.7 \text{ V}$$

Classic Bias circuit design

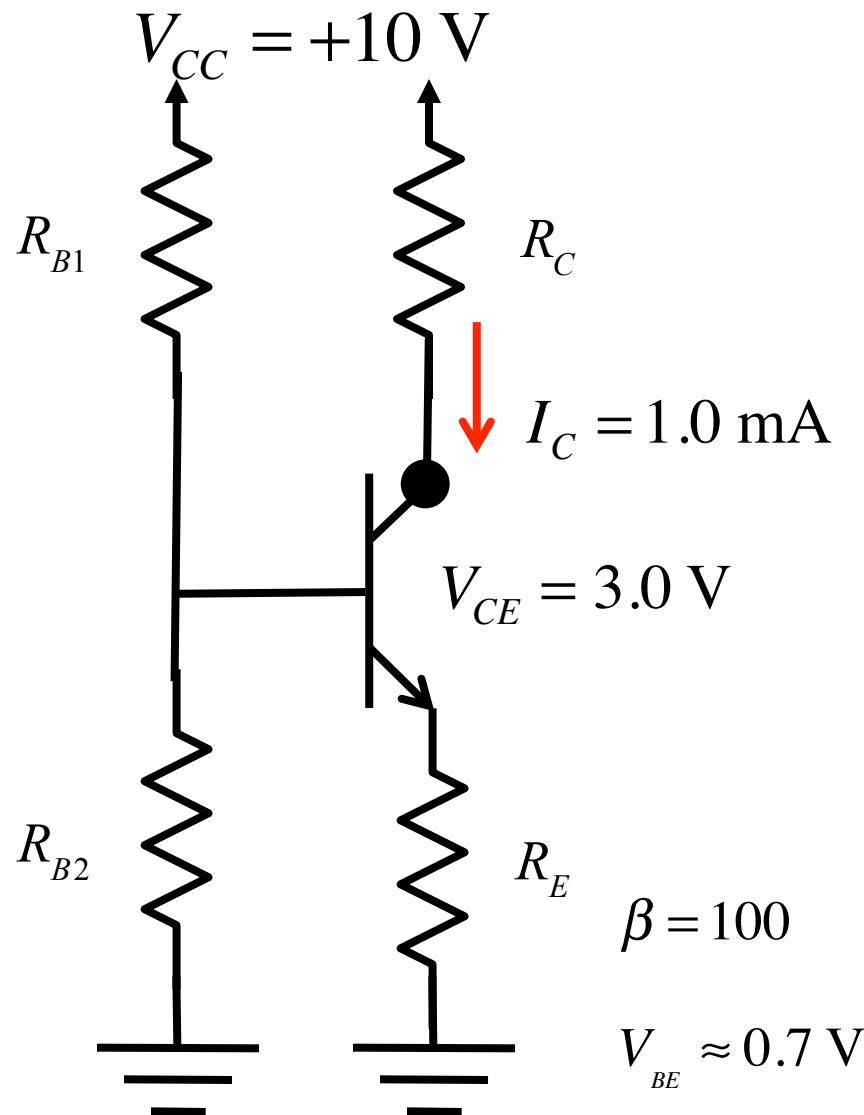

Start at the output:


Have 7 V to split between 2 resistors.

Let: $V_{R_C} = V_{R_E} = 3.5\text{ V}$

$$R_C = \frac{3.5\text{ V}}{1.0\text{ mA}} = 3.5\text{ k}\Omega$$

$$R_E = \frac{3.5\text{ V}}{1.01\text{ mA}} \approx 3.5\text{ k}\Omega$$

Classic Bias circuit design

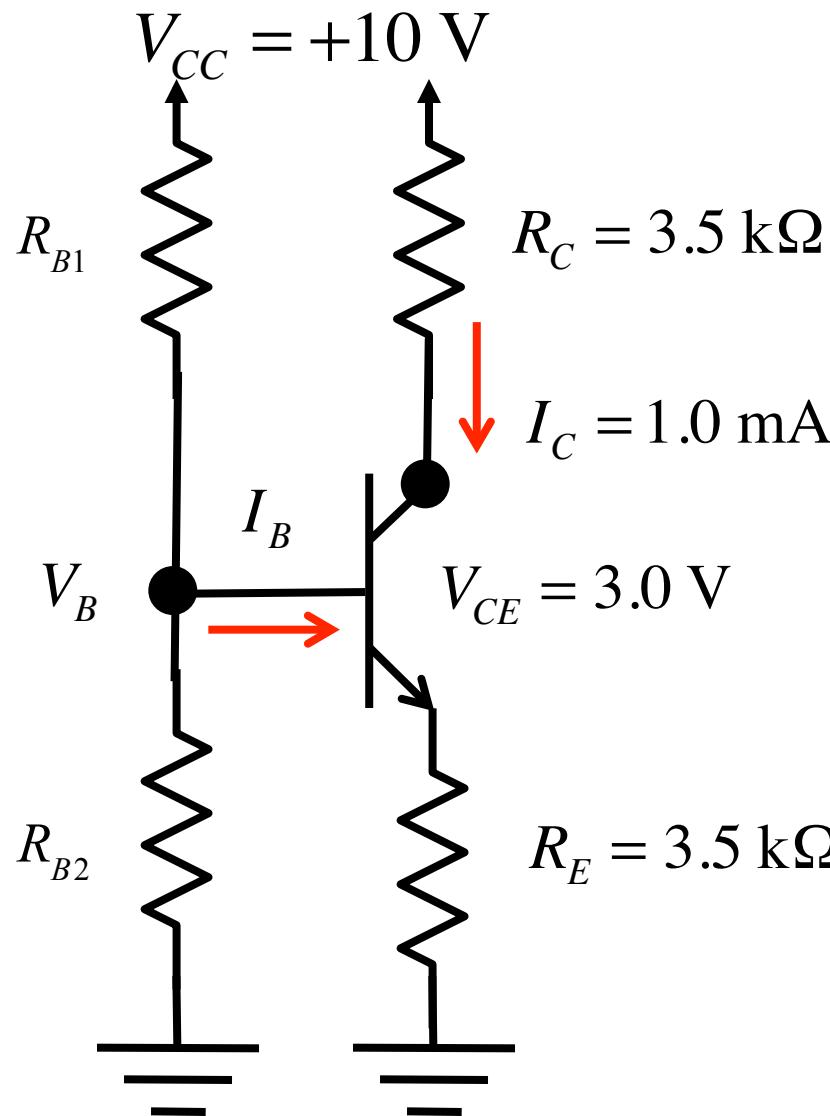

Now move to the input:


$$\begin{aligned}V_B &= V_{R_E} + 0.7 \\&= 3.5 + 0.7 = 4.2\text{ V}\end{aligned}$$

$$I_B = \frac{I_C}{100} = \frac{0.01\text{ mA}}{100}$$

$$\beta = 100$$

$$V_{BE} \approx 0.7\text{ V}$$

Classic Bias circuit design

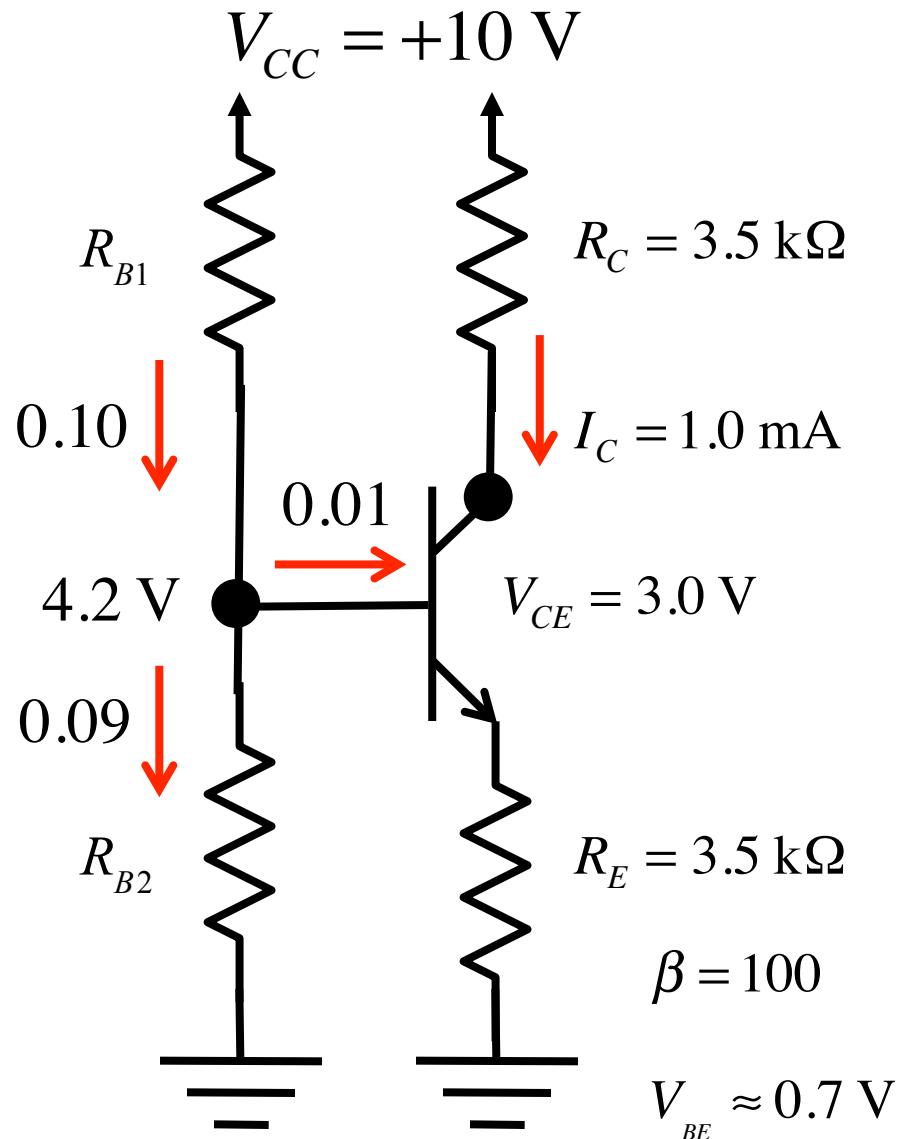

Choose:


$$I_{R_{B1}} = 10I_B = 0.1 \text{ mA}$$

$$I_{R_{B1}} = 0.1 \text{ mA} = \frac{(10 - 4.2)\text{V}}{R_{B1}} \rightarrow 58 \text{ k}\Omega$$

$$\begin{aligned} I_{R_{B2}} &= I_{R_{B1}} - I_B \\ &= 10I_B - I_B = 0.09 \text{ mA} \end{aligned}$$


$$I_{R_{B2}} = 0.09 \text{ mA} = \frac{4.2\text{V}}{R_{B2}} \rightarrow 46.7 \text{ k}\Omega$$

Classic bias circuit analysis

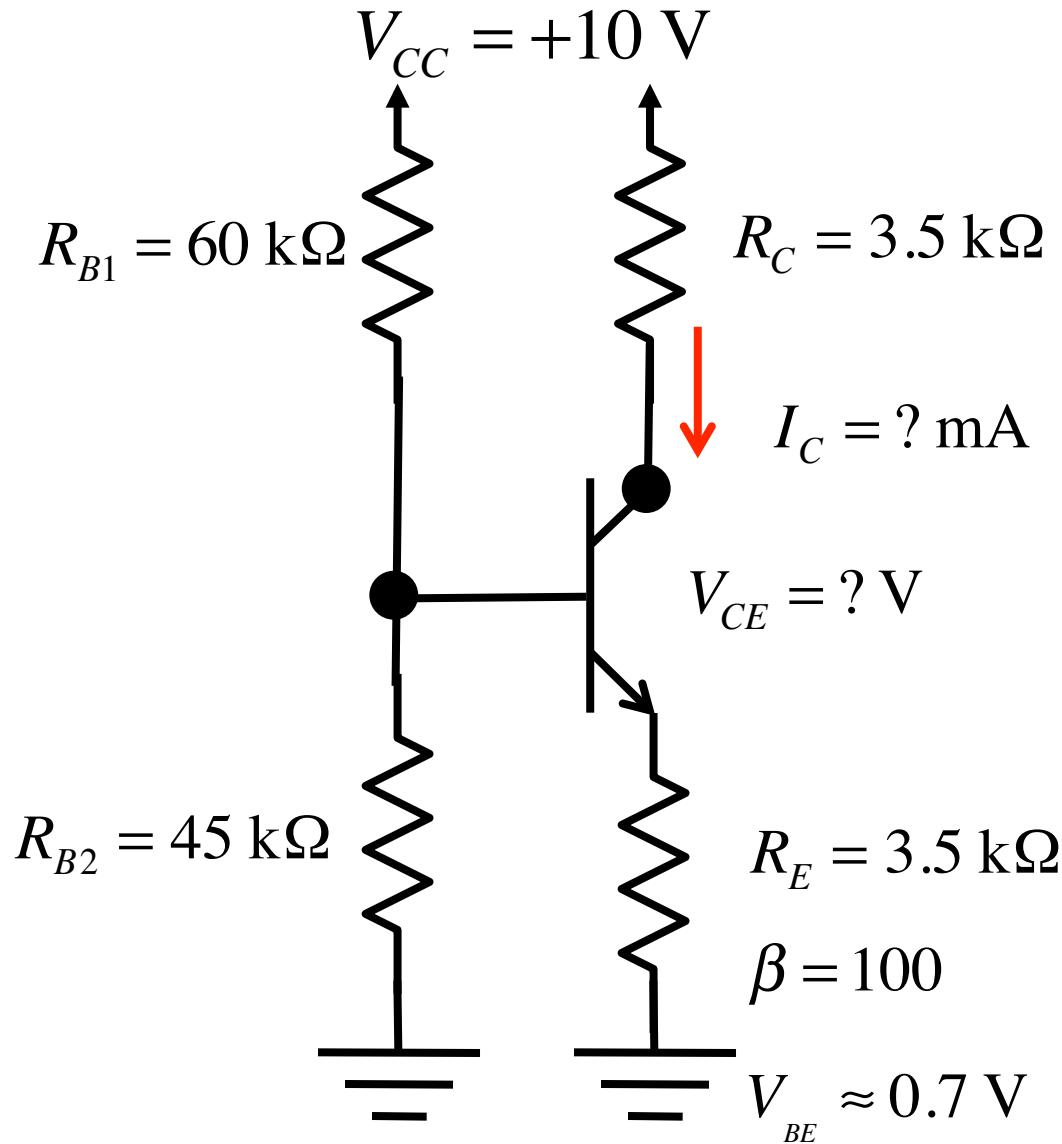


Now that everything is specified, we can **analyze** the circuit.


Classic Bias circuit analysis

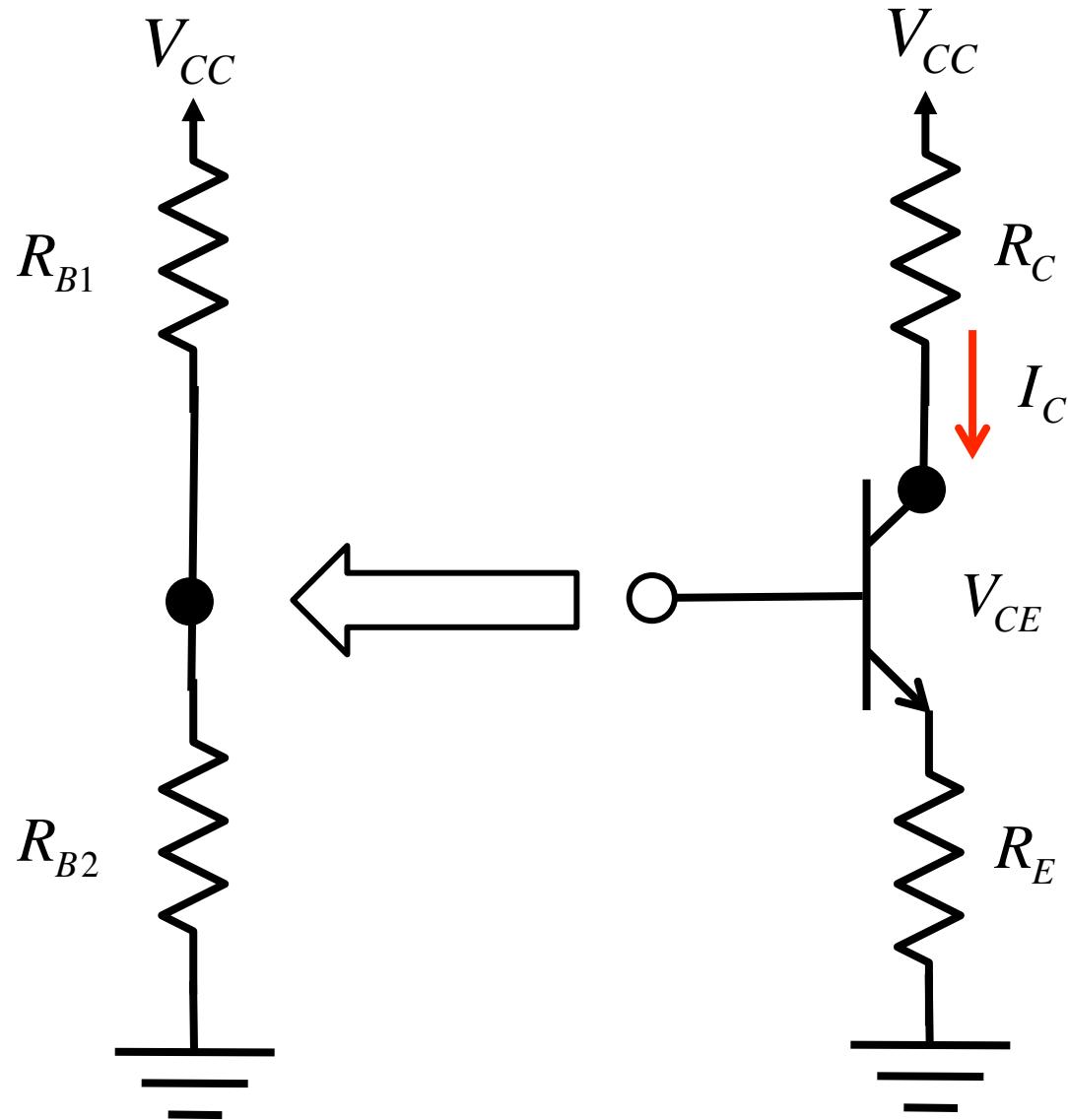

Classic Bias circuit analysis

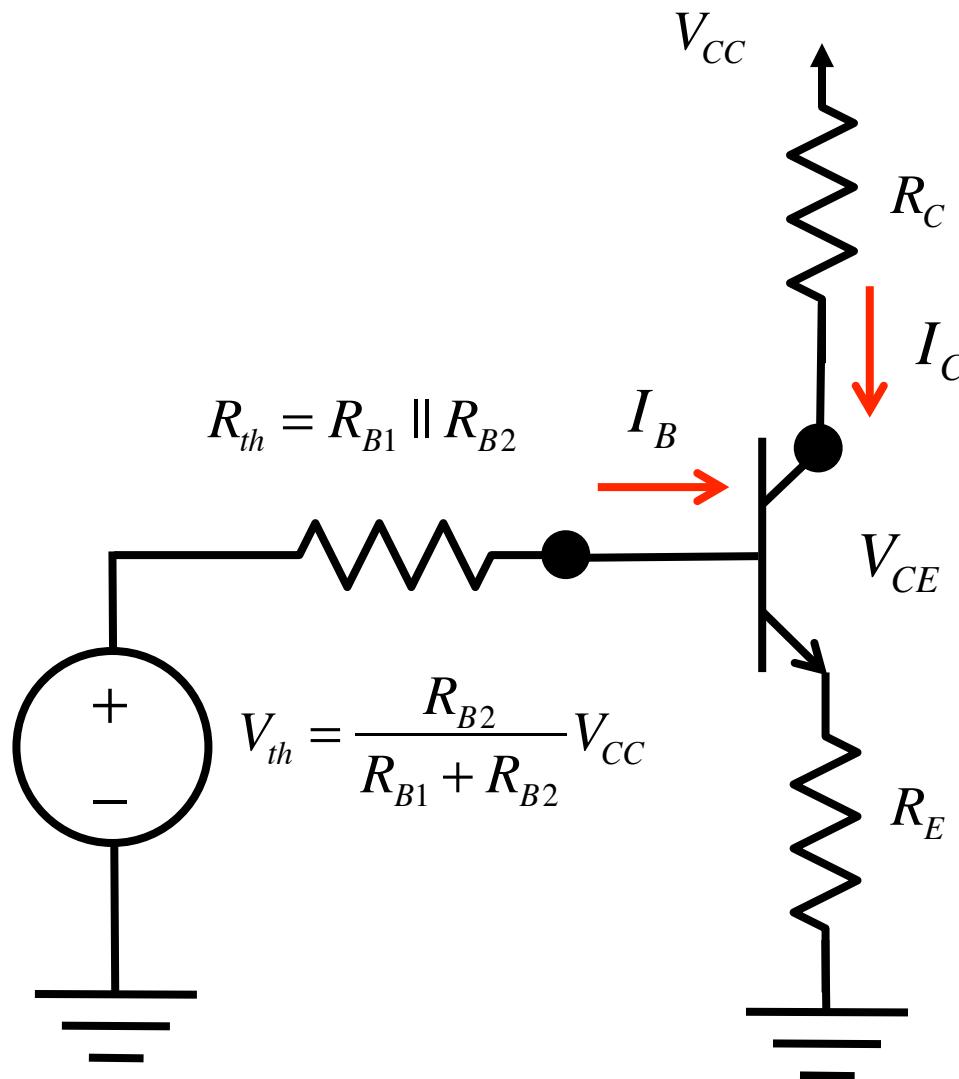

Classic bias circuit design

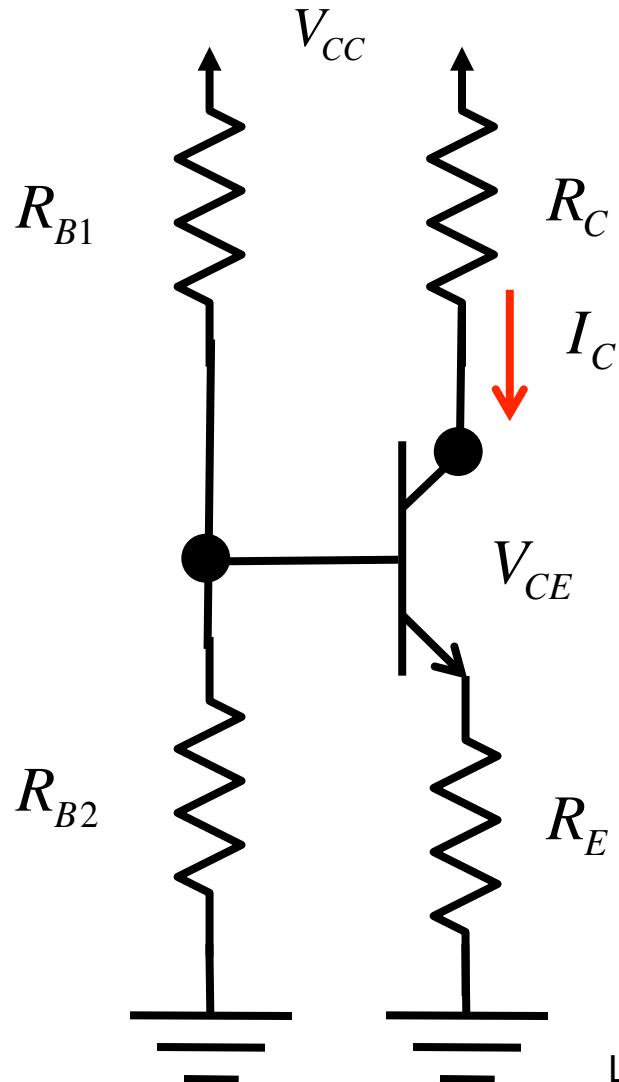


$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$R_{th} = R_{B1} \parallel R_{B2}$$

$$V_{th} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

Classic bias circuit analysis

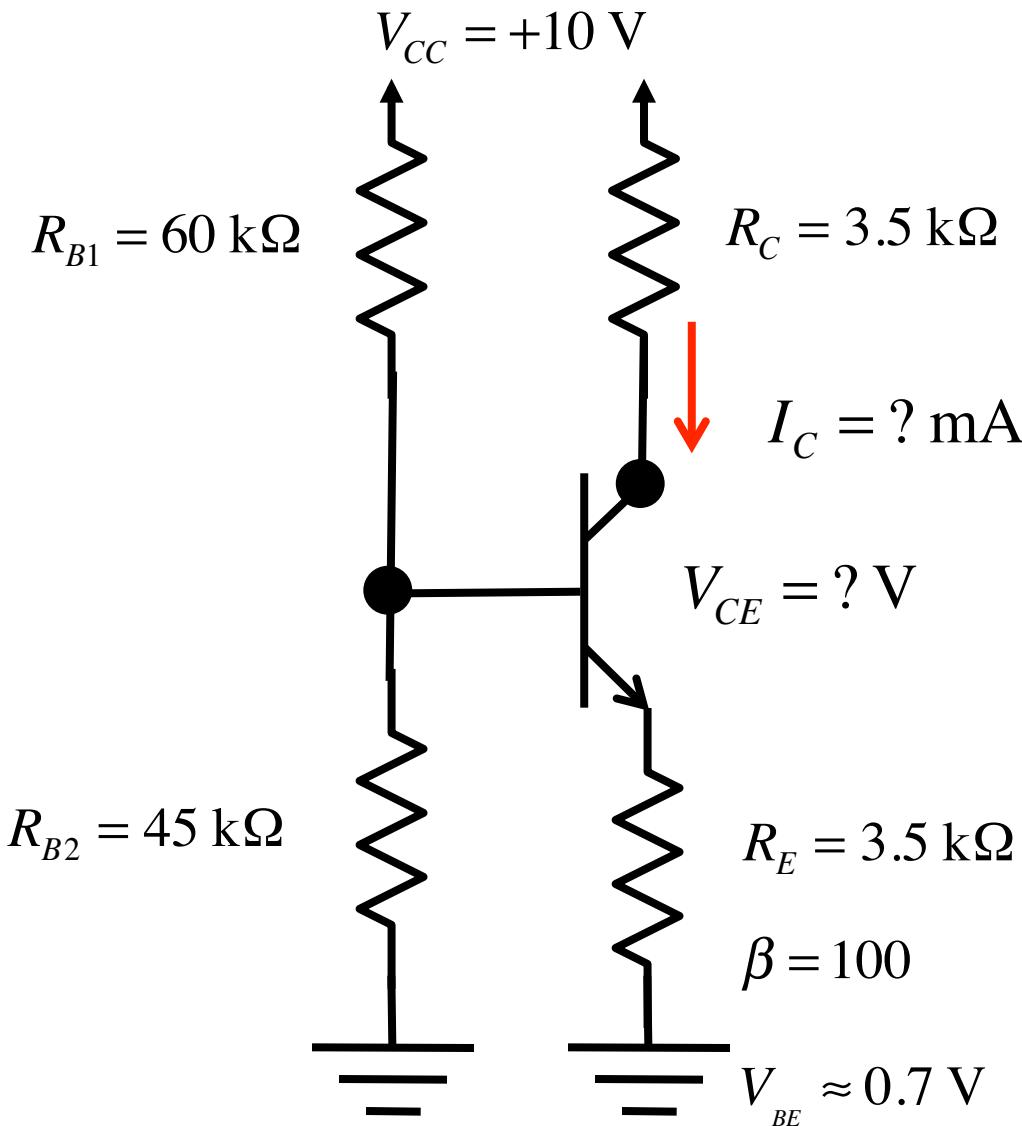


$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$I_C = 0.95 \text{ mA}$$

$$V_{CE} = 3.4 \text{ V}$$

Classic Bias circuit design

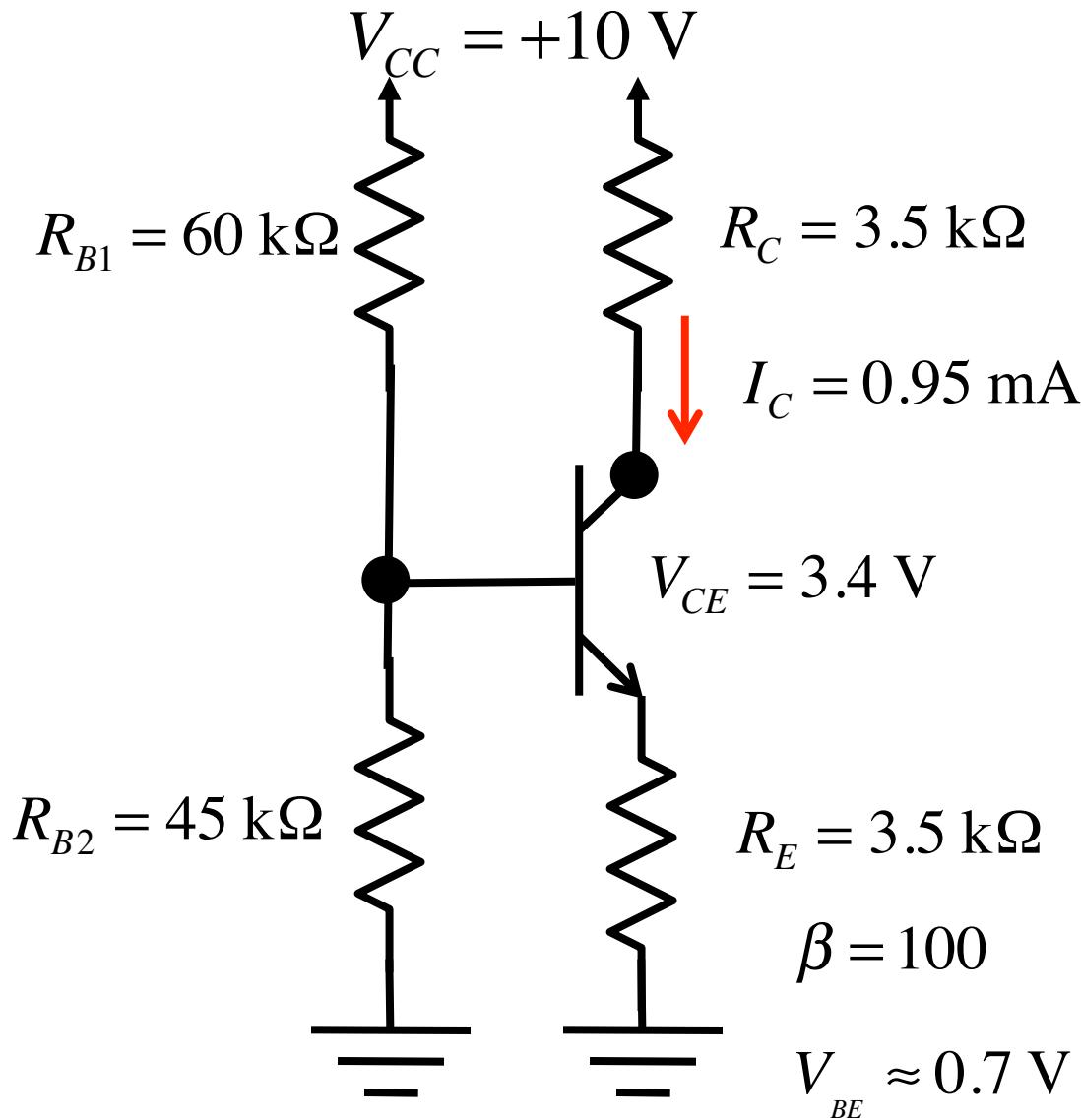


What if beta doubles?

$$I_C = 0.95\text{ mA} \\ \rightarrow 1.02\text{ mA}$$


**Why is the circuit
so good?**

Negative feedback

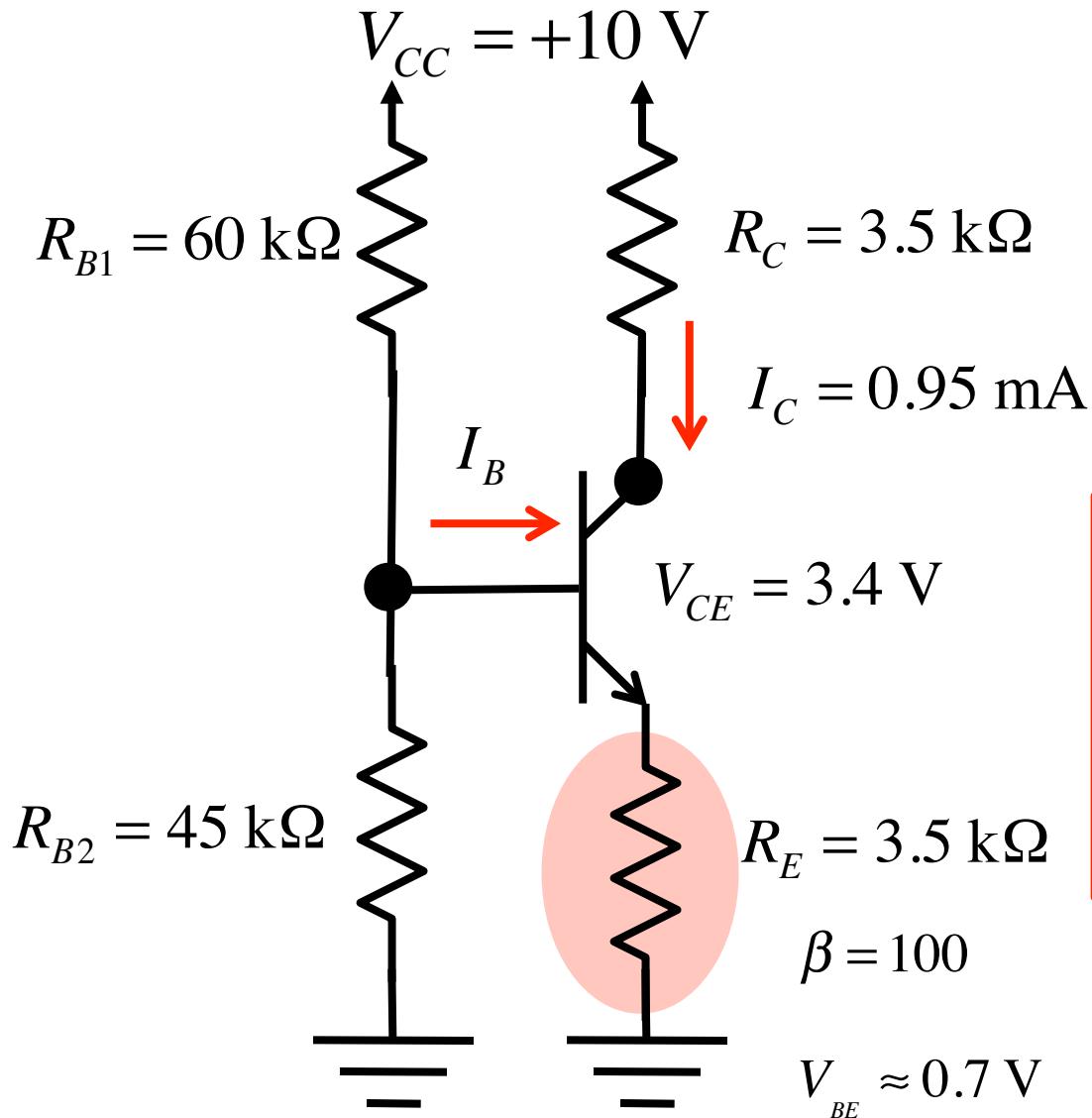

$I_C \uparrow$	$V_{R_E} \uparrow$	$I_B \downarrow$	$I_C \downarrow$
$I_C \downarrow$	$V_{R_E} \downarrow$	$I_B \uparrow$	$I_C \uparrow$

From the equations

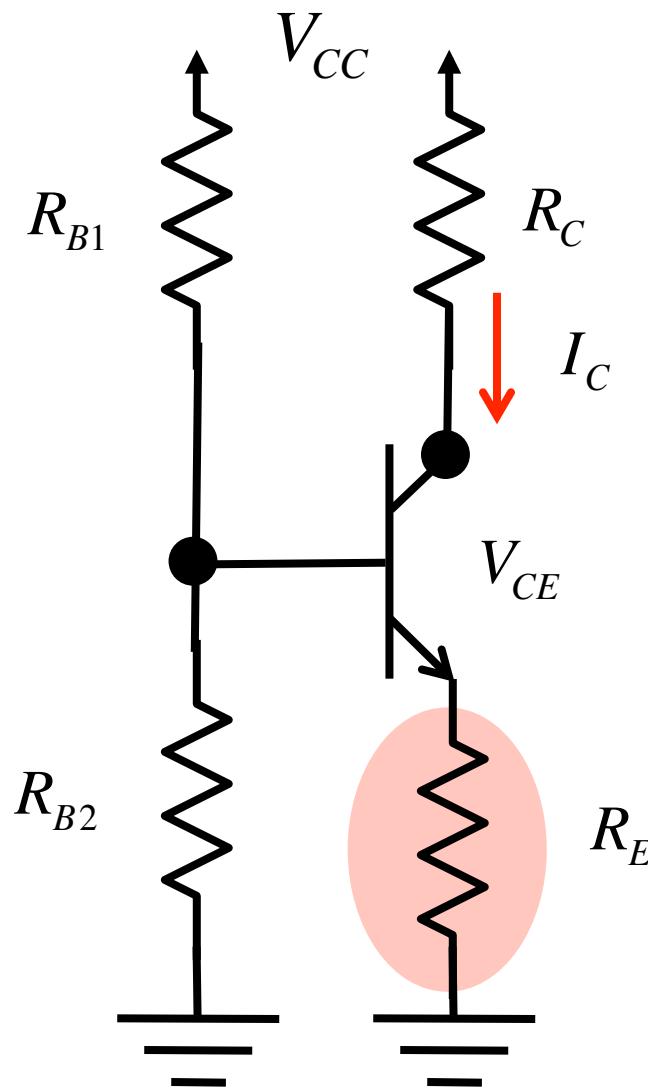

$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$(\beta + 1)R_E \gg R_{th}$$

$$I_C \approx \frac{\beta}{(\beta + 1)} \frac{V_{th} - V_{BE}}{R_E}$$

$$I_C \approx \frac{V_{th} - V_{BE}}{R_E}$$

Summary

Be comfortable analyzing NPN, PNP, and NPN-PNP DC circuits.

The classic 4-resistor bias circuit for discrete transistors makes use of negative feedback to deal with variations in beta.

For IC design, we don't use the 4-resistor bias circuit because high value resistors are “expensive”. Instead, we make use of transistors, because they are cheap.

BJT bias circuits

- 1) NPN and PNP circuits
- 2) Bias circuits (discrete)

