

Spring 2019 Purdue University

ECE 255: L15

DC MOSFET Circuits

(Sedra and Smith, 7th Ed., Sec. 5.3)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA

Lundstrom: 2019

Announcements

- 1) HW5 due Monday, Feb 18 5:00 PM in EE-209 Dropbox
- 2) Exam 1 can be picked up from Mary Ann Satterfield in MSEE 140

Outline

- 1) DC MOSFET Circuit **Analysis**
- 2) DC MOSFET Circuit **Design**
- 3) Examples

IV Summary (enhancement mode)

N-channel saturation

$$V_{GS} > V_{tn} \quad V_{tn} > 0 \text{ V}$$

$$V_{DS} > V_{DSsat} \quad V_{DSsat} = V_{GS} - V_{tn}$$

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2 (1 + \lambda V_{DS})$$

P-channel saturation


$$V_{SG} > |V_{tp}| \quad V_{tp} < 0 \text{ V}$$

$$V_{SD} > V_{SDsat} \quad V_{SDsat} = V_{SG} - |V_{tp}|$$

$$I_D = \frac{k'_p W}{2 L} (V_{SG} - |V_{tp}|)^2$$

$$I_D = \frac{k'_p W}{2 L} (V_{SG} - |V_{tp}|)^2 (1 + \lambda V_{SD})$$

MOSFET circuit analysis

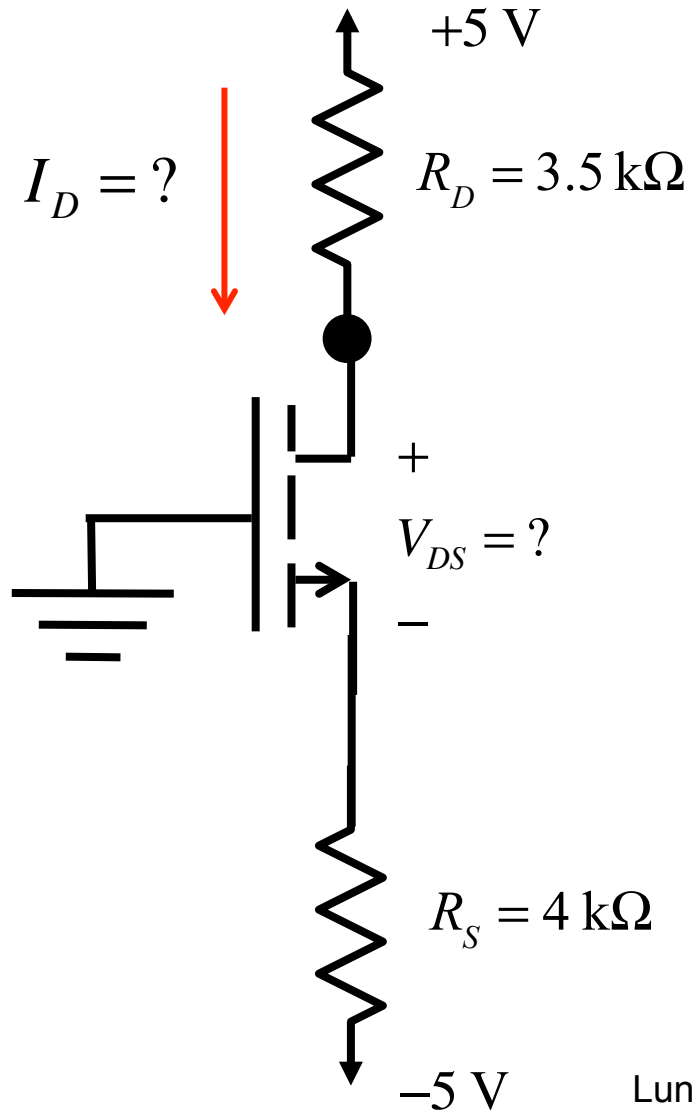

Transistor model:


$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

$$\frac{k'_n W}{2 L} = 1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

$$I_D = 1(V_{GS} - 1.0)^2$$

$$V_{GS} = ?$$

MOSFET circuit analysis (ii)

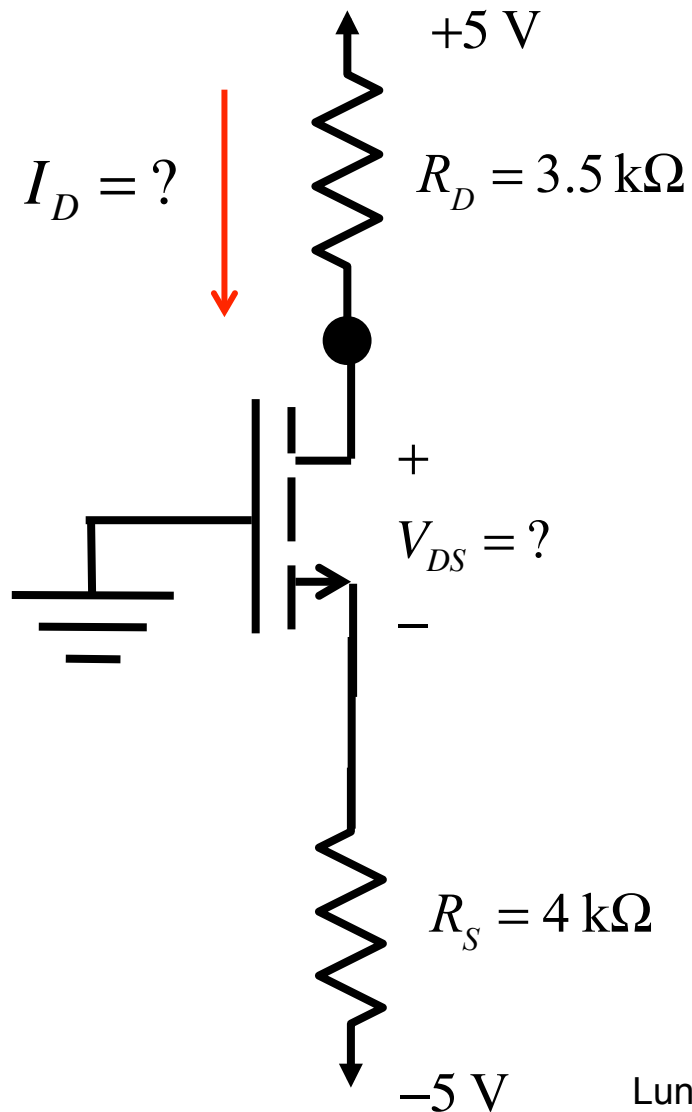

$$I_D = 1(V_{GS} - 1.0)^2$$

$$V_{GS} = ?$$


$$V_{GS} = V_G - V_S$$

$$V_S = -5 + I_D R_S$$

$$V_{GS} = 5 - I_D R_S$$

$$I_D = (5 - I_D R_S - 1.0)^2$$

MOSFET circuit analysis (iii)

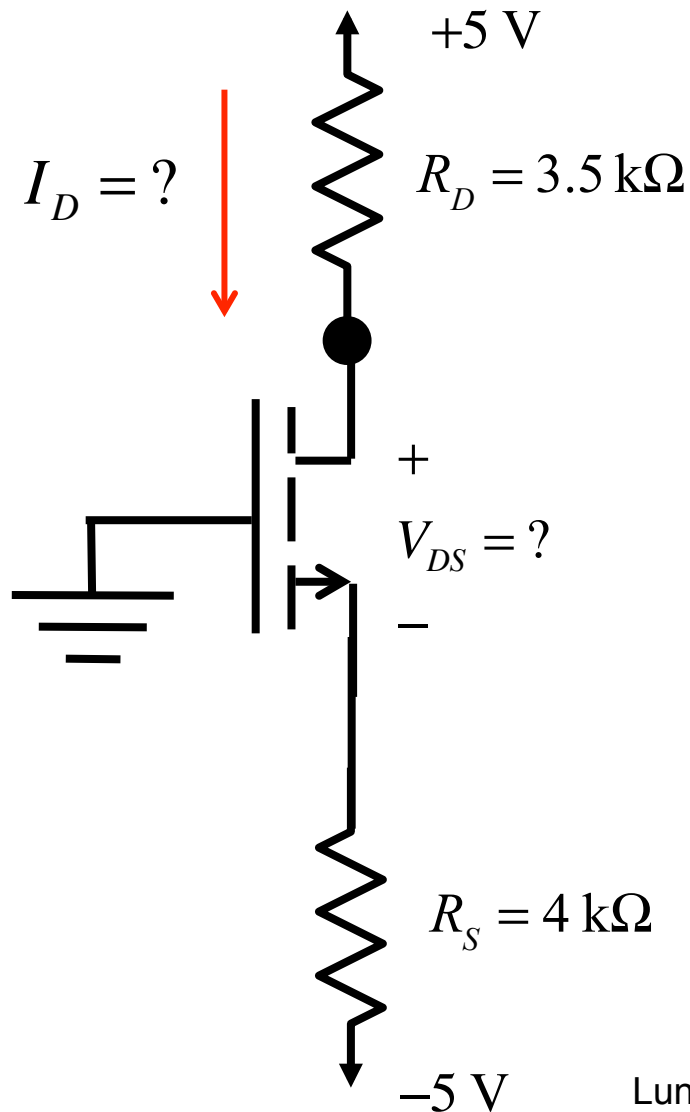

$$I_D = (5 - I_D R_S - 1.0)^2$$

$$I_D = (4 - I_D R_S)^2 = 16 - 8I_D R_S + I_D^2 R_S^2$$


$$I_D^2 R_S^2 - 8I_D R_S - I_D + 16 = 0$$

$$16I_D^2 - 33I_D + 16 = 0$$

$$I_D^2 - 2.06I_D + 1 = 0$$


$$I_D = \frac{2.06 \pm \sqrt{(2.06)^2 - 4}}{2} = 1.28 / 0.76$$

MOSFET circuit analysis (iv)

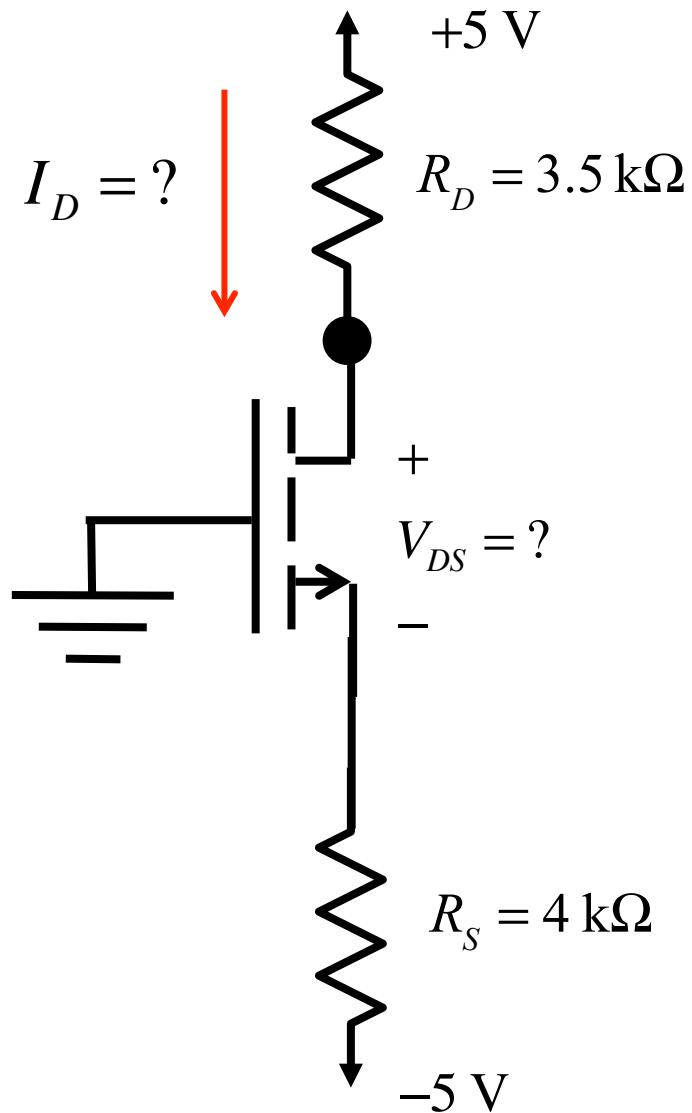

$I_D = 1.28 \text{ mA}$ **Does not work.**

MOSFET circuit analysis (iv)

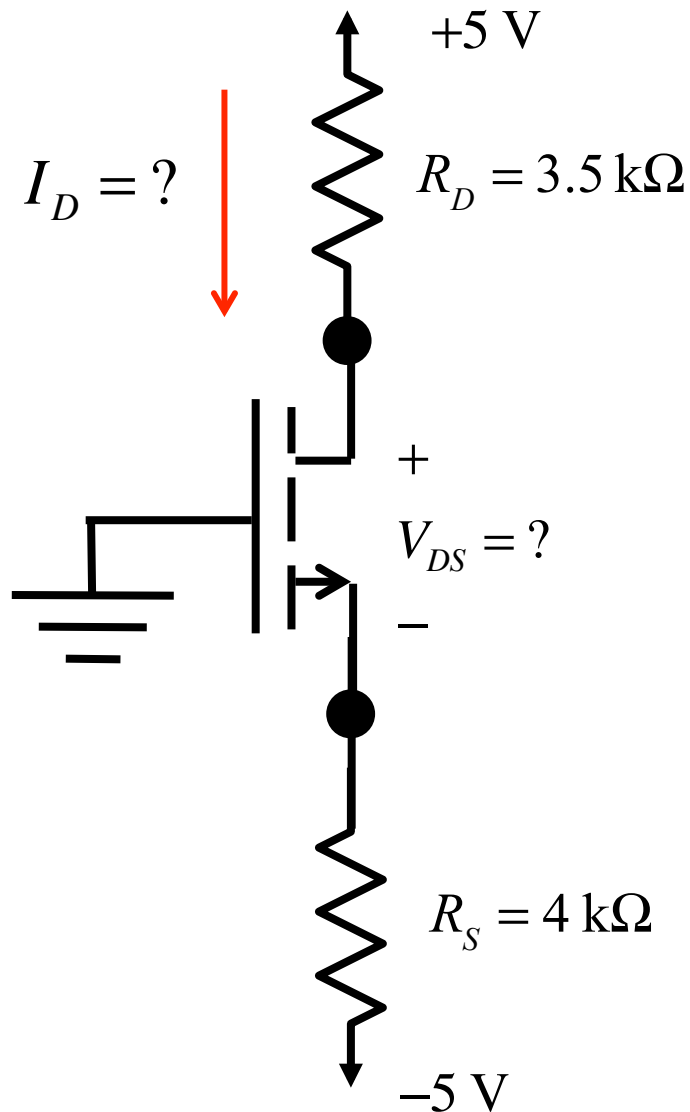

$$I_D = 0.76\text{ mA}$$

$$V_D = 5 - I_D R_D = 2.3\text{ V}$$

$$V_S = -5 + I_D R_S = -1.96\text{ V}$$


$$V_{GS} = -V_S = 1.96\text{ V} > V_{tn} \quad \checkmark$$

$$V_{DS} = V_D - V_S = 4.26\text{ V}$$

$$V_{DSsat} = V_{GS} - V_{tn} = 0.96\text{ V}$$

$$V_{DS} > V_{DSsat} \quad \checkmark$$

MOSFET circuit design

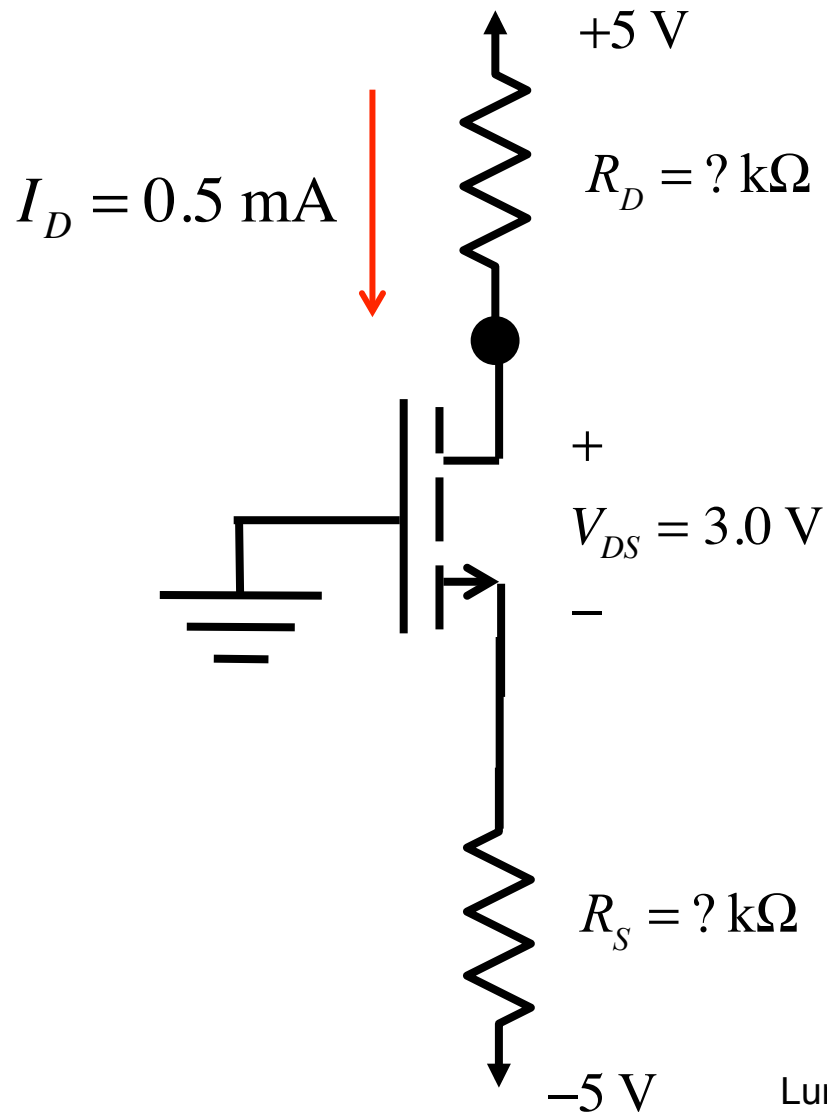

Transistor model:


$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

$$\frac{k'_n W}{2 L} = 1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

$$I_D = 1(V_{GS} - 1.0)^2 = 0.5$$

$$V_{GS} = 1.707$$

MOSFET circuit design (ii)

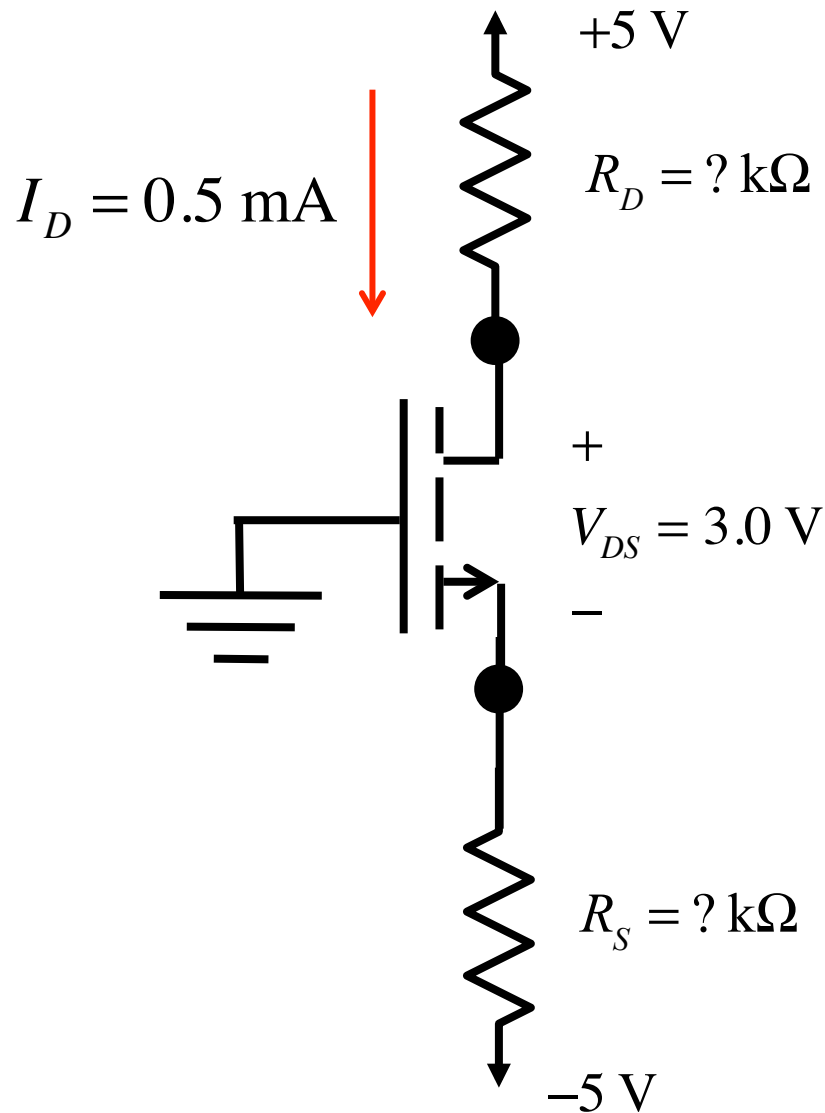

$$V_{GS} = 1.707$$

$$V_{GS} = V_G - V_S = 1.707$$

$$V_S = -1.707 = -5 + I_D R_S$$

$$R_S = 6.6 \text{ k}\Omega \quad \checkmark$$

$$V_{DS} = V_D - V_S = V_D + 1.707 = 3.0$$


$$V_D = 1.29 = 5 - 0.5 R_D$$

$$R_D = 7.4 \text{ k}\Omega \quad \checkmark$$

Outline

- 1) DC MOSFET Circuit **Analysis**
- 2) DC MOSFET Circuit **Design**
- 3) Examples

MOSFET circuit design

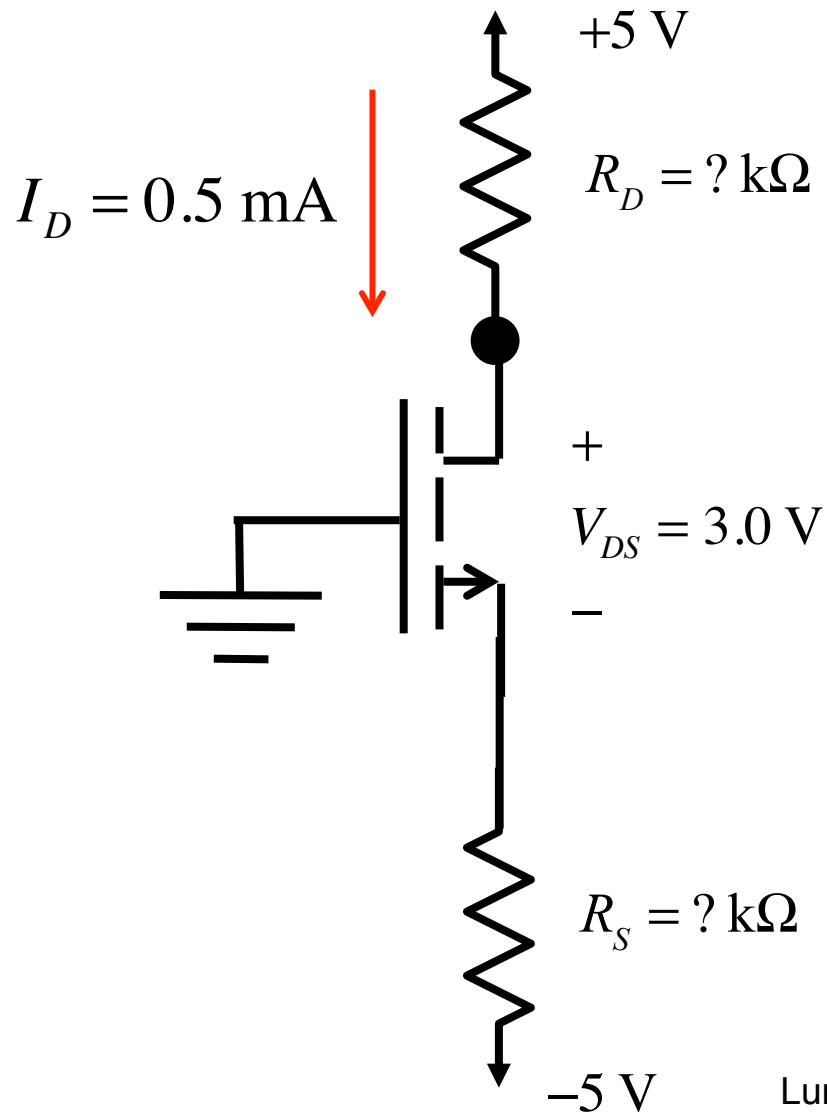


Transistor model:

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$


$$\frac{k'_n W}{2 L} = 1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

Select the resistors to produce a given I_D and V_{DS}

MOSFET DC model

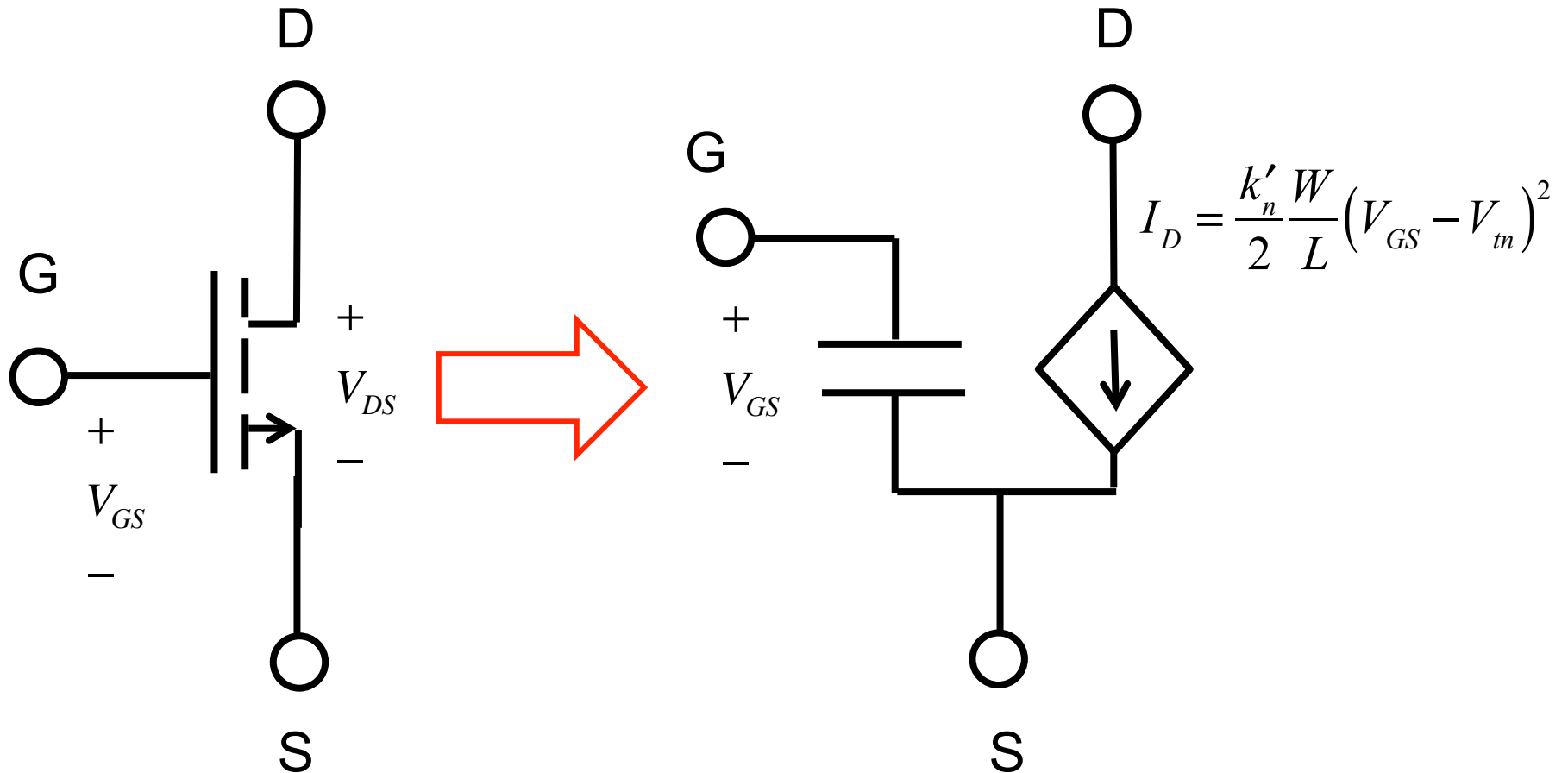

P-MOSFET circuit design

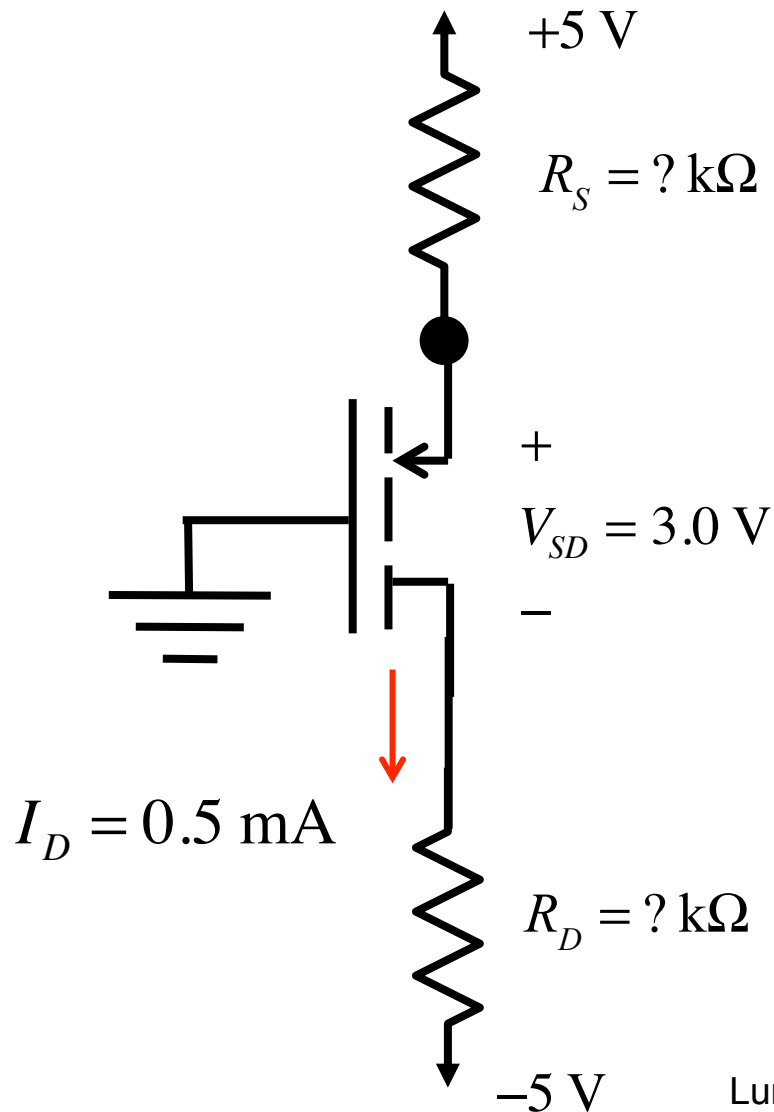

Transistor model:


$$I_D = \frac{k'_p}{2} \frac{W}{L} (V_{SG} - |V_{tp}|)^2$$

$$\frac{k'_p}{2} \frac{W}{L} = 1 \text{ mA/V}^2 \quad V_{tp} = -1.0 \text{ V}$$


$$I_D = 1(V_{SG} - 1.0)^2 = 0.5$$

$$V_{SG} = 1.707$$

P-MOSFET circuit design (ii)

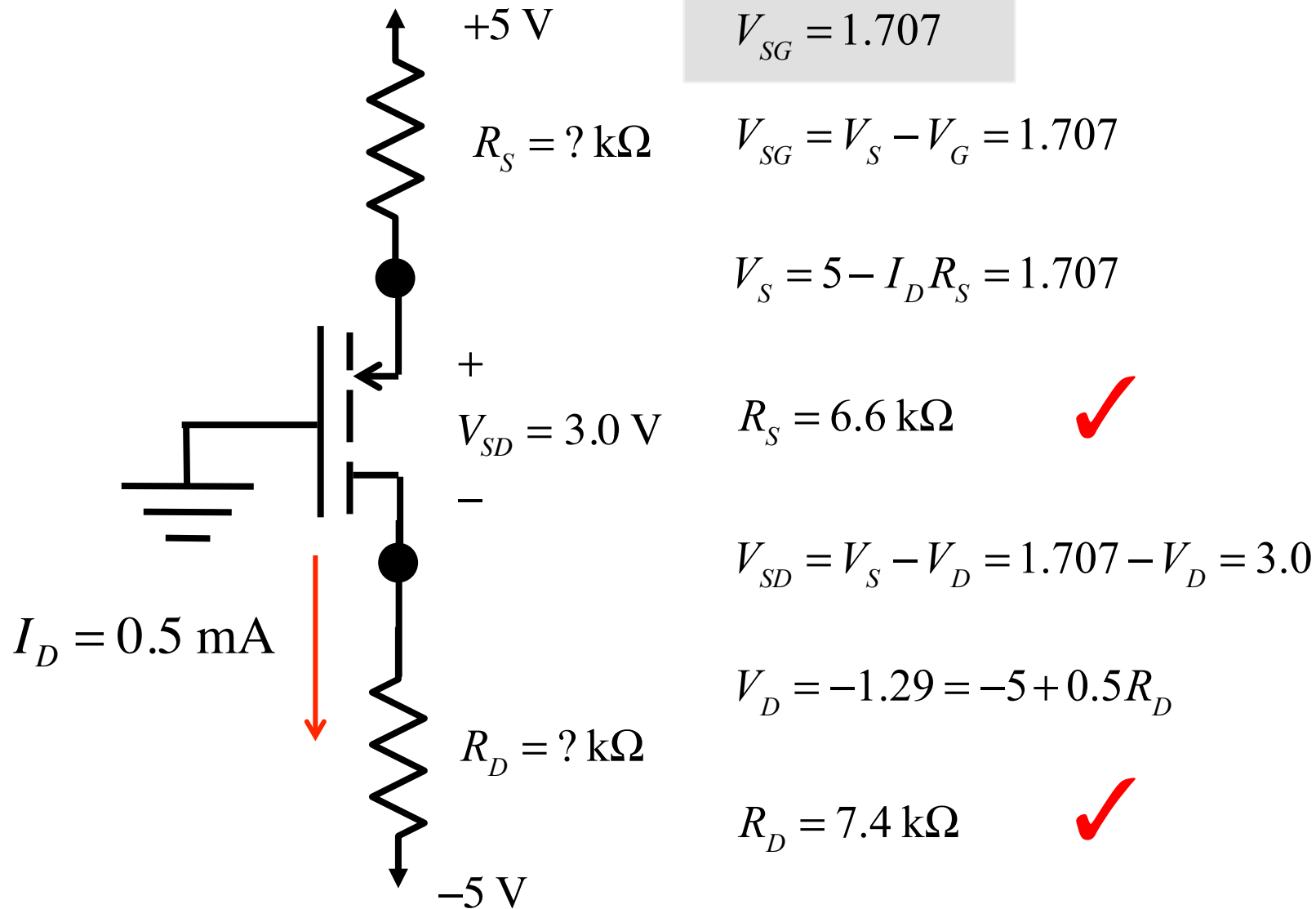

MOSFET circuit analysis

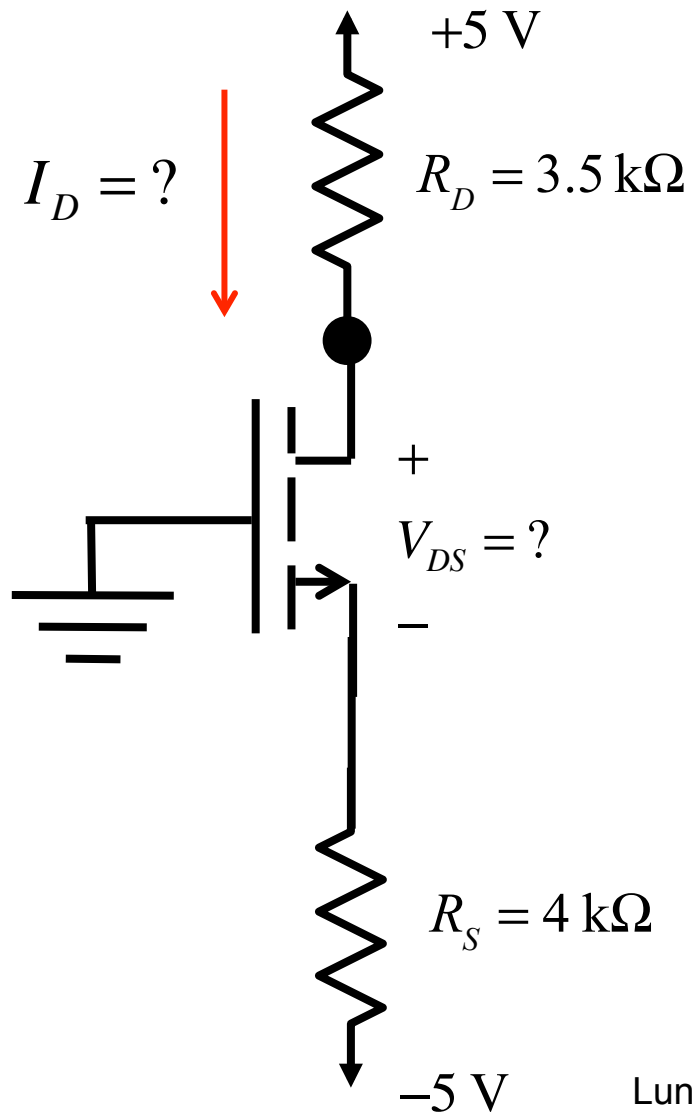


Transistor model:

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

$$\frac{k'_n W}{2 L} = 1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

Given a transistor and a circuit, find I_D and V_{DS}

P-MOSFET circuit analysis

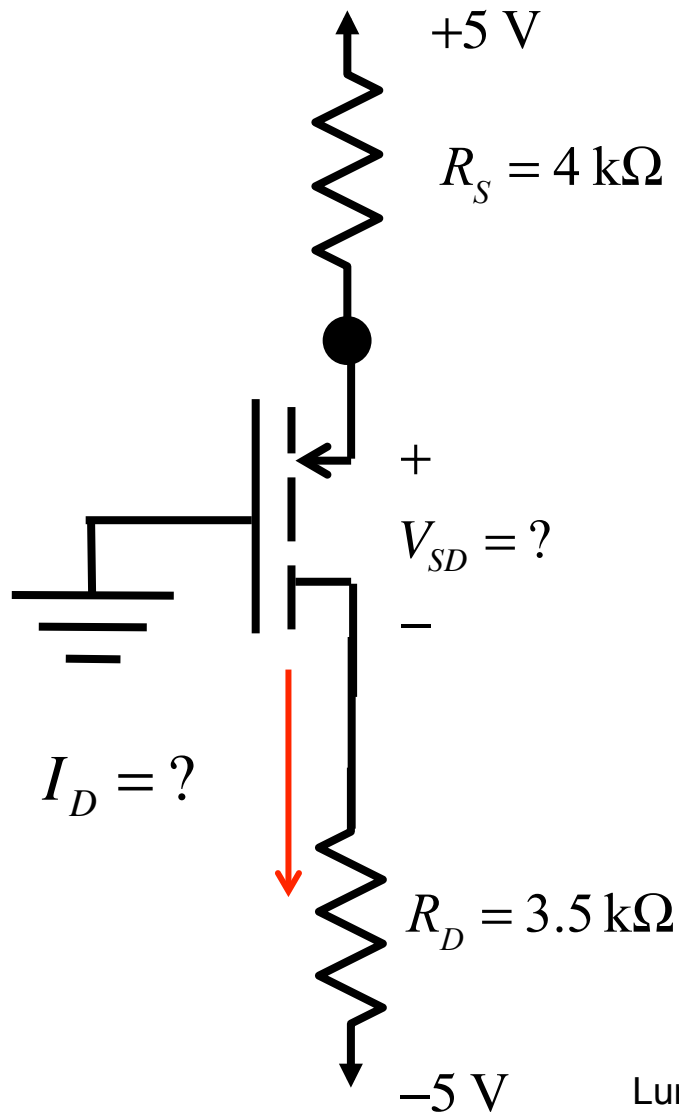

Transistor model:

$$I_D = \frac{k'_p W}{2 L} (V_{SG} - |V_{tp}|)^2$$

$$\frac{k'_p W}{2 L} = 1 \text{ mA/V}^2 \quad V_{tp} = -1.0 \text{ V}$$

$$I_D = 1(V_{SG} - 1.0)^2$$

$$V_{SG} = 5 - I_D R_S$$

P-MOSFET circuit analysis

$$I_D = 1(V_{SG} - 1.0)^2$$

$$V_{SG} = 5 - I_D R_S$$

$$I_D = (5 - I_D R_S - 1.0)^2$$

$$I_D = (5 - V_{SG}) / R_S = (5 - V_{SG}) / 4$$

$$I_D^2 - 2.06I_D + 1 = 0$$

$$4V_{SG}^2 - 7V_{SG} - 1 = 0$$

$$I_D = 1.28 \text{ or } 0.76$$

$$V_{SG} = 1.88 \text{ or } -0.13$$

$$I_D = 0.76$$


$$V_{SG} = 1.88$$

$$I_D = 0.77$$

Examples

To *really* learn this, we need to work out a lot of examples.

Example 1a: analysis

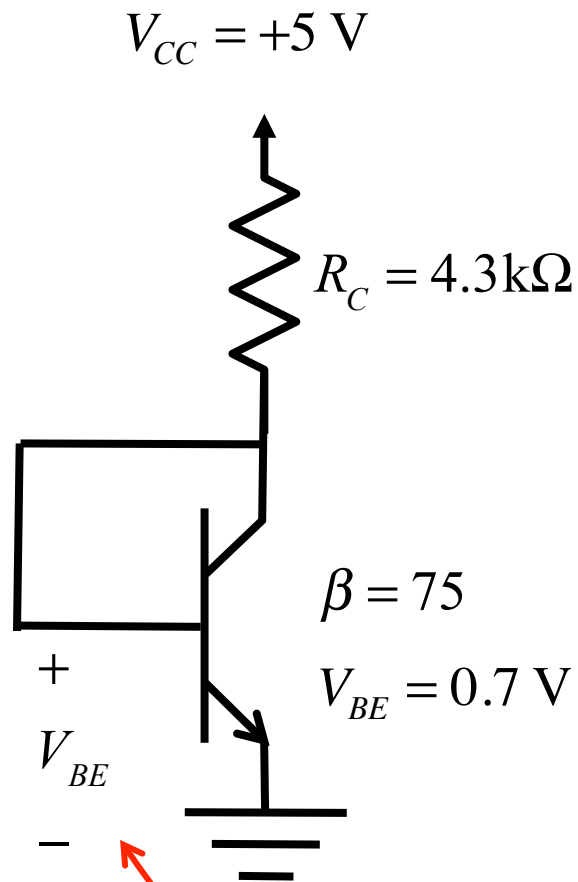

1) Operating region?


$$I_R = \frac{5 - 0.7}{R_C} = \frac{4.3}{4.3} = 1.0 \text{ mA}$$

$$I_C + I_B = I_R$$

$$I_C = I_R \frac{\beta}{\beta + 1} = 1.0 \frac{75}{76} = 0.99 \text{ mA}$$

We can guess this voltage

Example 1b: analysis

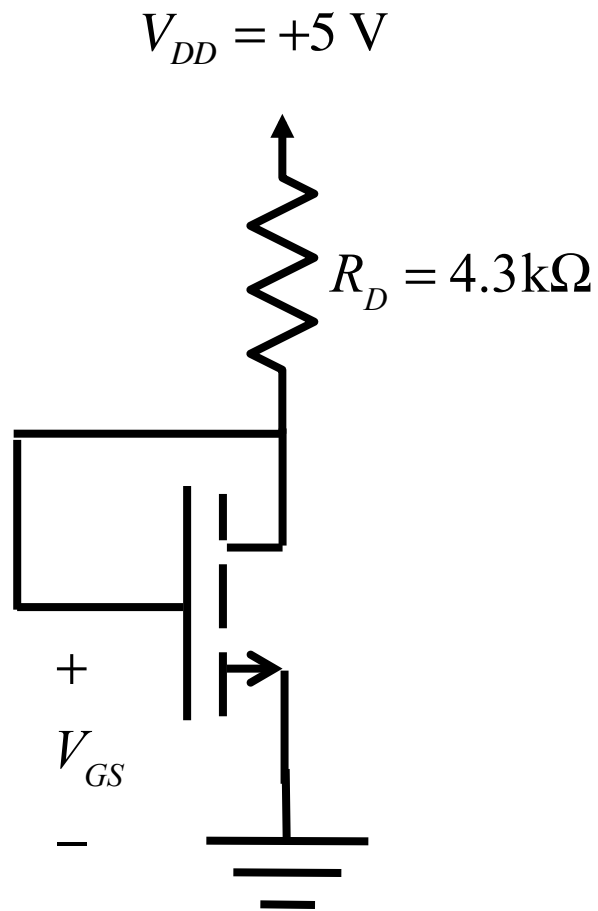

1) Operating region?

$$V_{GS} = V_D$$


$$V_{DS} = V_D$$

$$V_{DS} > V_{GS} - V_{tn}$$


Saturation

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

Example 1b: analysis

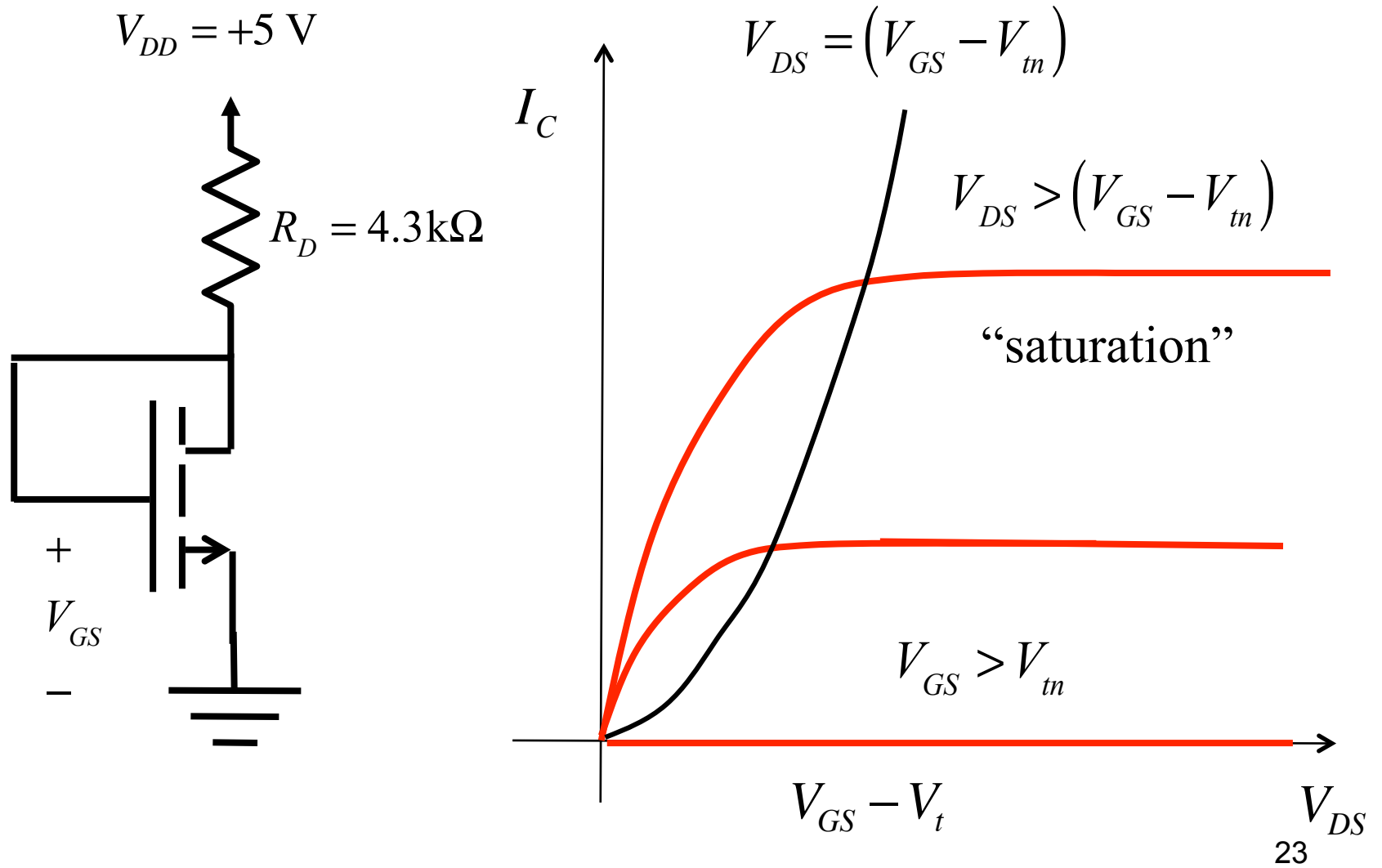

Example 1b: analysis

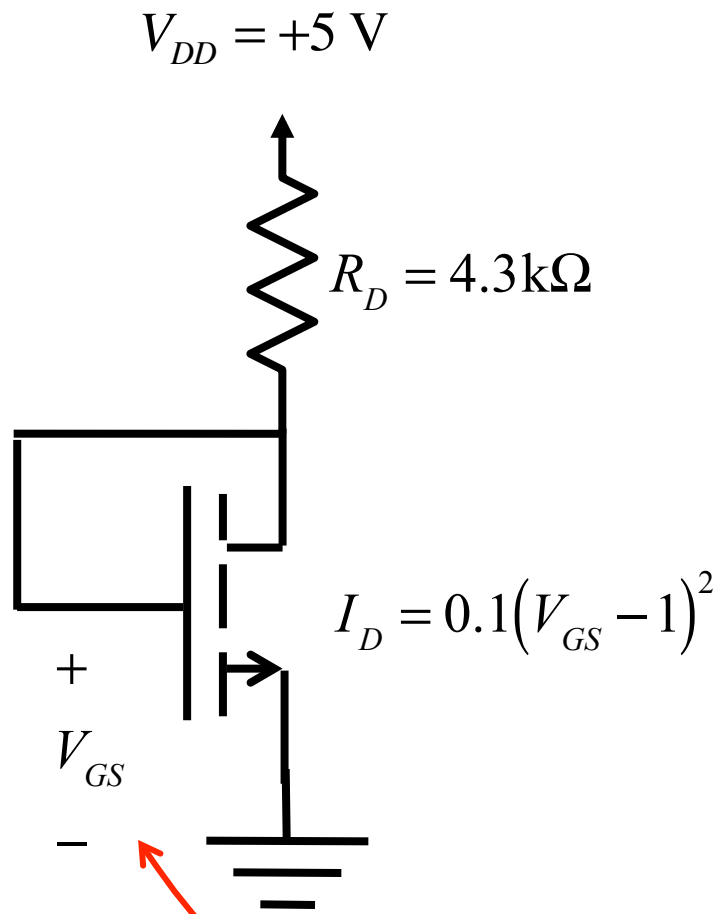

$$I_D = 0.1(V_{GS} - 1)^2$$

$$V_{GS} = 5 - I_D R_D = 5 - 4.3I_D$$


$$I_D^2 - 2.86I_D + 1.35 = 0$$

$$I_D = 2.26 \text{ or } 0.60$$

$$I_D = 0.60$$

We can't guess this voltage

Practice

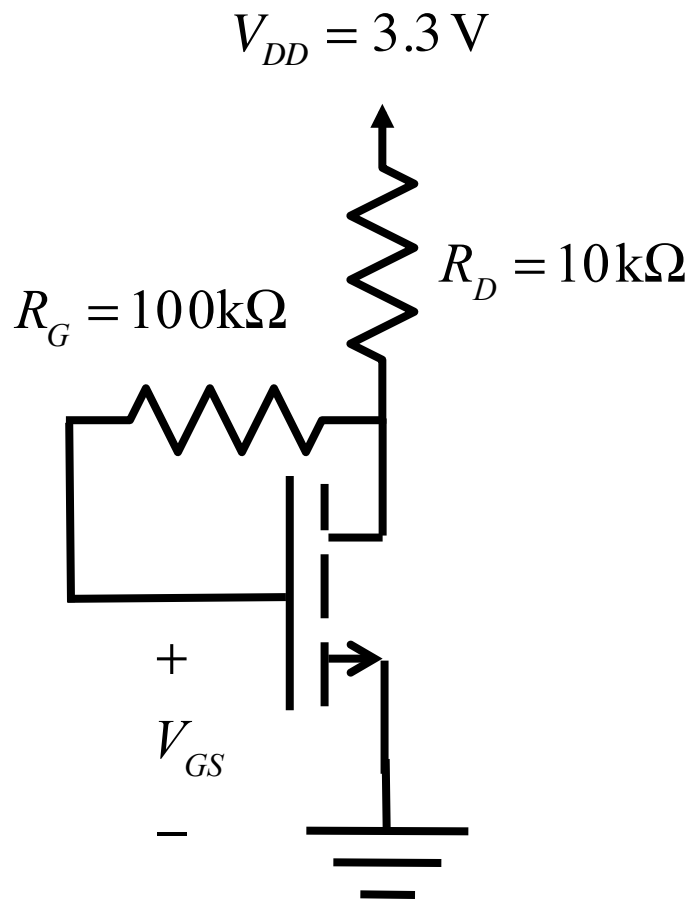

Transistor model:

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - |V_{tn}|)^2$$

$$I_D = \frac{k_n}{2} (V_{GS} - |V_{tn}|)^2$$


$$k_n = 260 \mu\text{A}/\text{V}^2 \quad V_{tn} = 1.0 \text{ V}$$

Show that:

$$I_D = 0.13 \text{ mA}$$

$$V_{DS} = 2.0 \text{ V}$$

Example 2a: design

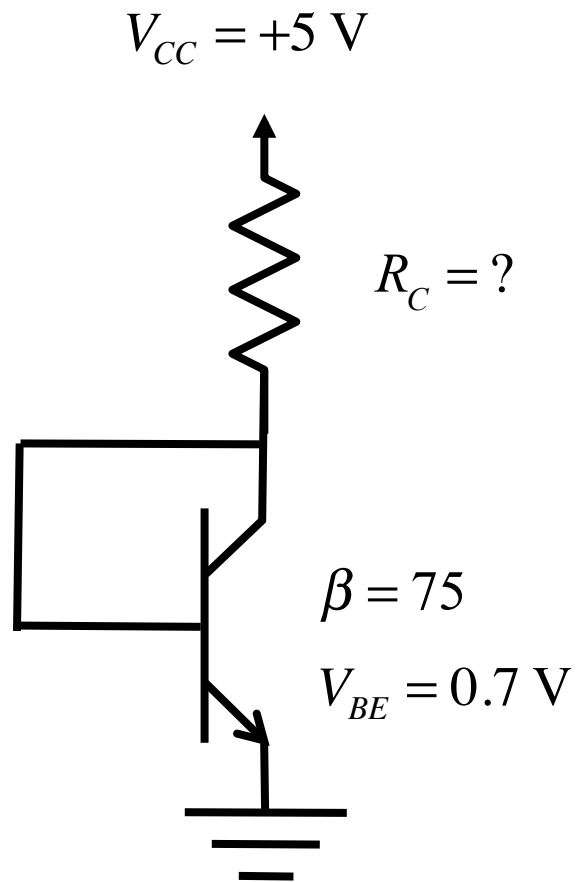

Design for: $I_C = 0.5 \text{ mA}$


$$I_R = I_C \frac{\beta + 1}{\beta}$$

$$I_R = 0.5 \frac{76}{75} = \frac{5 - 0.7}{R_C}$$

$$R_C = 8.49 \text{ k}\Omega$$

Example 2b: design

$$V_{DD} = +5 \text{ V}$$

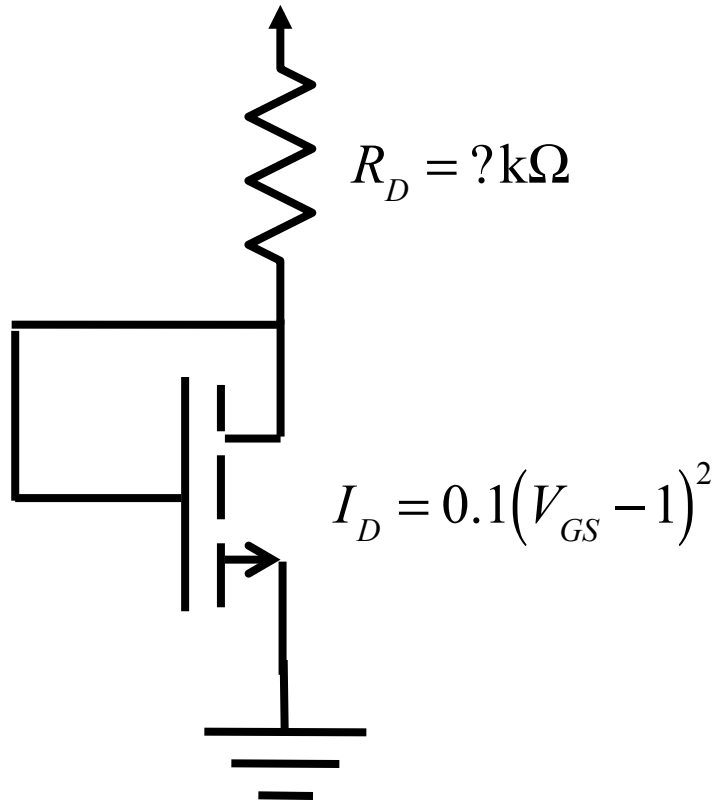

Design for: $I_D = 0.5 \text{ mA}$

$$I_D = 0.1(V_{GS} - 1)^2$$

$$0.5 = 0.1(V_{GS} - 1)^2$$


$$V_{GS} = 3.24 \text{ V}$$

$$V_{GS} = V_D = 3.24 \text{ V}$$

$$R_D = \frac{5 - 3.24}{0.5} = 3.53 \text{ k}\Omega$$

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_{tn})^2$$

Example 3: design (i)

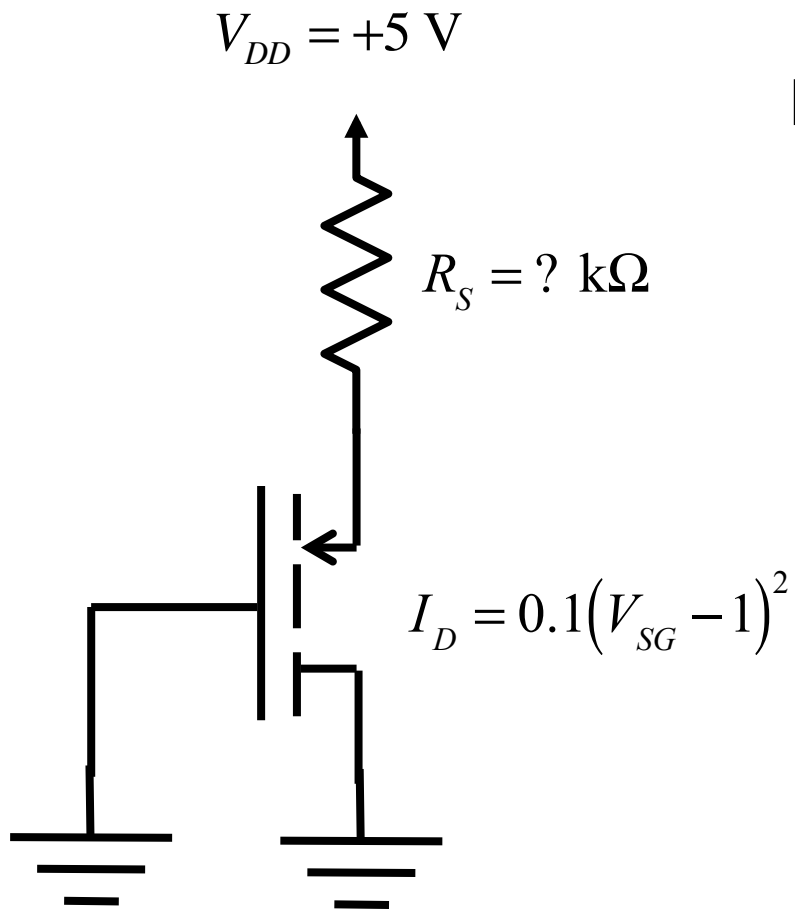

Design for: $I_D = 0.5\text{ mA}$

1) Operating region?

$$V_{DS} > V_{GS} - V_{tn} ?$$


$$V_{SD} > V_{SG} - |V_{tp}| ?$$

saturation

$$I_D = \frac{k'_p}{2} \frac{W}{L} (V_{SG} - |V_{tp}|)^2$$

Example 3: design (ii)

$$V_{DD} = +5 \text{ V}$$

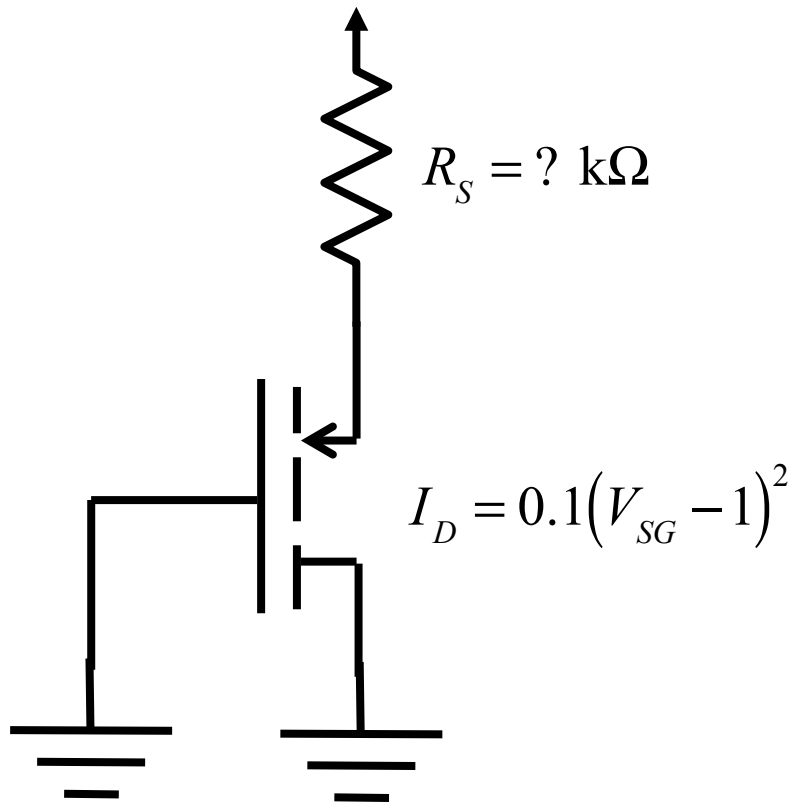

Design for: $I_D = 0.5 \text{ mA}$

$$I_D = 0.1(V_{SG} - 1)^2$$

$$0.5 = 0.1(V_{SG} - 1)^2$$


$$V_{SG} = 3.24 \text{ V}$$

$$V_{SG} = V_S = 3.24 \text{ V}$$

$$R_D = \frac{5 - 3.24}{0.5} = 3.53 \text{ k}\Omega$$

$$I_D = \frac{k'_p W}{2 L} (V_{SG} - |V_{tp}|)^2$$

Example 4

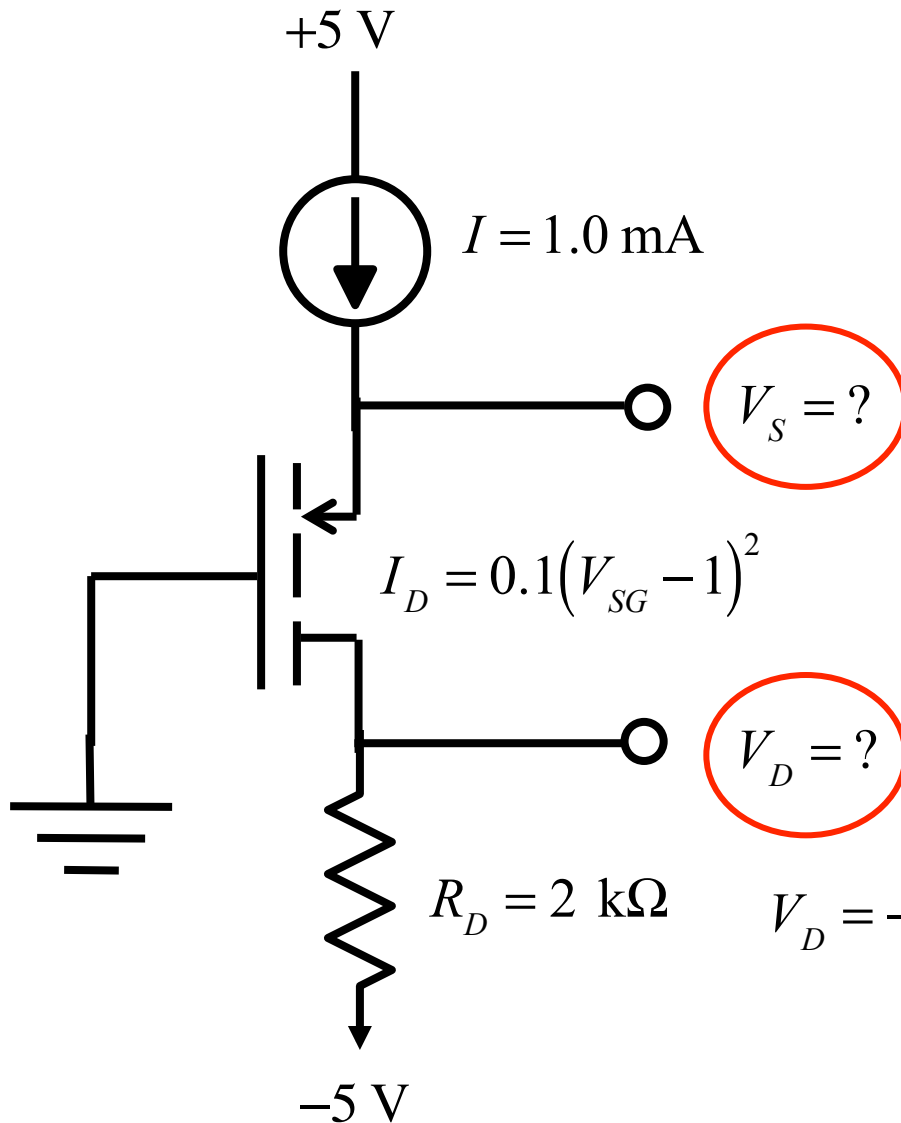


$$V_S = V_{SG}$$

$$1 = 0.1(V_{SG} - 1)^2$$

$$V_{SG} = V_S = 4.16 \text{ V}$$

$$V_D = -5 + I_D R_D = -5 + 1 \times 2 = -3 \text{ V}$$

Example 5

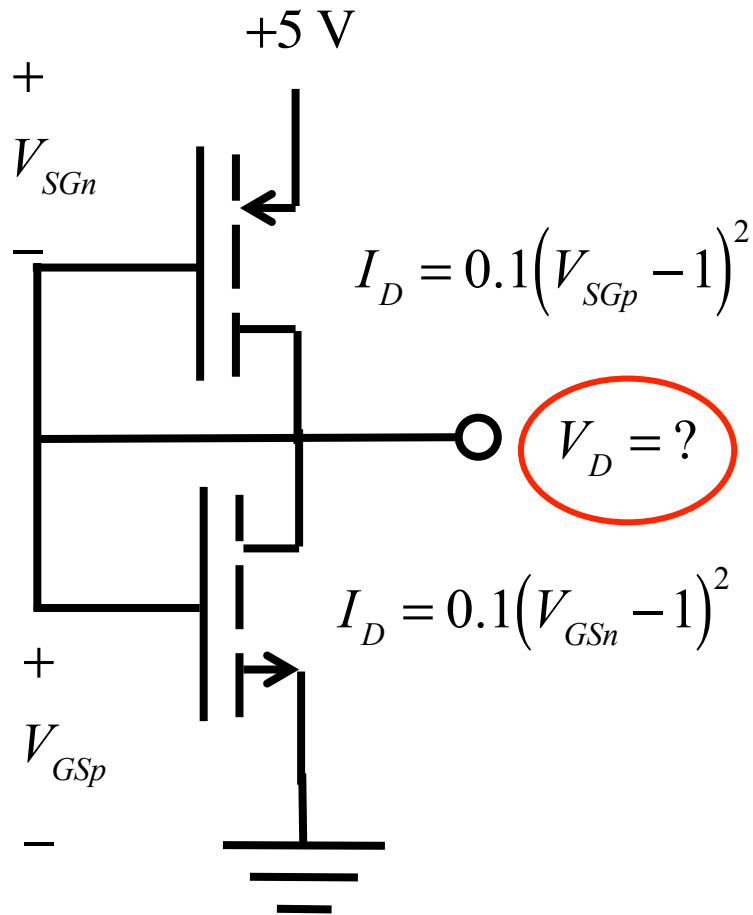

1) Operating region?

$$V_{DSn} = V_D \quad V_{GSn} = V_D$$


$$V_{DSn} > (V_{GSn} - V_{tn})$$

$$V_{SDp} = 5 - V_D \quad V_{SGp} = 5 - V_D$$

$$V_{SDp} > (V_{SGp} - |V_{tp}|)$$

saturation

Example 5

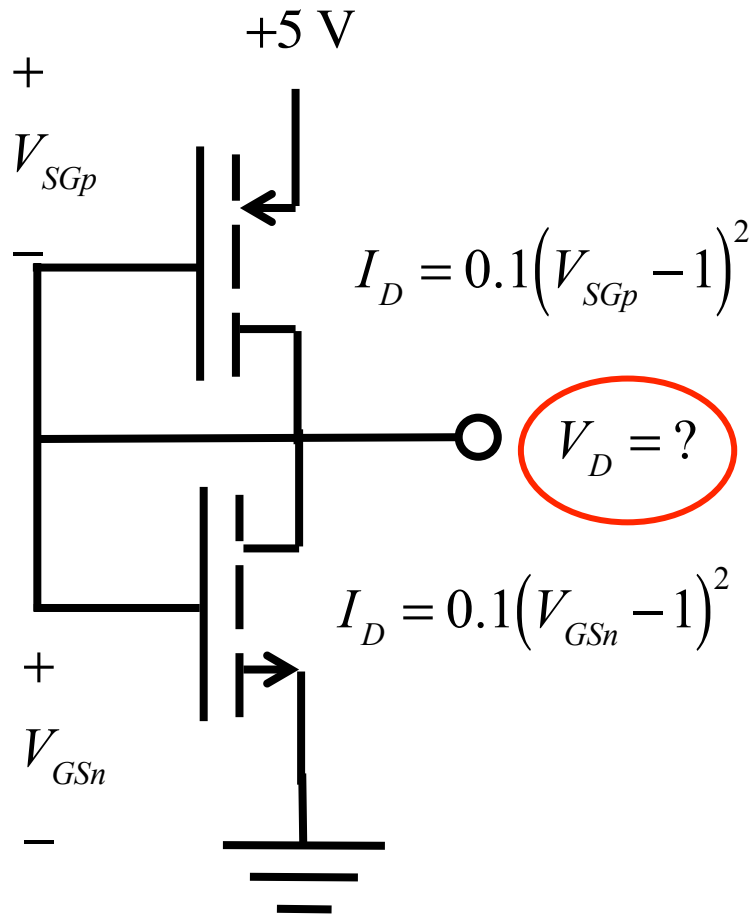


$$V_{GSn} = V_{SGp} \quad \text{Why?}$$

$$V_{GSn} + V_{SGp} = 5$$

$$V_D = 2.5$$

$$I_D = 0.1(2.5 - 1)^2 = 0.225 \text{ mA}$$

Example 6: Analysis

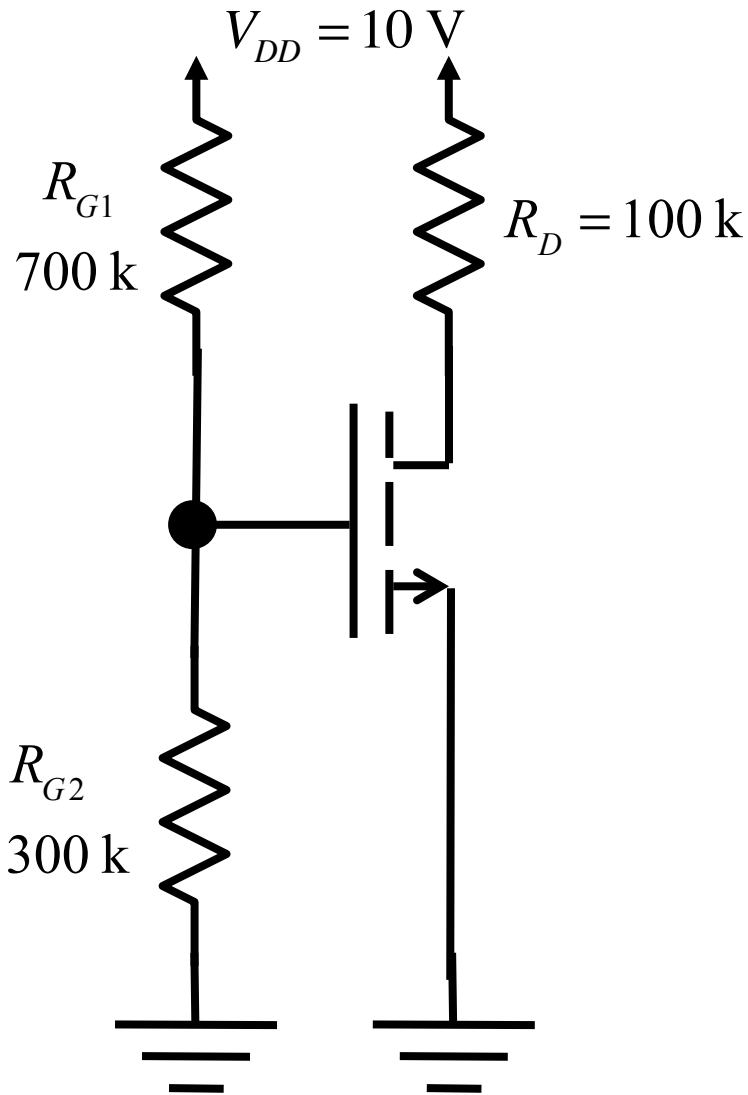

Transistor model:

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - |V_{tn}|)^2$$

$$I_D = \frac{k_n}{2} (V_{GS} - |V_{tn}|)^2$$

$$k_n = 25 \mu\text{A}/\text{V}^2 \quad V_{tn} = 1.0 \text{ V}$$

$$I_D = \frac{0.025}{2} (V_{GS} - 1)^2 \text{ mA} \quad V_{GS} = 3$$

$$I_D = 0.05 \text{ mA}$$

$$V_{DS} = 5 \text{ V} > V_{GD} - V_{tn}$$

Summary

- 1) DC MOSFET **analysis** often involves solving a quadratic equation and throwing away the unphysical solution.
- 2) DC MOSFET **design** is easier.

DC MOSFET Circuits

- 1) DC MOSFET Circuit **Analysis**
- 2) DC MOSFET Circuit **Design**
- 3) Examples

