

Spring 2019 Purdue University

ECE 255: L16

Biasing MOSFETs and BJTs

(Sedra and Smith, 7th Ed., Sec. 7.4)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA


Lundstrom: 2019

PURDUE
UNIVERSITY


Outline

- 1) Bias circuit design
- 2) BJT bias circuits
- 3) Load line analysis
- 4) MOSFET bias circuits
- 5) Load line analysis

Operating point and bias circuit design

 


Classic 4-resistor Bias circuit

 


Suitable for
discrete transistors.


Classic bias circuit analysis

 


Classic Bias circuit analysis

 

Classic Bias circuit analysis

 

Classic Bias circuit analysis

 


$$V_{th} = I_B R_{th} + V_{BE} + (I_B + I_C) R_E$$

$$V_{th} = I_B R_{th} + V_{BE} + (\beta + 1) I_B R_E$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$I_C = \frac{\beta (V_{th} - V_{BE})}{R_{th} + (\beta + 1) R_E}$$

Classic bias circuit analysis

 


$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$R_{th} = R_{B1} \parallel R_{B2}$$

$$V_{th} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

Classic bias circuit analysis

 


$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$V_{CE} = V_{CC} - I_C R_C - \frac{I_C}{\alpha} R_E$$

$$I_C = 0.95 \text{ mA}$$

$$V_{CE} = 3.4 \text{ V}$$

Sensitivity to beta

 


What if beta doubles?

$$I_C = 0.95\text{ mA} \\ \rightarrow 1.02\text{ mA}$$


**Why is the circuit
so good?**

Negative feedback

 

$I_C \uparrow$	$V_{R_E} \uparrow$	$I_B \downarrow$	$I_C \downarrow$
$I_C \downarrow$	$V_{R_E} \downarrow$	$I_B \uparrow$	$I_C \uparrow$

From the equations

 


$$I_C = \beta \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$

$$(\beta + 1)R_E \gg R_{th}$$

$$I_C \approx \frac{\beta}{(\beta + 1)} \frac{V_{th} - V_{BE}}{R_E}$$

$$I_C \approx \frac{V_{th} - V_{BE}}{R_E}$$

Classic Bias circuit design

 

Start at the output:


Have 7 V to split between 2 resistors.

Let: $V_{R_C} = V_{R_E} = 3.5\text{ V}$

$$R_C = \frac{3.5\text{ V}}{1.0\text{ mA}} = 3.5\text{ k}\Omega$$

$$R_E = \frac{3.5\text{ V}}{1.01\text{ mA}} \approx 3.5\text{ k}\Omega$$

Classic Bias circuit design

 

Now move to the input:


$$\begin{aligned}V_B &= V_{R_E} + 0.7 \\&= 3.5 + 0.7 = 4.2\text{ V}\end{aligned}$$

$$I_B = \frac{I_C}{100} = \frac{0.01}{100} \text{ mA}$$

$$\beta = 100$$

$$V_{BE} \approx 0.7\text{ V}$$

Classic Bias circuit design

 

Choose:


$$I_{R_{B1}} = 10I_B = 0.1 \text{ mA}$$

$$I_{R_{B1}} = 0.1 \text{ mA} = \frac{(10 - 4.2) \text{ V}}{R_{B1}} \rightarrow 58 \text{ k}\Omega$$

$$\begin{aligned} I_{R_{B2}} &= I_{R_{B1}} - I_B \\ &= 10I_B - I_B = 0.09 \text{ mA} \end{aligned}$$

$$I_{R_{B2}} = 0.09 \text{ mA} = \frac{4.2 \text{ V}}{R_{B2}} \rightarrow 46.7 \text{ k}\Omega$$

Load line analysis (input)

 


1) Device:

$$I_B = \frac{I_S}{\beta} e^{V_{BE}/V_T}$$


2) Circuit:

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$


Load line analysis (input)

 

Load line analysis (output)

 

1) Device:

 


2) Circuit:


$$V_{CC} = I_C R_C + V_{CE} + \frac{I_C}{\alpha} R_E$$

$$I_C \approx \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

Load line analysis (output)

 


MOSFET 4-resistor bias circuit

 

Analysis: Given the resistors, power supply voltage, transistor parameters, find the currents and voltages.

Design: given the transistor parameters, power supply, and desired currents and voltages, find the resistor values.

MOSFET 4-resistor bias circuit design

 

Transistor model:

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$

$$\frac{k'_n}{2} \frac{W}{L} = 0.1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$


$$I_D = 0.1(V_{GS} - 1)^2 \quad 1) \text{ device}$$

$$1 = 0.1(V_{GS} - 1)^2 \quad 2) \text{ given current}$$

3) Solve for V_{GS}

4) Select resistors to produce V_{GS} and V_{DS}

MOSFET 4-resistor bias circuit design

 

Transistor model:


$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$

$$\frac{k'_n}{2} \frac{W}{L} = 0.1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

$$1 = 0.1 (V_{GS} - 1)^2$$

$$V_{GS} = 4.16$$

MOSFET 4-resistor bias circuit design

 

$$1 = 0.1(V_{GS} - 1)^2$$

$$V_{GS} = 4.16$$

(some arbitrary choices)


$$V_S = 2.5 \quad R_S = R_D = 2.5 \text{ k}\Omega$$

$$V_G = 2.5 + 4.16 = 6.66$$

$$R_S = 2.5 \text{ k}\Omega \quad R_{G1} = 50 \text{ k}\Omega$$

$$R_D = 2.5 \text{ k}\Omega \quad R_{G2} = 100 \text{ k}\Omega$$

MOSFET 4-resistor bias circuit analysis

 

Transistor model:

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$


$$\frac{k'_n}{2} \frac{W}{L} = 0.1 \text{ mA/V}^2 \quad V_{tn} = 1.0 \text{ V}$$

$$I_D = 0.1(V_{GS} - 1)^2 \text{ mA} \quad (1)$$

(device)

$$V_{GS} = V_G - V_S = V_G - I_D R_S \quad (2)$$

MOSFET 4-resistor bias circuit analysis

 

Transistor model:

$$I_D = 0.1(V_{GS} - 1)^2$$


$$V_G = \frac{100}{50+100} 10 = 6.66$$

$$V_{GS} = V_G - I_D R_S$$

$$I_D = 0.1(V_G - I_D R_S - 1)^2$$

Lundstrom: 2019

MOSFET 4-resistor bias circuit analysis

 

$$I_D = 0.1(V_G - I_D R_S - 1)^2$$

$$10I_D = (6.66 - 2.5I_D - 1)^2$$

$$I_D^2 - 6.13I_D + 5.12 = 0$$


$$I_D = 5.14 \text{ mA or } 1.0 \text{ mA}$$

$$I_D = 1.0 \text{ mA}$$

$$V_{DS} = 5.0 \text{ V}$$

Lundstrom: 2019

Load line analysis

 


1) Device:

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$


2) Circuit:

$$V_{GS} = V_G - I_D R_S$$

Load line analysis

 

Load line analysis (without R_s)

 


Device:

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$


Circuit:

$$V_{GS} = V_G$$

Load line analysis

 

Also a good bias circuit

 

See Lecture 12

$$I_C = \frac{V_{CC} - V_{BE}}{R_C \left(1 + \frac{1}{\beta} \right) + R_B \frac{1}{\beta}}$$

$$\beta \rightarrow \infty$$

$$I_C \rightarrow \frac{V_{CC} - V_{BE}}{R_C}$$

Summary

The classic 4-resistor bias circuit for discrete transistors makes use of negative feedback to deal with variations in beta or threshold voltage.

Other bias circuits can also make use of negative feedback to stabilize the operating point against transistor variations.

Bias circuits should also be designed so that the transistor stays in the active (BJT) or saturation (MOSFET) region.

DC MOSFET Circuits

- 1) Bias circuit design
- 2) BJT bias circuits
- 3) Load line analysis
- 4) MOSFET bias circuits
- 5) Load line analysis

