

*Spring 2019 Purdue University*

## ECE 255: L17

# BJT Transistor Amplifiers

(Sedra and Smith, 7<sup>th</sup> Ed., Sec. 7.1, 7.2.2)

Mark Lundstrom  
School of ECE  
Purdue University  
West Lafayette, IN USA

Lundstrom: 2019

**PURDUE**  
UNIVERSITY

## Announcements

---


- 1) LTspice Project 2 is posted. The due date for it is Wed. Feb. 27th by 5:00PM electronically. You should find your assigned your beta value in your grade book.
- 2) HW6 will be posted today
- 3) Exam 2 in on Tuesday, March 5, 6:30-7:30 PM PHYS 112

# Outline


---

- 1) Voltage transfer characteristic (VTC)
- 2) Small signal model for BJT
- 3) Small signal analysis


# Voltage Transfer Characteristic

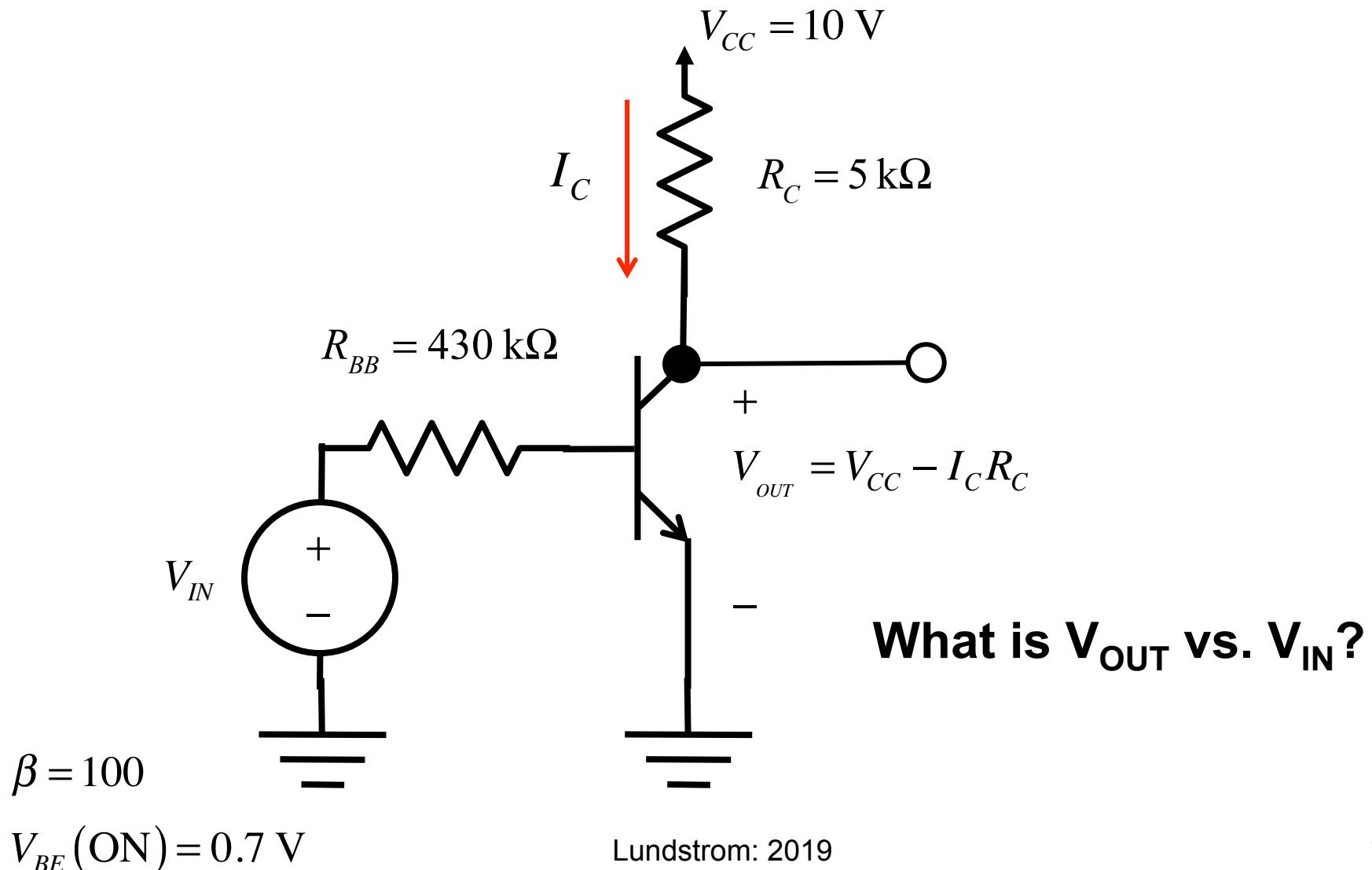


# VTC

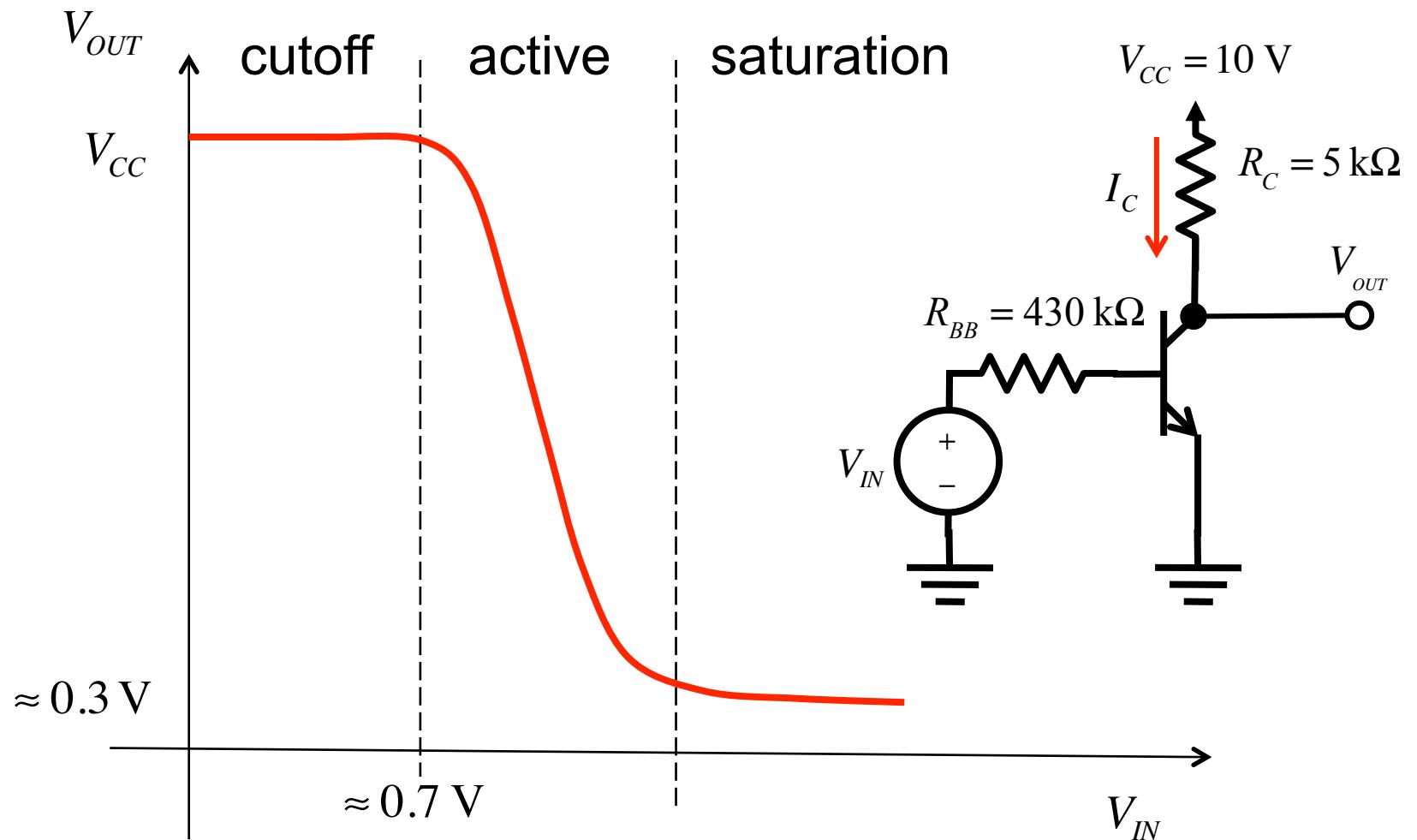


# Biasing in the active region

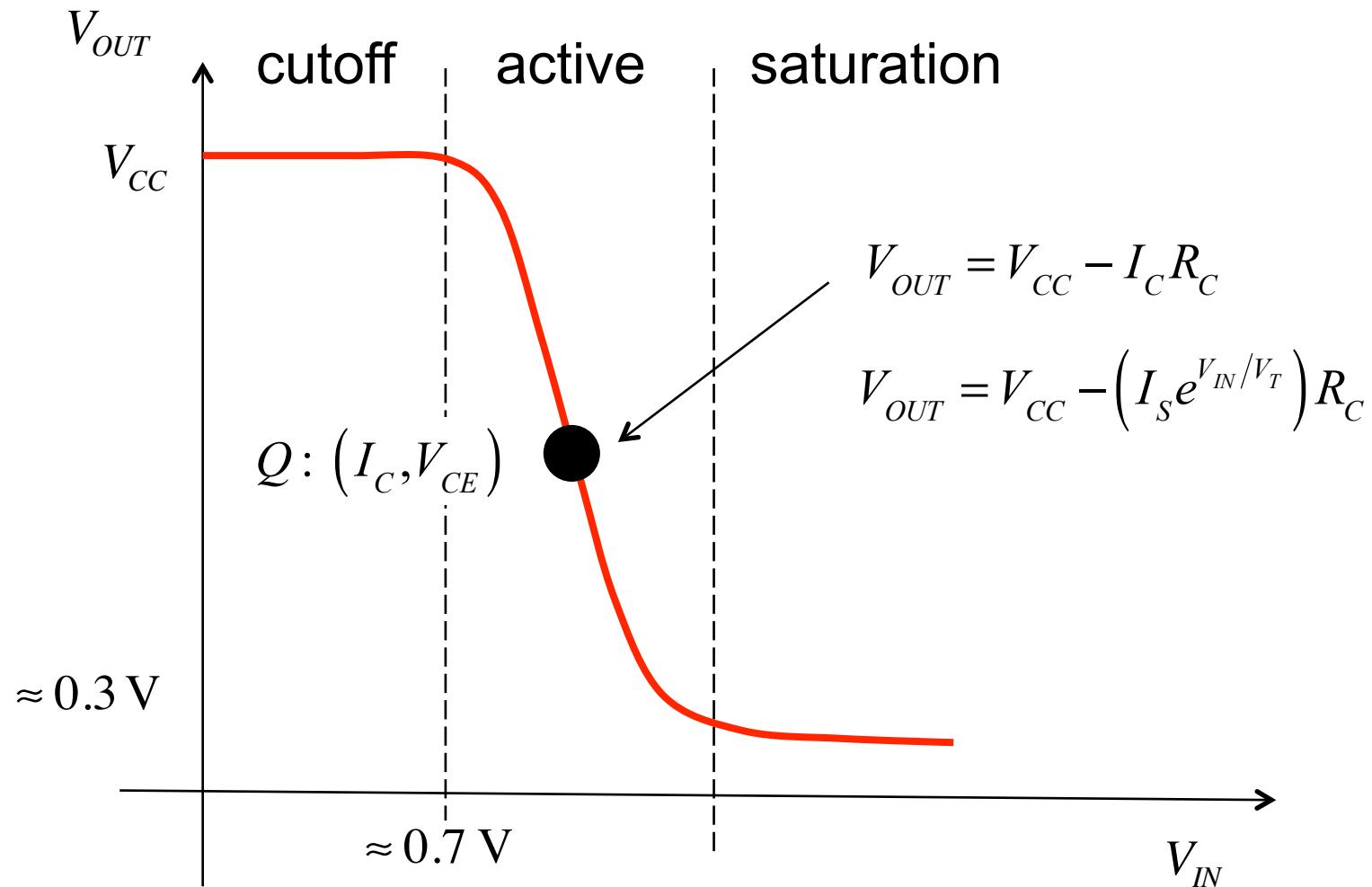

# Bias Circuit

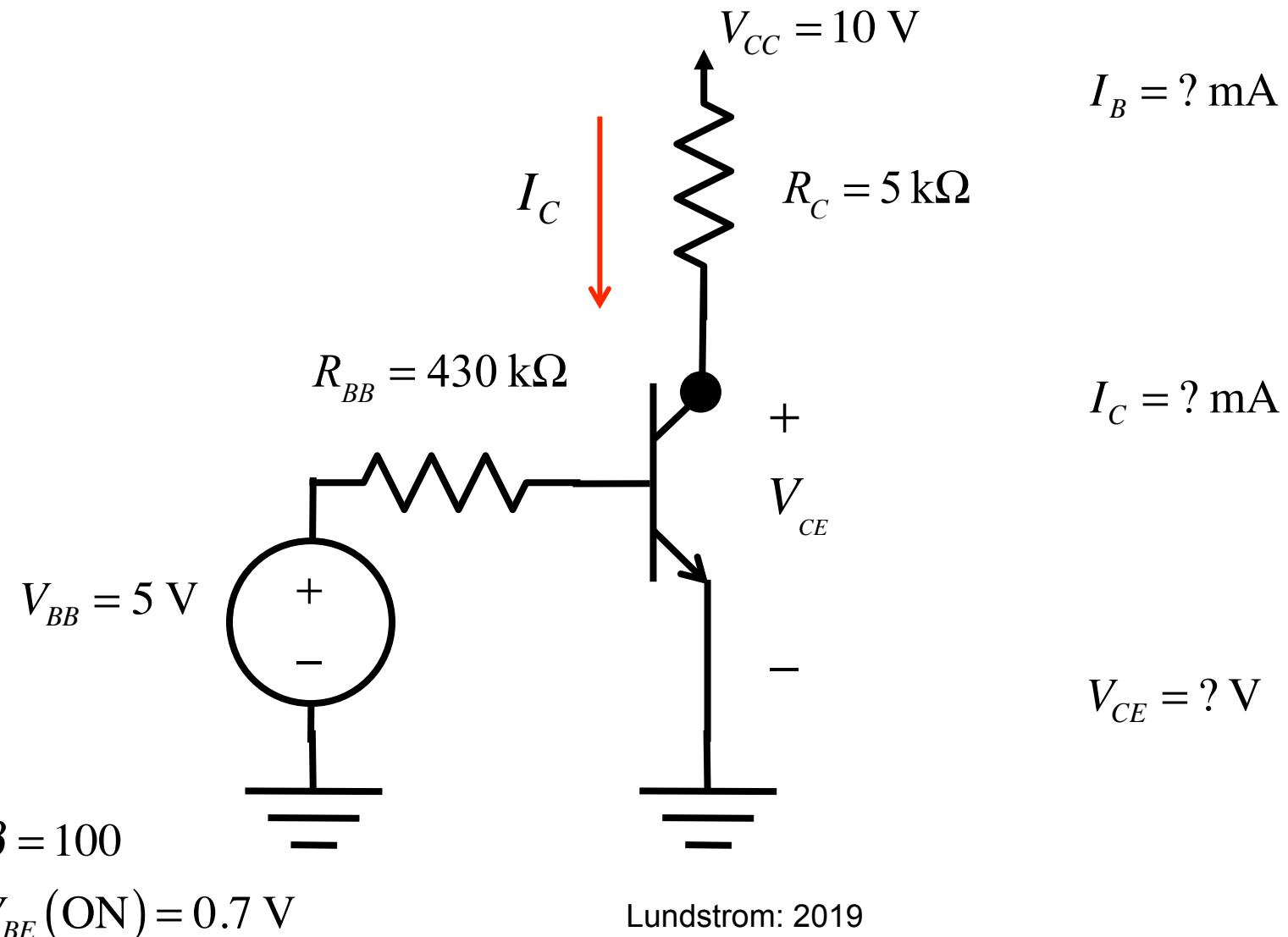


# Bias Circuit

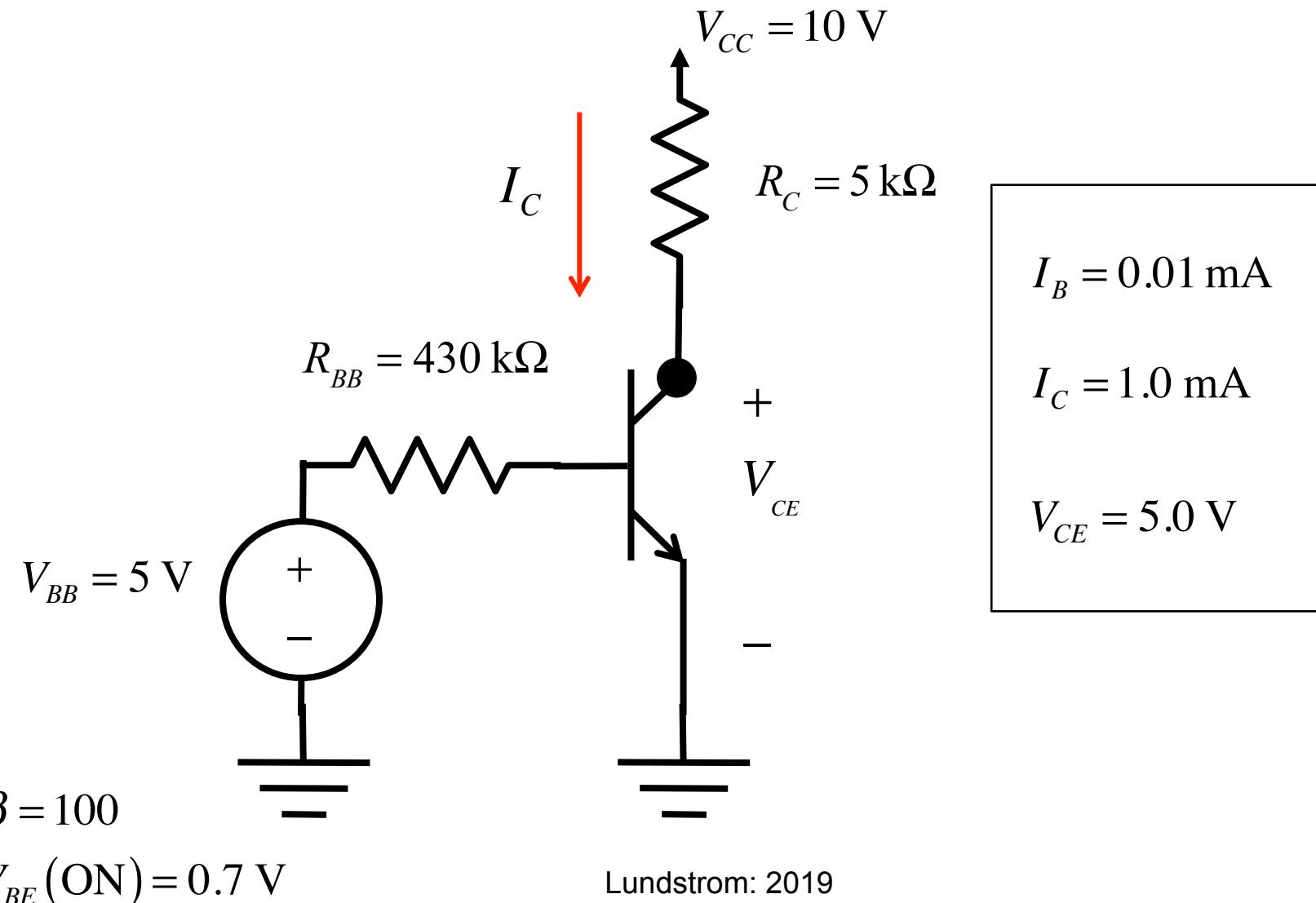


Lundstrom: 2019

# Biasing

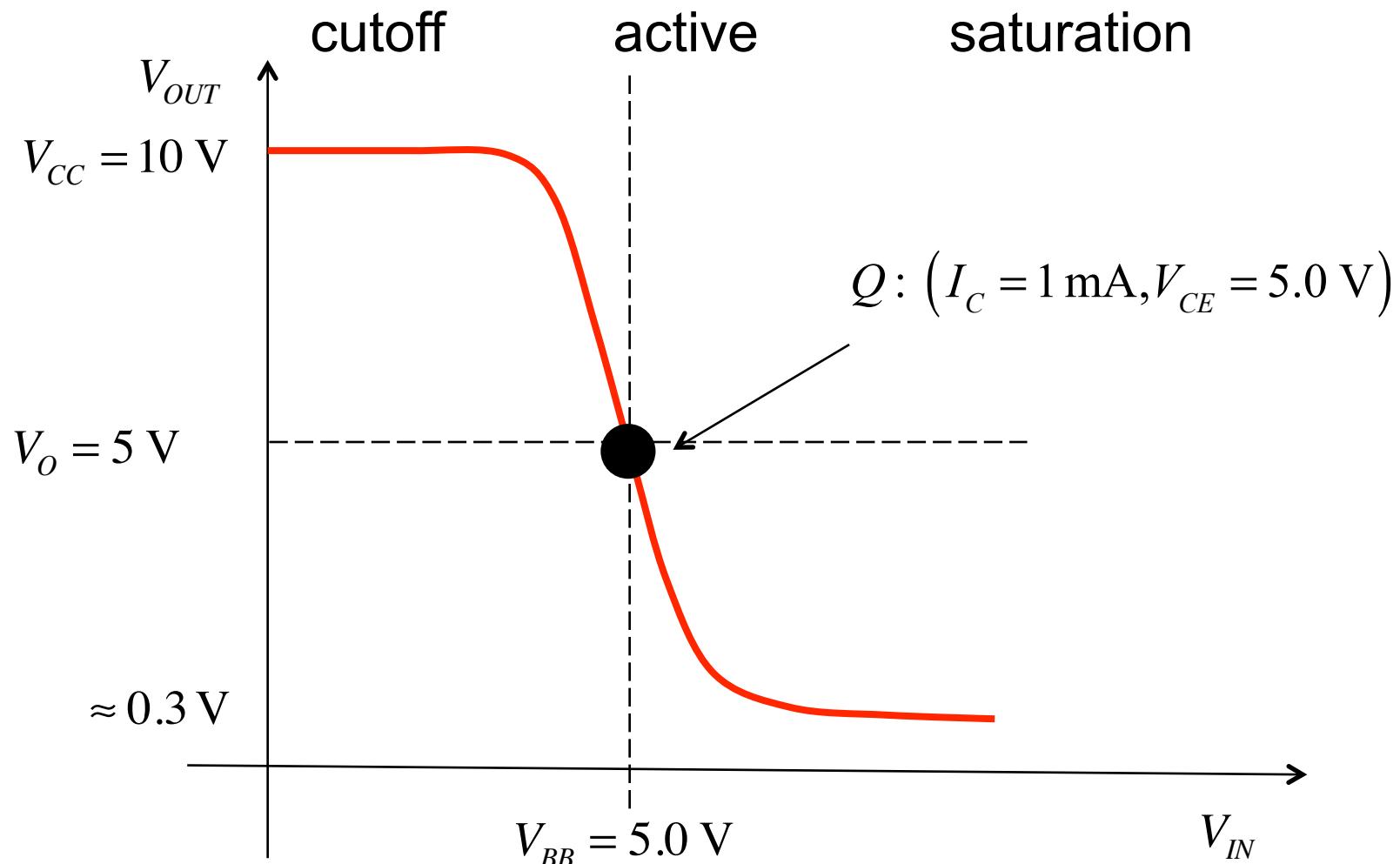


# Add ac small signal

“Common emitter amplifier”

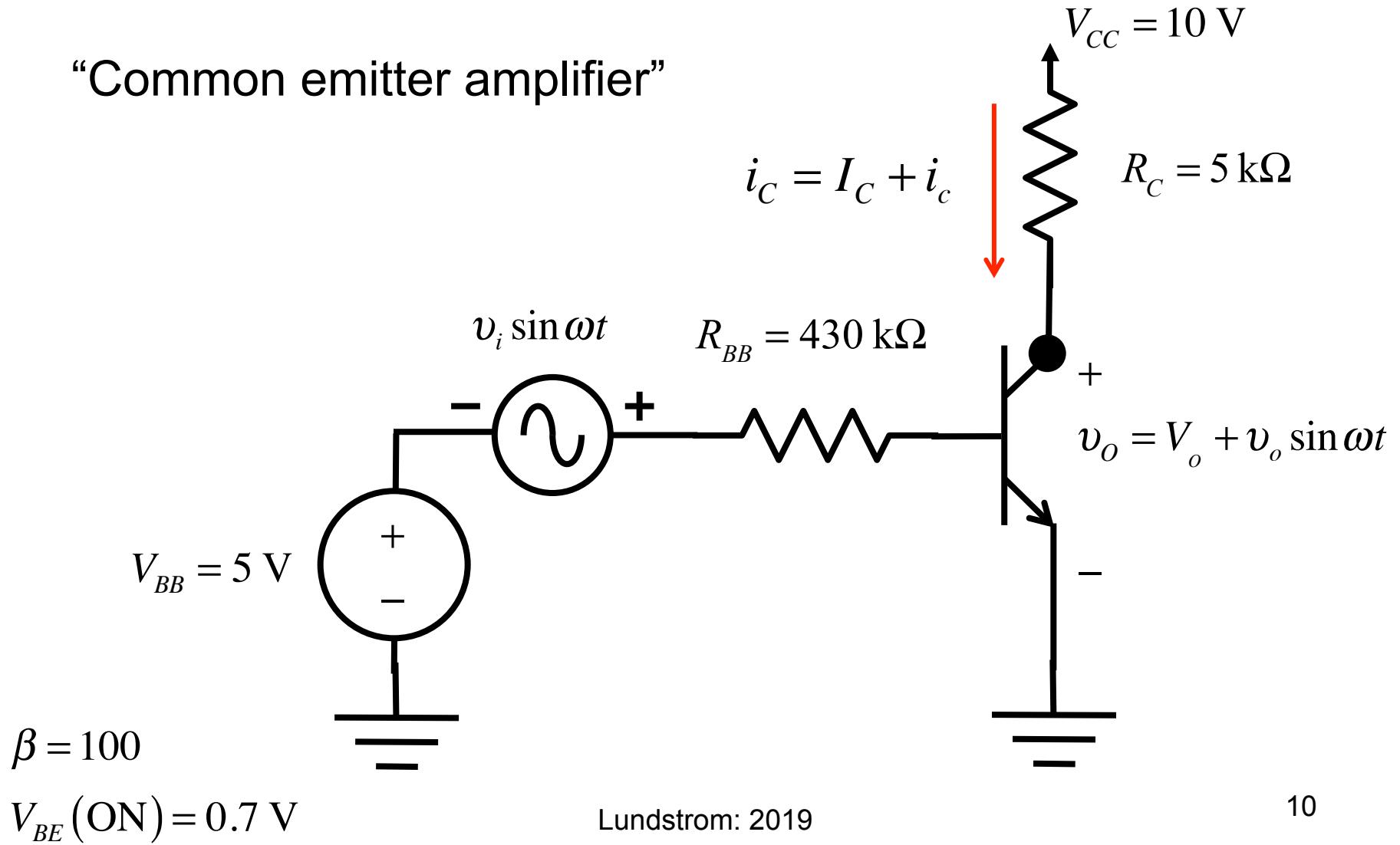


# Qualitative

---

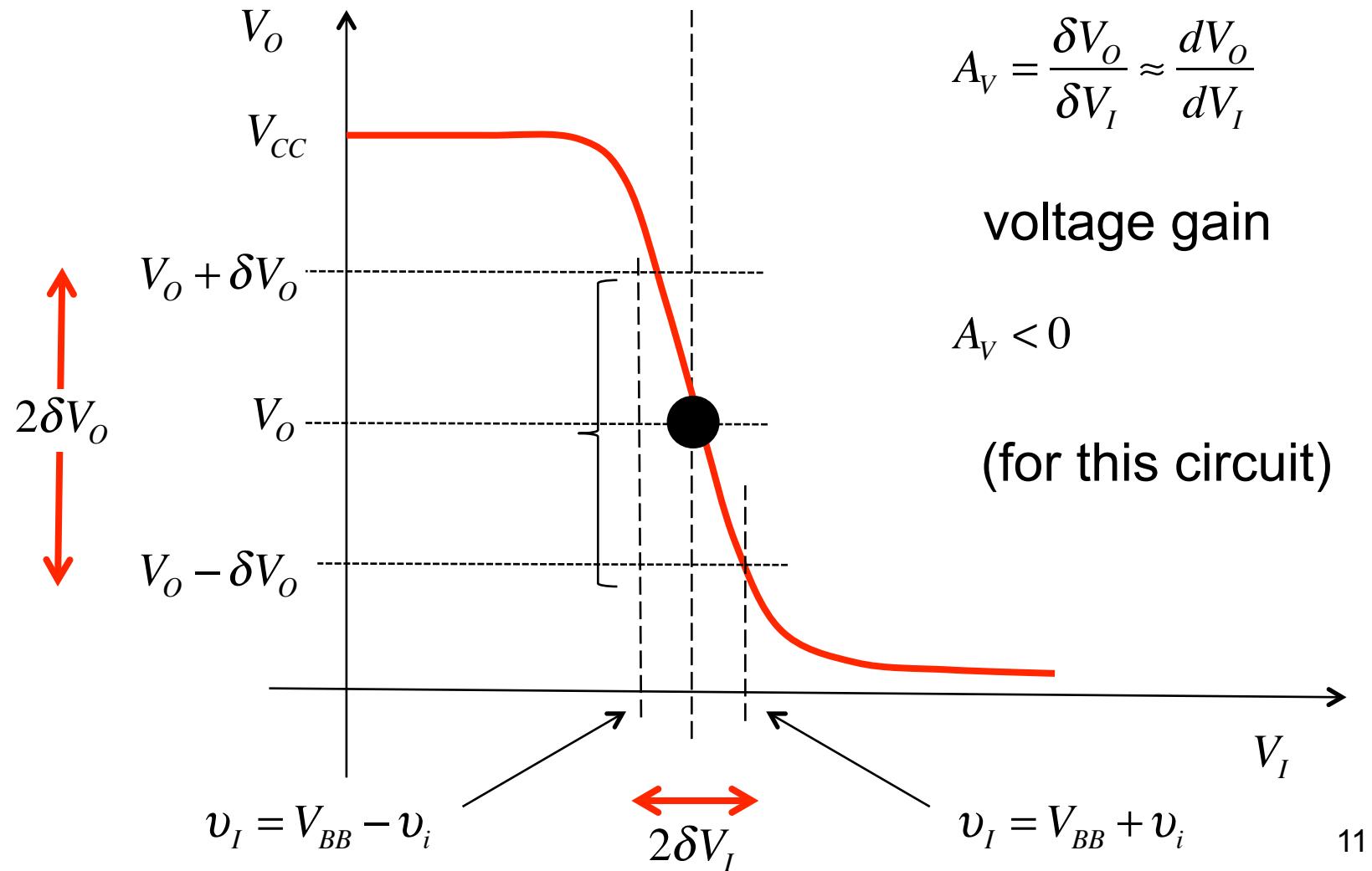

# Qualitative

---

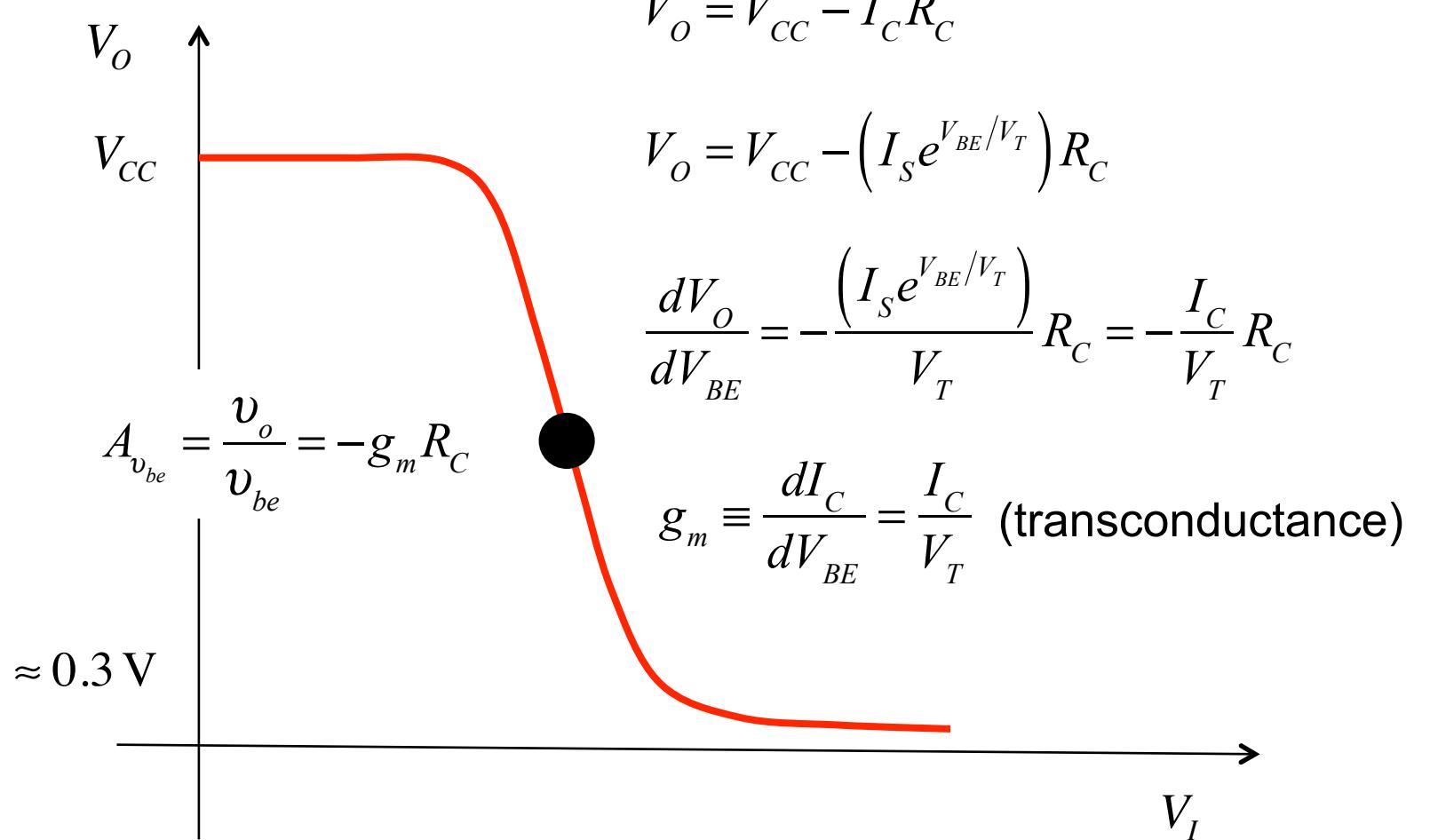

# Voltage gain of CE amplifier

$$A_{v_{be}} = \frac{v_o}{v_{be}} = -g_m R_C$$


$$A_{v_i} = \frac{v_o}{v_i} = ?$$

$$\beta = 100$$

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$i_C = I_C + i_c$$

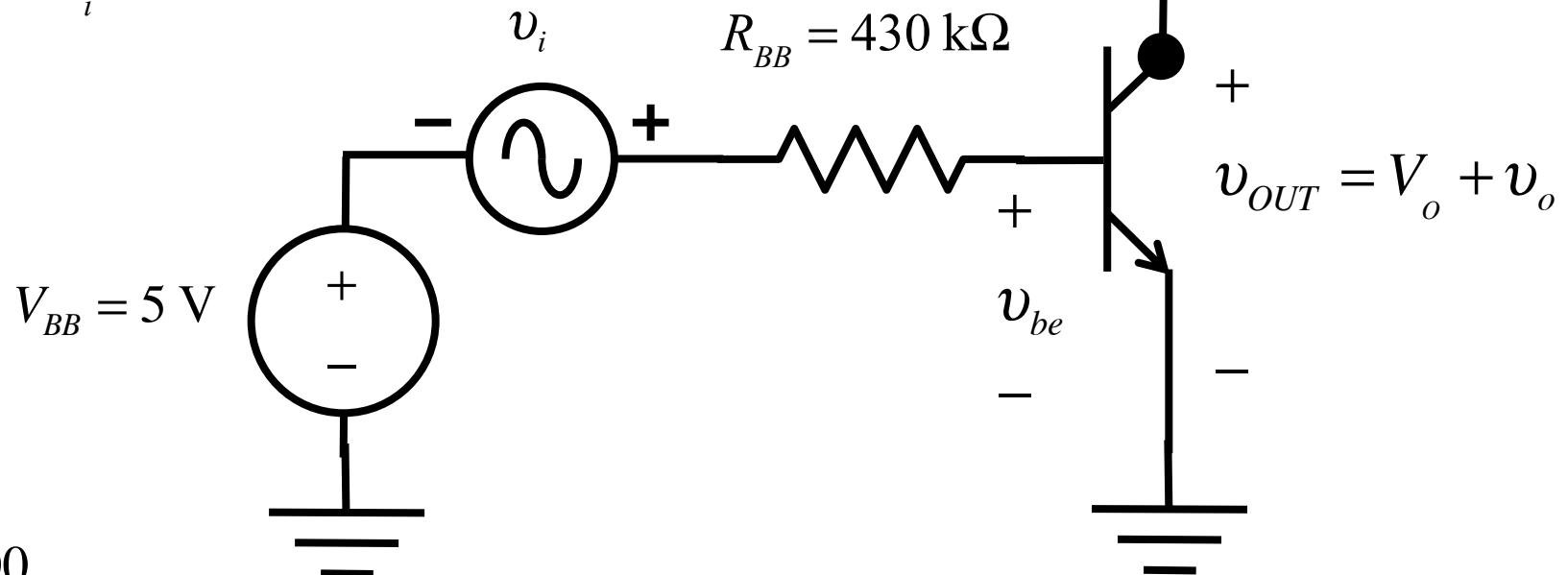
$V_{CC} = 10 \text{ V}$   
 $R_C = 5 \text{ k}\Omega$



Lundstrom: 2019

# Analysis by superposition

- 1) DC first
- 2) Then AC

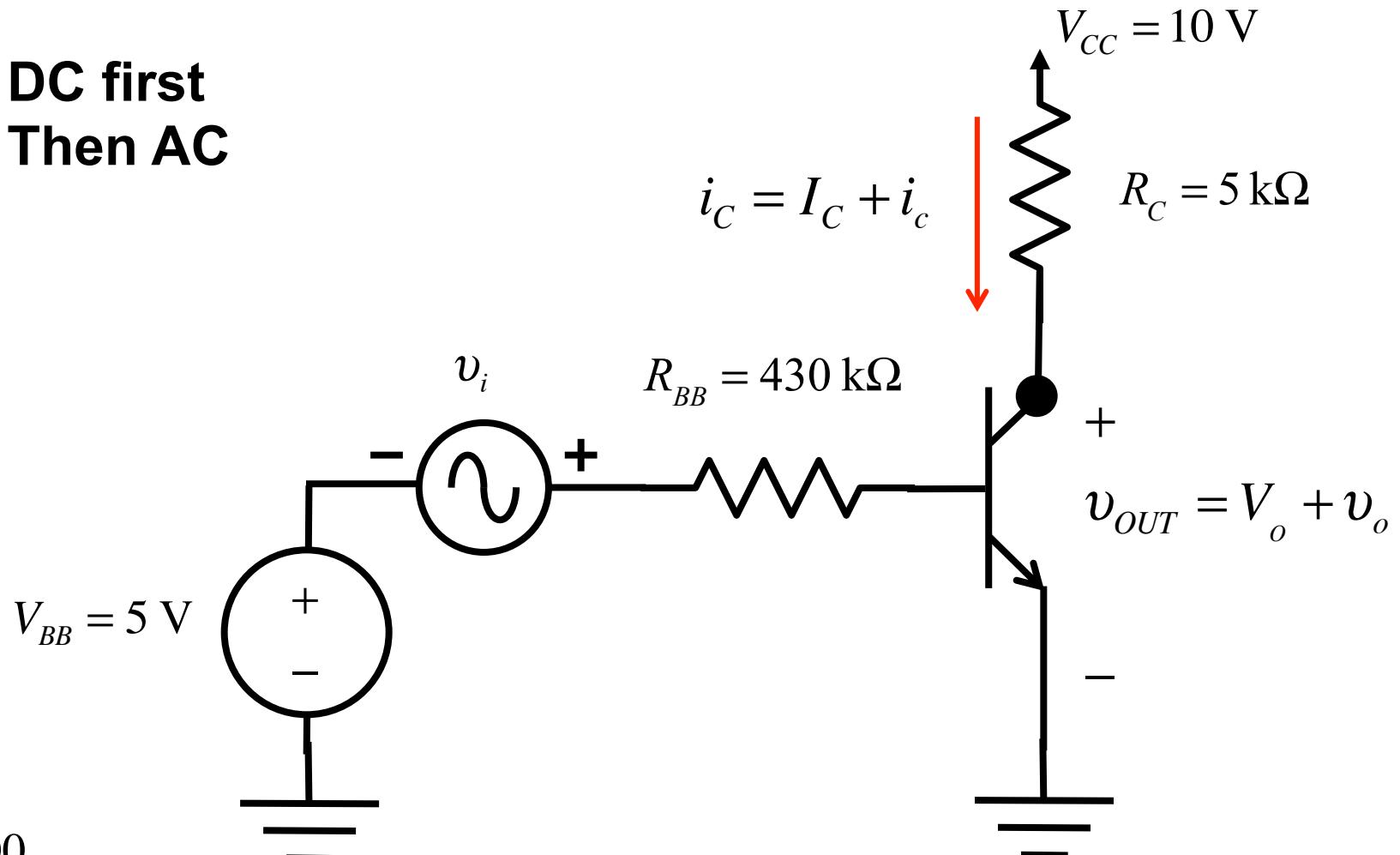


$$\beta = 100$$

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

Lundstrom: 2019


# 1) DC analysis

---

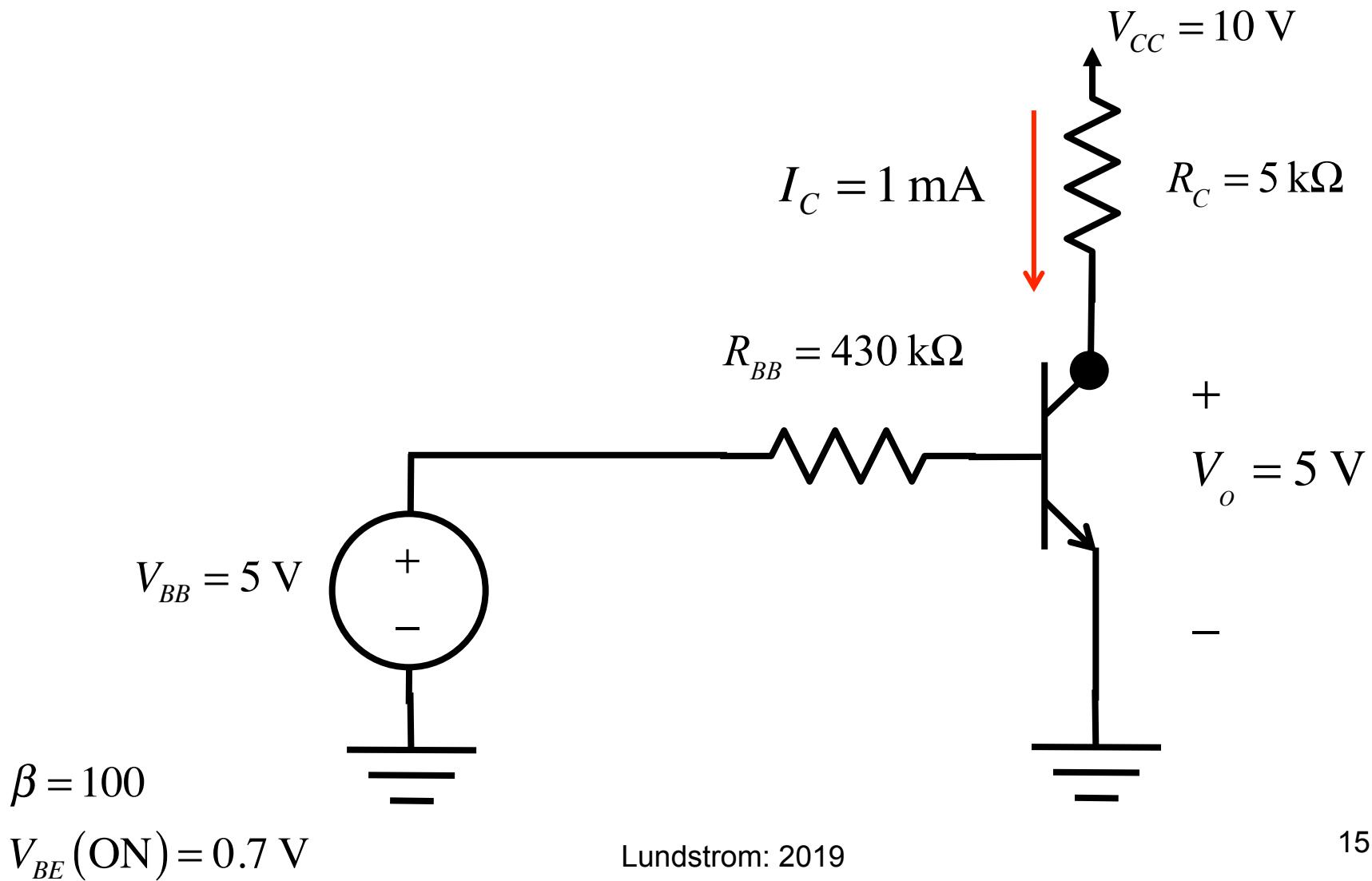


## 2) AC analysis

---

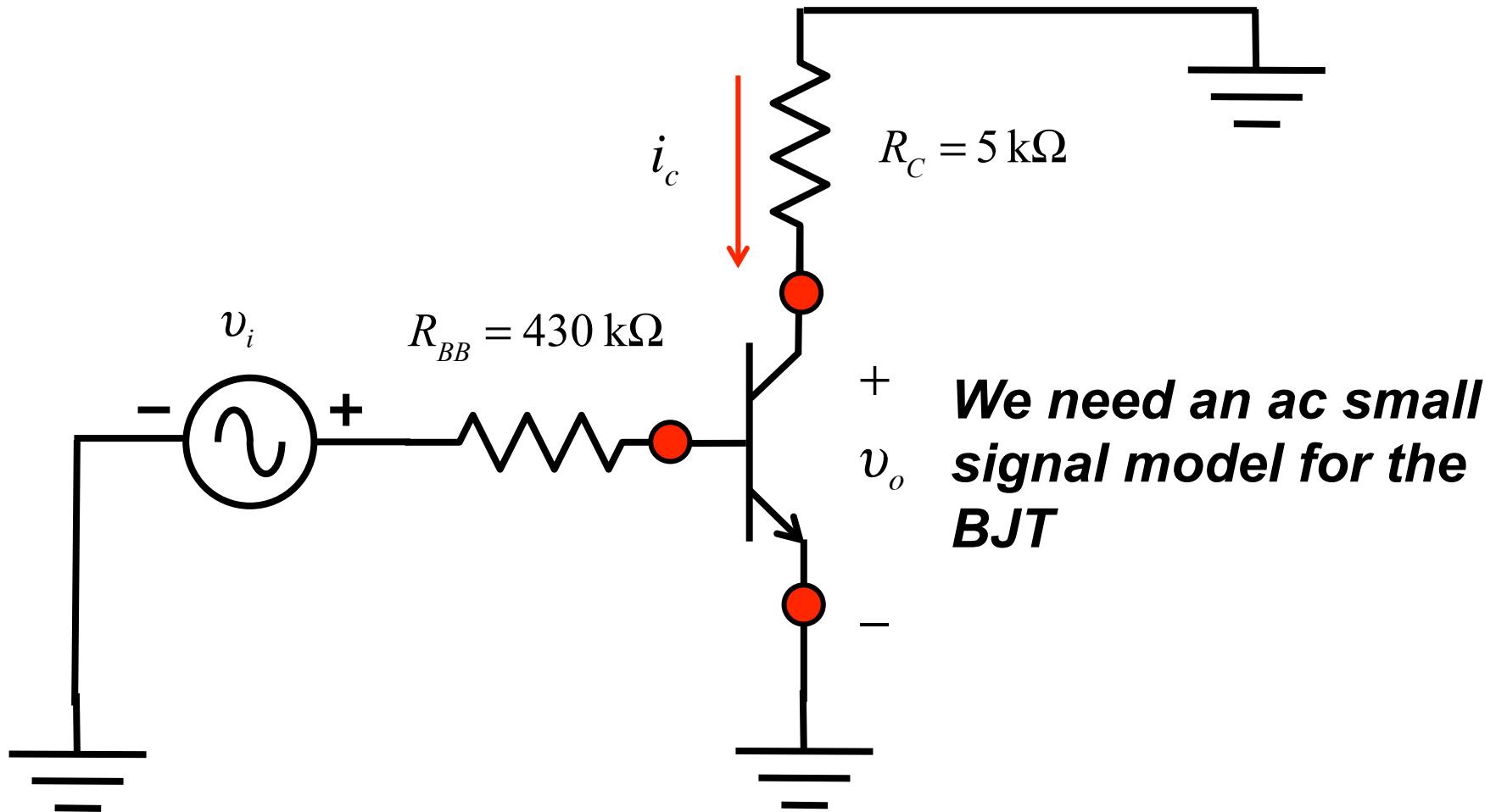


## Recall: DC currents

---

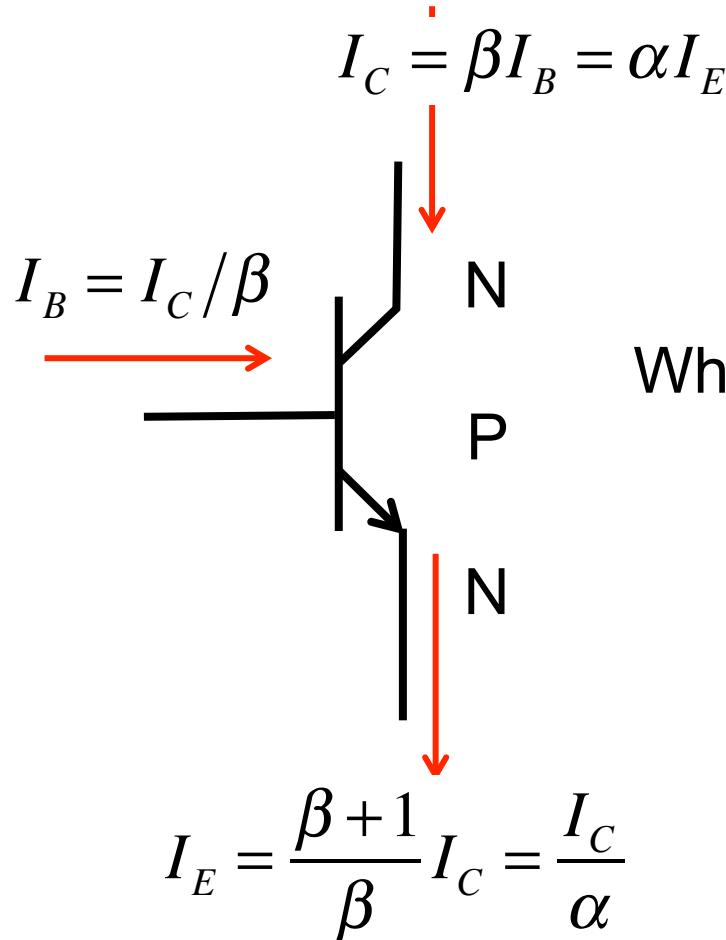


What is the a.c. small signal model?

## ac collector current

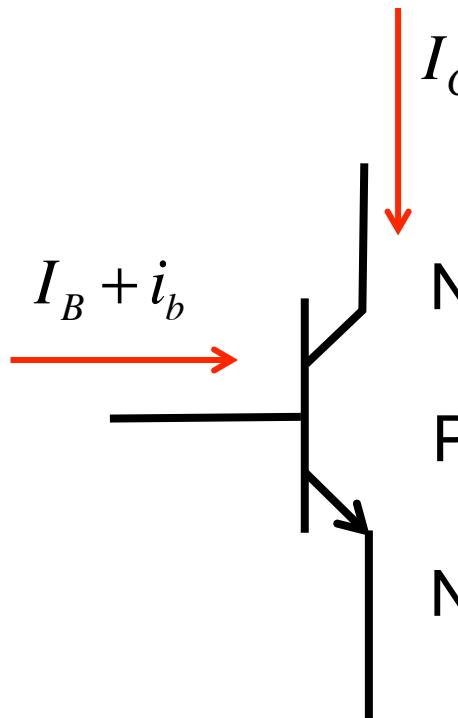
$$I_C + i_c \quad I_C = I_S e^{V_{BE}/V_T} \rightarrow I_C + i_c = I_S e^{(V_{BE} + v_{be})/V_T}$$
$$I_C + i_c = I_S e^{V_{BE}/V_T} e^{v_{be}/V_T}$$
$$I_C + i_c = I_S e^{V_{BE}/V_T} \left(1 + v_{be}/V_T\right)$$
$$i_c = I_S e^{V_{BE}/V_T} \left(v_{be}/V_T\right) = I_C \left(v_{be}/V_T\right)$$
$$i_c = \frac{I_C}{V_T} v_{be} = g_m v_{be} \quad \text{Ohm's Law}$$

## Summary: s.s. collector current

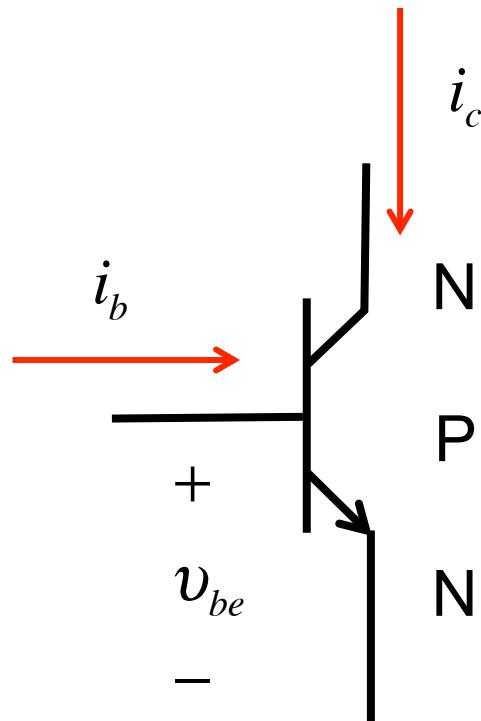


$$i_c = g_m v_{be}$$
$$g_m = \frac{I_C}{V_T}$$

“transconductance”

Note that the ac model parameter,  $g_m$ , depends on the dc bias current,  $I_C$ .

## s.s. base current

---

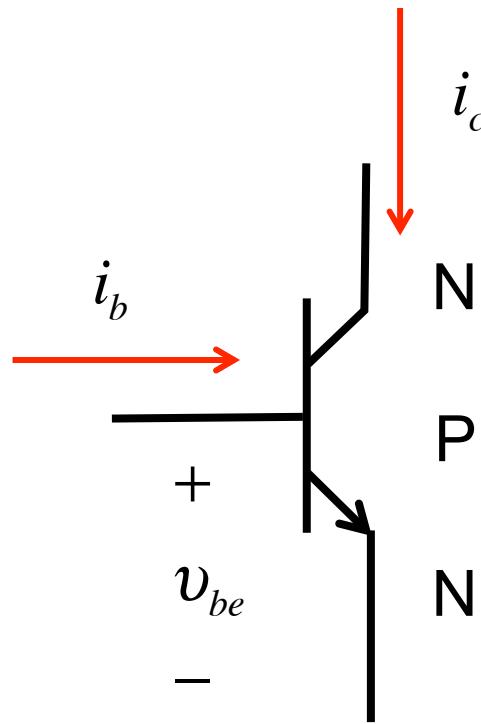

$$i_b = \frac{i_c}{\beta} = \frac{g_m}{\beta} v_{be} = \frac{v_{be}}{\beta/g_m} = \frac{v_{be}}{r_\pi}$$

$$i_b = \frac{v_{be}}{r_\pi}$$


$$g_m r_\pi = \beta$$

$$i_c = g_m v_{be}$$

$$g_m = \frac{I_c}{V_T}$$


Lundstrom: 2019

## s.s. eqv. circuit model: $g_m$ form

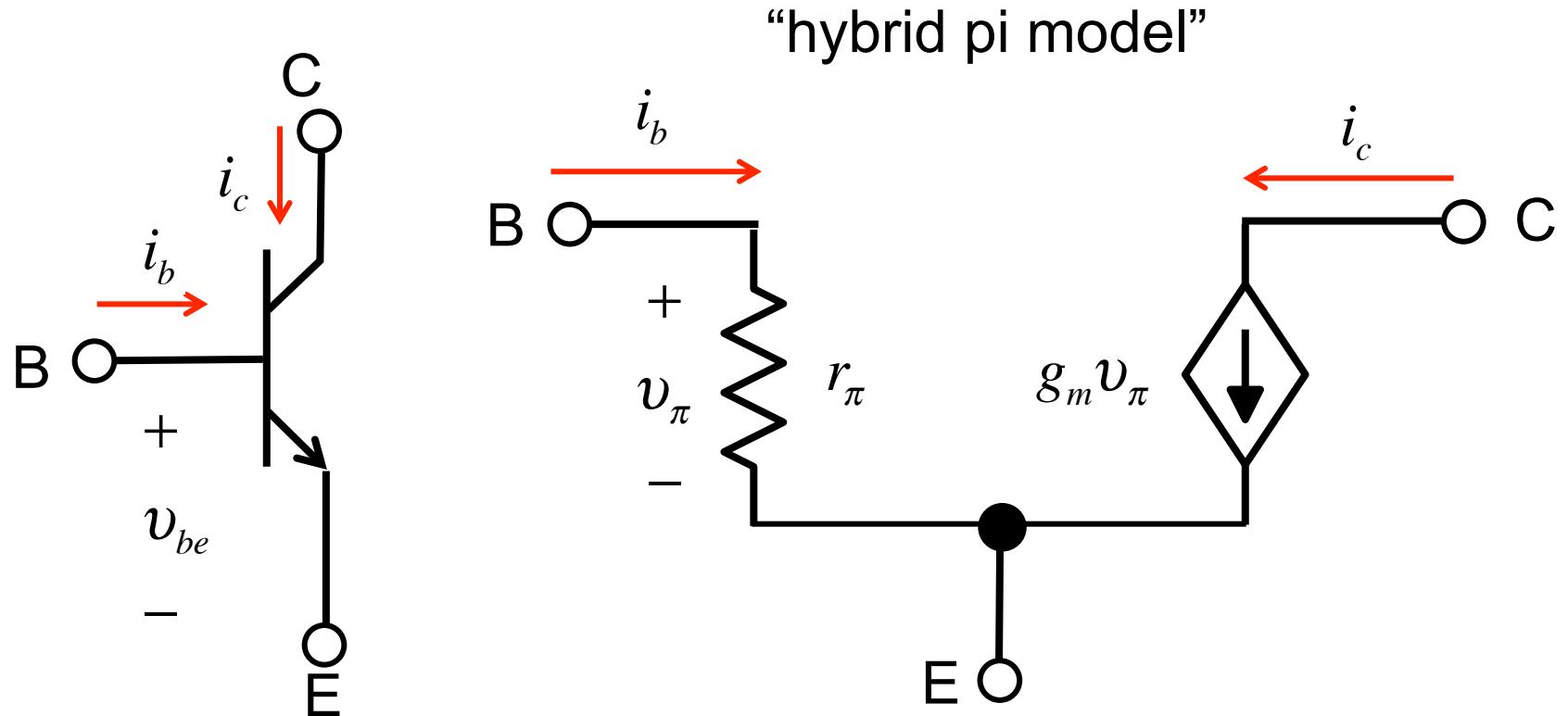

$$g_m = I_C/V_T \quad g_m r_\pi = \beta$$

## s.s. eqv. circuit model: beta form

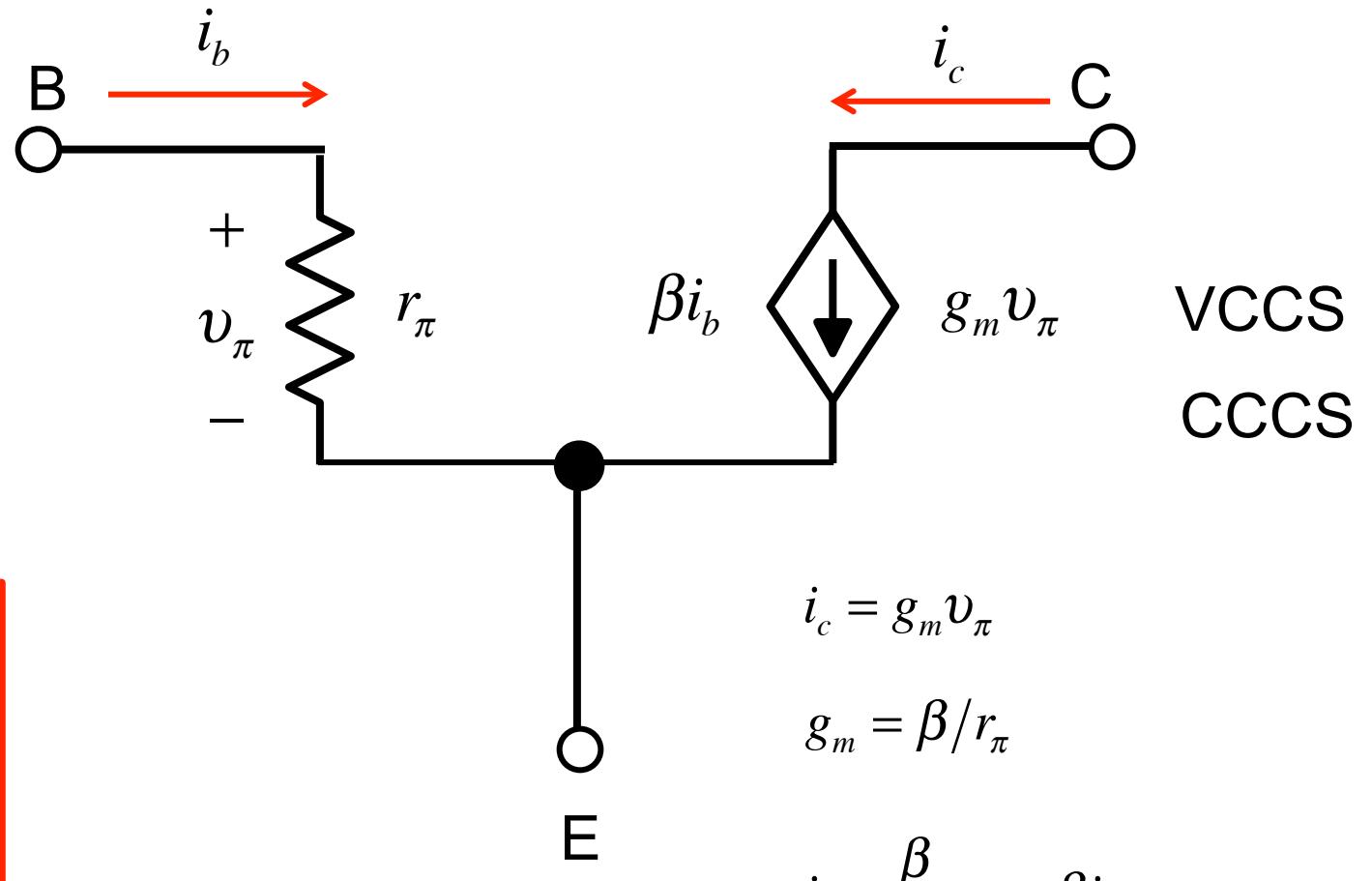


$$g_m = \frac{I_C}{V_T}$$


$$g_m r_\pi = \beta$$

Lundstrom: 2019
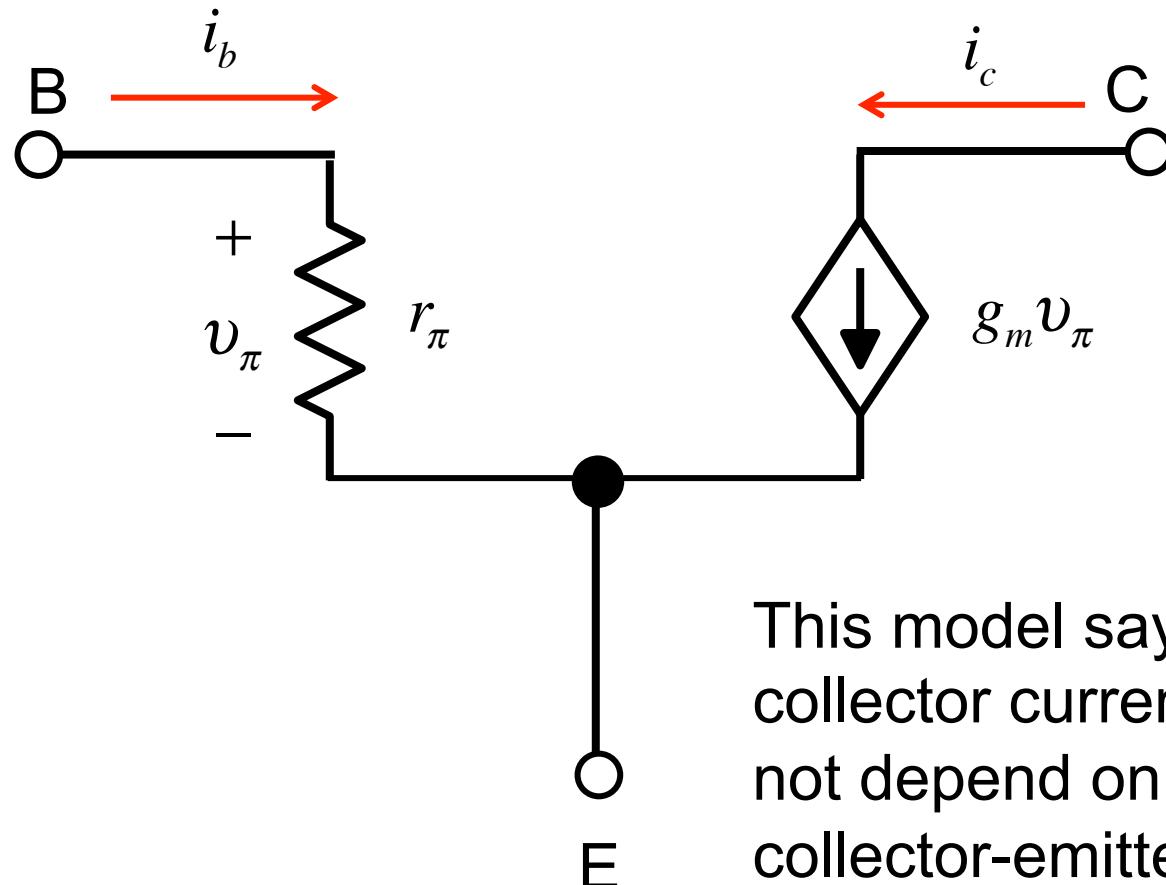
## s.s. eqv. circuit model: $v_{ce}$ dependence



# Output resistance

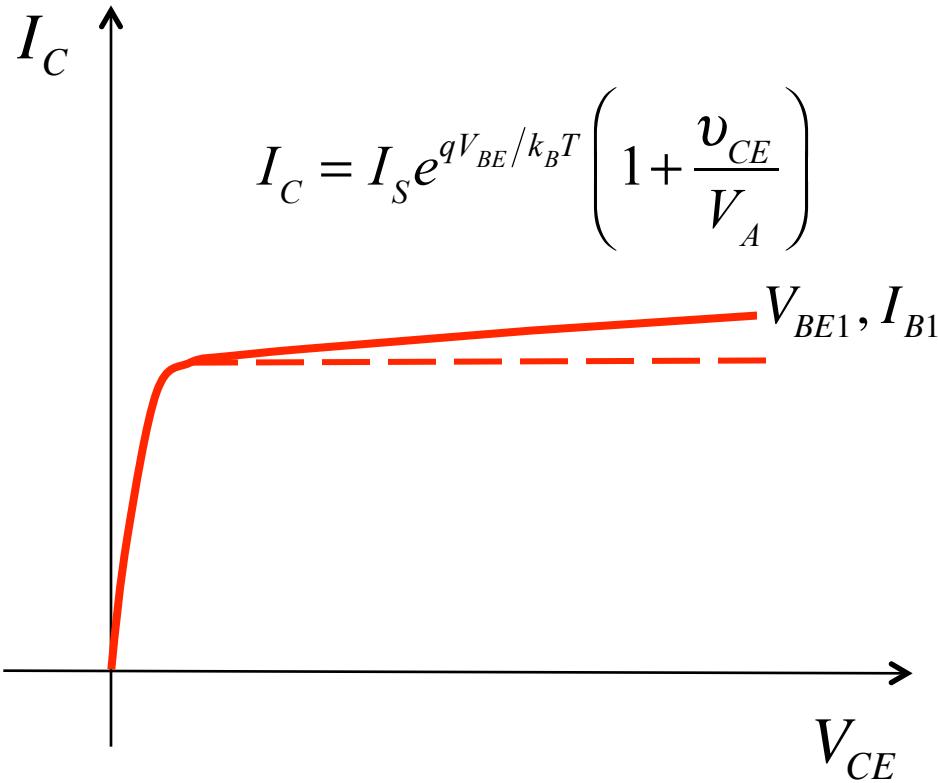

$$\frac{dI_C}{dV_{CE}} = I_S e^{qV_{BE}/k_B T} \left( \frac{1}{V_A} \right) = \frac{I'_C}{V_A}$$


$$\frac{dI_C}{dV_{CE}} \approx \frac{i_c}{v_{ce}}$$

$$i_c = \frac{v_{ce}}{r_0}$$


$$r_o \approx \frac{V_A}{I_C}$$

$V_A$  = “Early Voltage”


# Hybrid pi model

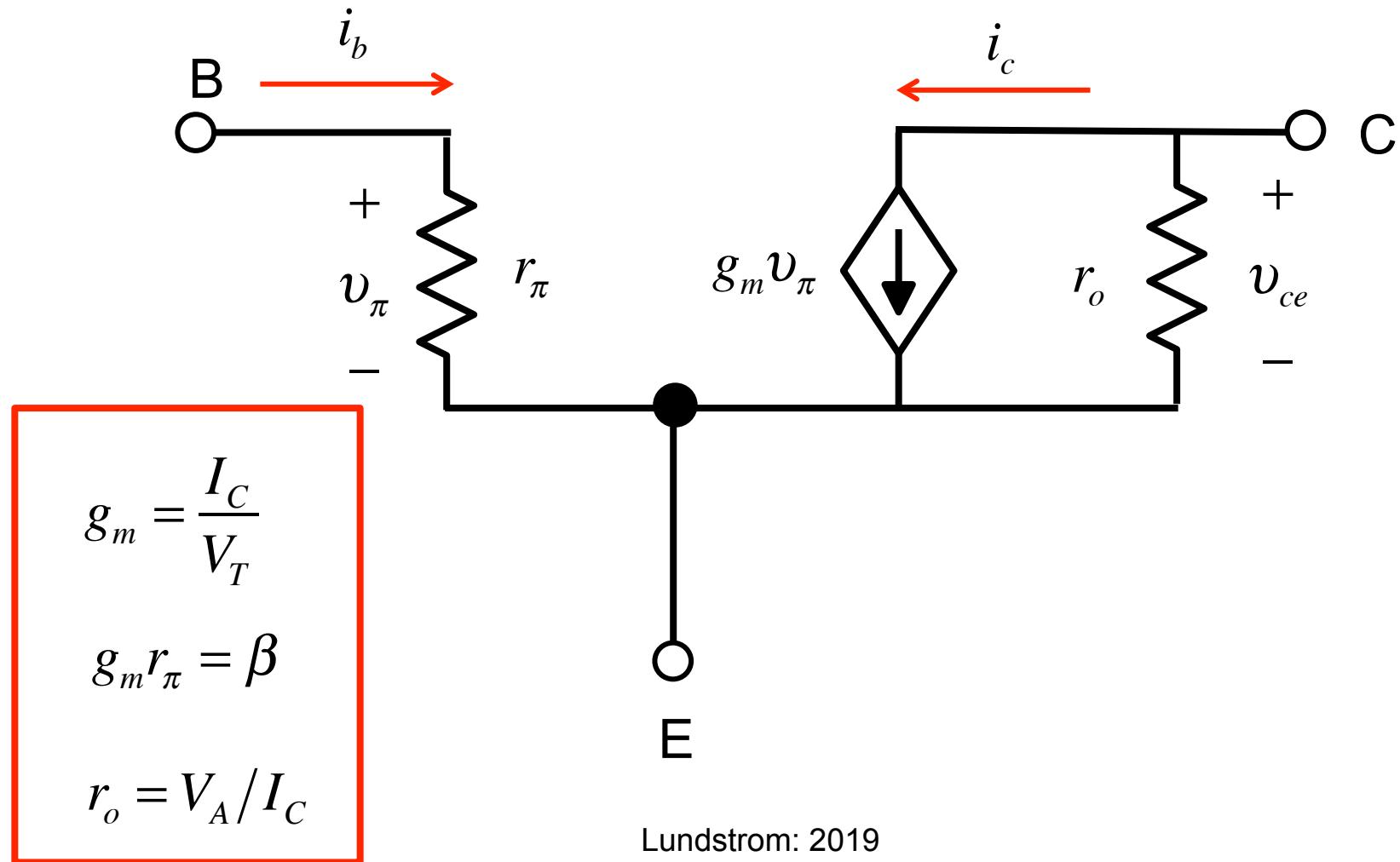


## Small signal circuit

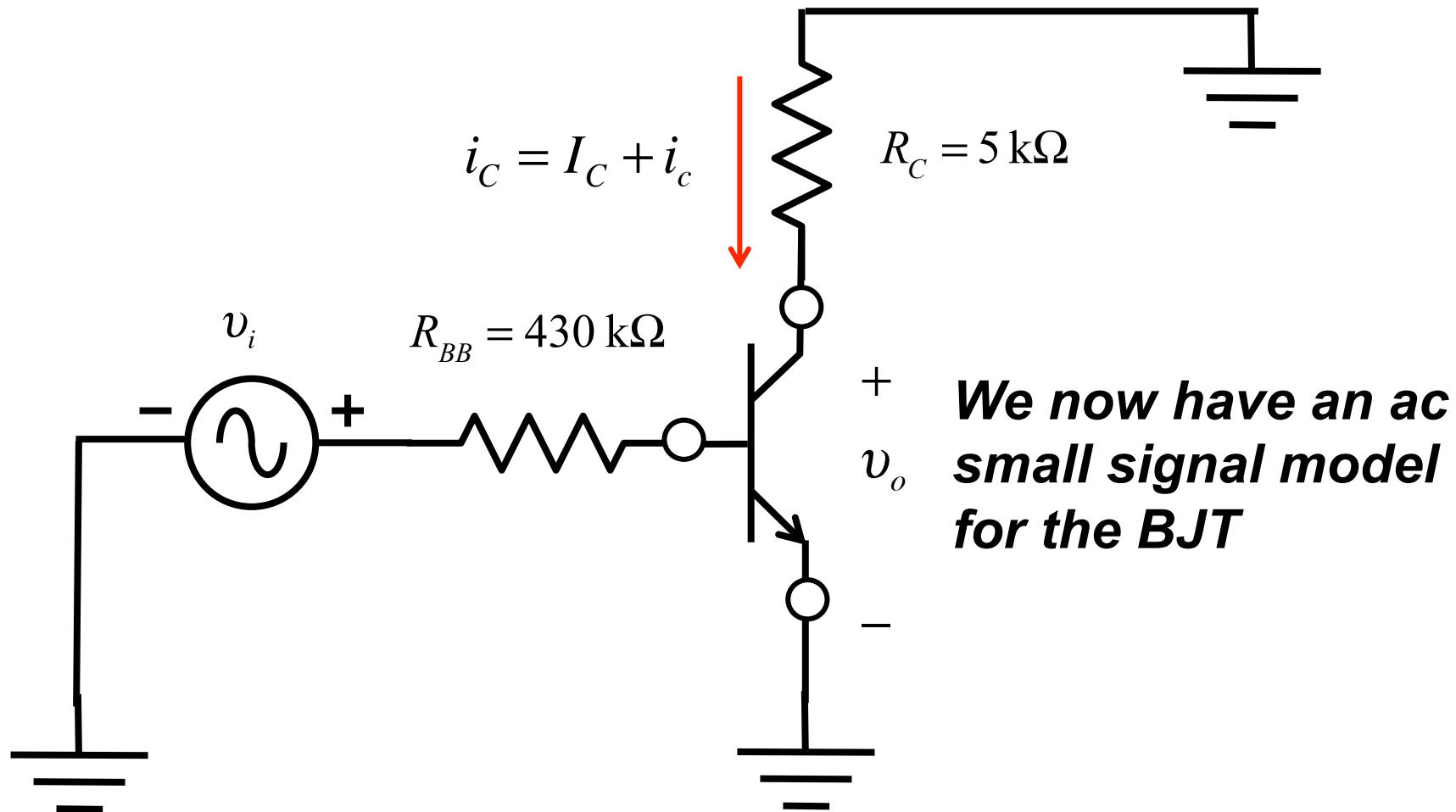


# Simple s.s. model

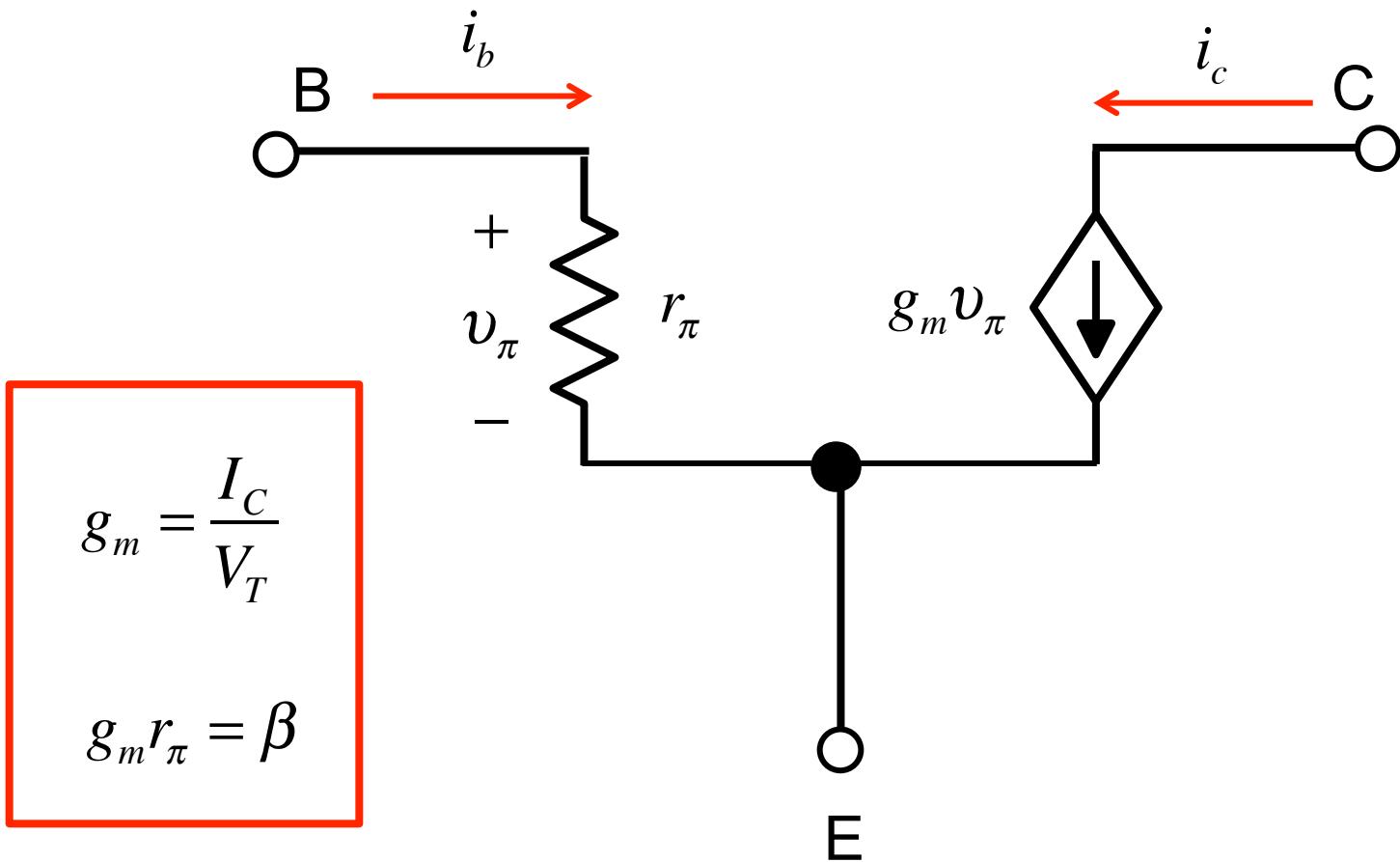

## ac analysis

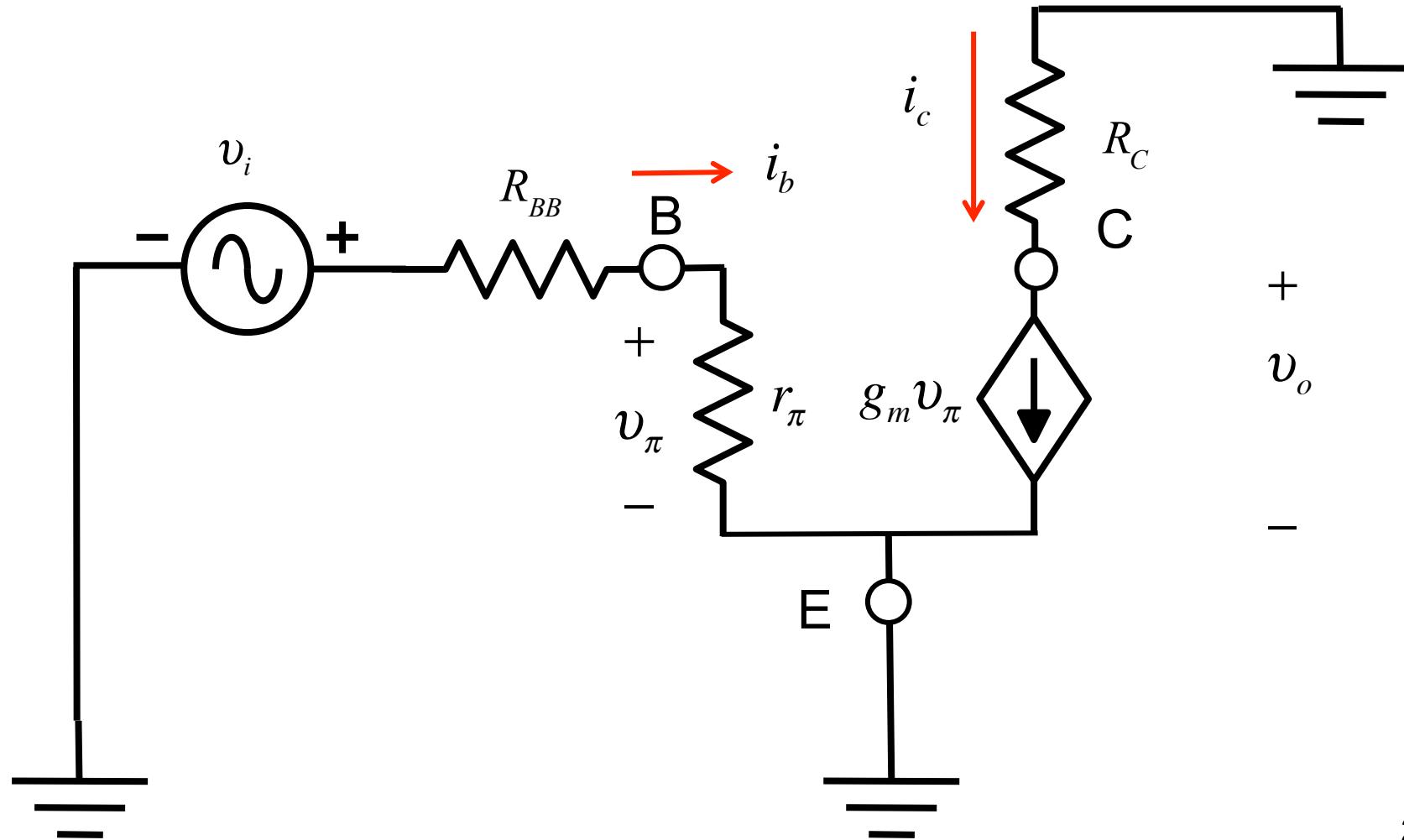

## Same circuit

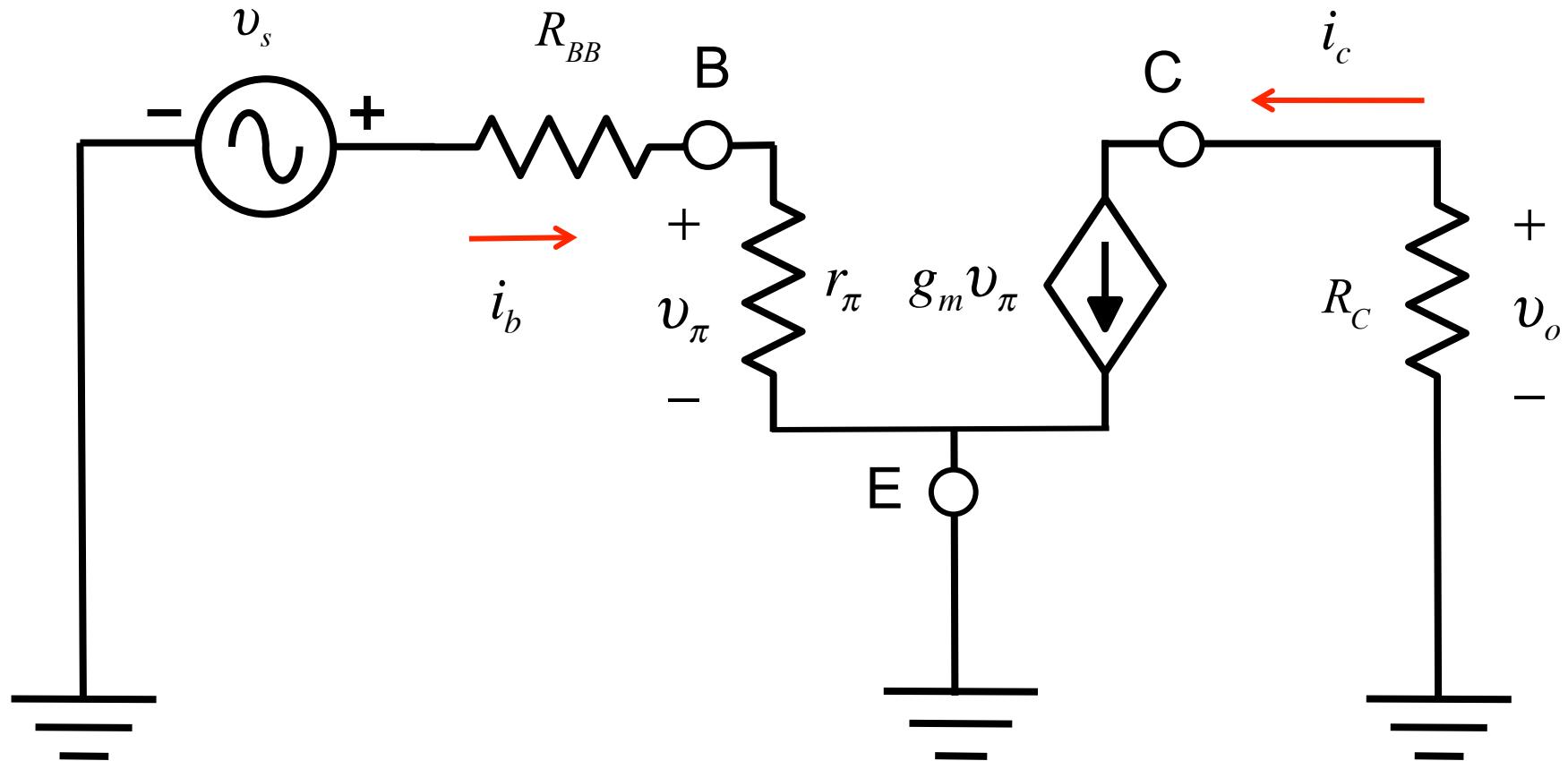

## ac analysis

$$v_o = -g_m v_\pi R_C$$

$$v_\pi = \frac{r_\pi}{r_\pi + R_{BB}} v_s$$

$$v_o = -\left( \frac{r_\pi}{r_\pi + R_{BB}} \right) g_m R_C v_s$$

$$\frac{v_o}{v_s} = A_{v_s} = -\left( \frac{r_\pi}{r_\pi + R_{BB}} \right) g_m R_C$$

$$\beta = 100$$

$$R_{BB} = 430 \text{ k}\Omega$$

$$I_C = 1 \text{ mA} \quad R_C = 5 \text{ k}\Omega$$


$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{0.026 \text{ V}} = 38.5 \text{ mS}$$

$$g_m r_\pi = \beta$$


$$r_\pi = \beta / g_m = 100 / 0.039 = 2.6 \text{ k}\Omega$$

$$A_{v_s} = -1.2$$

# Hybrid pi model with output resistance

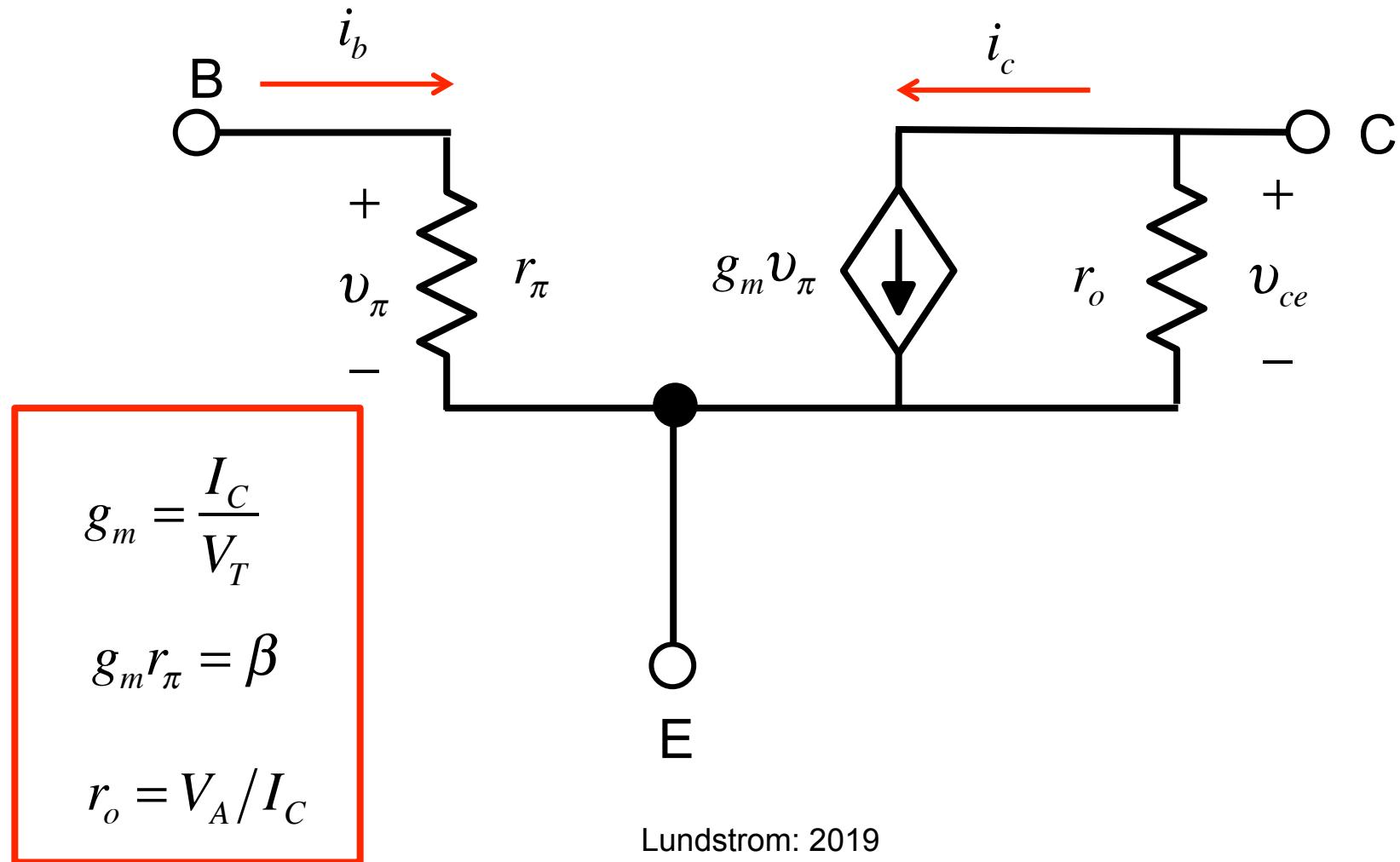


# Circuit with output resistance

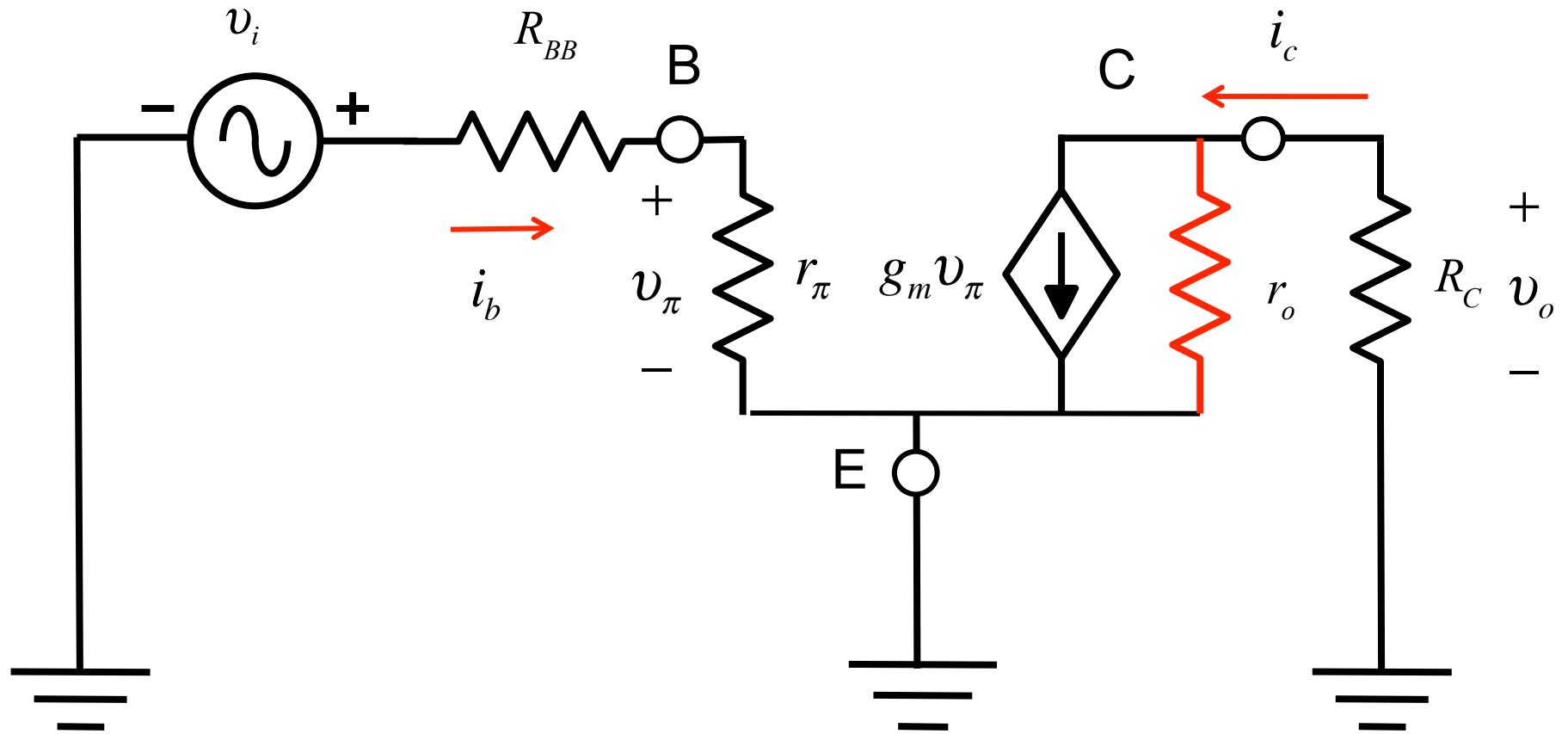

# Transistor parameters

---

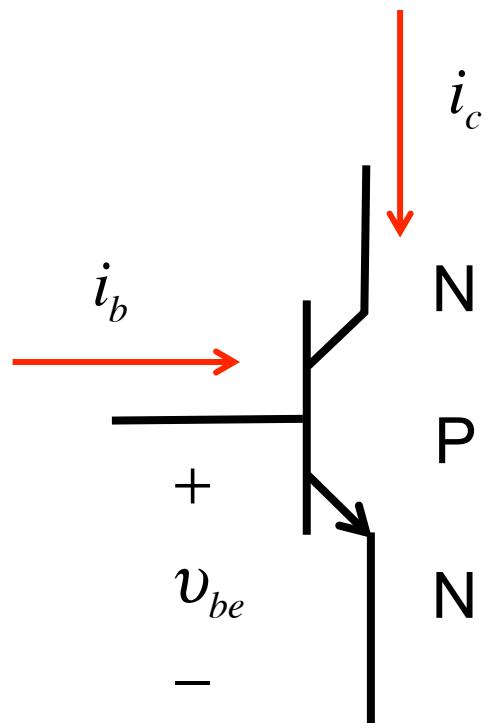

$$\beta = 100$$

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_A = 100 \text{ V}$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

## 2) AC analysis with output resistance

---


$$\frac{v_o}{v_i} = A = -\left( \frac{r_\pi}{r_\pi + R_{BB}} \right) g_m R_C \quad (\text{without } r_o)$$

$$\frac{v_o}{v_i} = A = -\left( \frac{r_\pi}{r_\pi + R_{BB}} \right) g_m R_C \parallel r_0 \quad (\text{with } r_o)$$

$$5 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 4.76 \text{ k}\Omega$$

$$A_v = -1.2 \rightarrow A_v = -1.1$$

# Hybrid pi model of BJT

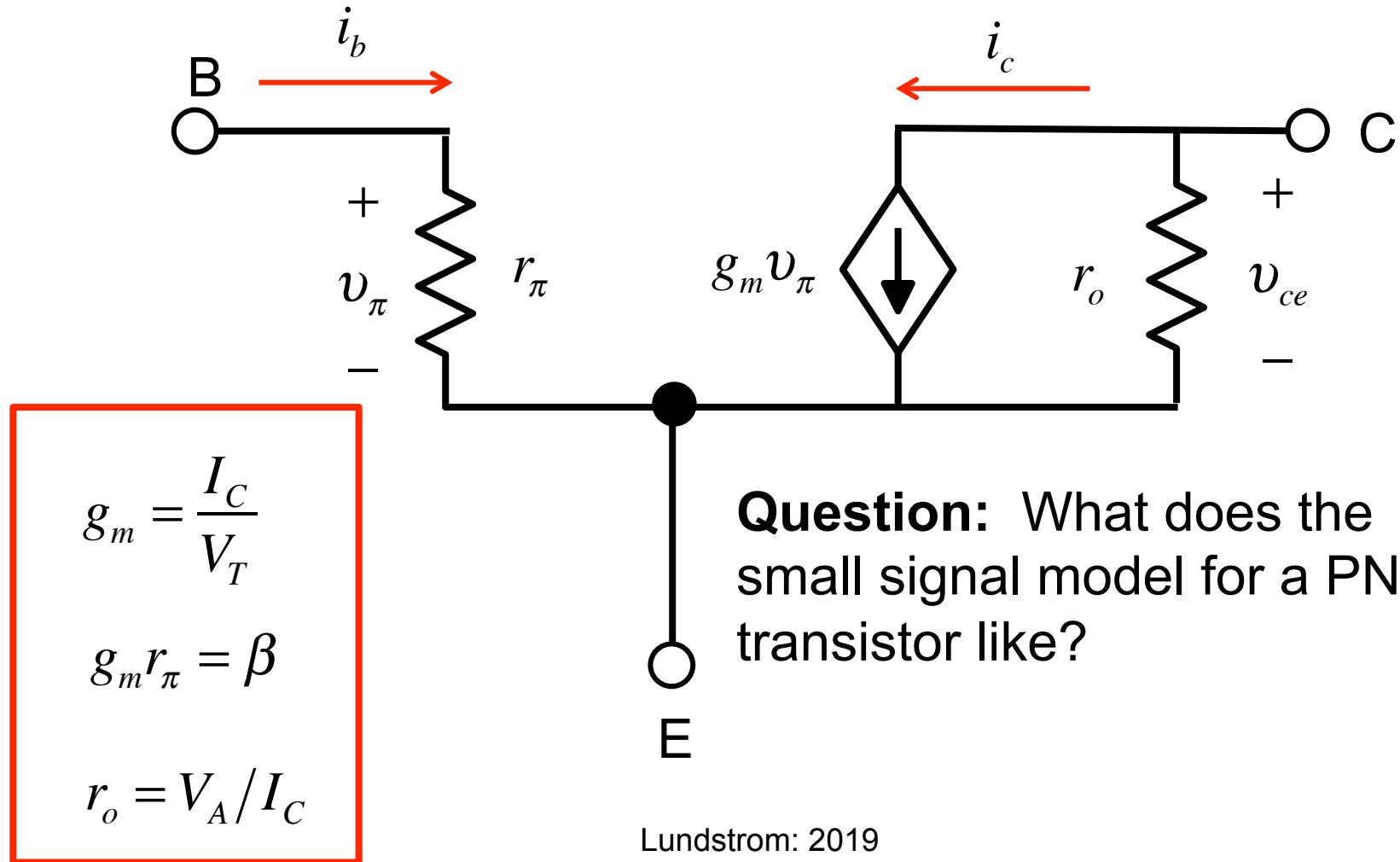

# Summary

---

The DC bias circuit places the operating point in the portion of the Voltage Transfer Characteristics where the output voltage changes rapidly with input voltage.

The small signal model of a BJT consists of two resistors and one voltage-controlled current source. The values of the ac model parameters are determined by the dc bias current.

Circuit analysis consists of two steps: 1) dc analysis to determine the OP, and 2) ac small signal analysis using the ac circuit model.

# Transistor Amplifiers

---

- 1) Voltage transfer characteristic (VTC)
- 2) Small signal model for BJT
- 3) Small signal analysis

