

Spring 2019 Purdue University

ECE 255: L18

MOS Transistor Amplifiers

(Sedra and Smith, 7th Ed., Sec. 7.1, 7.2.1)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA



Lundstrom: 2019

PURDUE
UNIVERSITY

Announcements

- 1) LTspice Project 2 is posted. The due date for it is Wed. Feb. 27th by 5:00PM electronically. You should find your assigned your beta value in your grade book.
- 2) HW6 will be posted today
- 3) Exam 2 in on Tuesday, March 5, 6:30-7:30 PM PHYS 112


Hybrid pi model for NPN

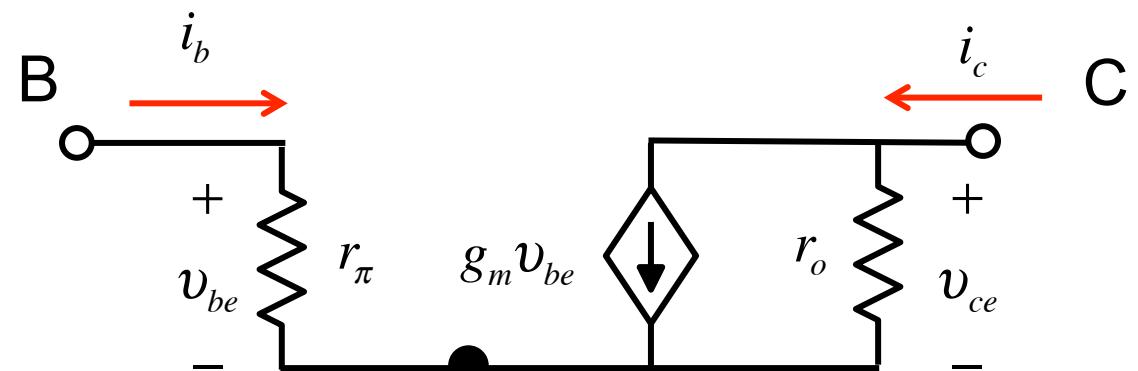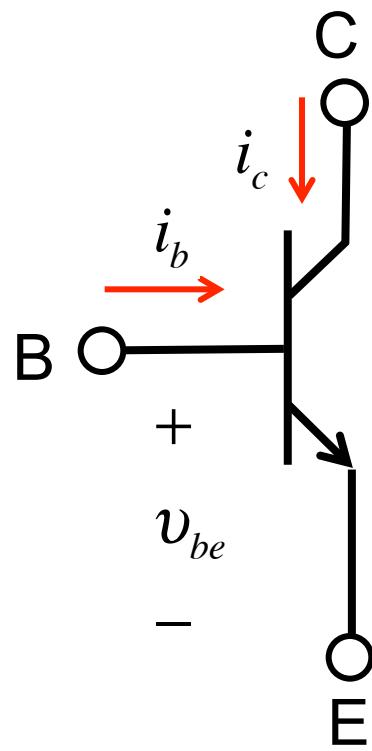



$$\boxed{\begin{aligned} g_m &= I_C / V_T \\ g_m r_\pi &= \beta \\ r_o &= V_A / I_C \end{aligned}}$$

Lundstrom: 2019

Hybrid pi model for PNP?


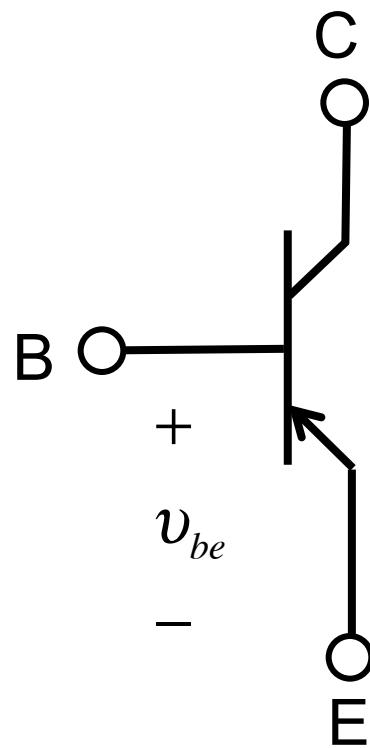


NPN DC to AC

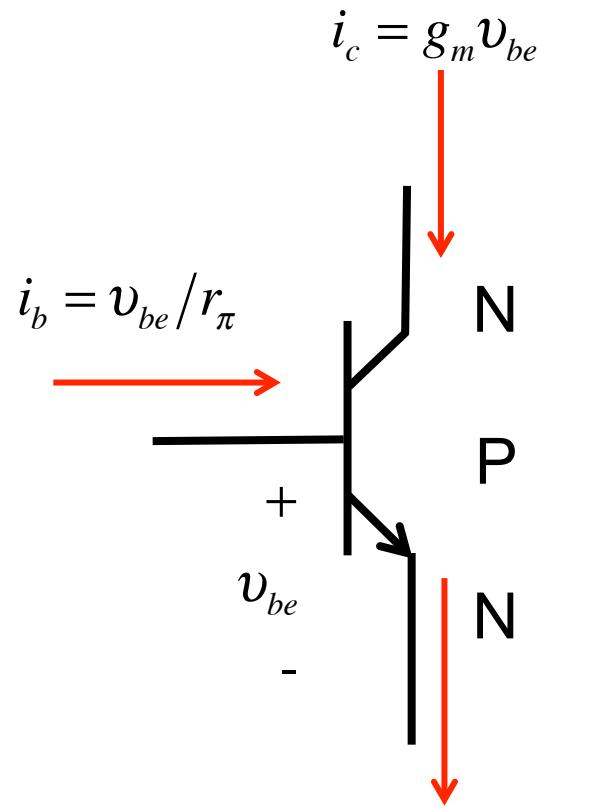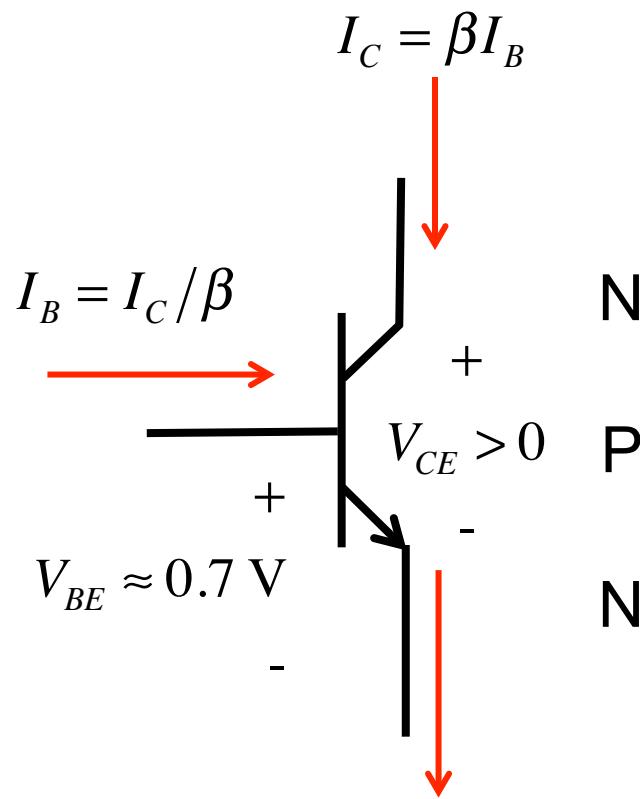

Lundstrom: 2019

PNP DC to AC

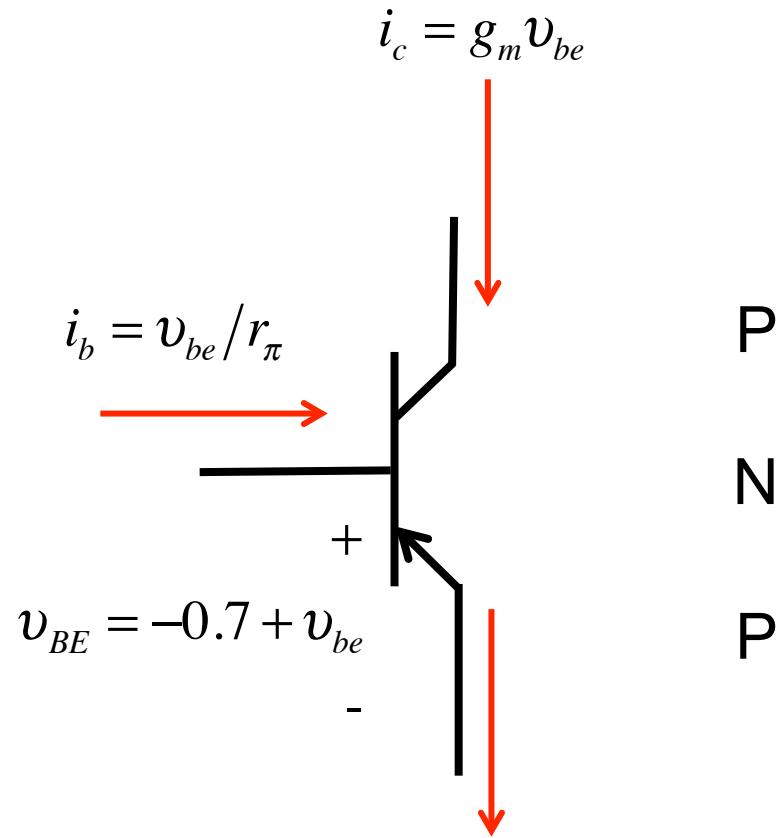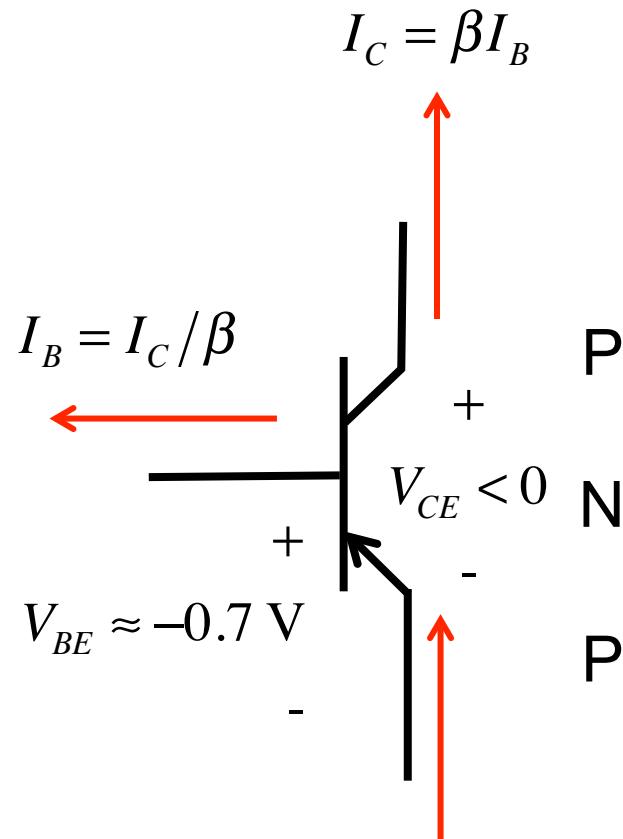


$$I_E = \frac{\beta + 1}{\beta} I_C$$

$$i_e = \left(g_m + \frac{1}{r_\pi} \right) v_{be}$$

Lundstrom: 2019

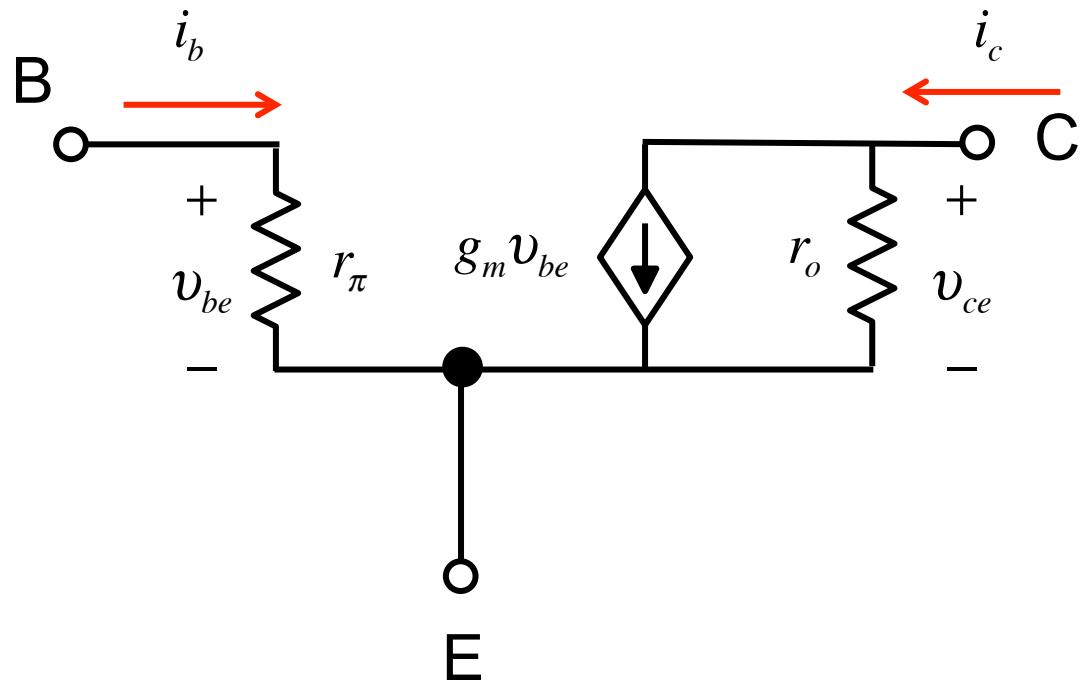Small signal hybrid pi model for NPN or PNP




$$g_m = I_C / V_T$$

$$g_m r_\pi = \beta$$

$$r_o = V_A / I_C$$


Quiz: Draw the s.s. equivalent circuit

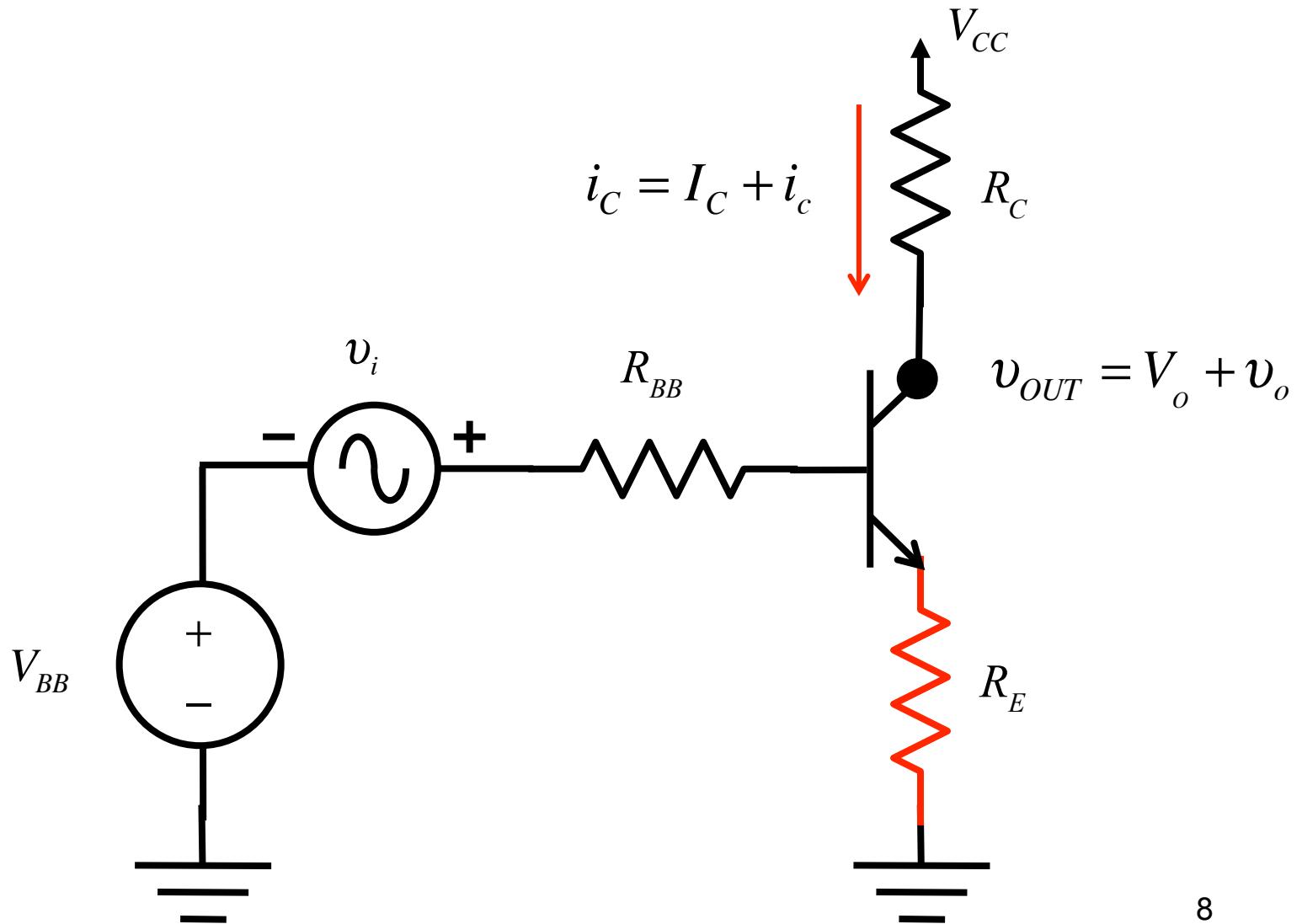

Outline

- 1) Voltage transfer characteristic (MOSFET)
- 2) Small signal model (hybrid pi)
- 3) Small signal analysis
- 4) Small signal model (T-model)


Voltage Transfer Characteristic (BJT)

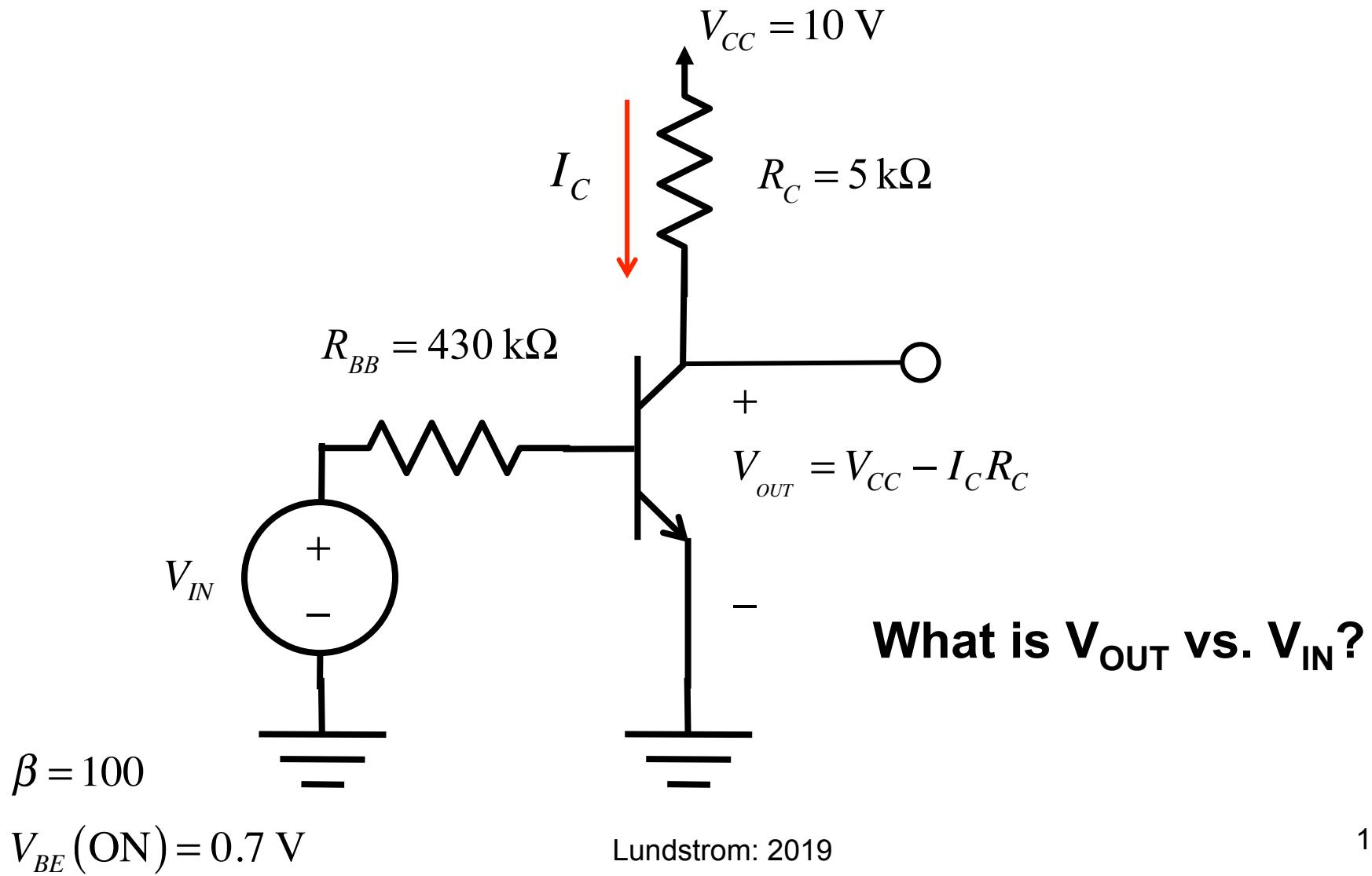

Voltage Transfer Characteristic (MOSFET)


$$k_n = 2 \text{ mA/V}^2$$

$$V_{tn} = 1.0 \text{ V}$$

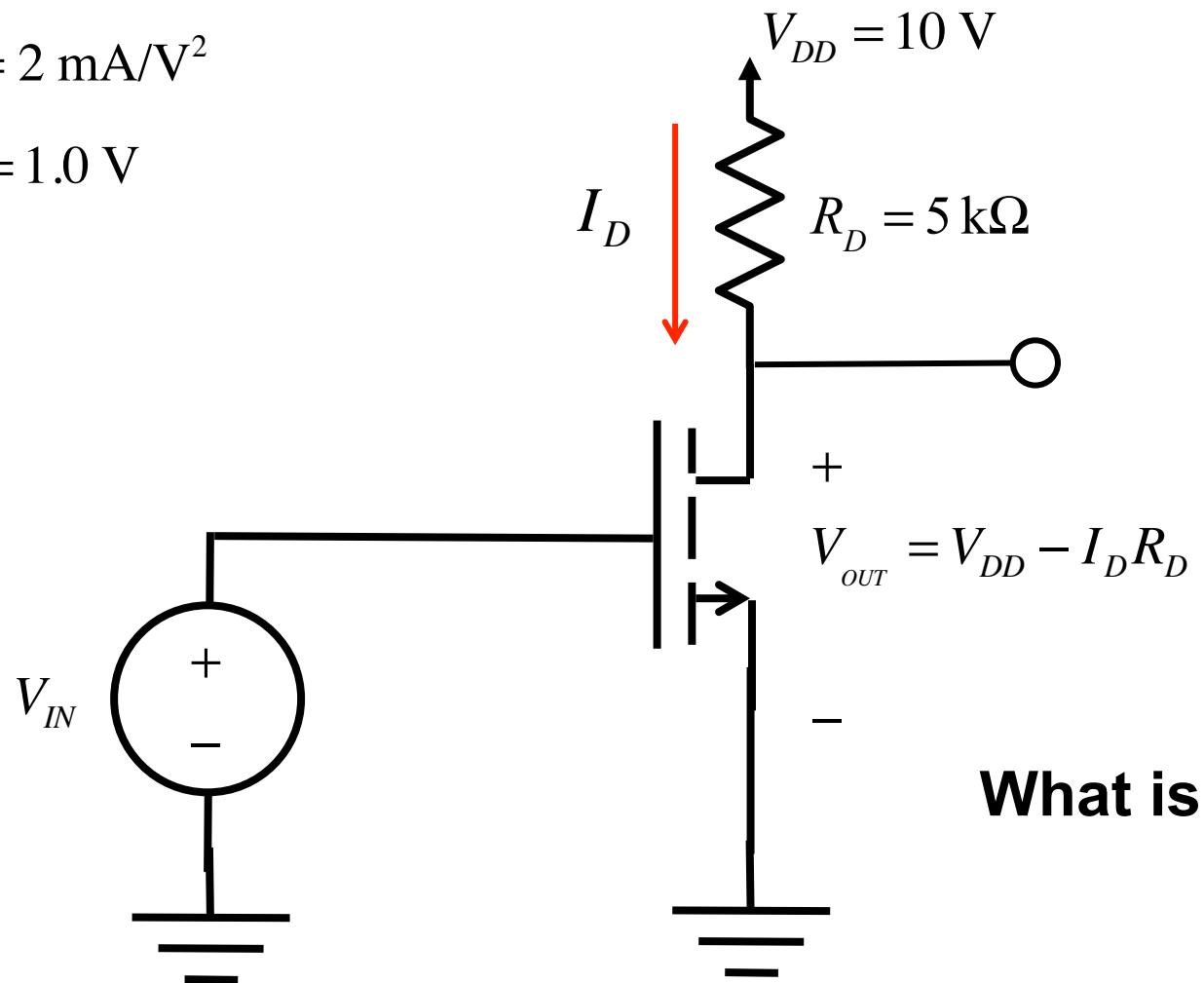


What is V_{OUT} vs. V_{IN} ?

VTC

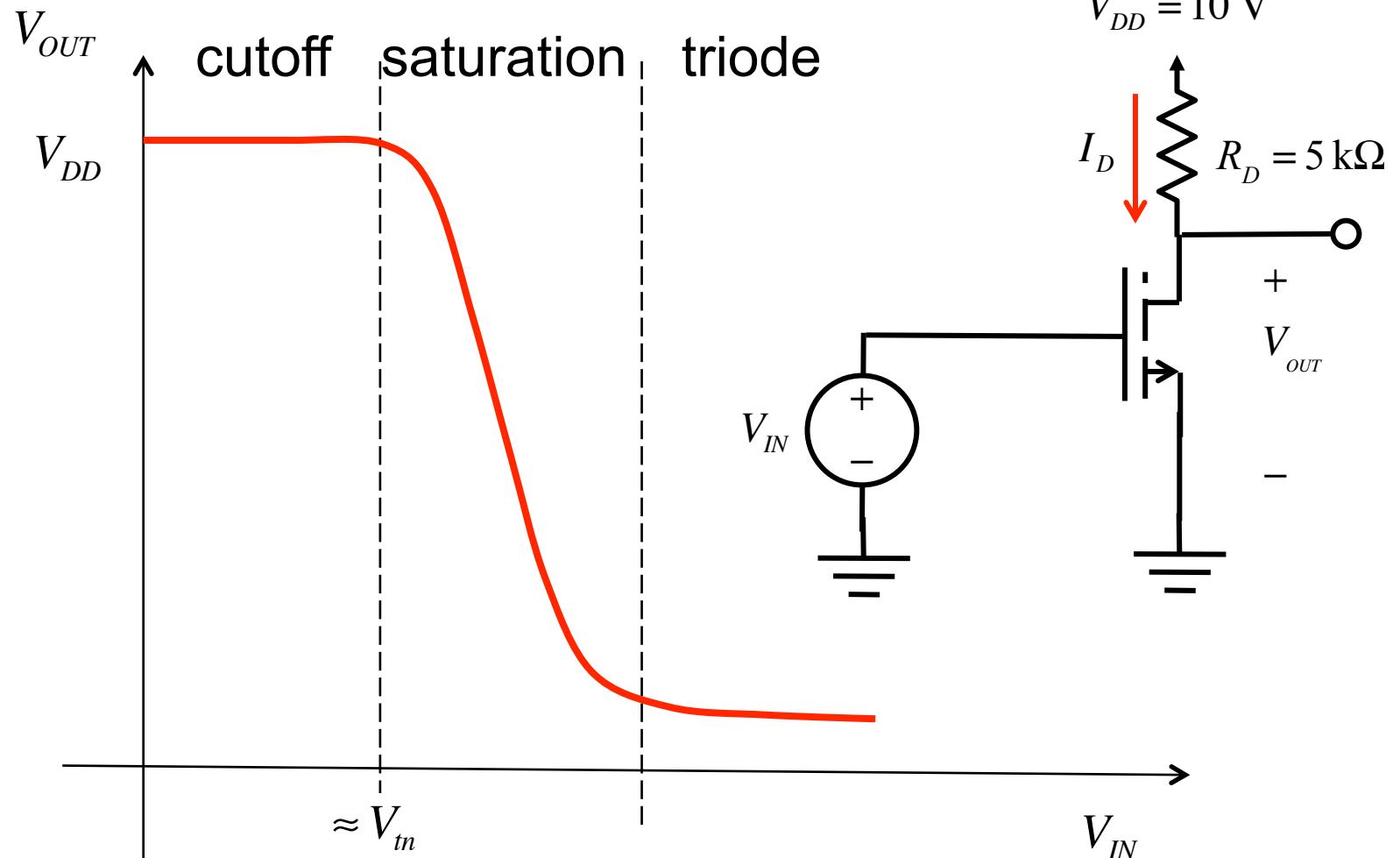


Biasing in the active region

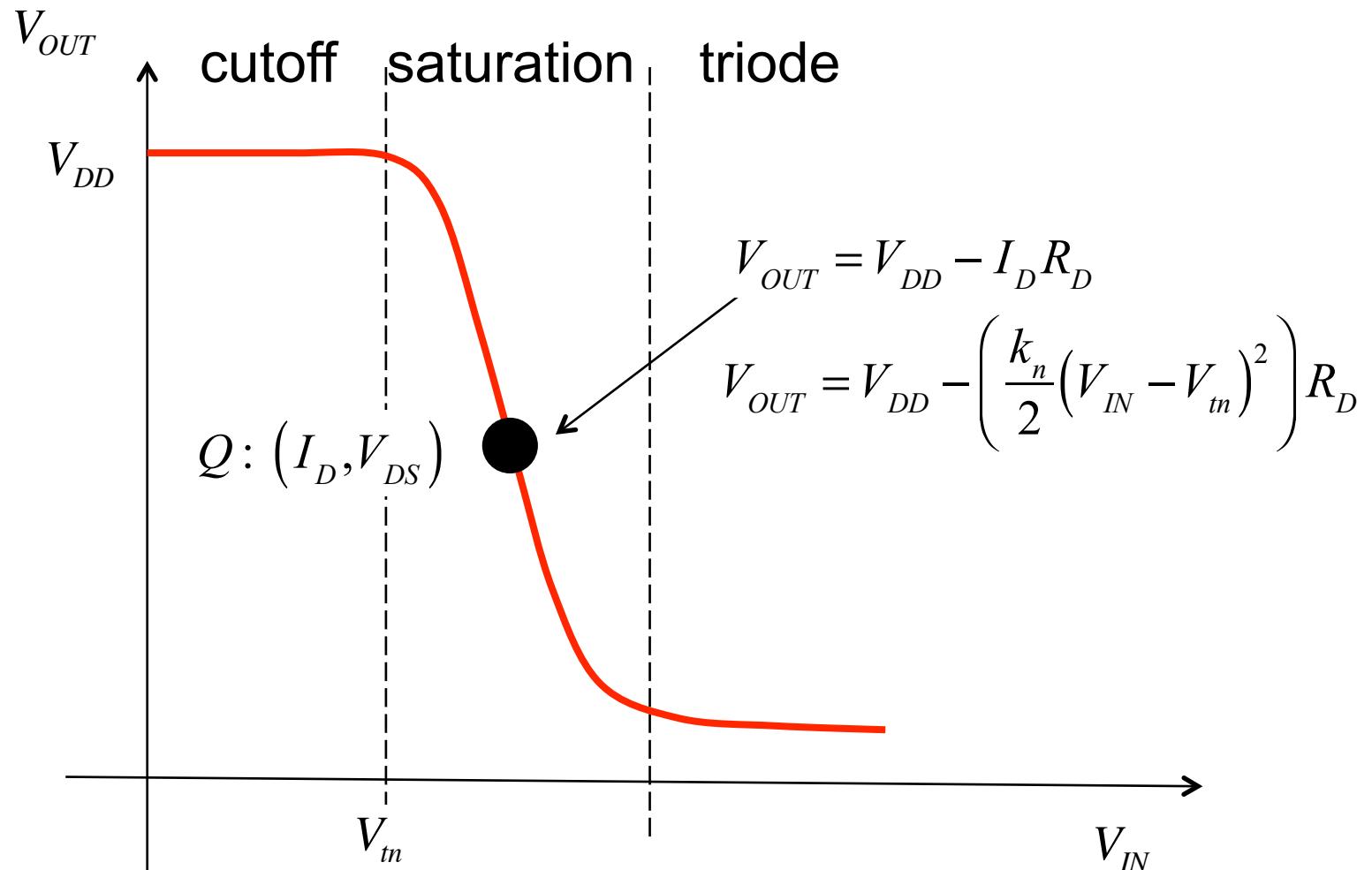


Add ac small signal

“Common **source** amplifier”

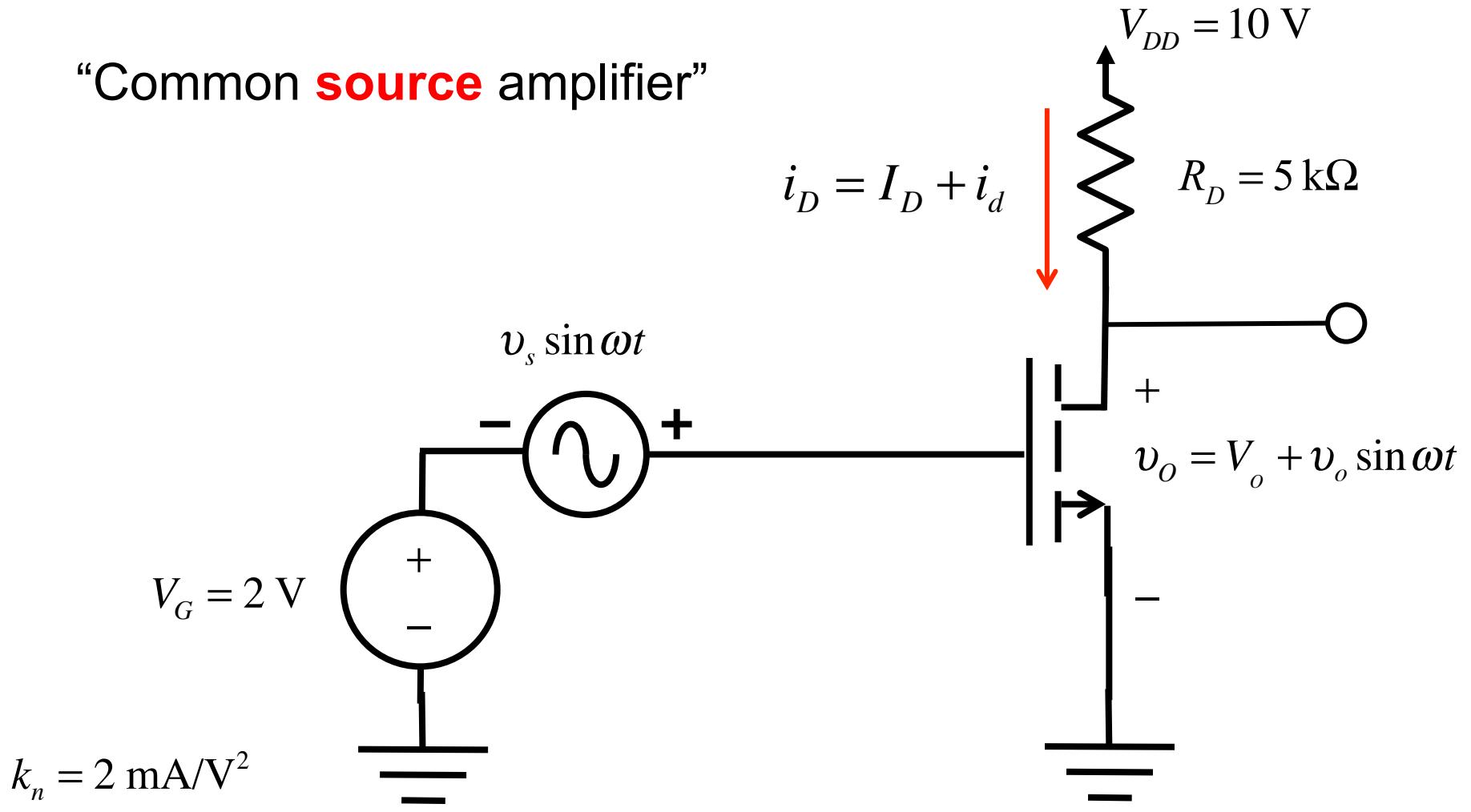


Analysis by superposition


- 1) DC first
- 2) Then AC

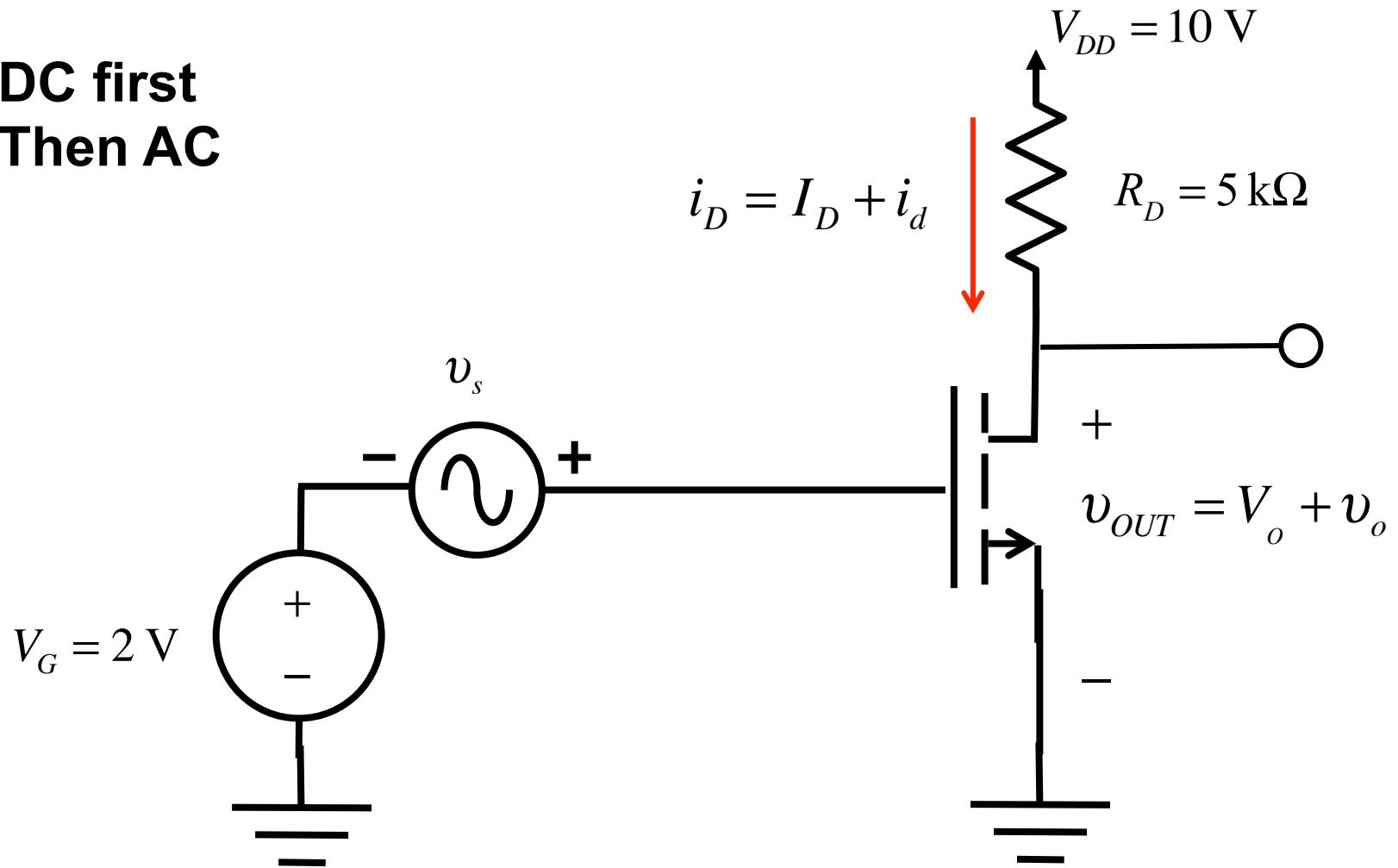


1) DC analysis

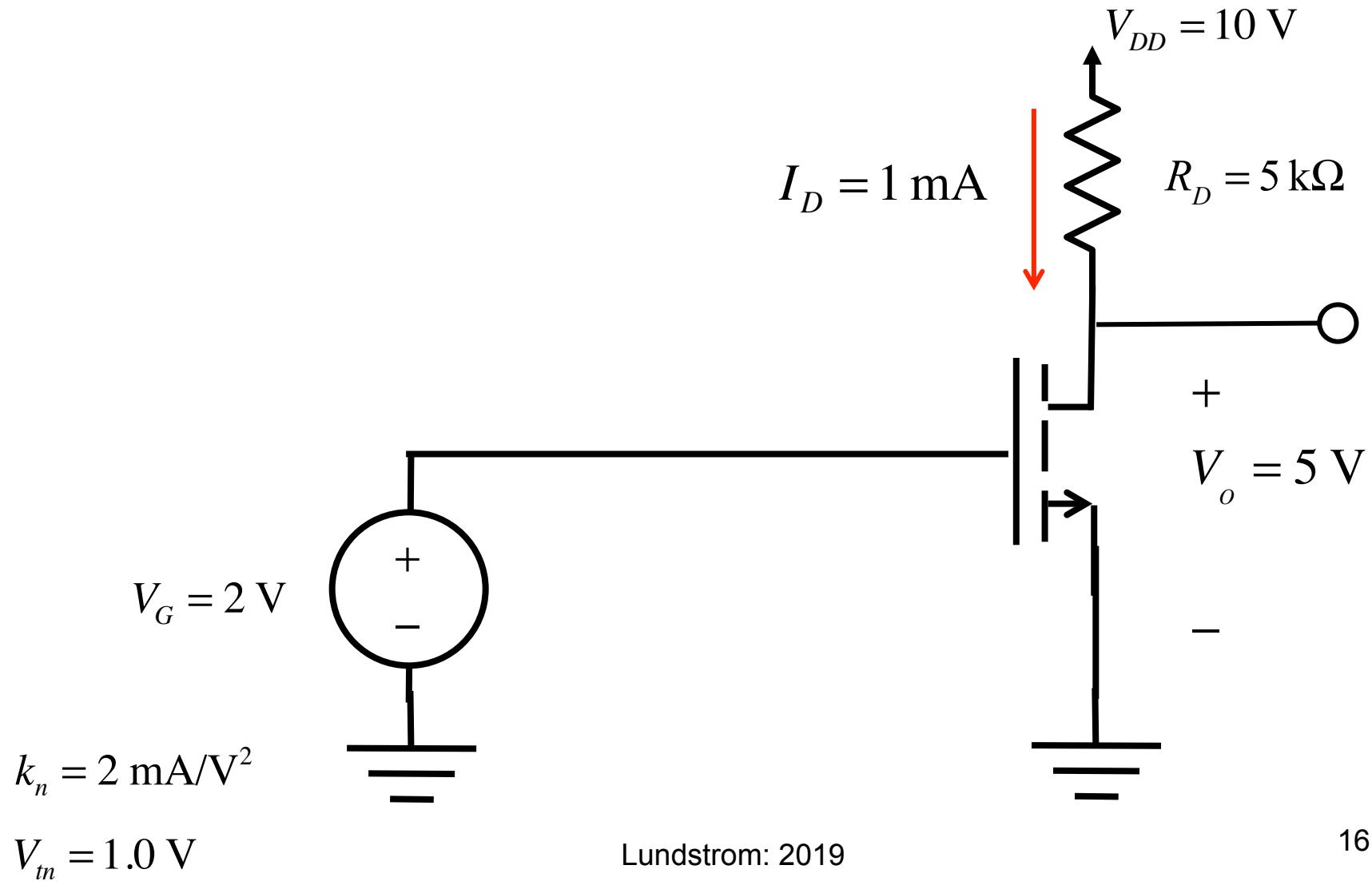


2) AC analysis

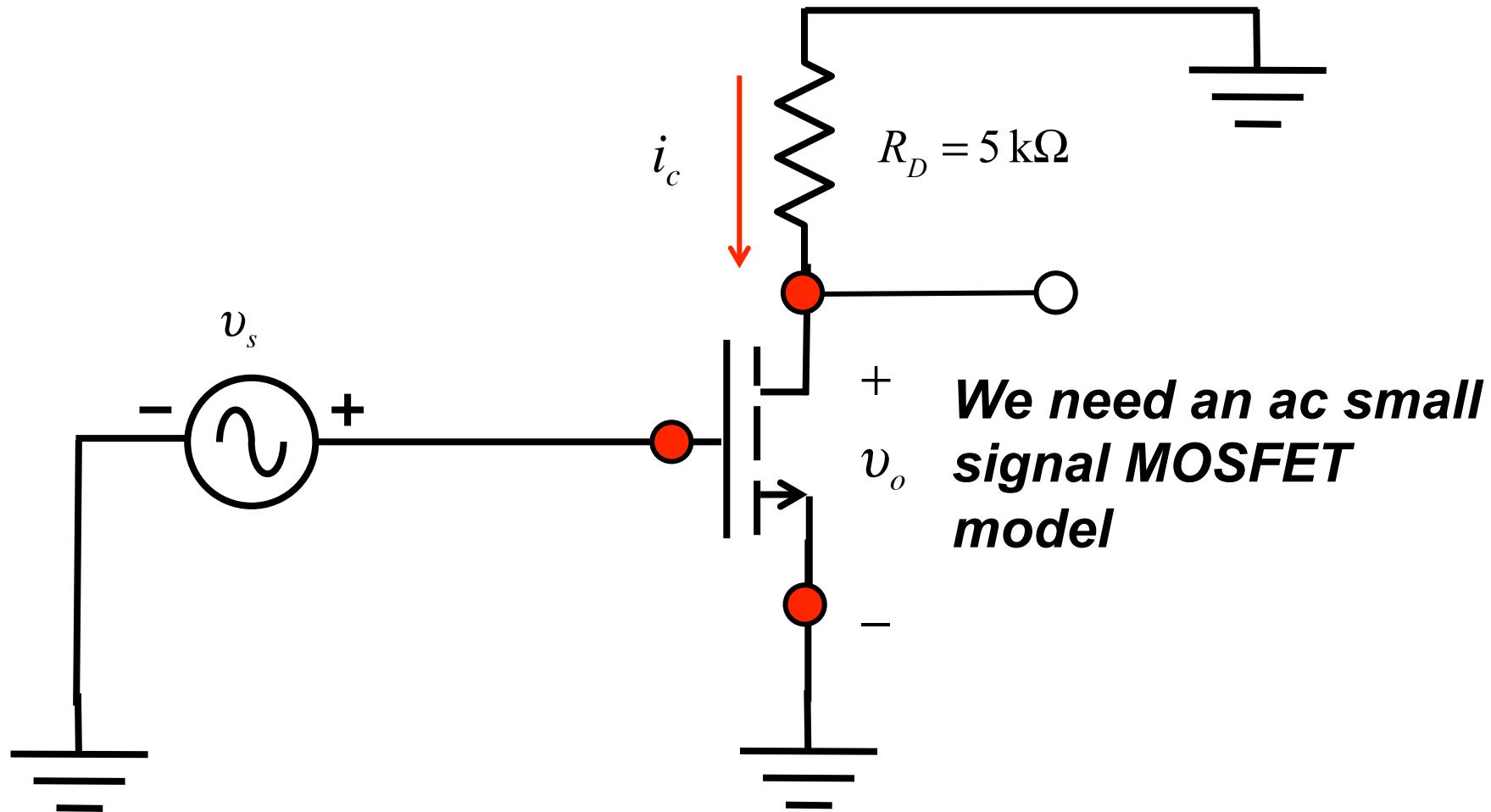

MOSFET s.s. model

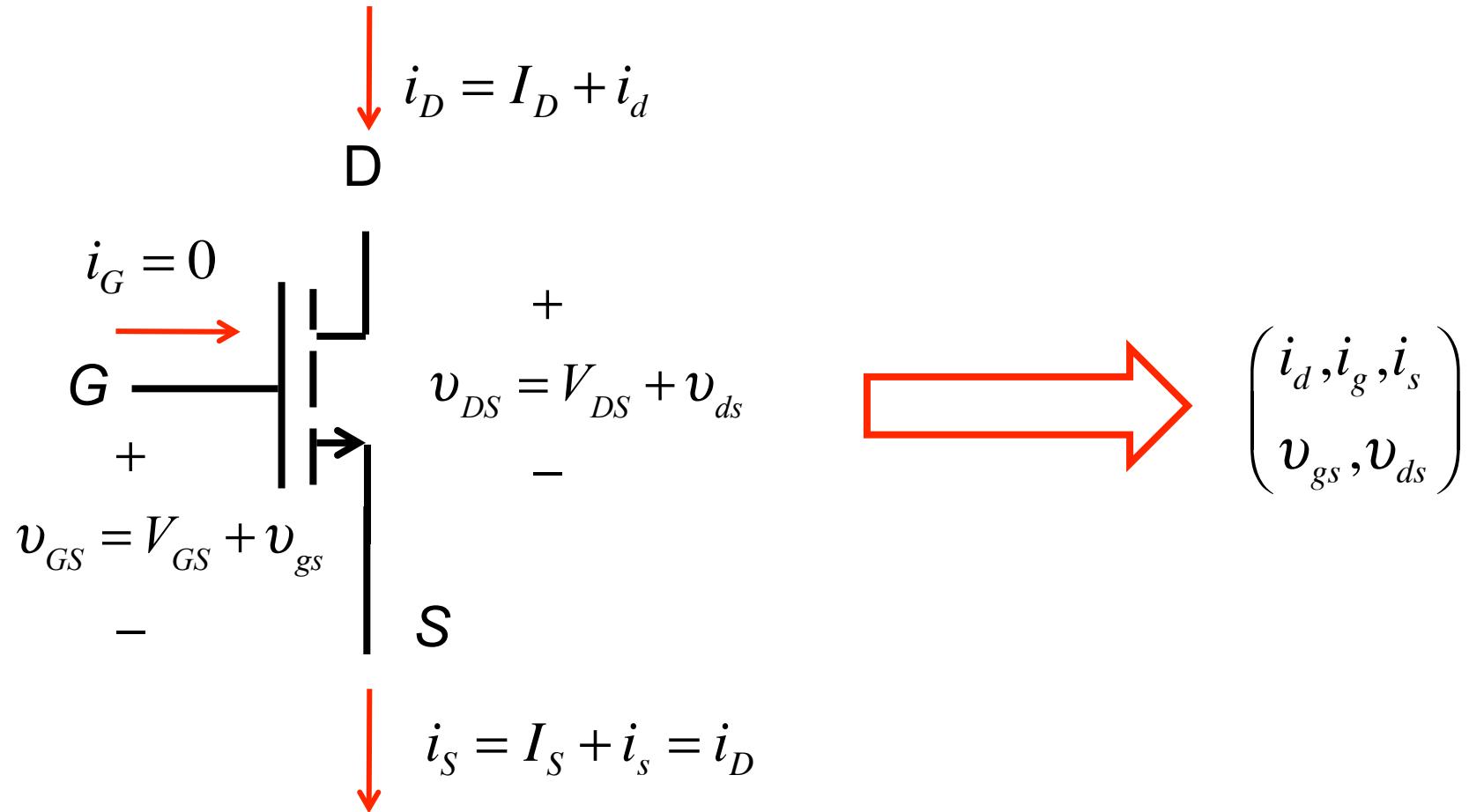


Result: MOSFET hybrid pi model

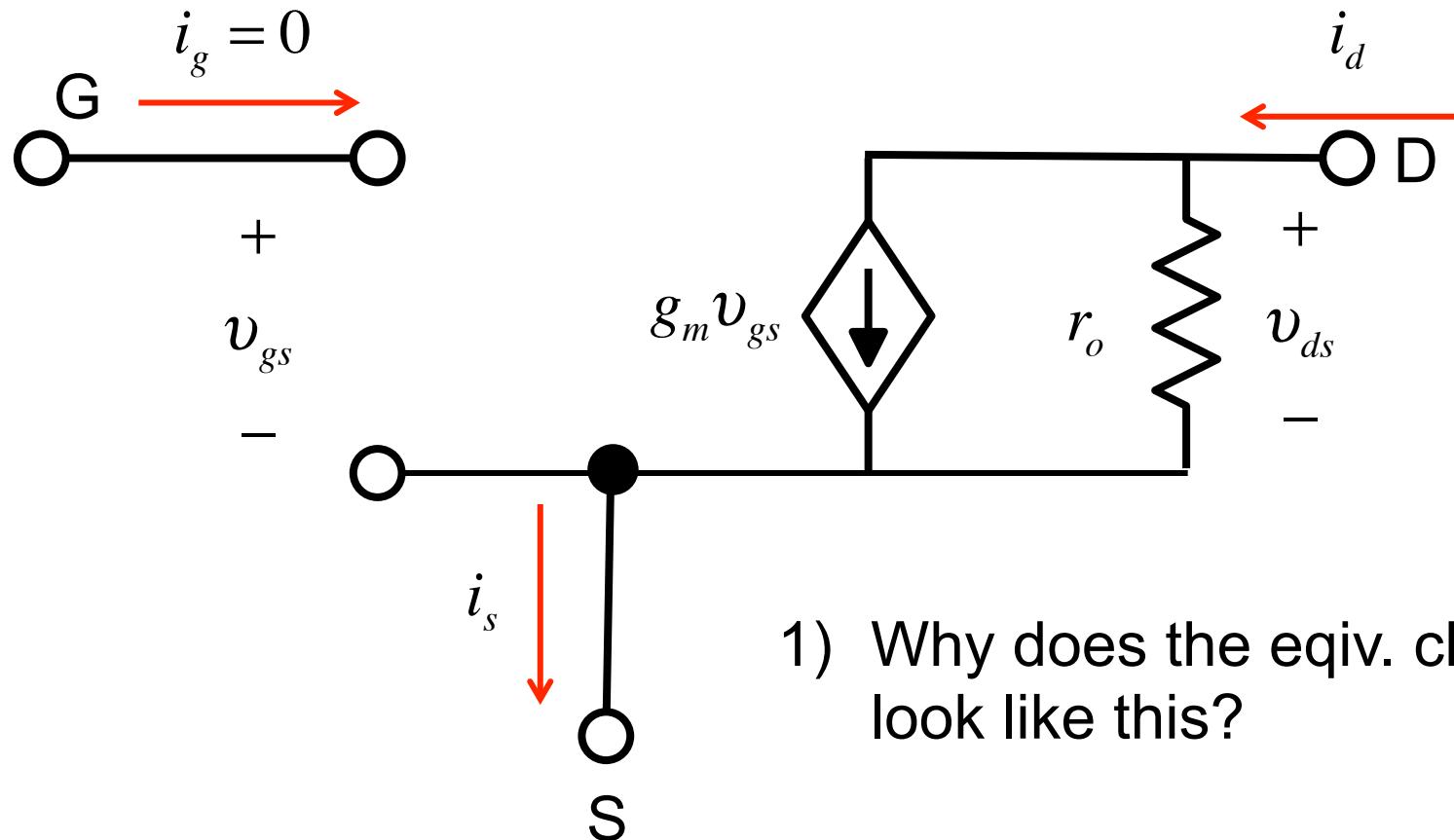

- 1) Why does the equiv. ckt. look like this?
- 2) What are the expressions for g_m and r_o ?

Taylor series

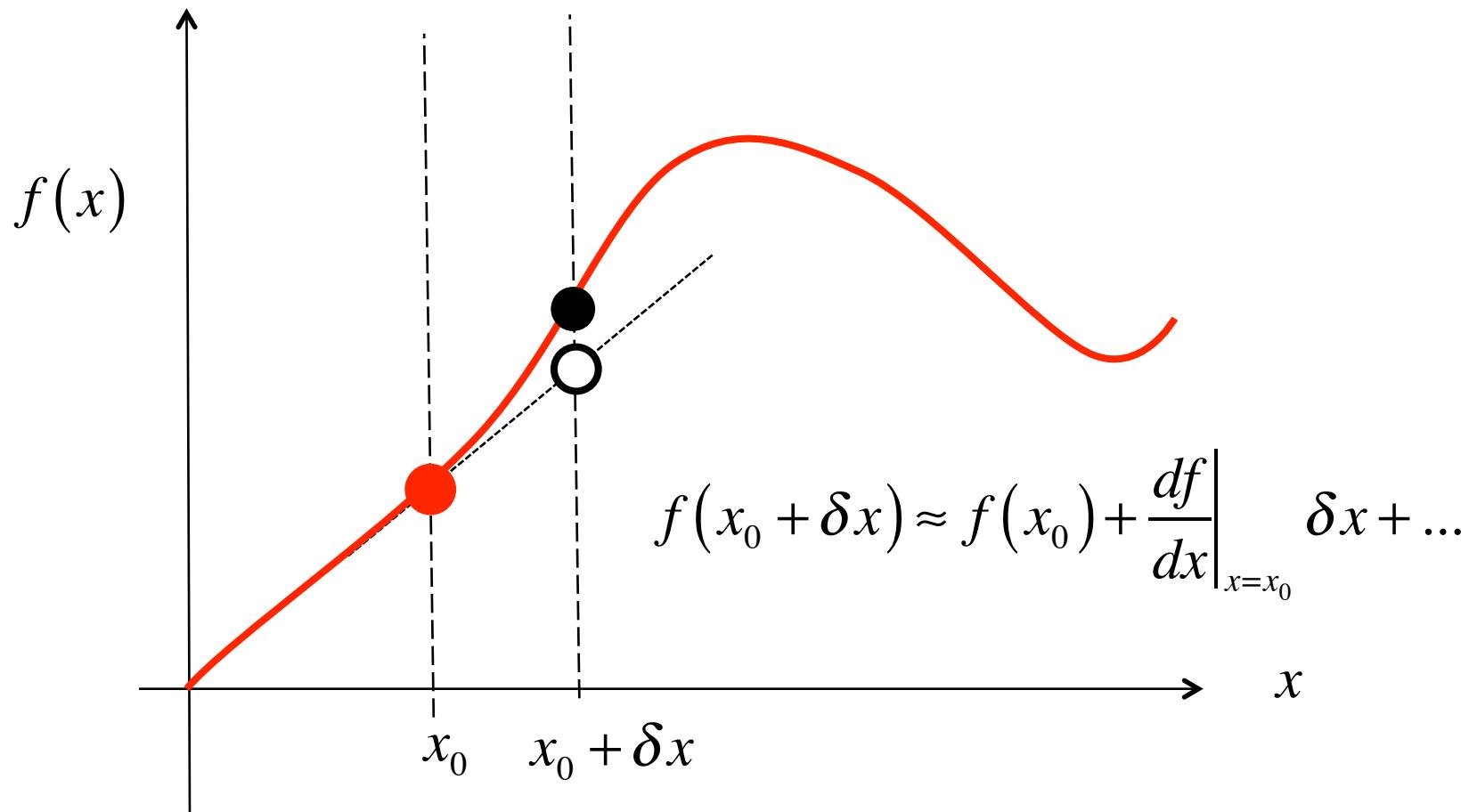

Taylor series in two variables

$$f(x,y)$$

$$f(x_0, y_0)$$

$$f(x_0 + \delta x, y_0 + \delta y) = ?$$

$$f(x_0 + \delta x, y_0 + \delta y) \approx f(x_0, y_0) + \frac{\partial f}{\partial x} \Big|_{x_0, y_0} \delta x + \frac{\partial f}{\partial y} \Big|_{x_0, y_0} \delta y$$

$$\delta f = f(x_0 + \delta x, y_0 + \delta y) - f(x_0, y_0)$$

$$\delta f = \frac{\partial f}{\partial x} \Big|_{x_0, y_0} \delta x + \frac{\partial f}{\partial y} \Big|_{x_0, y_0} \delta y$$

Taylor series expansion of I_D

$$I_D(V_{GS}, V_{DS}) = \frac{k_n}{2} (V_{GS} - V_{tn})^2 \left(1 + V_{DS}/V_A\right) \quad [f(x_0, y_0)]$$

$$I_D(V_{GS} + \delta V_{GS}, V_{DS} + \delta V_{DS}) = ? \quad [f(x_0 + \delta x, y_0 + \delta y)]$$

$$\begin{aligned} I_D(V_{GS} + \delta V_{GS}, V_{DS} + \delta V_{DS}) &= I_D(V_{GS}, V_{DS}) \\ &\quad + \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}, V_{DS}} \delta V_{GS} + \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}, V_{DS}} \delta V_{DS} + \dots \end{aligned}$$

$$\delta I_D = I_D(V_{GS} + \delta V_{GS}, V_{DS} + \delta V_{DS}) - I_D(V_{GS}, V_{DS})$$

$$\delta I_D = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}, V_{DS}} \delta V_{GS} + \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}, V_{DS}} \delta V_{DS}$$

Taylor series (ii)


$$\delta I_D = \frac{\partial I_D}{\partial V_{GS}} \Bigg|_{V_{GS}, V_{DS}} \delta V_{GS} + \frac{\partial I_D}{\partial V_{DS}} \Bigg|_{V_{GS}, V_{DS}} \delta V_{DS}$$

$$\delta I_D = g_m \delta V_{GS} + g_d \delta V_{DS}$$

$$\delta I_D = g_m \delta V_{GS} + \frac{\delta V_{DS}}{r_o}$$

$$g_m \equiv \frac{\partial I_D}{\partial V_{GS}} \Bigg|_{V_{GS}, V_{DS}}$$
$$i_d = g_m v_{gs} + \frac{1}{r_o} v_{ds}$$
$$\frac{1}{r_o} \equiv \frac{\partial I_D}{\partial V_{DS}} \Bigg|_{V_{GS}, V_{DS}}$$

MOSFET in saturation (DC)

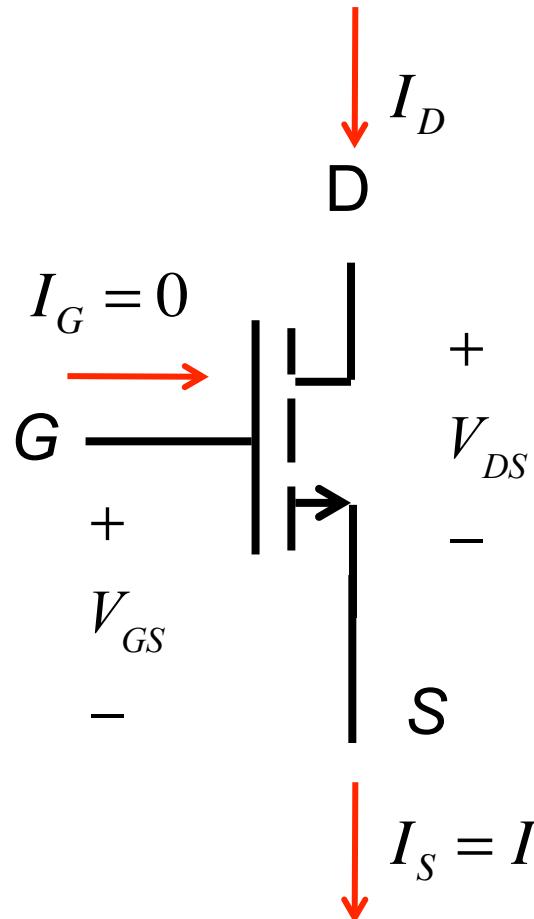

$$I_D = \frac{k_n}{2} (V_{GS} - V_{tn})^2 (1 + \lambda V_{DS})$$

$$k_n = \frac{W}{L} \mu_n C_{ox} \quad \lambda = \frac{1}{V_A}$$

$$V_{DS} > (V_{GS} - V_{tn}) \quad V_{GS} > V_{tn}$$

Transconductance

$$g_m \equiv \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}, V_{DS}}$$

$$I_D = \frac{k_n}{2} (V_{GS} - V_{tn})^2 (1 + \lambda V_{DS})$$

$$g_m = k_n (V_{GS} - V_{tn}) (1 + V_{DS}/V_A)$$

$$I_D \approx \frac{k_n}{2} (V_{GS} - V_{tn})^2$$

$$(V_{GS} - V_{tn}) = \sqrt{\frac{2I_D}{k_n}}$$

$$g_m = \frac{2I_D}{(V_{GS} - V_{tn})}$$

$$g_m \approx k_n (V_{GS} - V_{tn})$$

$$g_m \approx \sqrt{2k_n I_D}$$

Output resistance

$$\frac{1}{r_o} \equiv \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}, V_{DS}}$$

$$I_D(V_{GS}, V_{DS}) = \frac{k_n}{2} (V_{GS} - V_{tn})^2 \left(1 + \frac{V_{DS}}{V_A} \right)$$

$$\frac{1}{r_0} = \frac{k_n}{2} (V_{GS} - V_{tn})^2 \left(1/V_A \right) \approx \frac{I_D}{V_A}$$

Final result in equations

$$i_d = g_m v_{gs} + \frac{1}{r_0} v_{ds}$$


$$i_g = 0$$

$$i_s = i_d$$

$$g_m = \frac{I_D}{(V_{GS} - V_{tn})/2}$$

$$r_o \approx \frac{V_A}{I_D}$$

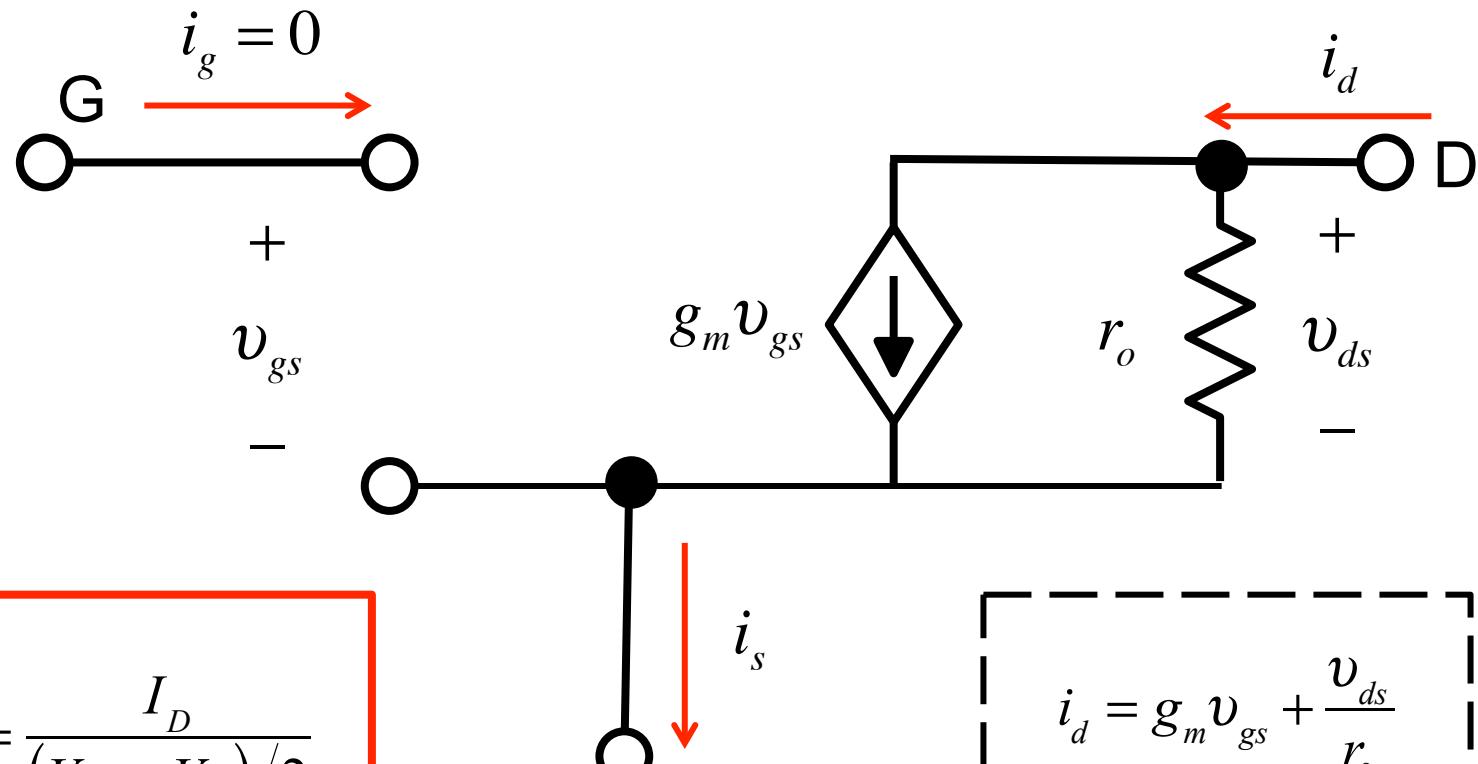Final result in circuit form (hybrid pi model)



$$g_m = \frac{I_D}{(V_{GS} - V_{tn})/2}$$

$$r_o = \frac{V_A}{I_D}$$

$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_0}$$

$$i_g = 0$$

$$i_s = i_d$$

BJT vs. MOSFET

BJT

$$g_m = \frac{I_C}{V_T}$$

$$I_C = 1 \text{ mA}$$

$$V_T = 0.025 \text{ V}$$

$$g_m = 40 \frac{\text{mA}}{\text{V}} = 40 \text{ mS}$$

MOSFET

$$g_m = \frac{I_D}{(V_{GS} - V_{tn})/2}$$

$$I_D = 1 \text{ mA} \quad V_{GS} = 2.0 \text{ V} \quad V_{tn} = 1 \text{ V}$$

$$g_m = 2 \text{ mS}$$

BJT vs. MOSFET


Bipolar transistors are much better amplifying devices than MOSFETs.

A typical BJT provides roughly 10 X the transconductance of a typical MOSFET.


But the hybrid pi models are very similar.
(For the MOSFET, $r_\pi \rightarrow \text{infinity}$.)

Analysis by superposition


- 1) DC first
- 2) Then AC

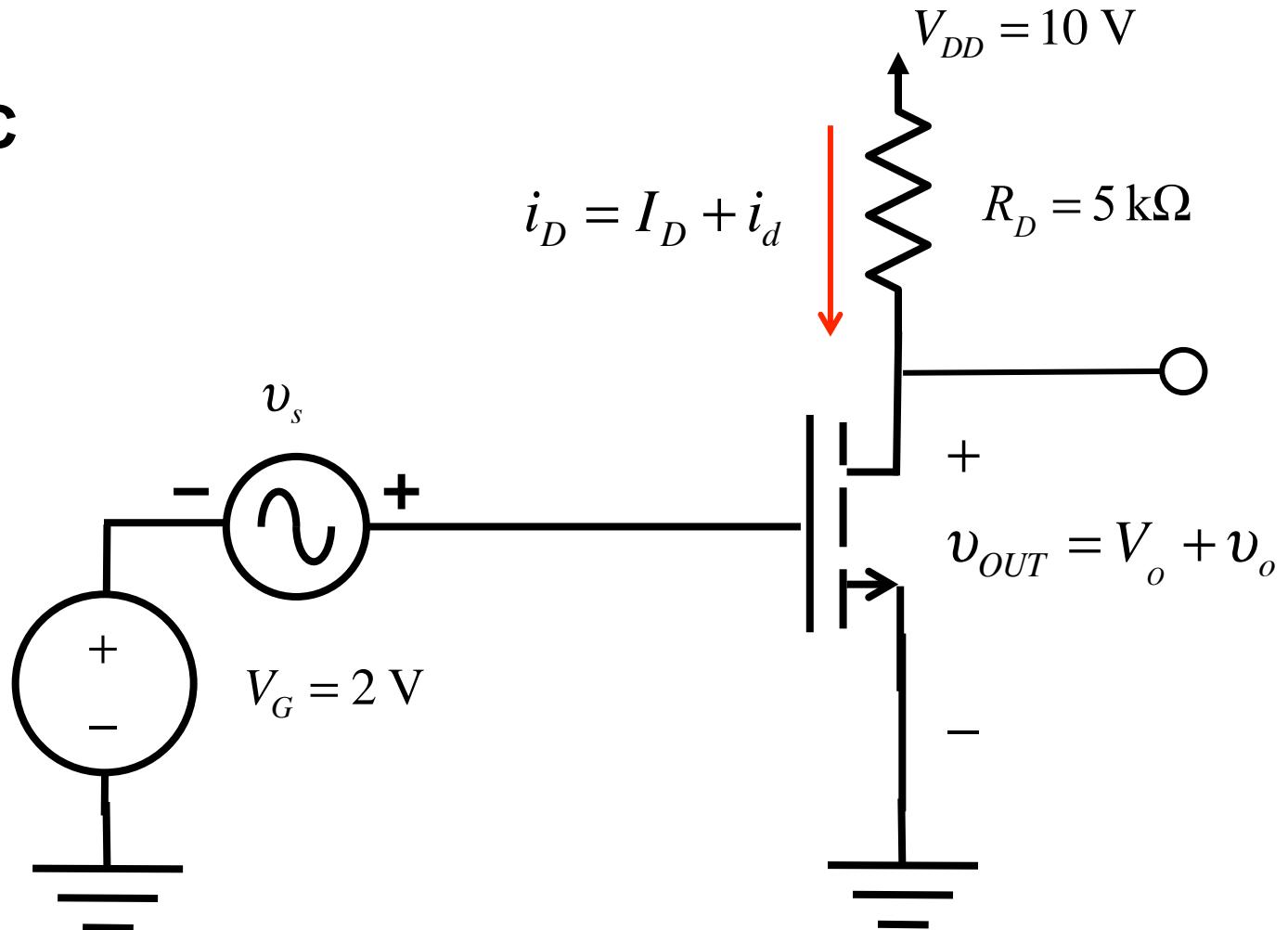

Small signal circuit

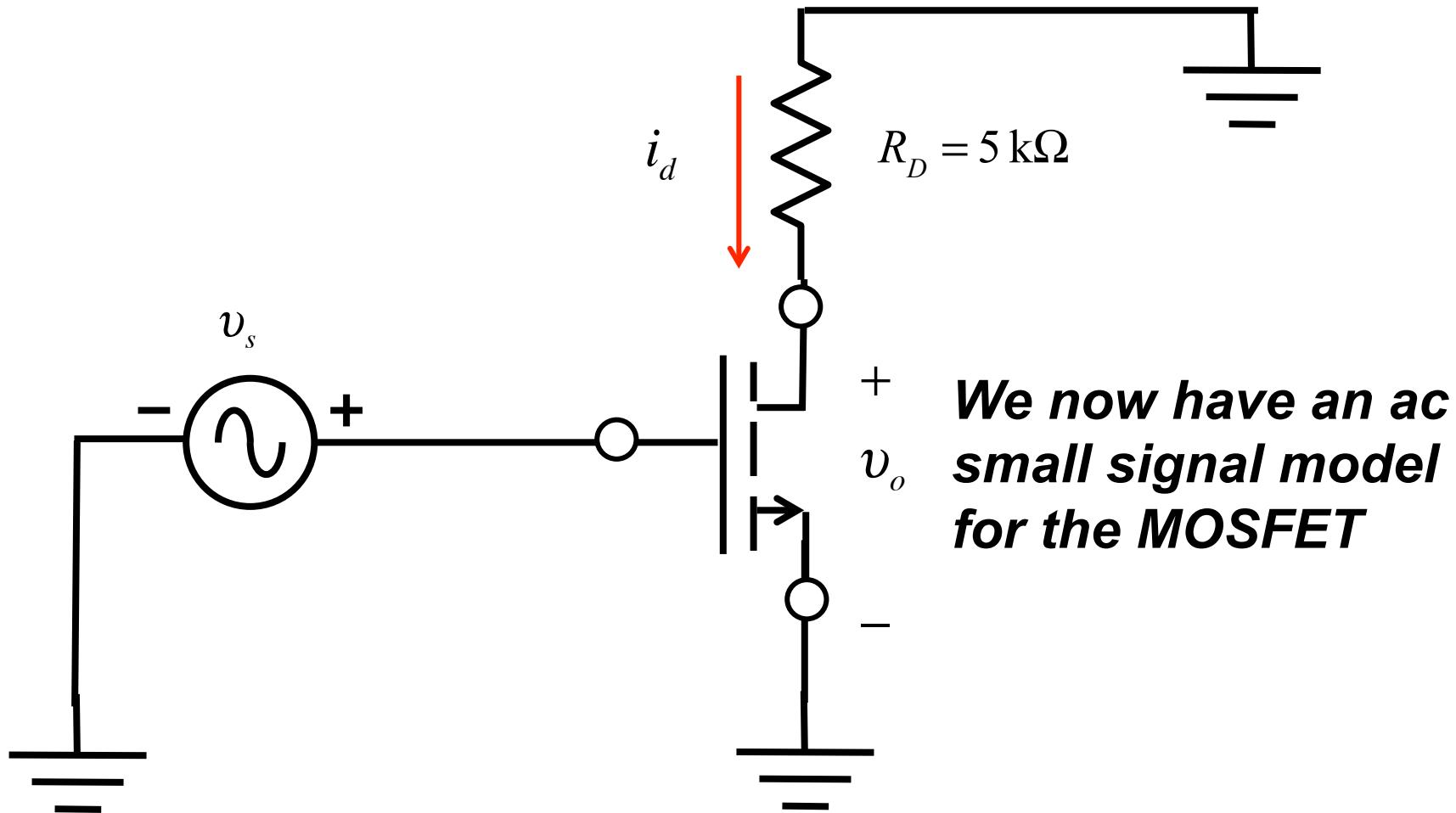


Simple s.s. model

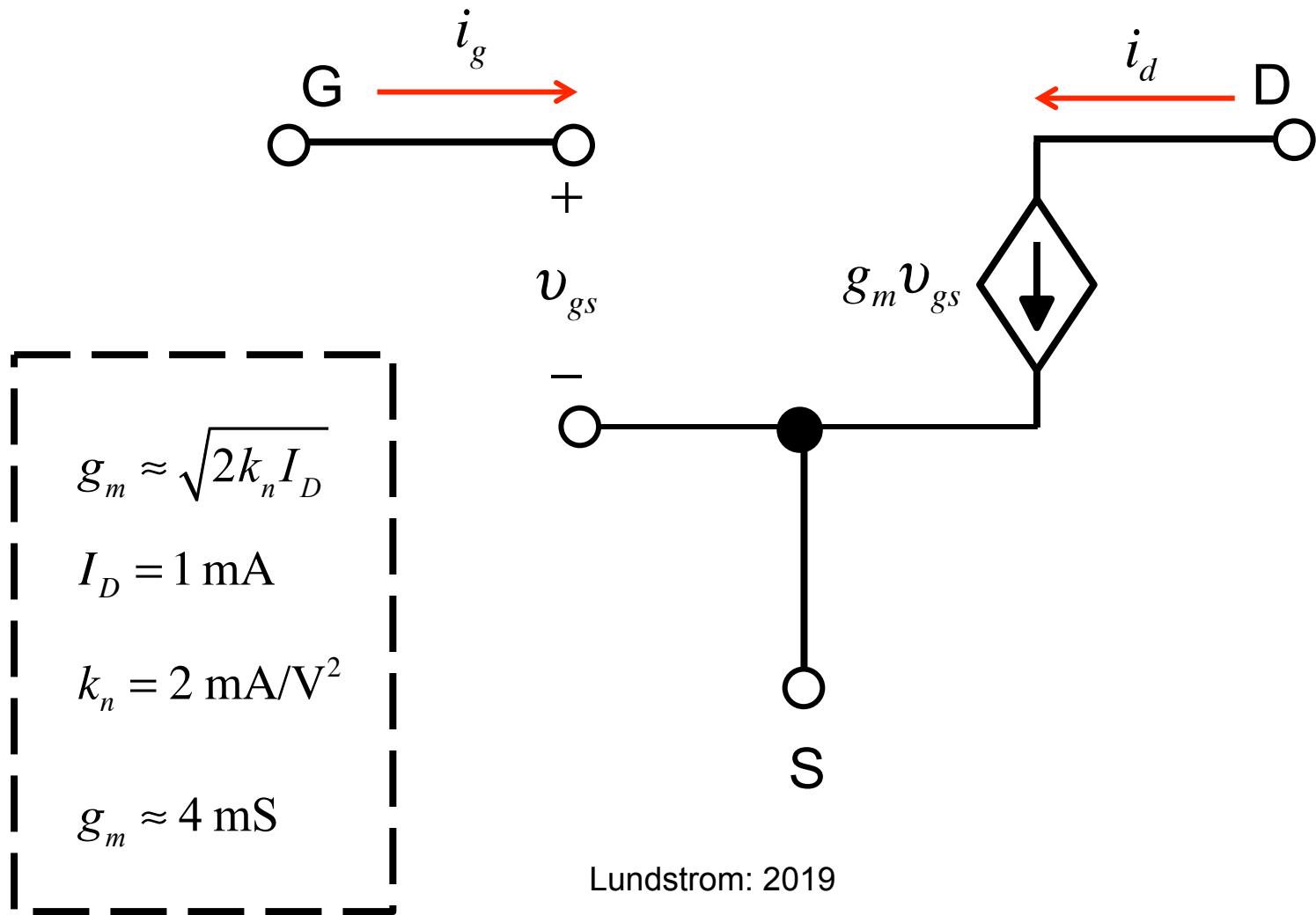


Lundstrom: 2019

Draw the small signal equivalent circuit

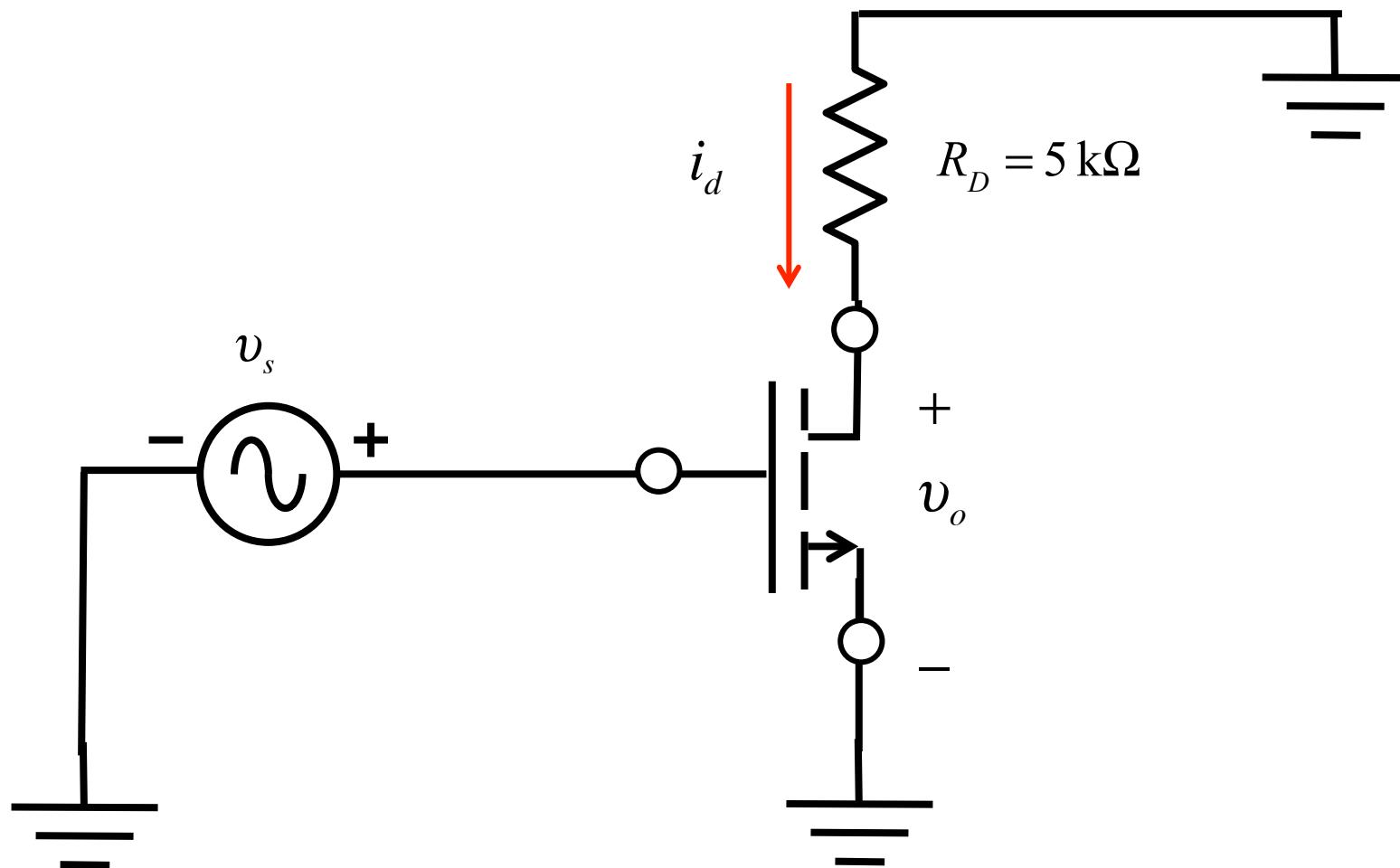

Result

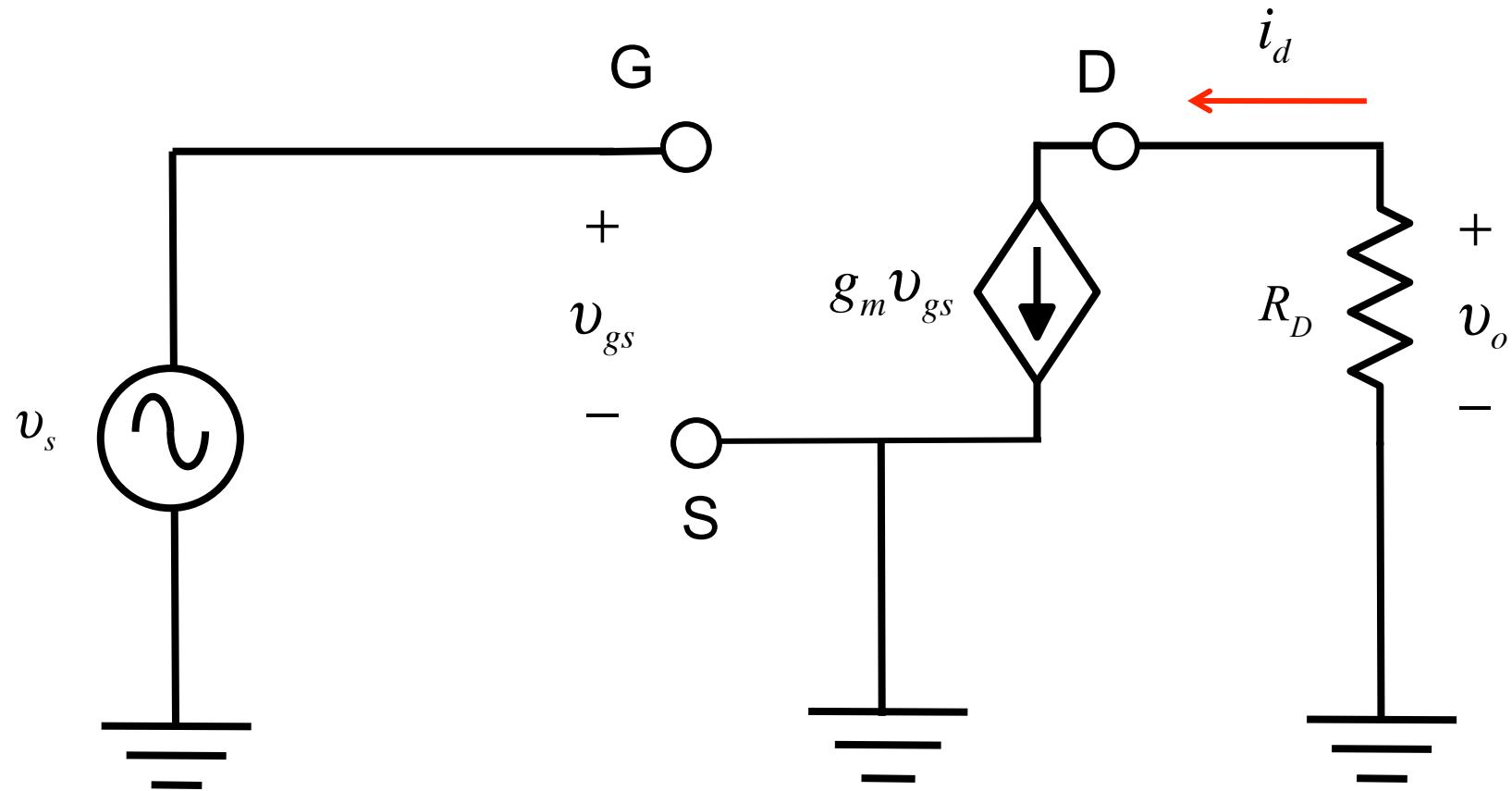

ac analysis

$$v_o = -g_m v_{gs} R_D$$

$$v_{gs} = v_s$$


$$v_o = -g_m R_D v_s$$

$$g_m \approx 4 \text{ mS}$$


$$A_{v_s} = -20$$

$$\frac{v_o}{v_s} = A_{v_s} = -g_m R_D$$

Hybrid pi model with output resistance

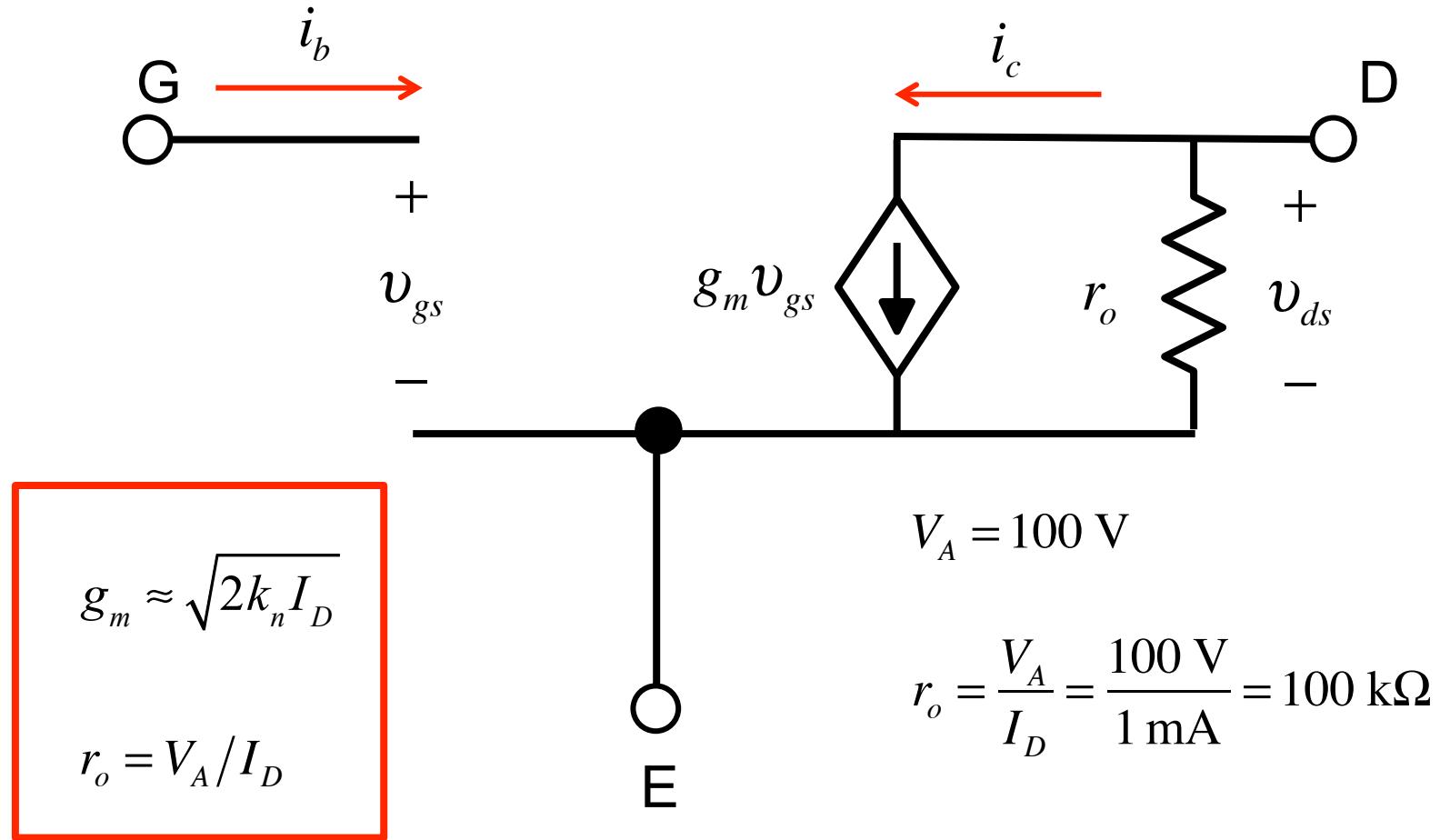

Circuit with output resistance

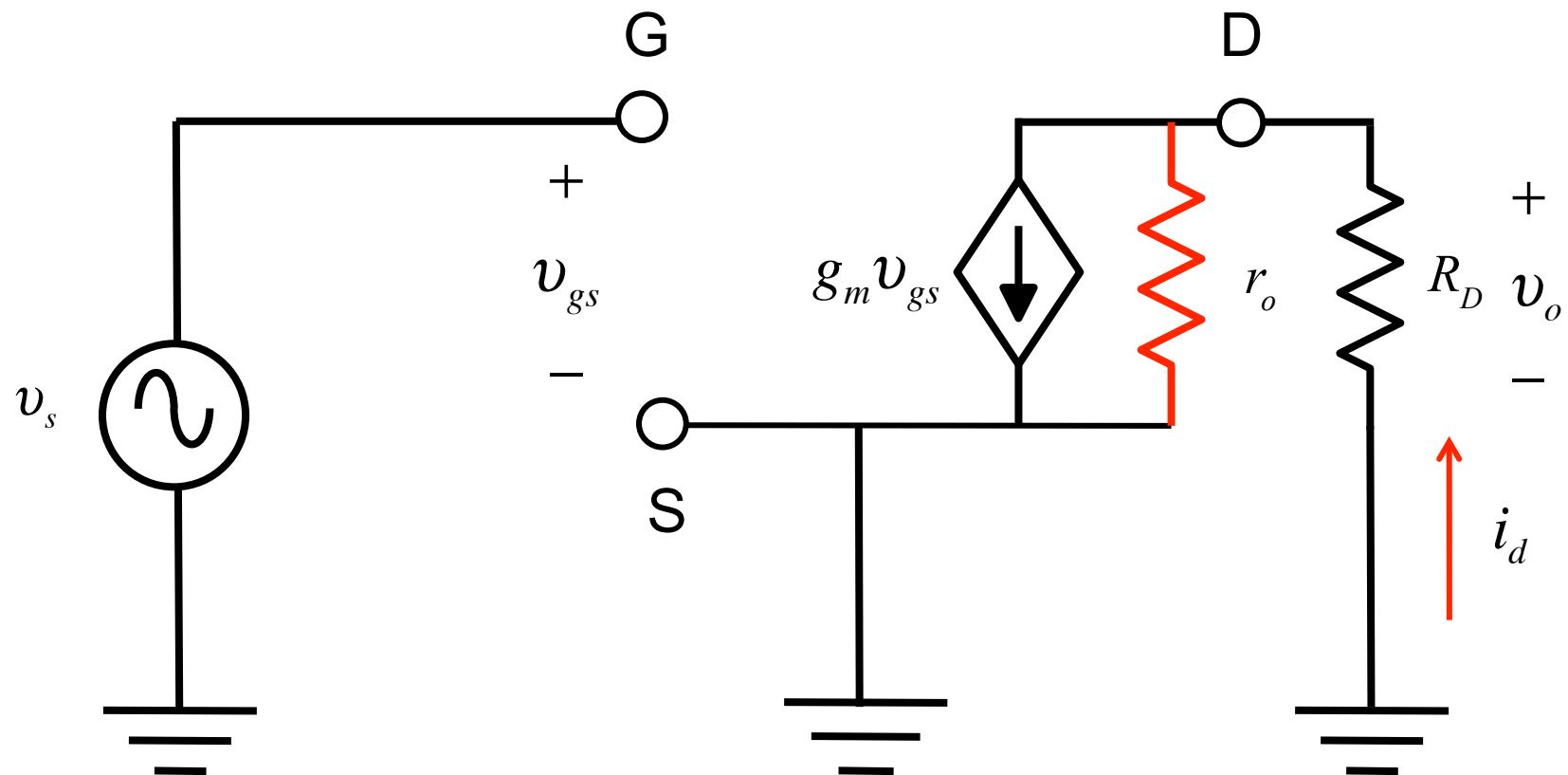

2) AC analysis with output resistance


$$\frac{v_o}{v_s} = A_{v_s} = -g_m R_D \quad (\text{without } r_o)$$

$$\frac{v_o}{v_s} = A_{v_s} = -g_m R_D \parallel r_0 \quad (\text{with } r_o)$$

$$5 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 4.76 \text{ k}\Omega$$


$$A_v = -20 \rightarrow A_v = -19$$

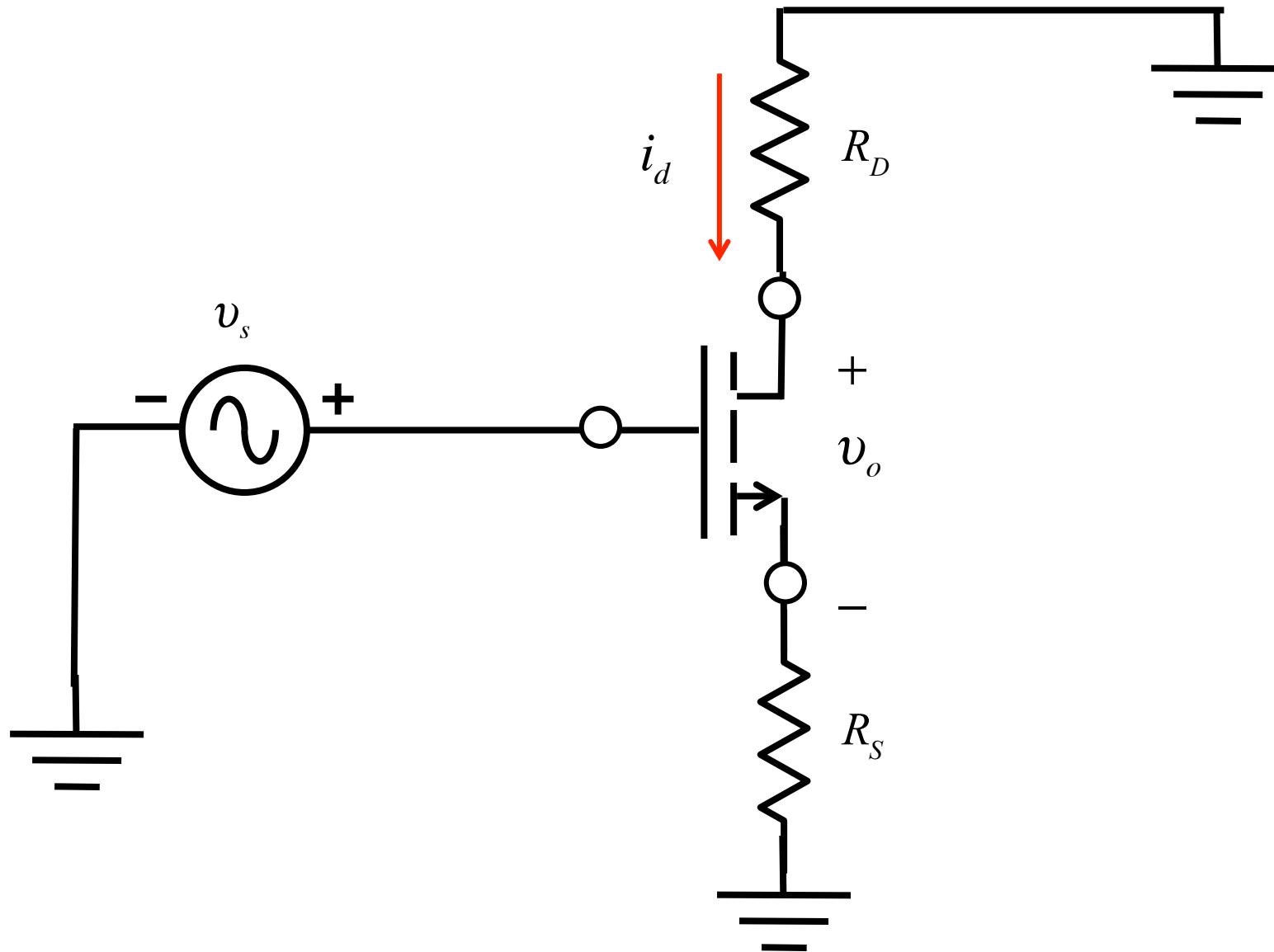Small signal circuit with source resistor




Draw the small signal circuit

The small signal circuit

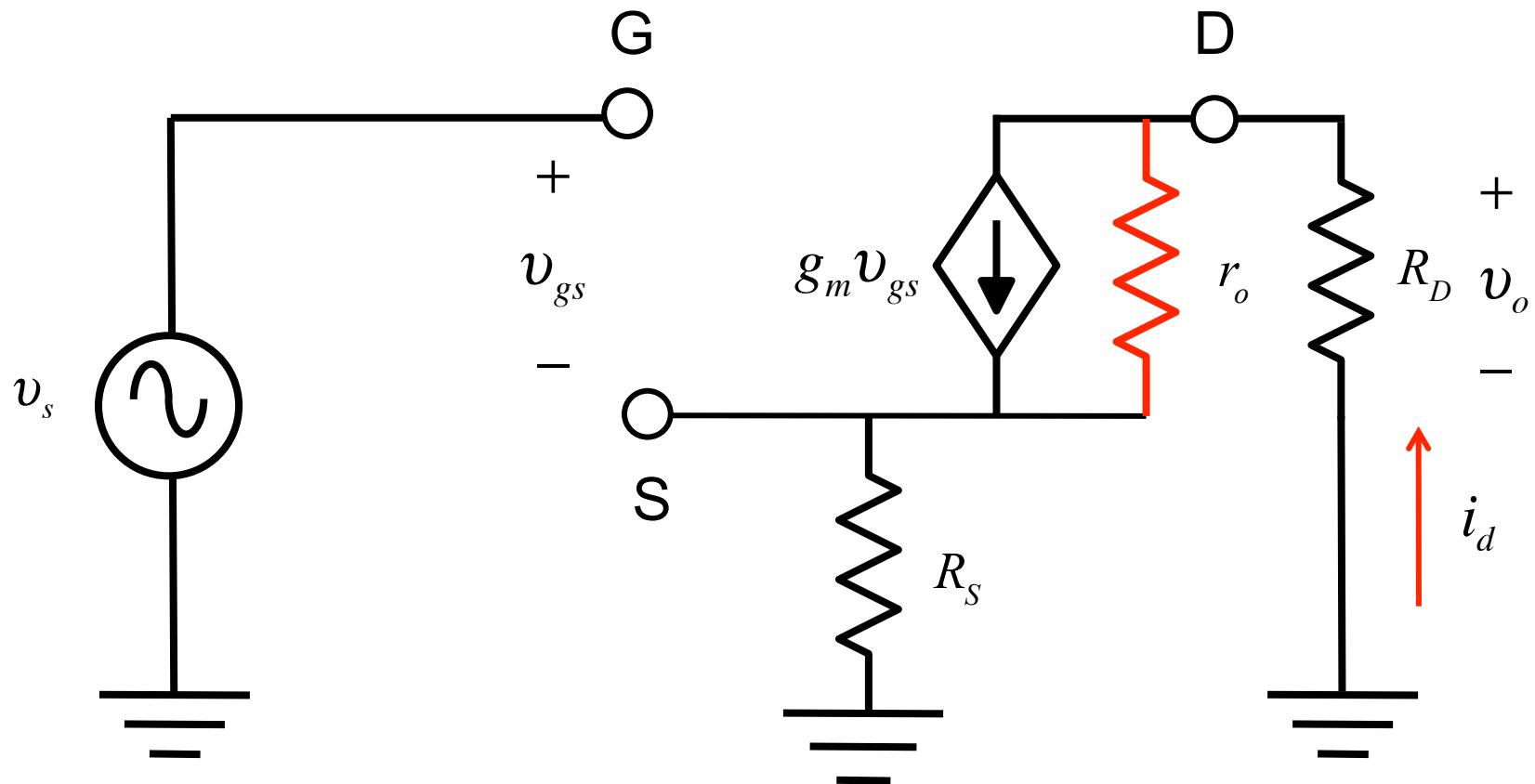

Compute the voltage gain

$$A_{v_s} = \frac{v_o}{v_s}$$

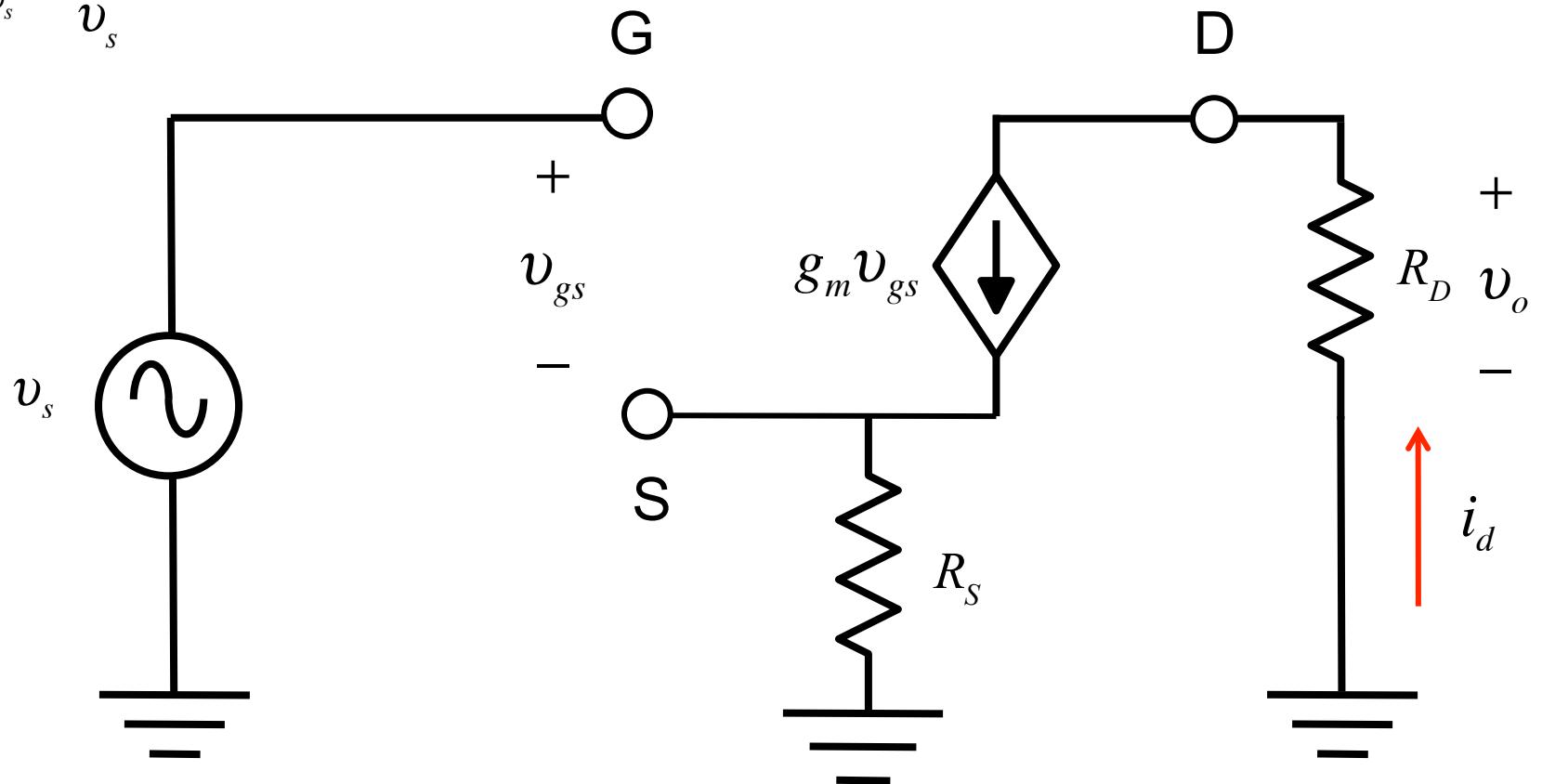

Result

$$A_{v_s} = \frac{v_o}{v_s}$$

$$A_{v_s} = -\frac{g_m R_D}{1 + g_m R_S}$$

$$|A_{v_s}| < g_m R_D$$

(negative
feedback from R_S)

$$g_m R_S \gg 1$$


$$A_{v_s} \rightarrow -\frac{R_D}{R_S}$$

(precision
amplifier)


Outline

- 1) Voltage transfer characteristic (MOSFET)
- 2) Small signal model (hybrid pi)
- 3) Small signal analysis
- 4) Small signal model (T-model)**


MOSFET hybrid pi model

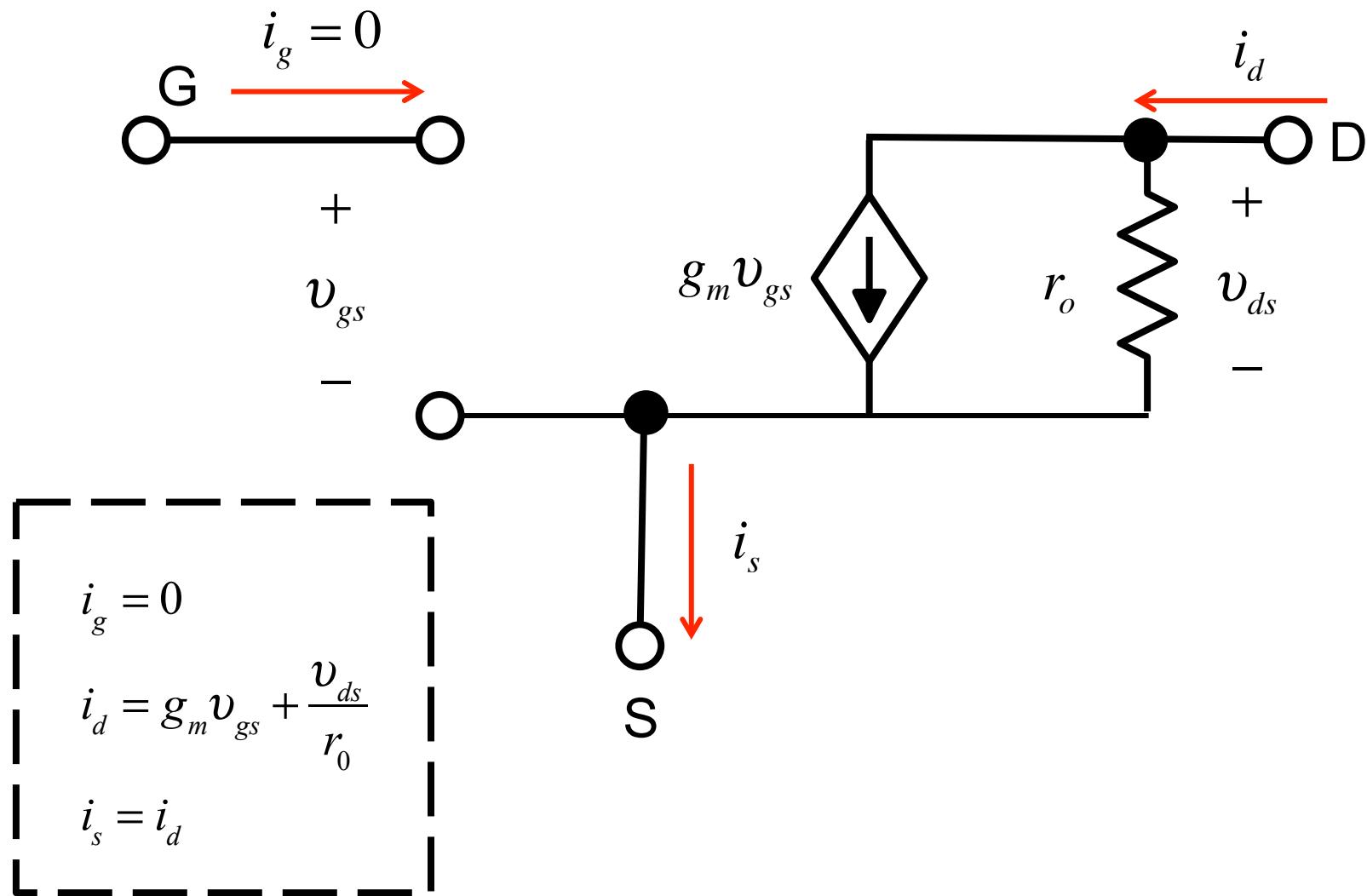

MOSFET T model

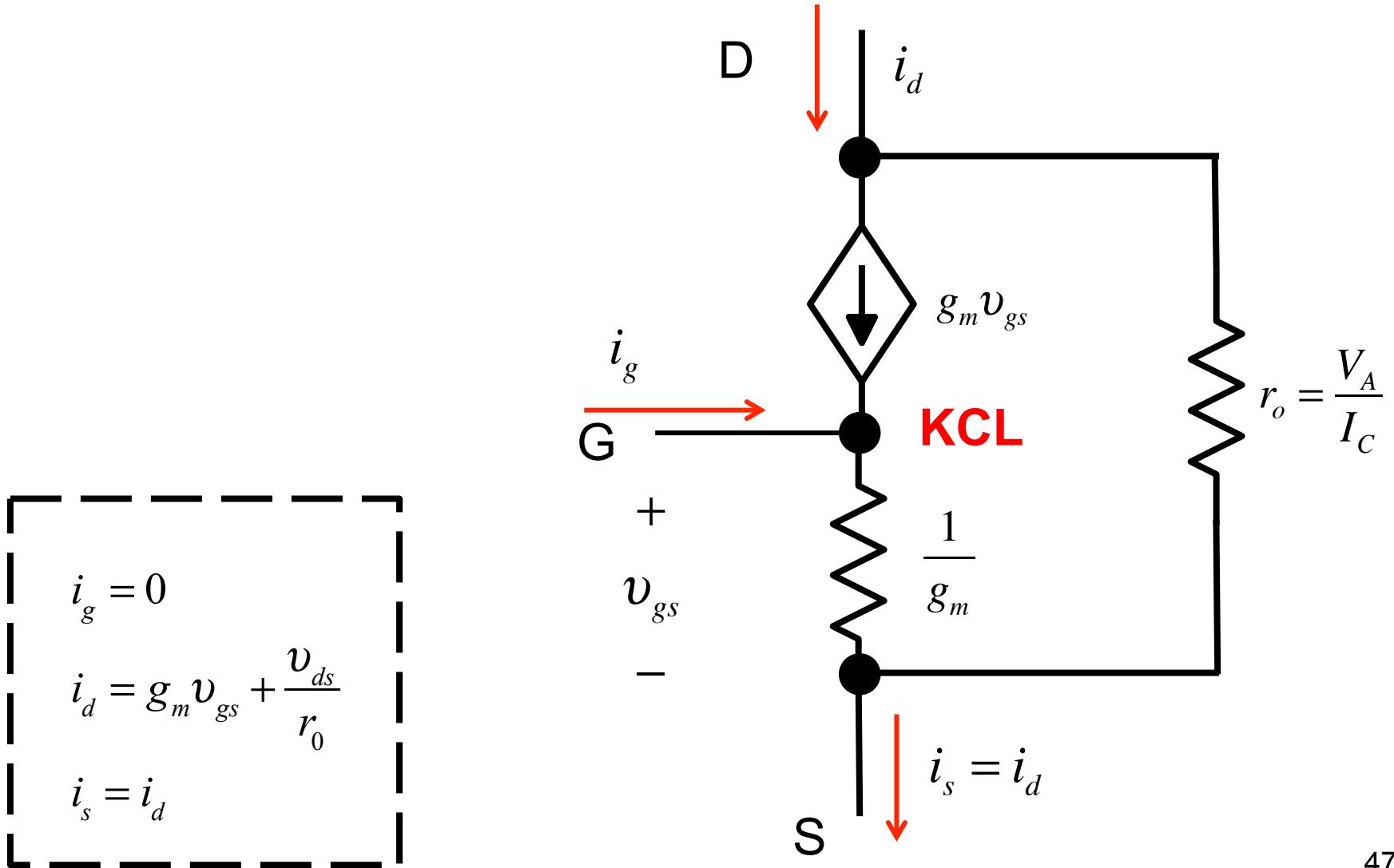

BJT T-Model

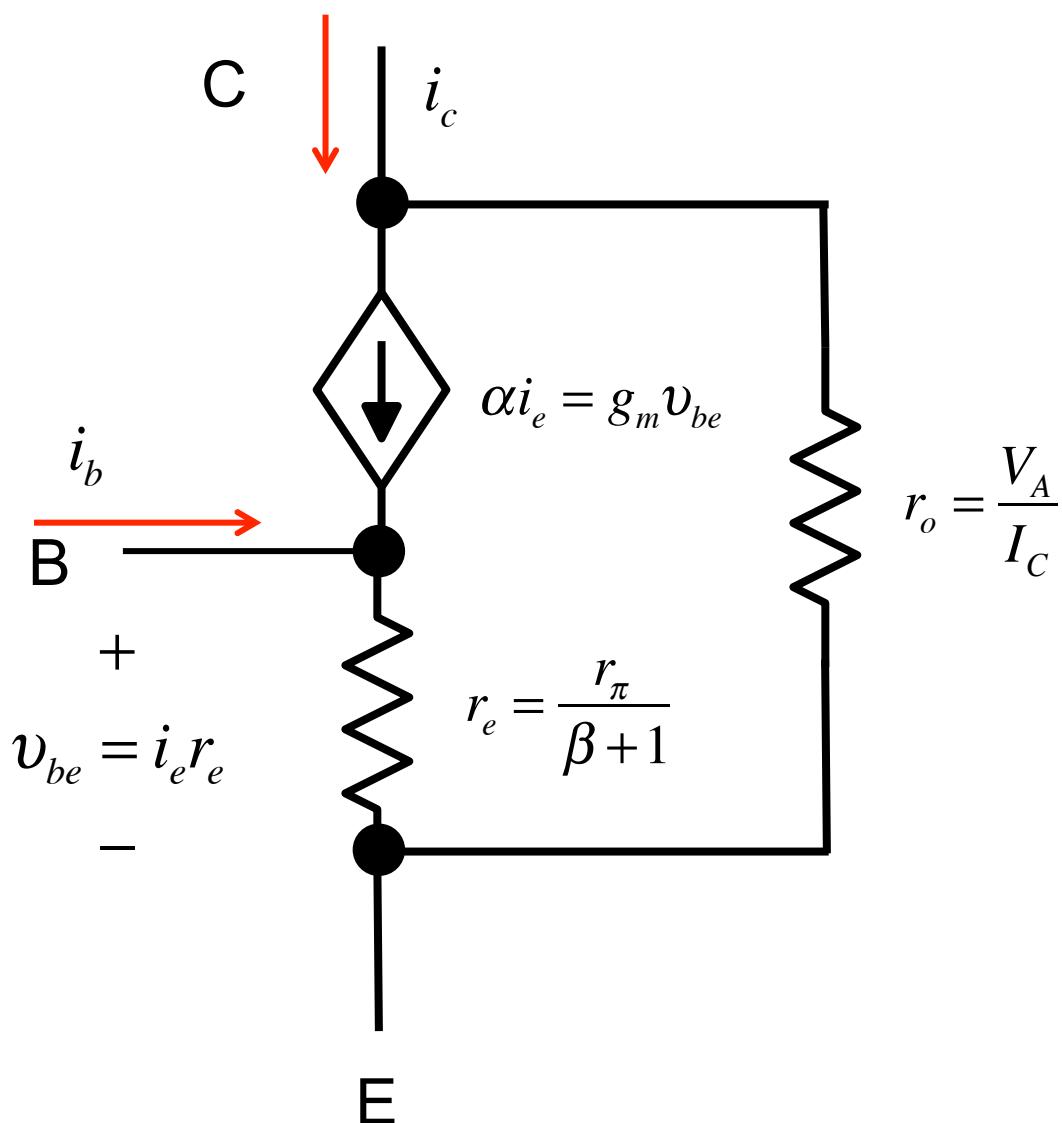


$$r_o = \frac{V_A}{I_C}$$

$i_b = v_{be}/r_\pi$
$i_c = g_m v_{be} + \frac{v_{ce}}{r_0}$
$i_e = i_b + i_c$

Exercise: Compute the voltage gain using the T model

$$A_{v_s} = \frac{v_o}{v_s}$$

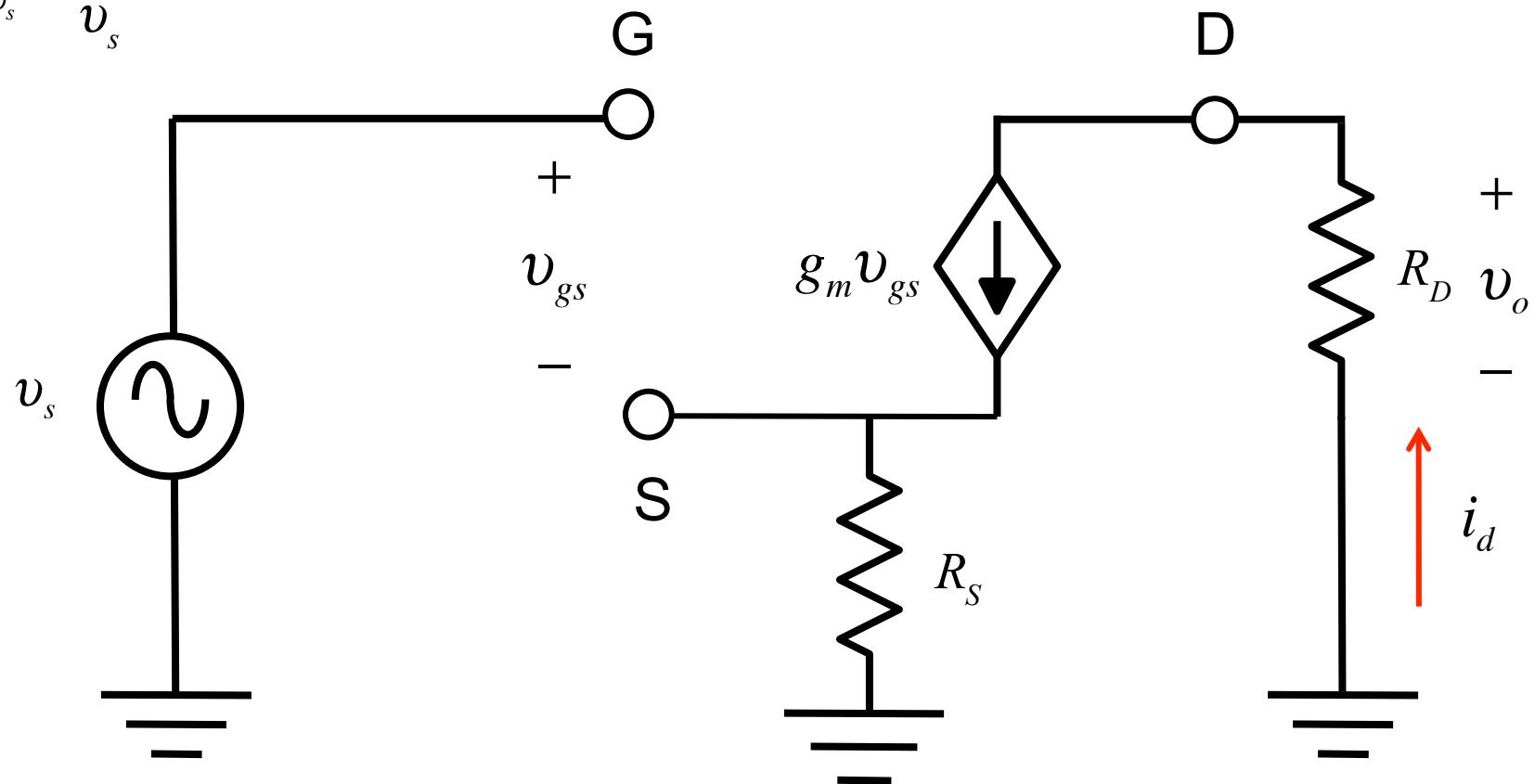

Summary

The Common Source MOSFET amplifier is much like the CE BJT amplifier.

The transconductance of a MOSFET is typically more than 10 times smaller than that of a BJT.

We will stick with the hybrid pi model for MOSFETs and BJTs, but the book also uses the T model from time to time.

MOS Transistor Amplifiers

- 1) Voltage transfer characteristic
- 2) Small signal model (hybrid pi)
- 3) Small signal analysis
- 4) Small signal model (T-model)

