

*Spring 2019 Purdue University*

# **ECE 255: L19**

## **Basic Amplifier Configurations**

(Sedra and Smith, 7<sup>th</sup> Ed., Sec. 7.3)

Mark Lundstrom  
School of ECE  
Purdue University  
West Lafayette, IN USA

# Announcements

---


- 1) LTspice Project 2 due Wed. Feb. 27th by 5:00PM electronically. You should find your assigned your beta value in your grade book.
- 2) HW6 due Monday 2/25 by 5:00 PM
- 3) Exam 2 is Tuesday, March 5, 6:30-7:30 PM PHYS 112

# Outline

---

- 1) T-model
- 2) Basic amplifier considerations
- 3) CE
- 4) CS

# Simple hybrid pi model

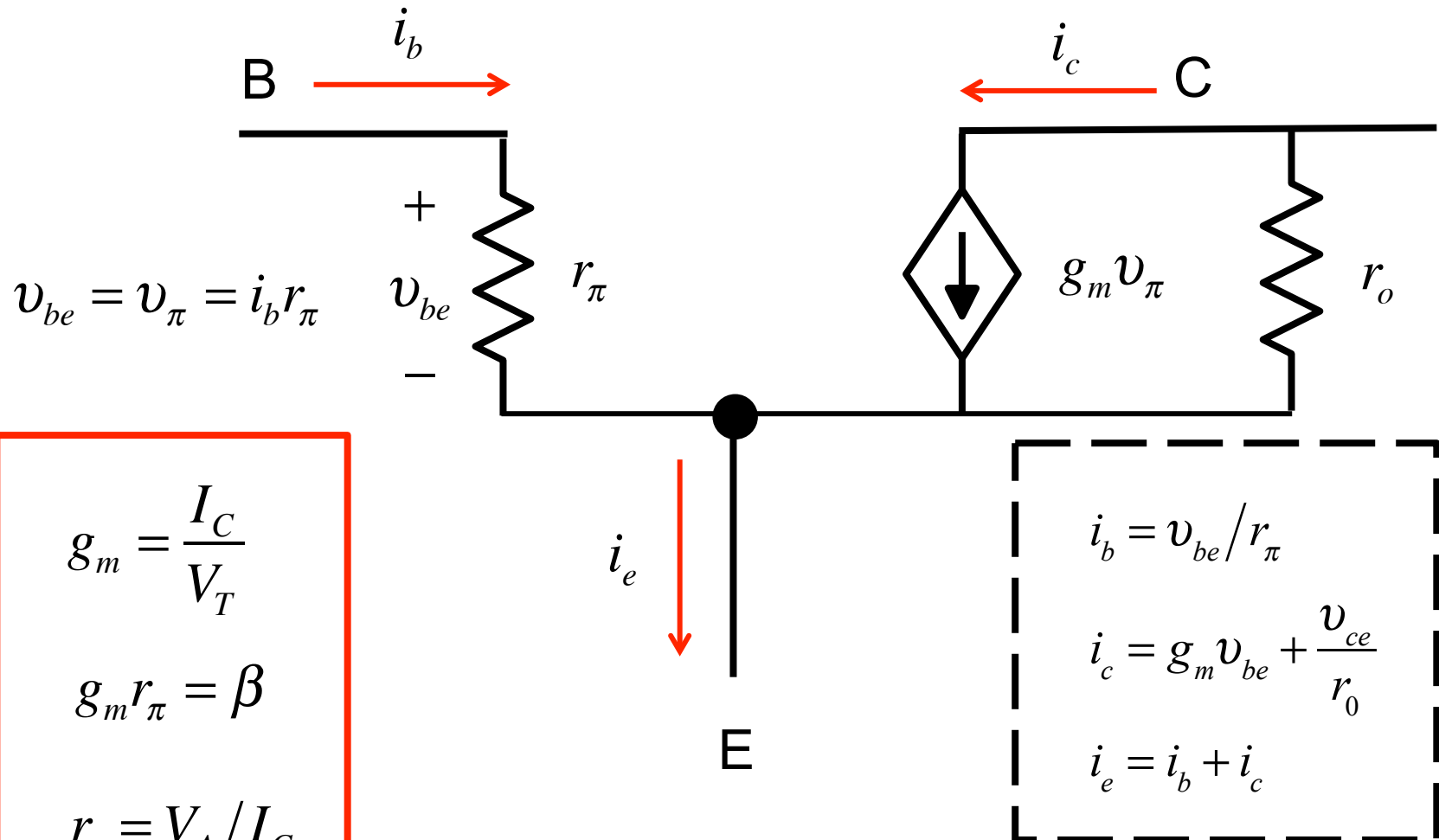


$$g_m = \frac{I_C}{V_T}$$

$$g_m r_{\pi} = \beta$$

$$r_o = V_A / I_C$$

# T-model...

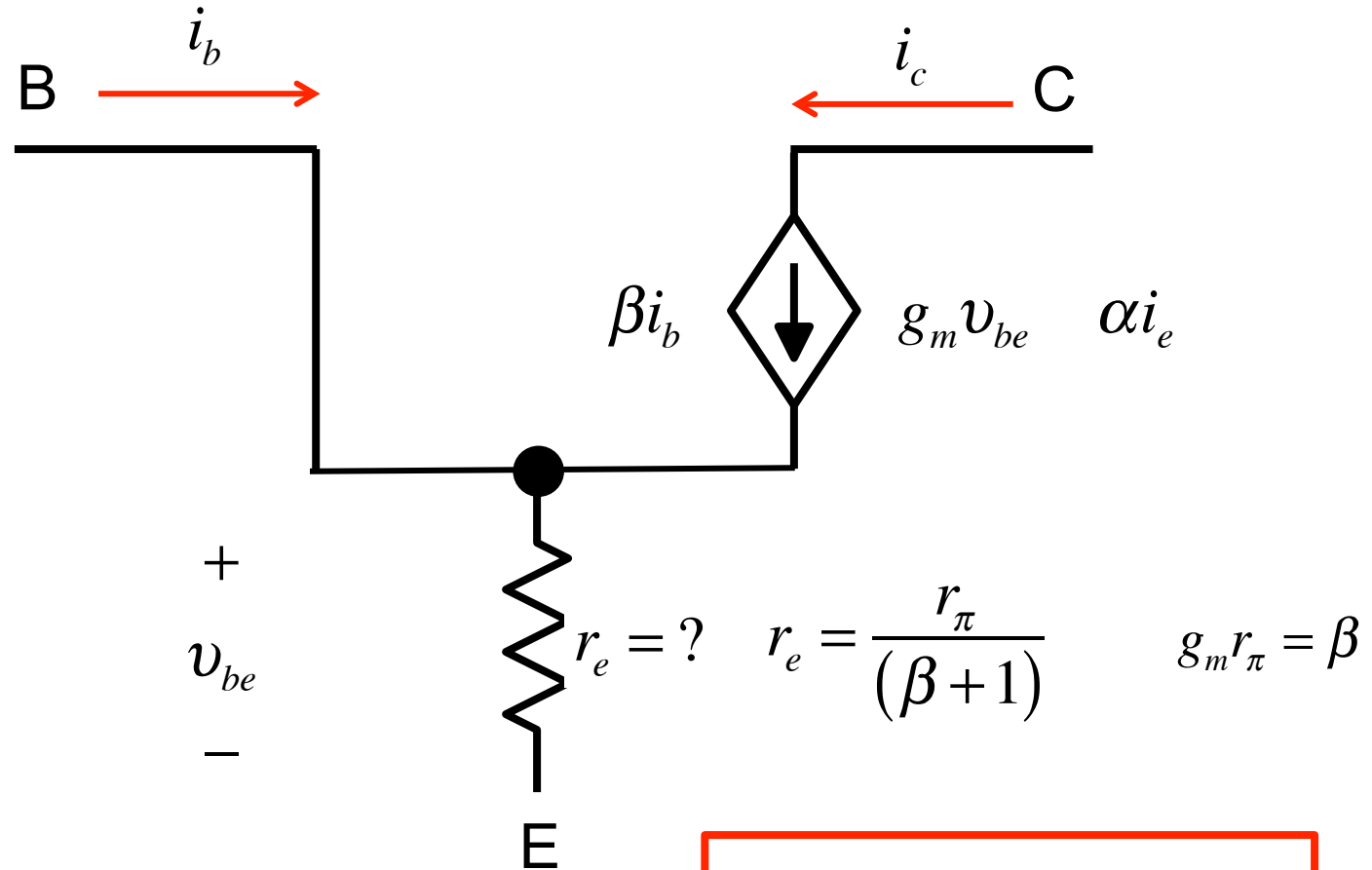

$$v_{be} = i_b r_\pi = (i_b + \beta i_b) r_e = i_b (\beta + 1) r_e$$

$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} \ll r_\pi$$

# The “T model” vs. hybrid -pi


$$i_b = v_{be} / r_\pi$$

$$i_c = g_m v_{be}$$

$$i_e = i_b + i_c$$

$$(\beta + 1)i_b = v_{be}(\beta + 1) / r_\pi$$

$$i_c = g_m i_e r_e = \alpha i_e$$

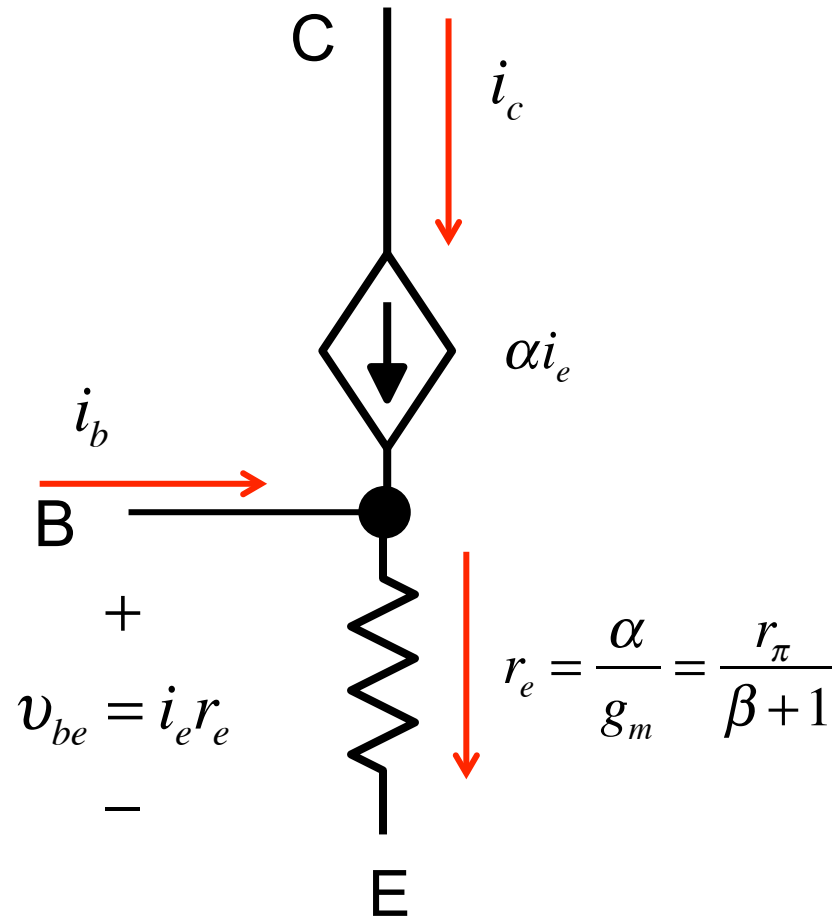

# The “T model” vs. hybrid -pi

$$I_C = 1.0 \text{ mA}$$

$$\beta = 100$$


$$g_m = \frac{I_C}{V_T} = 39 \text{ mS}$$

$$g_m r_\pi = \beta$$

$$r_\pi = \frac{\beta}{g_m} = 2.6 \text{ k}\Omega$$

$$\alpha = \frac{\beta}{\beta + 1} = 0.99$$
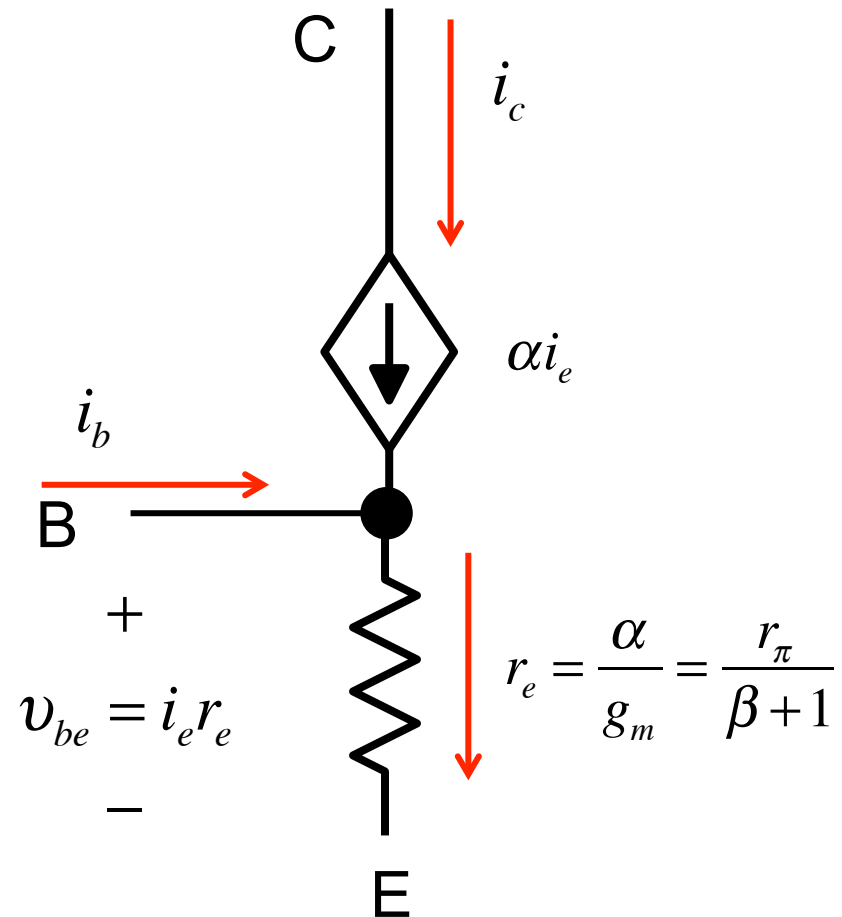
$$r_e = \frac{\alpha}{g_m} = \frac{0.99}{39 \times 10^{-3}} = 25 \text{ }\Omega$$



# Outline

---

- 1) T-model
- 2) Basic amplifier considerations**
- 3) CE
- 4) CS



# Generic Amplifier (2-port)


---



Transistors have 3 terminals, so one must be **common** between the input and output.


# Common emitter

---

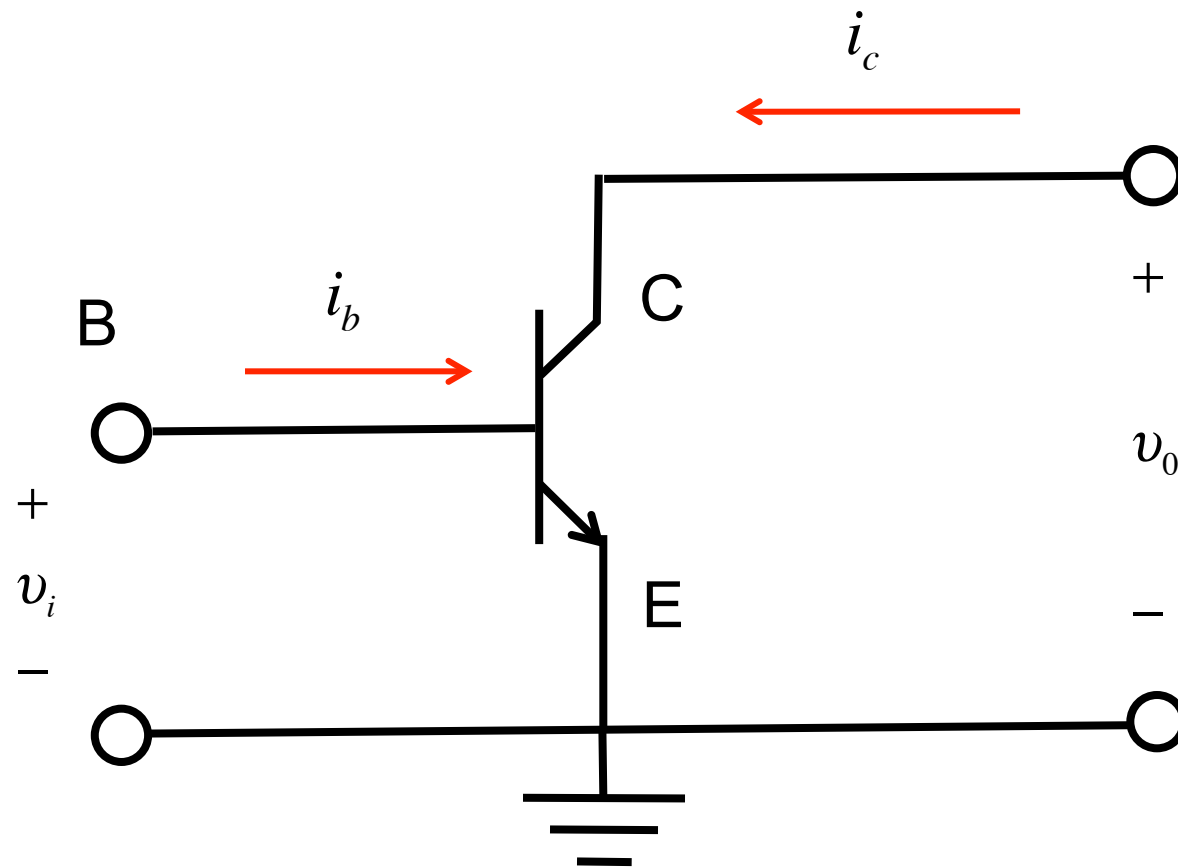


# Common base

---

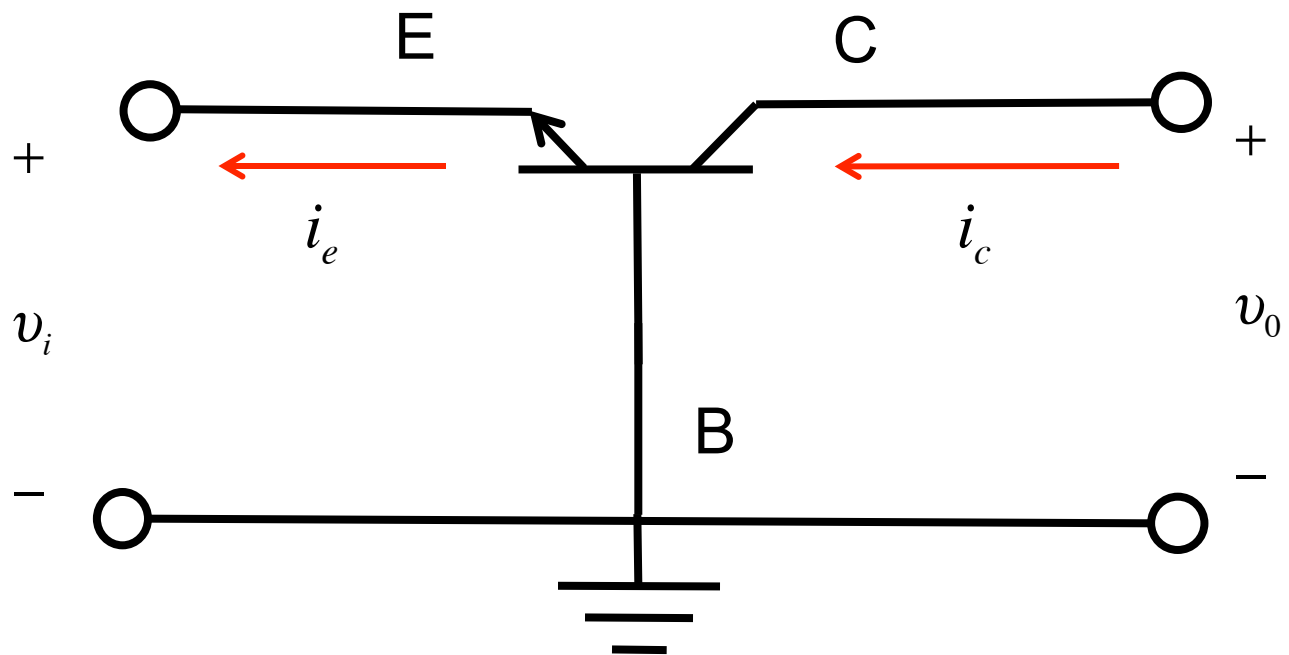


## Also common base

---

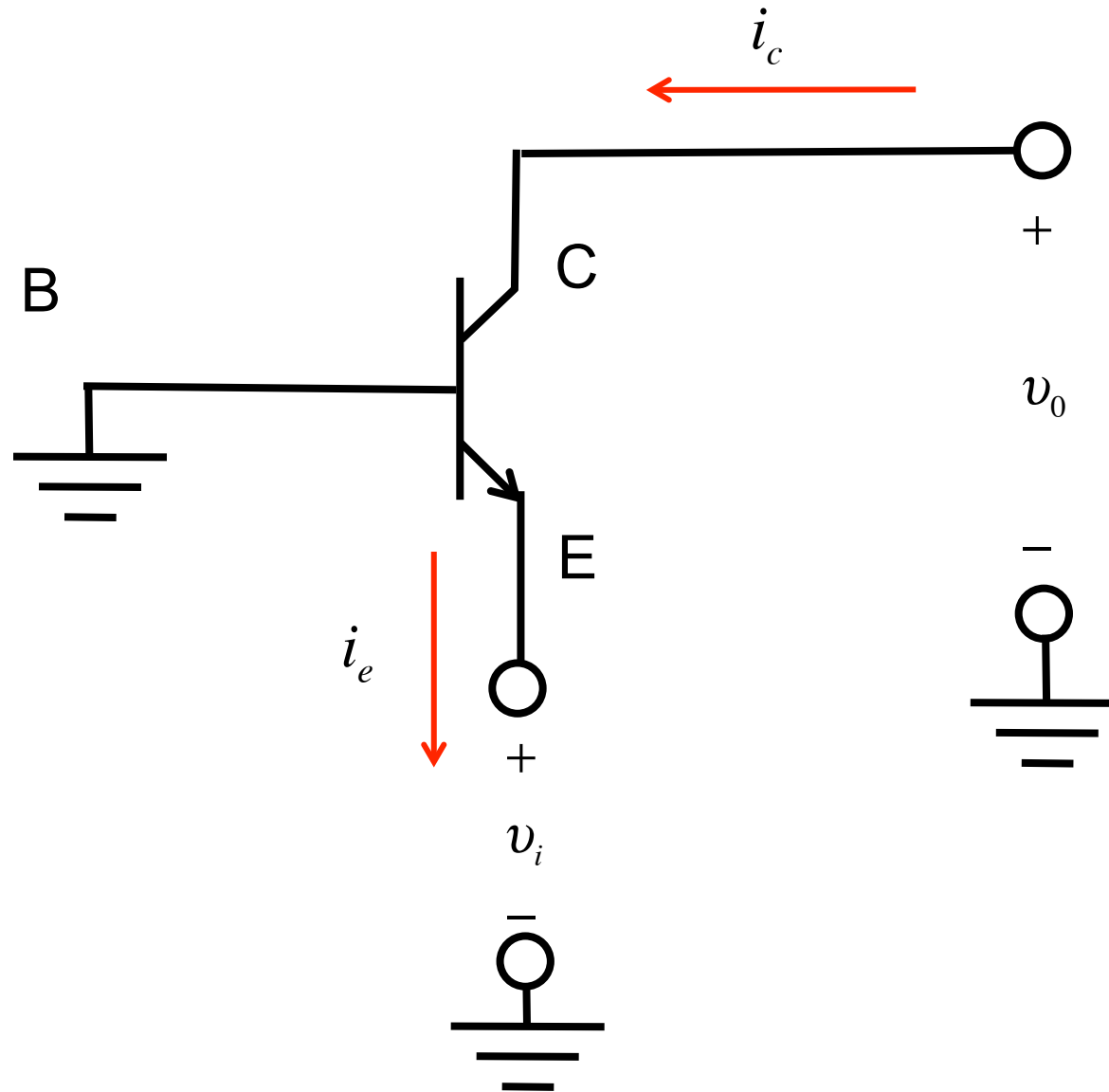


# Common collector

---

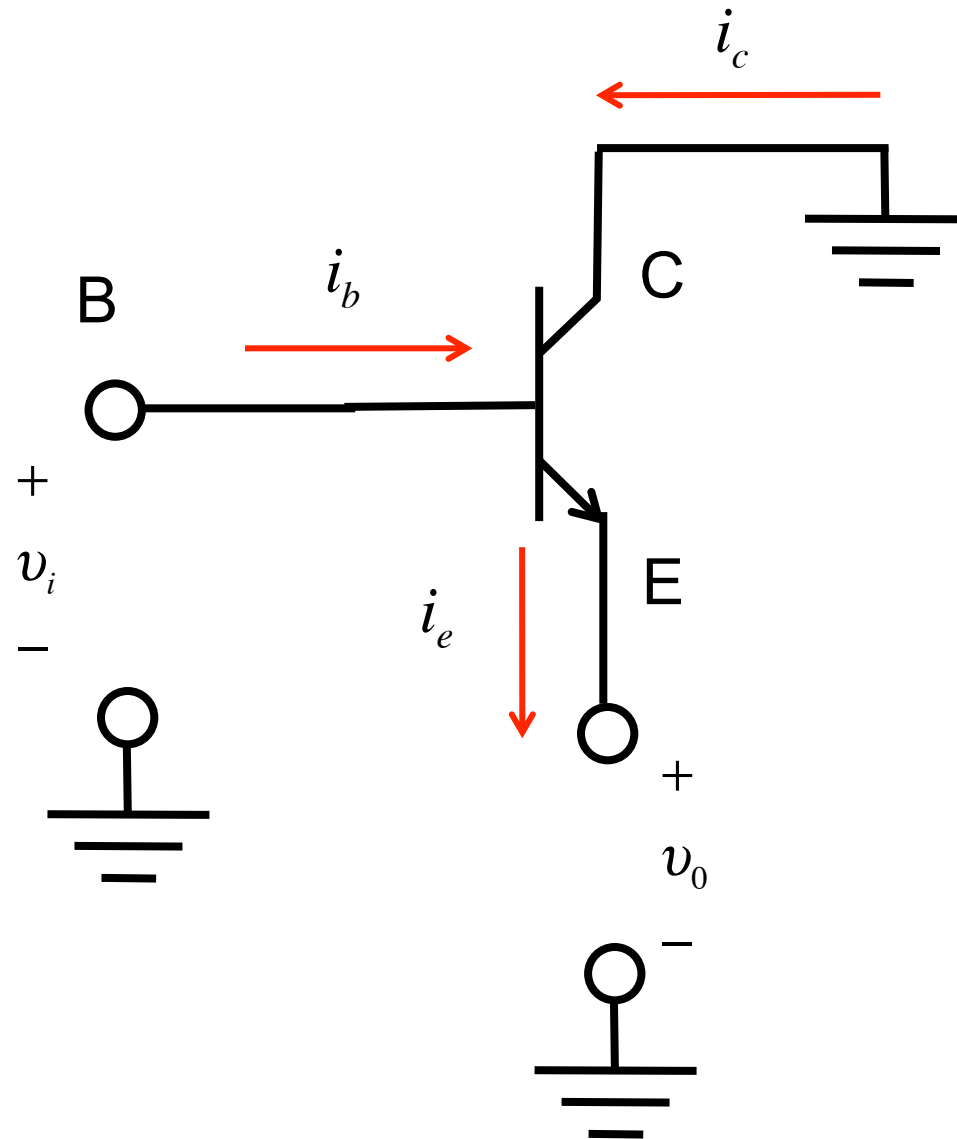

# Amplifier model


---

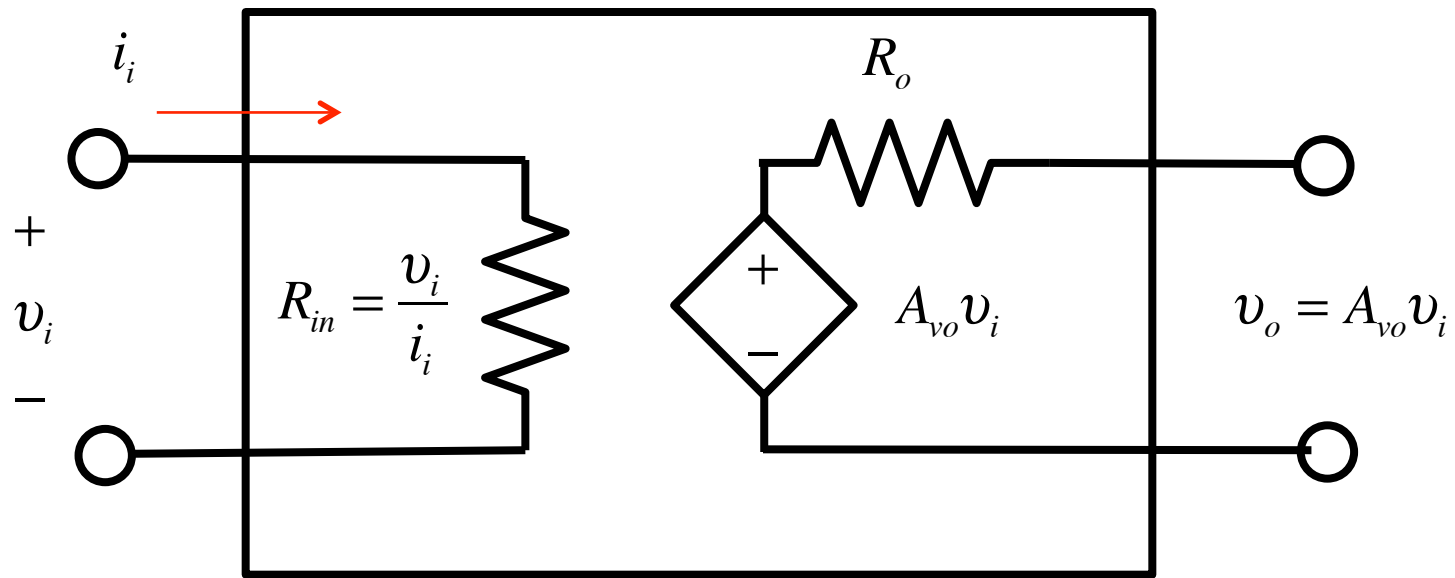


Open circuit voltage gain  $A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$
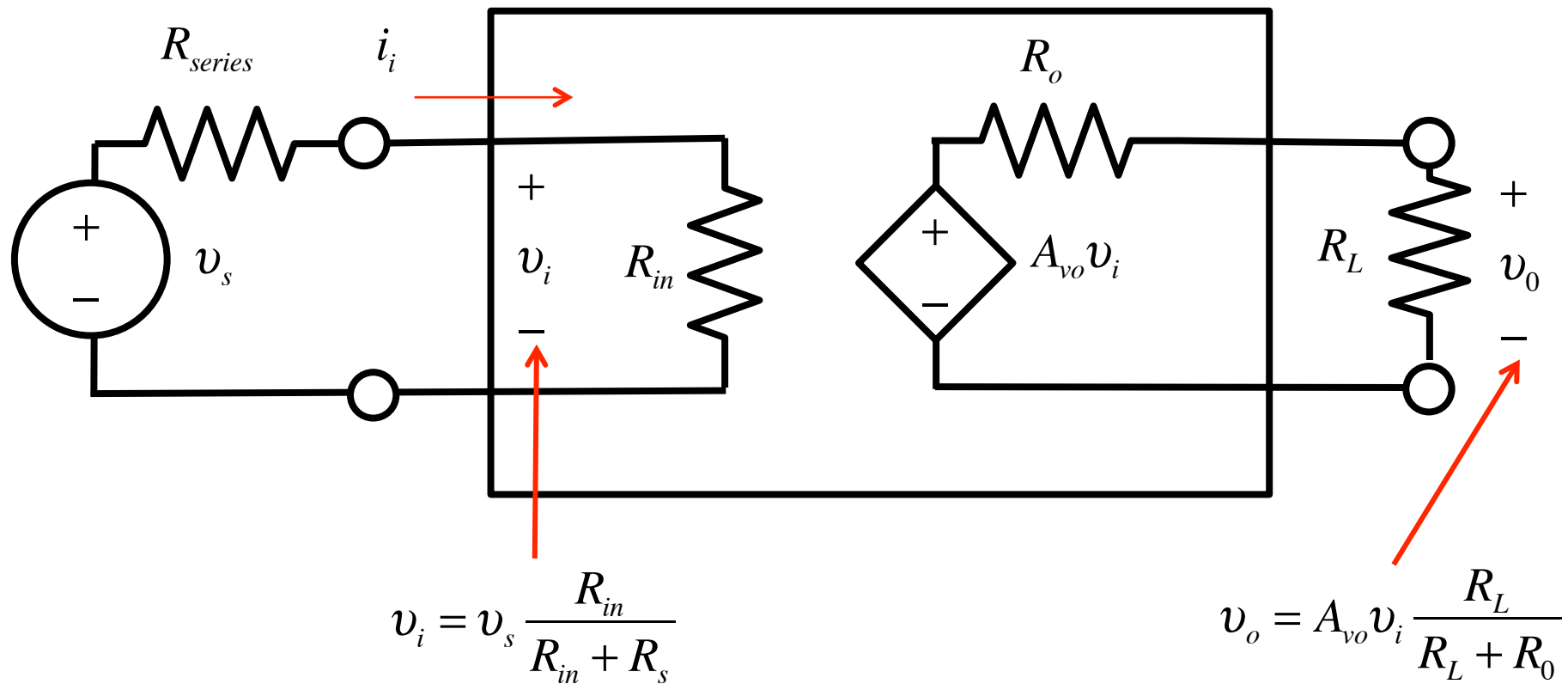
# Amplifier with source and load

$$G_v = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_s} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$



# Amplifier with source and load

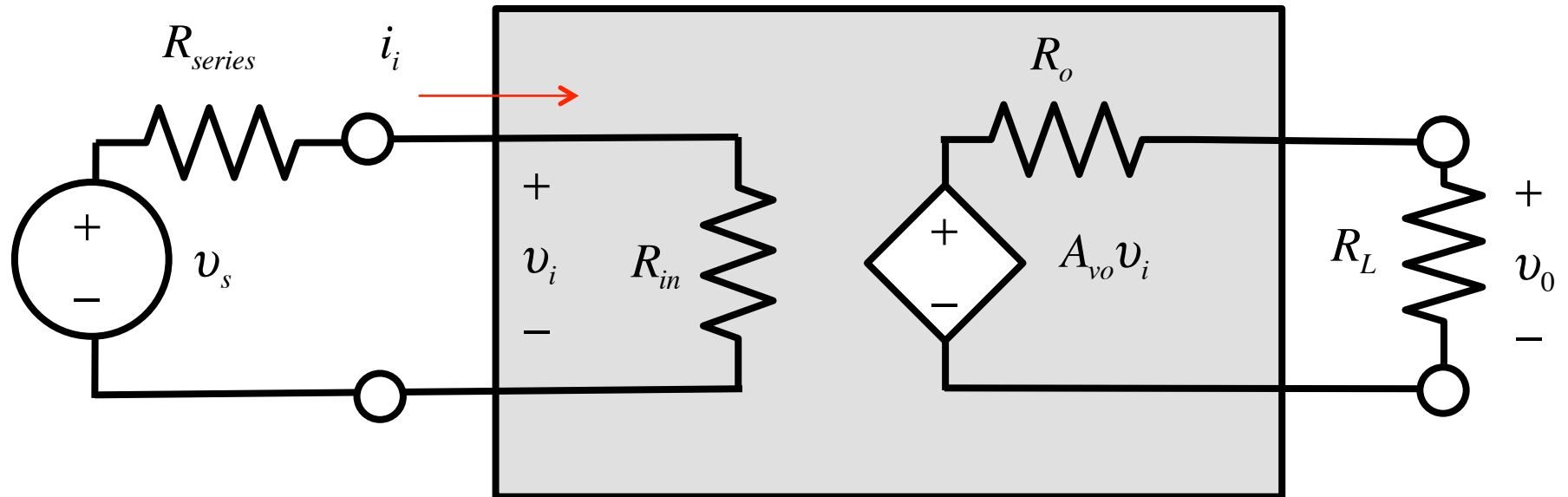

$$G_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{v_i/R_{in}} = A_{vo} \frac{R_{in}}{R_L}$$

$$G_p = \frac{p_o}{p_i} = \frac{v_o i_o}{v_s i_i} = G_v G_i$$




# Outline

---

- 1) T-model
- 2) Basic amplifier considerations
- 3) **CE**
- 4) CS

# Common emitter

---

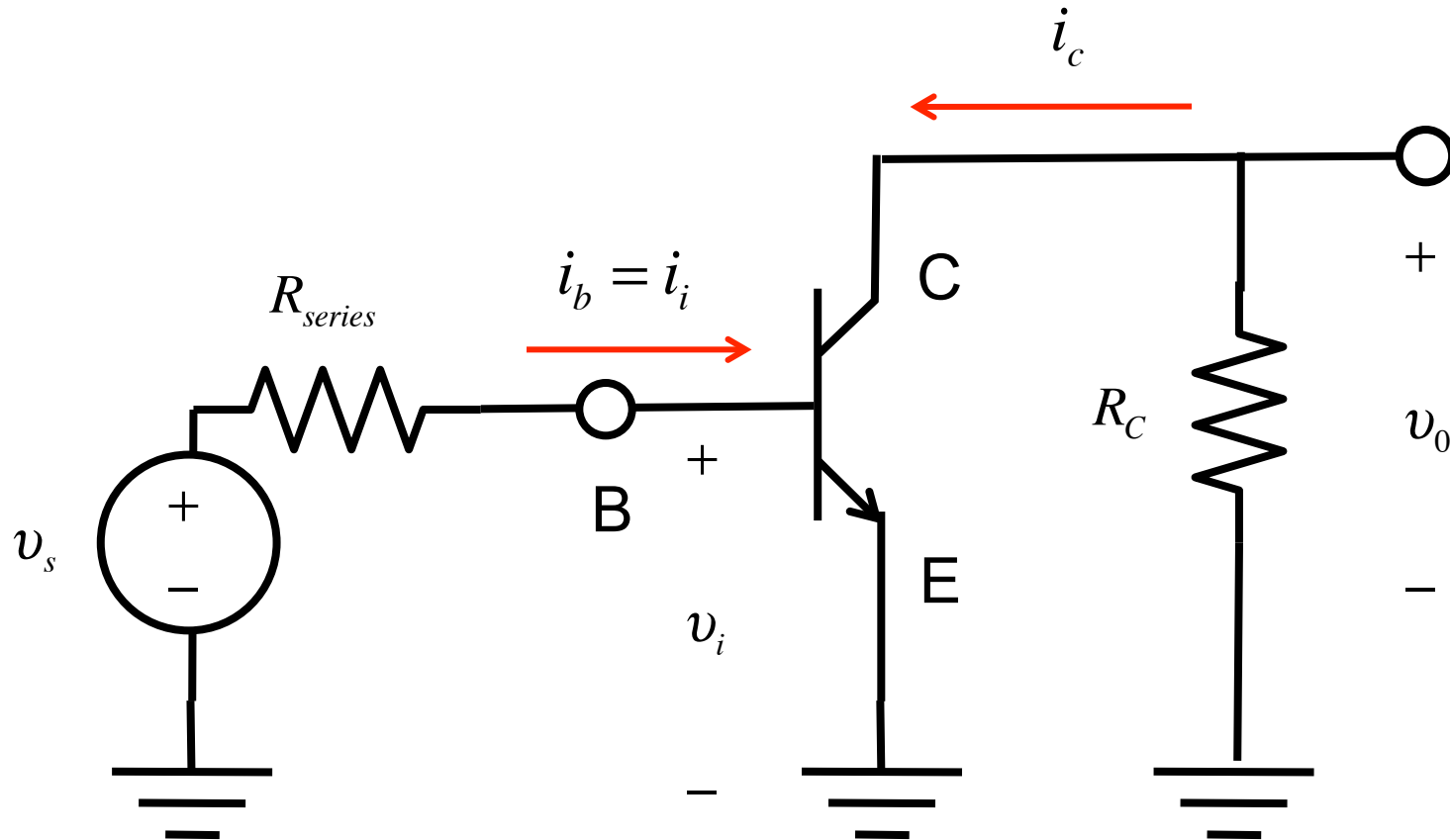


Draw the common emitter s.s. equiv. ckt.

---

# Common emitter s.s. equiv. ckt.

---

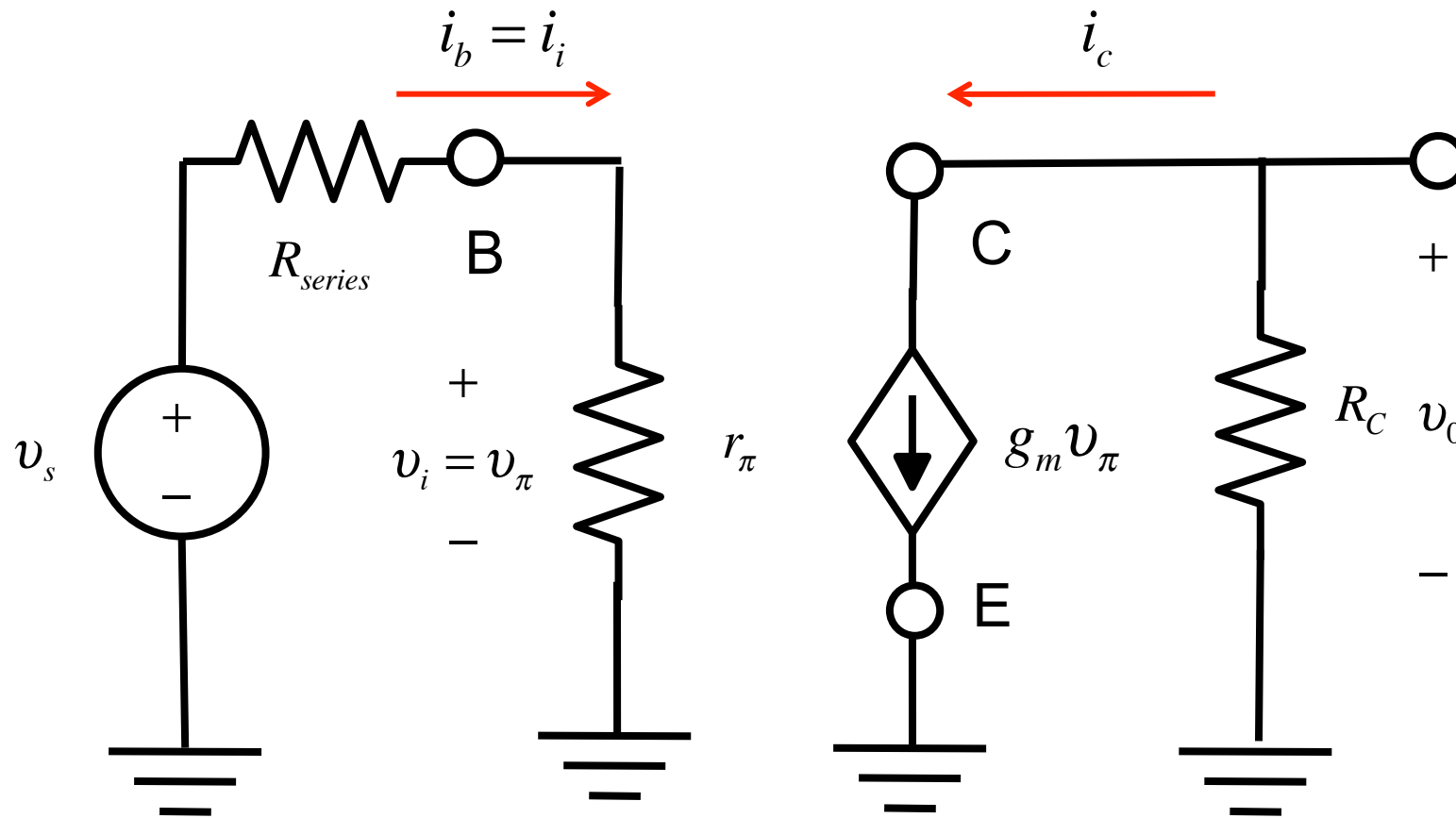

# Common emitter analysis

---

$$A_{v_o} = \frac{v_o}{v_i}$$

$$R_{in} = \frac{v_i}{i_i}$$

$$R_o = \frac{v_o}{i_o}$$

# Common emitter analysis

---

$$v_o = -g_m v_\pi R_C = -g_m v_i R_C$$

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_C$$

open circuit voltage gain

$$R_{in} = r_\pi$$

**Effect of  $r_o$ ?**

$$R_o = R_C$$


$$A_v = -g_m (R_C \parallel R_L)$$

with load attached

$$G_v = \frac{v_o}{v_s} = \frac{v_i}{v_s} \frac{v_o}{v_i} = - \left( \frac{r_\pi}{r_\pi + R_S} \right) g_m (R_C \parallel R_L)$$

# Common emitter

---

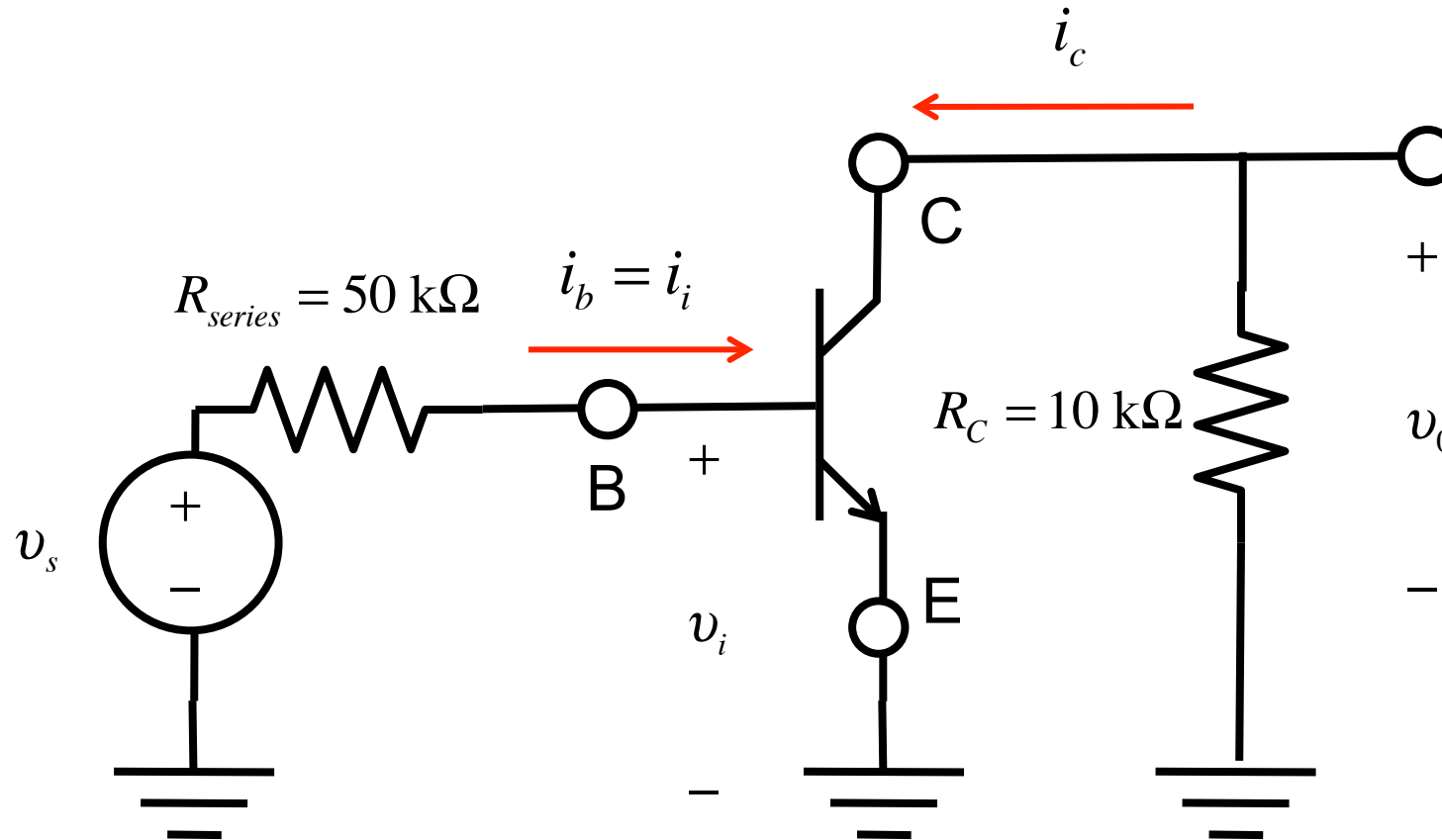

$$I_C = 1 \text{ mA}$$

$$\beta = 100$$

$$kT/q = 0.026 \text{ V}$$

$$V_A = 100 \text{ V}$$

## Common emitter results

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_C$$

$$R_{in} = r_\pi$$

$$R_o = R_C$$

$$A_v = -g_m (R_C \parallel R_L)$$

$$G_v = \frac{v_o}{v_s} = -\left(\frac{r_\pi}{r_\pi + R_S}\right) g_m (R_C \parallel R_L)$$

$(R_L = 5 \text{ k}\Omega)$

$$I_C = 1.0 \text{ mA}$$

$$g_m = I_C / V_T = 39 \text{ mS}$$

$$g_m r_\pi = \beta$$

$$r_\pi = \beta / g_m = 2.6 \text{ k}\Omega$$

$$R_{in} = 2.6 \text{ k}\Omega$$

$$R_o = 10 \text{ k}\Omega$$


$$A_{v_o} = -g_m R_C = -390$$

$$G_v = -\left(\frac{2.6}{2.6 + 50}\right) 39(10 \parallel 5) = -6.4$$


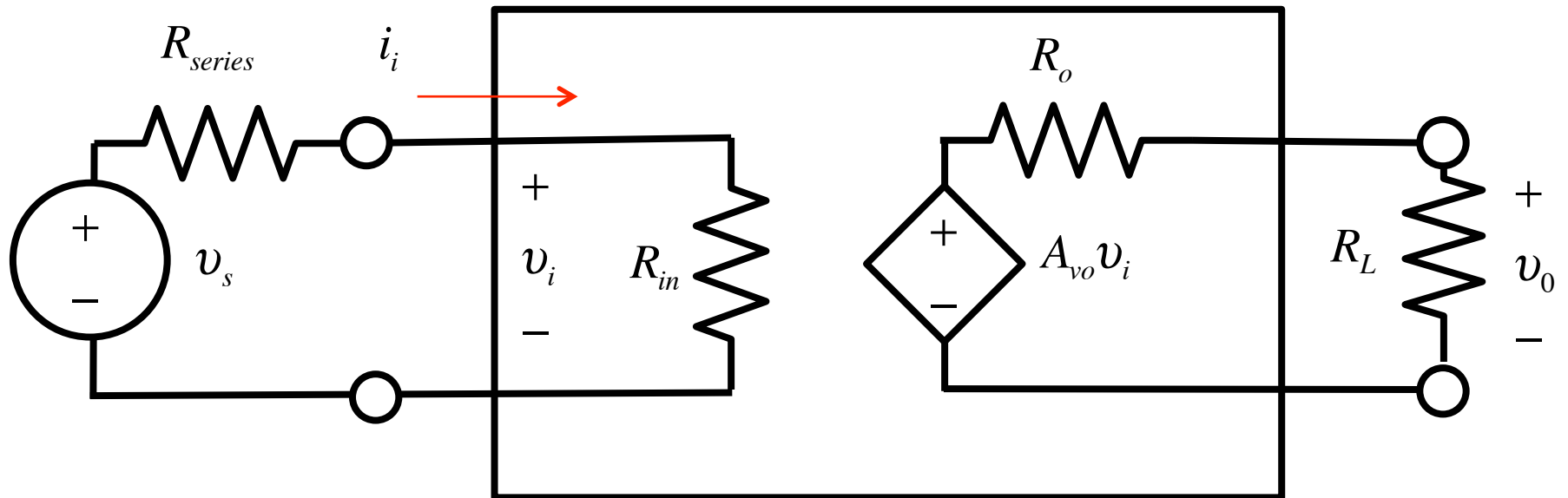
## Alternatively

$$G_v = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_s} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$




$$R_{in} = r_{\pi}$$

$$A_{vo} = \frac{v_o}{v_i} = -g_m R_C$$

$$R_o = R_C$$

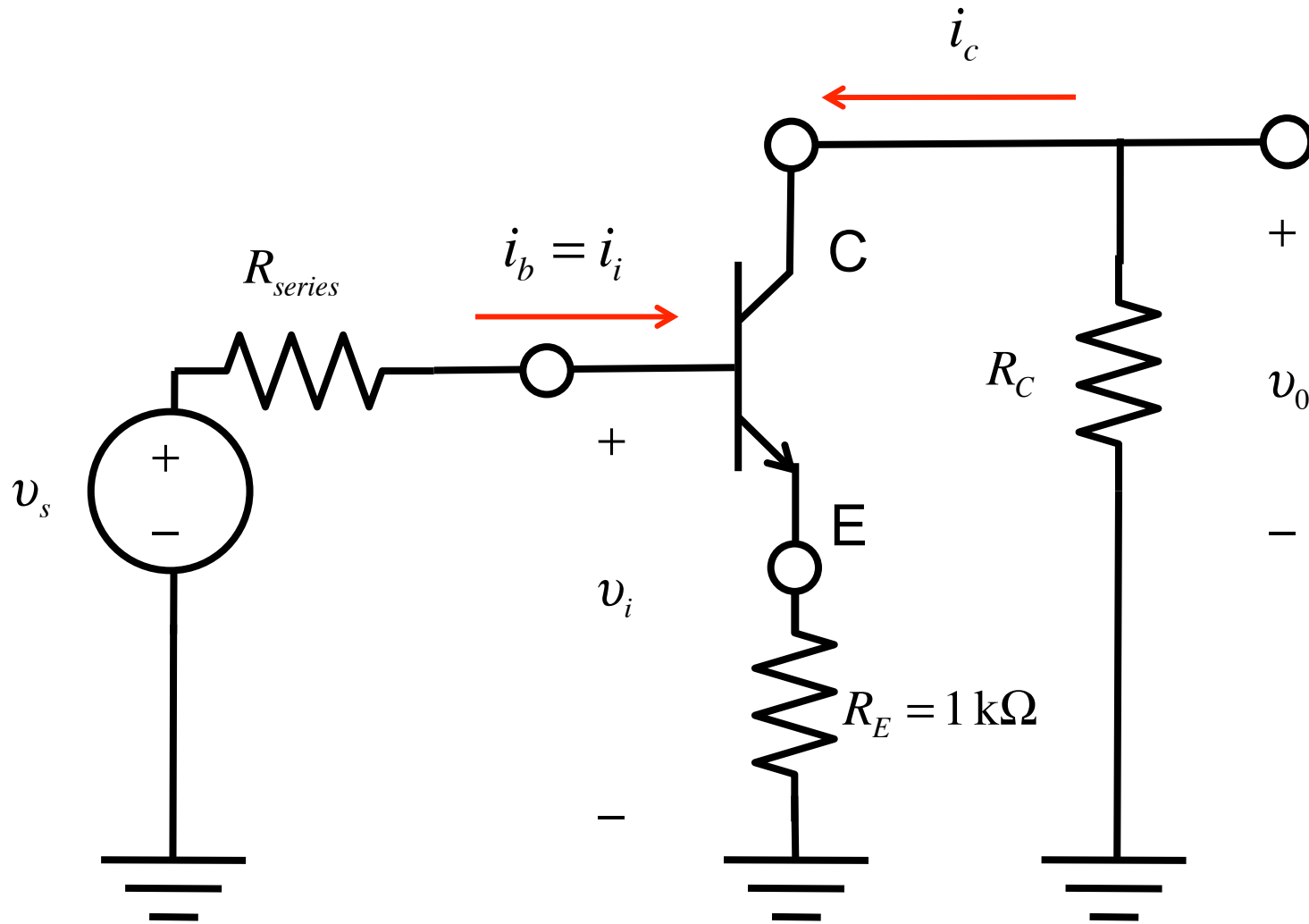
# Common emitter with “emitter degeneration”



Draw the small signal equiv. ckt.

---

# Small signal equiv. ckt.

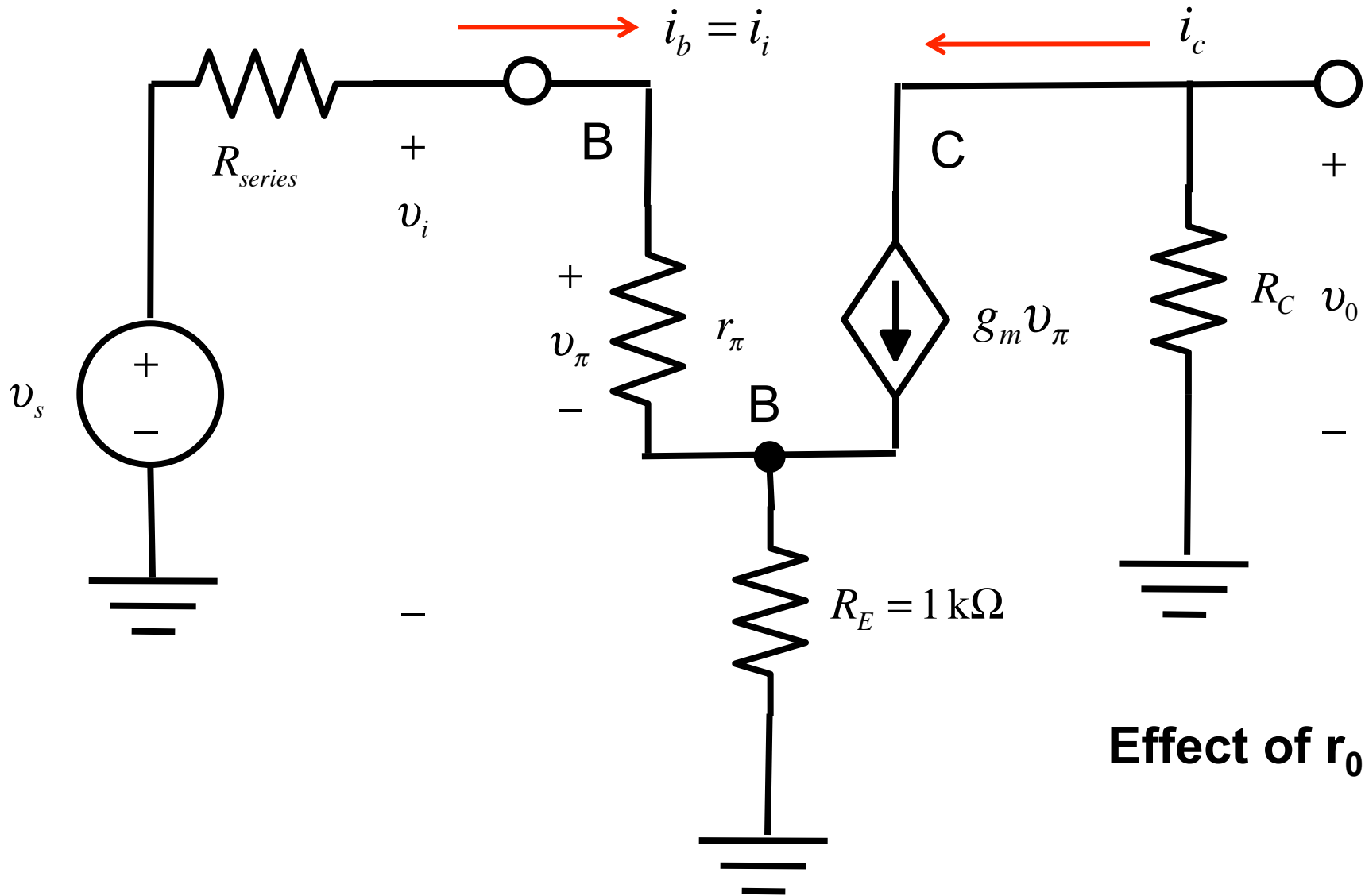

**Effect of  $r_o$ ?**

# Analysis

---

$$v_o = -g_m v_\pi R_C$$

$$v_i = v_\pi + v_{R_E}$$

$$v_i = v_\pi + (i_b + \beta i_b) R_E$$


$$v_i = v_\pi + (\beta + 1) \frac{v_\pi}{r_\pi} R_E$$

$$v_i = \frac{v_\pi}{r_\pi} (r_\pi + (\beta + 1) R_E)$$

$$v_\pi = v_i \frac{r_\pi}{r_\pi + (\beta + 1) R_E}$$

Do you see how to get this  
“by inspection”?


# “resistance reflection rule”

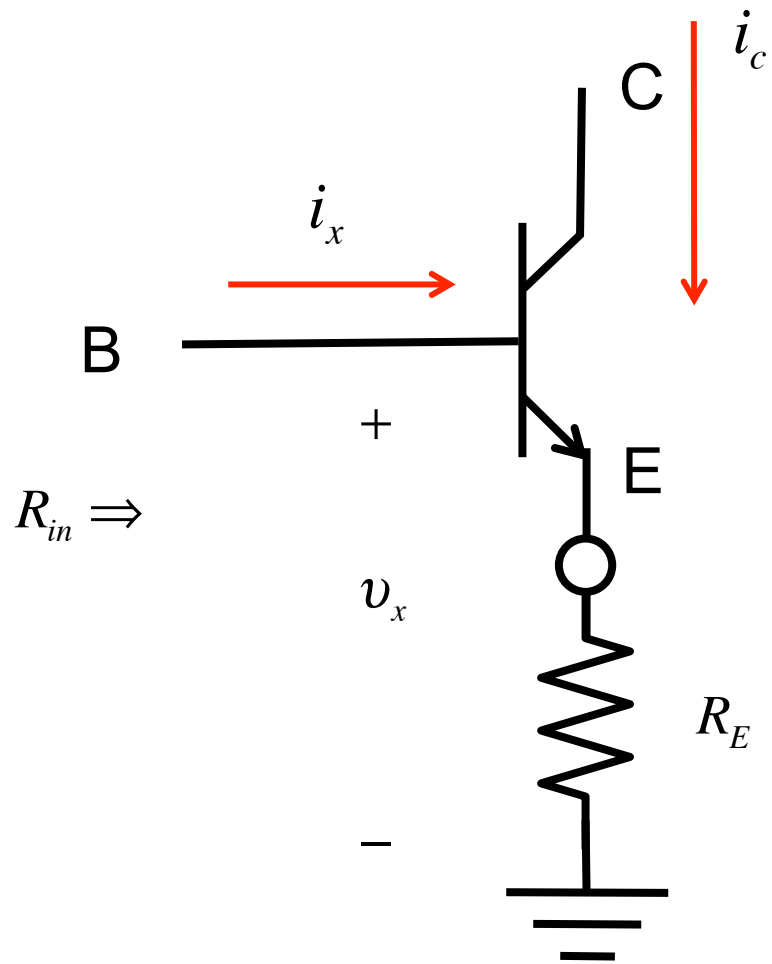

$$R_{in} = r_{\pi} + (\beta + 1)R_E$$

# V pi in terms of input voltage

---

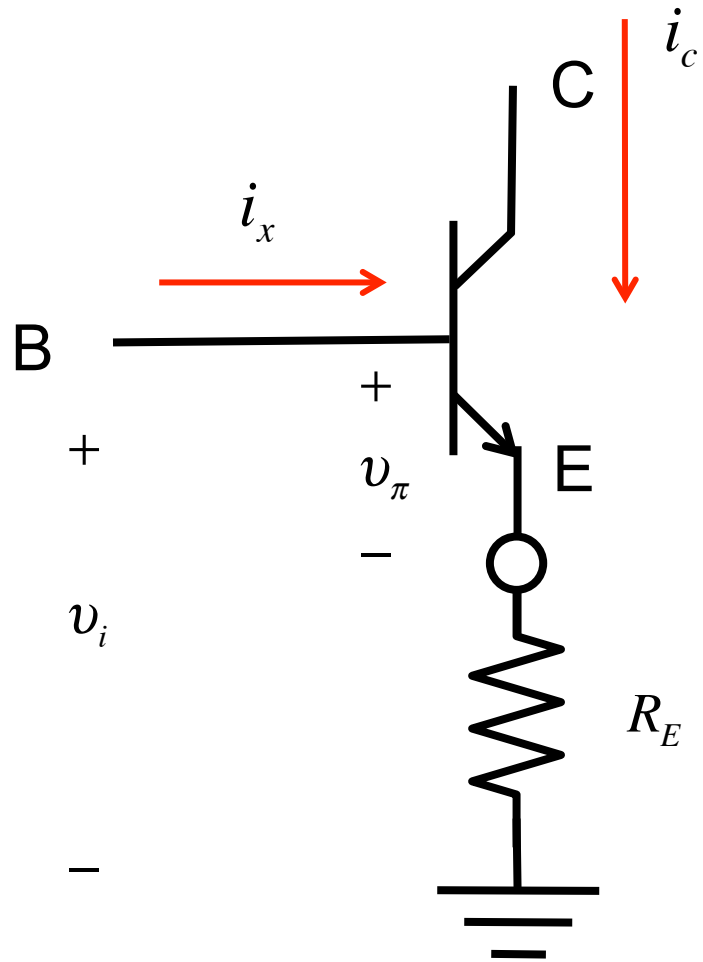

$$v_\pi = \frac{r_\pi}{r_\pi + (\beta + 1)R_E} v_i$$

# Common emitter with emitter resistor

$$v_o = -g_m v_\pi R_C$$

$$v_\pi = v_i \frac{r_\pi}{r_\pi + (\beta + 1)R_E}$$

$$A_{v_o} = -\frac{r_\pi}{r_\pi + (\beta + 1)R_E} (g_m R_C)$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_o = R_C$$

$$A_{v_o} = \frac{2.6}{2.6 + (101)1} (-390) = -9.8$$

$$(R_E = 0 : A_{v_o} = -390)$$

$$R_{in} = 2.6 + (101)1 = 103.6 \text{ k}\Omega$$

$$(R_E = 0 : R_{in} = 2.6 \text{ k}\Omega)$$

$$R_o = 10 \text{ k}\Omega$$

$$(R_E = 0 : R_o = 10 \text{ k}\Omega)$$



## “Precision amplifier”

---

$$A_{v_o} = \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C)$$

If:

$$(\beta + 1)R_E \gg r_\pi$$

$$A_{v_o} \approx -\frac{g_m r_\pi}{(\beta + 1)R_E} R_C = \frac{\beta}{(\beta + 1)} \left( -\frac{R_C}{R_E} \right)$$

$$A_{v_o} \approx -\frac{R_C}{R_E}$$

$$A_{v_o} \approx -\frac{10}{1} = -10$$

## CE with “emitter degeneration” summary

---

$$A_{v_o} = \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C) \approx -\frac{R_C}{R_E}$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_o = R_C$$

**Physical reason:**

Negative feedback

**Effect of  $R_L$ ?**


Compared to the  $R_E = 0$  case:

Lower voltage gain


Higher input resistance

Same output resistance

# Negative feedback

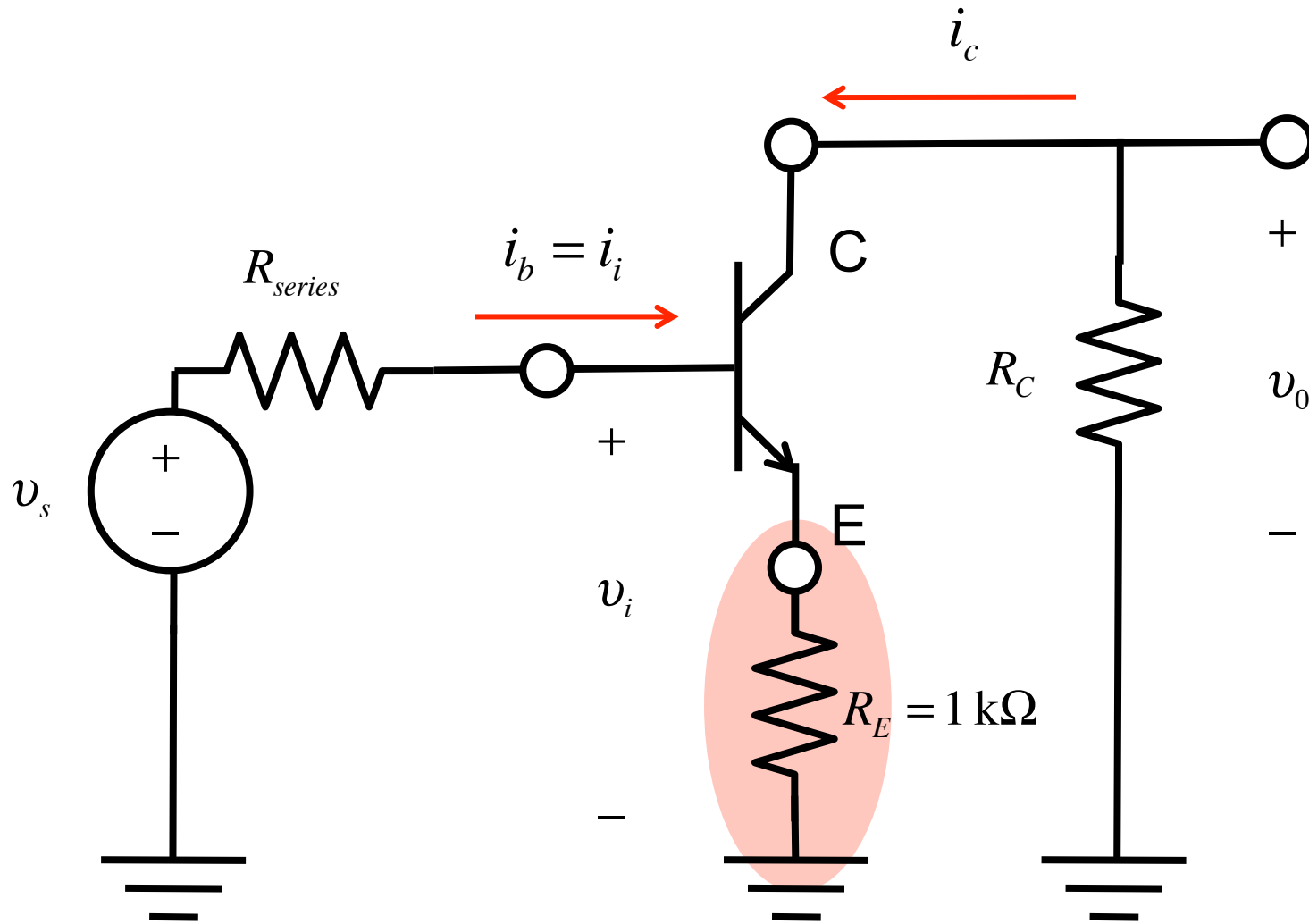

# Common source

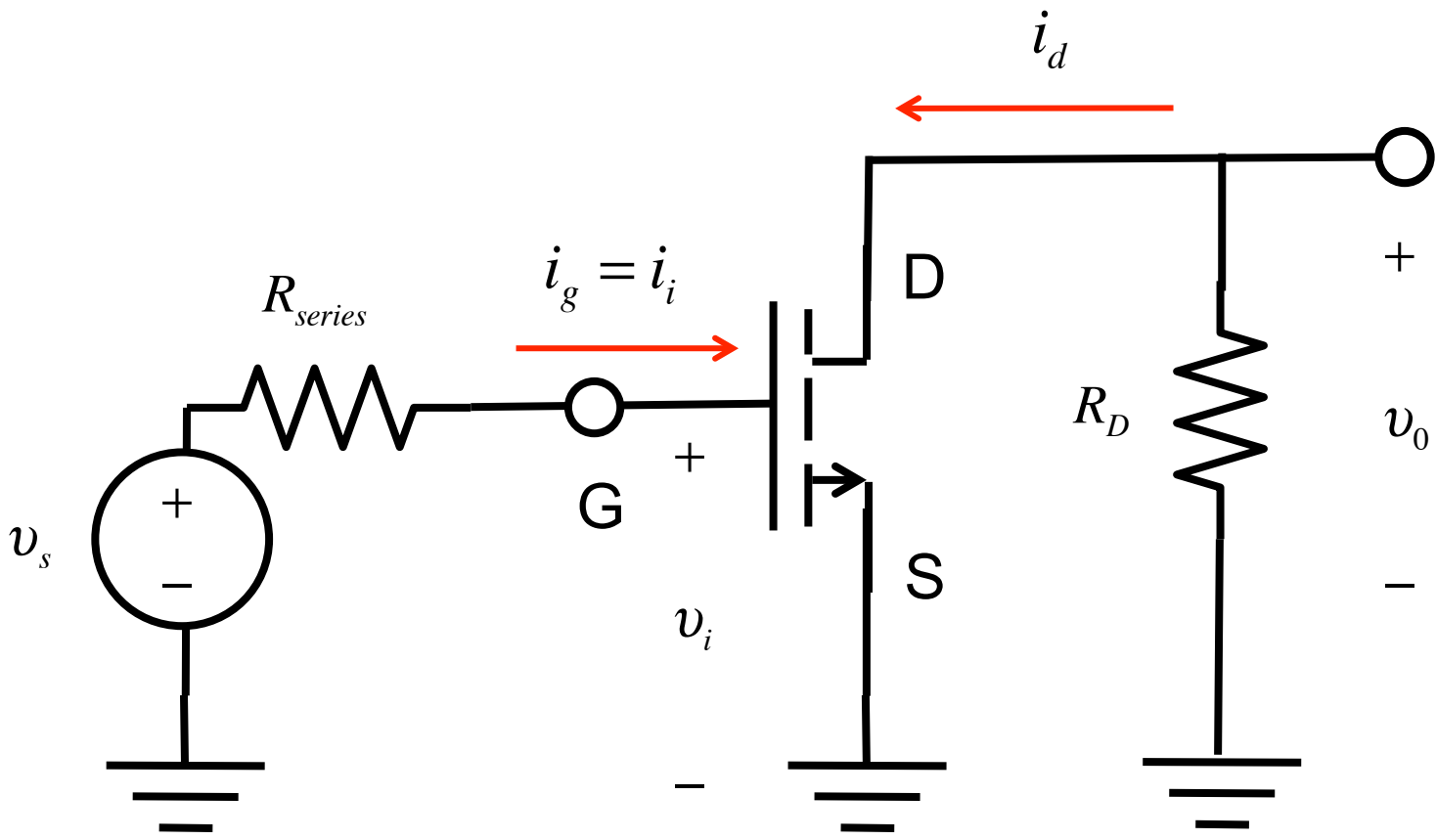

# CE vs. CS

---

## Common Emitter

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_C$$

$$R_{in} = r_\pi$$

$$R_o = R_C$$


## Common Source

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_D$$

$$R_{in} = \infty$$

$$R_o = R_D$$

# Common source with source degeneration

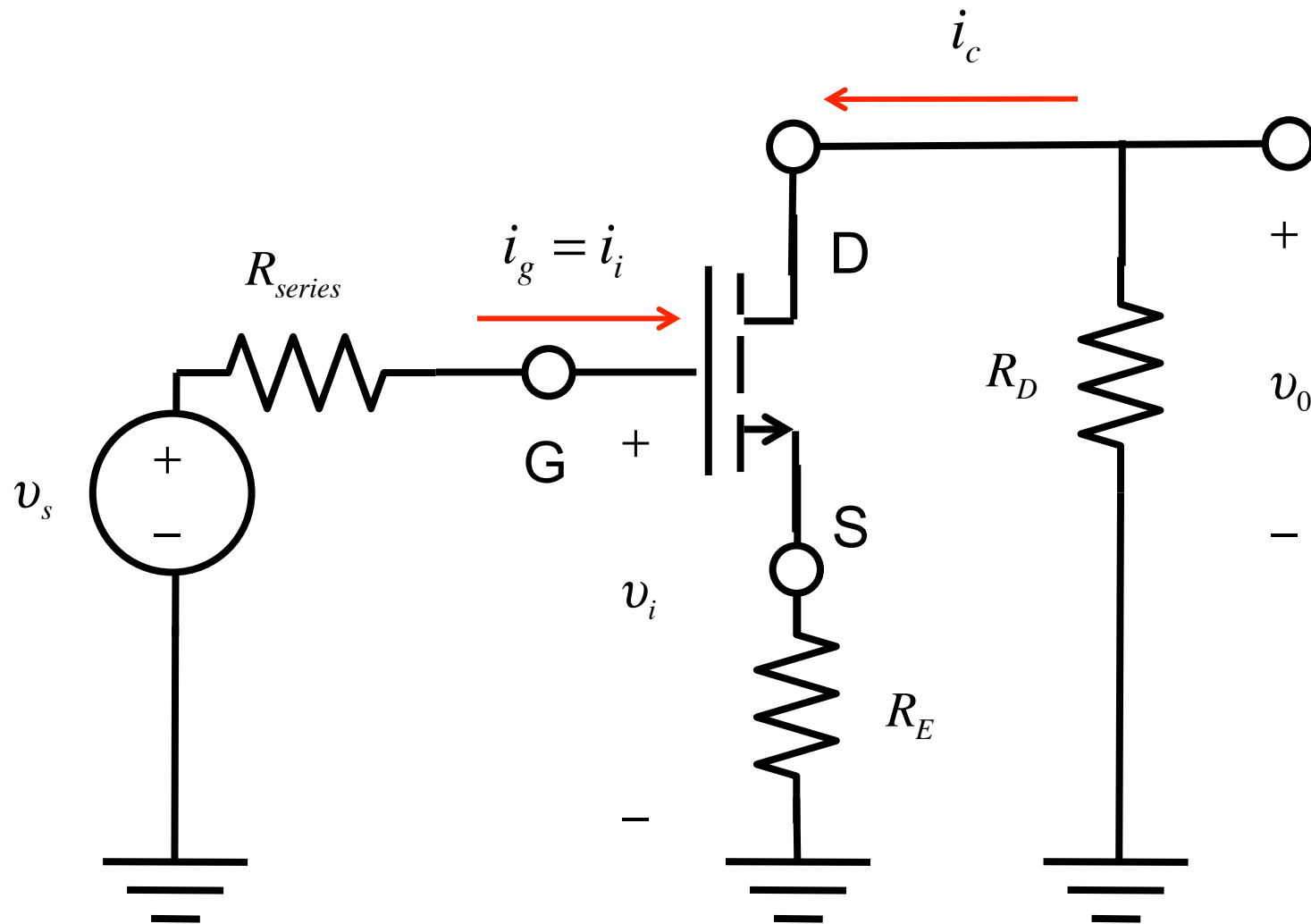

# CE vs. CS with emitter/source degeneration

---

Common Emitter

Common Source

$$A_{v_o} = \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C)$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_o = R_C$$

# CE vs. CS with emitter/source degeneration

---

## Common Emitter

$$A_{v_o} = \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C)$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_o = R_C$$

## Common Source

$$A_{v_o} = \frac{1}{1 + \frac{(\beta + 1)R_S}{r_\pi}} (-g_m R_D)$$

$$g_m r_\pi = \beta$$

$$A_{v_o} = \frac{1}{1 + g_m R_S} (-g_m R_D)$$

$$R_{in} = \infty$$

$$R_o = R_D$$



# Summary

---

Amplifiers are characterized in terms of their open-circuit voltage gain, input resistance, and output resistance.

The CE amplifier has high (negative) gain, moderate input impedance and moderate output resistance.

Emitter degeneration ( $R_E > 0$ ) lowers the gain but increases the input impedance.

The CS amplifier has moderate (negative) gain, high input impedance and moderate output resistance.

# Basic Amplifier Configurations

---

- 1) T-model
- 2) Basic amplifier considerations
- 3) CE
- 4) CS

