

*Spring 2019 Purdue University*

# ECE 255: L20

## Basic Amplifier Configurations: II

(Sedra and Smith, 7<sup>th</sup> Ed., Sec. 7.3)

Mark Lundstrom  
School of ECE  
Purdue University  
West Lafayette, IN USA

Lundstrom: 2019

**PURDUE**  
UNIVERSITY

## Announcements

---

- 1) There is no HW due Monday, but HW7 (Practice Problems for Exam 2) will be discussed in class on Monday.
- 2) Exam 2 is Tuesday, March 5, 6:30-7:30 PM PHYS 112
- 3) Professor Janes will hold a help session on Tuesday in ME 1061 at 1:30 PM.
- 4) No class on Friday, March 8




# Announcements

---




For Exam 2, you should be prepared on: (HW5- HW7)

- 1) DC analysis / design of 4-resistor bias circuit
- 2) Small signal models
- 3) Reducing a circuit diagram to a s.s. equiv. circuit
- 3) Amplifier configurations
- 4) CE and CS in detail

# Three basic BJT amplifiers

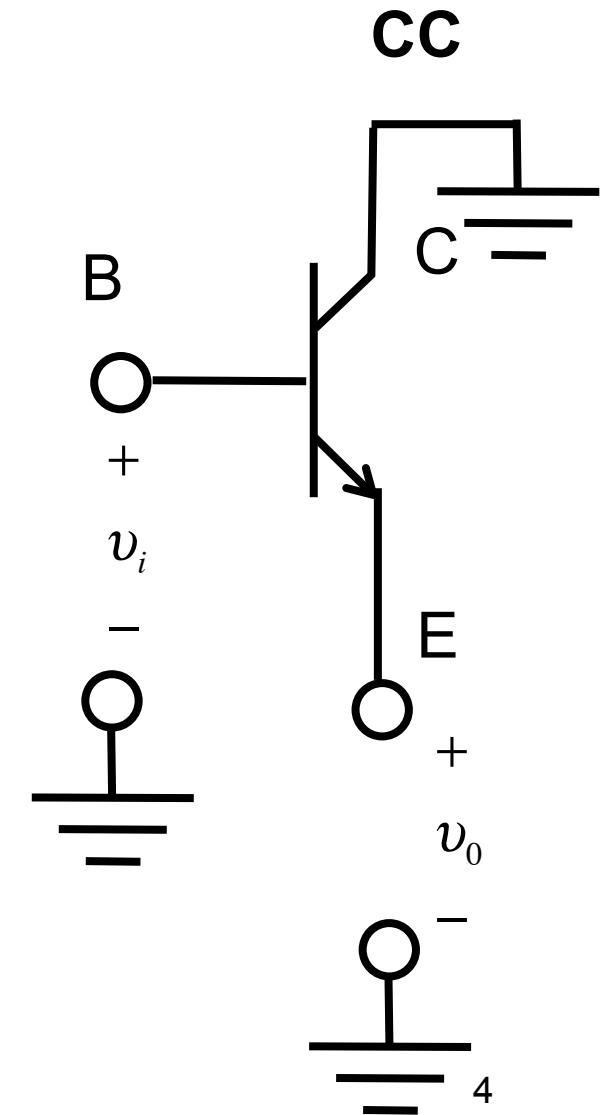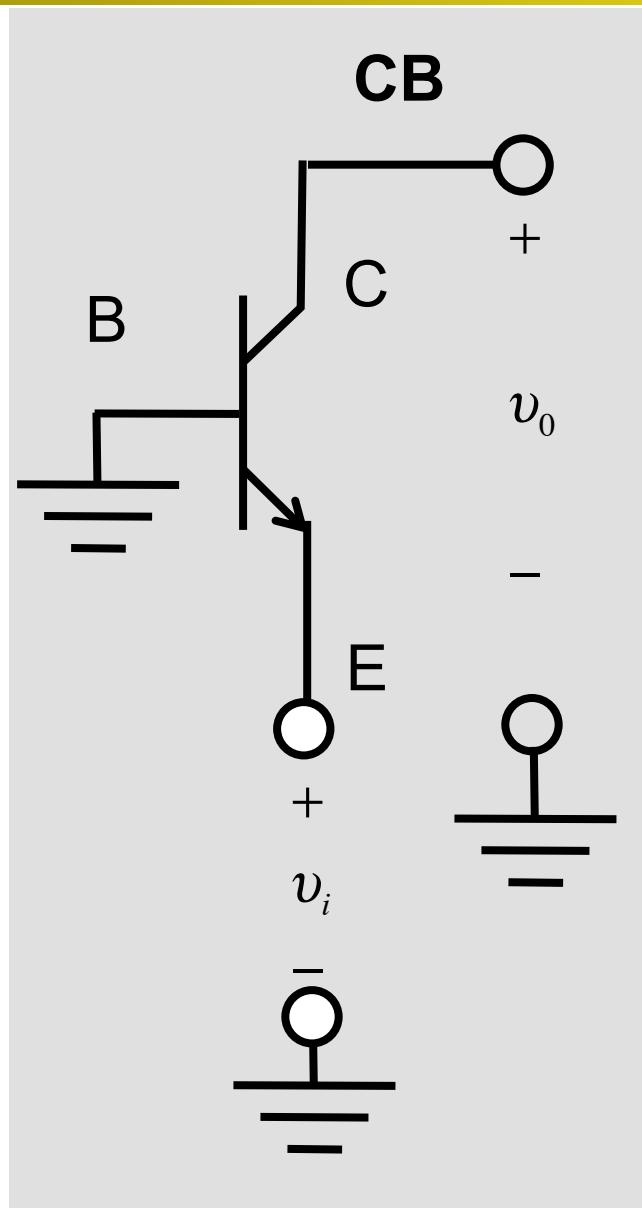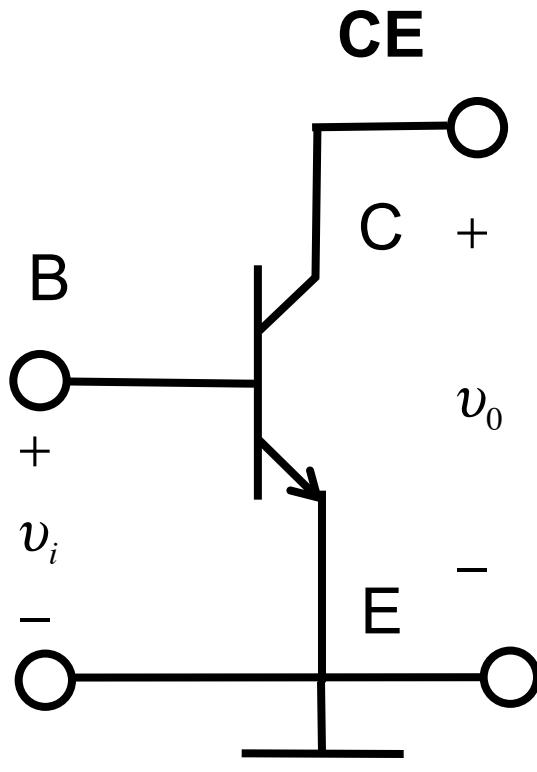

# Three basic MOS amplifiers

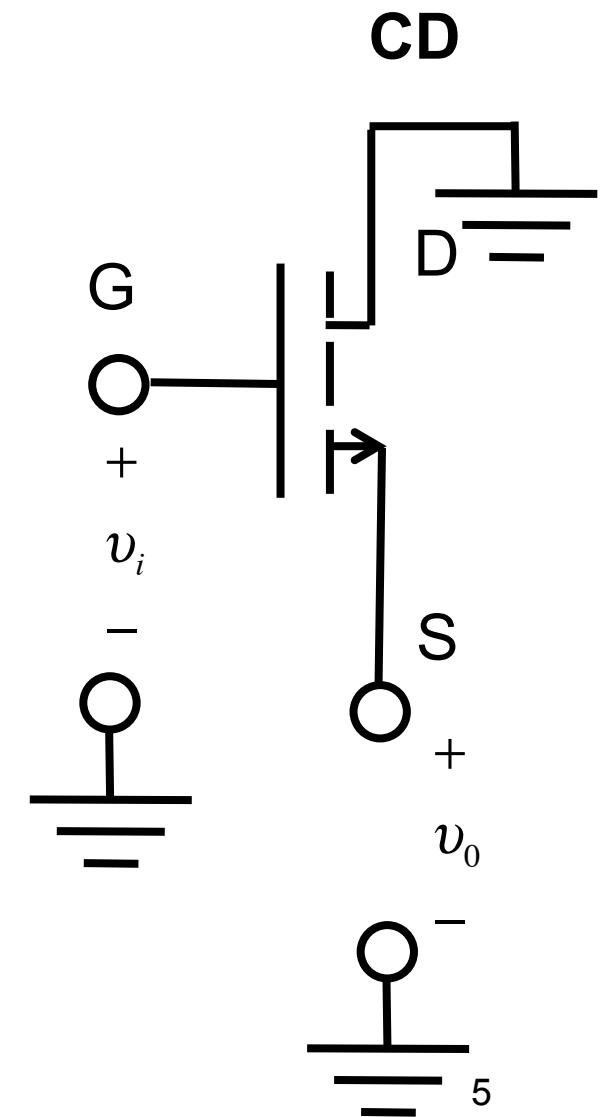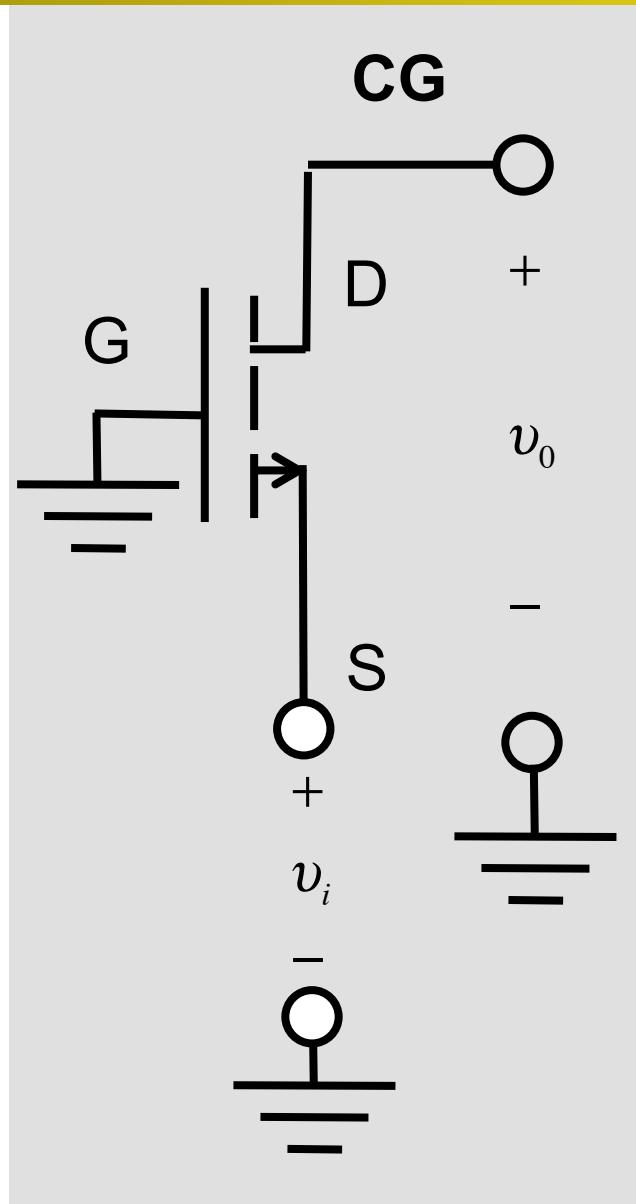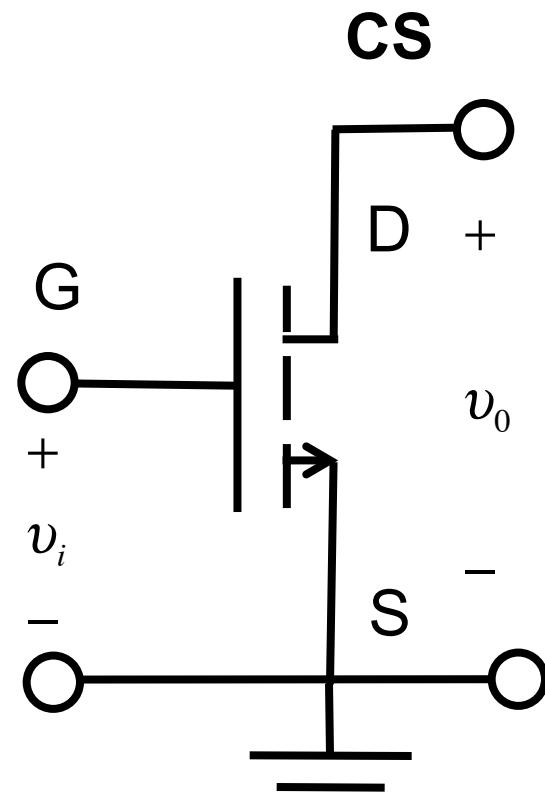


# Outline

---

- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG
- 4) Common base example

- 5) CC (emitter follower) / CD (source follower)

# Amplifier with source and load

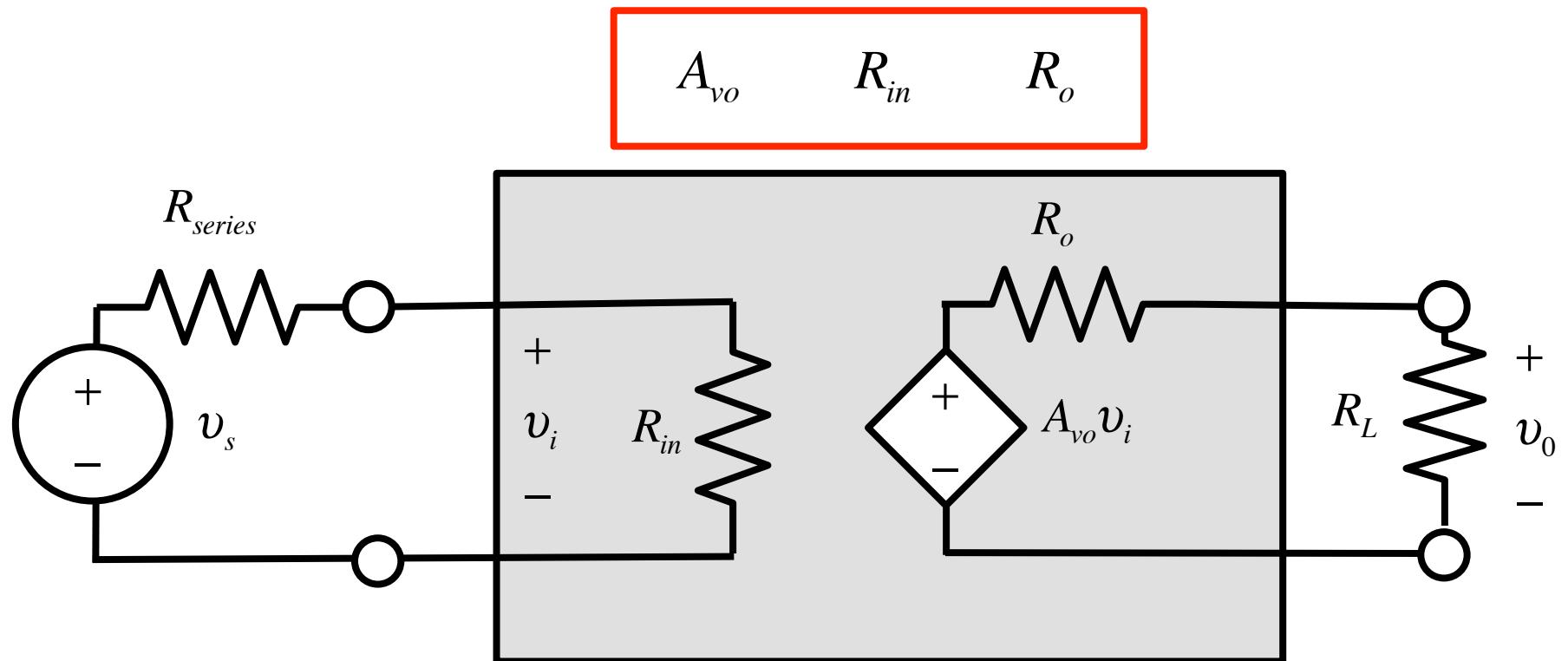


$$G_v = \frac{R_{in}}{R_{in} + R_{series}} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$

$$G_i = A_{vo} \frac{R_{in}}{R_L}$$

$$G_p = G_v G_i$$
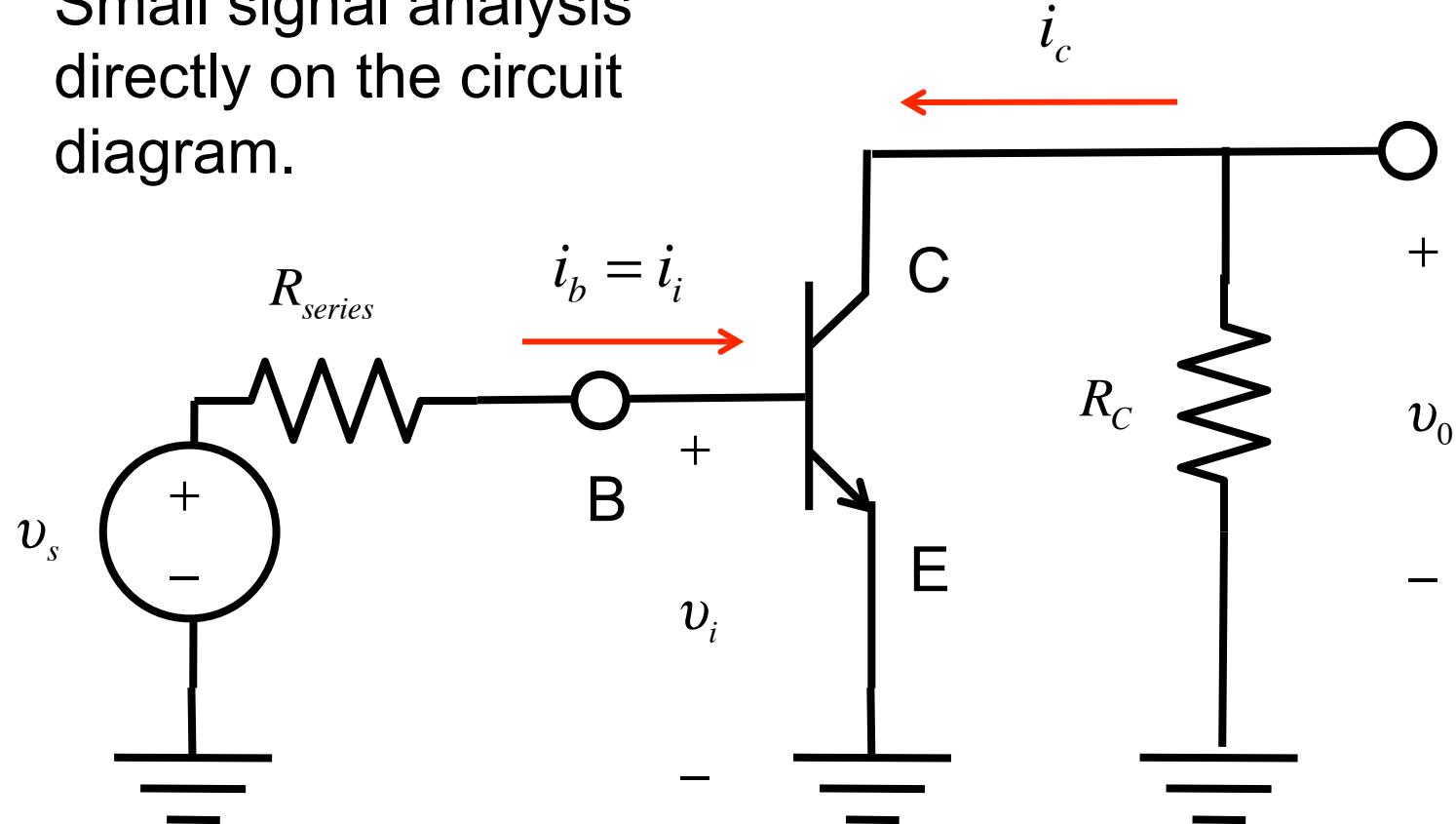
# Common emitter

Small signal analysis  
directly on the circuit  
diagram.



# Common emitter results

---

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_C \parallel r_o \quad \text{open circuit voltage gain}$$


$$A_v = -g_m (R_C \parallel r_o \parallel R_L) \quad \text{with load attached}$$

$$R_{in} = r_\pi$$

$$R_o = R_C \parallel r_o$$
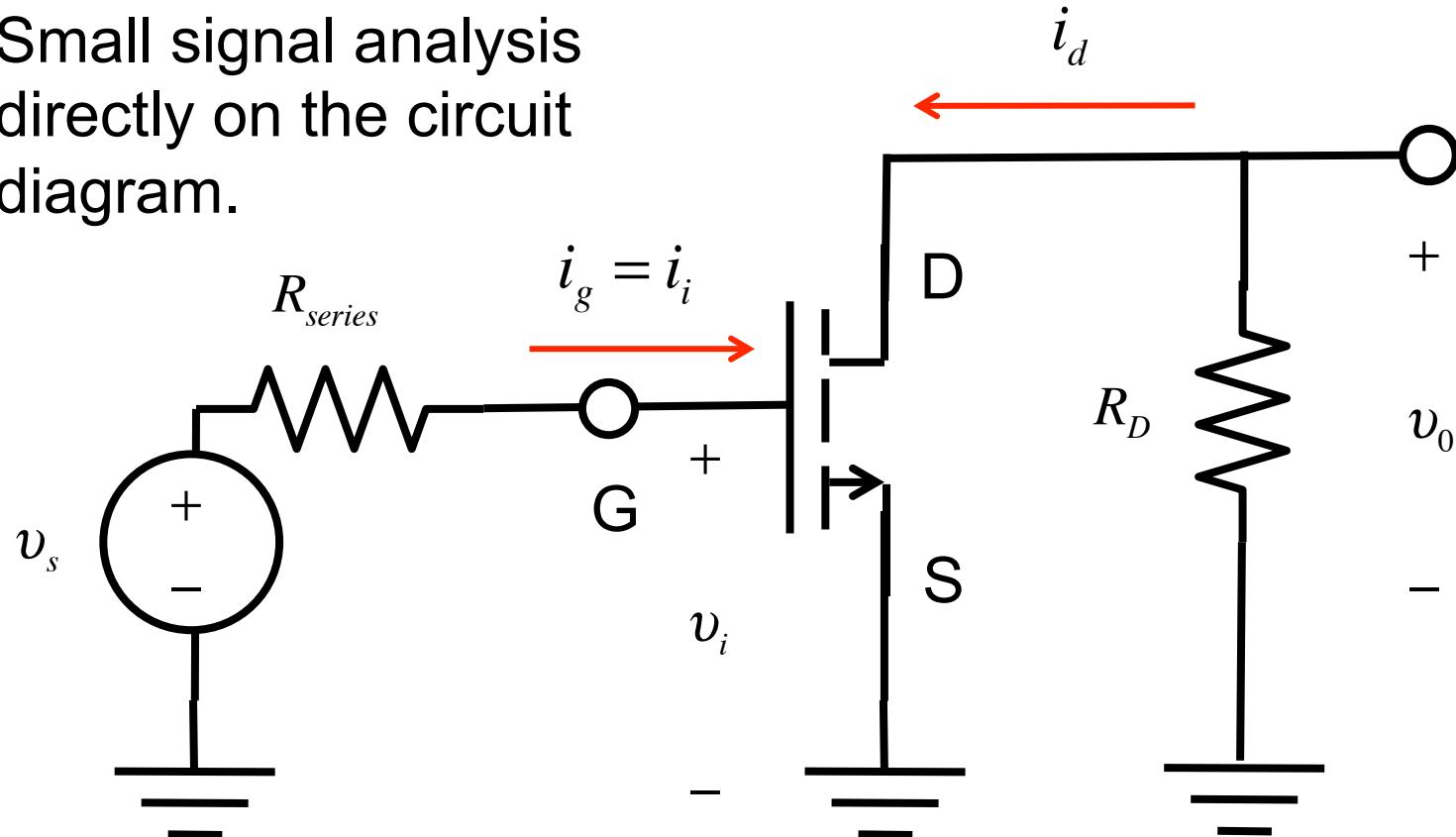
# Common source

Small signal analysis  
directly on the circuit  
diagram.



# Common source results

---

$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_D \parallel r_o \quad \text{open circuit voltage gain}$$


$$A_v = -g_m (R_D \parallel r_o \parallel R_L) \quad \text{with load attached}$$

$$R_{in} = \infty$$

$$R_o = R_D \parallel r_o$$
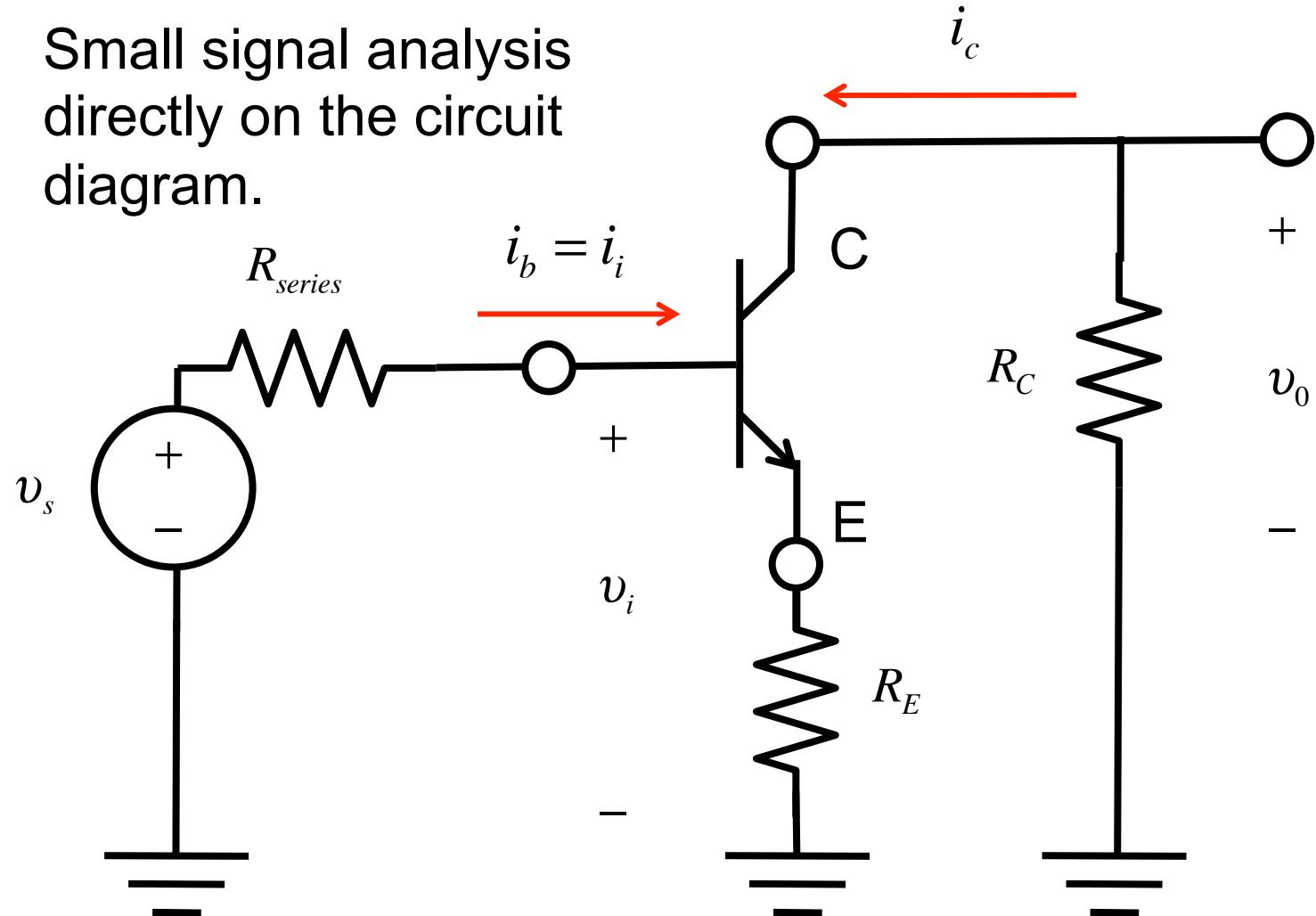
# Common emitter with “emitter degeneration”

Small signal analysis  
directly on the circuit  
diagram.



# Common emitter with emitter resistor

---


$$A_{v_o} = -\frac{r_\pi}{r_\pi + (\beta + 1)R_E} (g_m R_C) \quad \text{open circuit voltage gain}$$

$$A_{v_o} = -\frac{r_\pi}{r_\pi + (\beta + 1)R_E} (g_m R_C \parallel R_L) \quad \text{with load attached}$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_o = R_C$$

# Common source with source degeneration

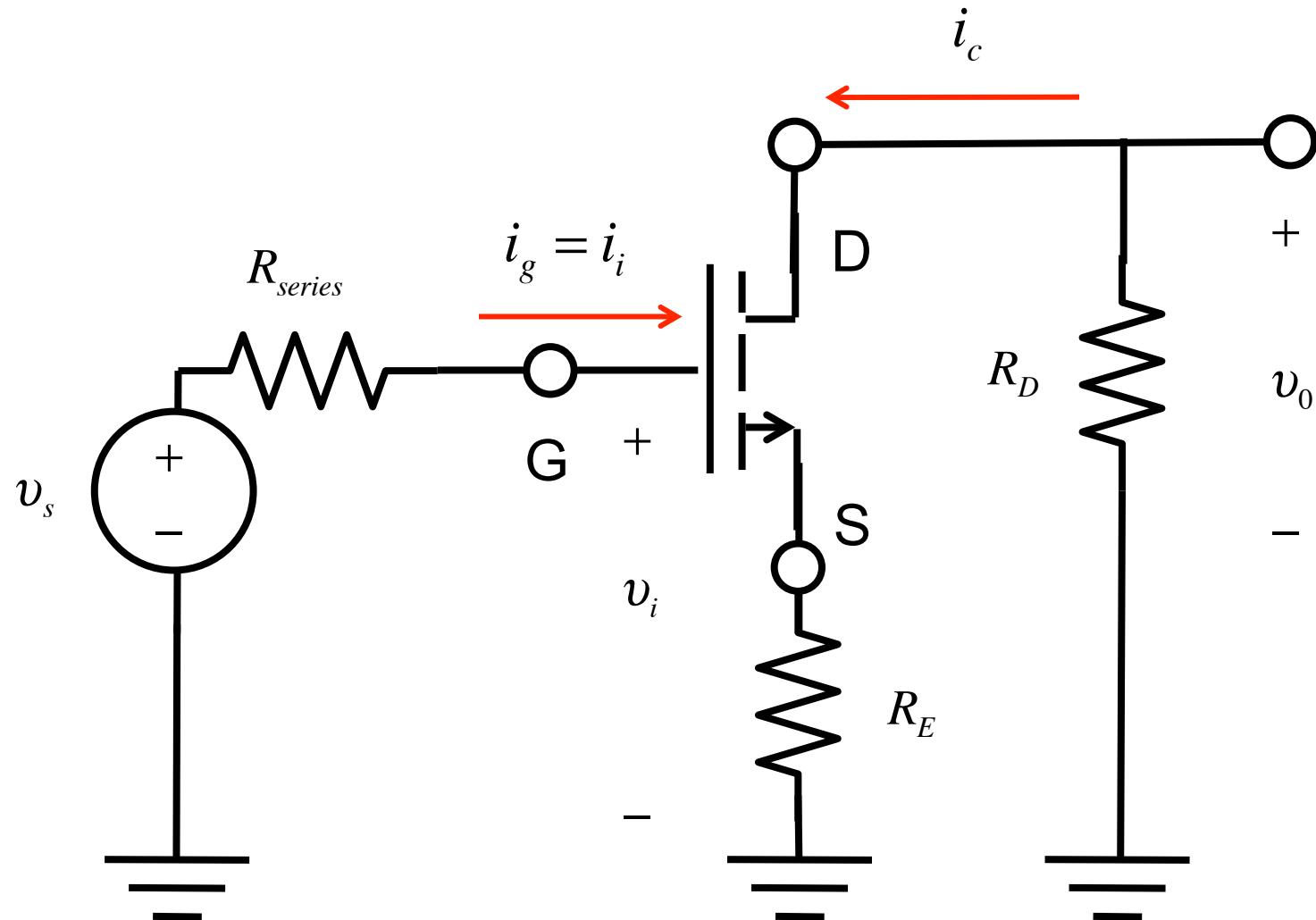

# Common source with source resistor

---

$$r_\pi \rightarrow \infty \quad \beta \rightarrow \infty$$

$$A_{v_o} = -\frac{1}{1 + g_m R_S} (g_m R_D) \quad \text{open circuit voltage gain}$$

$$A_{v_o} = -\frac{1}{1 + g_m R_S} (g_m R_D \parallel R_L) \quad \text{with load attached}$$

$$R_{in} = \infty$$

$$R_o = R_D$$

## Aside: taking limits


---

$$r_\pi \rightarrow \infty \quad \beta \rightarrow \infty$$


$$A_{v_o} = -\frac{r_\pi}{r_\pi + (\beta + 1)R_E} (g_m R_C)$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$



# CS analysis with equivalent circuits

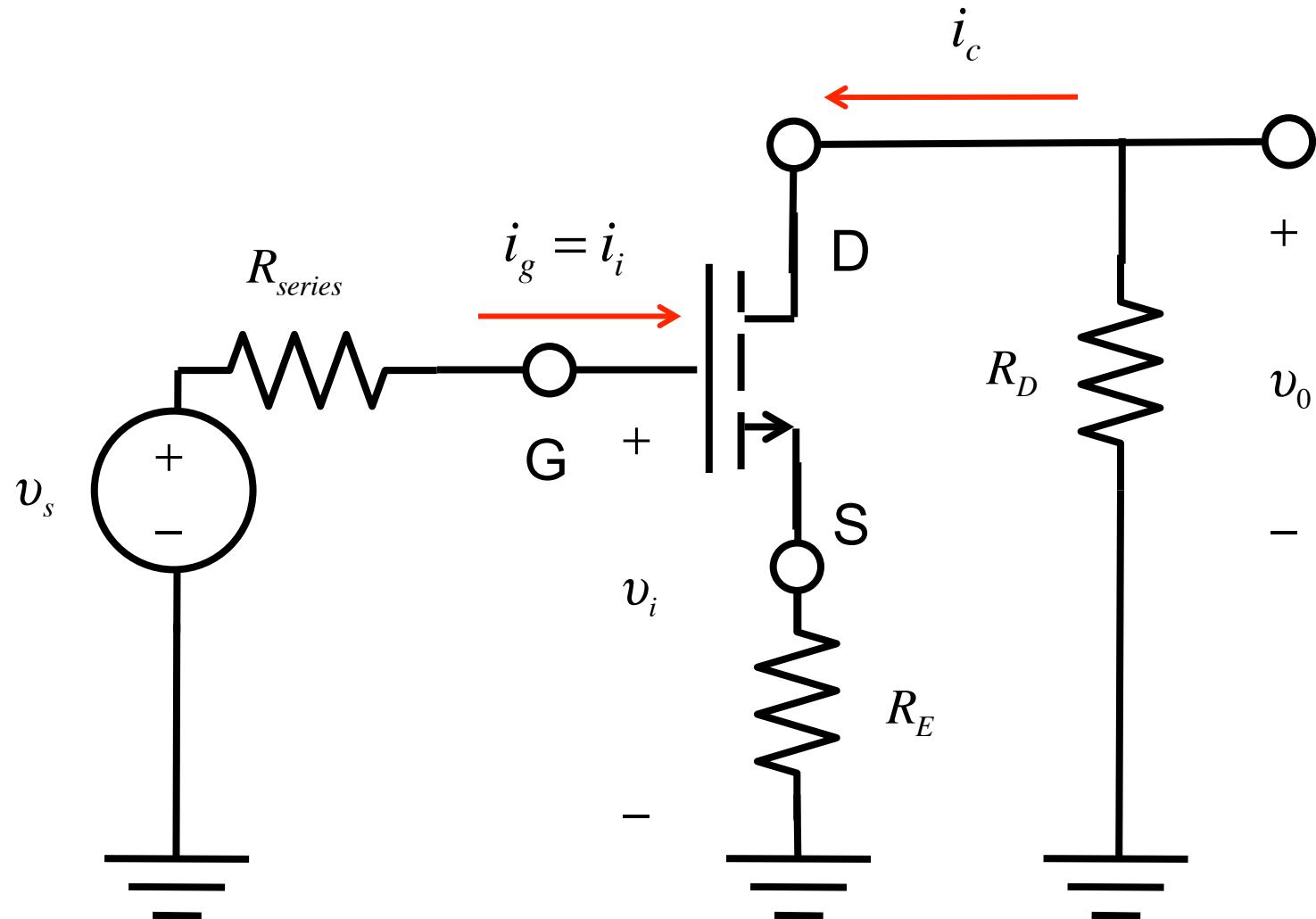


# 1) CS with hybrid-pi model

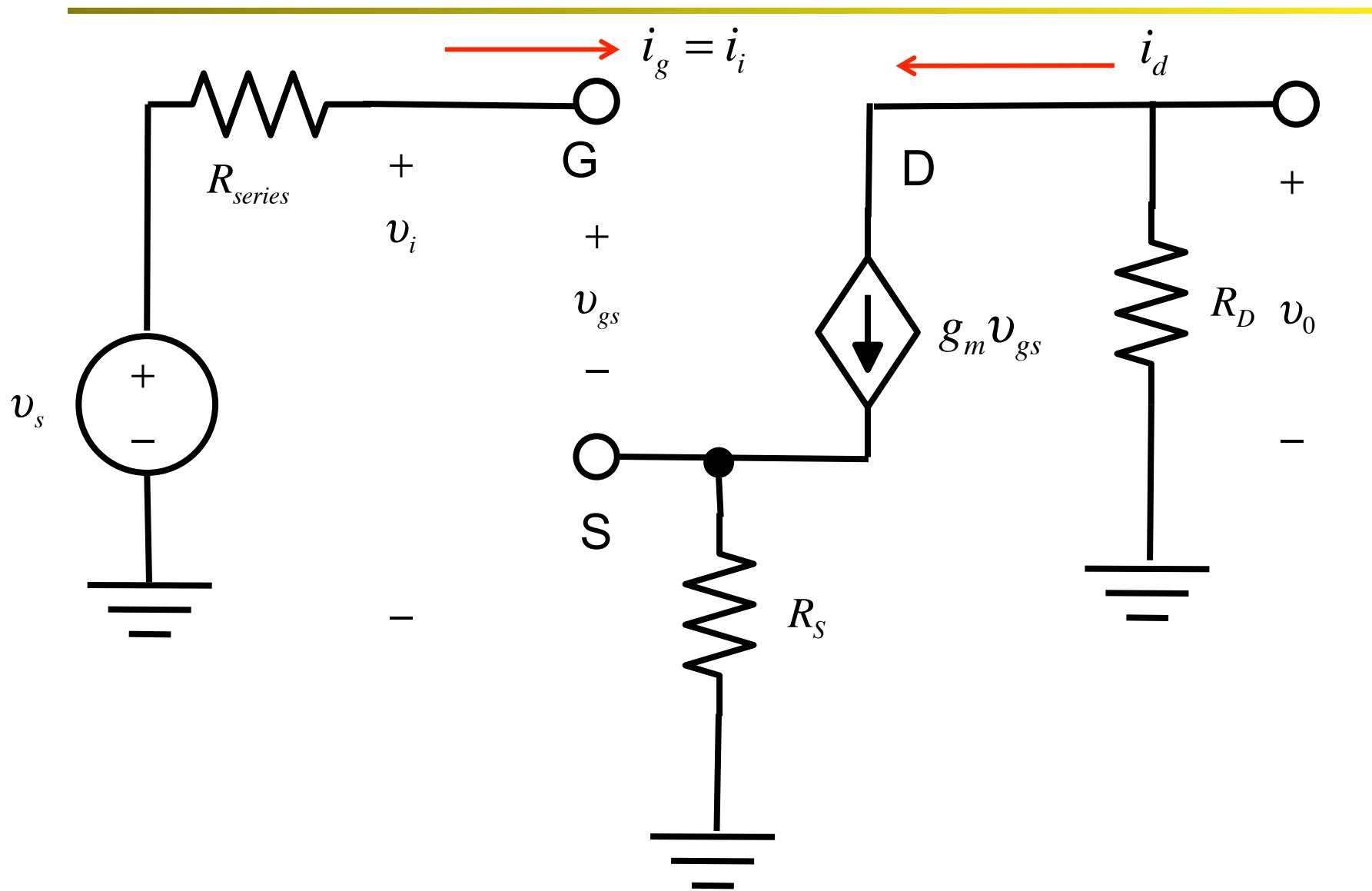


# Hybrid pi vs. T-model

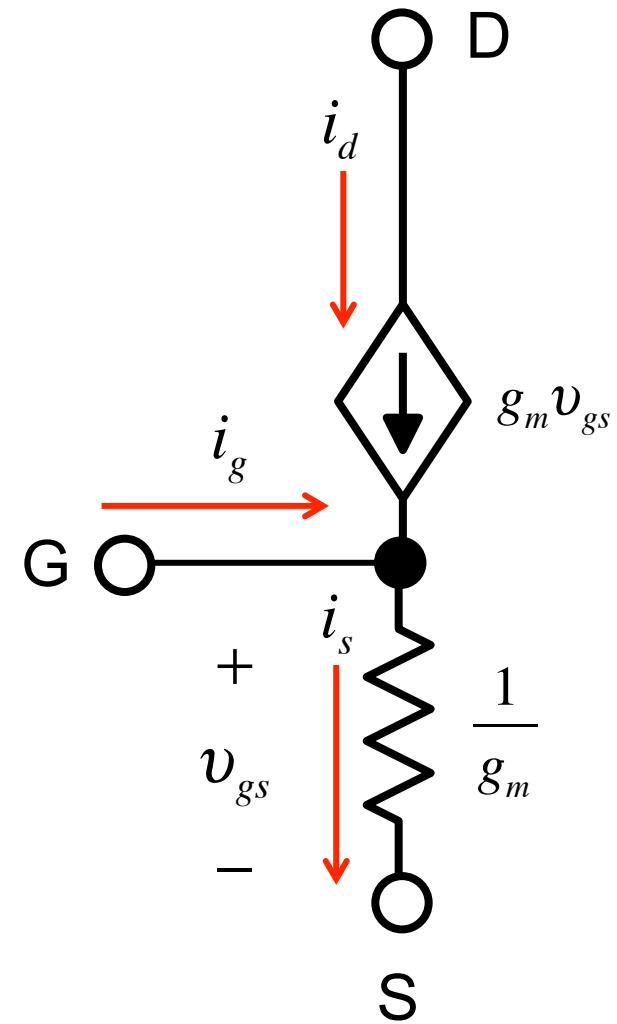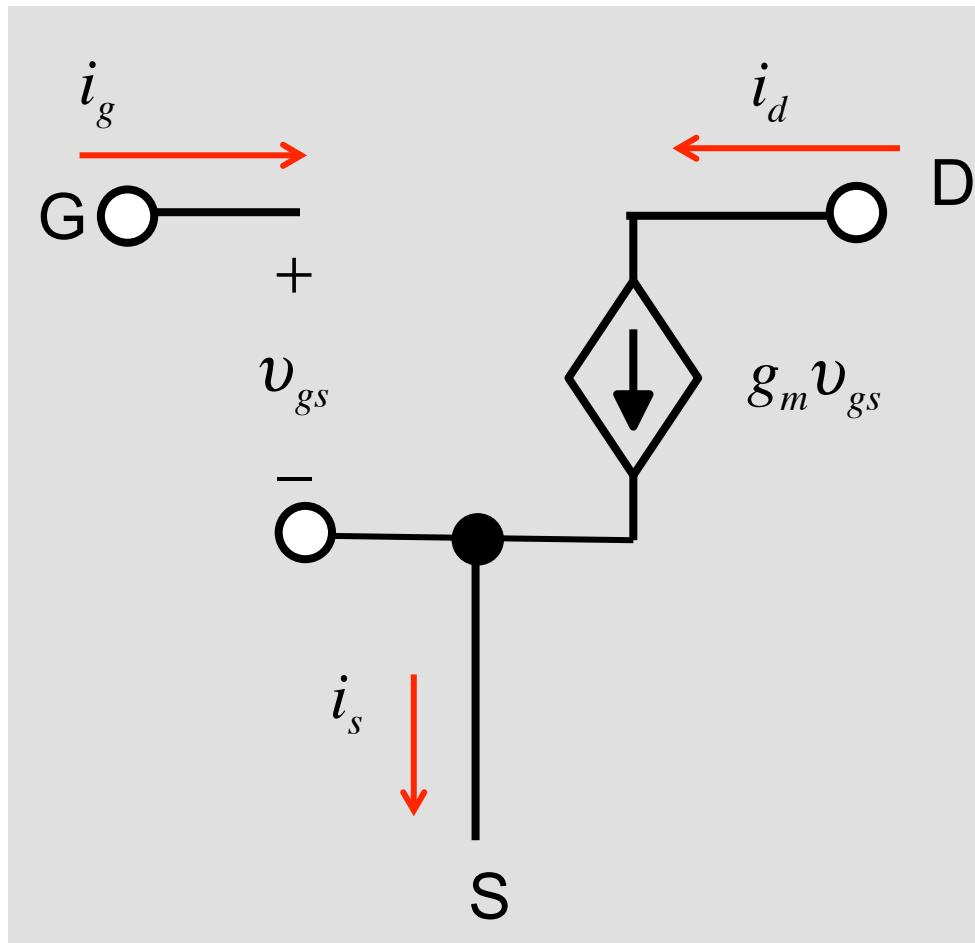

# Draw the s.s. model using T-model

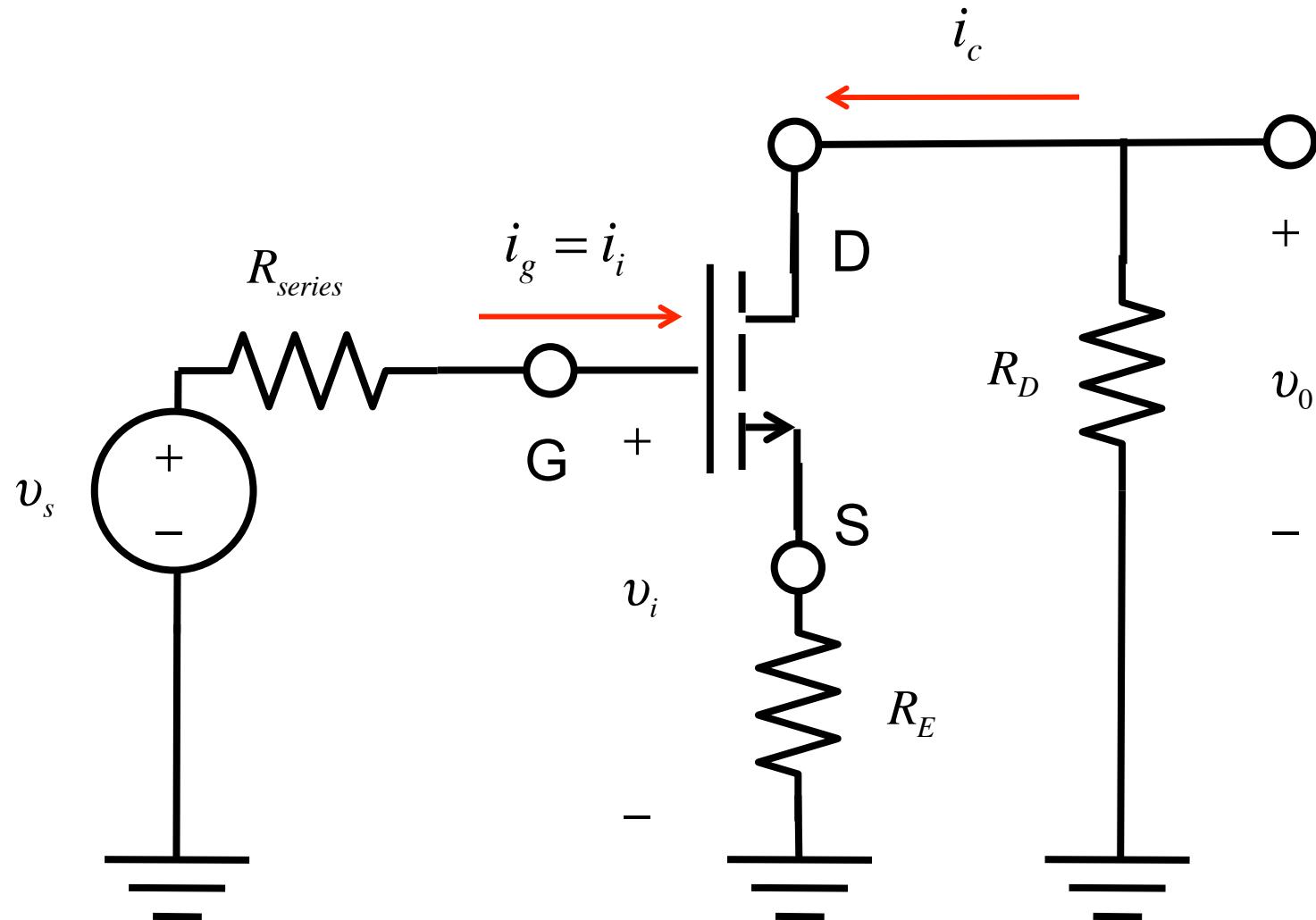

# Common source with source resistor

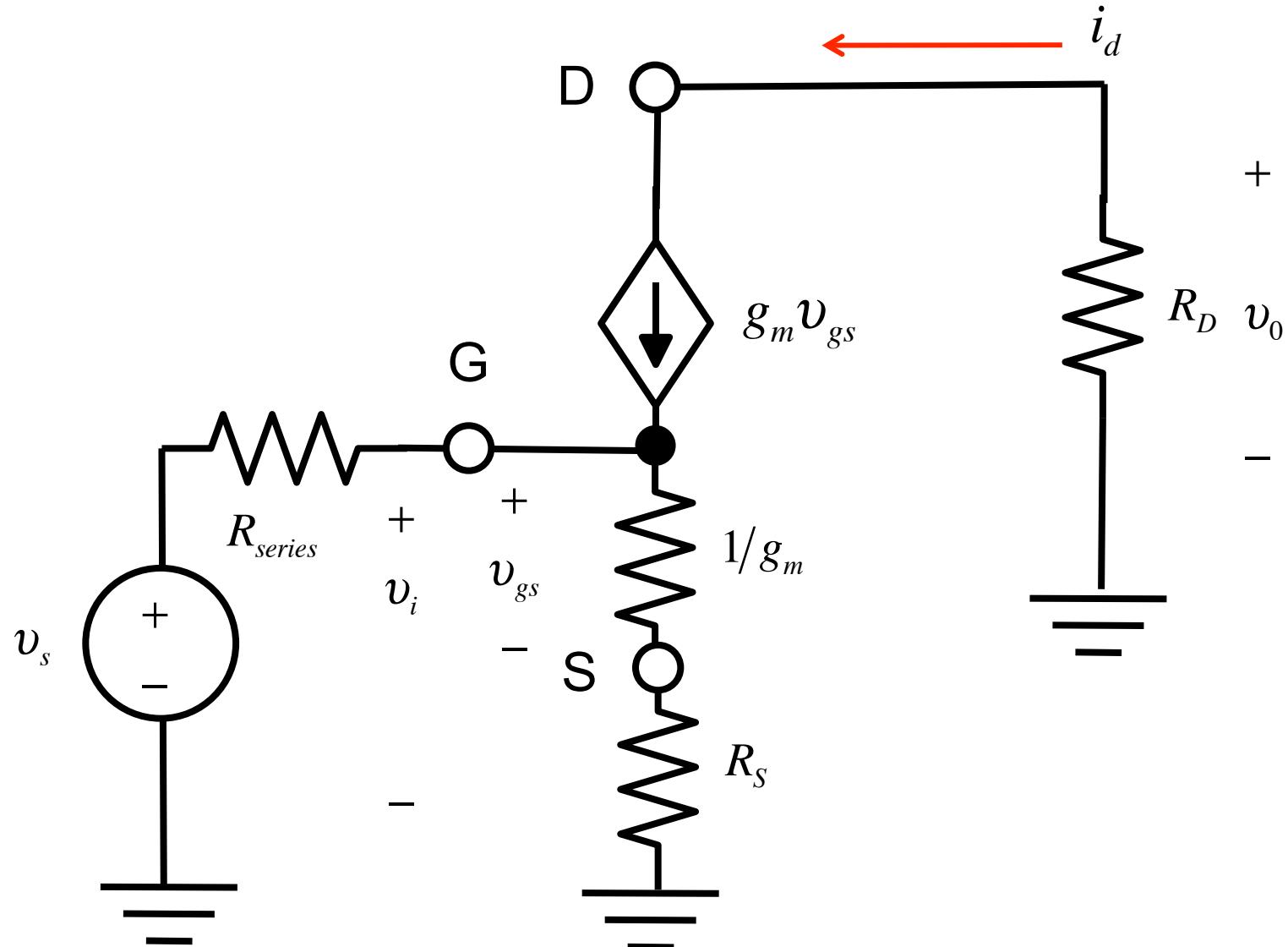

# Common source with source resistor

---

$$A_{v_o} = -\frac{1}{1 + g_m R_S} (g_m R_D) \quad \text{open circuit voltage gain}$$

$$A_{v_o} = -\frac{1}{1 + g_m R_S} (g_m R_D \parallel R_L) \quad \text{with load attached}$$

$$R_{in} = \infty$$

$$R_o = R_D$$


# Outline

---


- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG**
- 4) Common base example
- 5) CC (emitter follower) / CD (source follower)
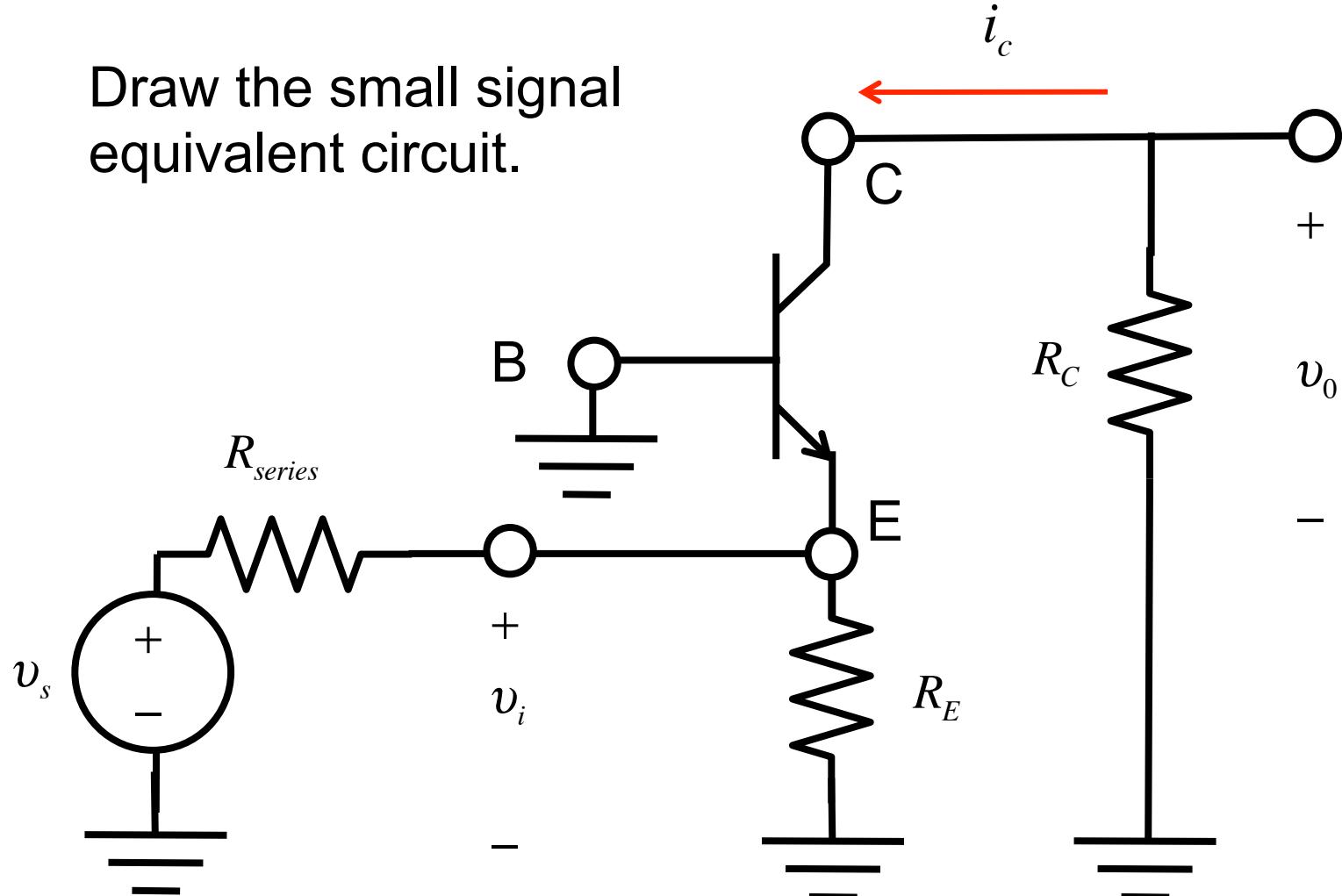
## Common base

Draw the small signal equivalent circuit.



# Common base amplifier

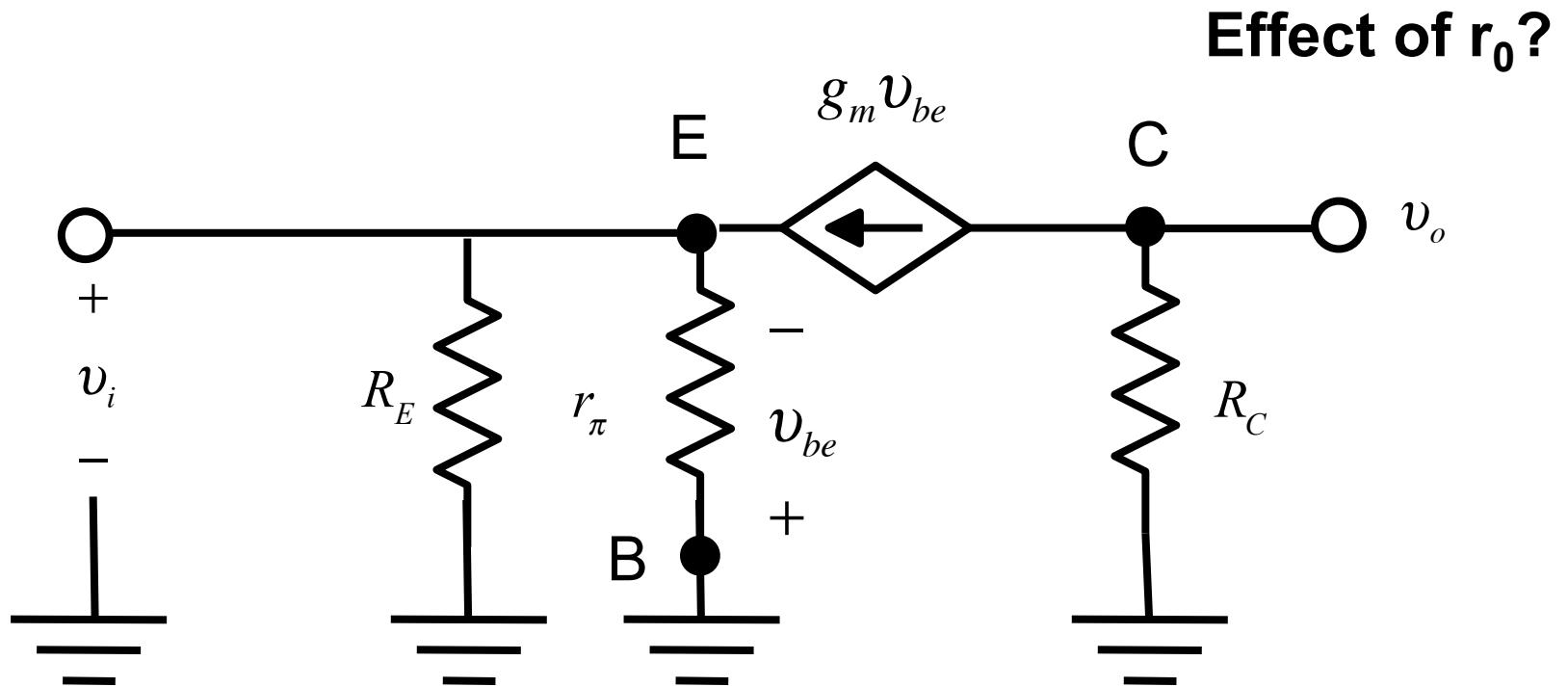

$$v_o = -g_m v_{be} R_C$$

$$v_o = +g_m v_i R_C$$


$$R_o = R_C$$

$$v_{be} = -v_i$$


$$A_v = \frac{v_o}{v_i} = +g_m R_C$$

$$R_{in} = ?$$

## Looking into current source

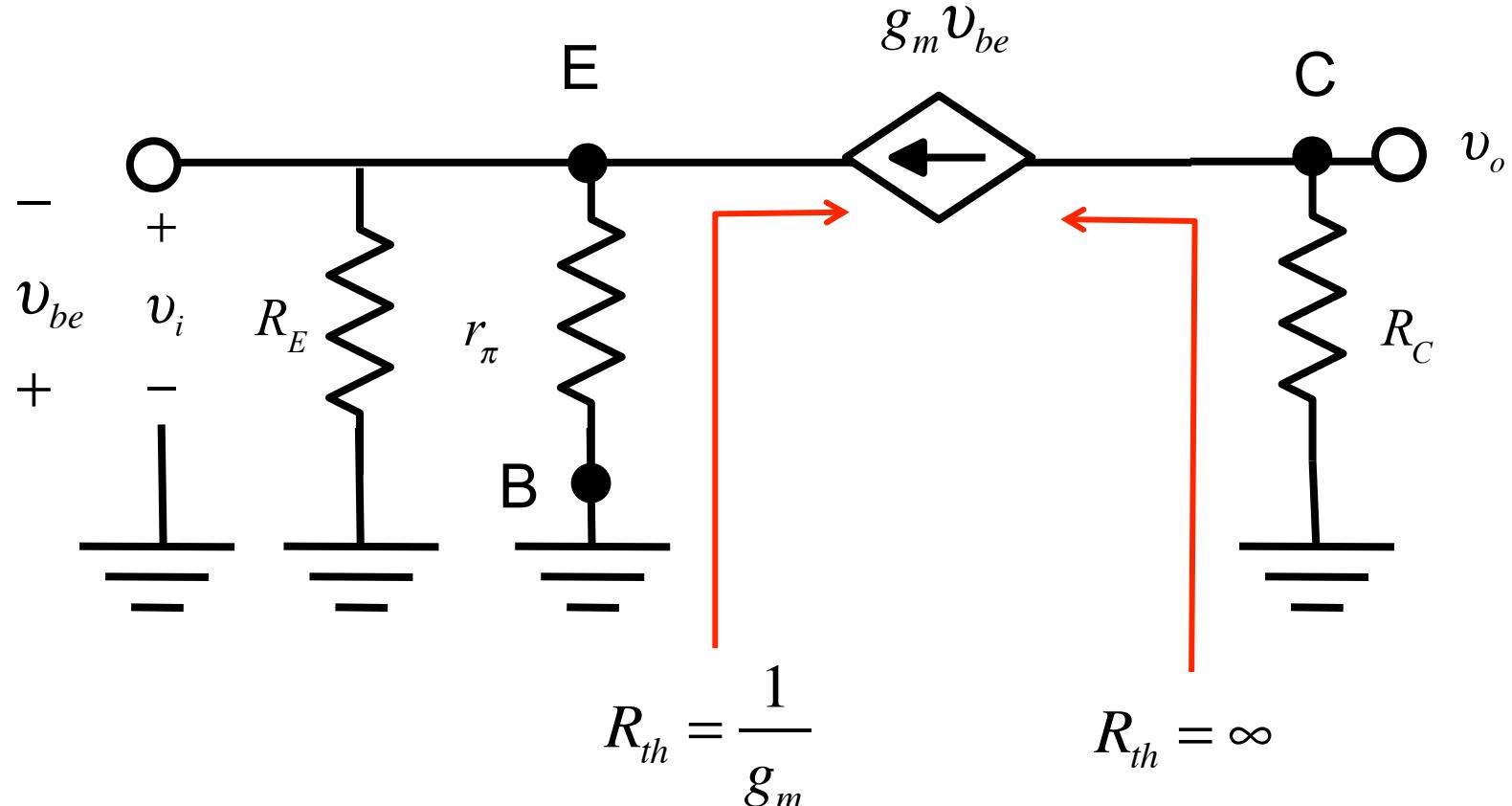


## CB input resistance

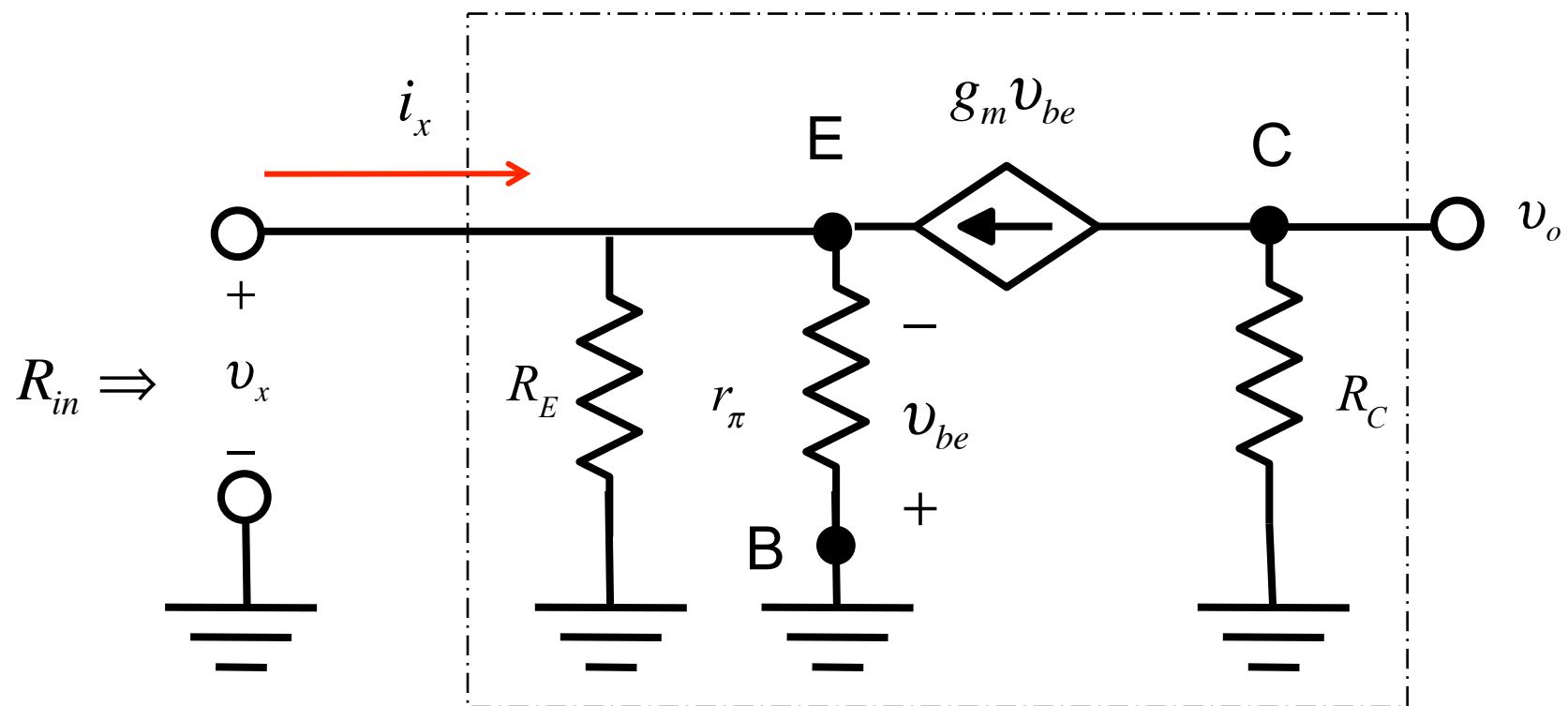

$$R_{in} = R_E \parallel ?$$


## CB input resistance (ii)

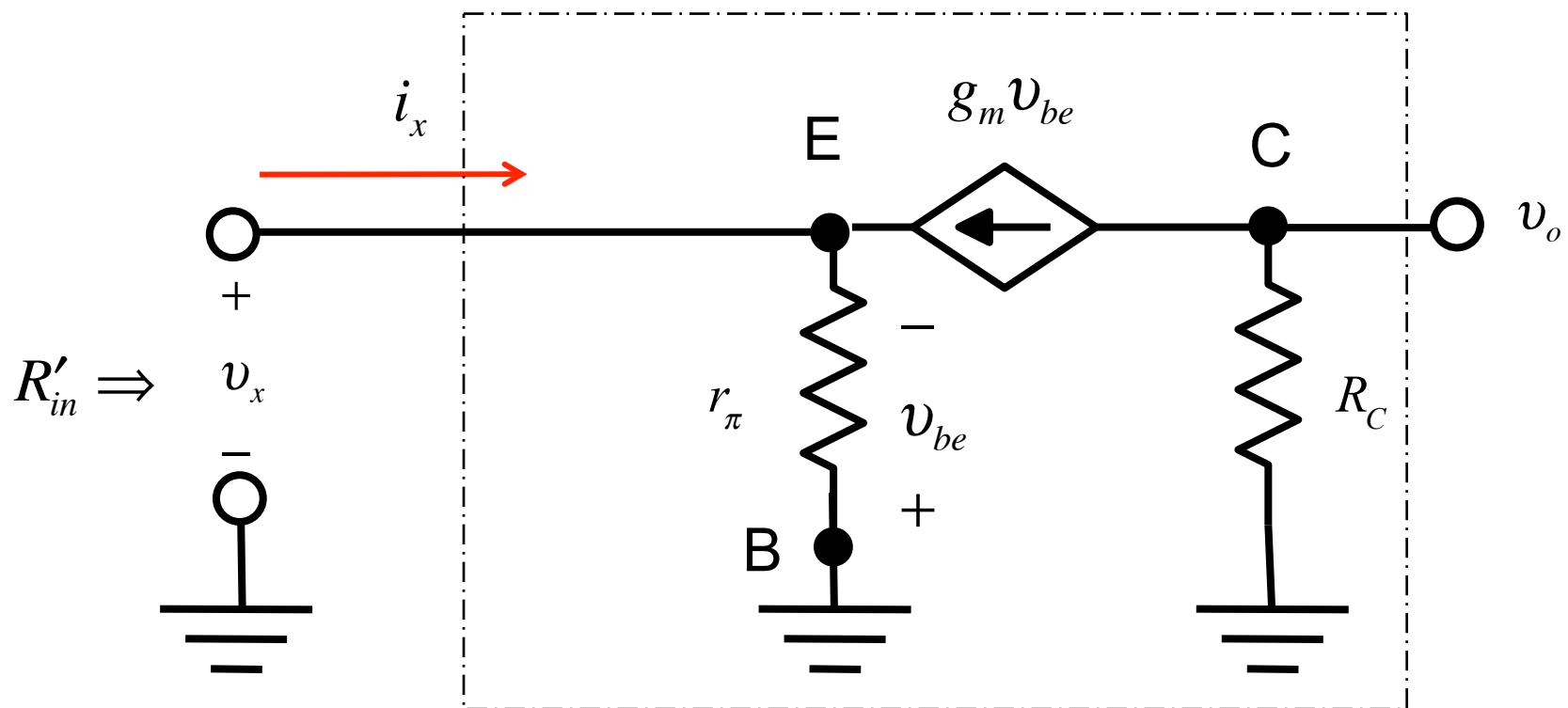

$$R'_{in} \Rightarrow$$

$$R_{in} = R_E \parallel r_\pi \parallel ?$$

## CB input resistance (iii)

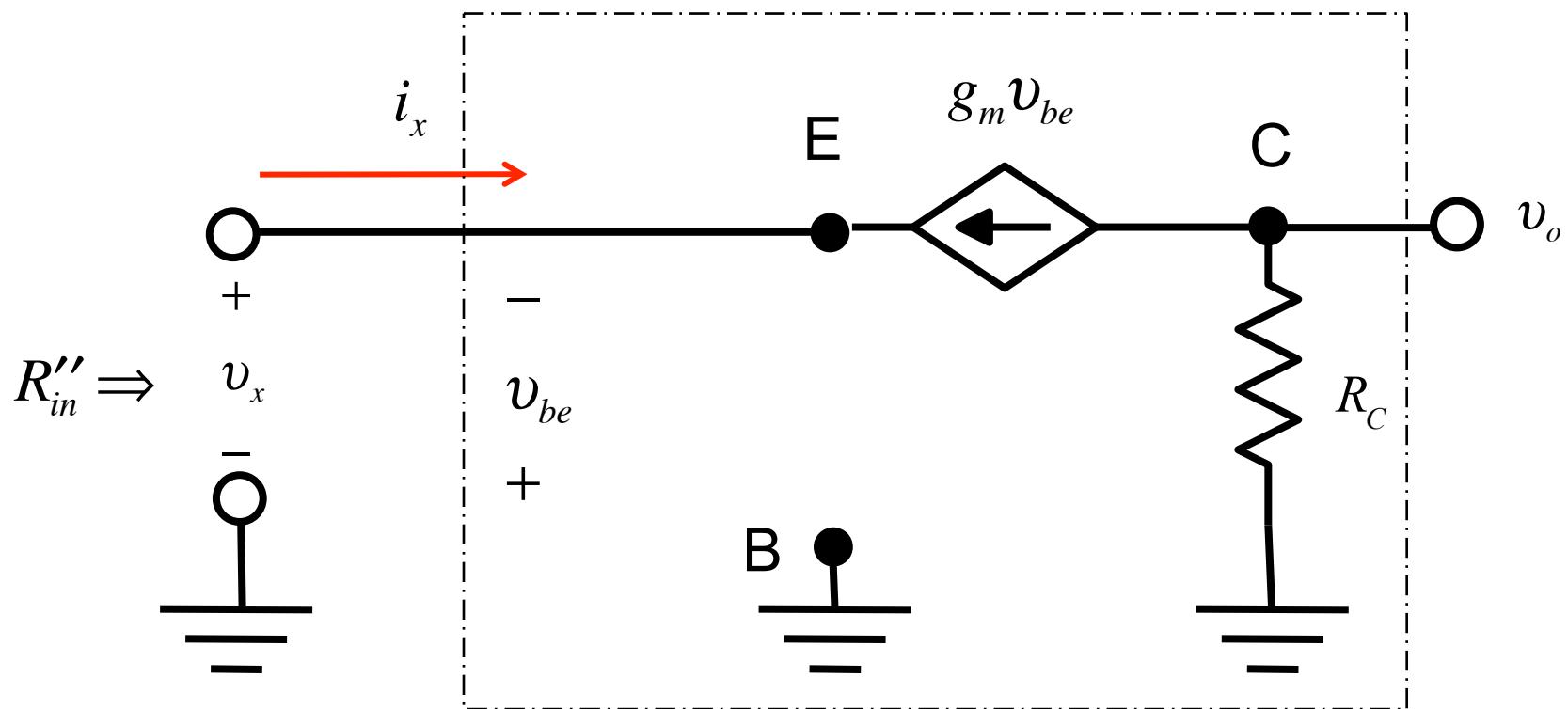

$$R_{in} = R_E \parallel r_\pi \parallel ?$$

$$R''_{in} = \frac{v_x}{i_x} = \frac{v_x}{g_m v_x} = \frac{1}{g_m}$$


Lundstrom: 2019

## Common base

$$A_v = \frac{v_o}{v_i} = +g_m R_C$$


$$R_o = R_C$$
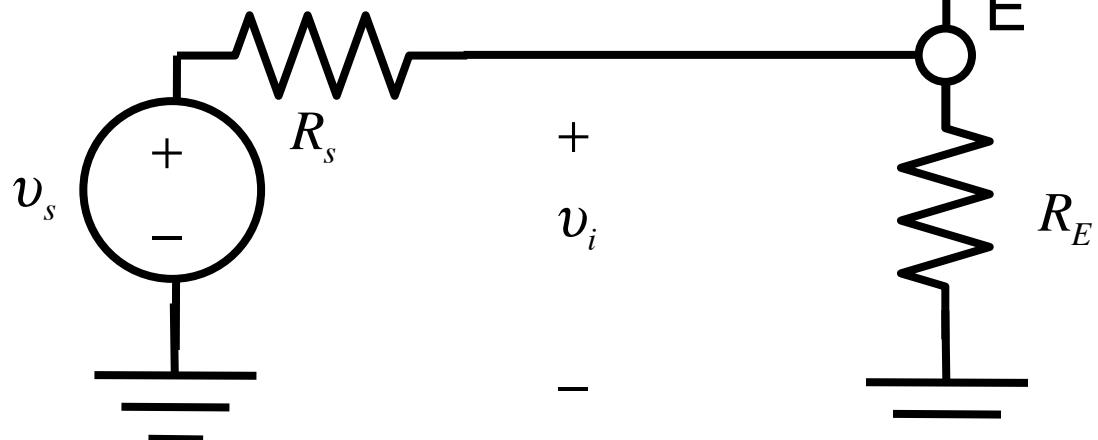
$$R_{in} = R_E \parallel r_\pi \parallel \frac{1}{g_m}$$



**Effect of  $R_L$ ?**

## CB analysis on the circuit diagram

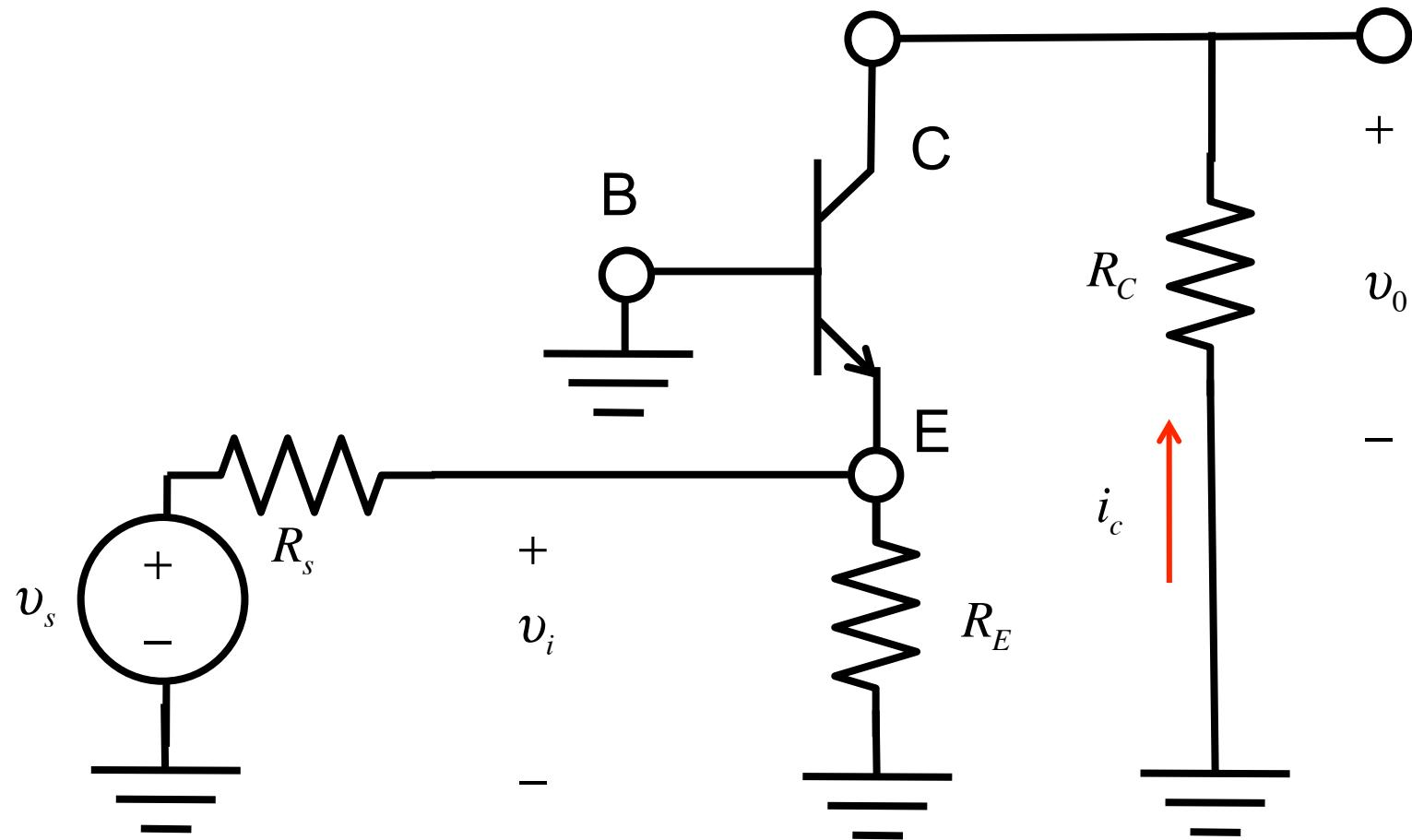

## Common base: results

---

$$A_v = \frac{v_o}{v_i} = +g_m R_C$$

$$R_o = R_C$$

$$R_{in} = R_E \parallel r_\pi \parallel \frac{1}{g_m}$$


$$A_v = \frac{v_o}{v_i} = +g_m R_C$$

$$R_o = R_C$$


$$R_{in} = R_E \parallel \frac{r_\pi}{\beta + 1}$$

$$r_\pi \parallel \frac{1}{g_m} = \frac{r_\pi}{\beta + 1}$$

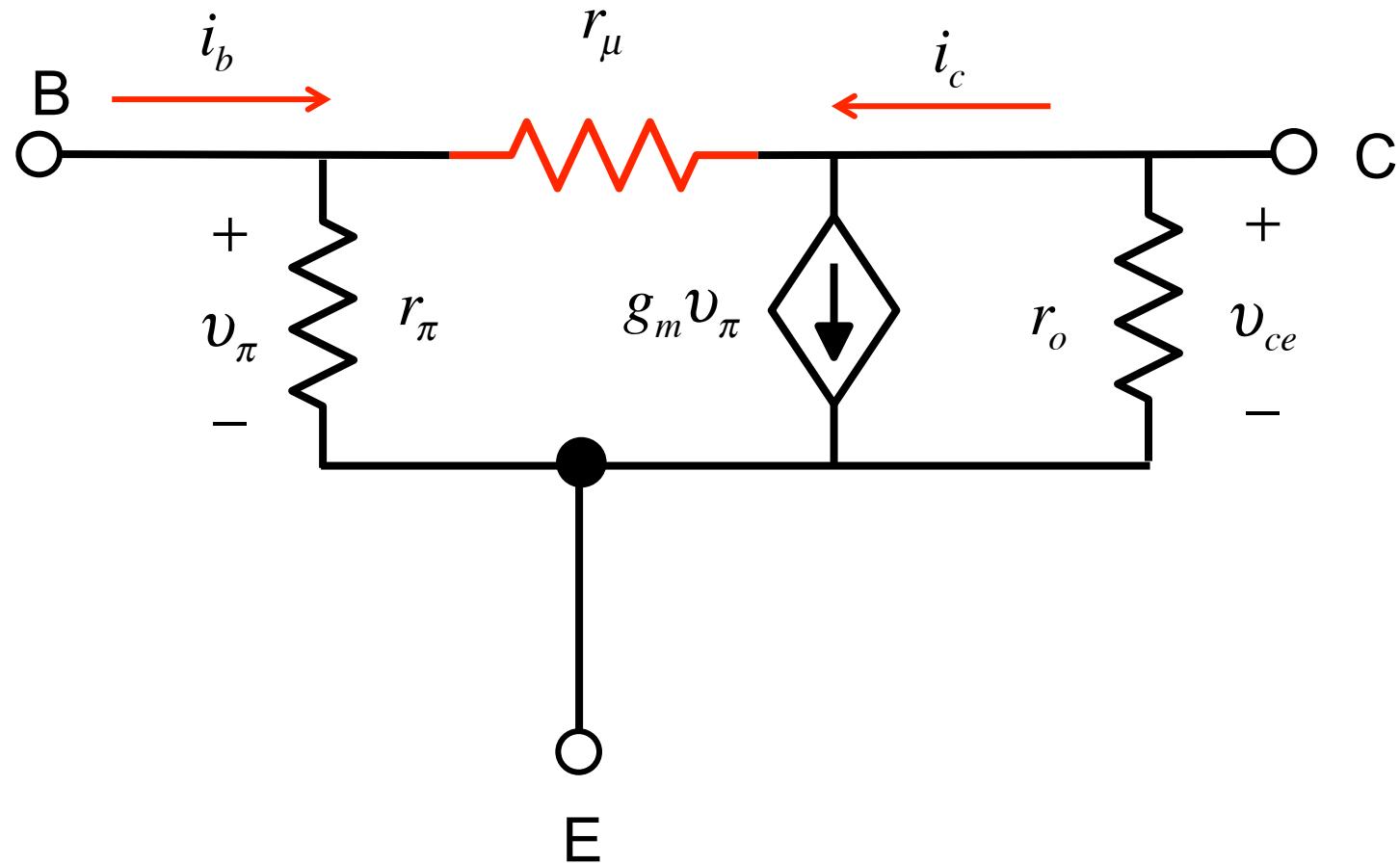
# When can we not do problems by inspection?



# Common emitter amplifier

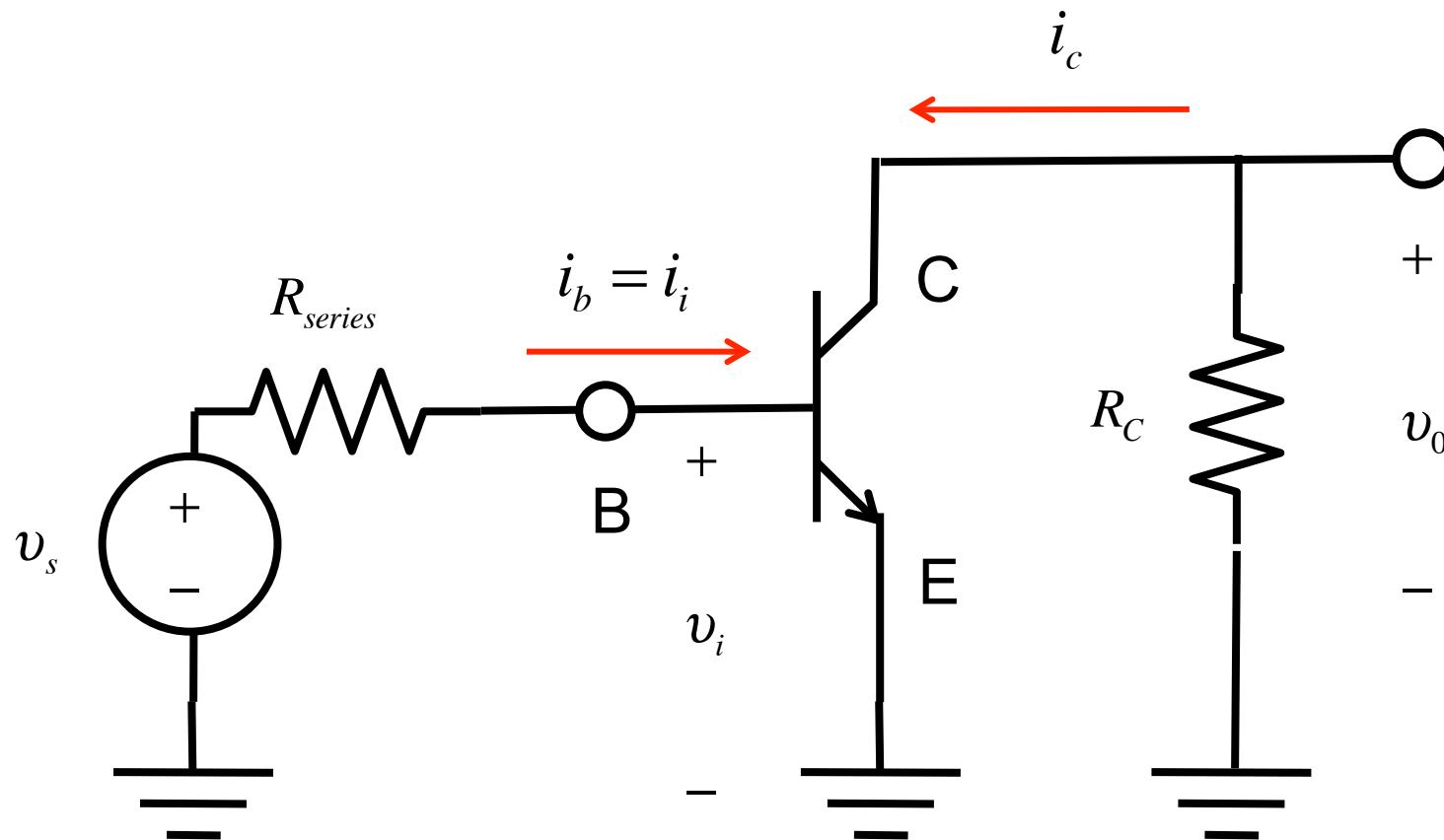

## Small signal equivalent circuit

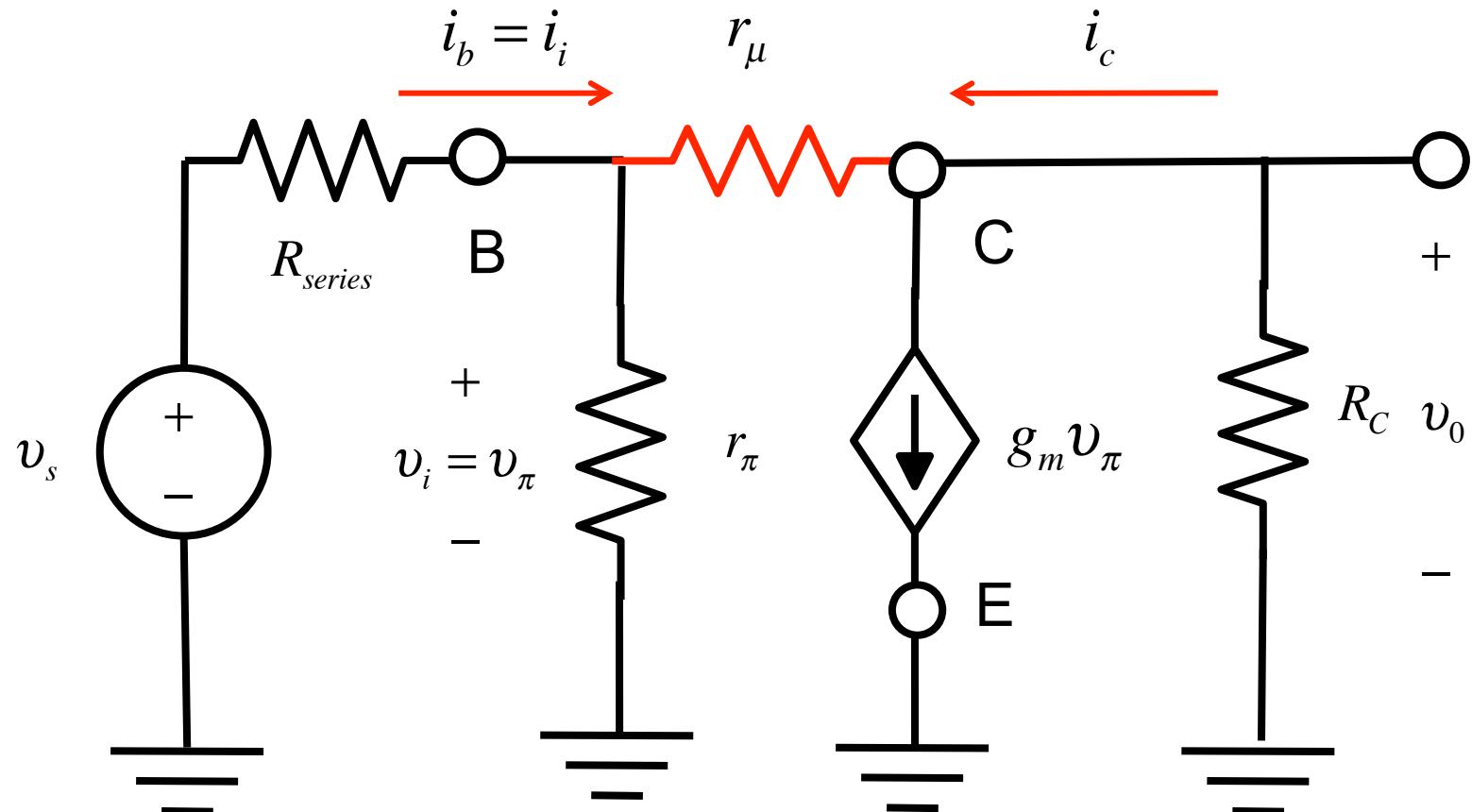

# Result

---

$$A_v = -g_m R_C$$

$$R_o = R_C$$

$$R_{in} = r_\pi$$

$$A_v = -g_m R_C \left[ \frac{1 - 1/(g_m r_\mu)}{1 + R_C/r_\mu} \right]$$

$$R_o = R_C \parallel r_\mu$$

$$R_{in} = r_\pi \parallel \left[ \frac{r_\mu + R_C}{1 + g_m R_C} \right]$$

Sedra and Smith, problem 7.63

# Common base numbers

$$R_C = 10 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega$$

$$I_C = 1.0 \text{ mA}$$

$$g_m = I_C/V_T = 39 \text{ mS}$$

$$g_m r_\pi = \beta \quad \beta = 100$$

$$r_\pi = \beta/g_m = 2.6 \text{ k}\Omega$$

$$A_v = +g_m R_C = +390$$


$$R_o = R_C = 10 \text{ k}\Omega$$

$$R_{in} = R_E \parallel r_\pi \parallel \frac{1}{g_m}$$

$$\frac{1}{g_m} = \frac{1}{39} \text{ k}\Omega = 26 \text{ }\Omega$$


$$R_{in} = 25 \text{ }\Omega$$

## Common base to common gate

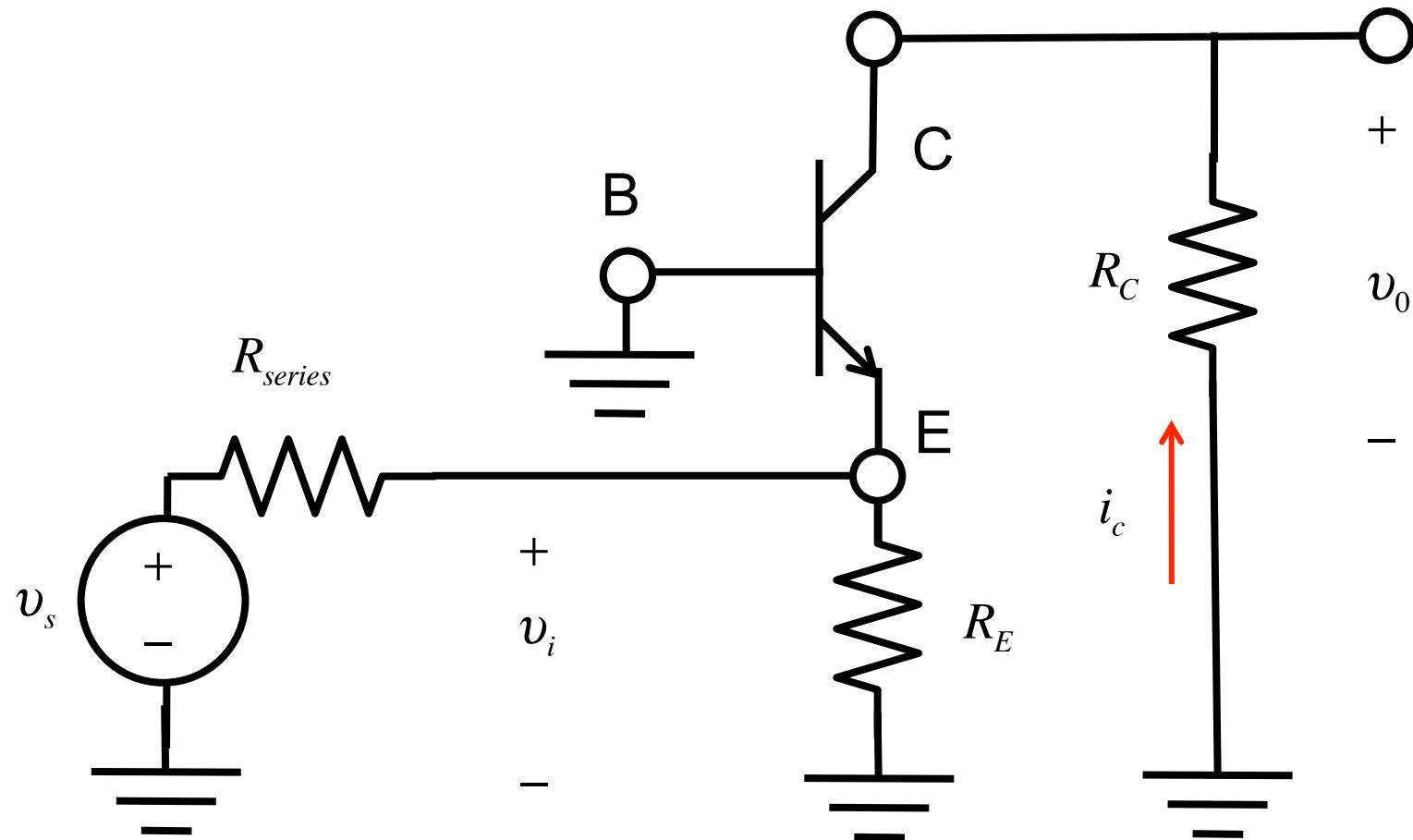

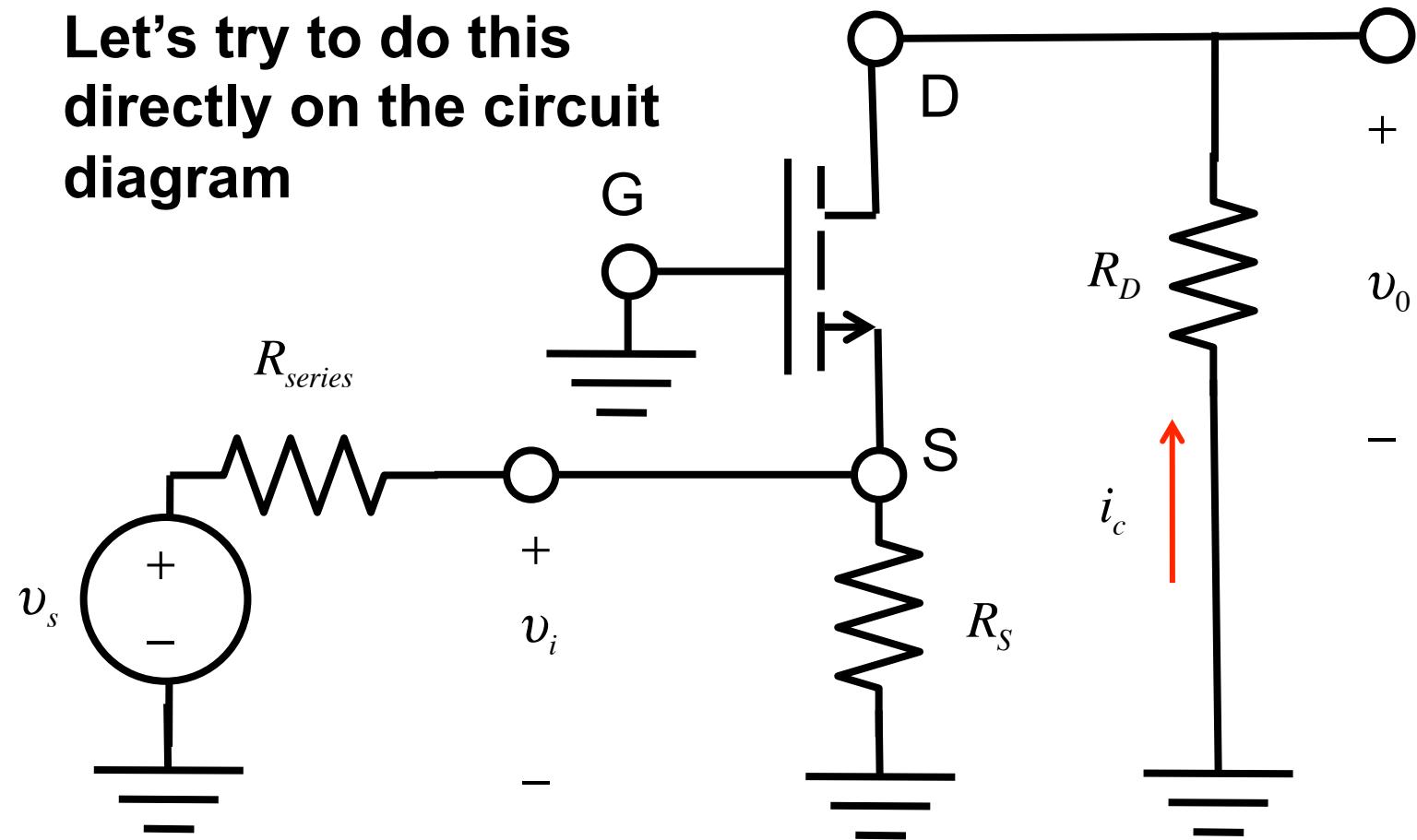
## Common gate

Let's try to do this  
directly on the circuit  
diagram




# Input resistance

---

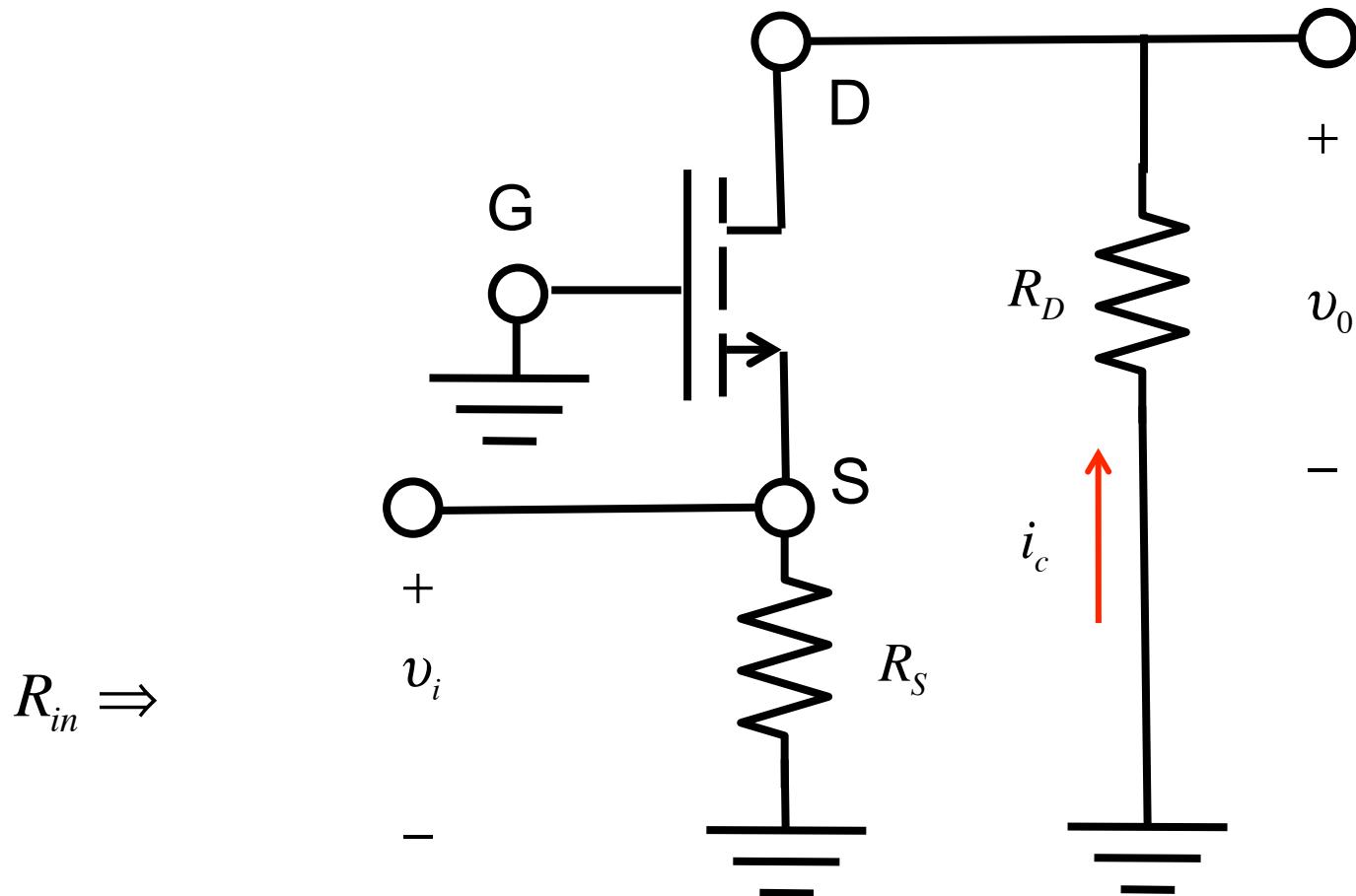

$$R_{in} \Rightarrow$$

## Input resistance (ii)

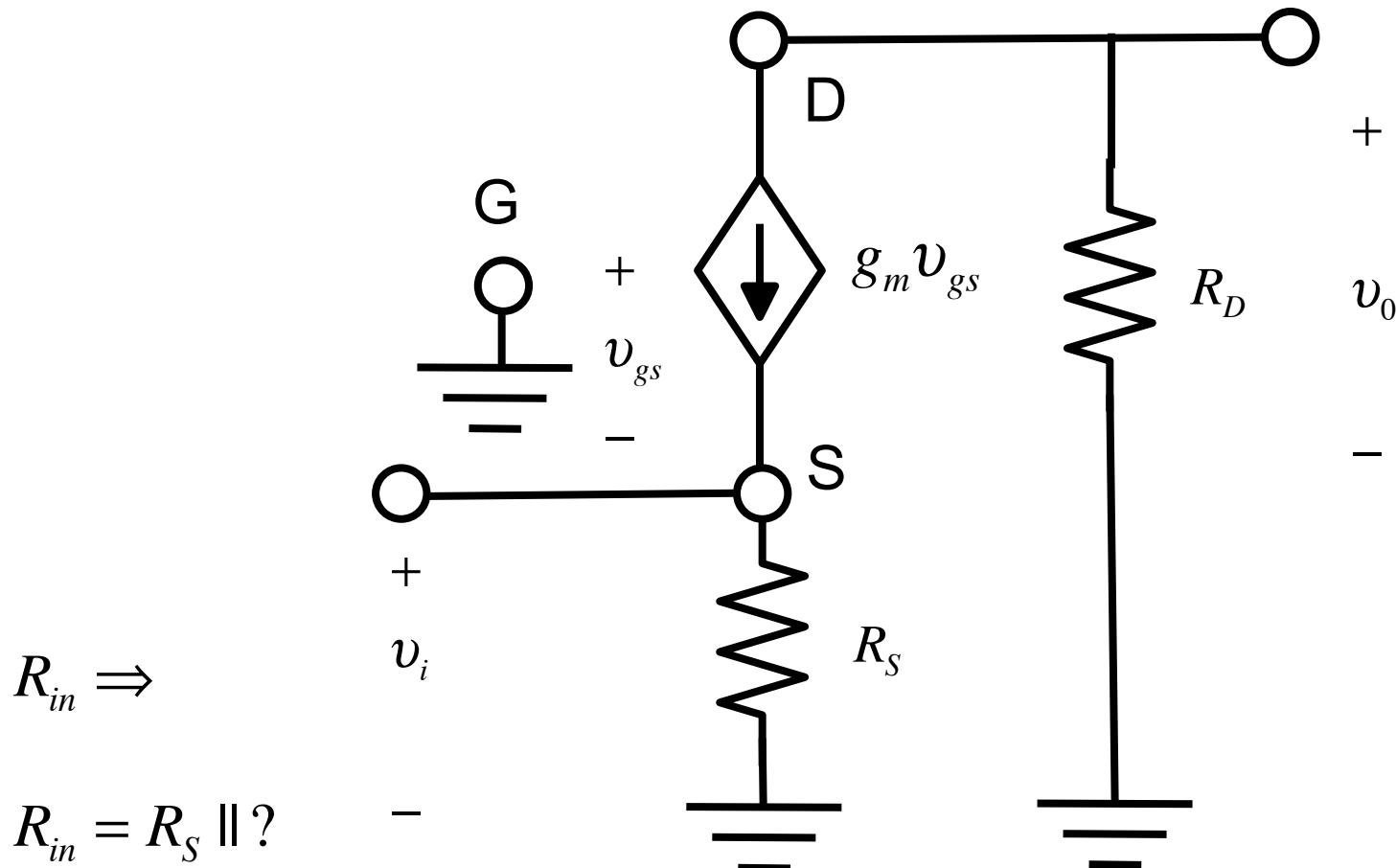


## Input resistance (iii)

$$i_x = -g_m v_{gs}$$

$$i_x = +g_m v_x$$

$$R_{th} = \frac{v_x}{i_x} = \frac{1}{g_m}$$

$$R_{th} \Rightarrow$$

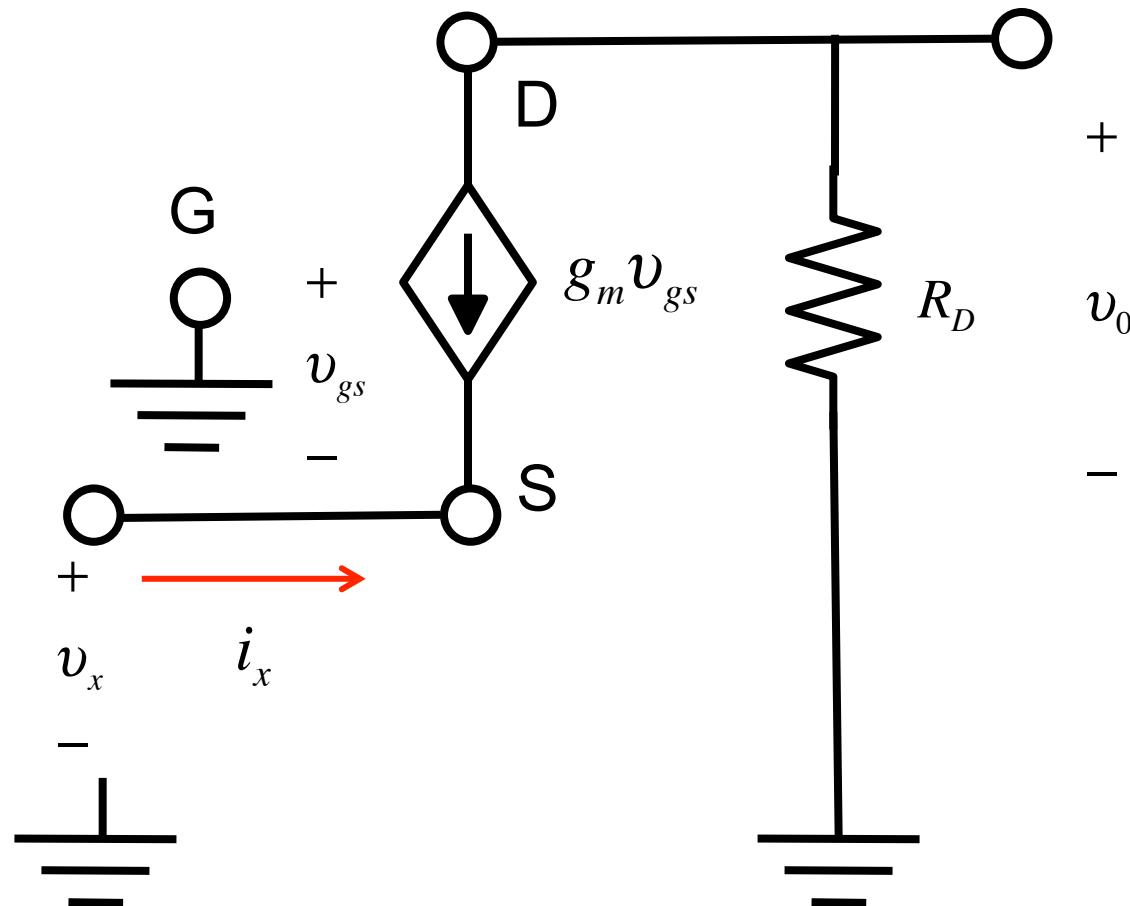

# Common base vs. common gate

---

CB

$$A_v = \frac{v_o}{v_i} = +g_m R_C$$

$$R_o = R_C$$

$$R_{in} = R_E \parallel r_\pi \parallel \frac{1}{g_m}$$

$$r_\pi \parallel \frac{1}{g_m} = \frac{r_\pi}{\beta + 1}$$

CG

$$A_v = \frac{v_o}{v_i} = +g_m R_D$$

$$R_o = R_D$$


$$R_{in} = R_S \parallel \frac{1}{g_m}$$

# Outline

---

- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG
- 4) Common base example**
- 5) CC (emitter follower) / CD (source follower)

# Realistic Common base amplifier

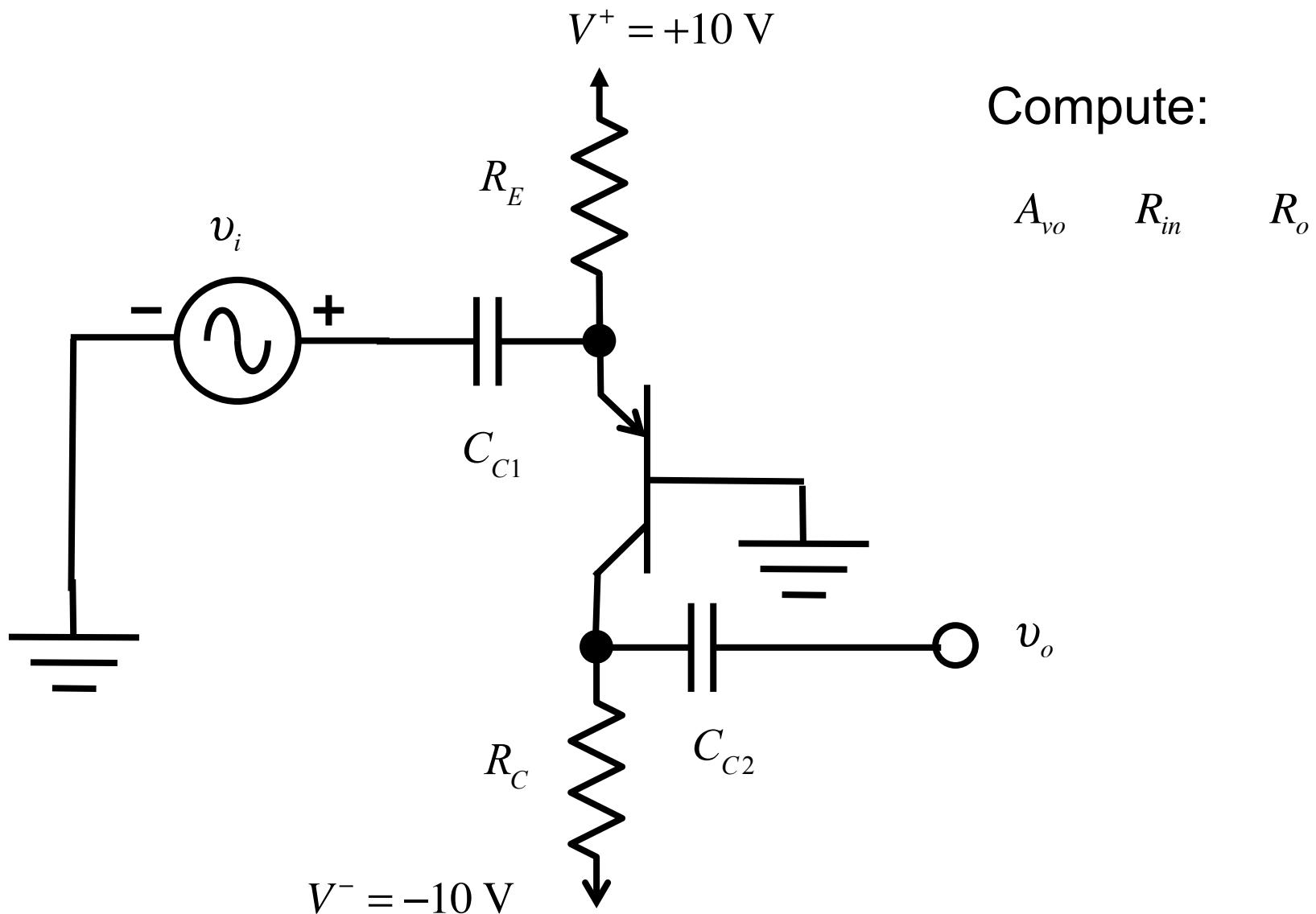


# Size of Capacitors?


---

Audio frequencies: 20 – 20,000 Hz


# Realistic Common base amplifier

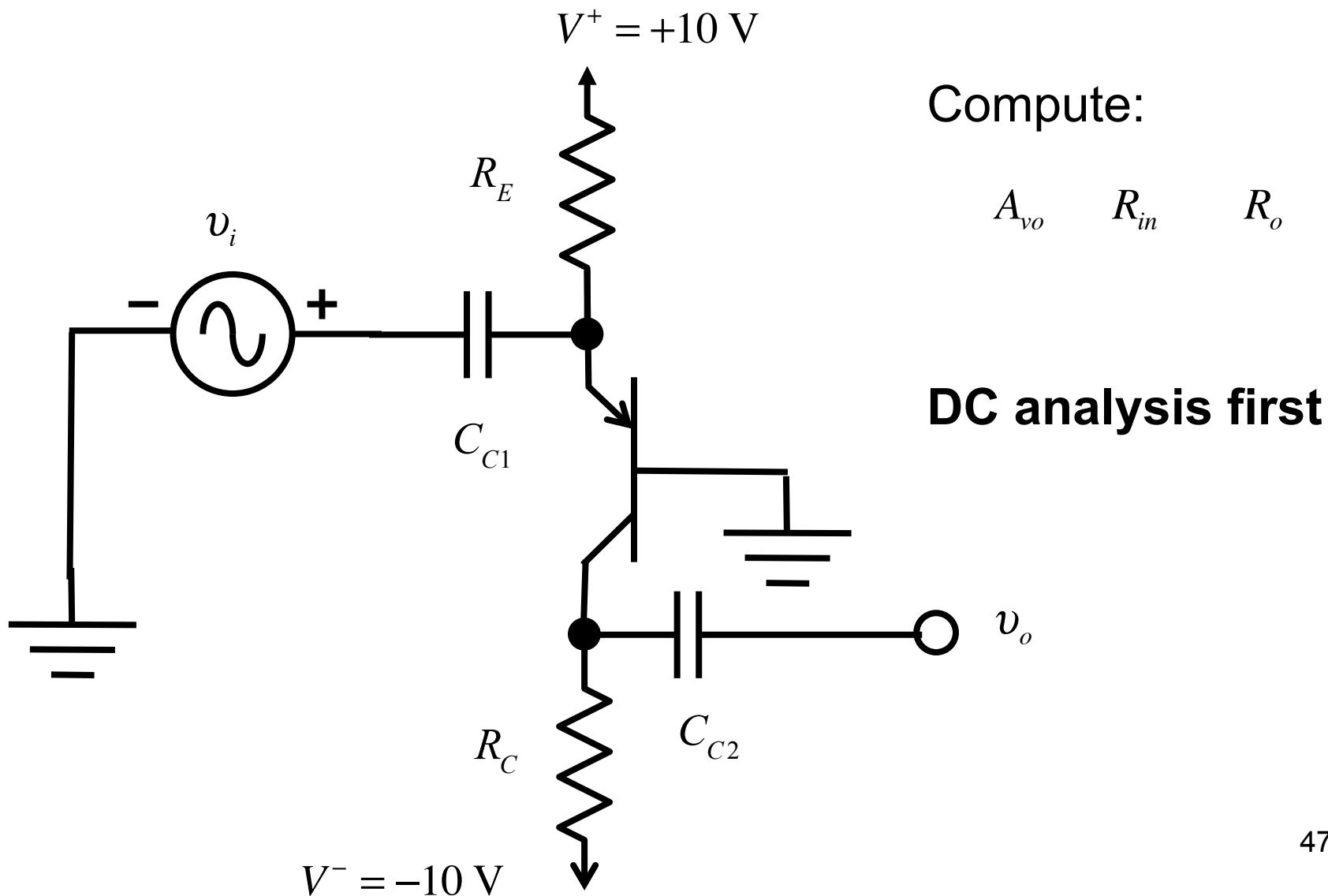

# DC analysis

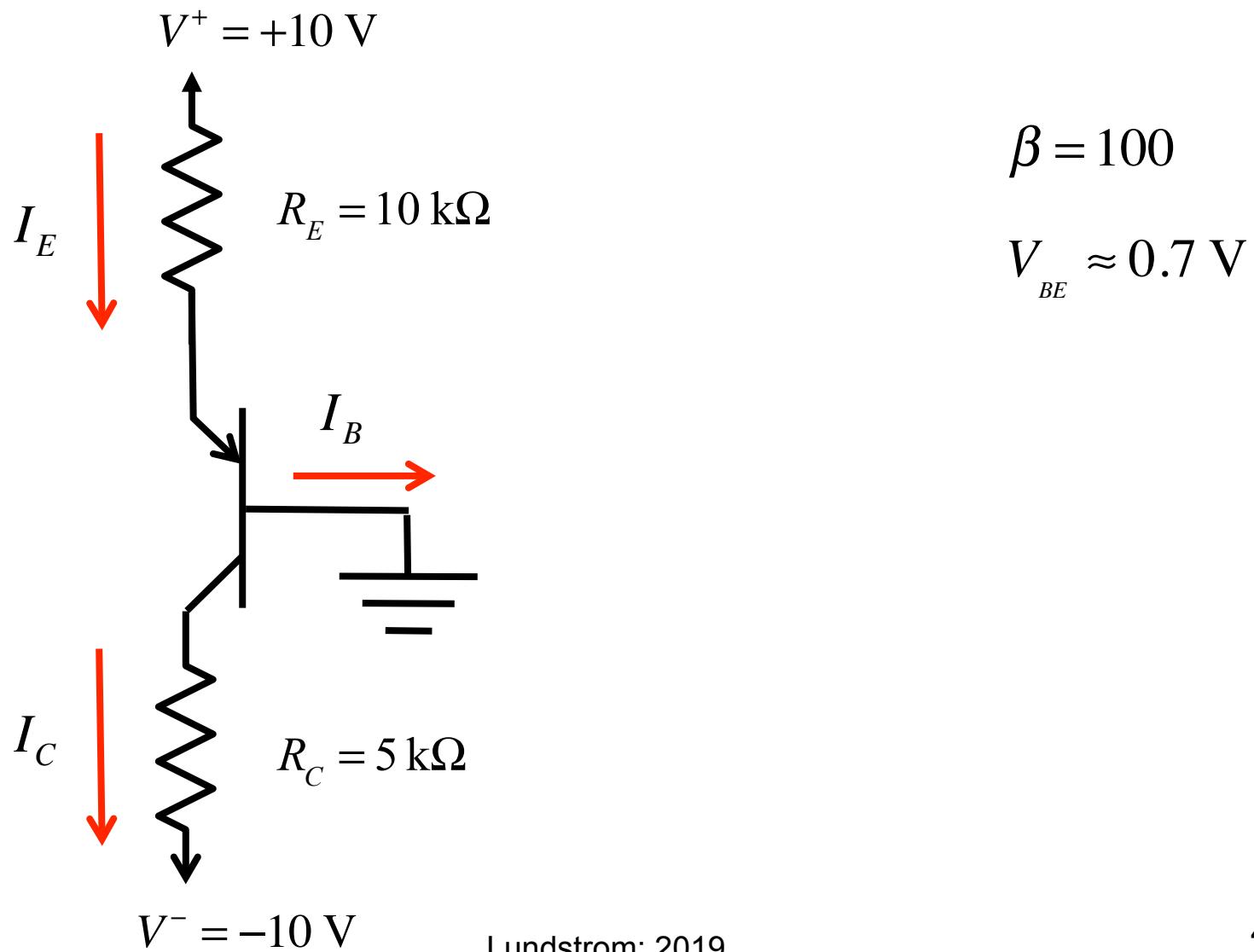

# DC analysis

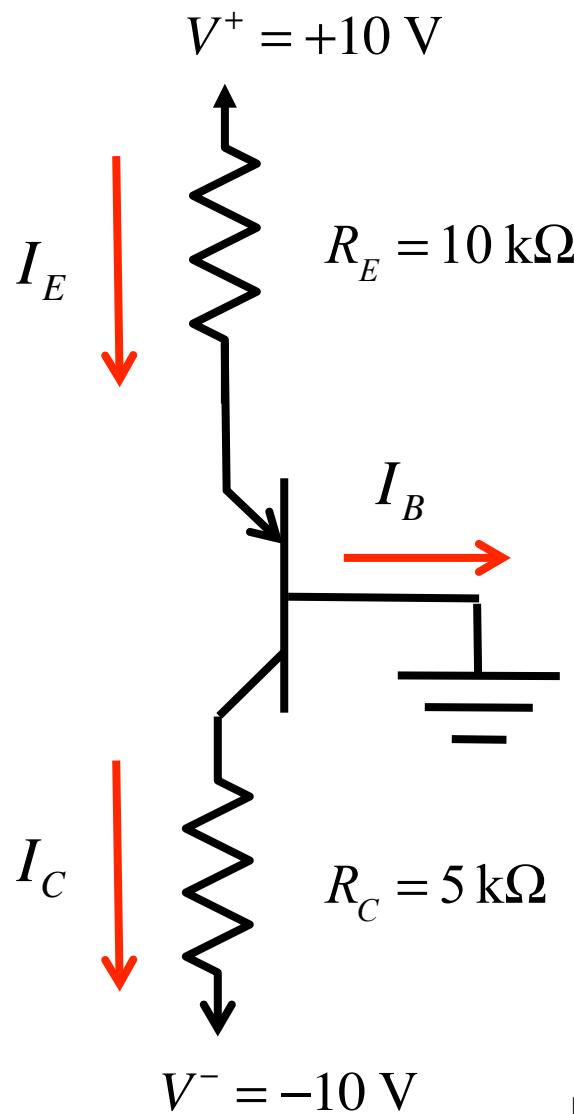

$$\beta = 100$$

$$V_{BE} \approx 0.7 \text{ V}$$

$$I_E = 0.93 \text{ mA}$$

$$I_C = 0.92 \text{ mA}$$


$$V_C = -5.4 \text{ V}$$

$$V_E = +0.7 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = 35.4 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = 2.8 \text{ k}\Omega$$

# Realistic Common base amplifier

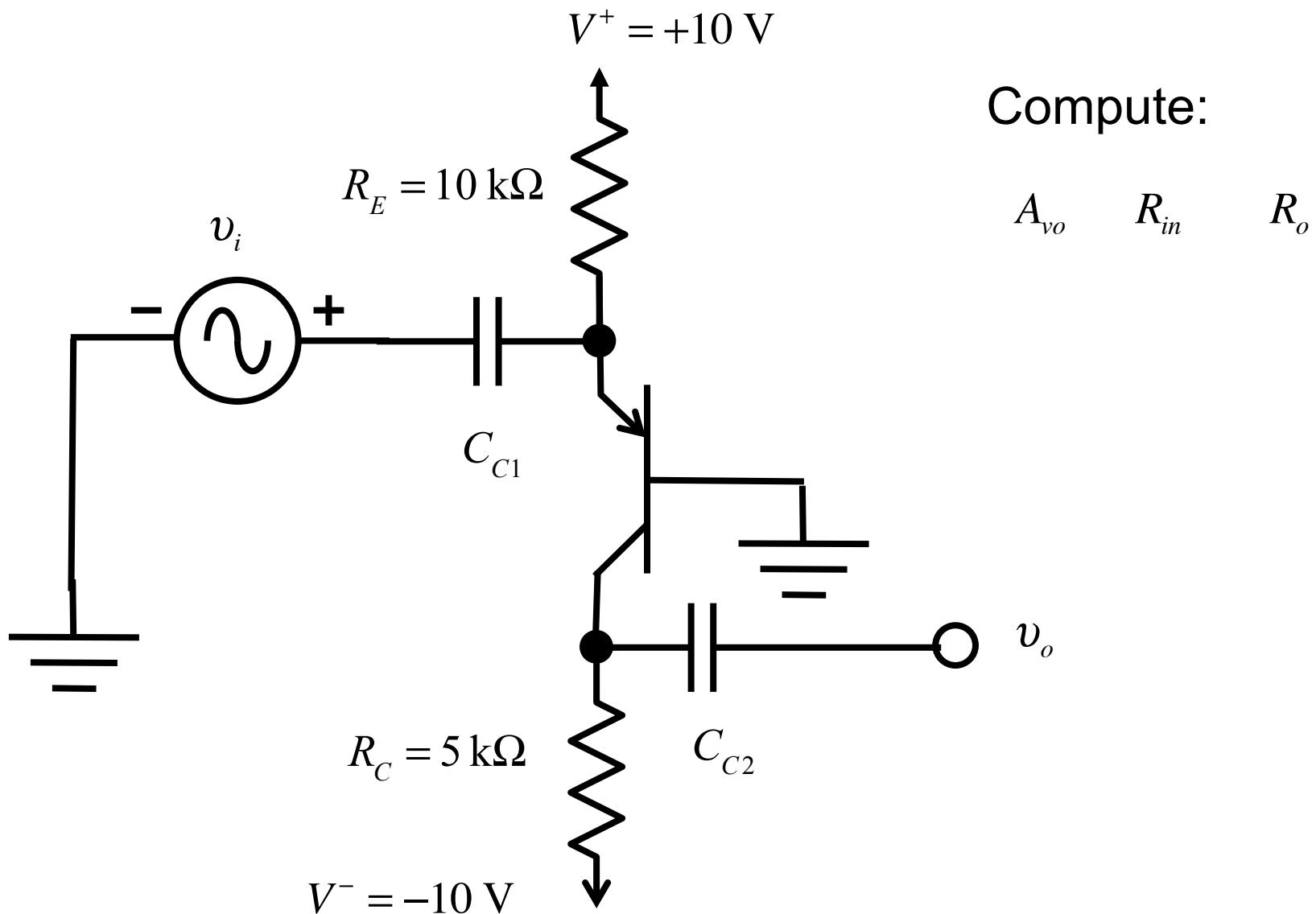


# Outline

---

- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG
- 4) Common base example
- 5) CC (emitter follower) / CD (source follower)**
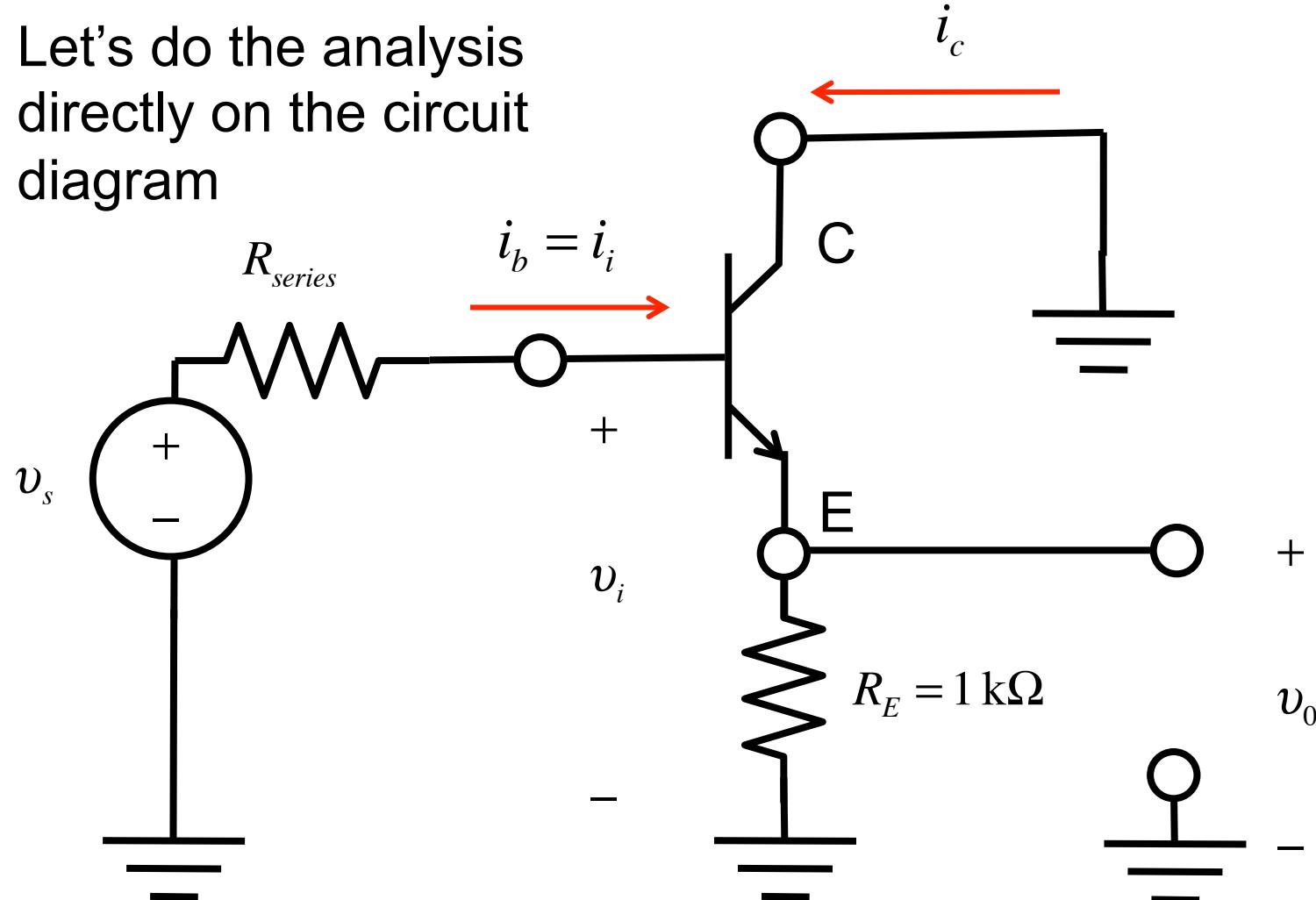
# Common collector (emitter follower)

Let's do the analysis directly on the circuit diagram



# CC by inspection

---

$$A_{v_o} = \frac{v_o}{v_i} = +\frac{(\beta+1)R_E}{r_\pi + (\beta+1)R_E}$$

$$R_{in} = r_\pi + (\beta+1)R_E$$

$$R_o = R_E \parallel \left( \frac{r_\pi + R_{series}}{\beta+1} \right)$$

$$A_{v_o} \approx 1$$

Emitter follower

CC is not a unilateral amplifier

# CC by inspection

---

$$A_{v_o} = \frac{v_o}{v_i} = + \frac{(\beta+1)R_E}{r_\pi + (\beta+1)R_E}$$

$$R_{in} = r_\pi + (\beta+1)R_E$$

$$R_o = R_E \parallel \left( \frac{r_\pi + R_{series}}{\beta+1} \right)$$

$$A_{v_o} = \frac{v_o}{v_i} = + \frac{R_E}{\frac{r_\pi}{\beta+1} + R_E} = \frac{R_E}{r_e + R_E}$$

$$R_{in} = r_\pi + (\beta+1)R_E = (\beta+1)(r_e + R_E)$$

$$R_o = R_E \parallel \left( r_e + \frac{R_{series}}{\beta+1} \right)$$

Hybrid pi model


Lundstrom: 2019

T model


54
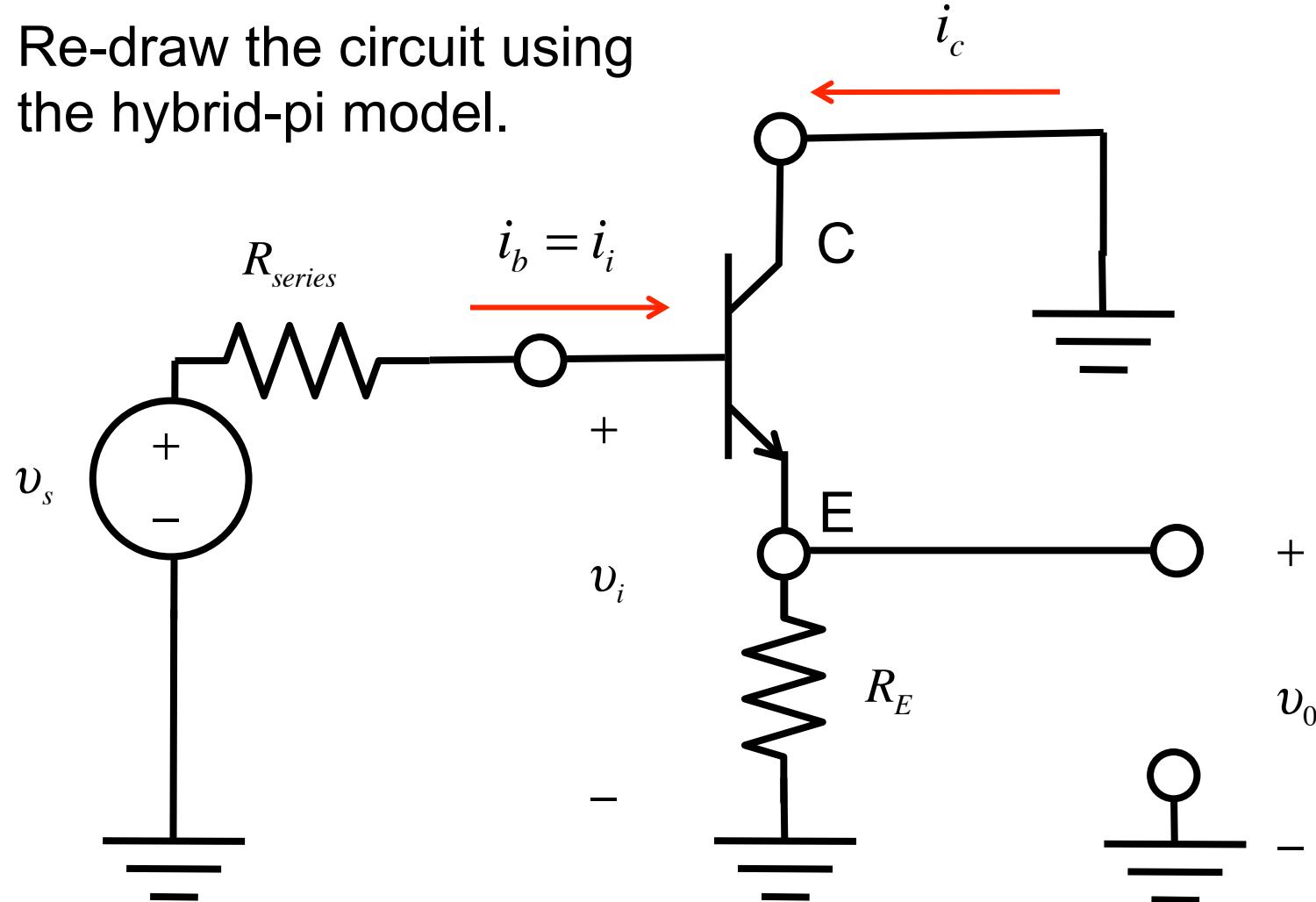
# Common collector analysis with hybrid-pi model

Re-draw the circuit using  
the hybrid-pi model.



# Small signal equivalent circuit

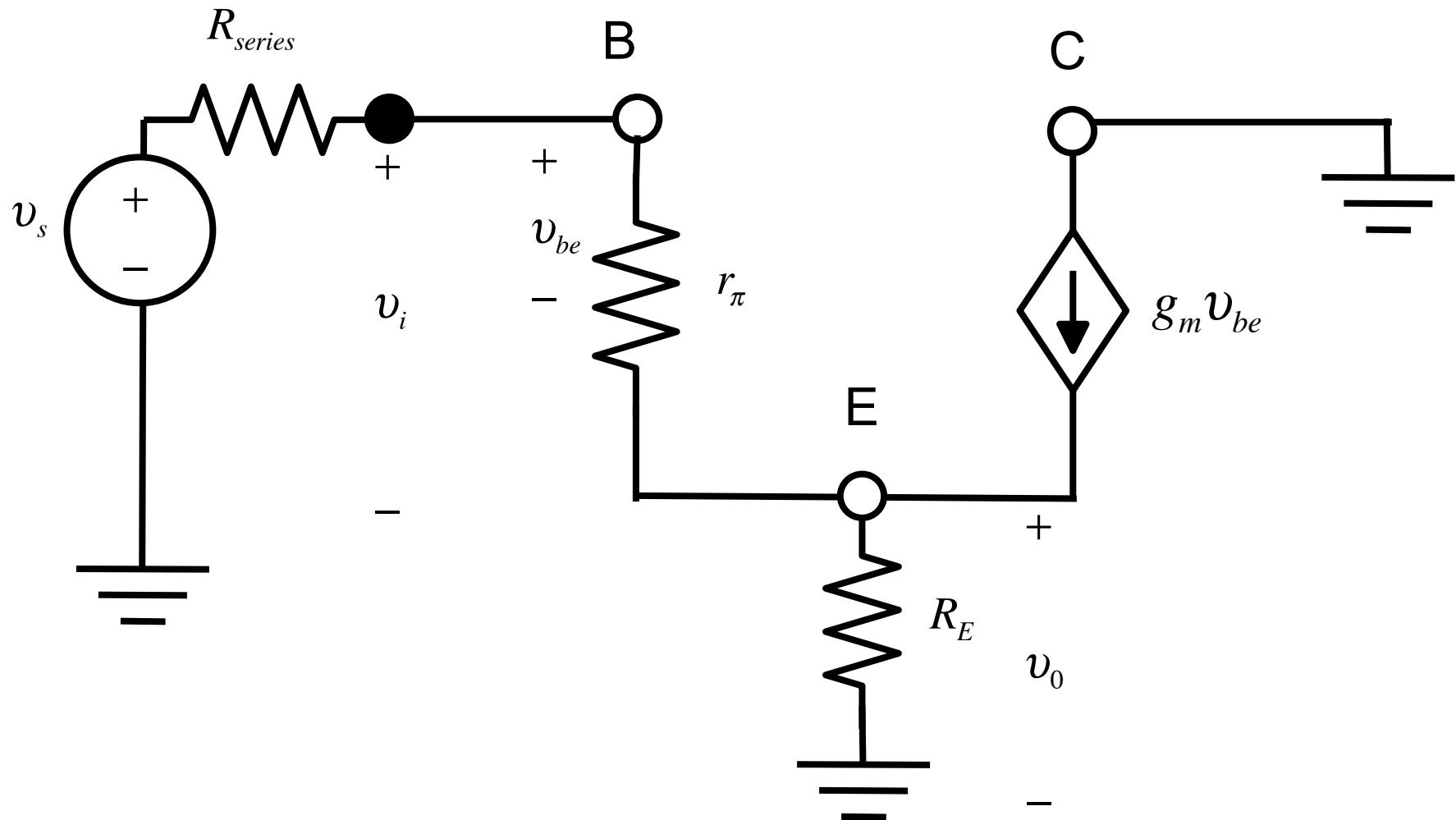

# Small signal analysis

---

$$A_{v_o} = ?$$

$$R_{in} = ?$$

$$R_E = 1 \text{ k}\Omega$$

$$R_o = ?$$

## CC numbers

$$A_{v_o} = \frac{v_o}{v_i} = +\frac{(\beta+1)R_E}{r_\pi + (\beta+1)R_E}$$

$$R_{in} = r_\pi + (\beta+1)R_E$$

$$R_o = R_E \parallel \left( \frac{r_\pi}{\beta+1} \right) \approx R_E \parallel \left( \frac{1}{g_m} \right)$$

$$I_C = 1.0 \text{ mA}$$

$$\beta = 100$$

$$g_m = 39 \text{ mS}$$

$$r_\pi = 2.6 \text{ k}\Omega$$

“emitter follower”

$$A_{v_o} = \frac{(101)1}{2.6 + (101)1} = +0.98$$

$$R_{in} = 2.6 \text{ k}\Omega + (101)1 \text{ k}\Omega = 104 \text{ k}\Omega$$


$$R_o = 1 \text{ k}\Omega \parallel \frac{2.6 \text{ k}\Omega}{101} = 25 \text{ }\Omega$$

$$\frac{1}{g_m} = \frac{1}{39} \text{ k}\Omega = 26 \text{ }\Omega$$



# CC is a “voltage buffer”

---

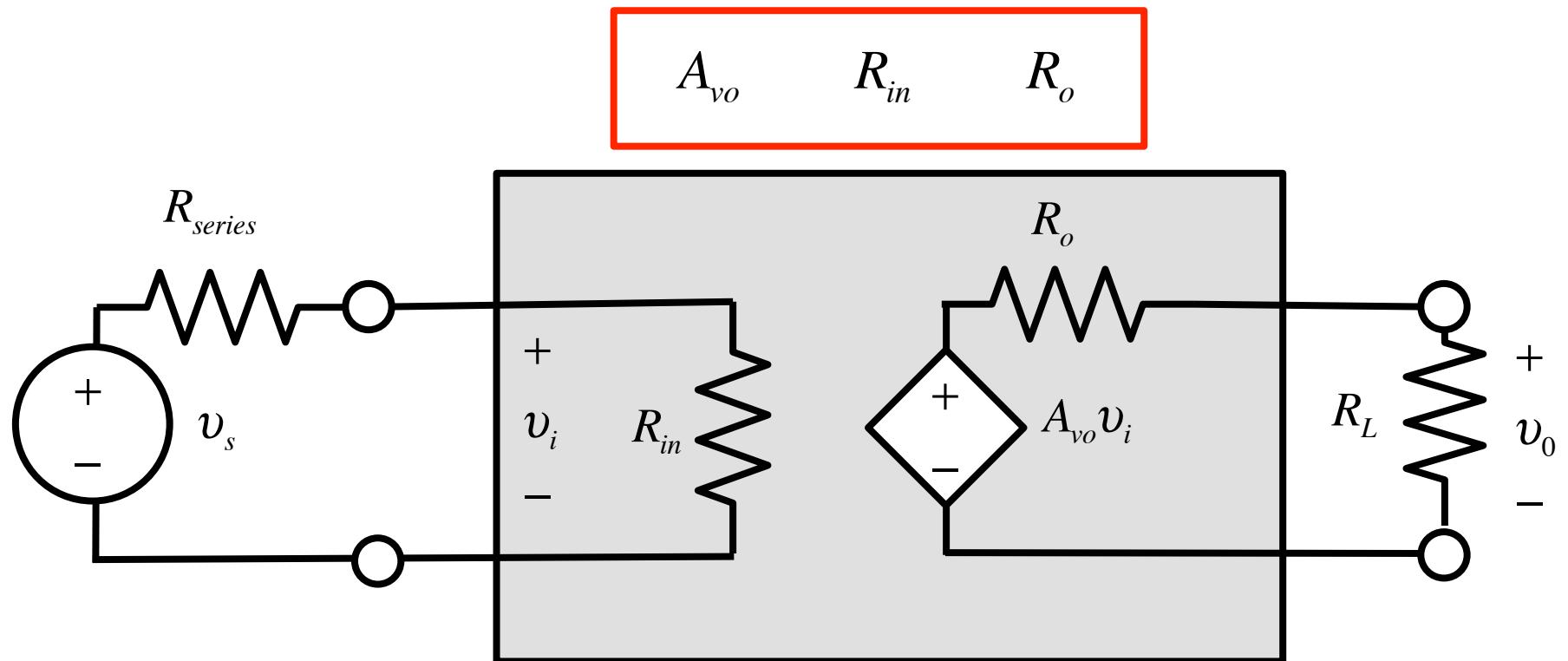


$$G_v = \frac{R_{in}}{R_{in} + R_{series}} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$

$$G_i = A_{vo} \frac{R_{in}}{R_L}$$


$$G_p = G_v G_i$$

## CC to CD

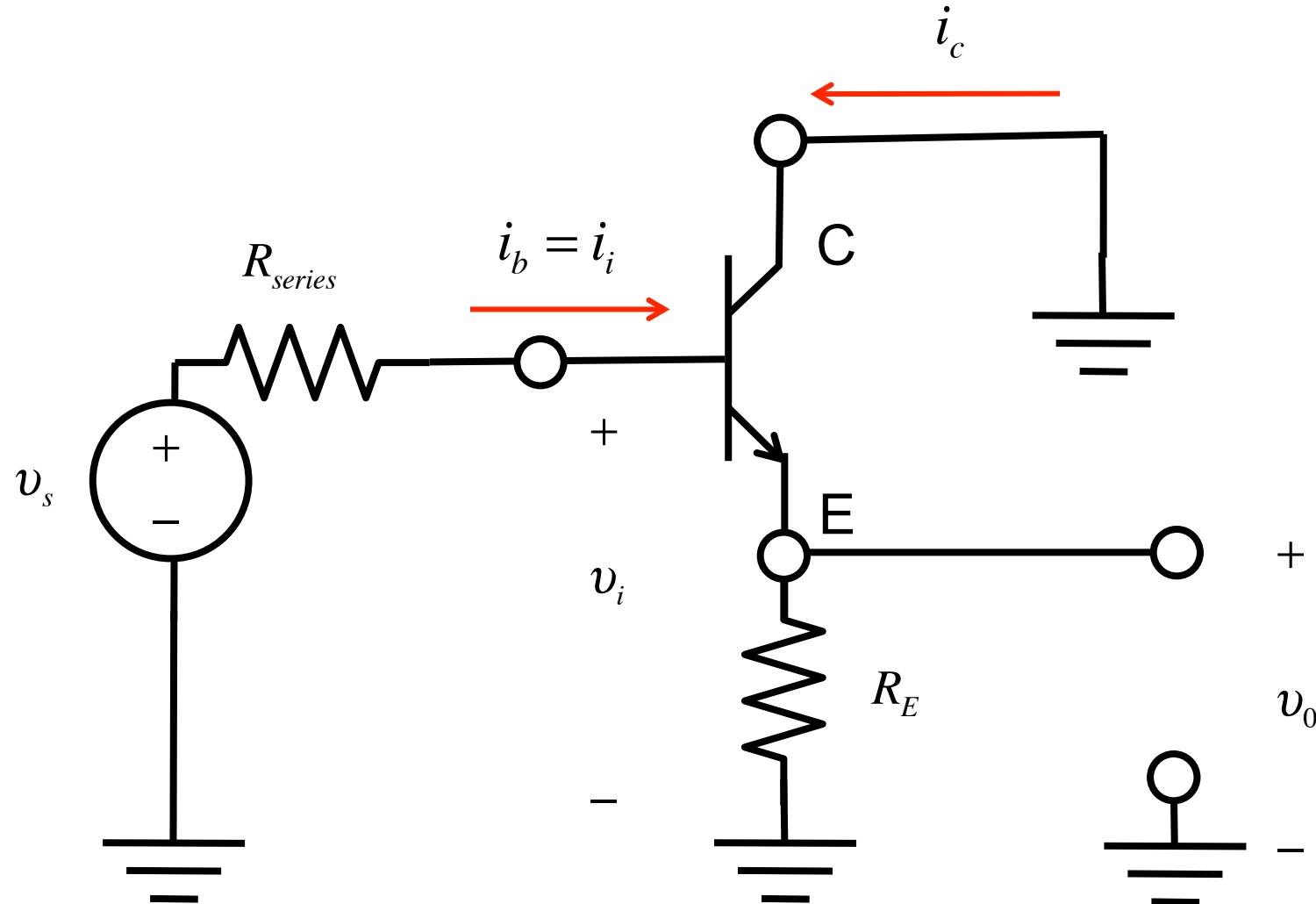
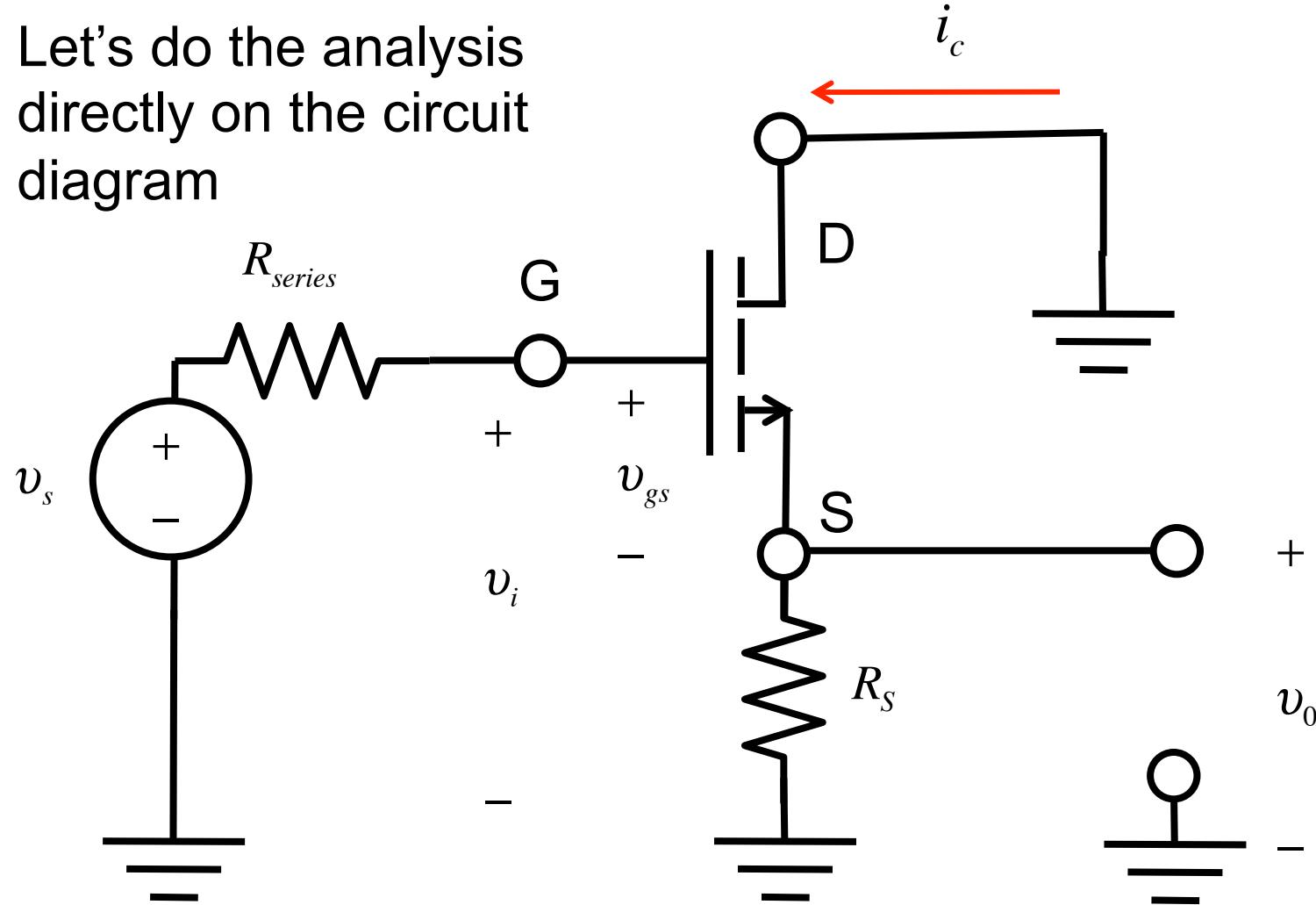
# Common Drain (Source follower)

Let's do the analysis directly on the circuit diagram



## CC vs. CD

source follower

$$A_{v_o} = \frac{v_o}{v_i} = + \frac{(\beta+1)R_E}{r_\pi + (\beta+1)R_E}$$


$$R_{in} = r_\pi + (\beta+1)R_E$$

$$R_o = R_E \parallel \left( \frac{r_\pi}{\beta+1} \right) \approx R_E \parallel \left( \frac{1}{g_m} \right)$$

$$A_{v_o} = \frac{v_o}{v_i} = + \frac{g_m R_S}{1 + g_m R_S}$$

$$R_{in} = \infty$$
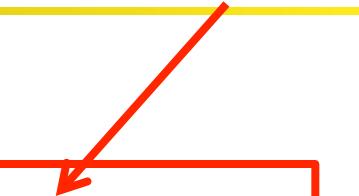
$$R_o = R_S \parallel \left( \frac{1}{g_m} \right)$$



# Outline

---

- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG
- 4) Common base example
- 5) CC (emitter follower) / CD (source follower)

# BJT Amplifier summary

## Common emitter

$$A_{v_o} = -g_m R_C$$

< 0, | high |

$$R_{in} = r_\pi$$

moderate

$$R_o = R_C$$

moderate

## Common base

$$A_{v_o} = +g_m R_C$$

>0, | high |

$$R_{in} = R_E \parallel \frac{r_\pi}{\beta+1}$$

low

$$R_o = R_C$$

moderate

## Common collector

$$A_v = \frac{(\beta+1)R_E}{r_\pi + (\beta+1)R_E}$$

~1

$$R_{in} = r_\pi + (\beta+1)R_E$$

high

$$R_o = R_E \parallel \left( \frac{r_\pi}{\beta+1} \right)$$

low

# BJT Amplifier summary

---

## Common emitter with $R_E$

$$A_{v_o} = -\frac{r_\pi}{r_\pi + (\beta + 1)R_E} (g_m R_C) \quad < 0, |\text{moderate}|$$

$$R_{in} = r_\pi + (\beta + 1)R_E \quad \text{high}$$

$$R_o = R_C \quad \text{moderate}$$

# MOS Amplifier summary

---

**Common source**

**Common gate**

**Common drain**

# Summary

---

The **Common Emitter** amplifier has a voltage gain that is large in magnitude and with a **negative** sign. It has moderate input and output resistance.

The **Common Source** amplifier has a voltage gain that is moderate in magnitude and with a **negative** sign. It has a high input resistance and moderate output resistance.

The **Common Base** amplifier has a voltage gain that is large in magnitude and with a **positive** sign. It has low input resistance and moderate output resistance.

The **Common Gate** amplifier has a voltage gain that is Imoderate in magnitude and with a **positive** sign. It has fairly low input resistance and moderate output resistance.

# Summary

---

The **Common Collector (emitter follower) amplifier** has a voltage gain of about one, It has high input resistance and a very low output resistance.

The **Common Drain (source follower) amplifier** has a voltage gain of a little less than one, It has a very high input resistance and a moderately low output resistance.

# Basic Amplifier Configurations: II

---

- 1) Basic amplifier considerations
- 2) CE / CS
- 3) CB / CG
- 4) Common base example
- 5) CC (emitter follower) / CD (source follower)

