

Spring 2019 Purdue University

ECE 255: L25

Cascode Amplifiers


(Sedra and Smith, 7th Ed., Sec. 8.5)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA

Announcements

- 1) HW8 due at 5:00 PM Friday, March 29
- 2) Exam 3 is at 6:30 PM, Tuesday, April 2
- 3) Spice Project 3 will be due on April 17

CS amplifier

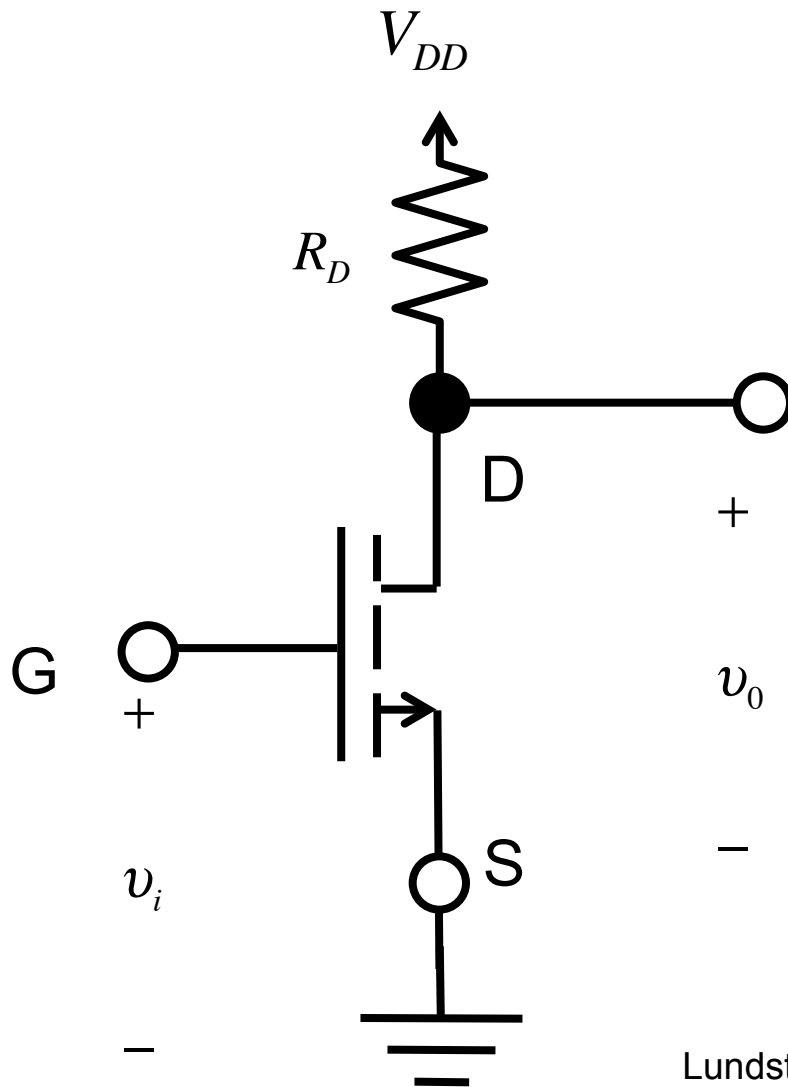


$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_D$$

$$R_{in} = \infty$$

$$R_o = R_D$$

CS amplifier with active load

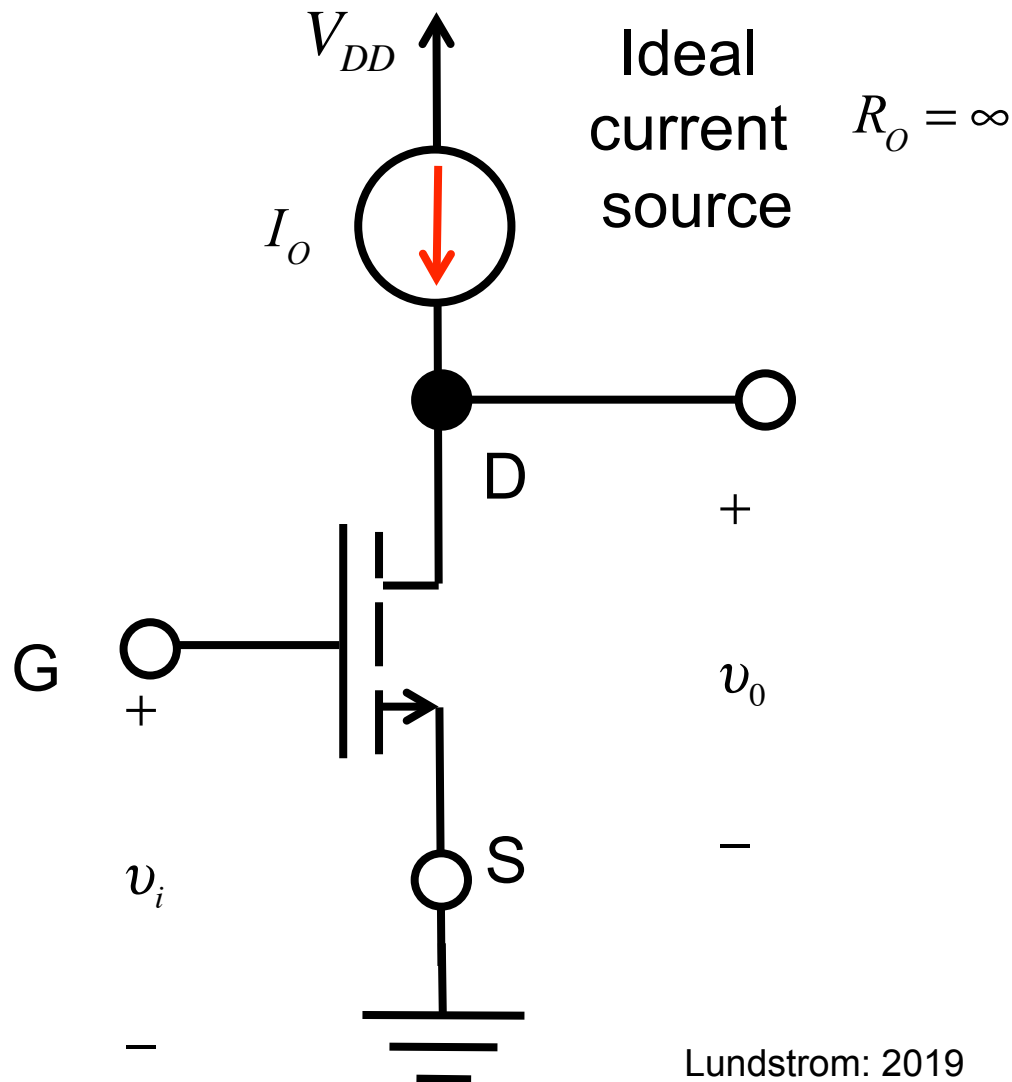

$$A_{v_o} = \frac{v_o}{v_i} = -g_m r_o$$


$$A_{v_o} = -A_0$$

$$R_{in} = \infty$$

$$R_o = r_o$$

But this gain is not large enough

Solution: cascade amplifiers

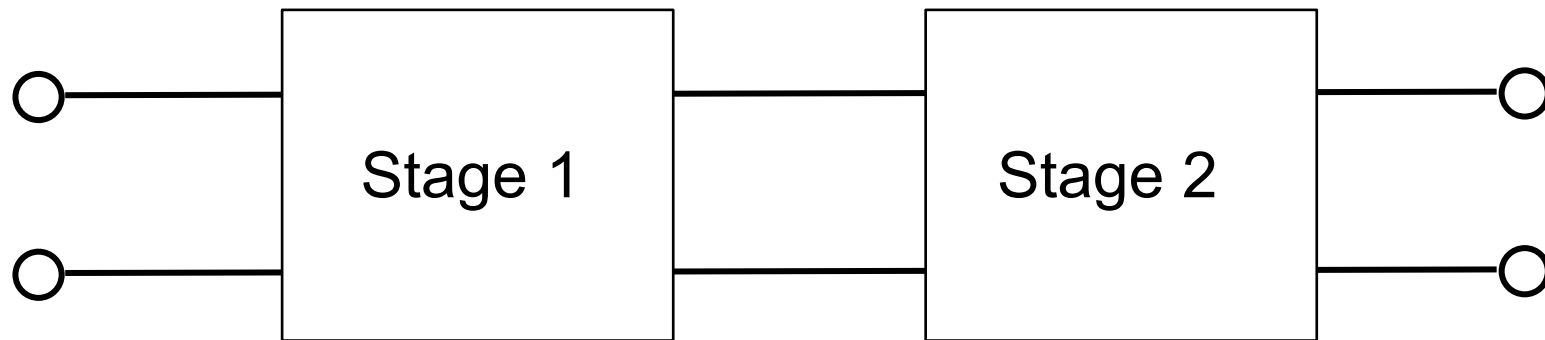


Examples: CE:CE

CC:CE


CE:CC

CE:CB or CS:CG = "cascode"

Basic cascode

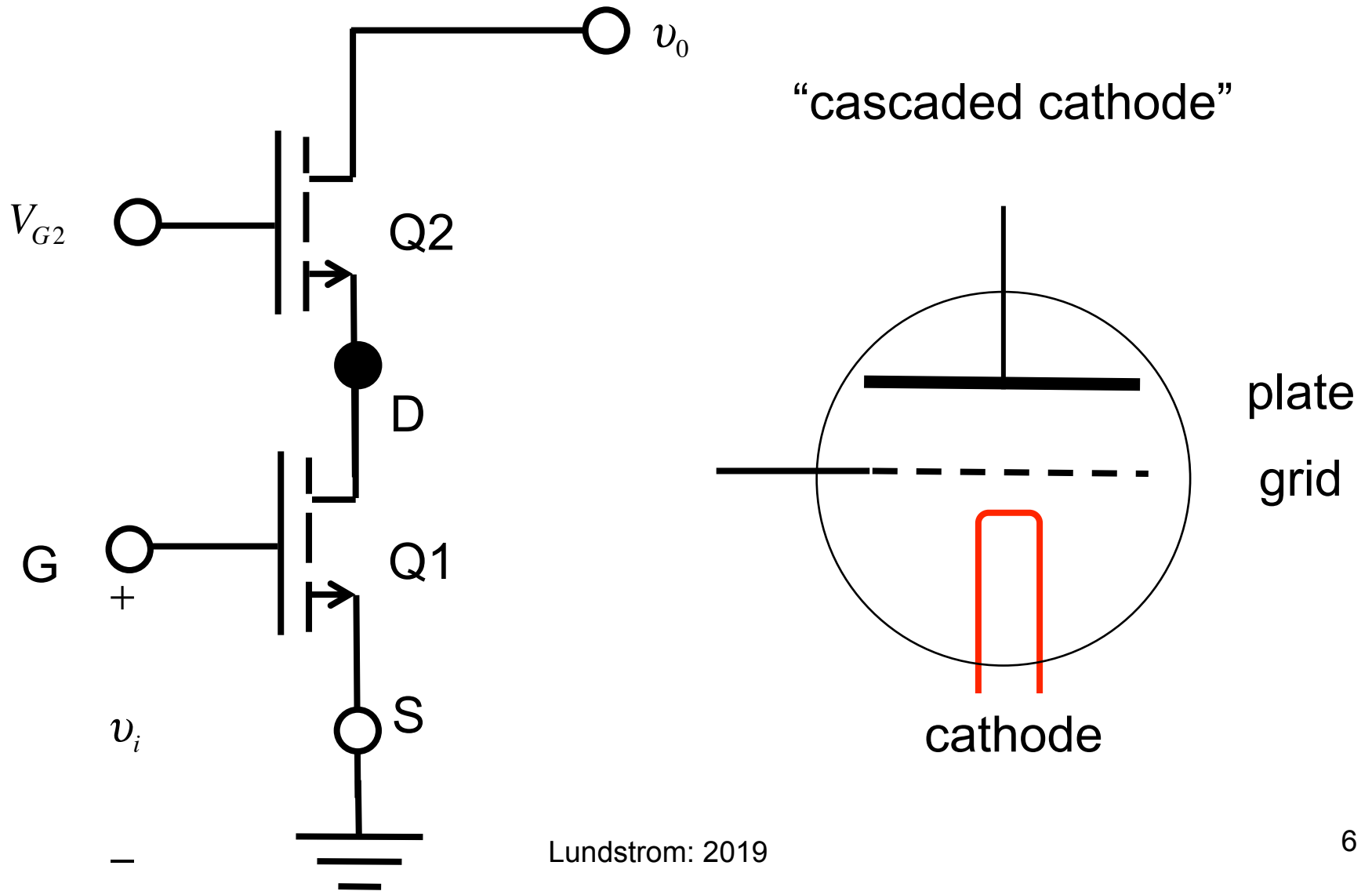

Cascode amplifiers

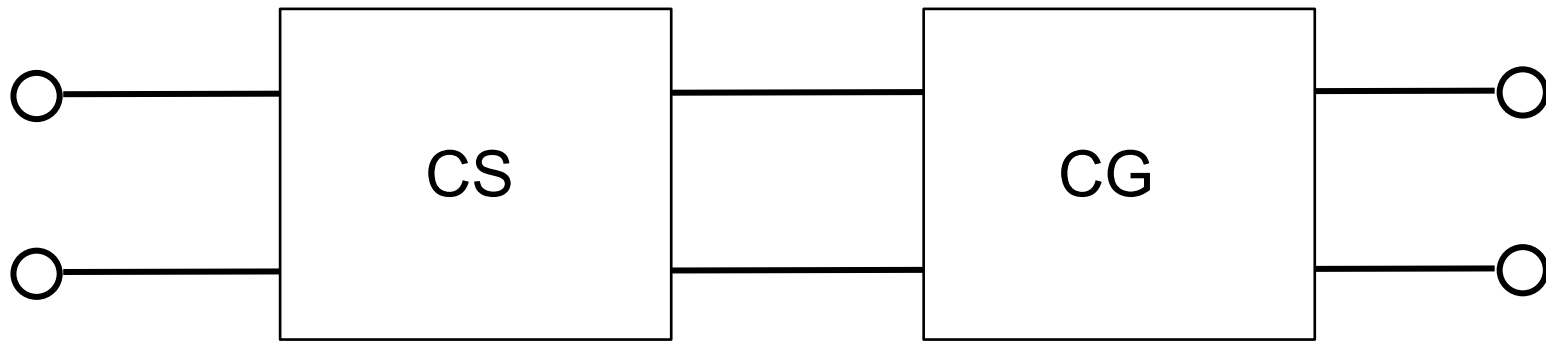


Discrete transistor version first

Then MOS IC cascodes

Outline

- 1) Introduction
- 2) Discrete cascode**
- 3) IC MOS cascode
- 4) Discussion
- 5) BJT cascode
- 6) Summary

Discrete CS:CG cascode

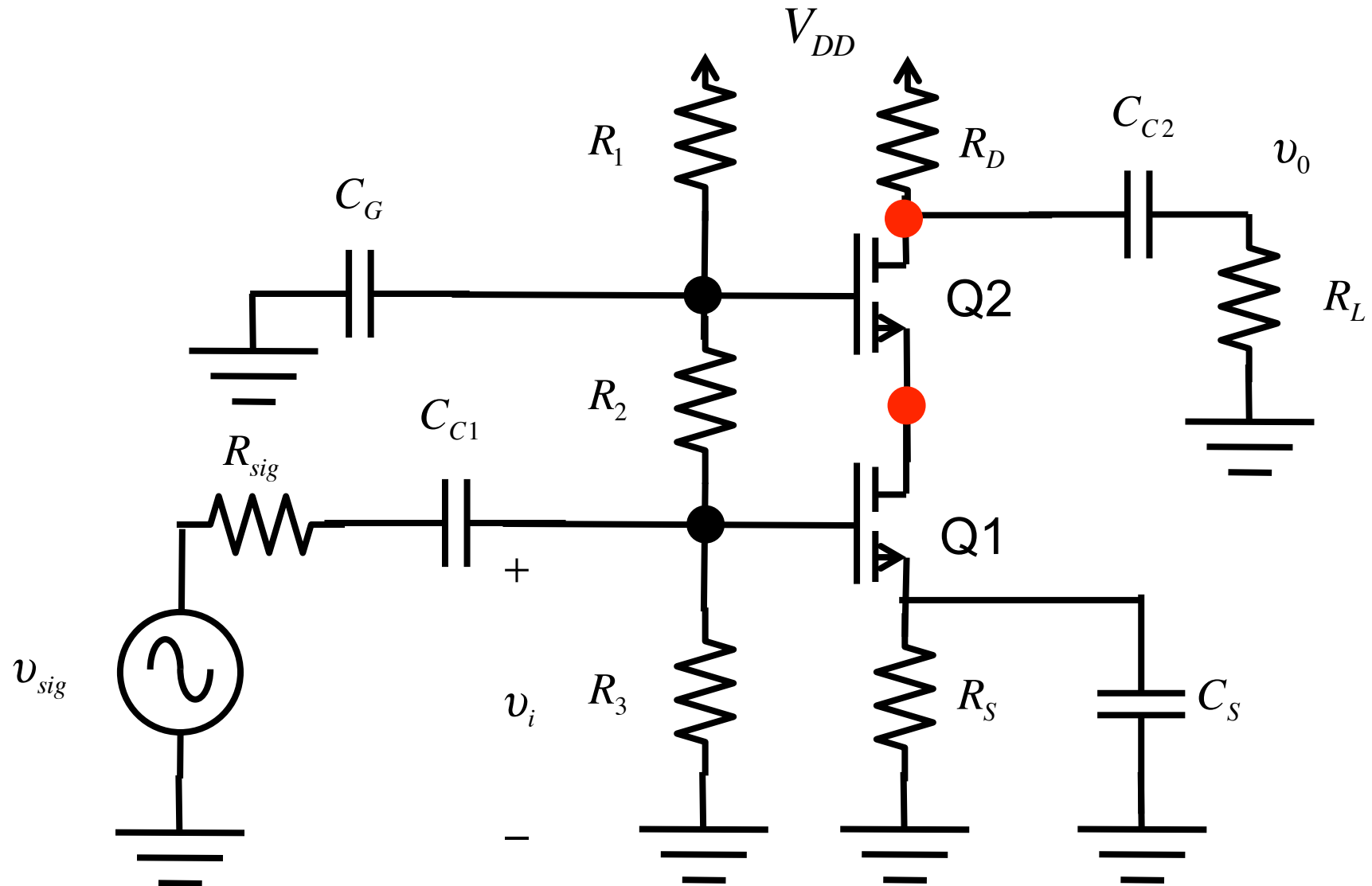


CS:CG discrete cascode (without bias resistors)

$$A_{v_o} = A_{v_1} \times A_{v_2}$$


$$R_o = R_D$$

$$A_{v_o} = -g_{m1} \left(\frac{1}{g_{m2}} \right) \times g_{m2} R_D$$

$$A_{v_o} = -g_{m1} R_D$$

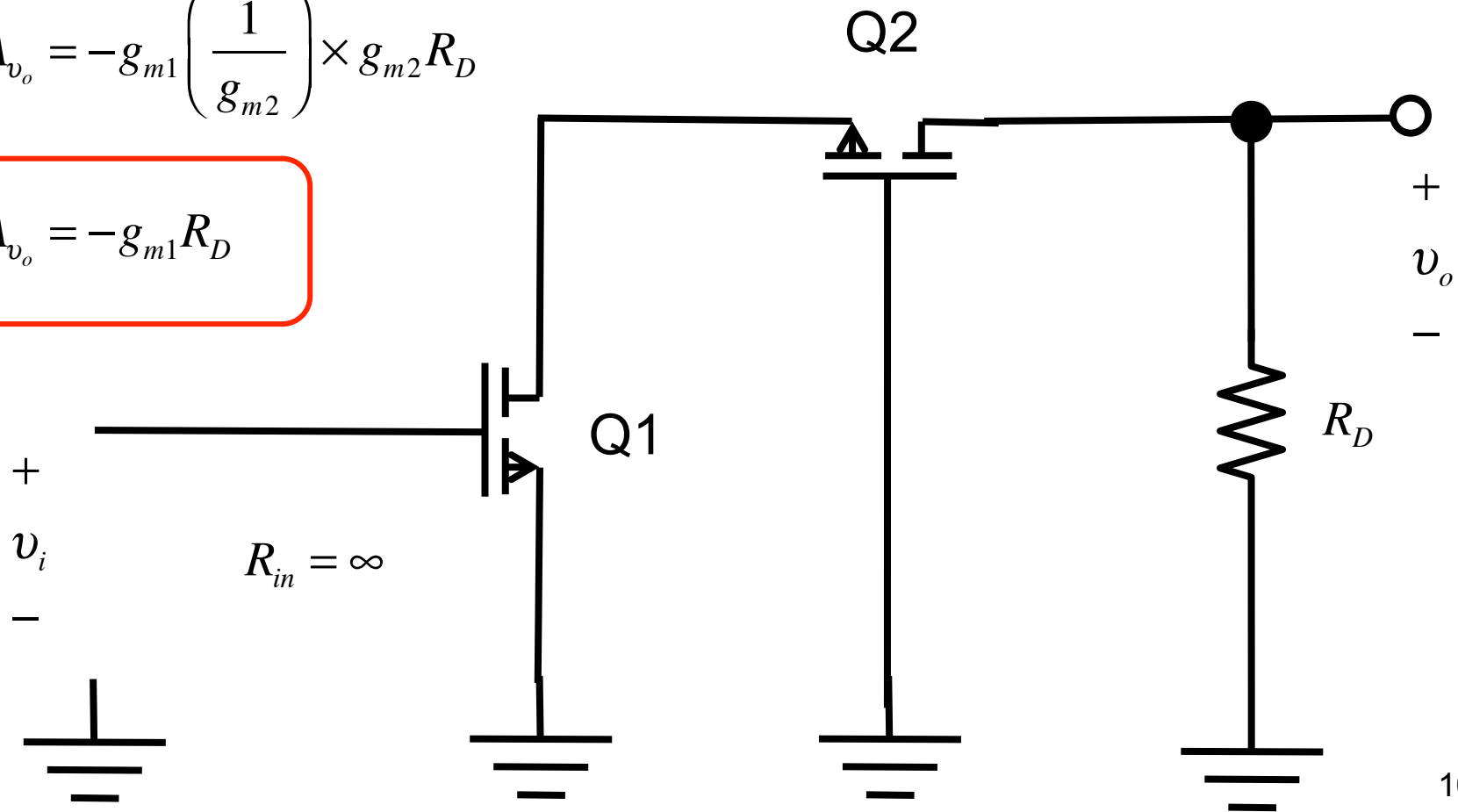

CS:CG cascode summary

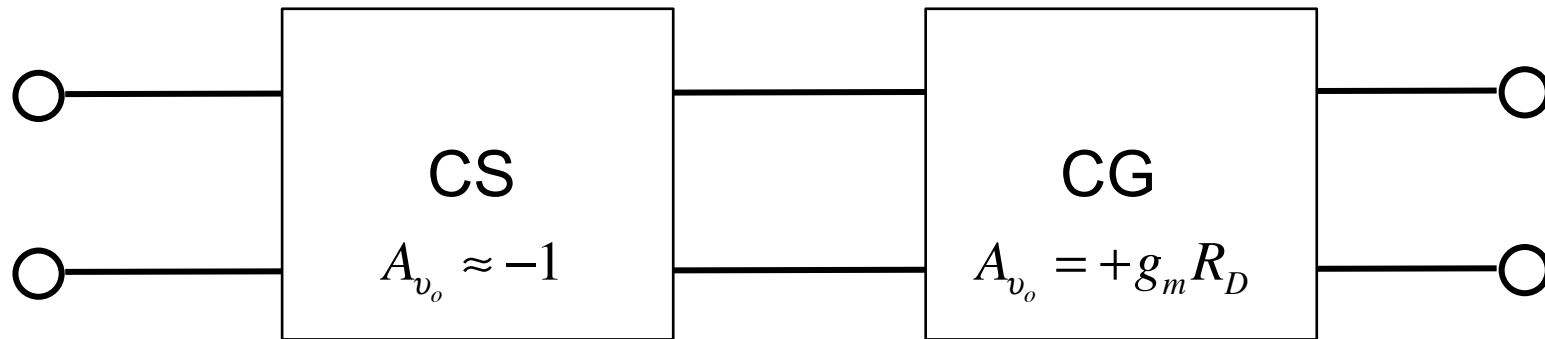

- Input resistance of CS
- Output resistance of CS
- Voltage gain of CS

(excellent high frequency response)


Outline

- 1) Introduction
- 2) Discrete cascode
- 3) IC MOS cascode**
- 4) Discussion
- 5) BJT cascode
- 6) Summary


CS:CG cascode (IC)

$$A_{v_o} = A_{v_1} \times A_{v_2}$$
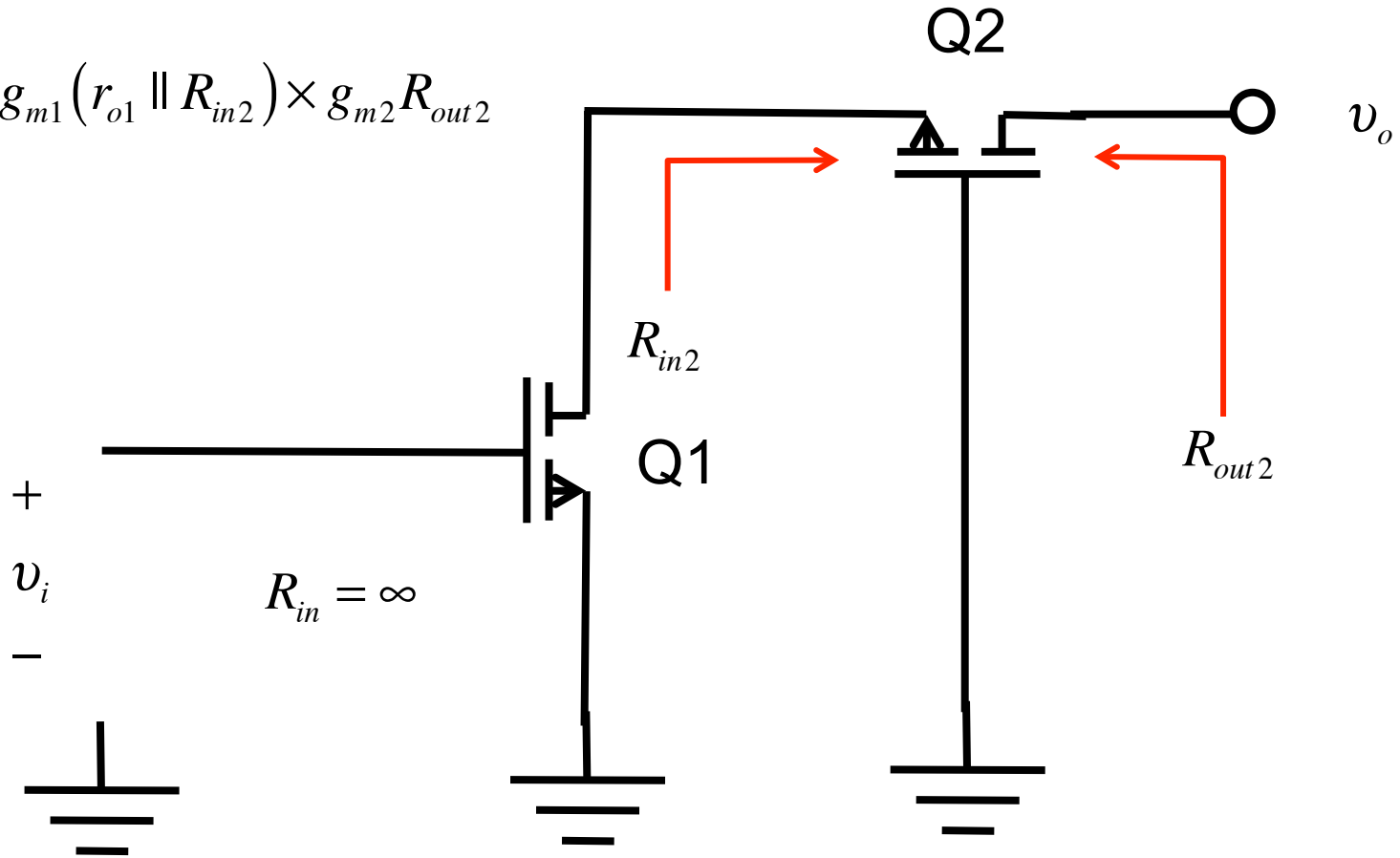
$$A_{v_o} = -g_{m1} (r_{o1} \parallel R_{in2}) \times g_{m2} R_{out2}$$



Recall L24

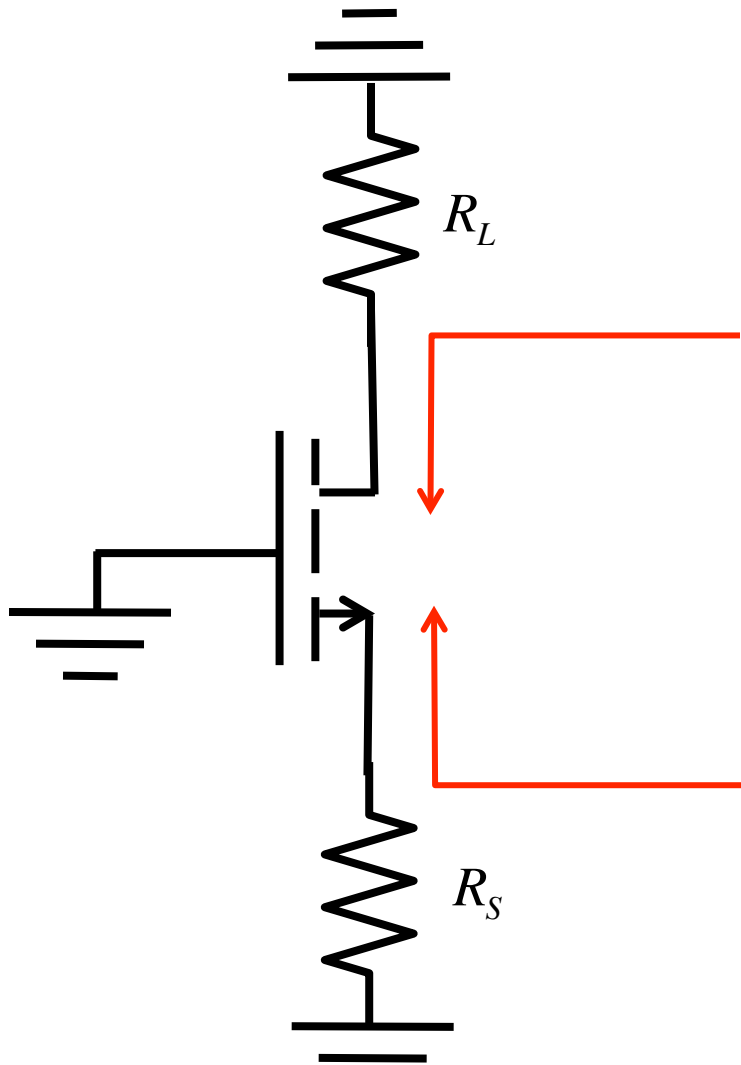

$$R_{out} = r_o + (1 + g_m r_o) R_{series}$$

$$R_{out} \approx r_o + (g_m r_o) R_S$$

$$R_{out} \approx (g_m r_o) R_S$$

$$R_{in} = \frac{(r_o + R_L)}{(1 + g_m r_o)}$$


$$R_{in} \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

First stage gain

$$A_{v_1} = -g_{m1}(r_{o1} \parallel R_{in2})$$

$$R_{in2} \approx \frac{1}{g_{m2}} + \frac{R_L}{g_{m2}r_{o2}}$$
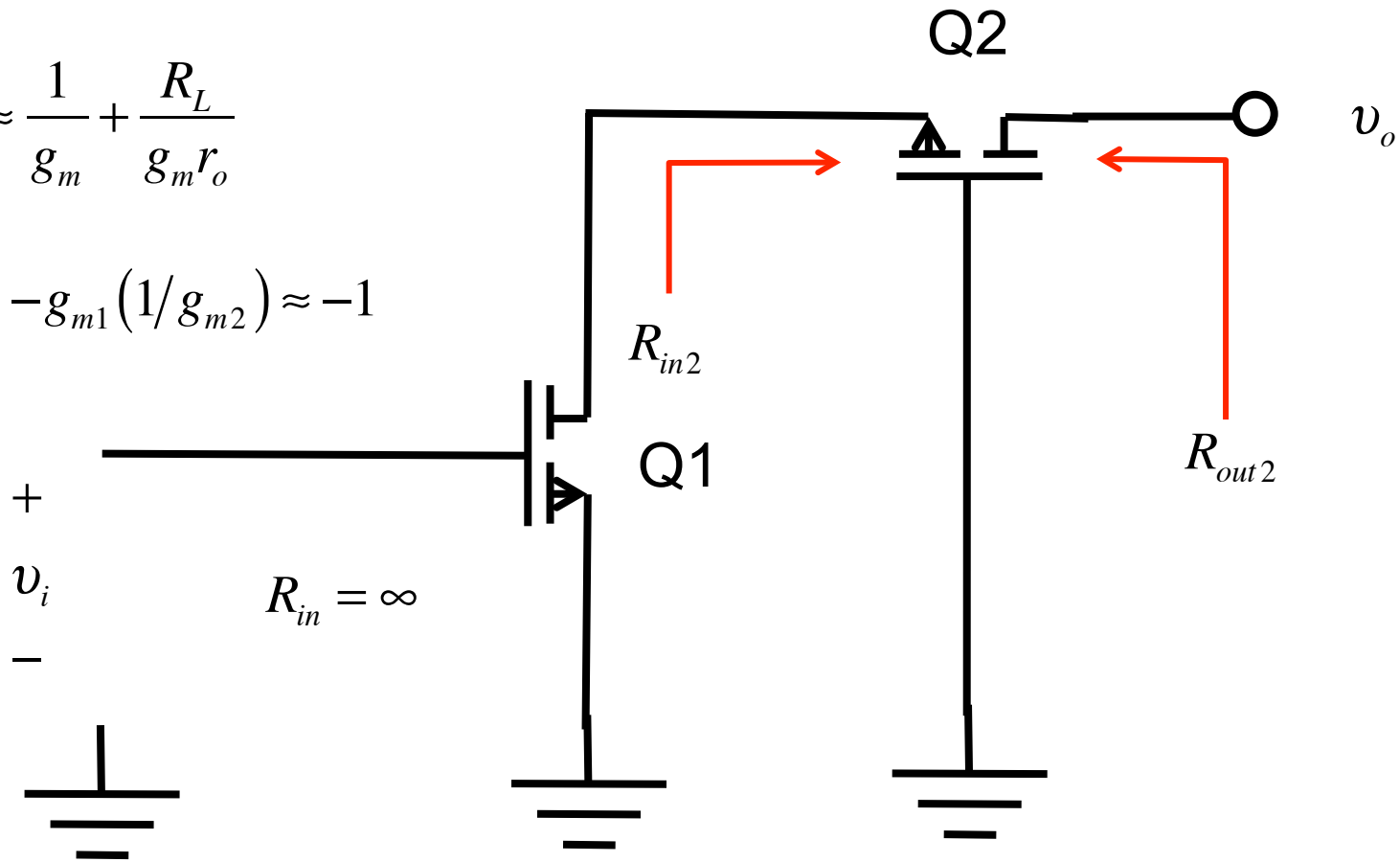
$$A_{v_1} = -g_{m1}(1/g_{m2}) \approx -1$$




Second stage gain

$$A_{v_2} = +g_{m2}R_{out2}$$

$$R_{out2} \approx r_{o2} + (g_{m2}r_{o2})R_S$$

$$R_{out2} \approx (g_{m2}r_{o2})r_{o1}$$
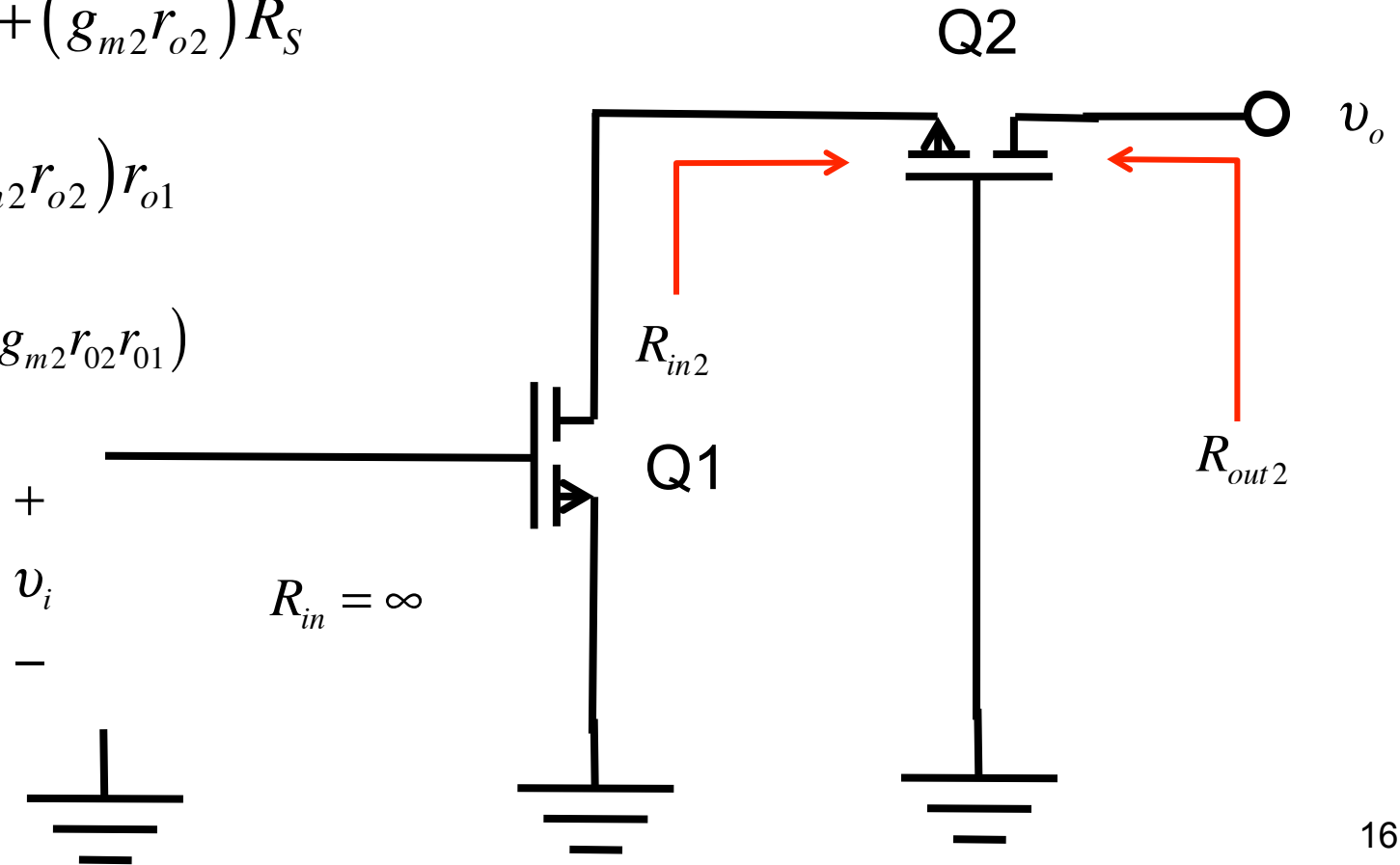
$$A_{v_2} = +g_{m2}(g_{m2}r_{o2}r_{o1})$$




Total gain

$$A_{v_o} = A_{v_1} \times A_{v_2}$$

$$A_{v_1} = -g_{m1} (1/g_{m2})$$

$$A_{v_2} = +g_{m2} (g_{m2} r_{o2} r_{o1})$$

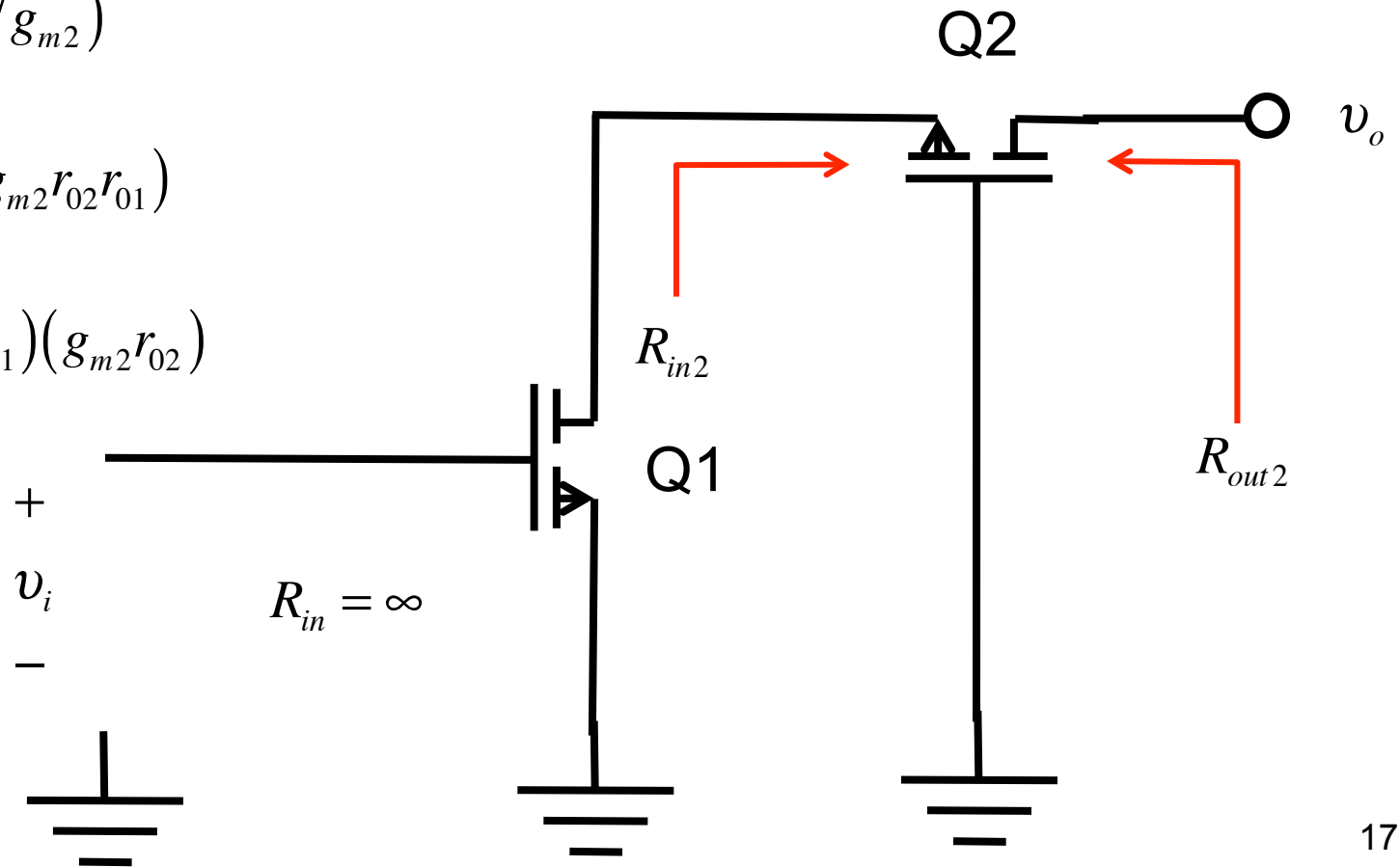
$$A_{v_o} = -(g_{m1} r_{o1}) (g_{m2} r_{o2})$$




Total gain of cascode

$$A_{v_o} = -(g_m r_0)^2$$

$$A_{v_o} = -A_0^2$$

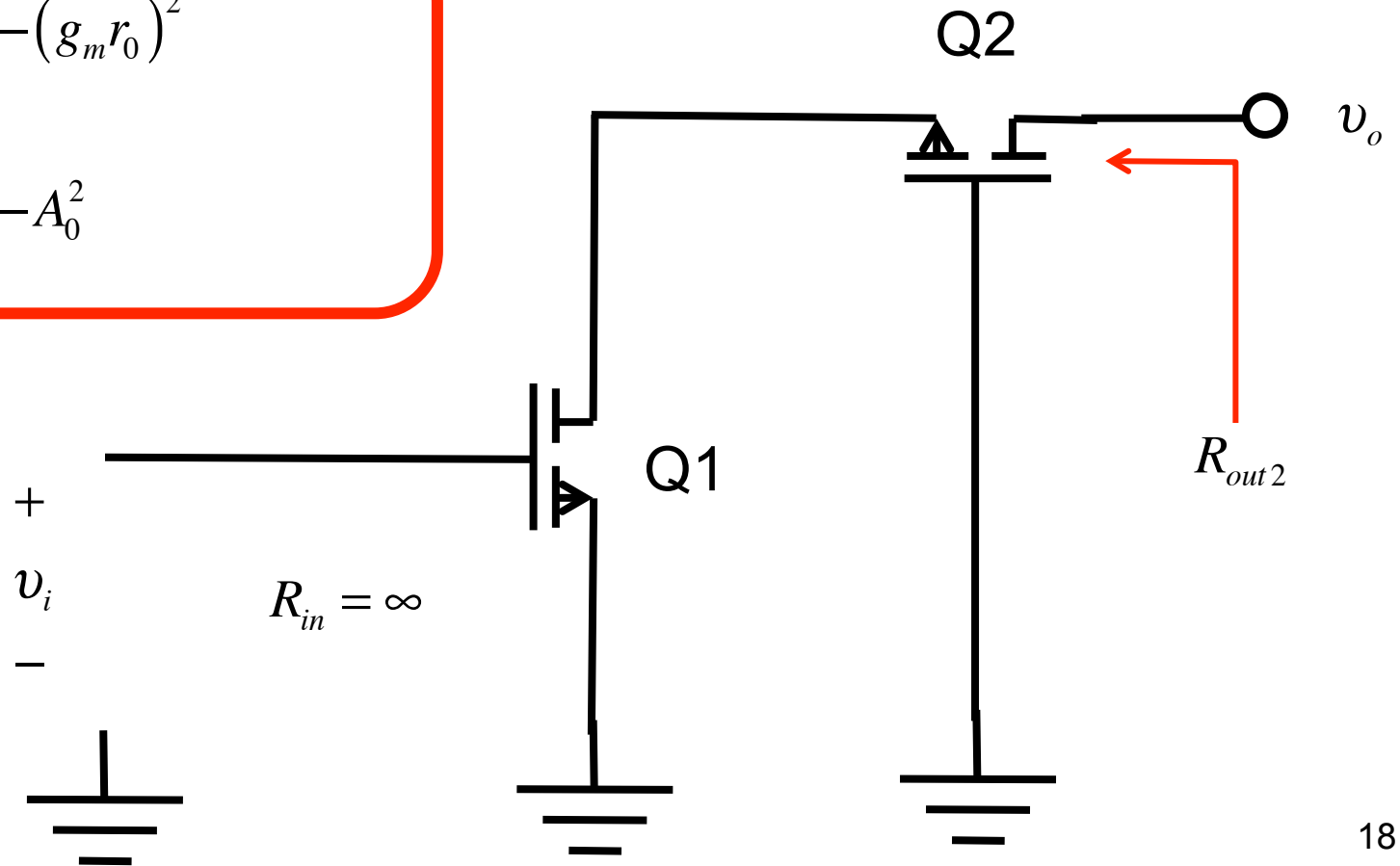

An easier way

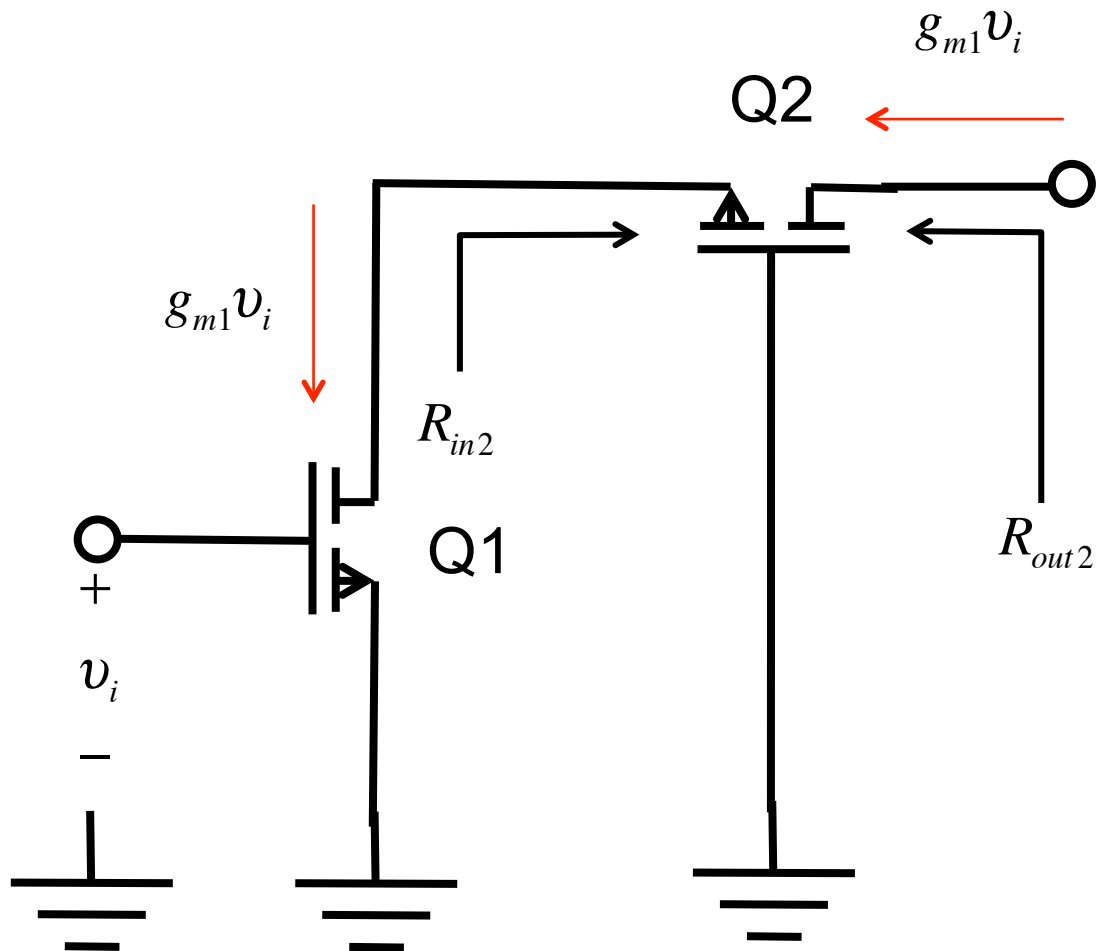


$$v_o = -(g_{m1}v_i)R_{out2}$$

$$R_{out2} \approx (g_{m2}r_{o2})r_{o1}$$

$$A_{v_i} = -(g_m r_o)^2$$

$$A_{v_o} = -A_0^2$$

Recall: CS amplifier with active load

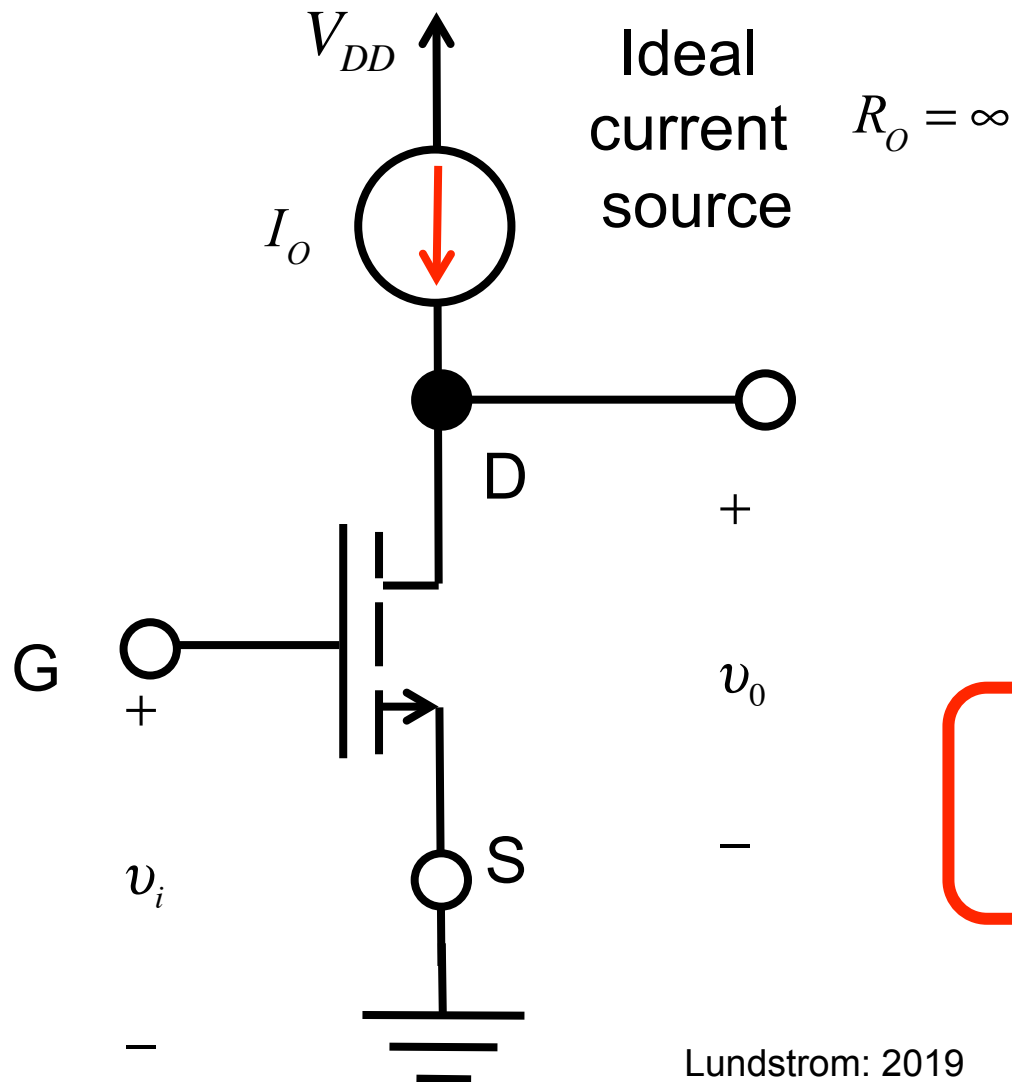

$$A_{v_o} = -g_m r_o$$


$$A_{v_o} = -A_0$$

Cascode:
$$A_{v_o} = -(A_0)^2$$


Outline

- 1) Introduction
- 2) Discrete cascode
- 3) IC MOS cascode
- 4) Discussion**
- 5) BJT cascode
- 6) Summary

Implementation

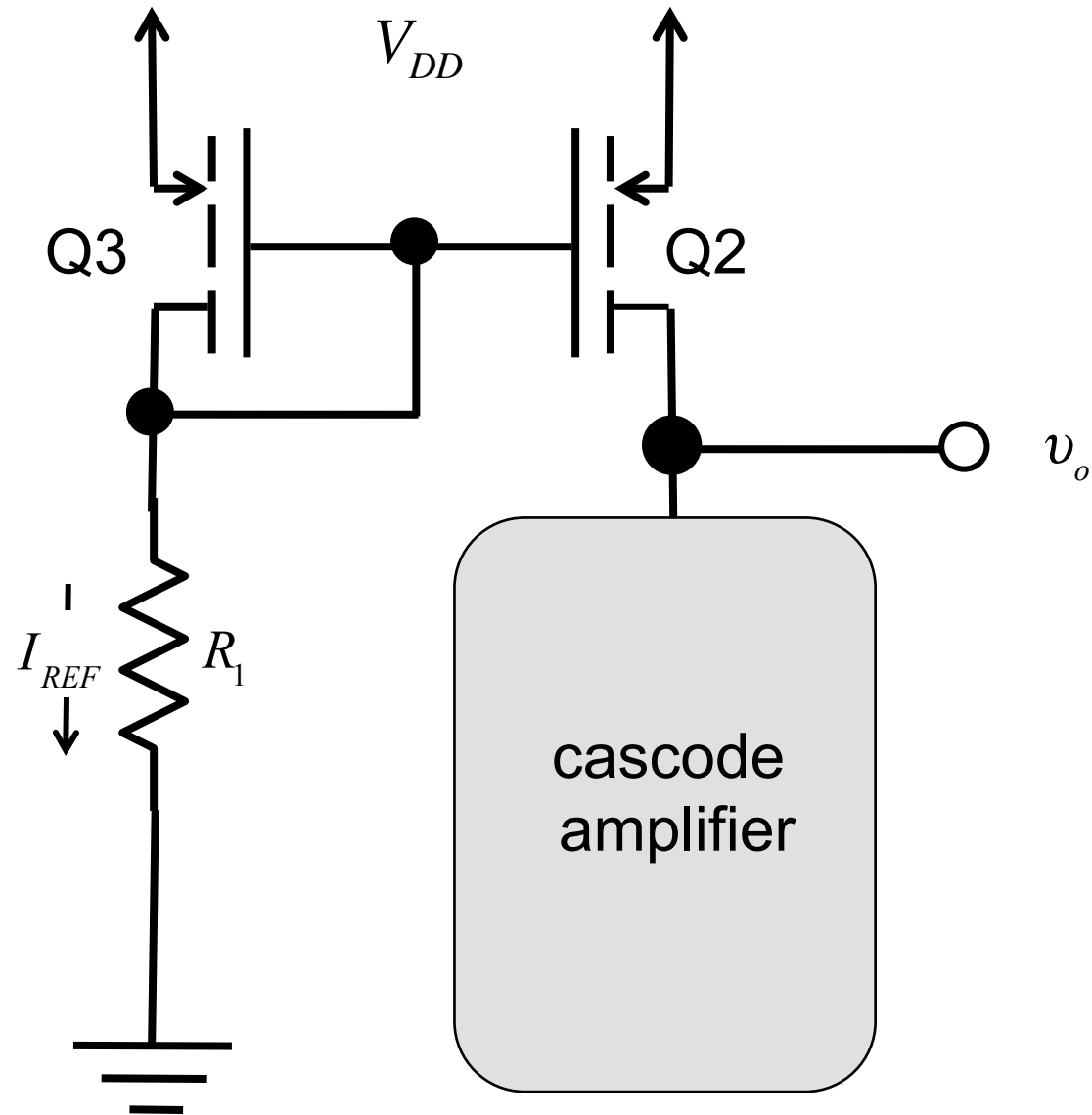

Implementation

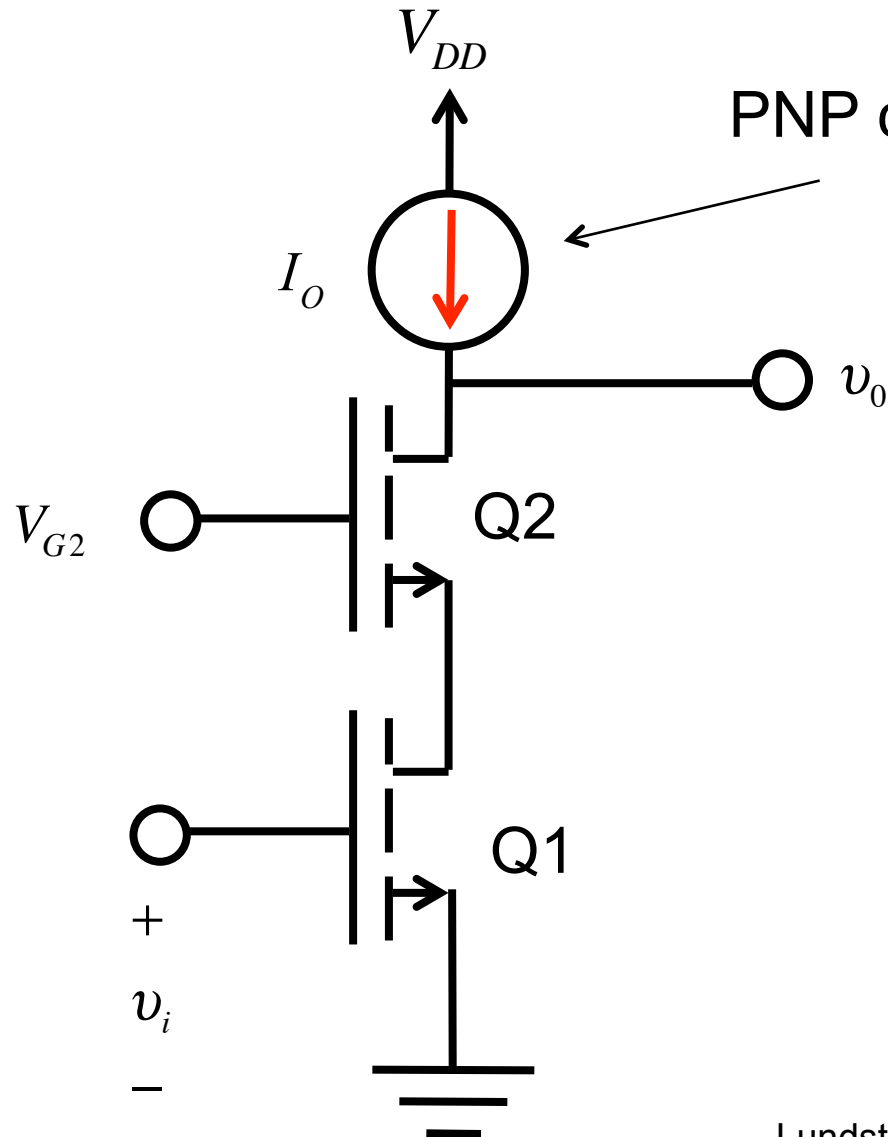


$$A_{v_o} = -(g_m r_o)^2$$

$$A_{v_o} = -g_m [(g_m r_o) r_o] \parallel r_{op}$$

$$A_{v_o} \approx -g_m r_o = -A_0$$


The solution is to use a cascode current source.
(S&S p. 549)

Include a load resistor

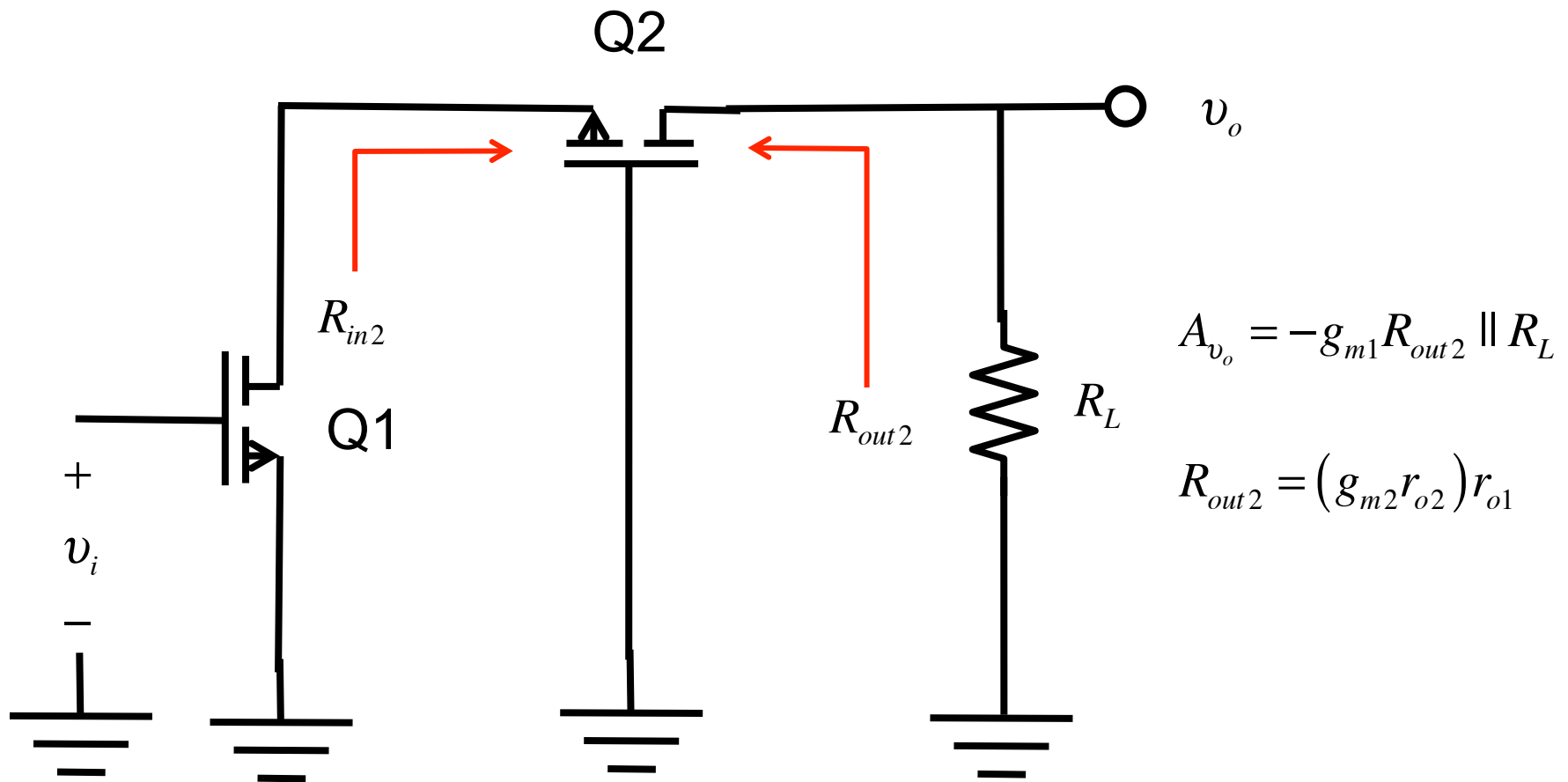

But now, can you find the gain of stage 1 (it depends on R_L !). See S&S, Sec. 8.5.3

Double cascode

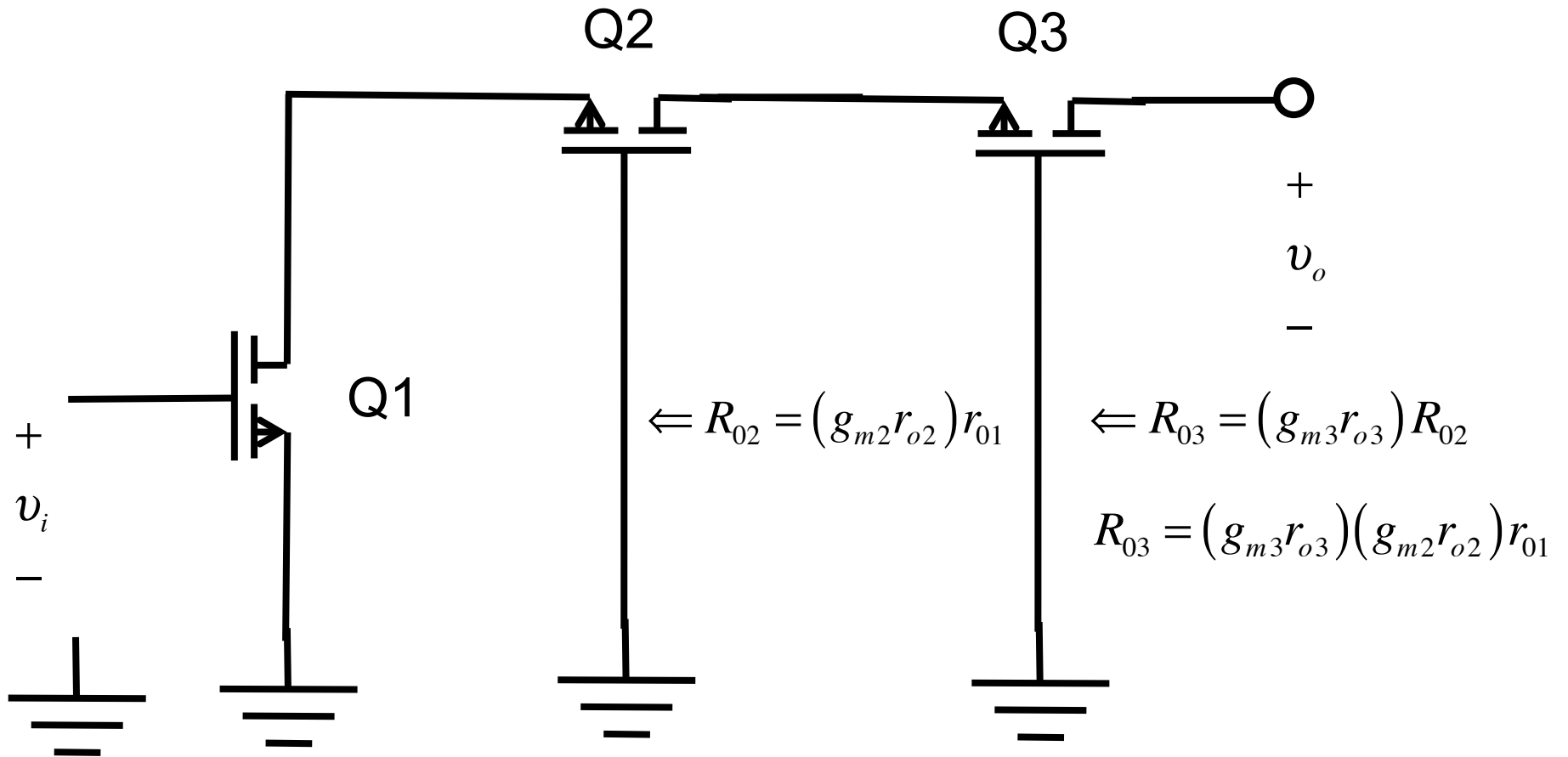


$$A_{v_o} = -g_m R_{o3}$$

$$A_{v_o} = -(g_m r_o)^3$$

Outline


- 1) Introduction
- 2) Discrete cascode
- 3) IC MOS cascode
- 4) Discussion
- 5) BJT cascode**
- 6) Summary

BJT cascode

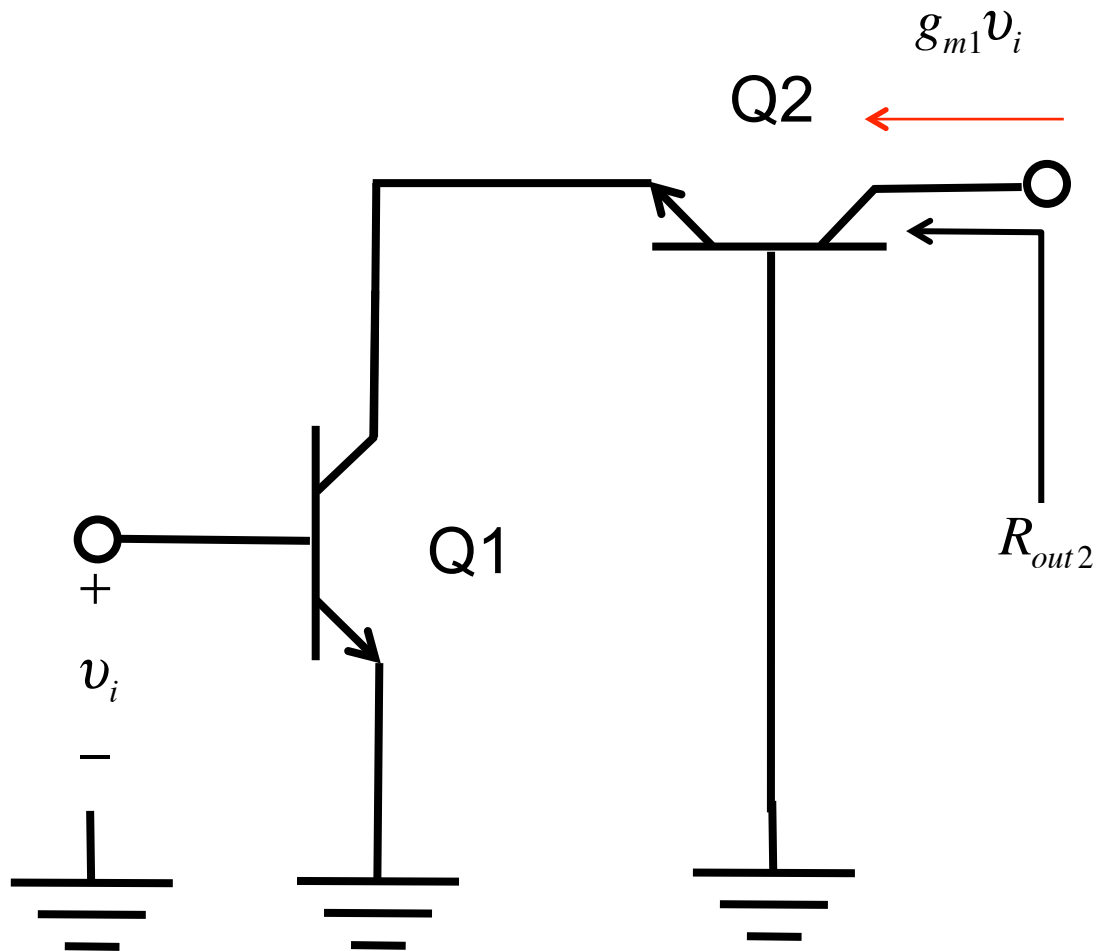

$$v_o = -(g_{m1} v_i) R_{out2}$$

Recall L24

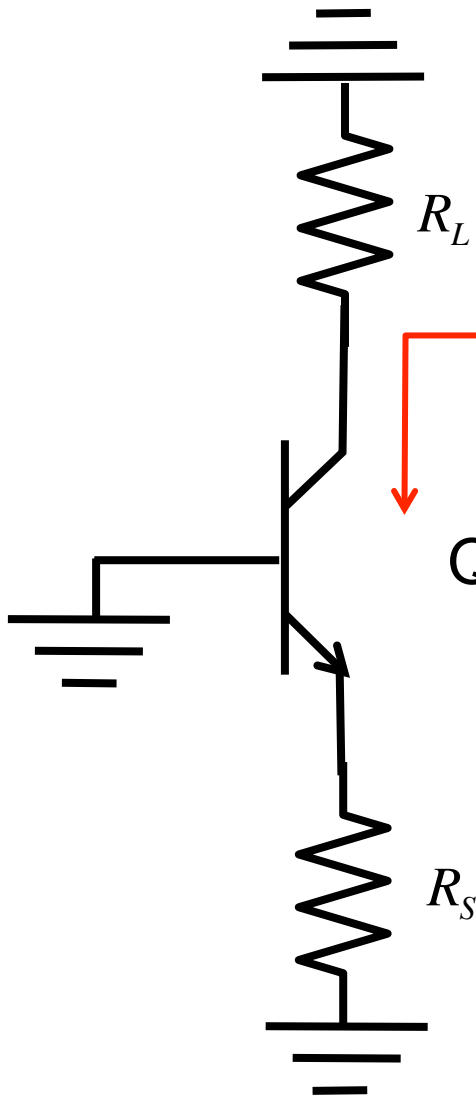


$$R_{out} = r_{o2} + (1 + g_{m2}r_{o2})(R_S \parallel r_{\pi2})$$

$$R_{out} = r_{o2} + (1 + g_{m2}r_{o2})(r_{o2} \parallel r_{\pi2})$$

$$R_{out} \approx (g_{m2}r_{o2})(r_{o2} \parallel r_{\pi2})$$

cannot be as large as
for the MOS case

BJT cascode

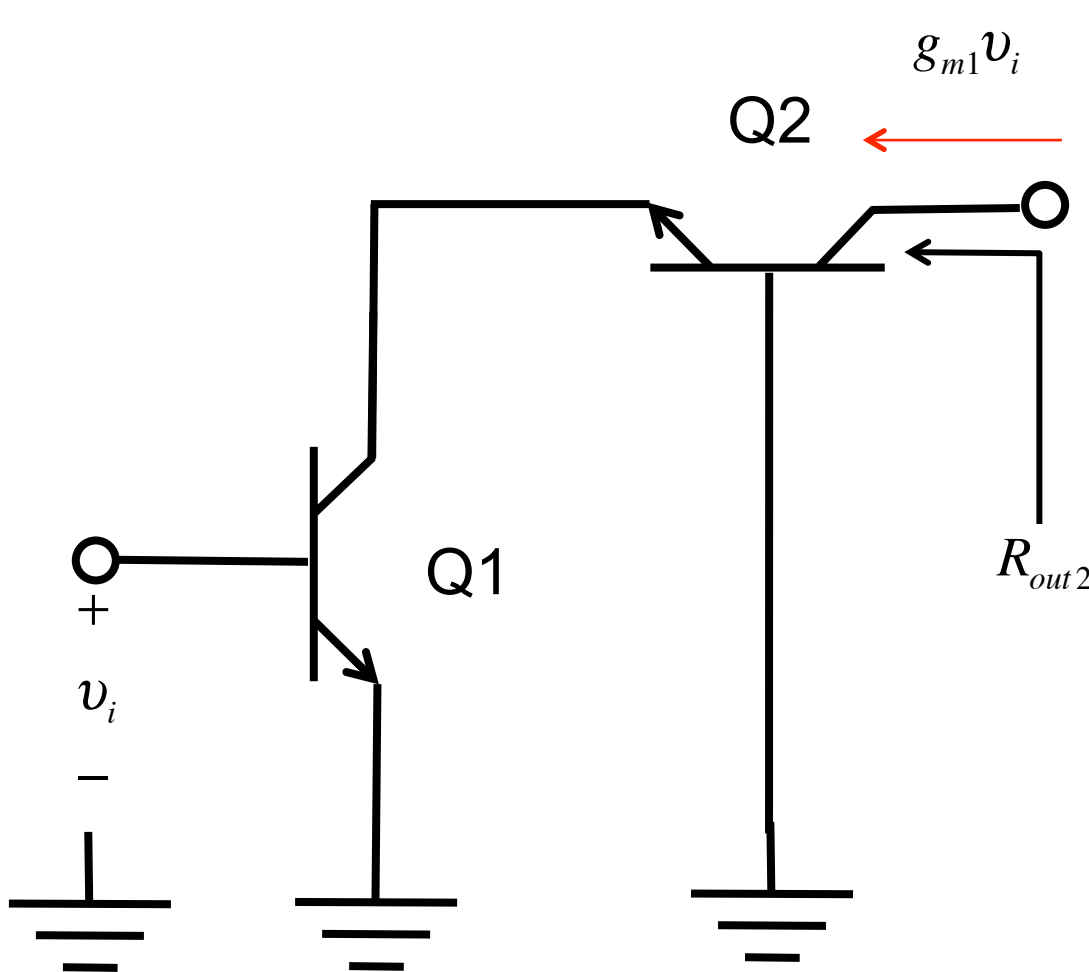

$$v_o = -(g_{m1} v_i) R_{out2}$$


$$R_{out} \approx (g_{m2} r_{o2}) (r_{o2} \parallel r_{\pi 2})$$

$$A_{v_o} = -g_{m1} (g_{m2} r_{o2}) (r_{o2} \parallel r_{\pi 2})$$

$$A_{v_o} \Big|_{\max} = -g_{m1} (g_{m2} r_{o2}) r_{\pi 2}$$

$$A_{v_o} \Big|_{\max} = -\beta g_m r_o = -\beta A_0$$

BJT cascode

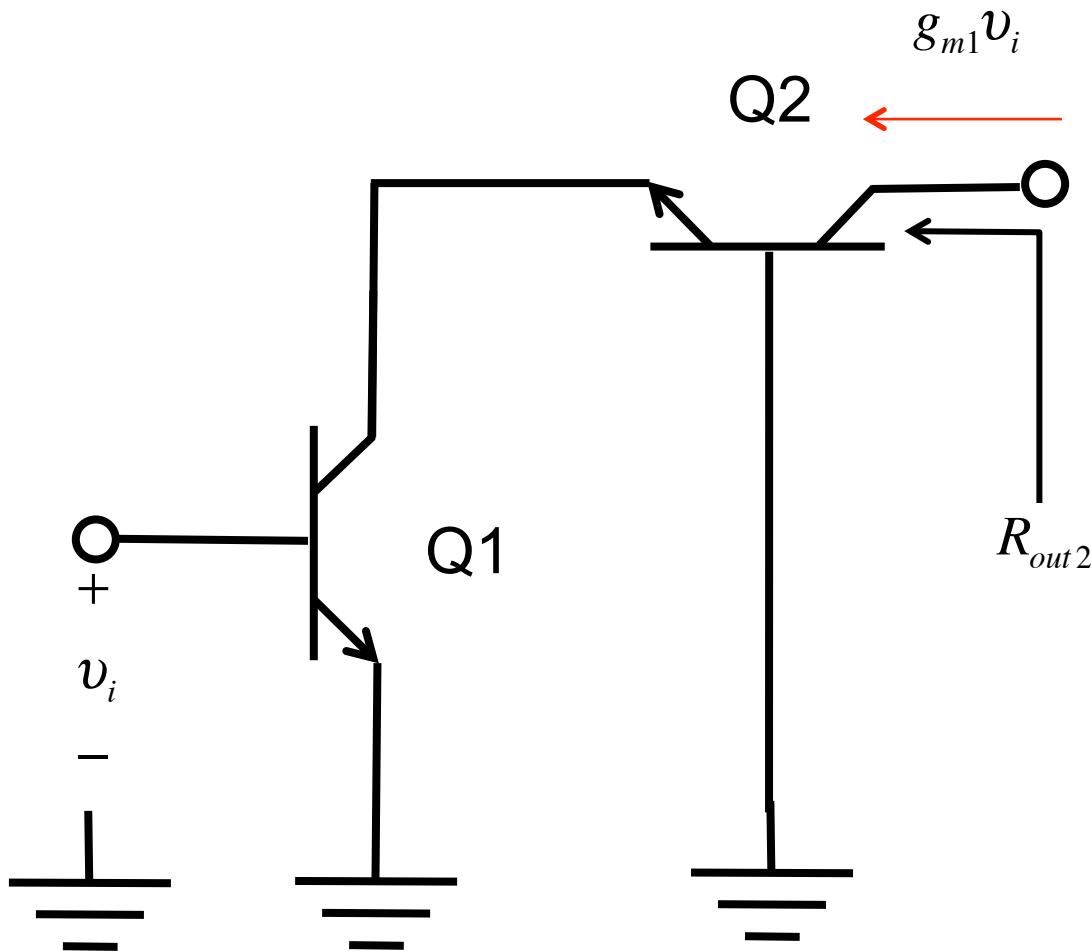


$$A_{v_o} \Big|_{\max} = -\beta A_0$$

See the discussion in
Sec. 8.5.6 of S&S

Outline

- 1) Introduction
- 2) Discrete cascode
- 3) IC MOS cascode
- 4) Discussion
- 5) BJT cascode
- 6) Summary**

Summary

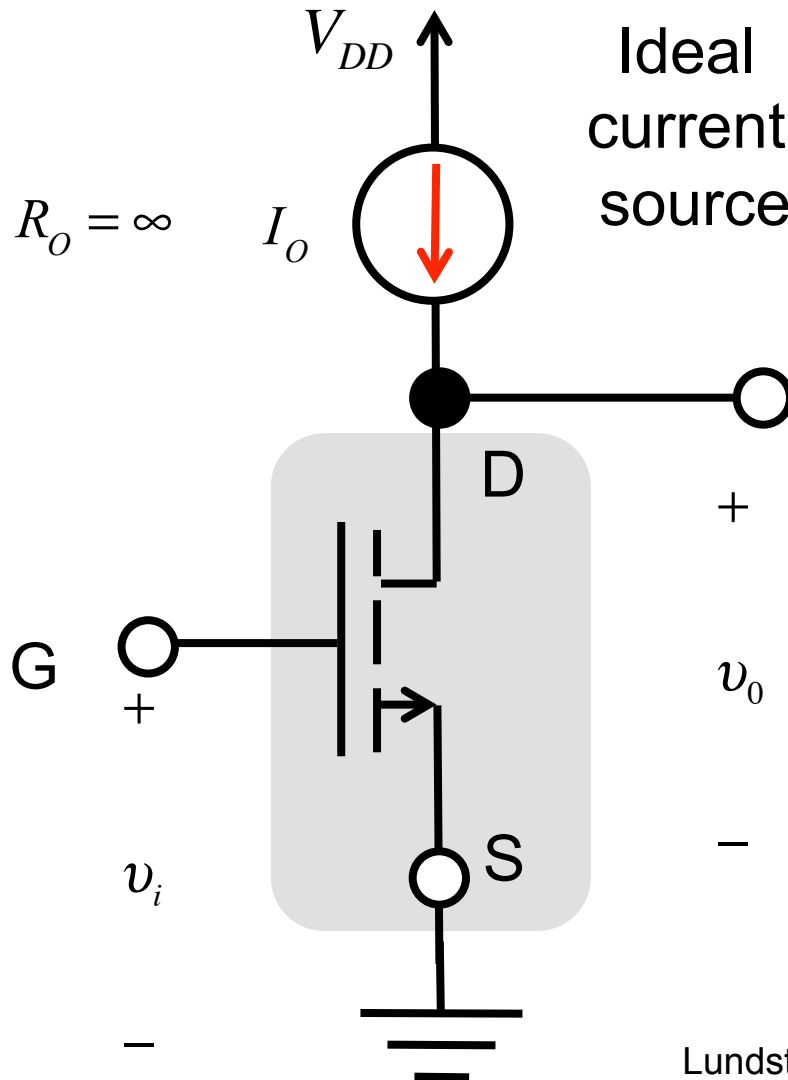

Common Source:

$$A_{v_o} = -g_m r_o$$

Cascode:

$$A_{v_o} = -(g_m r_o)^2$$

Double Cascode:

$$A_{v_o} = -(g_m r_o)^3$$

Questions

- 1) Introduction
- 2) Discrete cascode
- 3) IC MOS cascode
- 4) Discussion
- 5) BJT cascodes
- 6) Summary

