

Spring 2019 Purdue University

ECE 255: L27

Preparation for Exam 3

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA




Announcements

- 1) HW8 solutions have been posted
- 2) Exam 3 is at 6:30 PM, Tuesday, April 2
- 3) No class on Wed., April 3**
- 4) Spice Project 3 will be due on April 17
- 5) Professor Janes will conduct a help session on
Tuesday, 1:30 PM ME1061

Multi-stage amplifiers

3-Stage Example

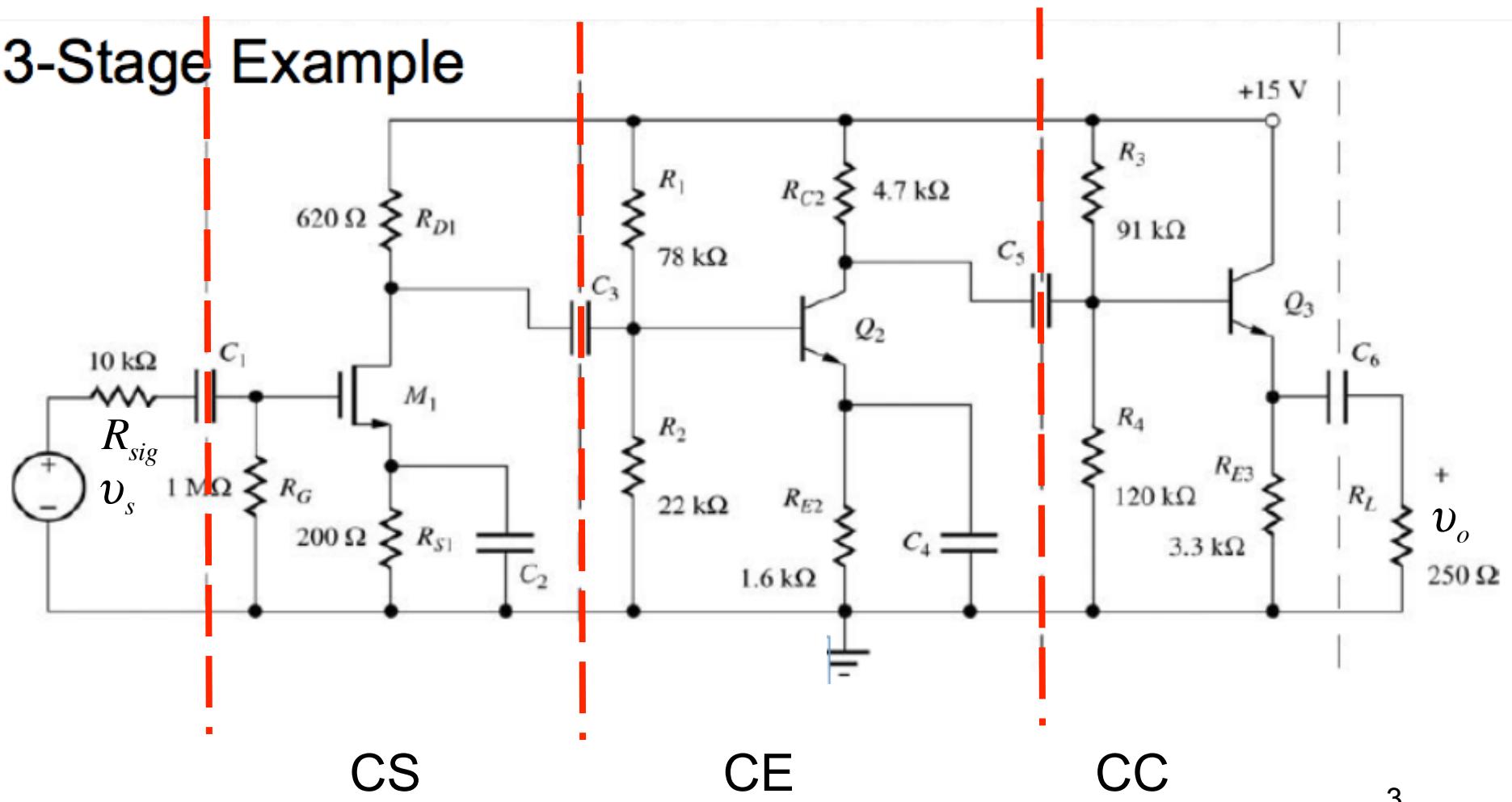

Voltage gain

$$A_v = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_{sig}} \times A_v \Big)_{CS} \times A_v \Big)_{CE} \times A_v \Big)_{CD}$$

$$\frac{R_{in}}{R_{in} + R_{sig}} = \frac{R_G}{R_G + R_{sig}}$$

$$A_{CS} = -g_{m1} R_{D1} \parallel \left[(R_1 \parallel R_2) \parallel r_{\pi 2} \right]$$

$$A_{CE} = -g_{m2} R_{C2} \parallel \left[(R_3 \parallel R_4) \parallel \left\{ r_{\pi 3} + (\beta + 1)(R_{E3} \parallel R_L) \right\} \right]$$


$$A_{CC} = \frac{(\beta + 1)(R_{E3} \parallel R_L)}{r_{\pi 3} + (\beta + 1)(R_{E3} \parallel R_L)}$$

Input and output resistance

$$R_{in} = R_G$$

$$R_{out} = R_{E3} \parallel \left[\frac{r_{\pi3} + (R_3 \parallel R_4) \parallel R_{C2}}{\beta + 1} \right]$$

HW7 Problem 1

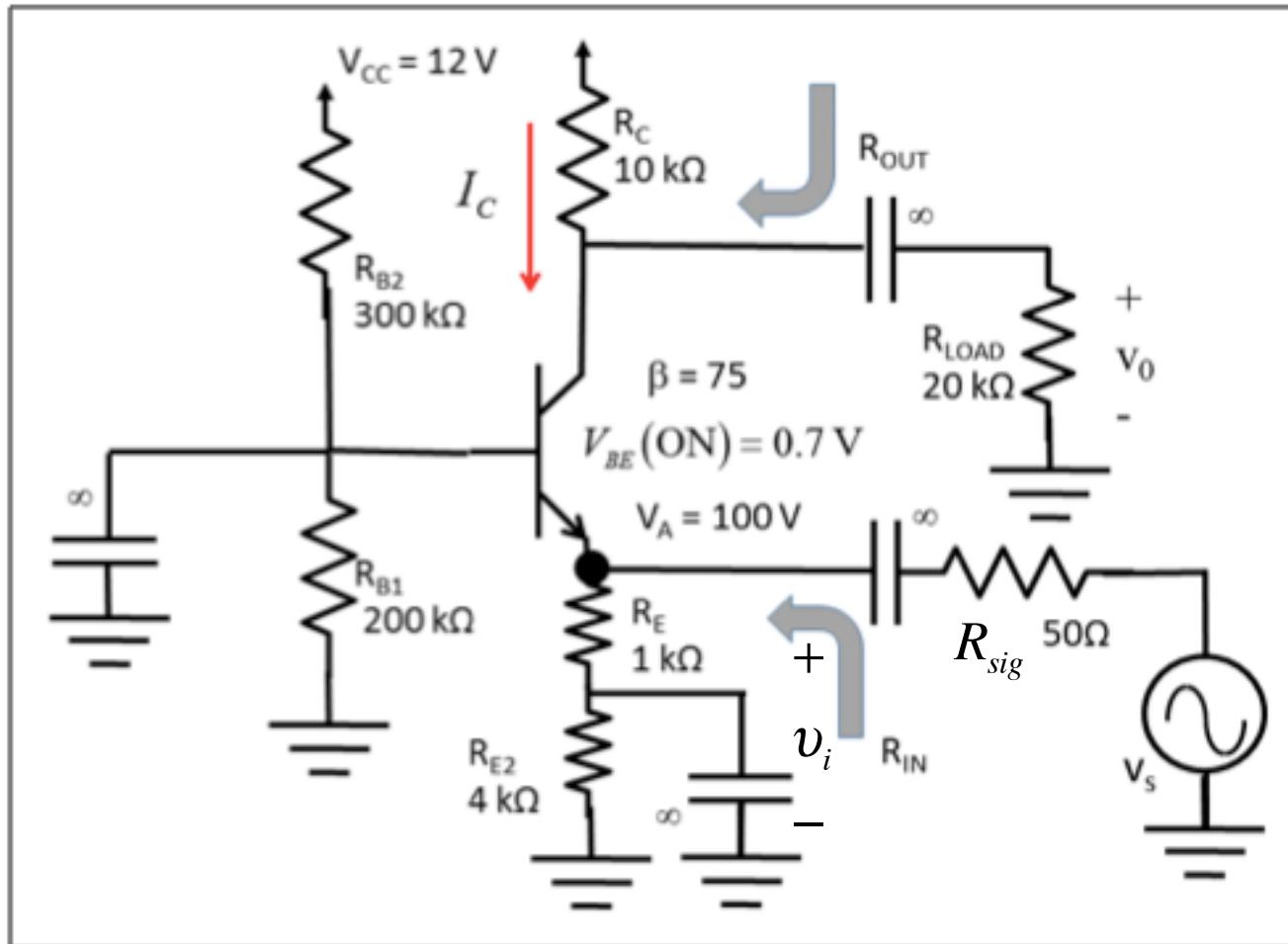

HW1 Prob. 1

R_{in}

R_{out}

First, assume that r_0 is infinite

$$A_{v_i} = \frac{v_o}{v_i}$$

Can you see that $A_{vi} \sim 10$?

$$A_{v_s} = \frac{v_o}{v_s}$$

HW1 Prob. 1

$$R_{in} = R_E \parallel \frac{r_\pi}{\beta + 1}$$

$$R_{out} = R_C$$

First, assume that ρ_0 is infinite

$$A_{v_s} = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C \parallel R_L)$$

HW1 Prob. 1


$$R_{in} = R_E \parallel \frac{r_\pi}{\beta + 1} \rightarrow ?$$

$$R_{out} = R_C \rightarrow ?$$

Now include ro

$$A_{v_s} = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_\pi}{r_\pi + (\beta + 1)R_E} (-g_m R_C \parallel R_{LOAD}) \rightarrow ?$$

HW 7 #1 with r_o

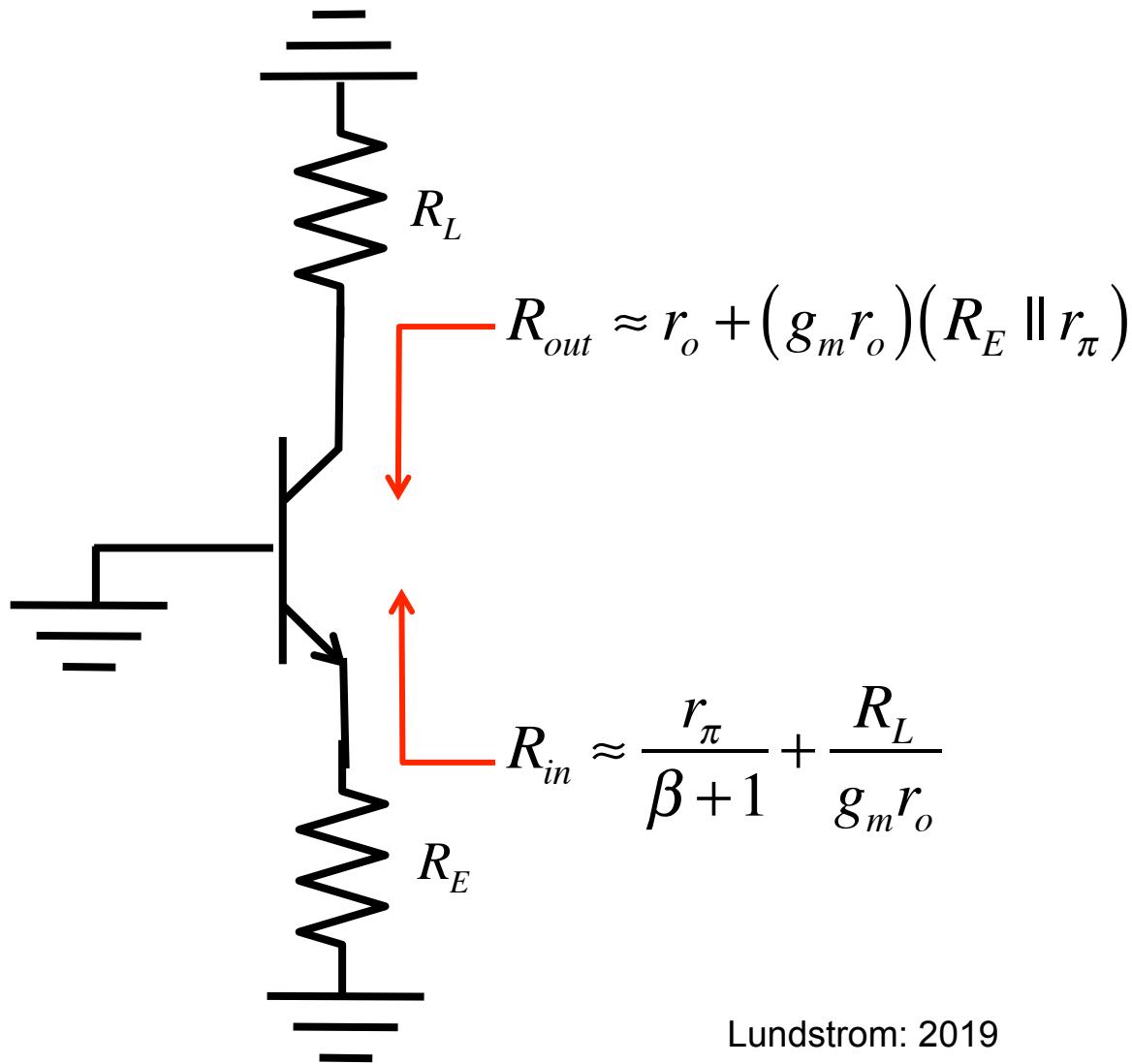

Lundstrom: 2019


HW1 Prob. 1

$$R_{in} = R_E \parallel \frac{r_\pi}{\beta+1} \rightarrow R_E \parallel \left[\frac{r_\pi}{\beta+1} + \frac{R_C \parallel R_{LOAD}}{g_m r_o} \right] \approx R_E \parallel \frac{r_\pi}{\beta+1}$$

$$R_{out} = R_C \rightarrow R_C \parallel \left[r_o + g_m r_o (R_E \parallel R_{sig} \parallel r_\pi) \right] \approx R_C$$

$$\begin{aligned} A_{v_s} &= \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_\pi}{r_\pi + (\beta+1)R_E} (-g_m R_C \parallel R_{LOAD}) \rightarrow \\ &\quad \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_\pi}{r_\pi + (\beta+1)R_E} \left(-g_m R_C \parallel \left[r_o + g_m r_o (R_E \parallel R_{sig} \parallel r_\pi) \right] \parallel R_{LOAD} \right) \end{aligned}$$

HW7 #2

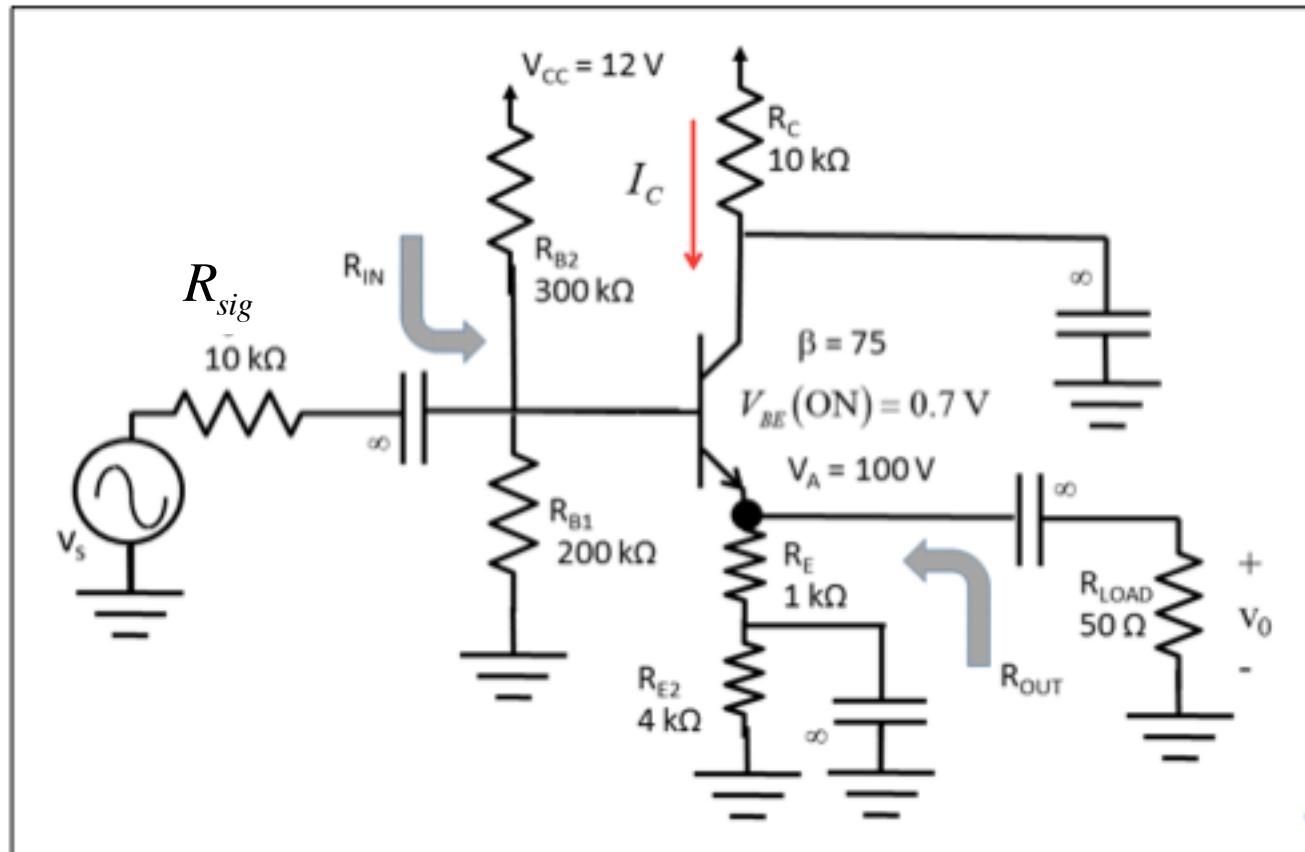

HW7 #2

R_{in}

R_{out}

Assume that ρ_0 is **finite**

$$A_{v_s} = \frac{v_o}{v_s}$$


HW7 #2

$$R_{in} = R_{B1} \parallel R_{B2} \parallel \left[r_\pi + (\beta + 1) (R_E \parallel R_{LOAD} \parallel r_o) \right]$$

$$R_{out} = R_E \parallel r_o \parallel \frac{r_\pi + R_{sig} \parallel (R_{B1} \parallel R_{B2})}{\beta + 1}$$

$$A_{v_s} = \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{(\beta + 1) R_E \parallel r_o \parallel R_{LOAD}}{r_\pi + (\beta + 1) R_E \parallel r_o \parallel R_{LOAD}}$$

HW7 #3

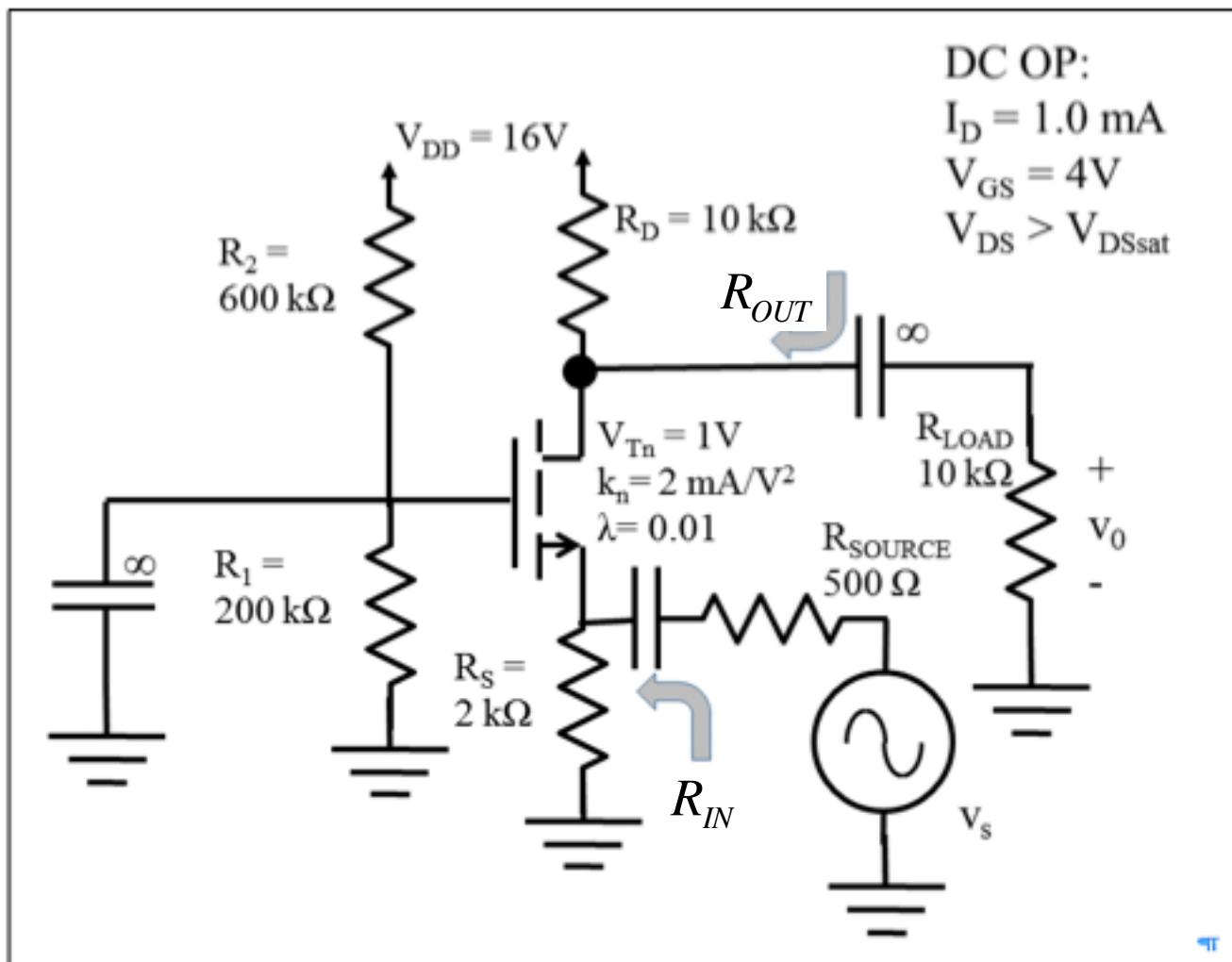

HW7 #3 with ρ_0 infinite

R_{in}

R_{out}

Assume that ρ_0 is **infinite**

$$A_{v_s} = \frac{v_o}{v_s}$$

HW7 #3 with ρ_0 finite


R_{in}

R_{out}

Assume that r_o is **finite**
(left as an exercise)

$$A_{v_s} = \frac{v_o}{v_s}$$

HW7 #3 with ro

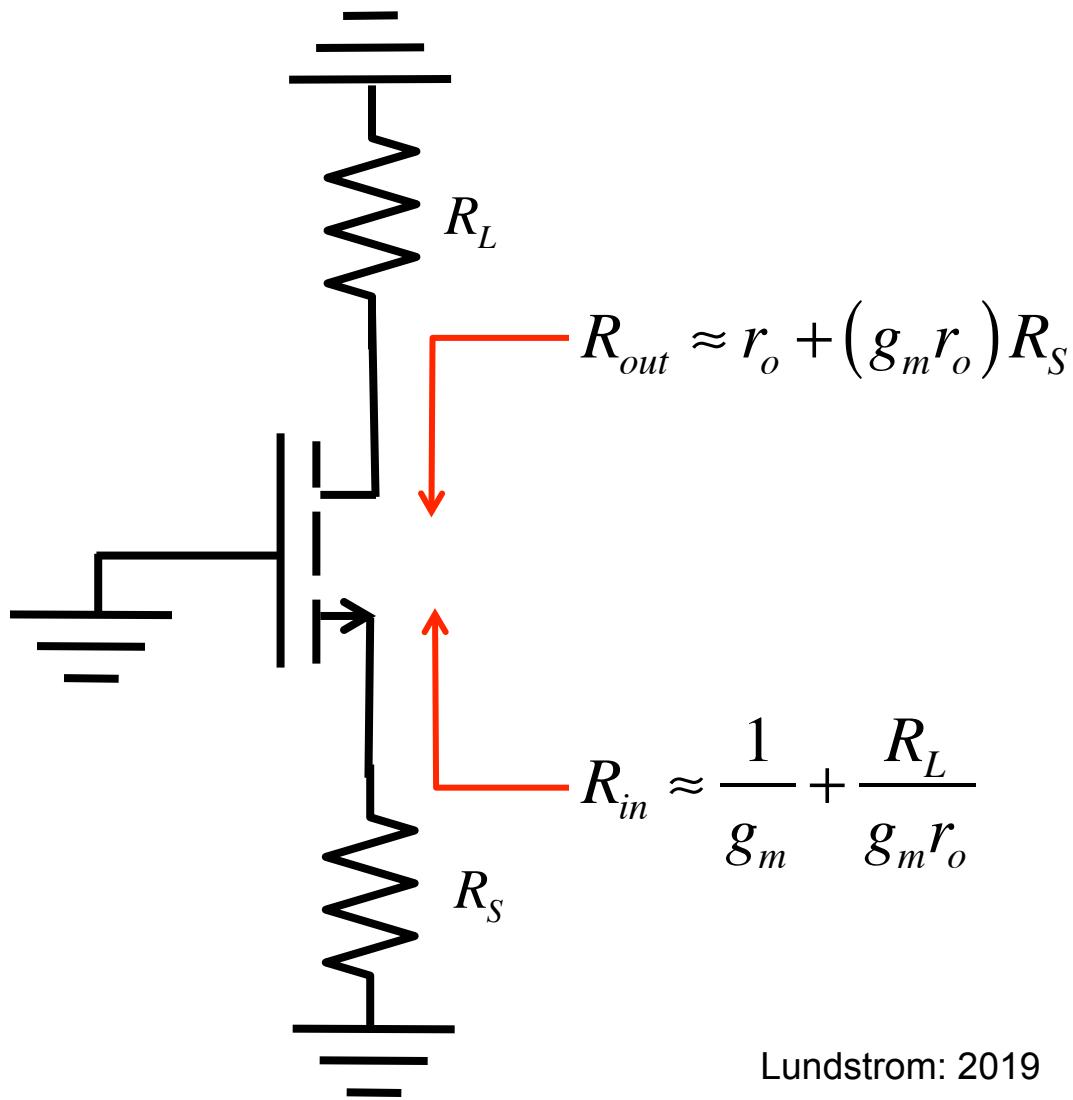


Lundstrom: 2019

HW7 #4 r_o infinite

$$R_{in} = ?$$

$$R_{out} = ?$$

$$A_{v_o} = \frac{v_o}{v_s} = ?$$

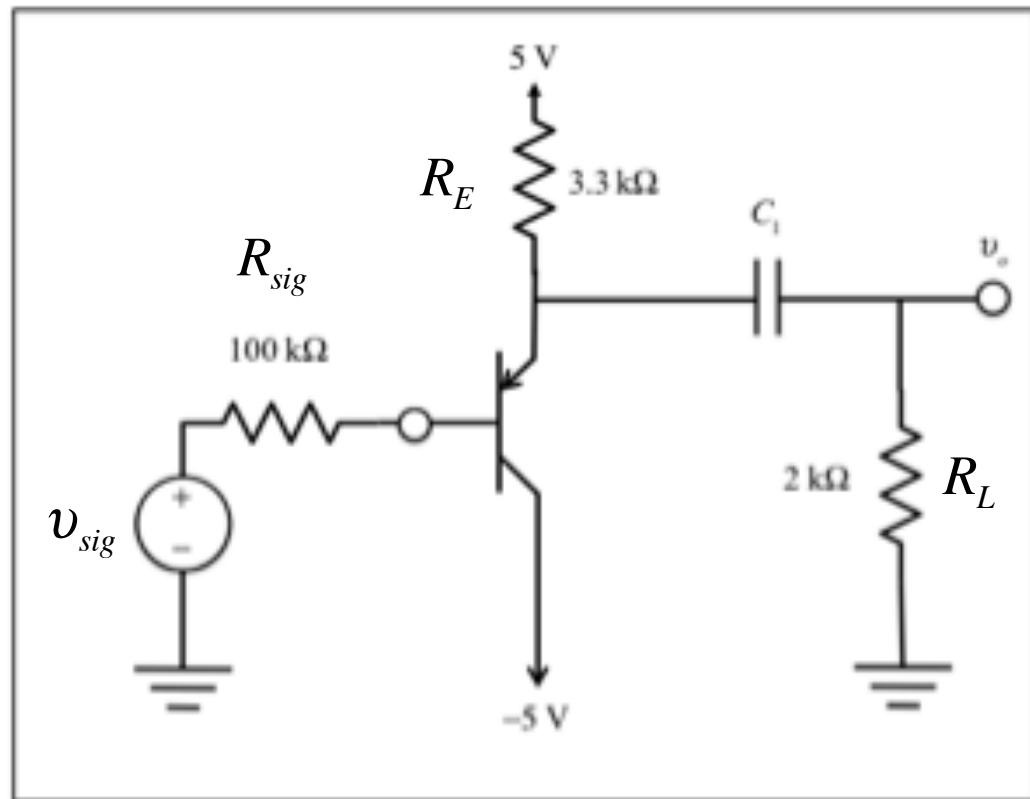


HW8 #5 include r_o

$$R_{in} = ?$$

$$R_{out} = ?$$

$$A_{v_s} = \frac{v_o}{v_s} = ?$$

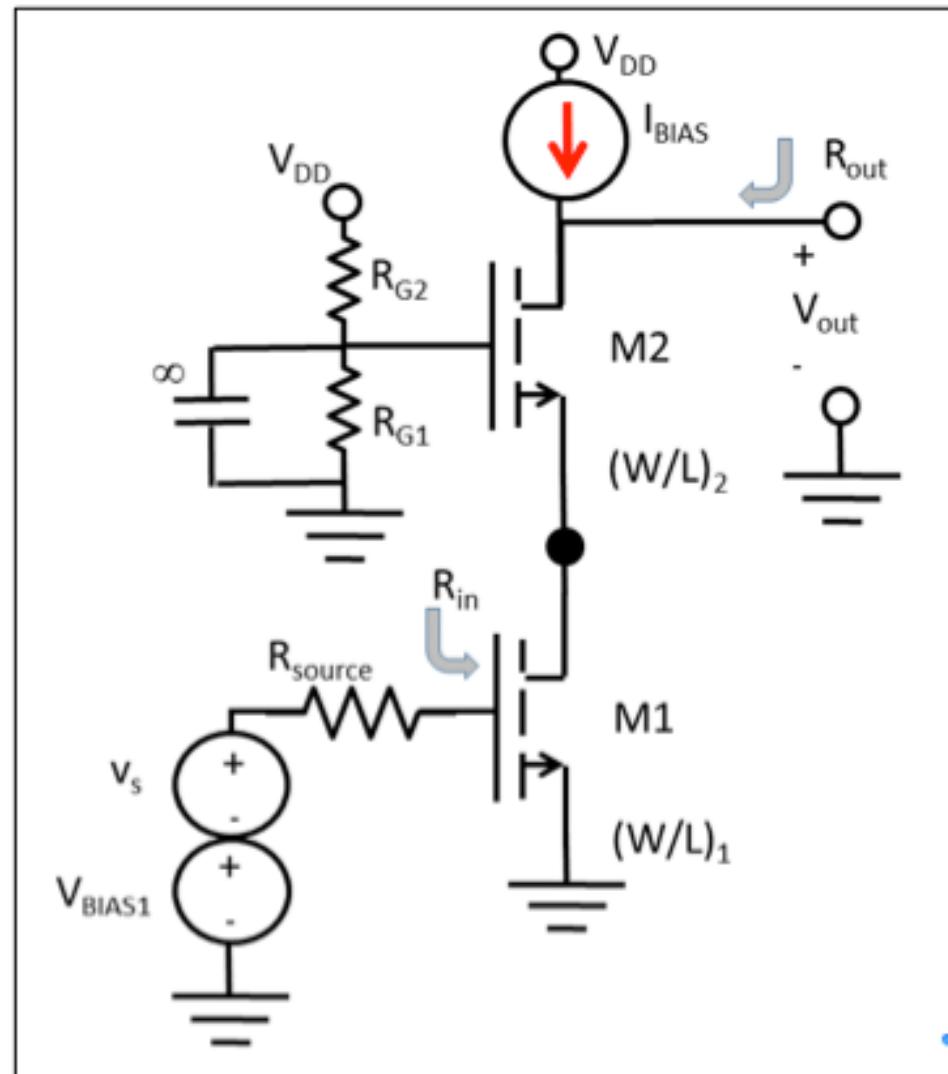

HW8 #5 include r_o

$$R_{in} = \infty$$

$$r_o = 100 \text{ k}\Omega$$

$$R_{out} = r_{o2} + (g_{m2}r_{o2})r_{o3}$$

$$g_m = 2 \text{ mS}$$

$$R_{out} = 100 + (200)100 = 20.1 \text{ M}\Omega$$

$$A_{v_s} = \frac{v_o}{v_s} = -g_{m1}R_{OUT}$$

$$A_{v_s} = -40,100$$