

Spring 2019 Purdue University

ECE 255: L29

MOS Differential Pair with Active Loads

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA


Announcements

HW9 Due 5:00 PM Friday, April 12 in EE-209 dropbox

Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary

Source coupled pair

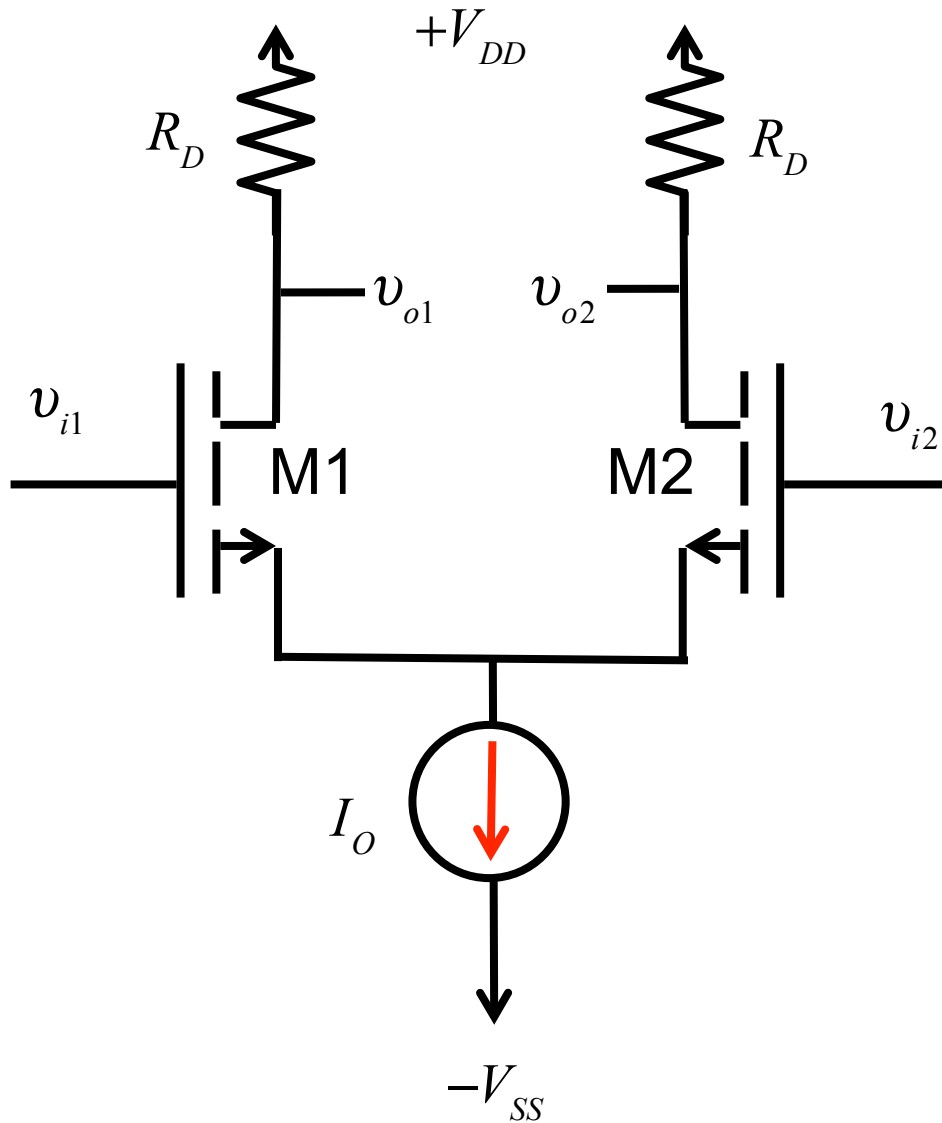


$$v_{id} = v_{i1} - v_{i2}$$

$$v_{ic} = (v_{i1} + v_{i2})/2$$

$$v_{od} = v_{o2} - v_{o1}$$

Small-signal results: differential

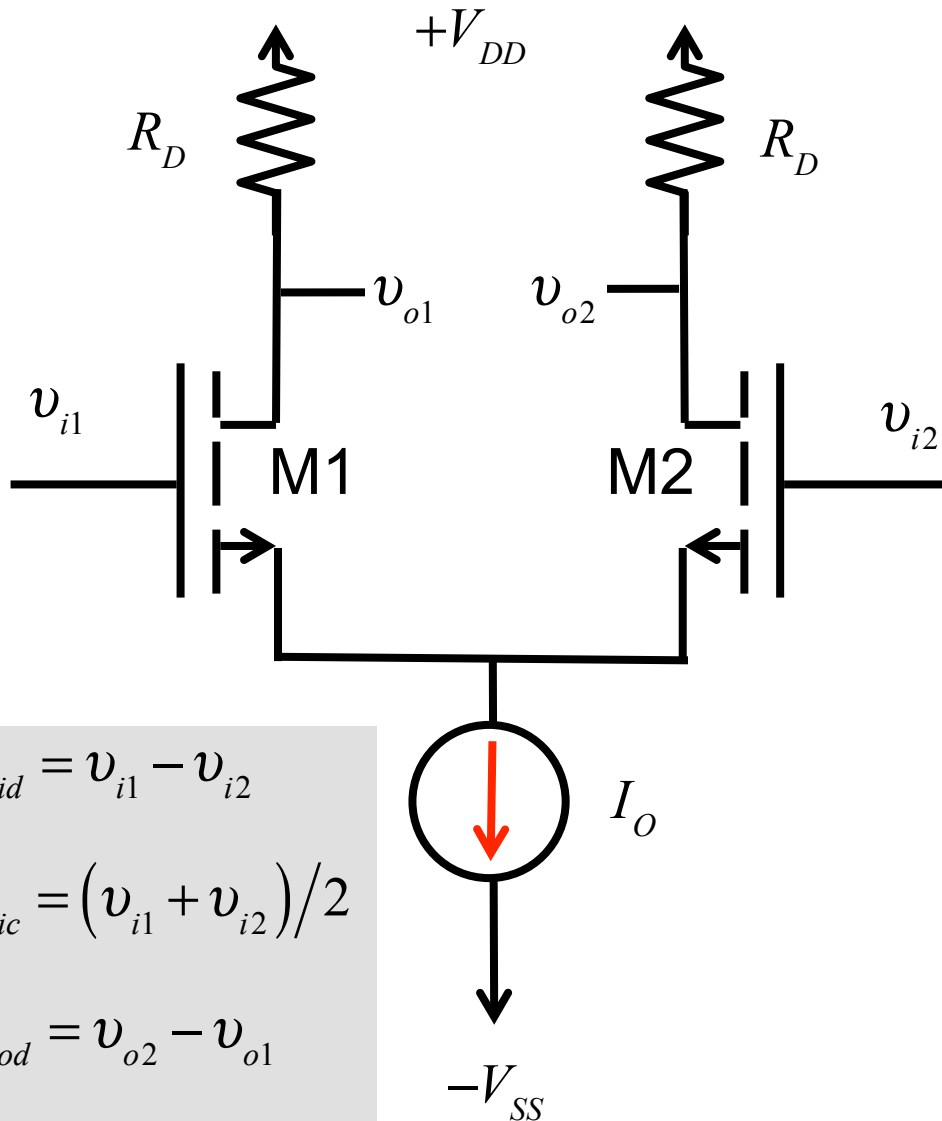

$$A_{dm} = \frac{v_{od}}{v_{id}}$$

$$A_{dm} = +g_m R_D$$

$$R_{in} = \infty$$


$$R_{out} = 2R_C$$

$$v_{id} = v_{i1} - v_{i2}$$

$$v_{ic} = (v_{i1} + v_{i2})/2$$

$$v_{od} = v_{o2} - v_{o1}$$

Small-signal results: common mode

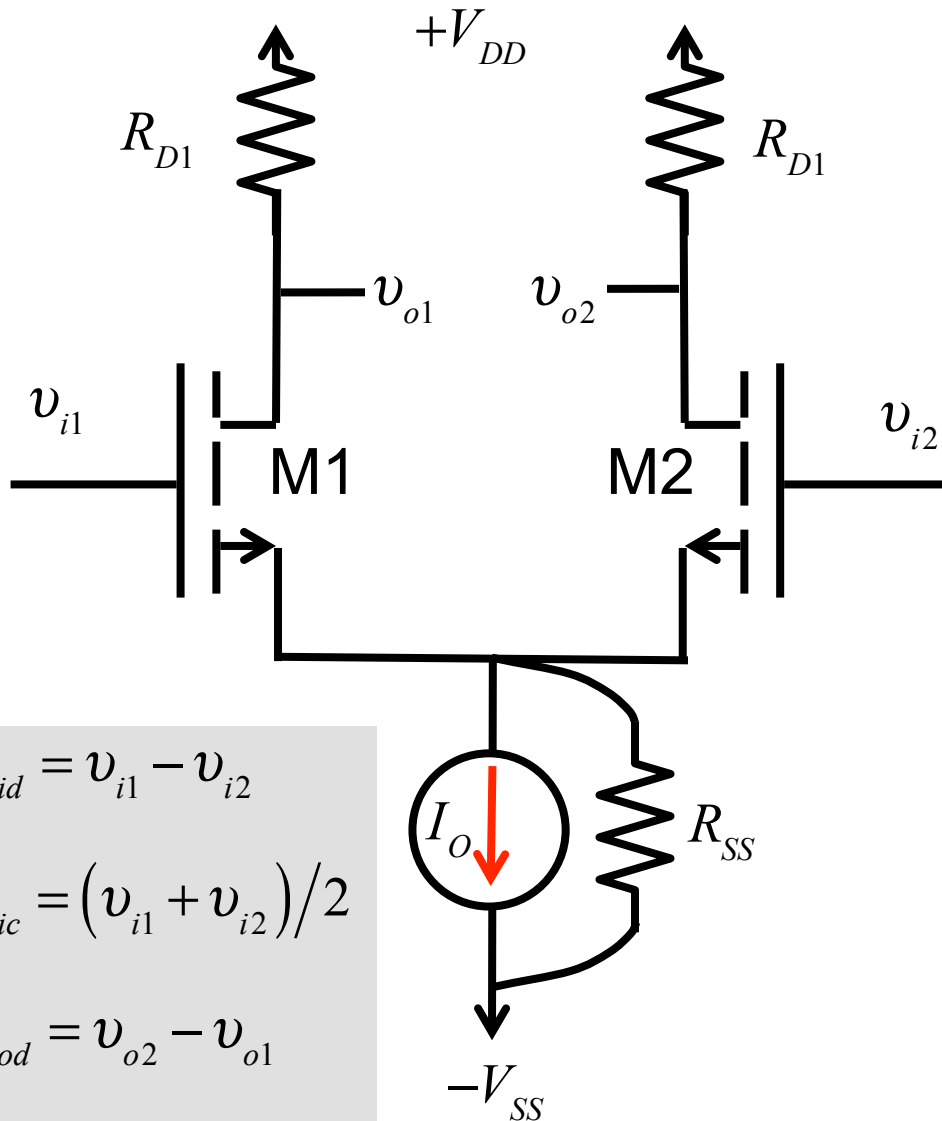

$$\frac{v_{o1}}{v_{ic}} = \frac{v_{o2}}{v_{ic}} \approx -\frac{R_D}{2R_{SS}}$$

$$A_{cm} = \frac{v_{od}}{v_{ic}} = 0$$

$$R_{D2} = R_{D1} + \Delta R_D$$

$$A_{cm} = -\frac{\Delta R_D}{2R_{SS}}$$


$$CMRR = \frac{|A_{dm}|}{|A_{cm}|}$$

$$CMRR = \frac{2g_m R_{SS}}{\Delta R_D / R_D}$$


Outline

- 1) Quick Review
- 2) MOS Op Amps**
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary

MOS Op Amp

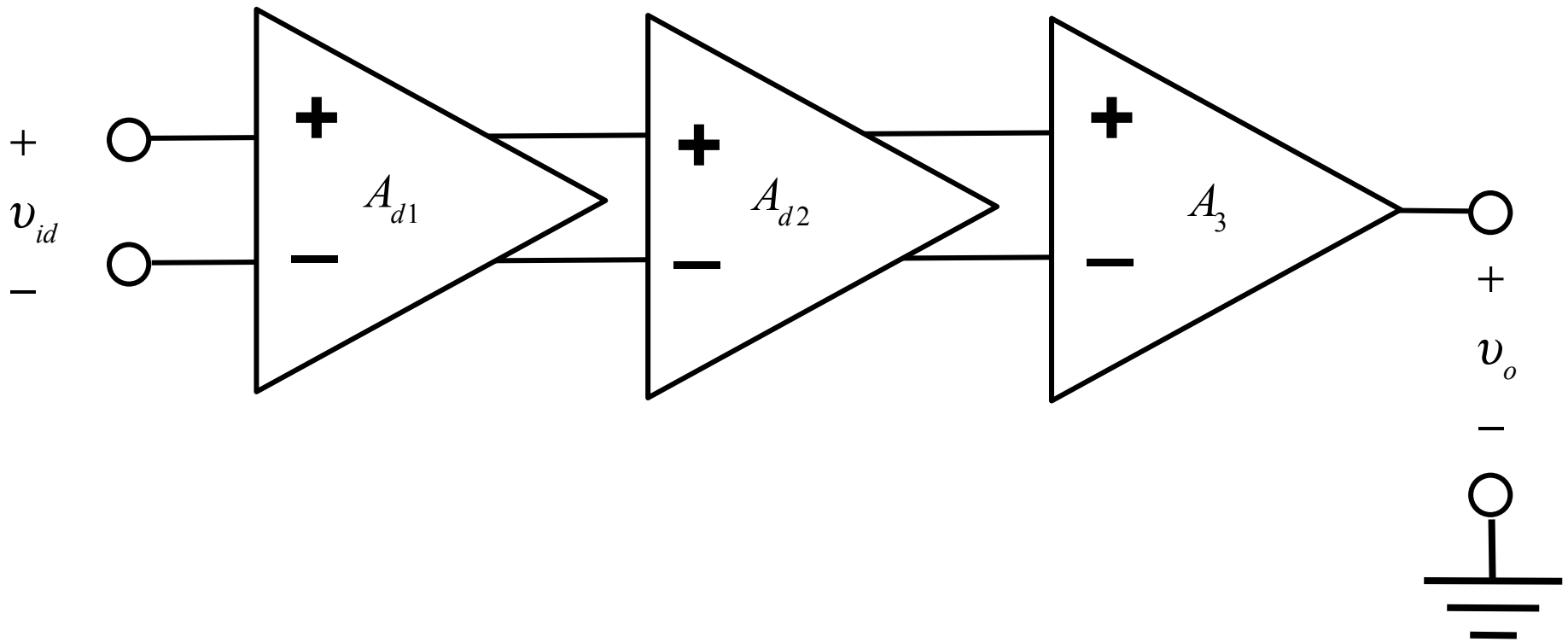

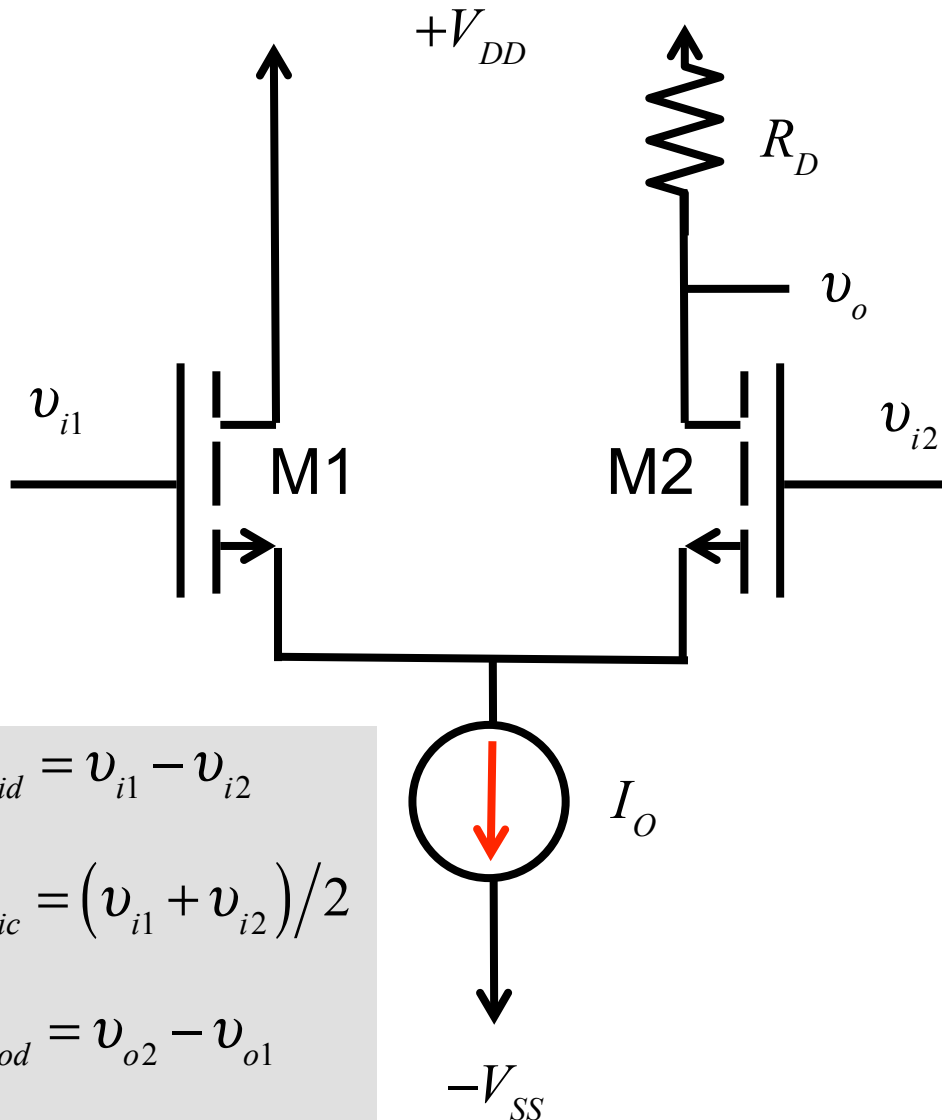Differential input to single ended output




$$A = \frac{v_o}{v_{id}}$$

$$A = \frac{g_m}{2} R_D$$

Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads**
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary

Recall: CS resistive load

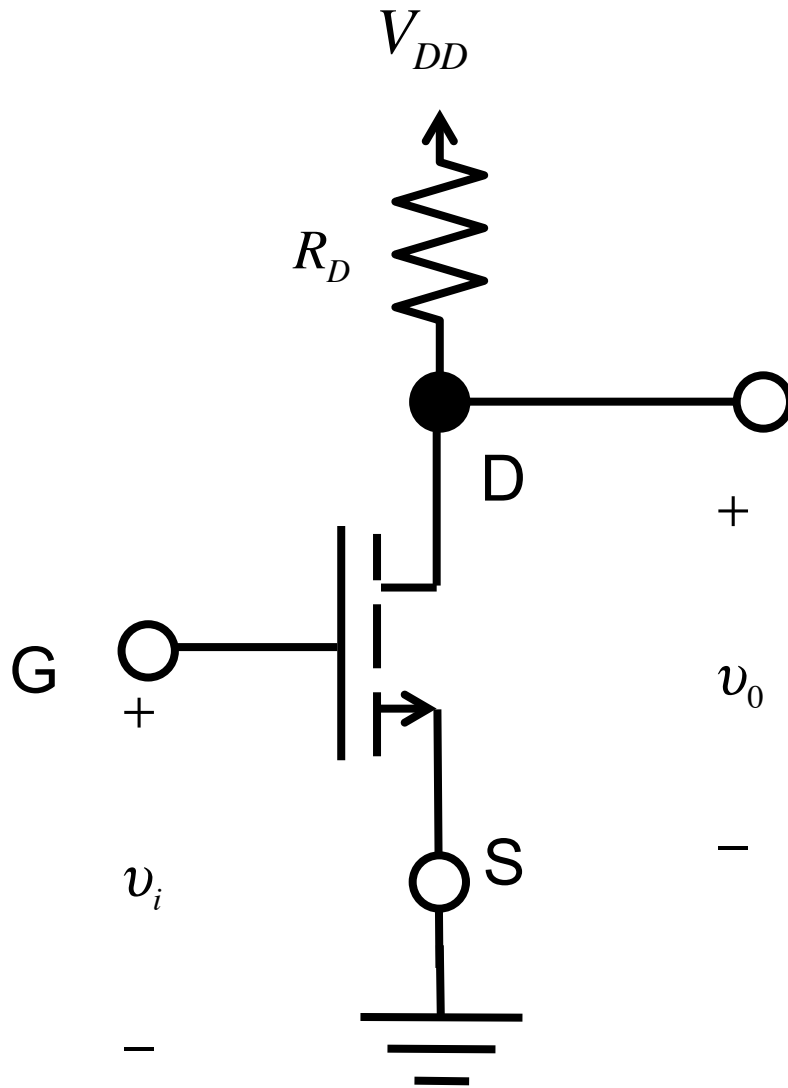


$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_D$$

$$R_{in} = \infty$$


$$R_o = R_D$$

Recall: CS Active load

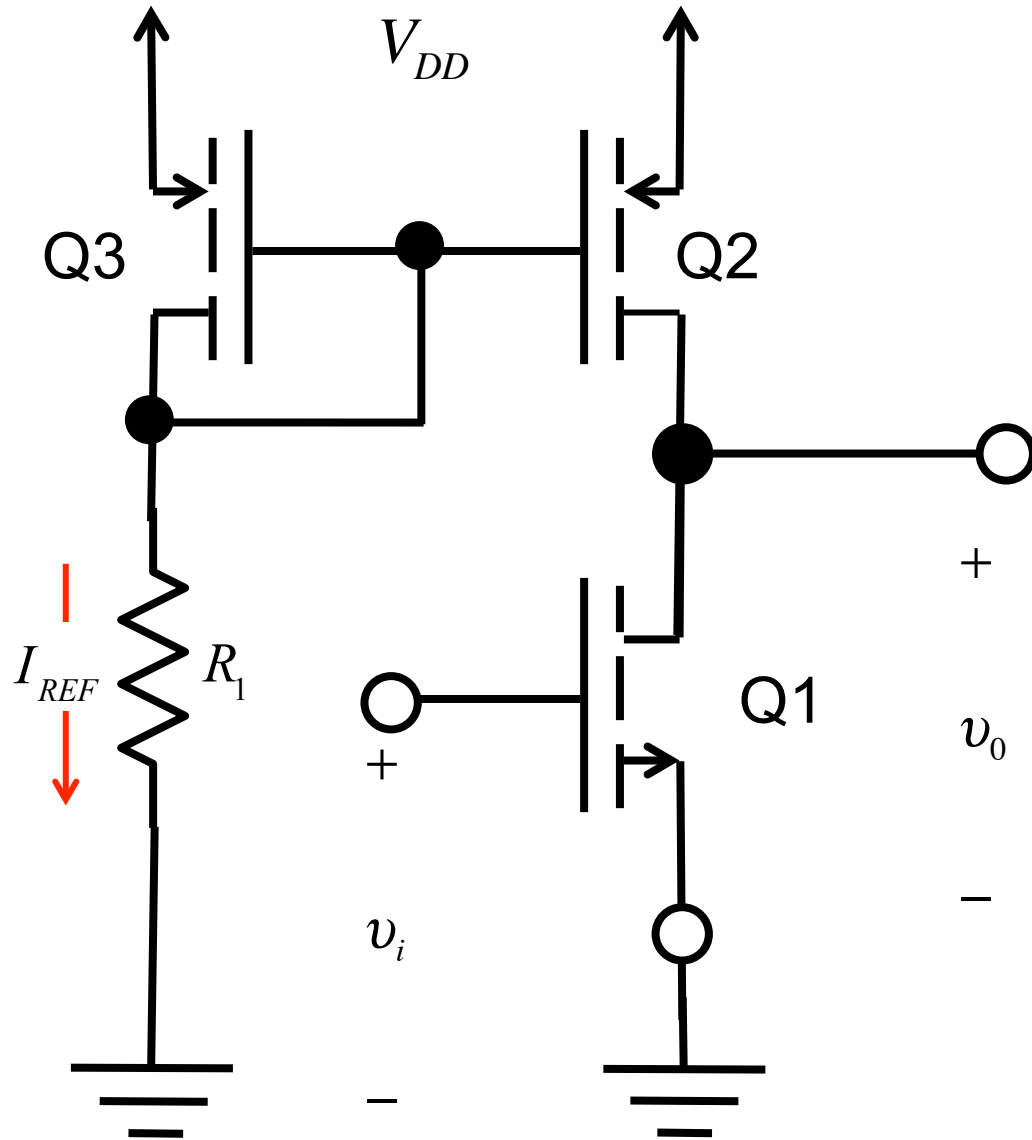


$$A_{v_o} = -g_m (r_{oN} \parallel r_{oP})$$

Differential pair with active load?

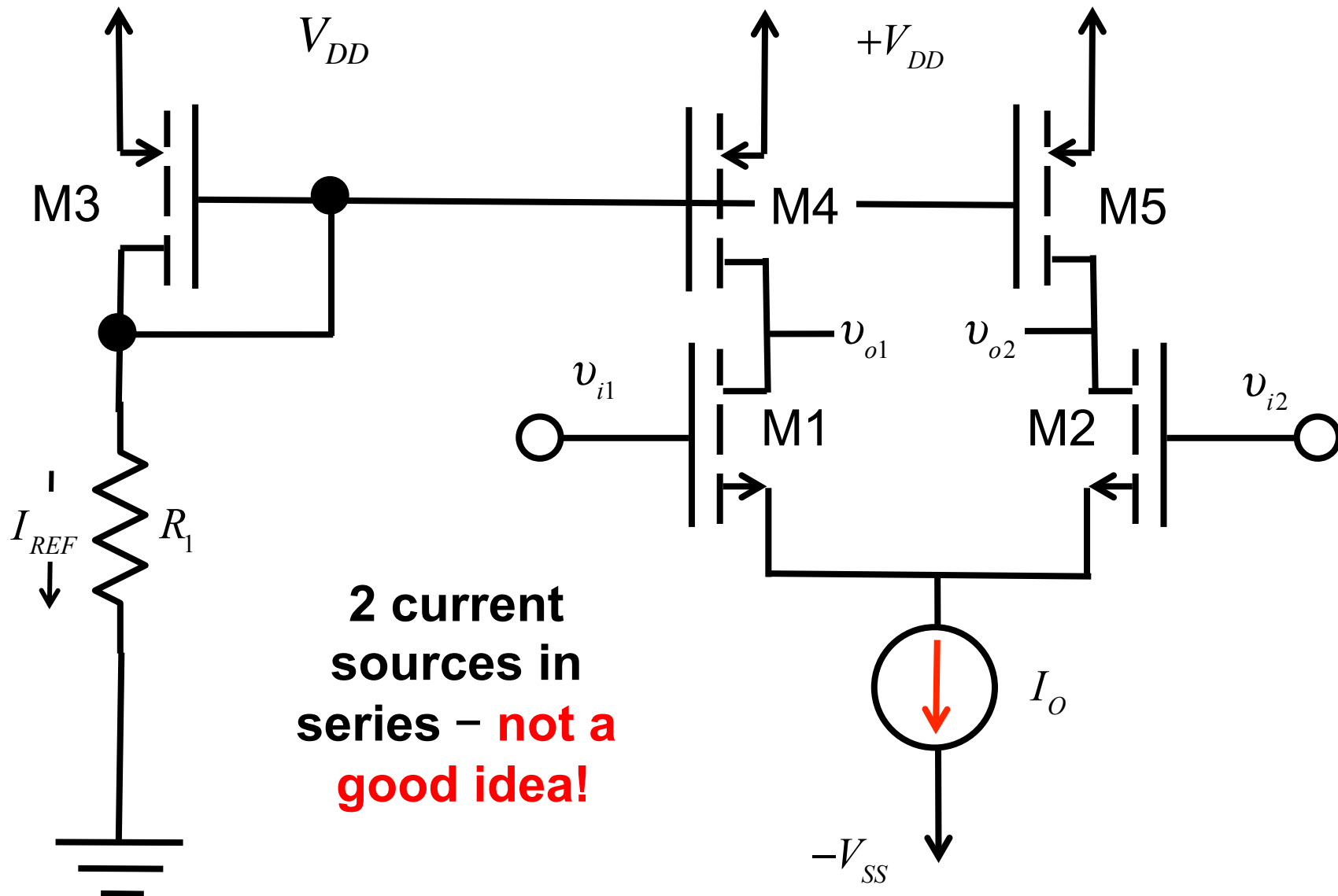


Current mirror loaded differential pair

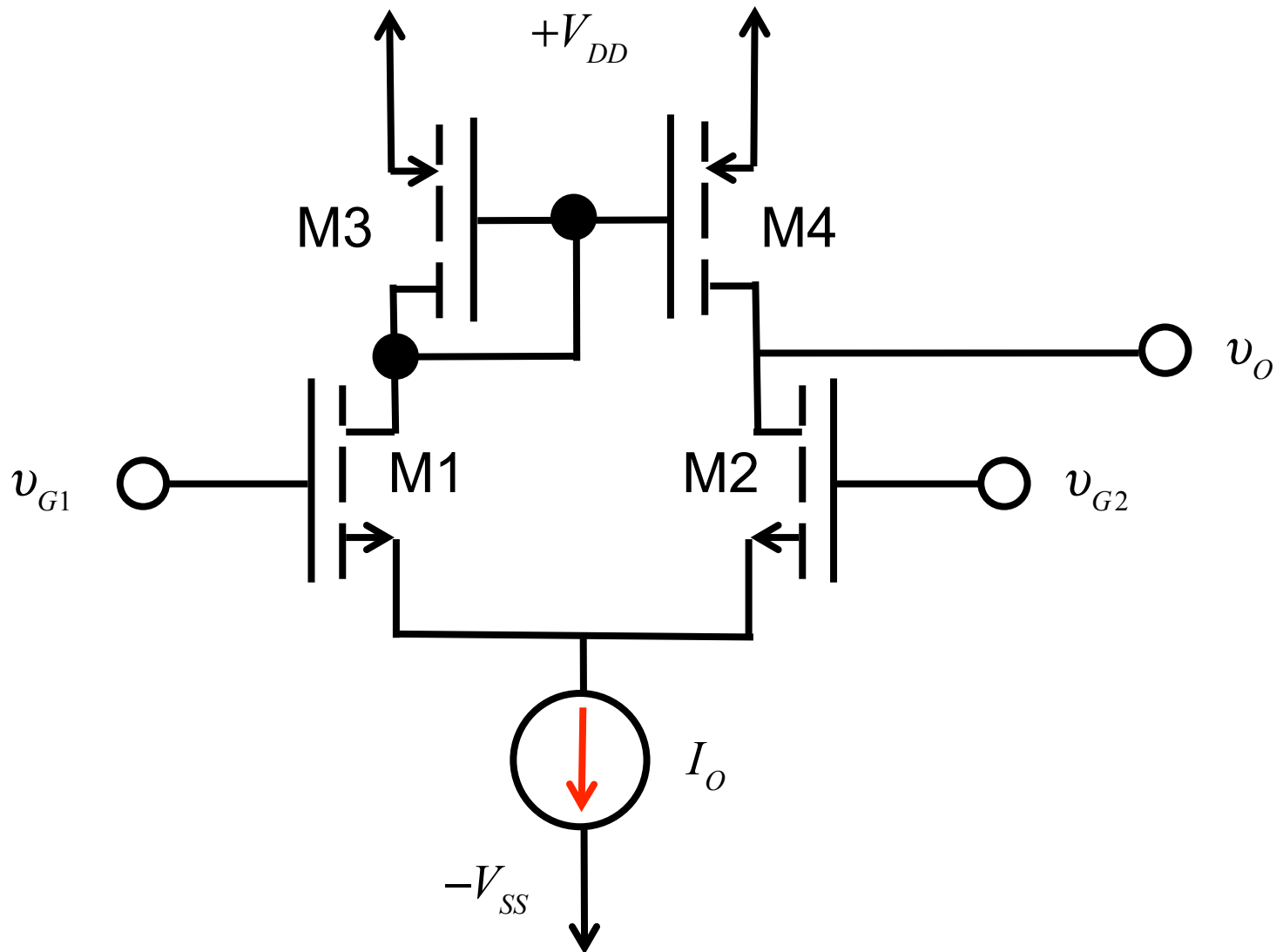


Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis**
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary


Small signal (differential)

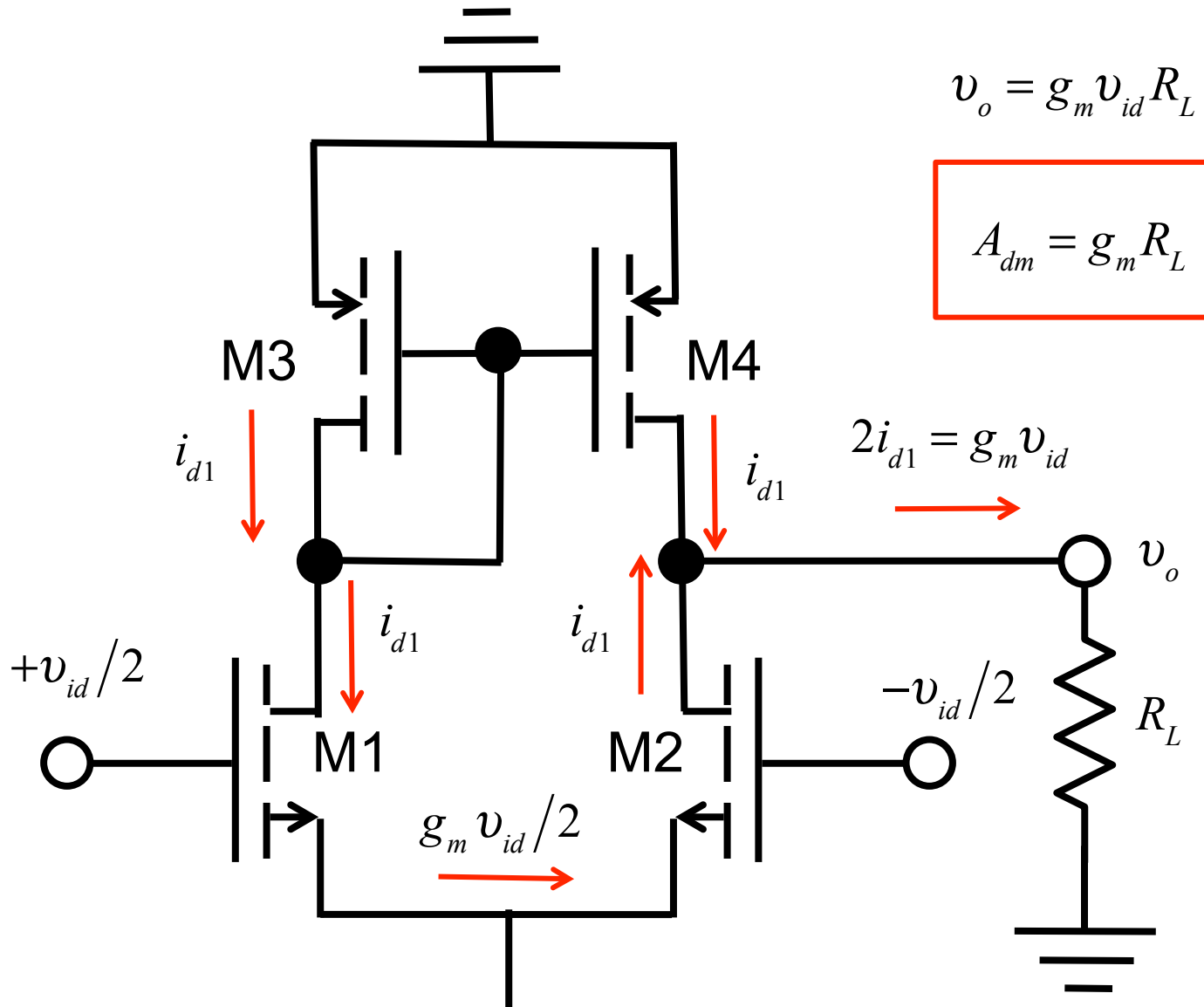

Small signal (common mode)

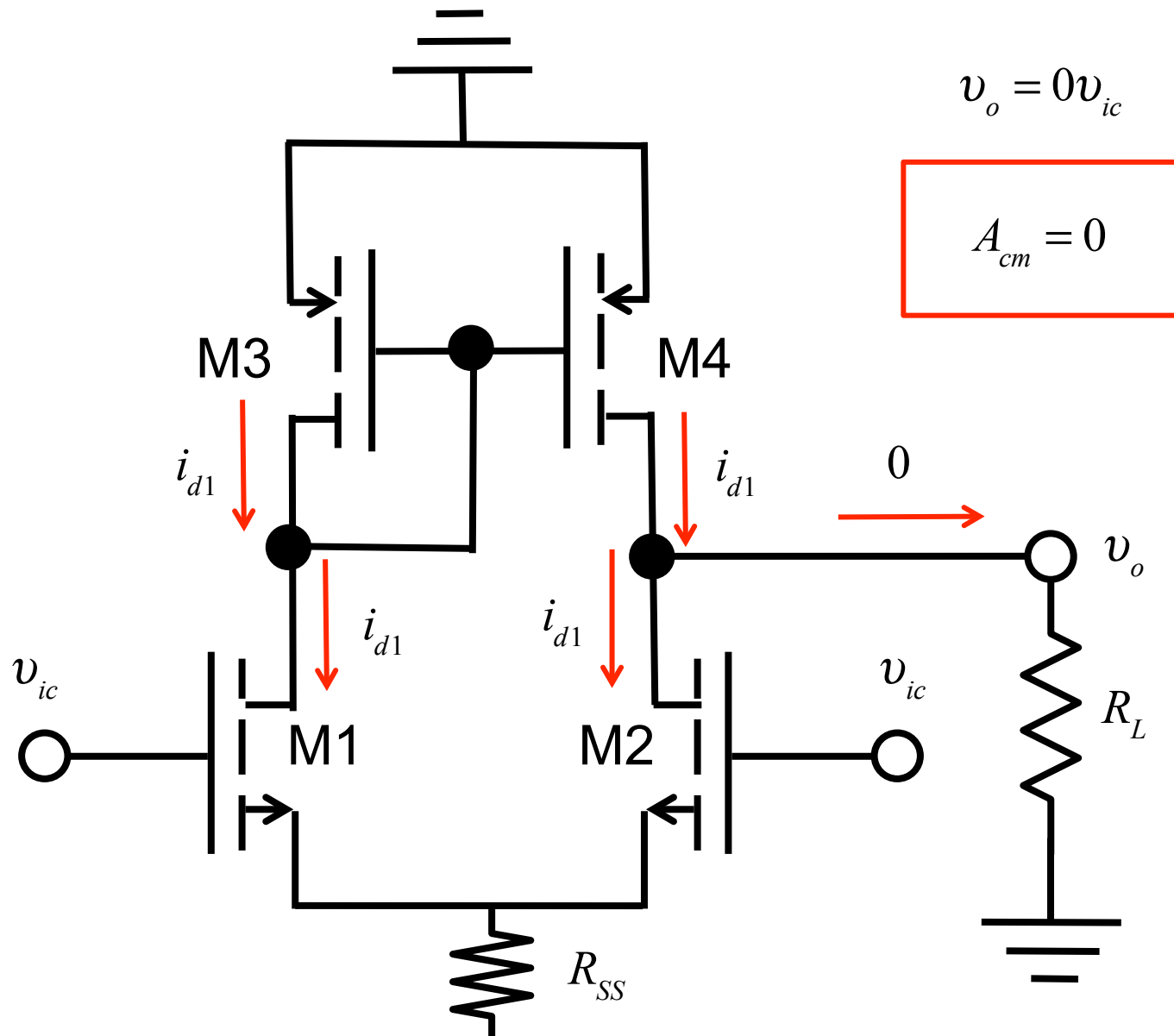

Current mirror loaded differential pair

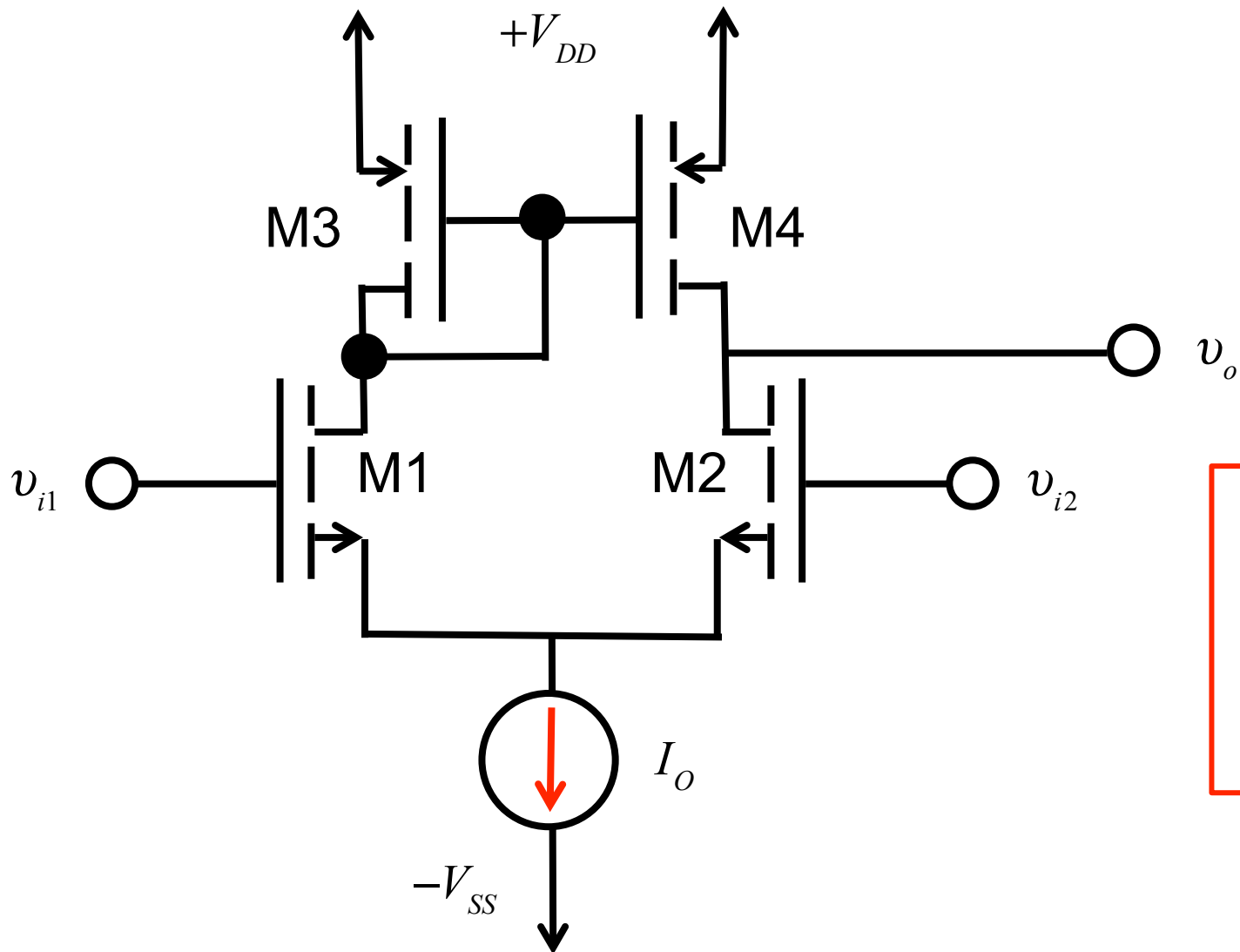


$$A_{dm} = g_m R_L$$

$$A_{cm} = 0$$


Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit**
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary



Small signal circuit

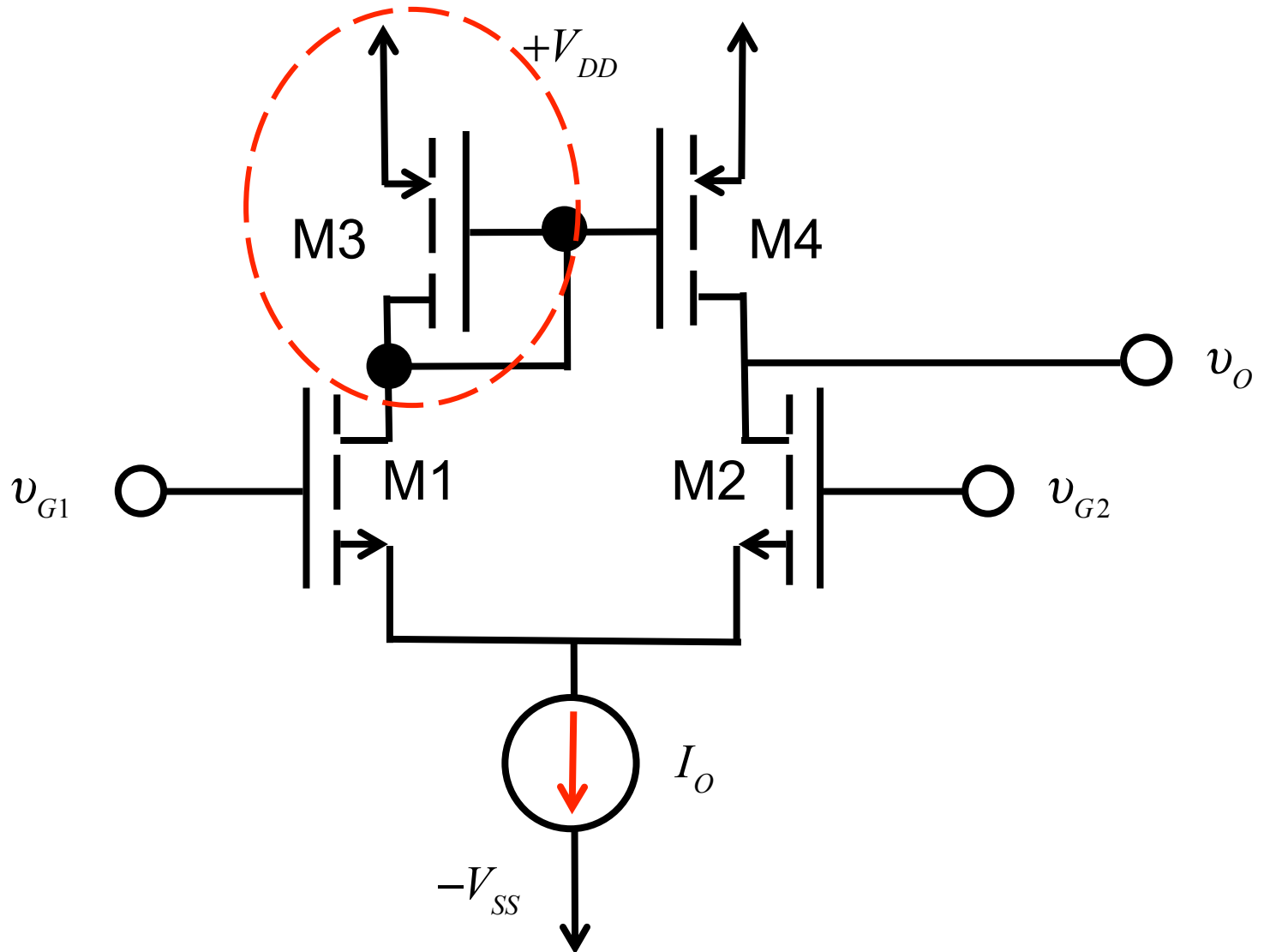


Hybrid-pi MOSFET model

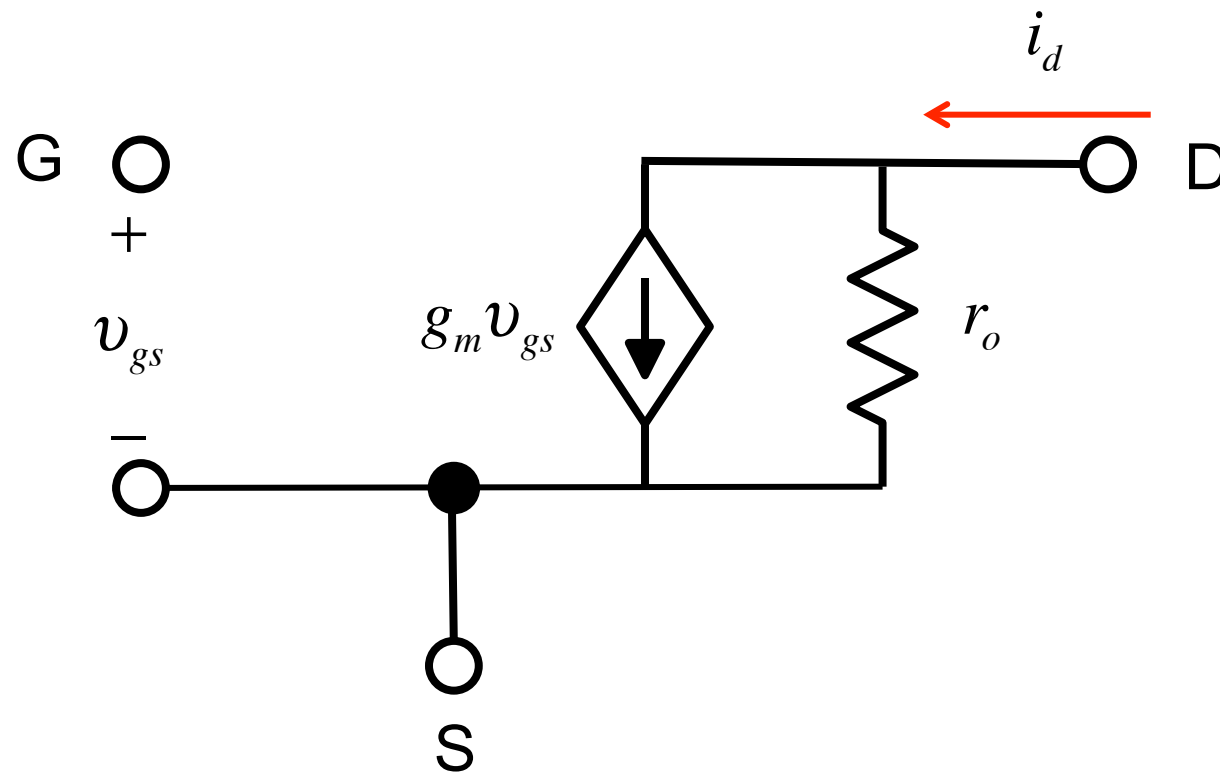


Diode connected MOSFET

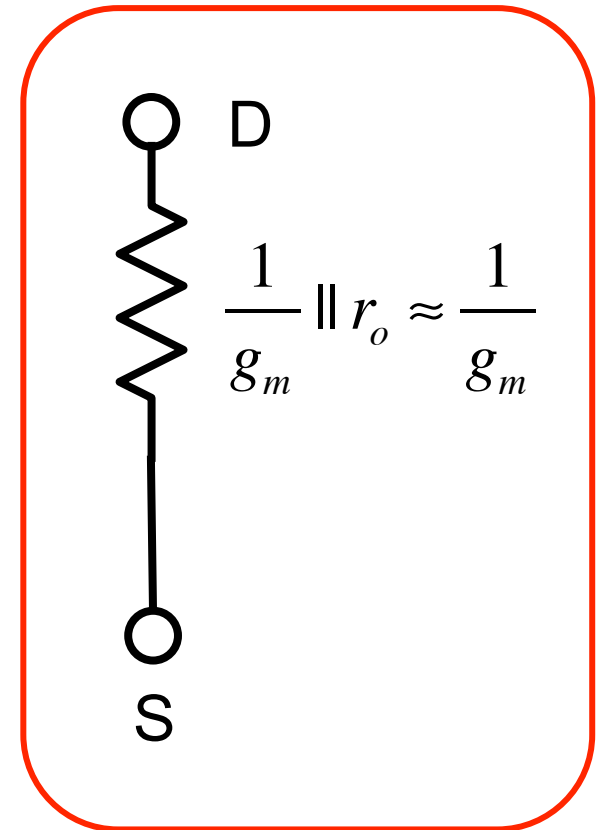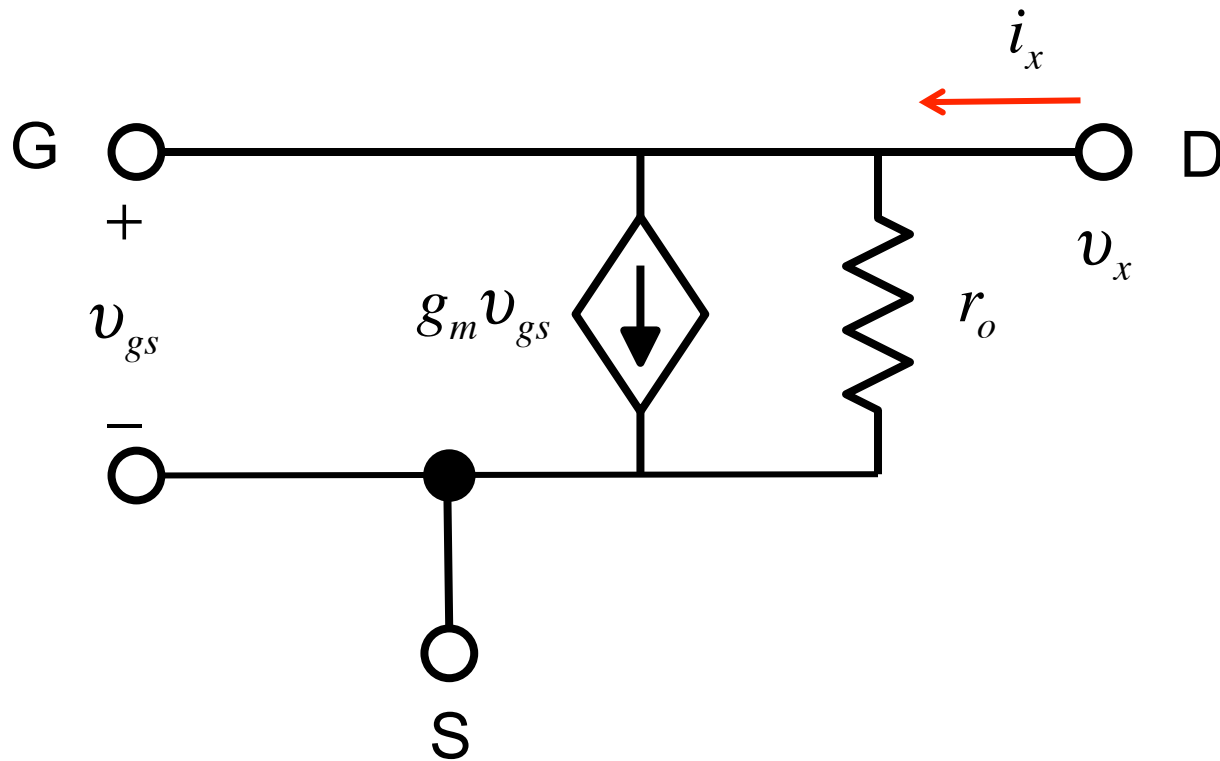

Small signal circuit

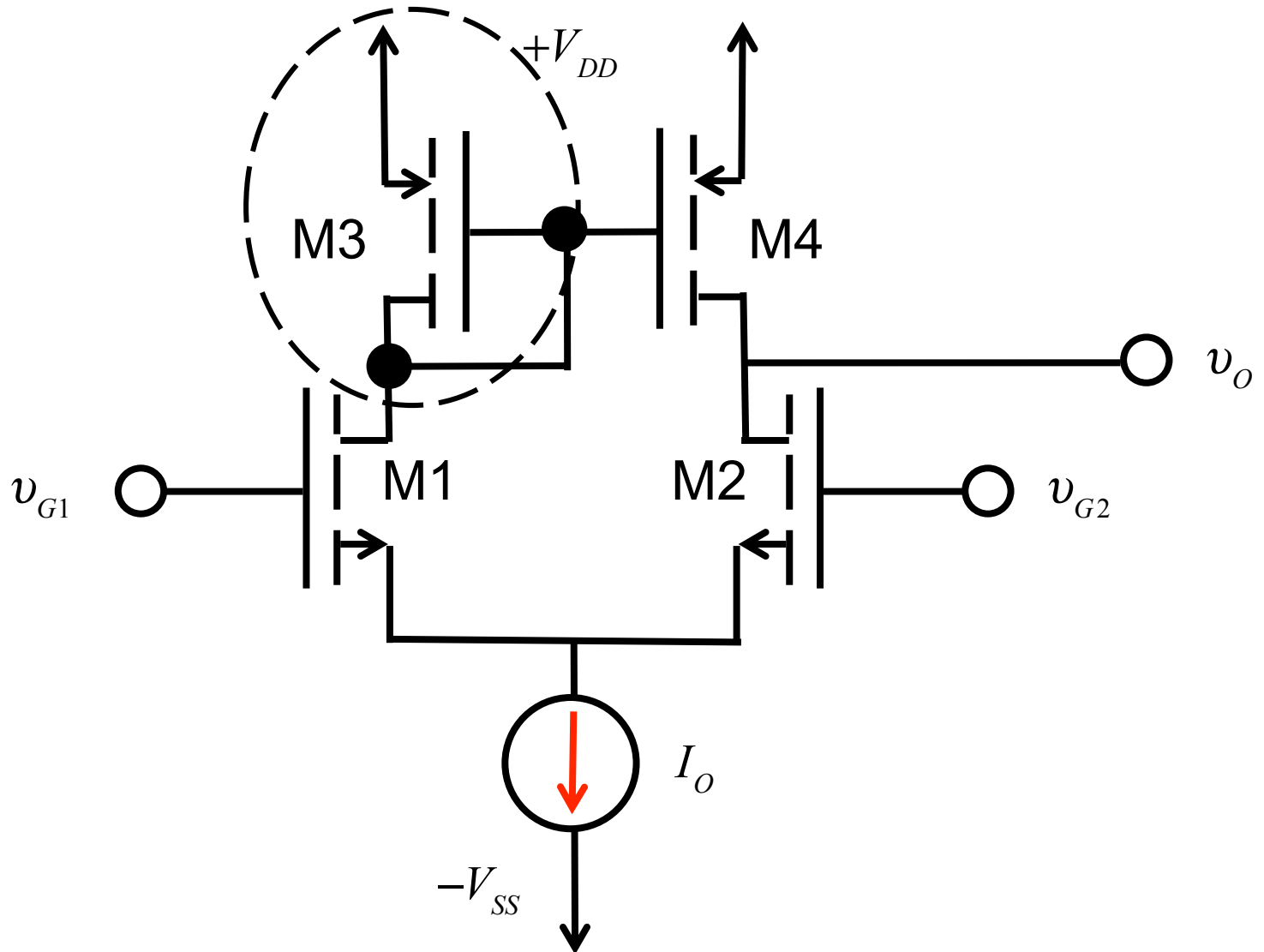


Small signal circuit

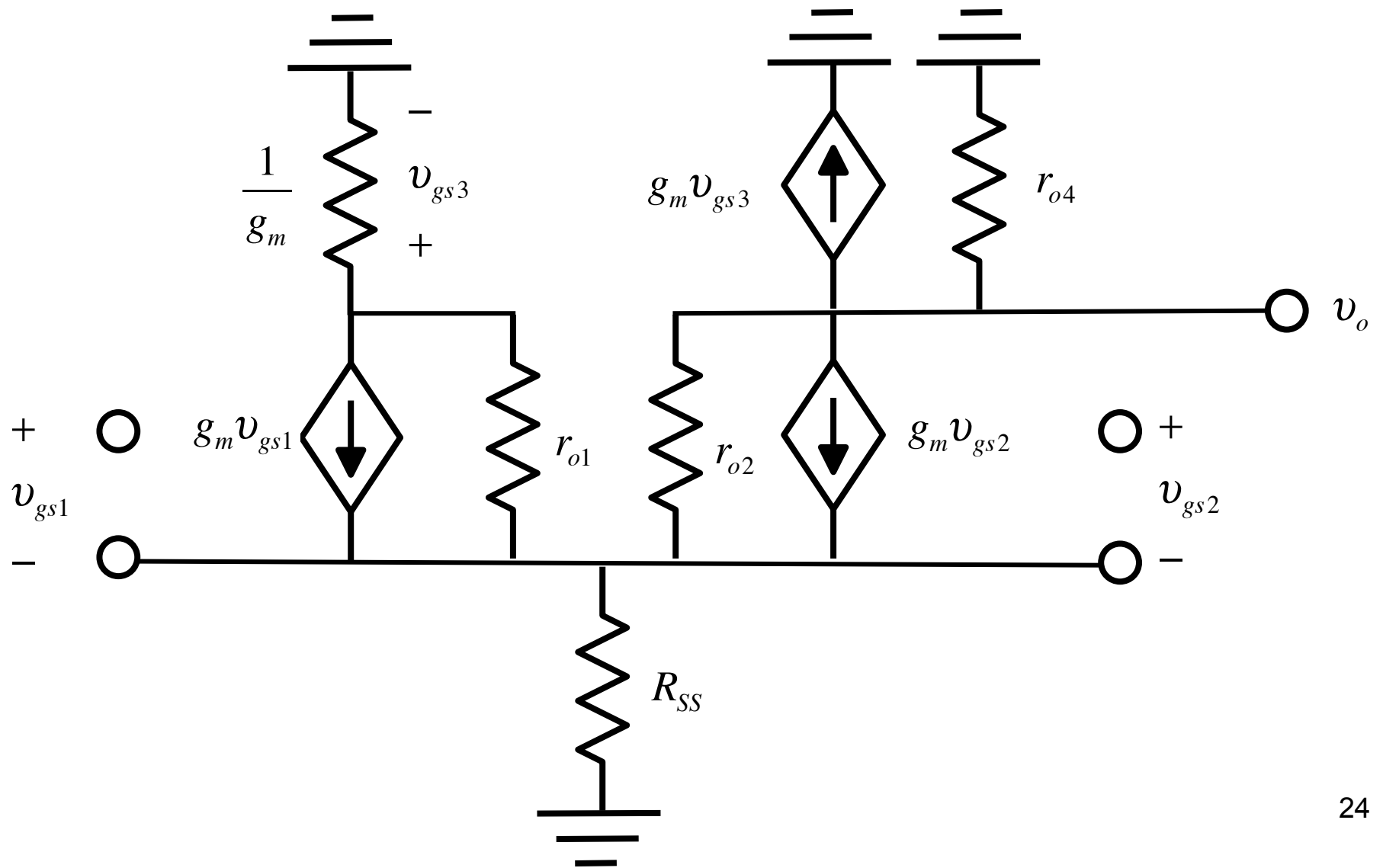


Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance**
- 7) Output resistance
- 8) Summary


Short circuit current / transconductance

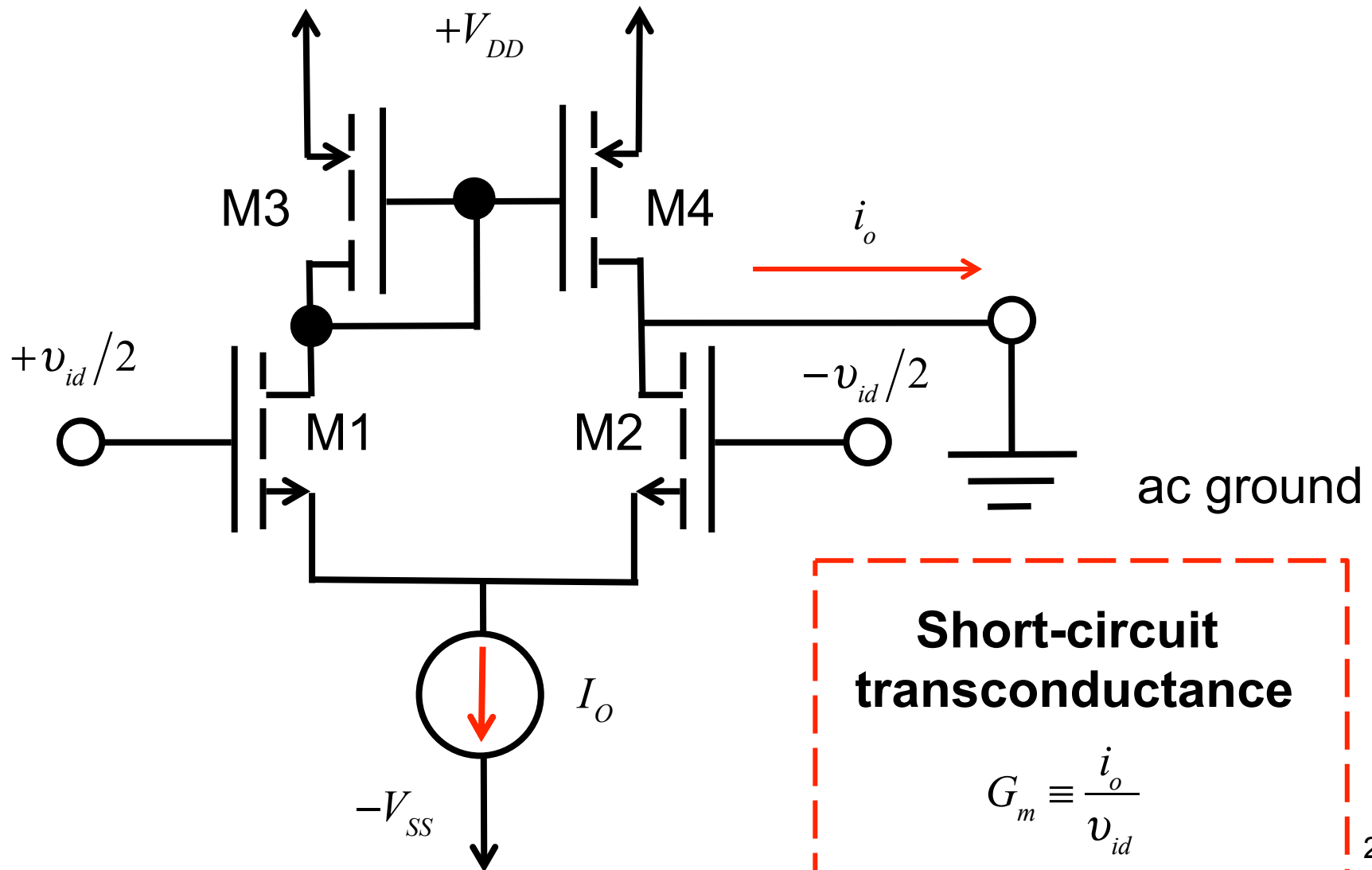


Short-circuit transconductance

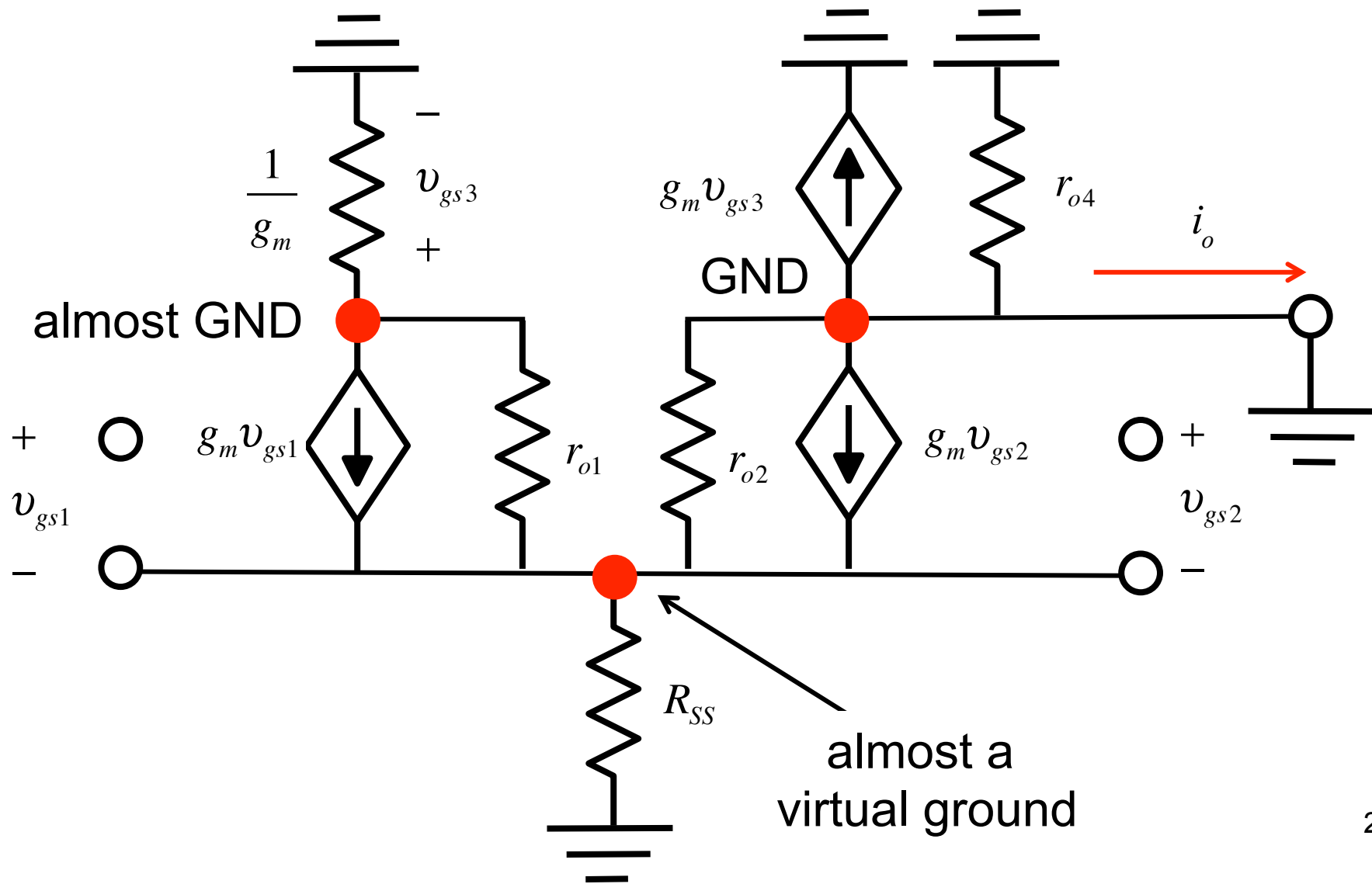

Short-circuit transconductance (2)

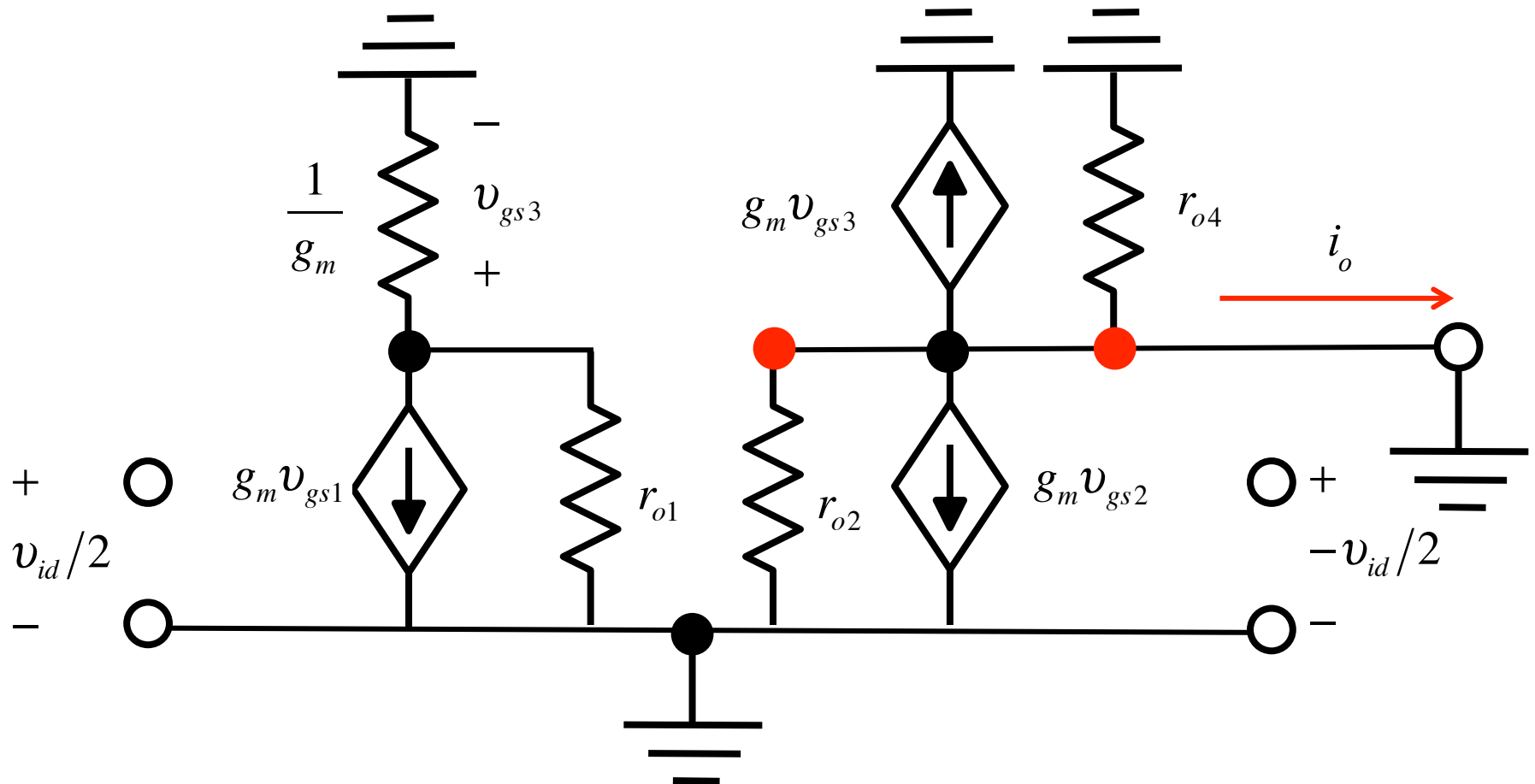


Short-circuit transconductance (3)

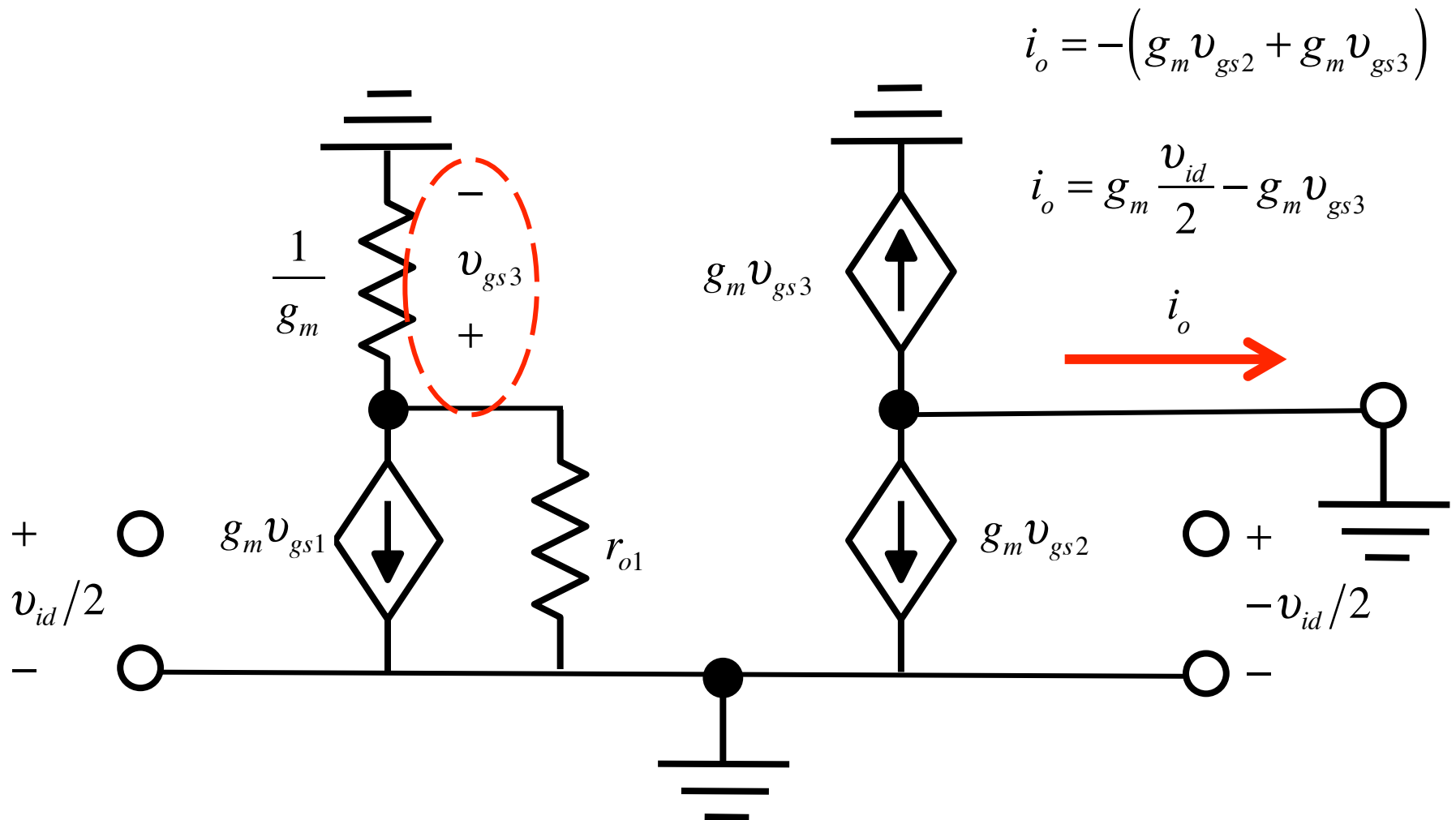

$$i_o = -(g_m v_{gs2} + g_m v_{gs3})$$


$$i_o = g_m \frac{v_{id}}{2} - g_m v_{gs3}$$

Short-circuit transconductance (4)

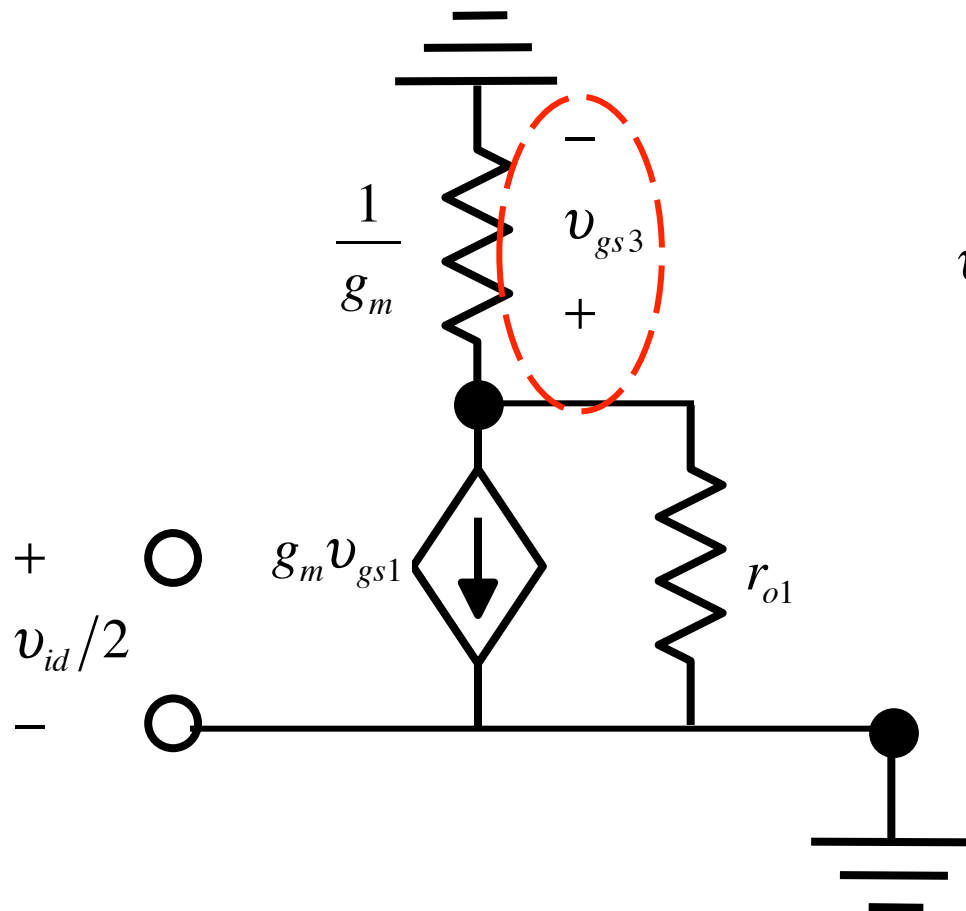


$$v_{gs3} = -g_m \frac{v_{id}}{2} \left(\frac{1}{g_m} \parallel r_{o1} \right) \approx -\frac{v_{id}}{2}$$

Short-circuit transconductance (5)

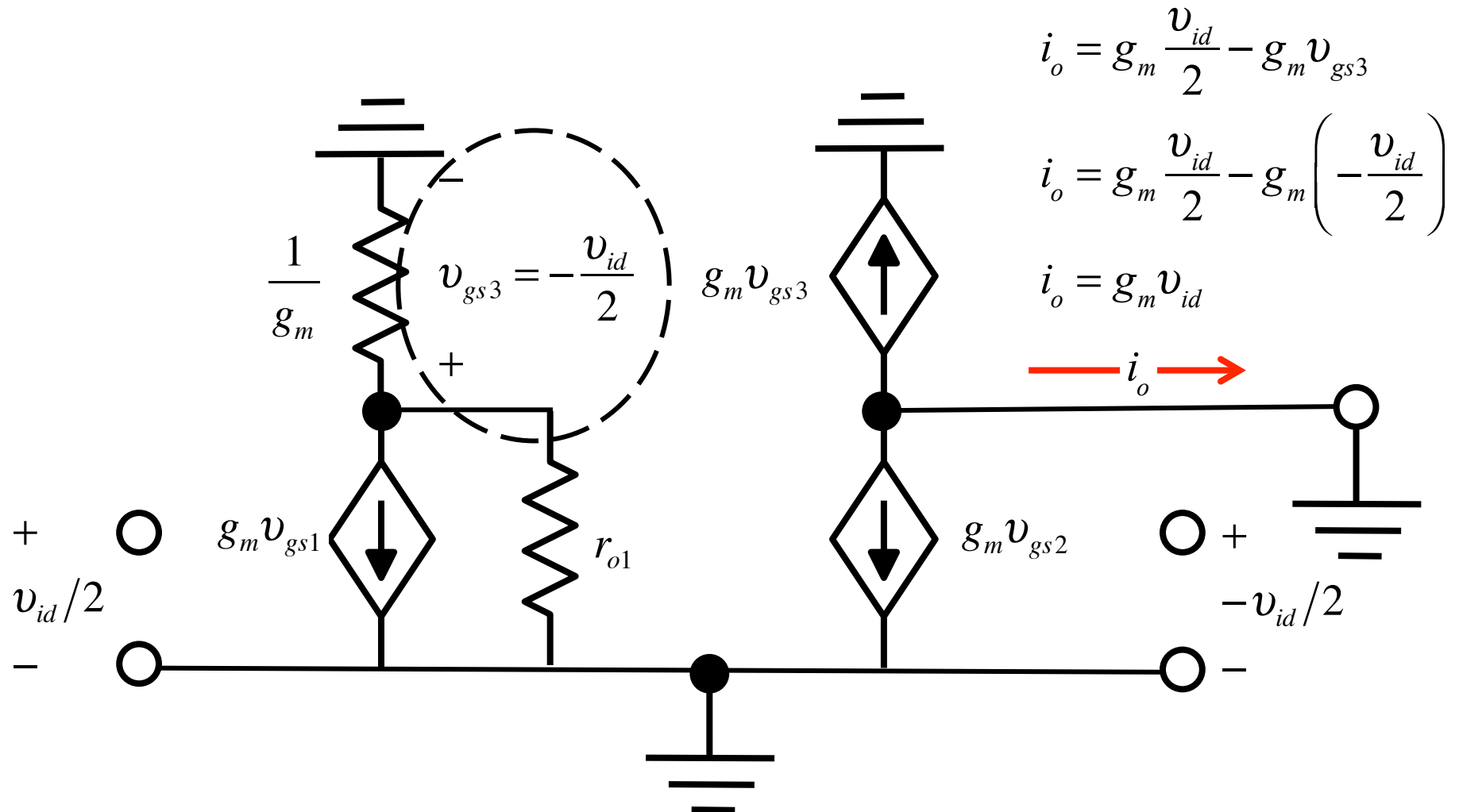


Short circuit transconductance

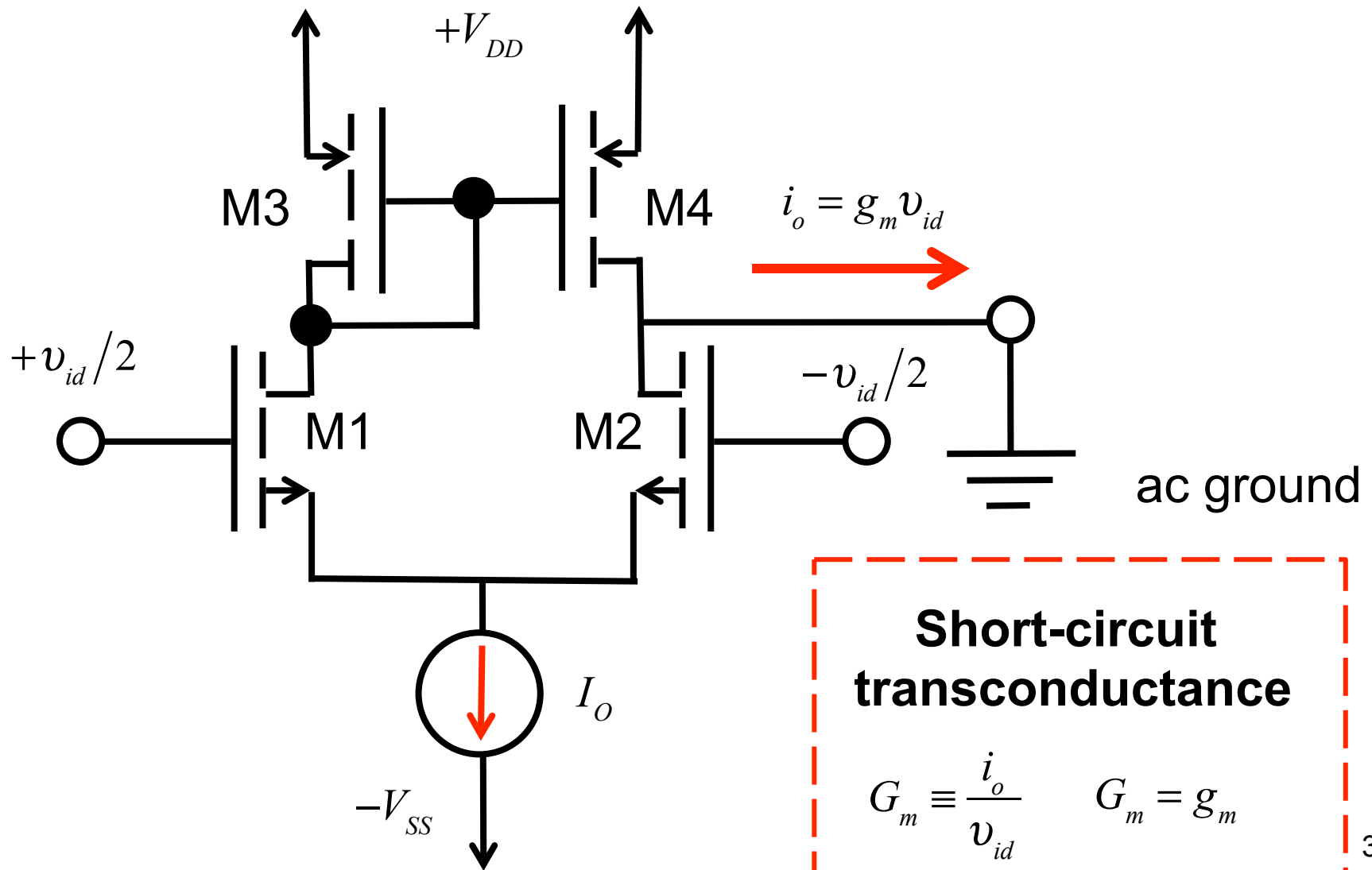


Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance**
- 8) Summary


Output resistance

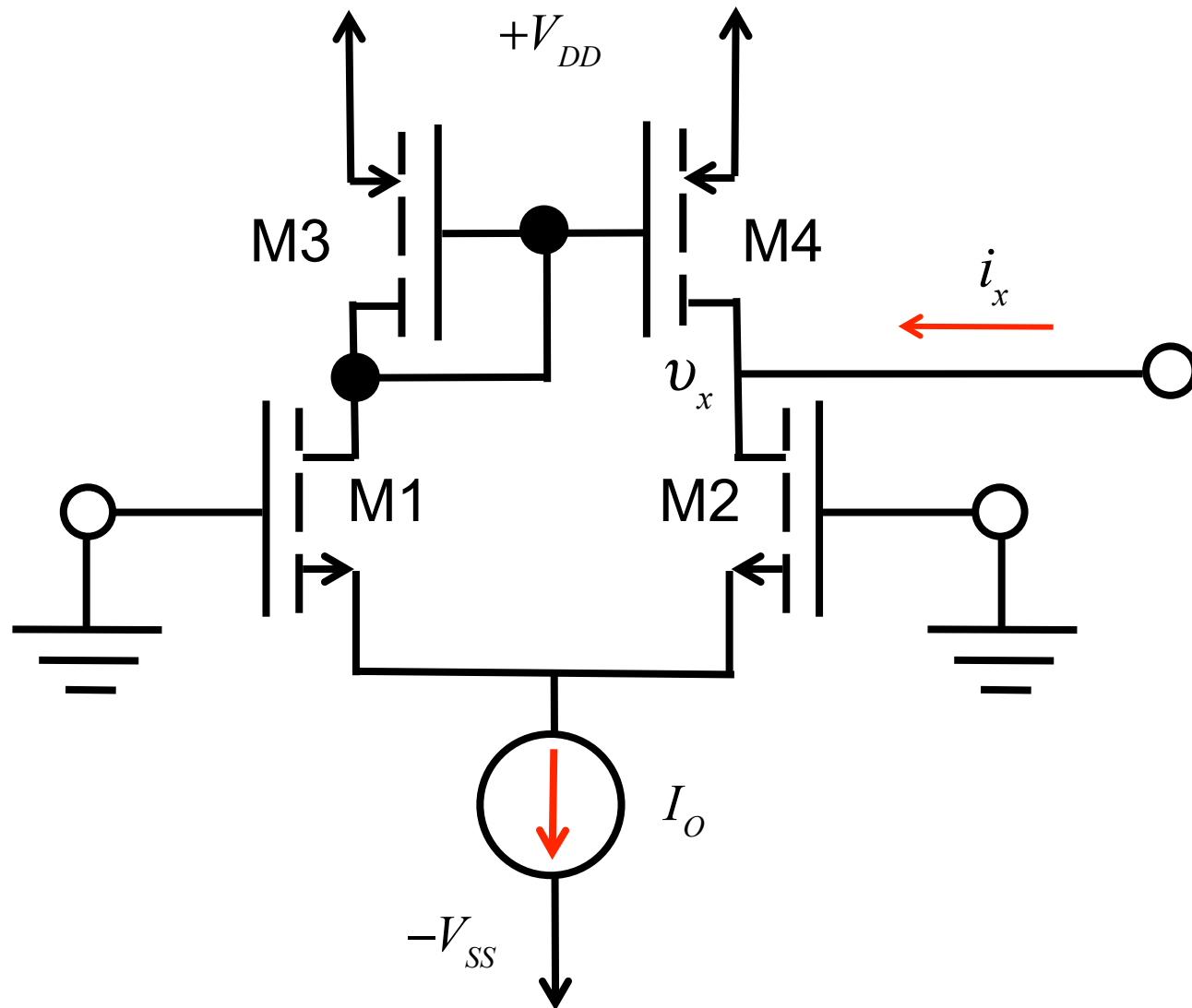

Output resistance (2)

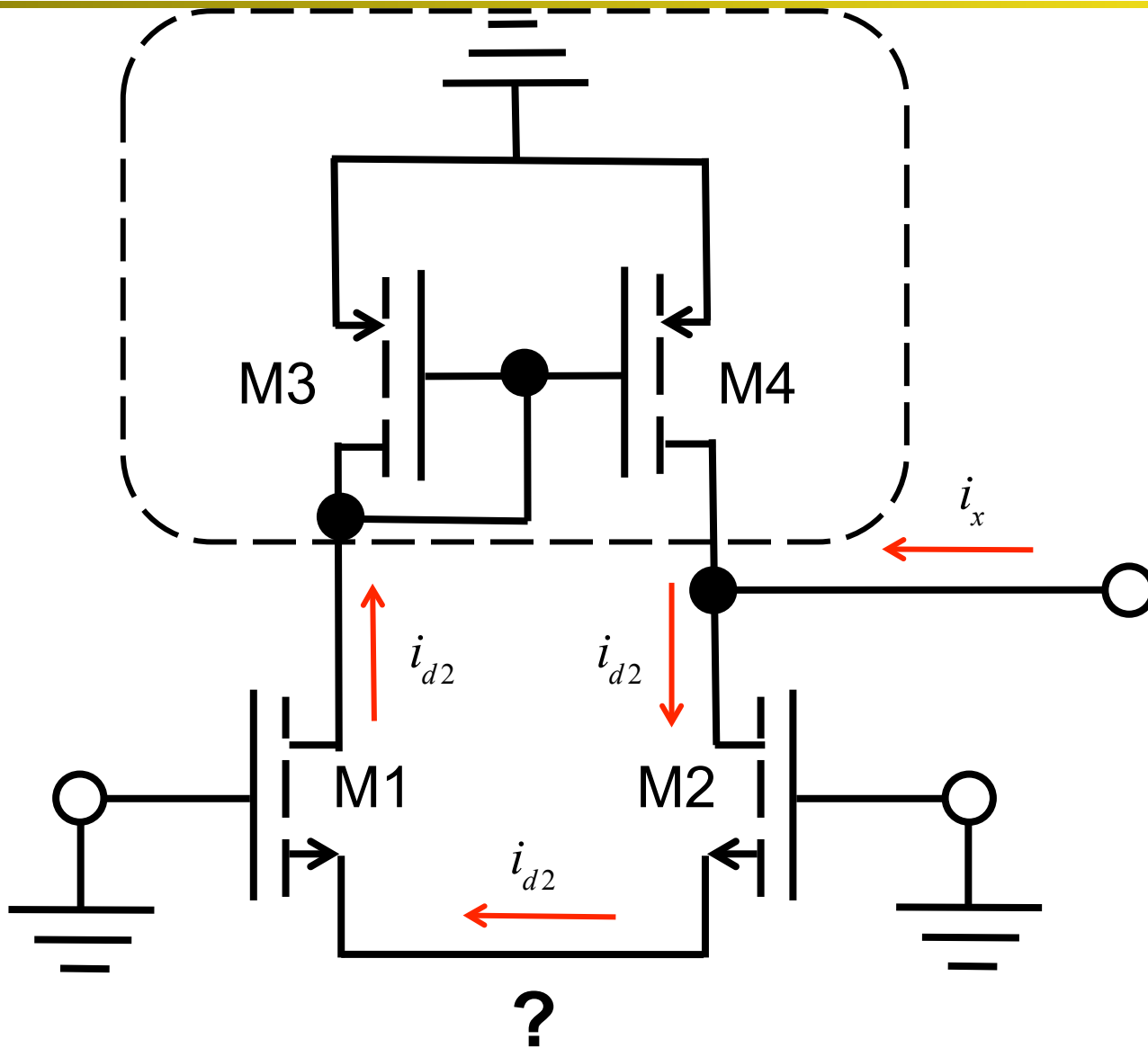

Output resistance (3)

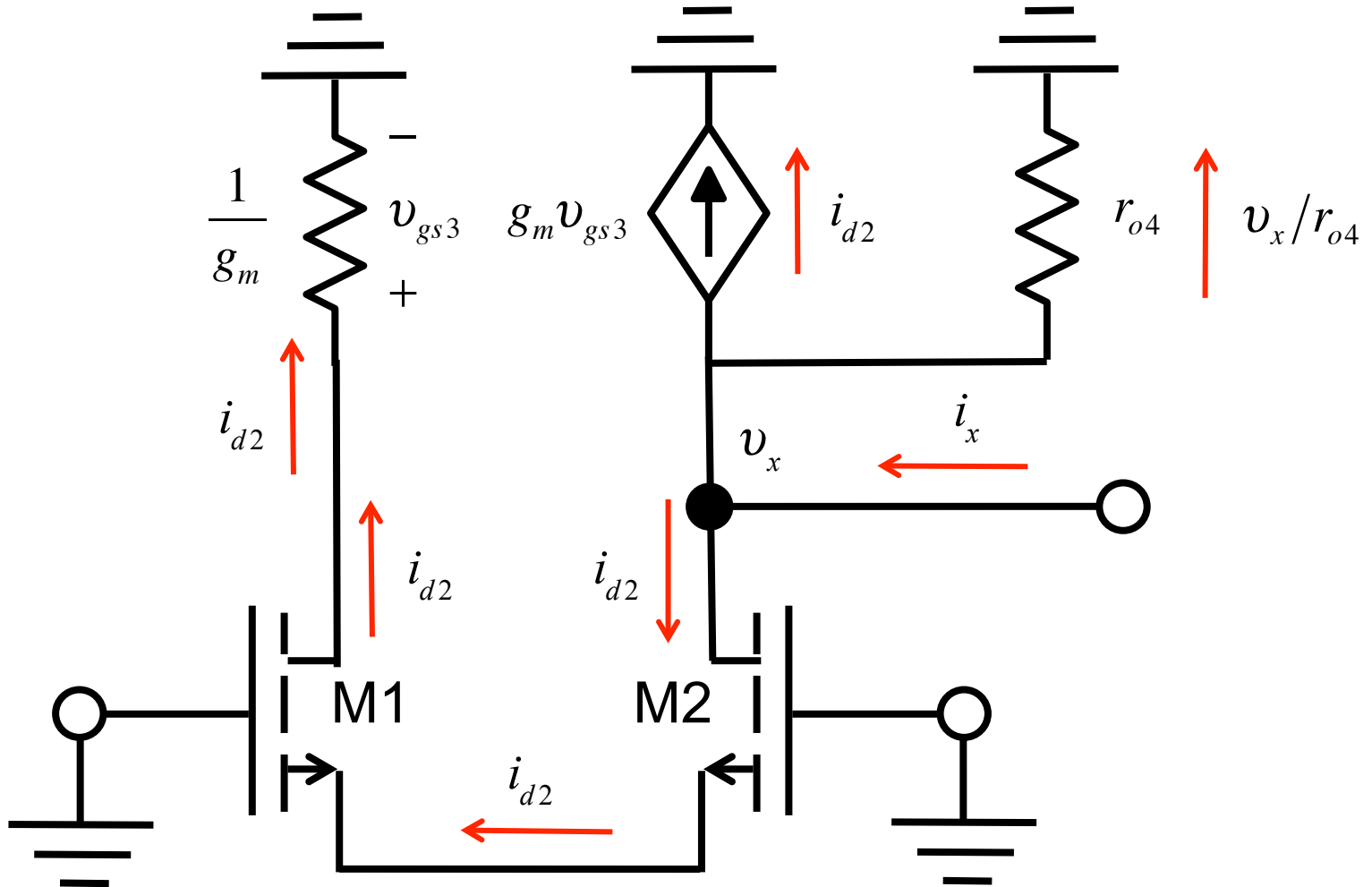


Output resistance looking into drain 2

$$i_{d2} = \frac{v_x}{R_{o2}}$$


$$R_{o2} = r_{o2} + g_m r_{o2} R_S$$

$$R_{o2} = r_{o2} + g_m r_{o2} \frac{1}{g_m}$$

$$R_{o2} = 2r_{o2}$$

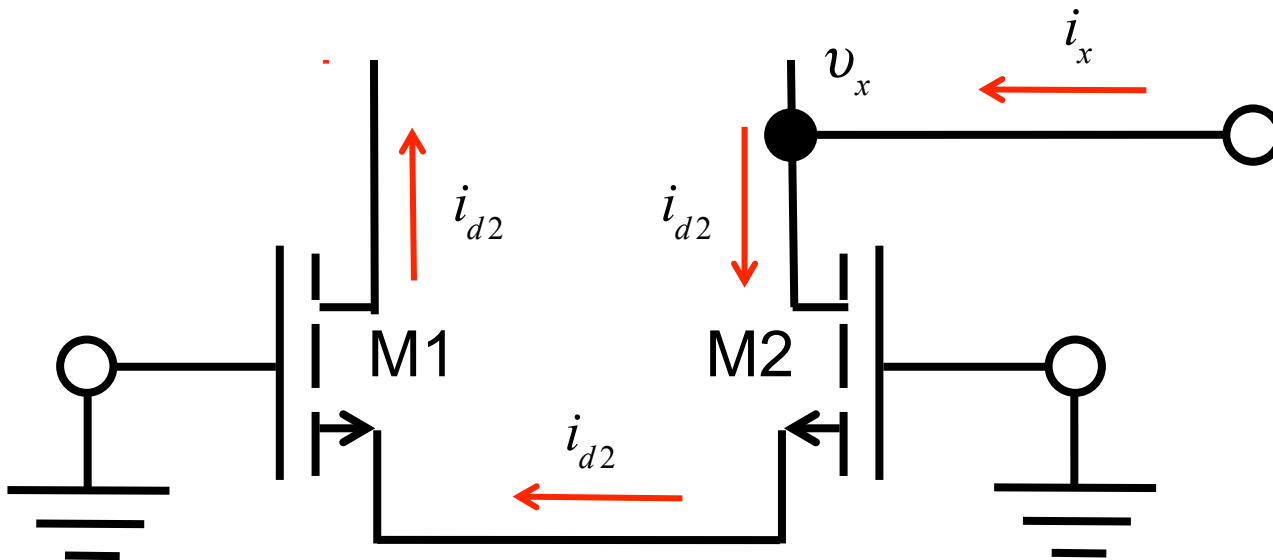

Finding i_x

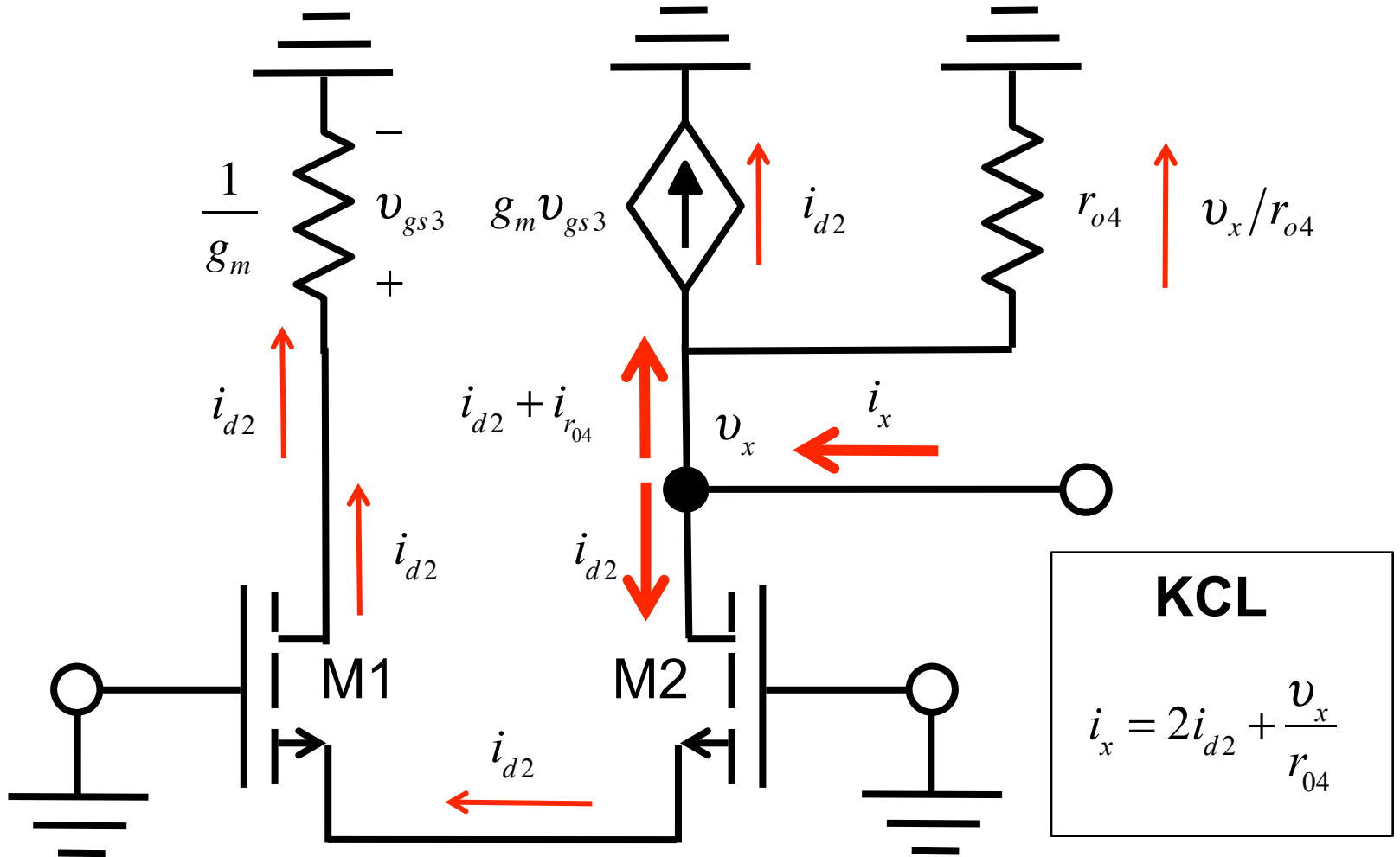

Small signal analysis

$$i_x = 2i_{d2} + \frac{v_x}{r_{o4}}$$

$$i_{d2} = \frac{v_x}{R_{o2}}$$

$$R_{o2} = 2r_{o2}$$


$$R_{out} = r_{o2} \parallel r_{o4}$$

$$i_x = \frac{2v_x}{2r_{o2}} + \frac{v_x}{r_{o4}} = v_x \left(\frac{1}{r_{o2}} + \frac{1}{r_{o4}} \right)$$

Outline

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) **Summary**

CM loaded differential pair

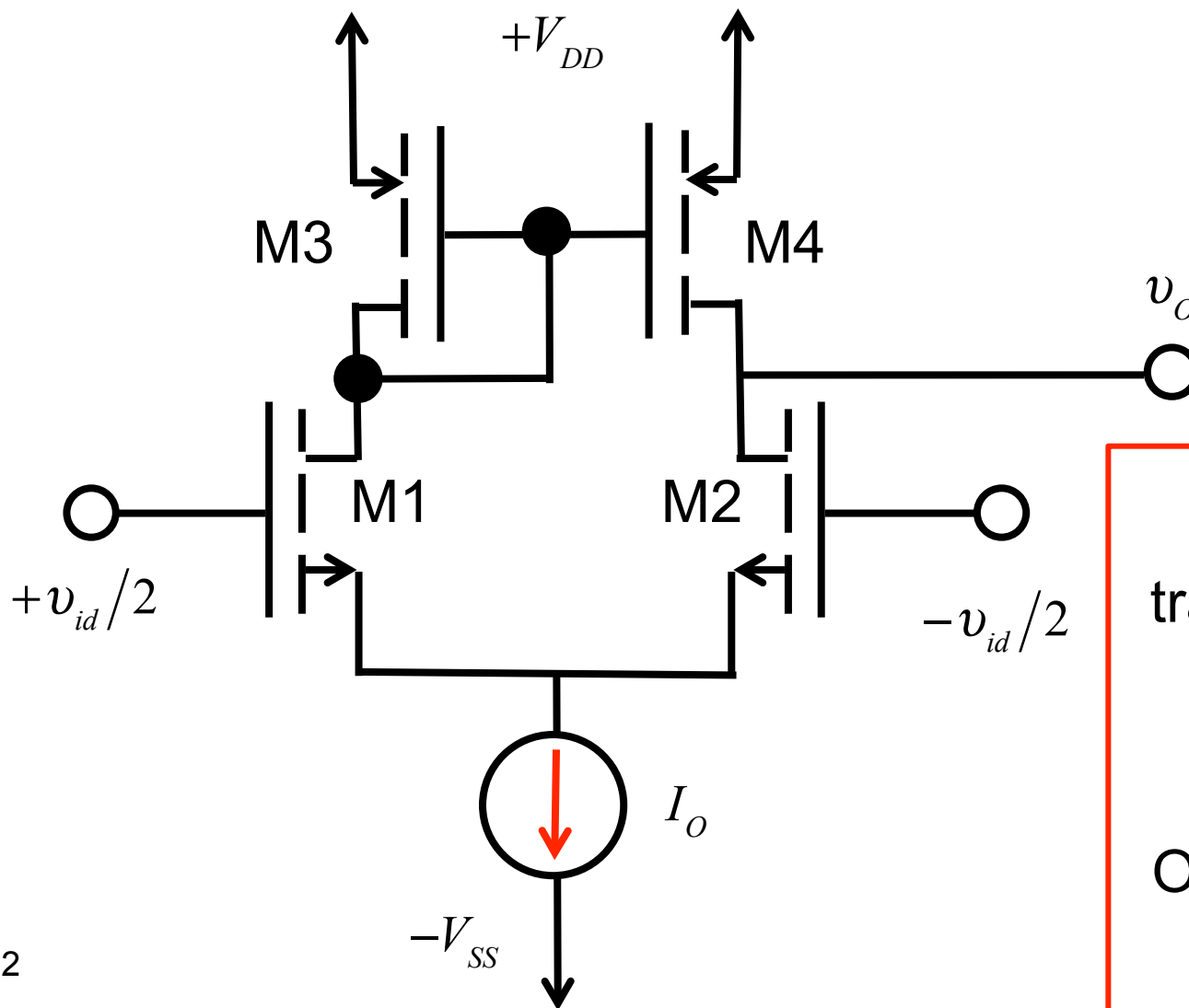


Short-circuit
transconductance

$$G_m \equiv \frac{i_o}{v_{id}} = g_m$$

Output resistance

$$R_{out} = r_{o2} \parallel r_{o4}$$

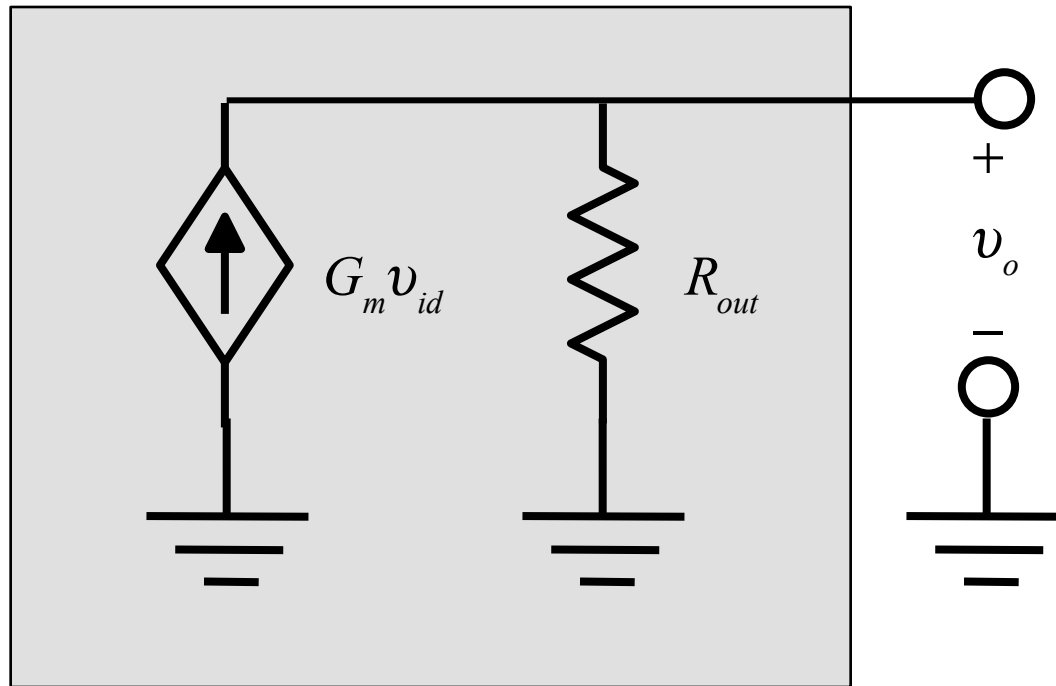SS output equivalent circuit of the amplifier



Questions

- 1) Quick Review
- 2) MOS Op Amps
- 3) Active loads
- 4) Simple analysis
- 5) Small signal circuit
- 6) Short circuit transconductance
- 7) Output resistance
- 8) Summary

