

Spring 2019 Purdue University

ECE 255: L30

Diff Amp Exercises


Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA




Announcements

HW9 Due 5:00 PM Friday, April 12 in EE-209 dropbox



Exam 1 + Exam 2 + Exam 3

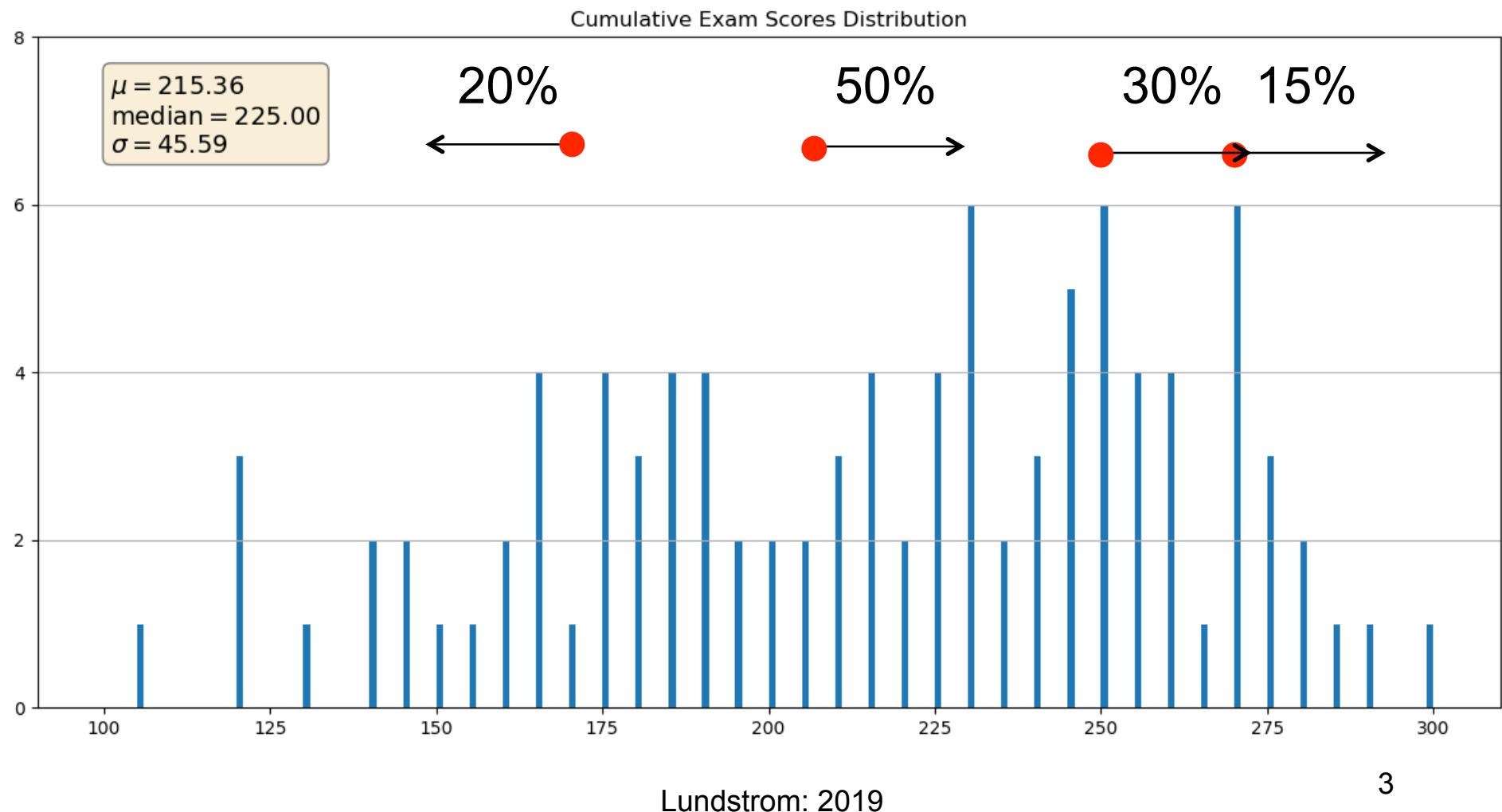

Spice Project 3

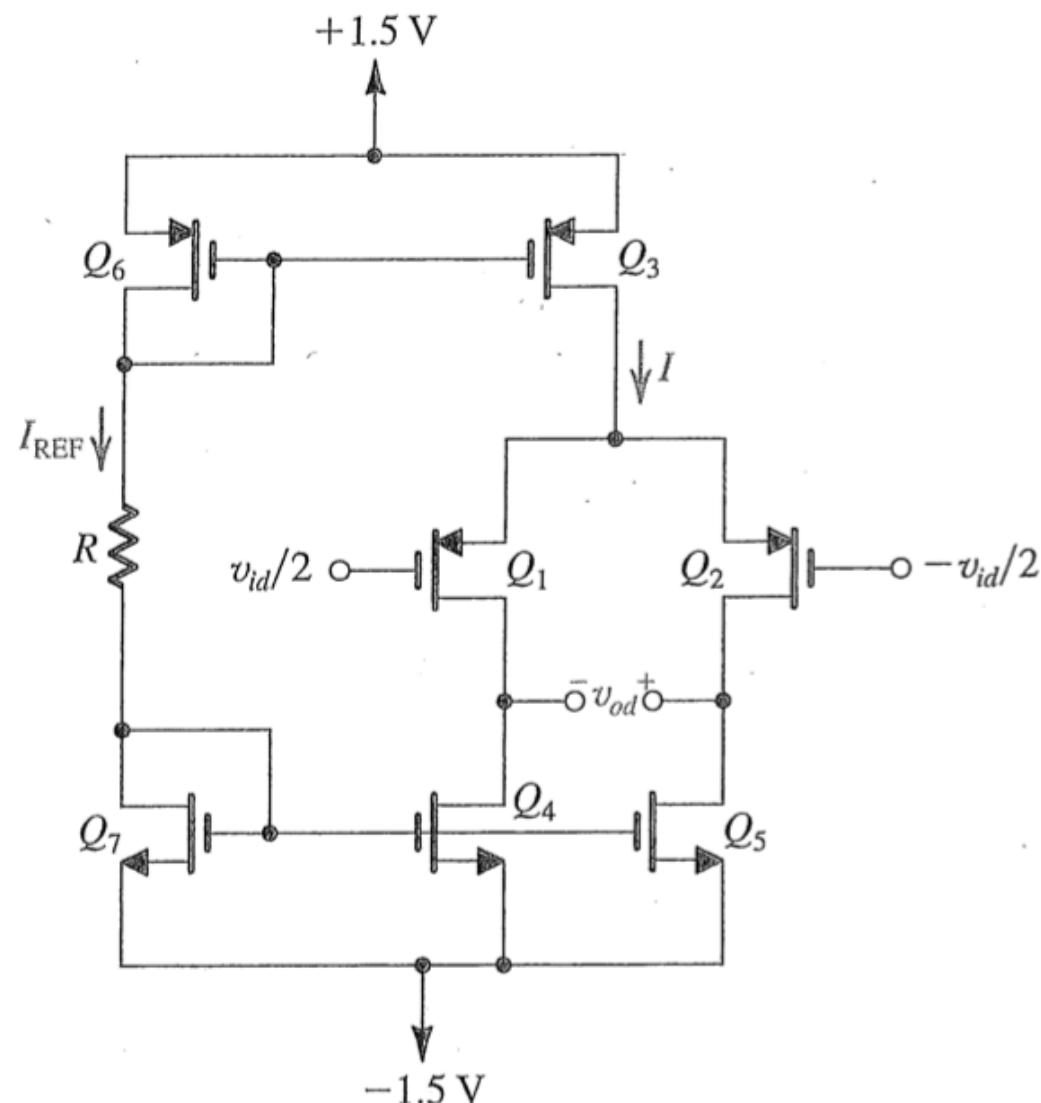



Spice Project 3

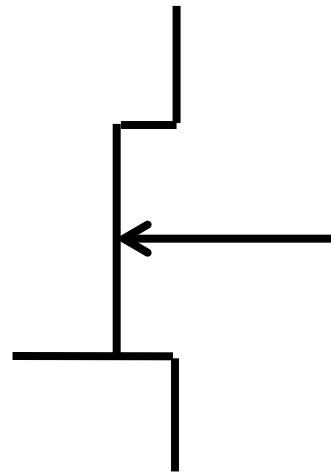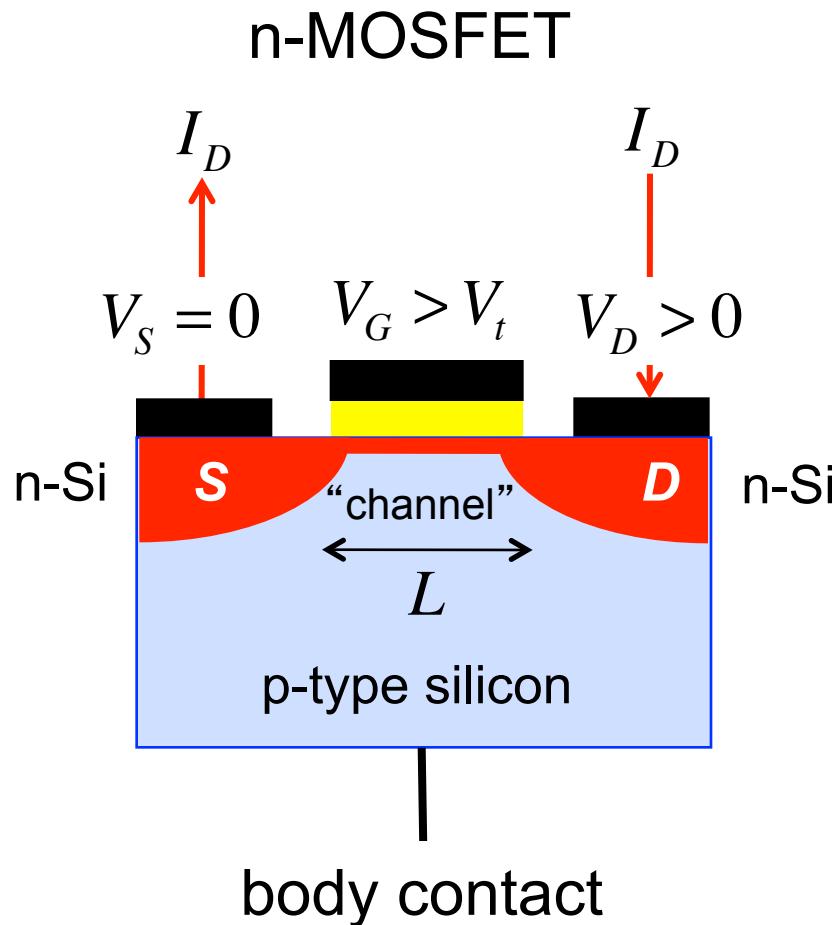

Short to source

The source is the terminal with the **lower** voltage


Spice Project 3

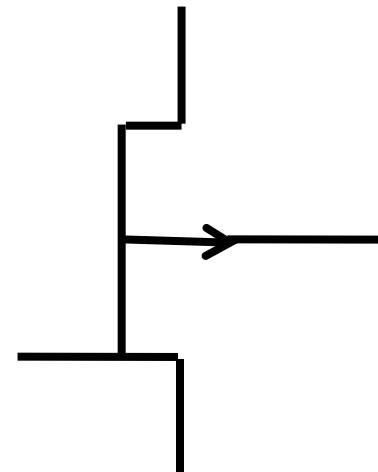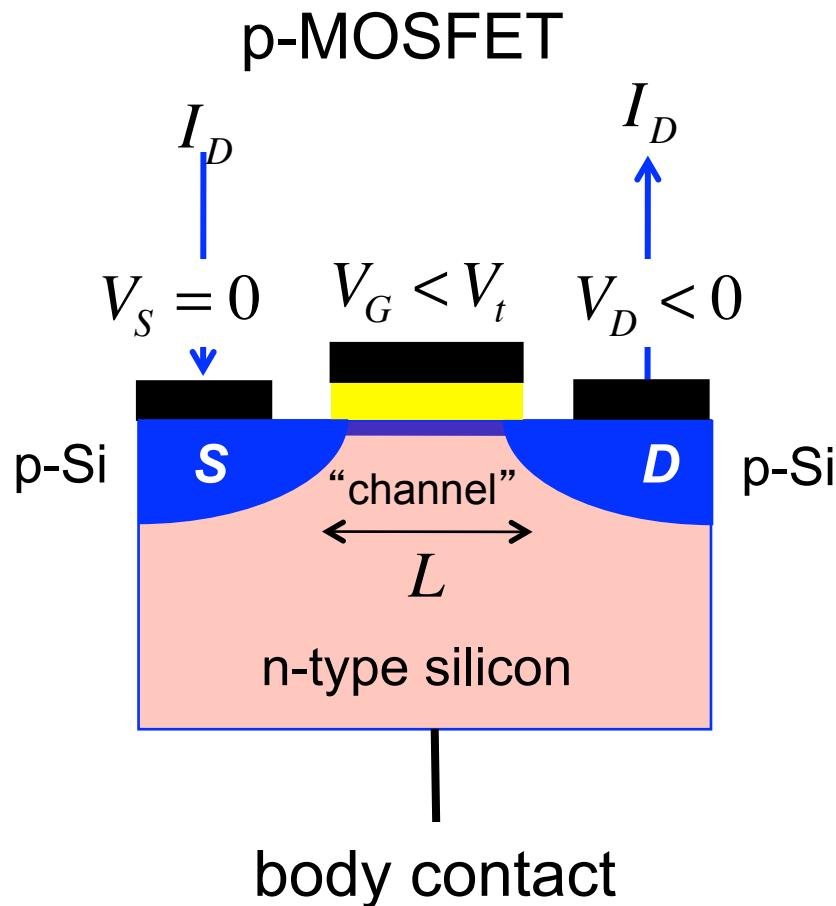

Short to source


The source is the terminal with the **higher** voltage

Problem 2.6

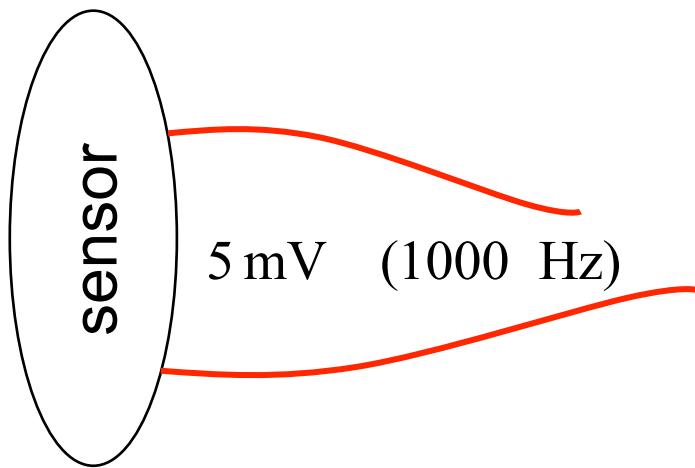

$v_{id} = ?$ $v_{ic} = ?$

$v_1 = ?$ $v_2 = ?$

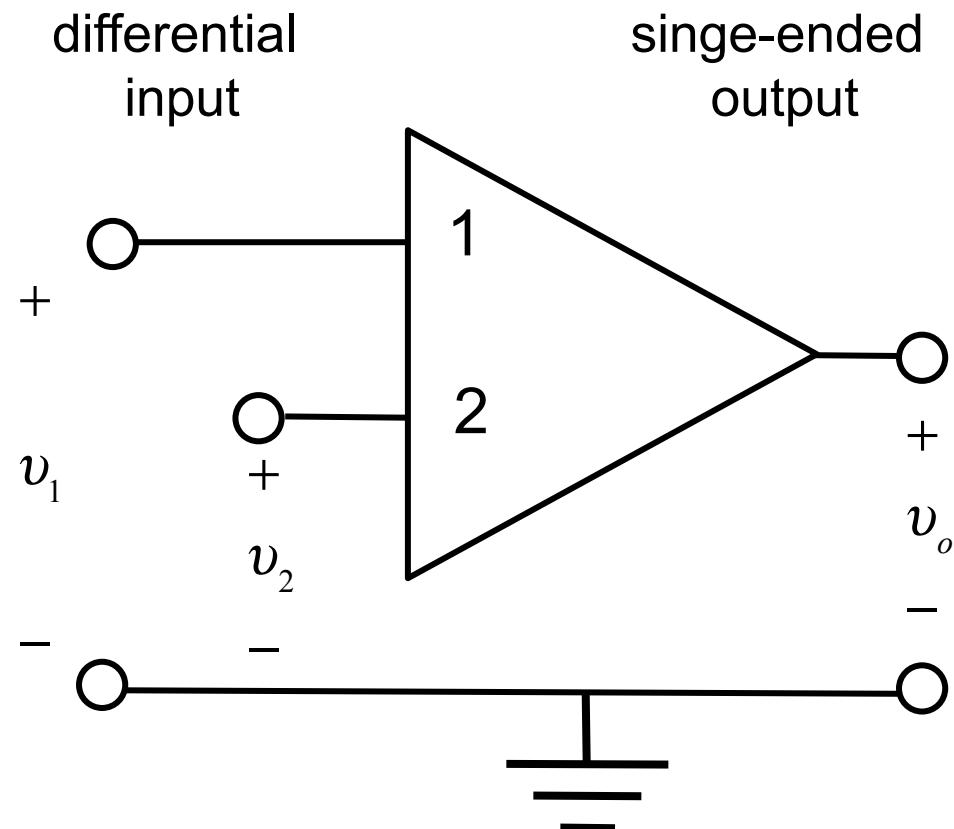

Problem 2.6 related


$$v_1 = 50 \text{ mV}$$

$$v_2 = 30 \text{ mV}$$


$$A_{dm} = 100 \text{ V/V}$$

$$A_{cm} = 0.1 \text{ V/V}$$

$v_o = ? \text{ mV}$

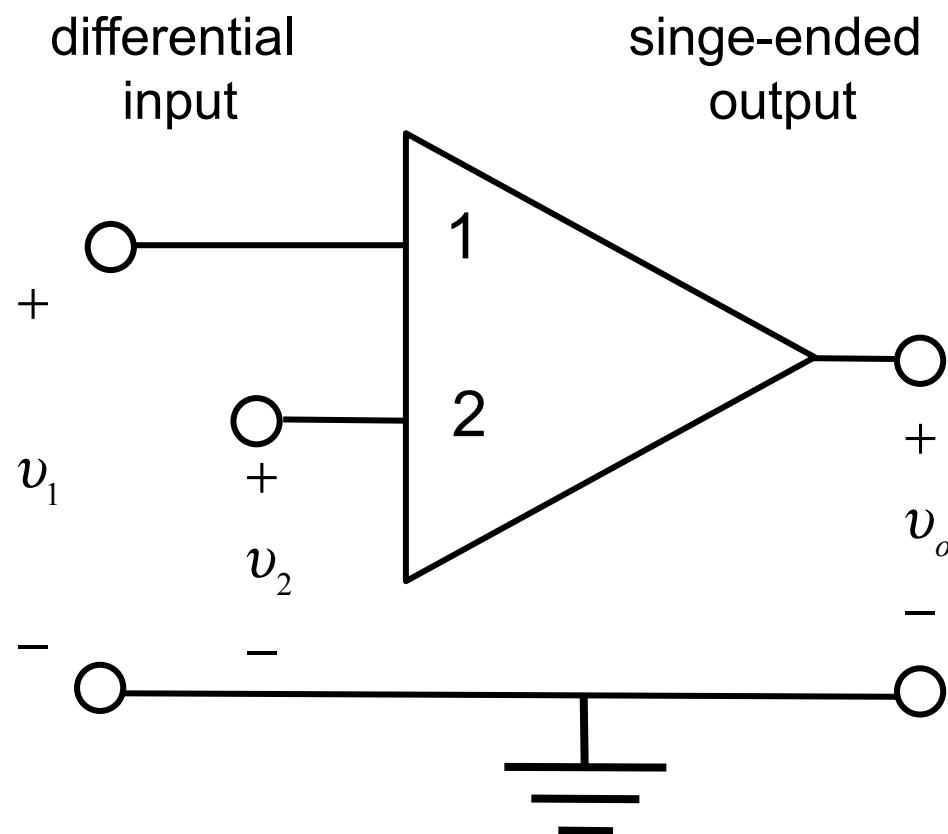

Problem 9.14 (design)

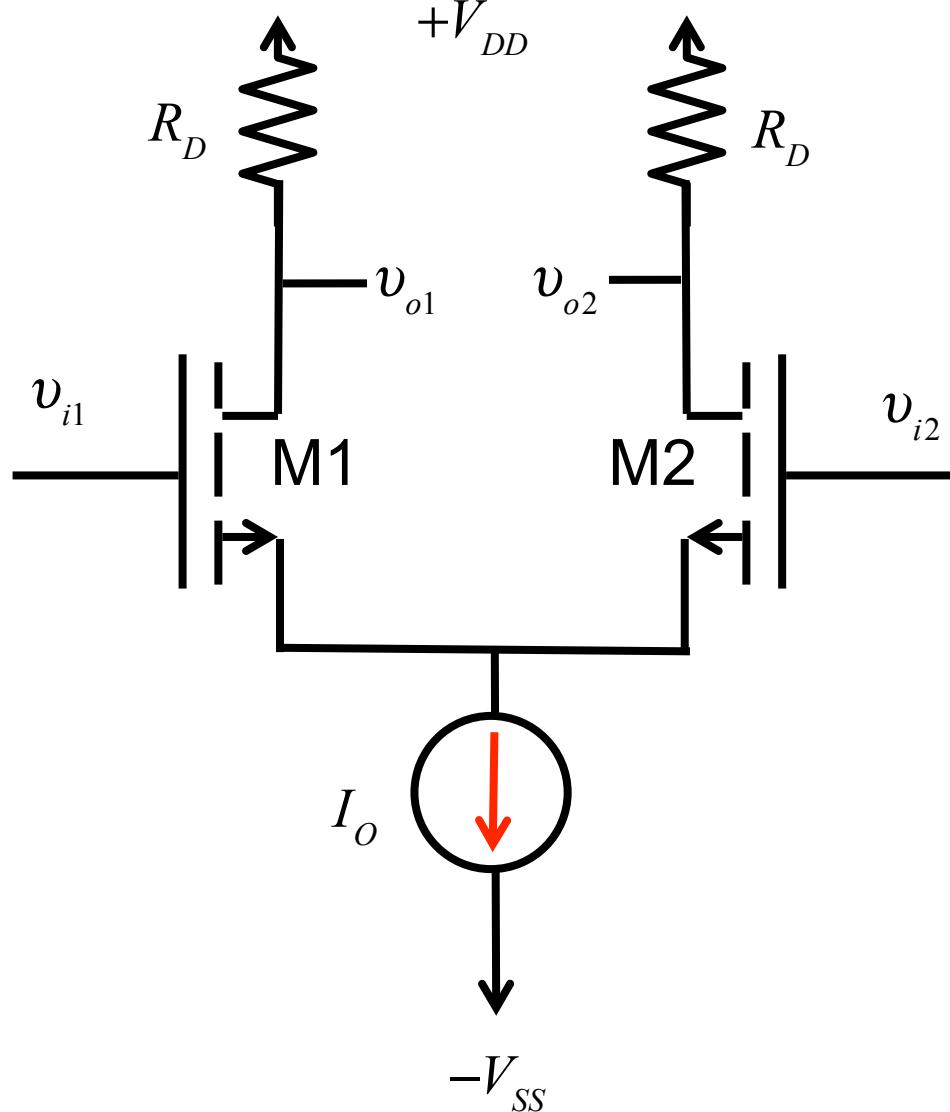

$$V_{DD} = V_{SS} = 1 \text{ V}$$

$$P_D < 1 \text{ mW} \text{ (equilibrium)}$$

$$v_{O1} = v_{O2} = 0.2 \text{ V}$$

$$A_{dm} = 10$$


$$\mu_n C_{ox} = 400 \mu\text{A/V}^2$$

$$V_A = \infty$$


$$I_0 = ? \quad W/L = ?$$

$$R_D = ?$$


Problem 9.16 (analysis-a)

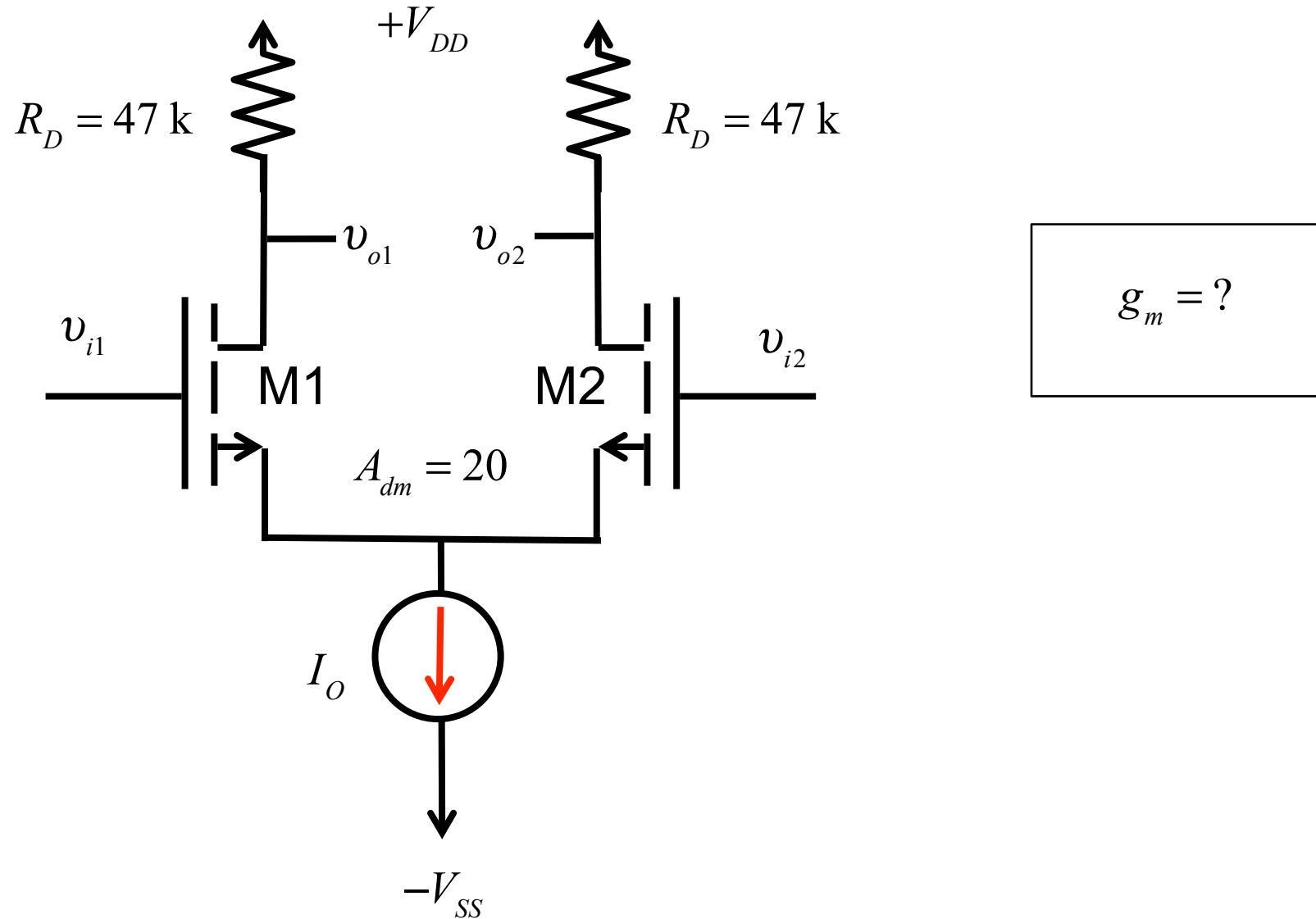


Problem 9.16 (analysis-b)

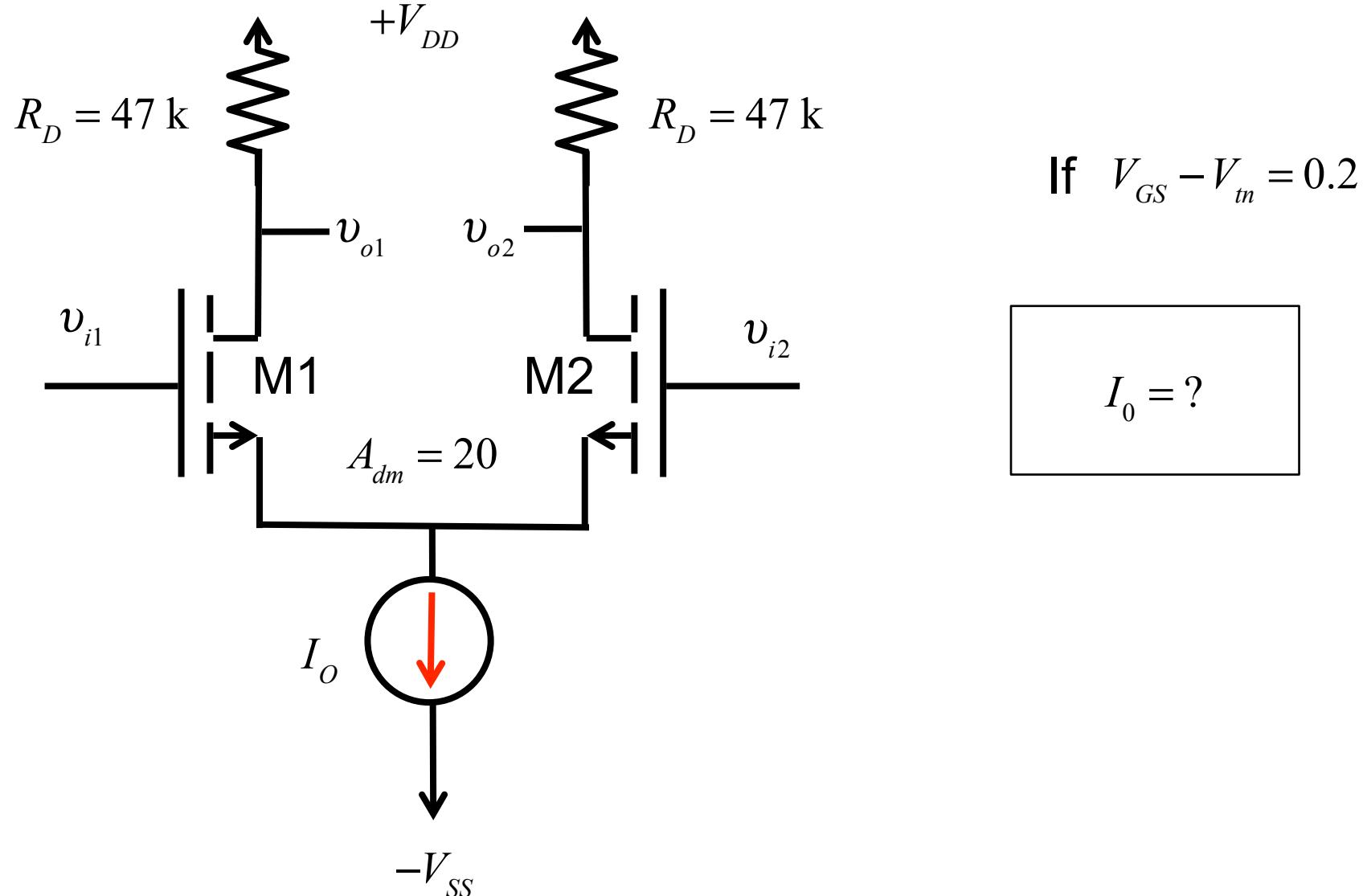


Problem 9.16 (analysis-c)

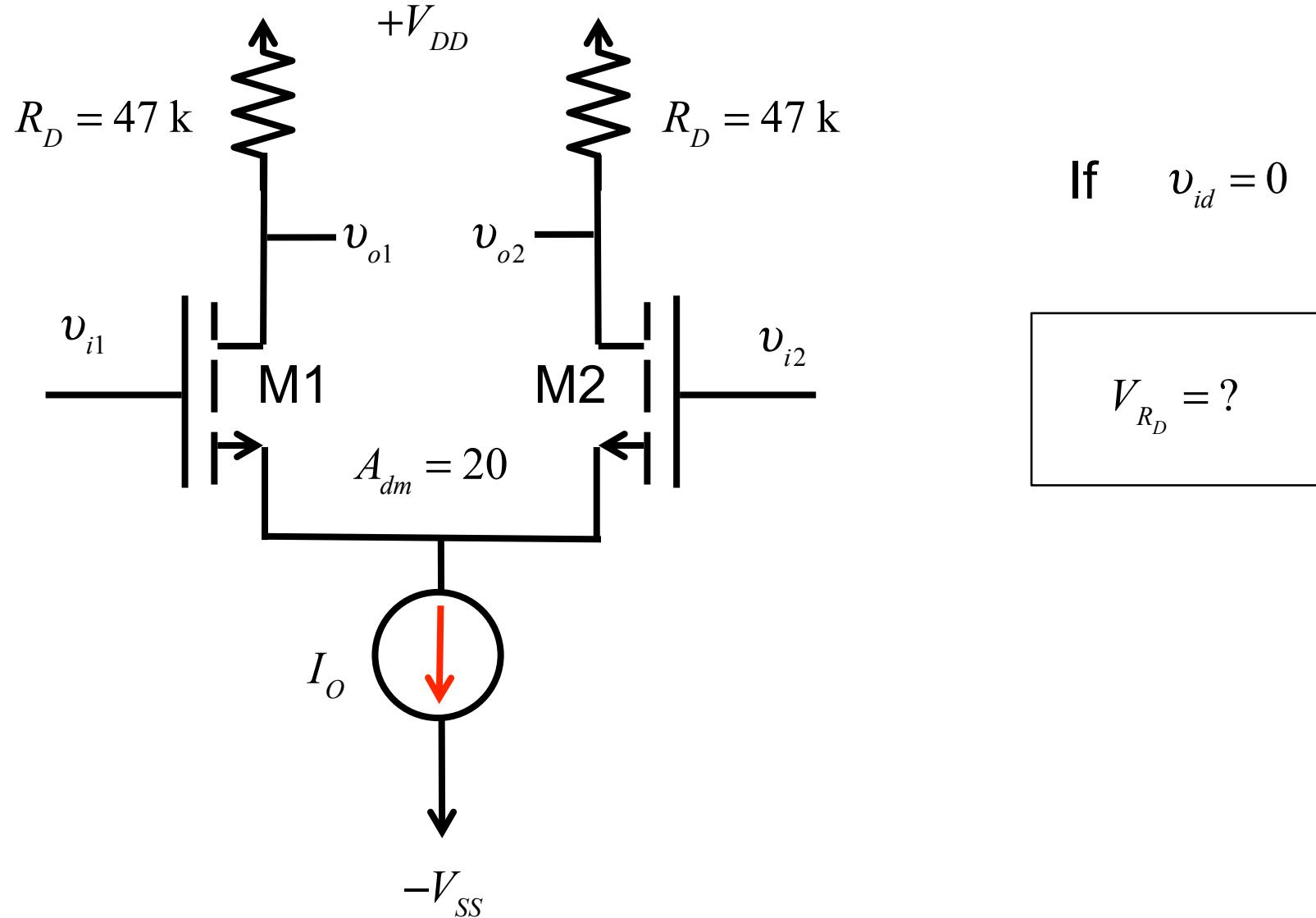


Problem 9.16 (analysis-d)

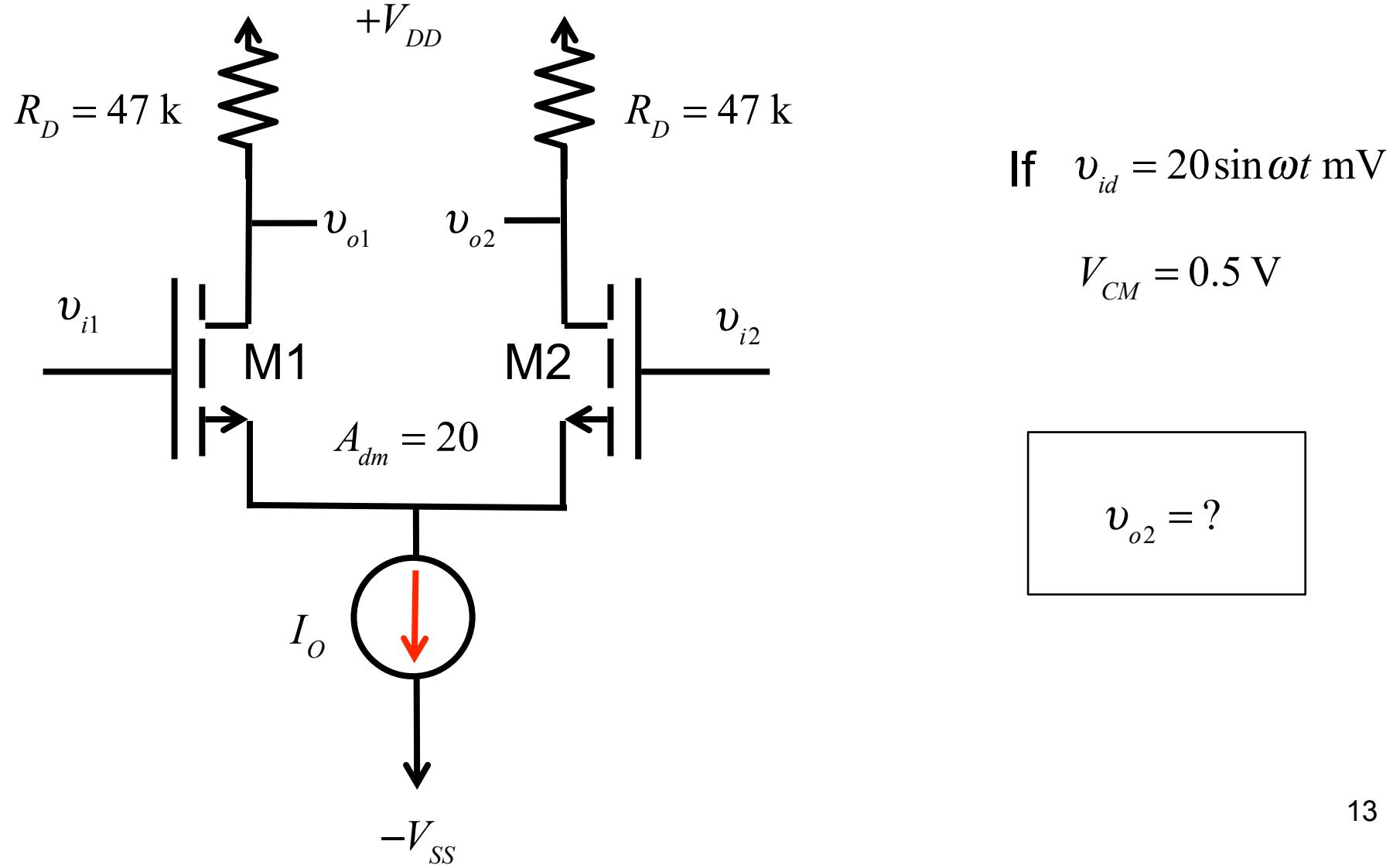

Problem 9.16 (analysis-e)

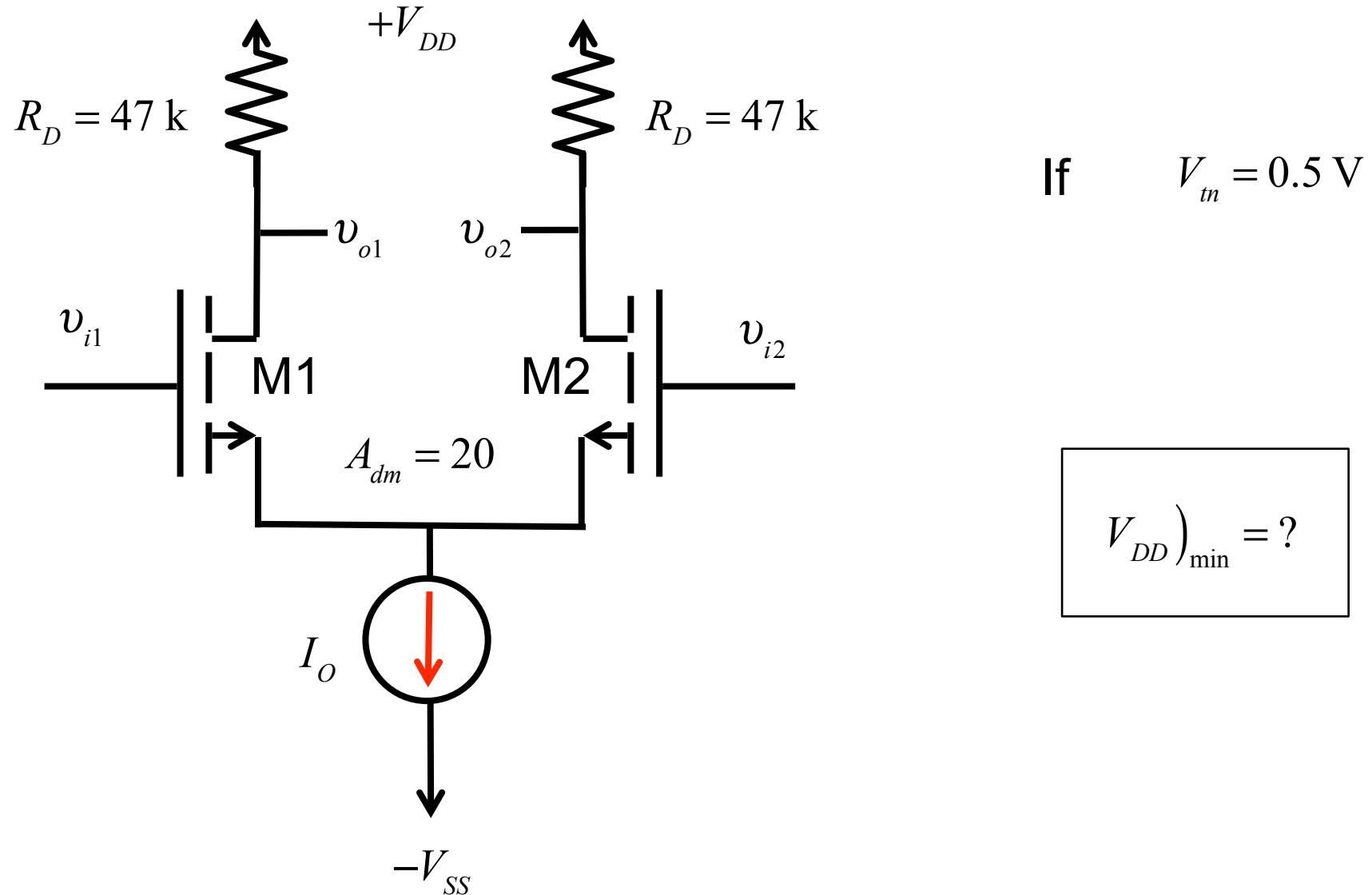

Problem 9.20

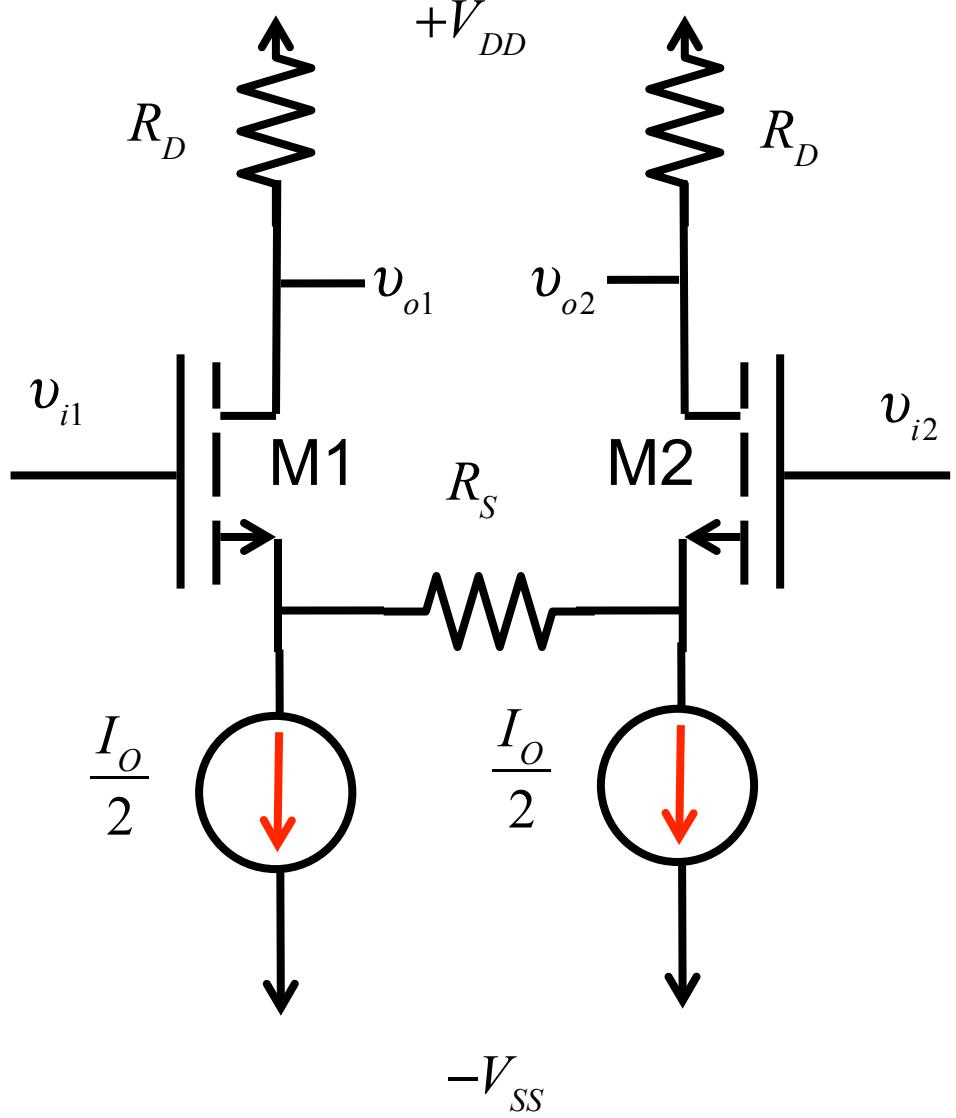


$$A_{dm} = ?$$


$$A_{dm}(R_S = 0) = ?$$

$$A_{dm}(R_S = ?) = \frac{A_{dm}(R_S = 0)}{2}$$


Problem 9.85

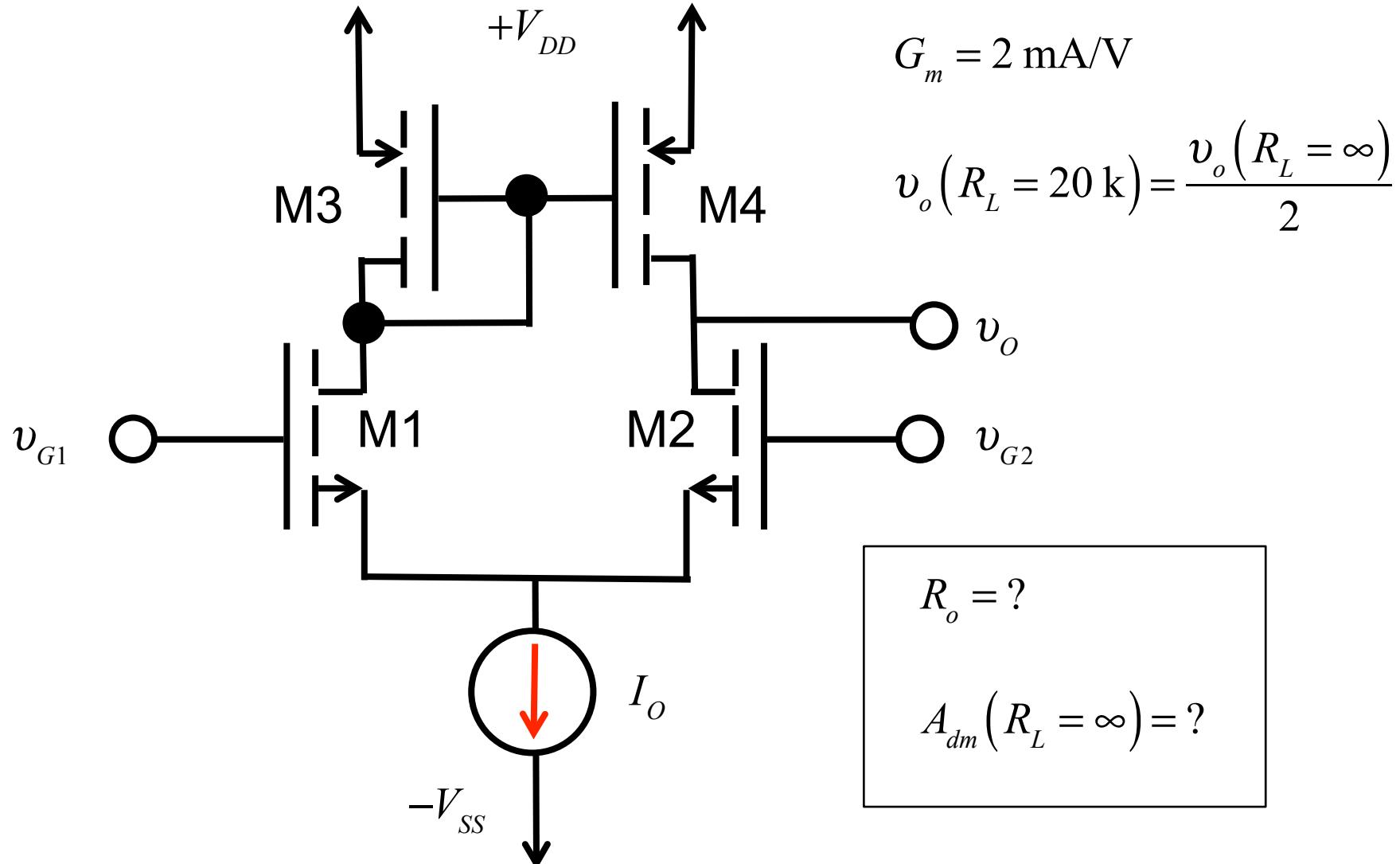


Problem 9.86

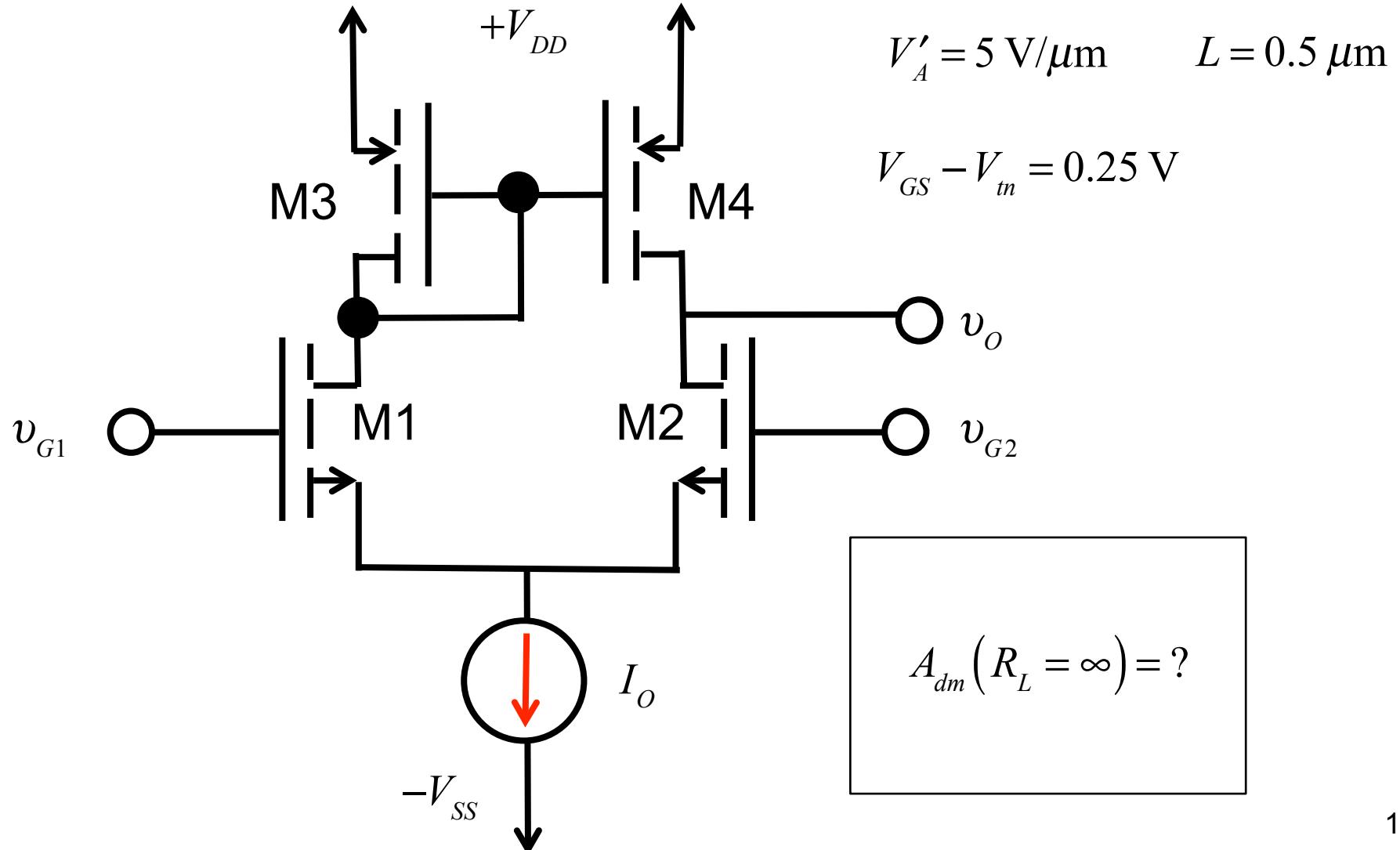

Problem 9.88

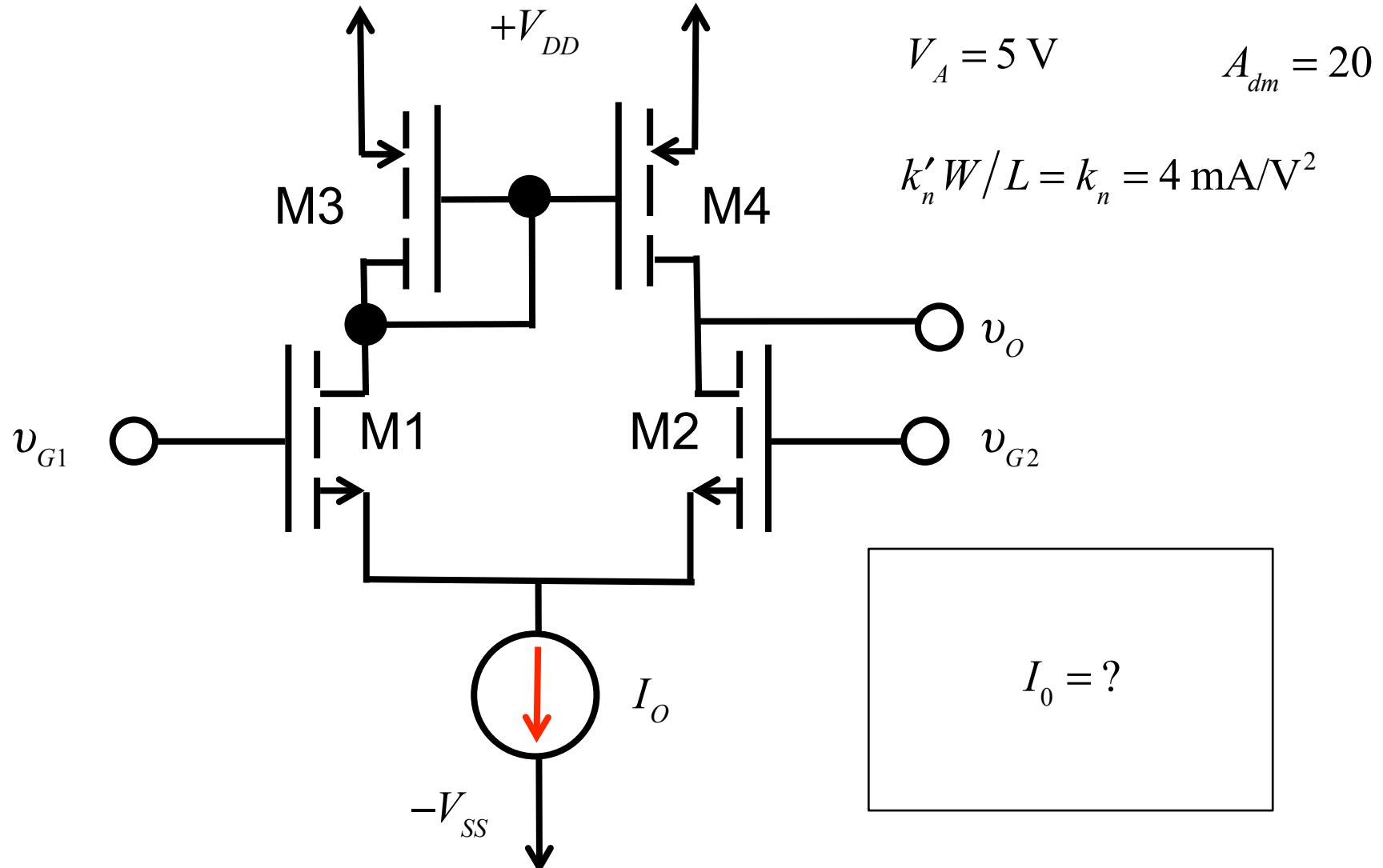

Problem 9.87

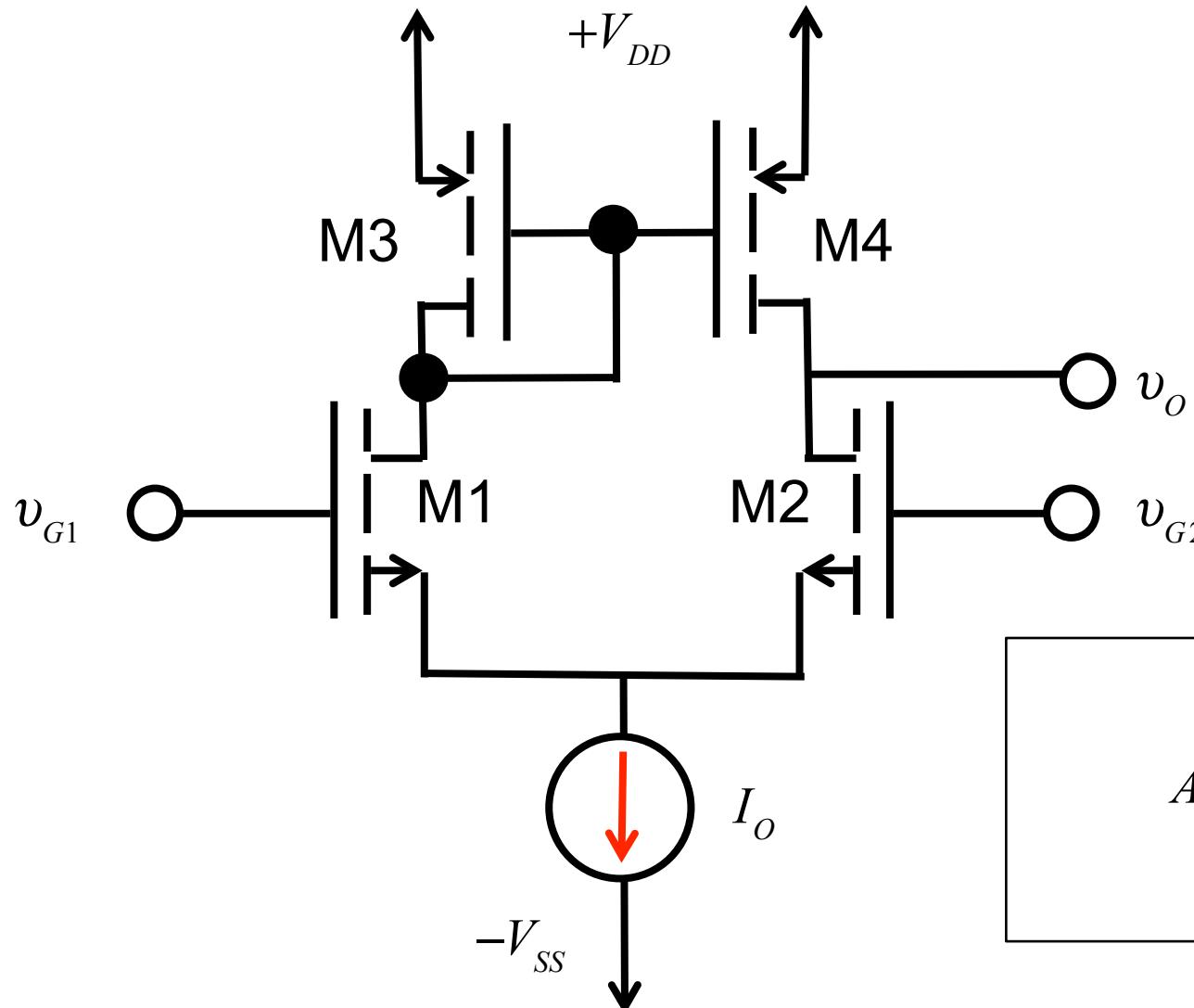

$$I_0 = 200 \mu\text{A}$$

$$W/L)_{M1} = W/L)_{M2} = 50$$


$$\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$$

$$L = 0.5 \mu\text{m}$$

$$V'_A = 5 \text{ V}/\mu\text{m}$$

$A_{dm} = ?$

Problem 9.23 (Design)

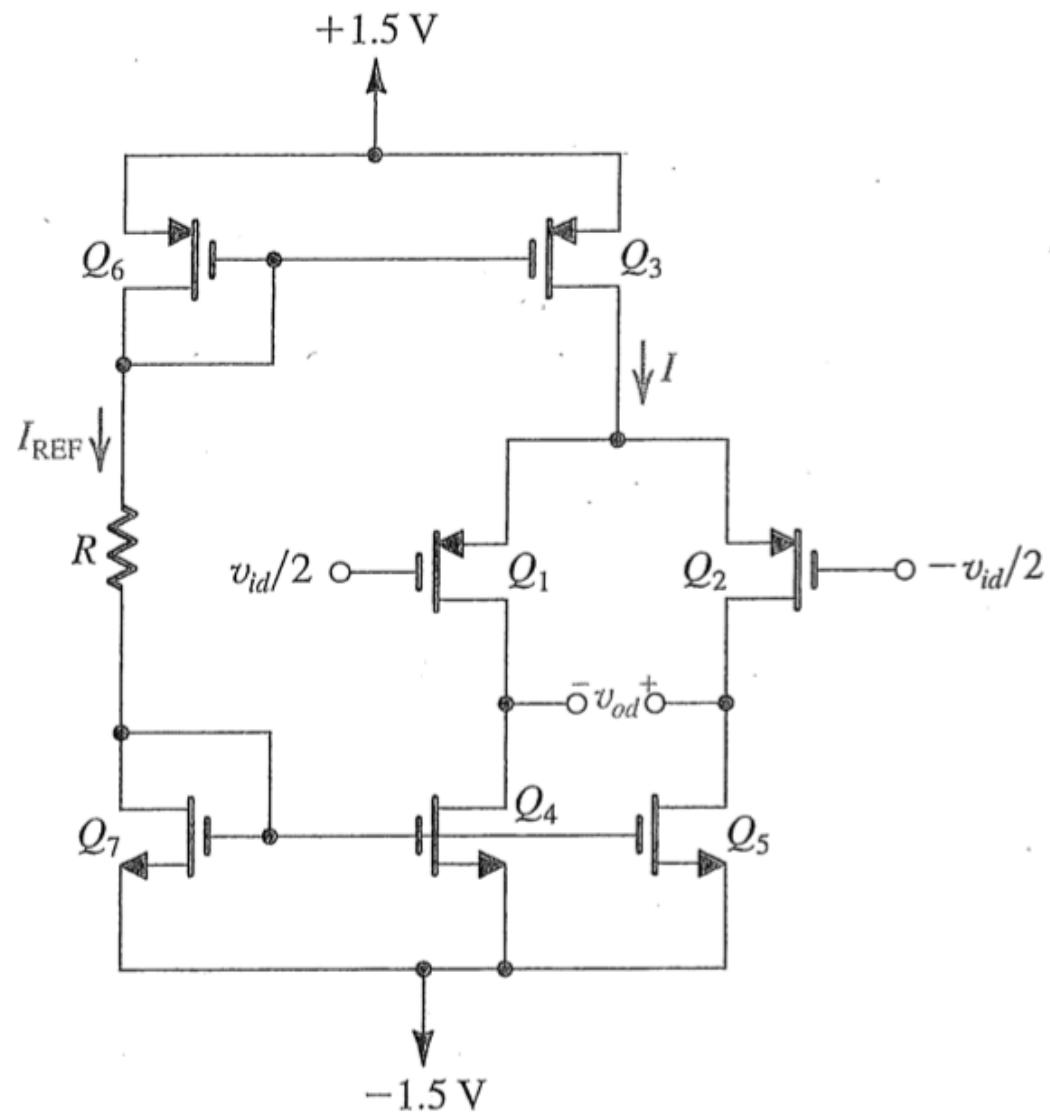

Problem 9.23 (Design)

$$I_{REF} = I = 200 \mu\text{A}$$

$$A_{dm} = 50$$

$$V_{G6} = V_{G3} = 0.8 \text{ V}$$

$$V_{G7} = V_{G4} = V_{G5} = -0.8 \text{ V}$$

$$R = ? \quad W/L = ?$$

$$I_D = ? \quad V_{GS} = ?$$

$$\mu_n C_{ox} = 2.5 \mu_p C_{ox} = 250 \mu\text{A/V}^2 \quad V_{tn} = |V_{tp}| = 0.5 \text{ V} \quad V_{An} = V_{Ap} = 10 \text{ V}$$

Problem 9.23 (Design)

$$I_{REF} = I = 200 \mu\text{A}$$

$$V_{tn} = |V_{tp}| = 0.5 \text{ V}$$

$$V_{An} = V_{Ap} = 10 \text{ V}$$

$$\begin{aligned}\mu_n C_{ox} &= 2.5 \mu_p C_{ox} \\ &= 250 \mu\text{A/V}^2\end{aligned}$$