

Spring 2019 Purdue University

ECE 255: L31

CMOS Op Amps

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA




Announcements

HW9 Due 5:00 PM Friday, April 12 in EE-209 dropbox

Outline

- 1) Review
- 2) PMOS input version
- 3) Two-Stage Op Amps (PMOS input)

CM loaded differential pair

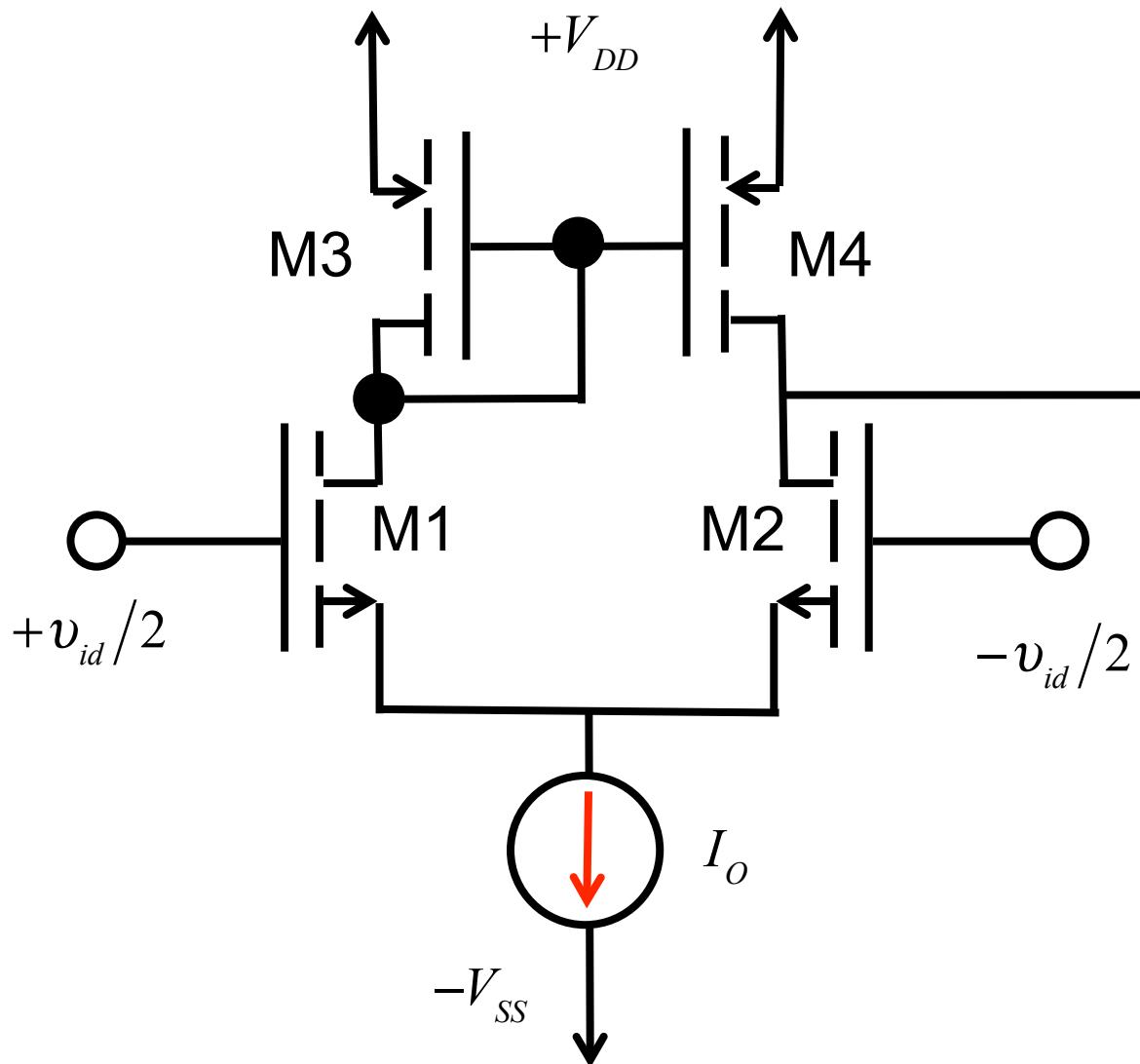


Short-circuit transconductance

$$G_m \equiv \frac{i_o}{v_{id}} = g_m$$

Output resistance


$$R_{out} = r_{o2} \parallel r_{o4}^4$$

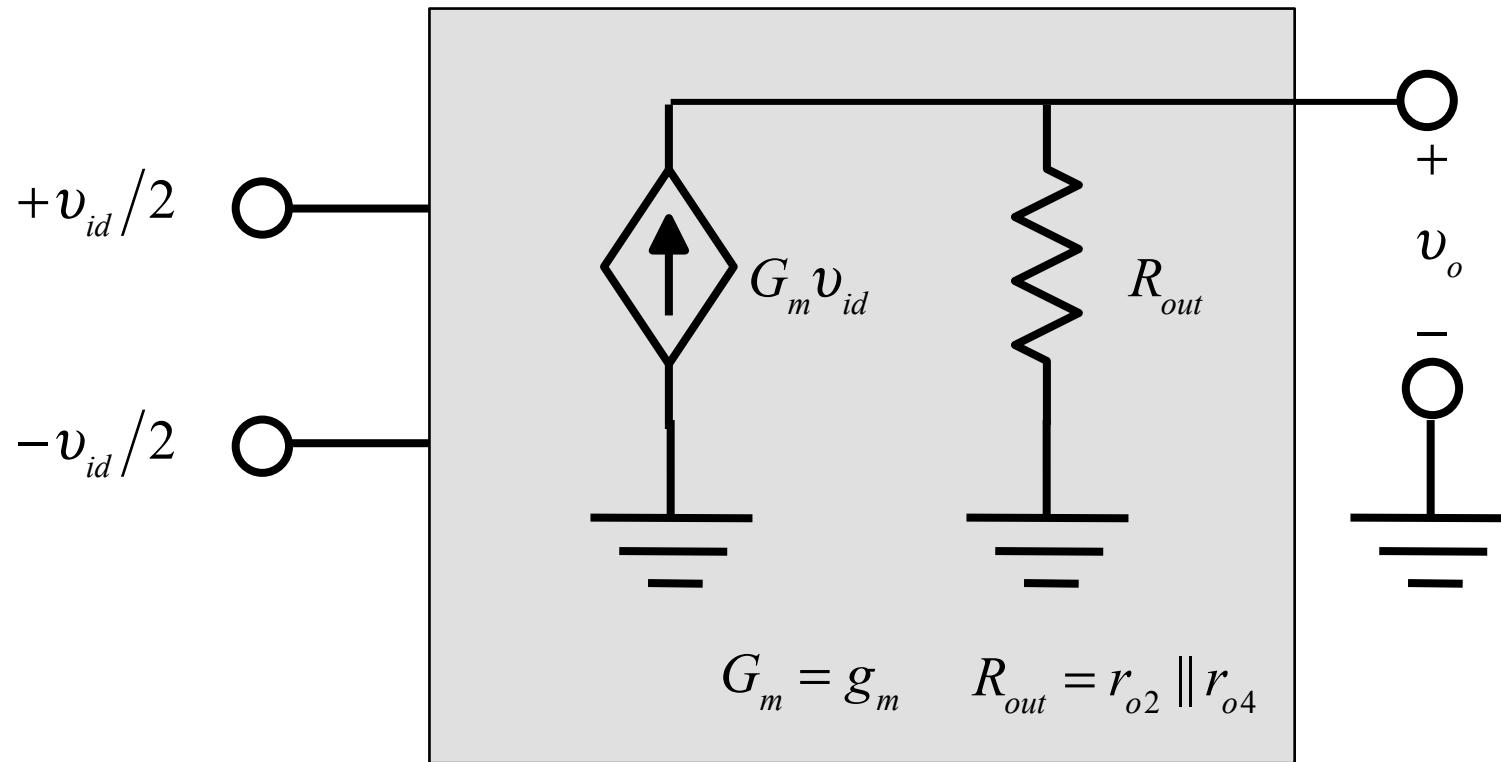CM loaded differential pair: equivalent circuit




$$v_o = G_m v_{id} R_{out} = g_m v_{id} (r_{o2} \parallel r_{o4})$$

CM loaded differential pair: With load

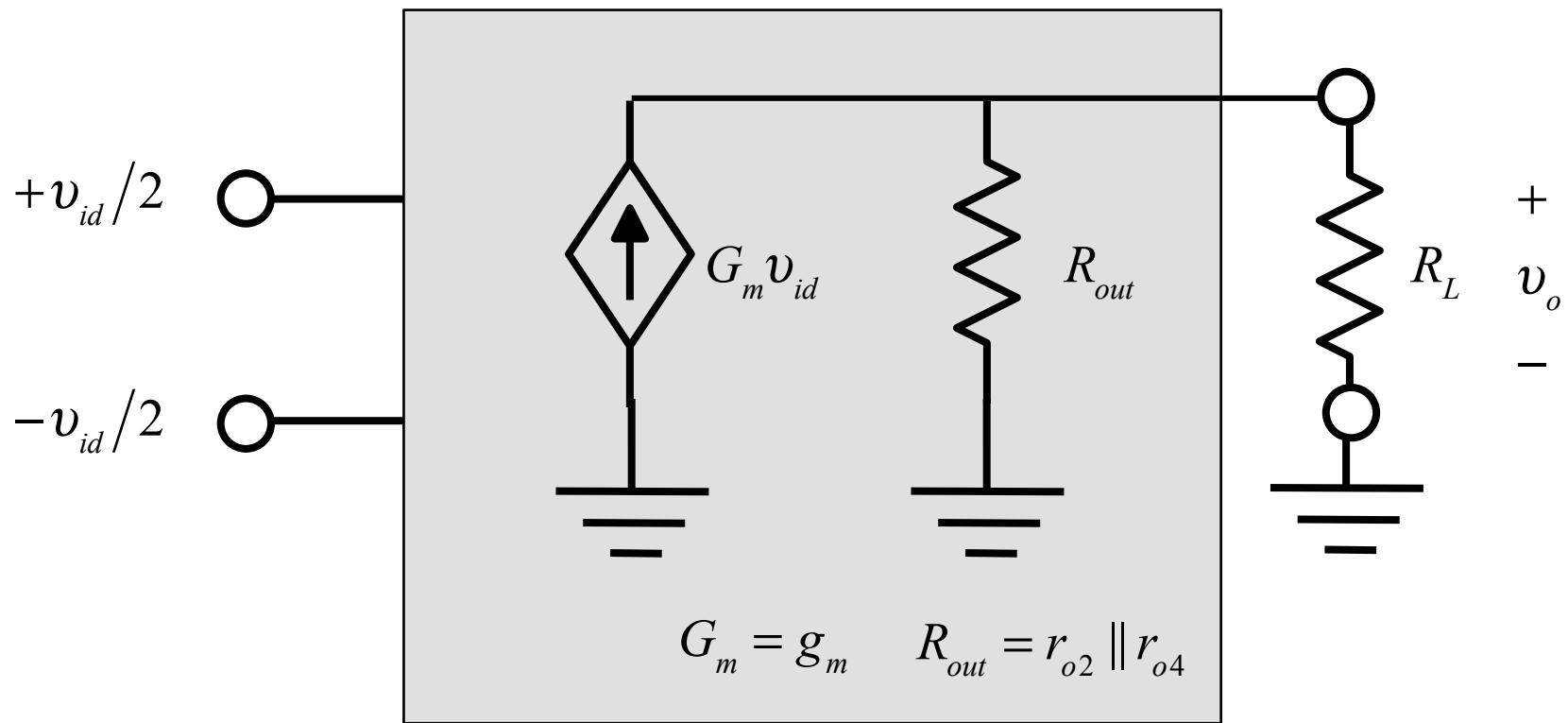


$$v_o = G_m v_{id} R_{out} \parallel R_L = g_m v_{id} (r_{o2} \parallel r_{o4}) \parallel R_L$$

CM loaded differential pair

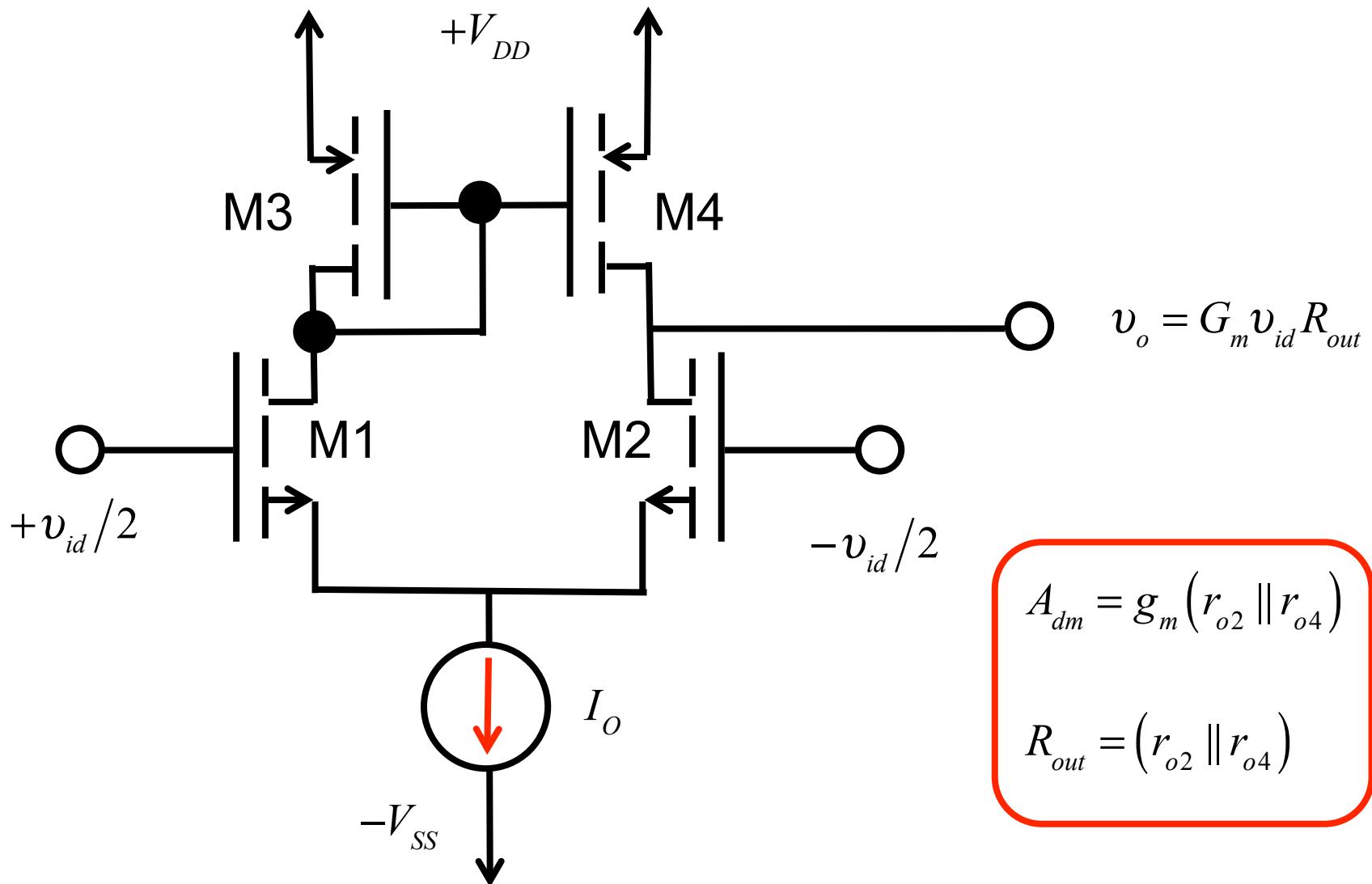


CM loaded differential pair: With load

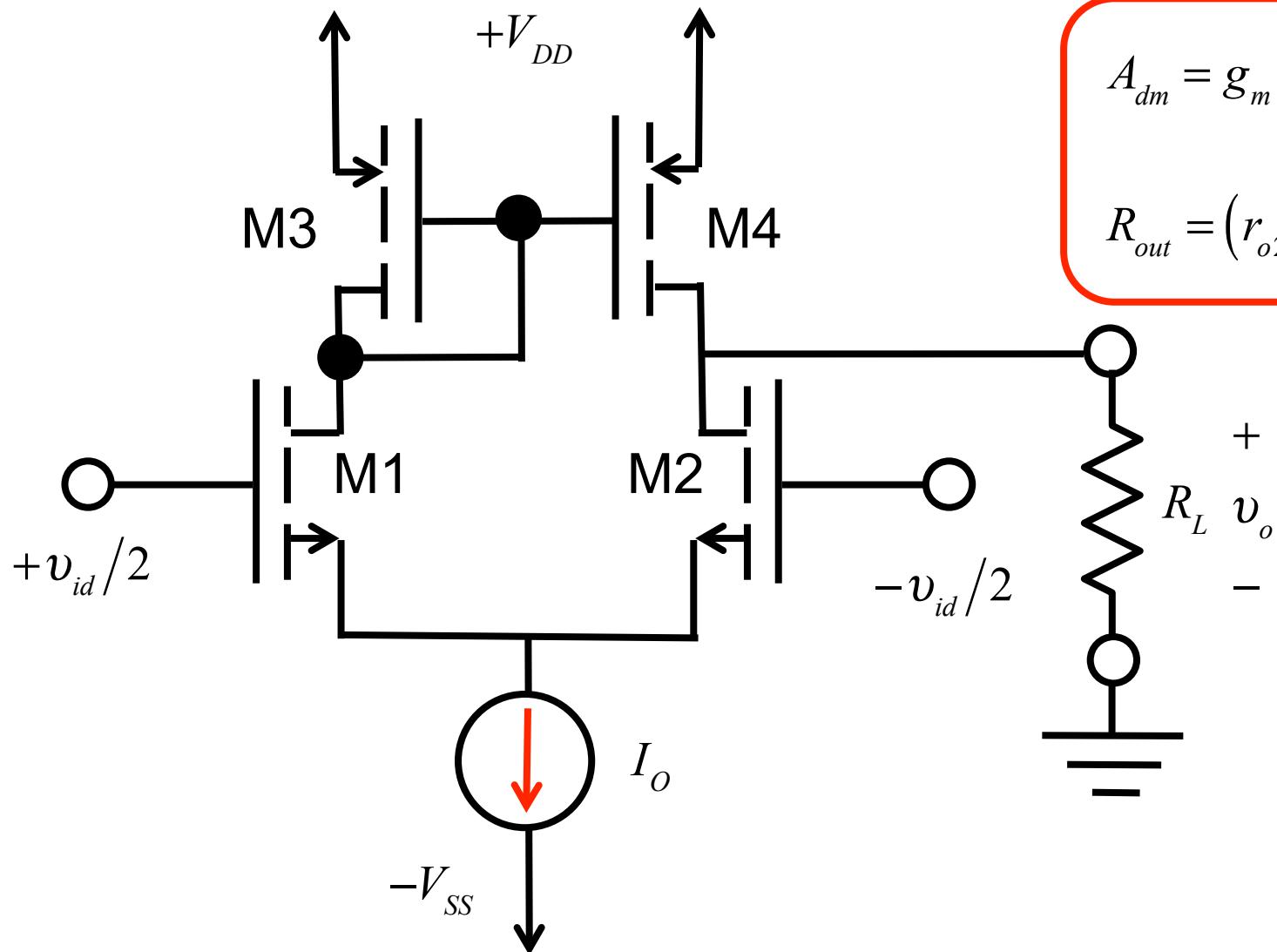


$$A_{dm} = g_m (r_{o2} \parallel r_{o4}) \parallel R_L$$

$$R_{out} = (r_{o2} \parallel r_{o4})$$


Problem 9.85

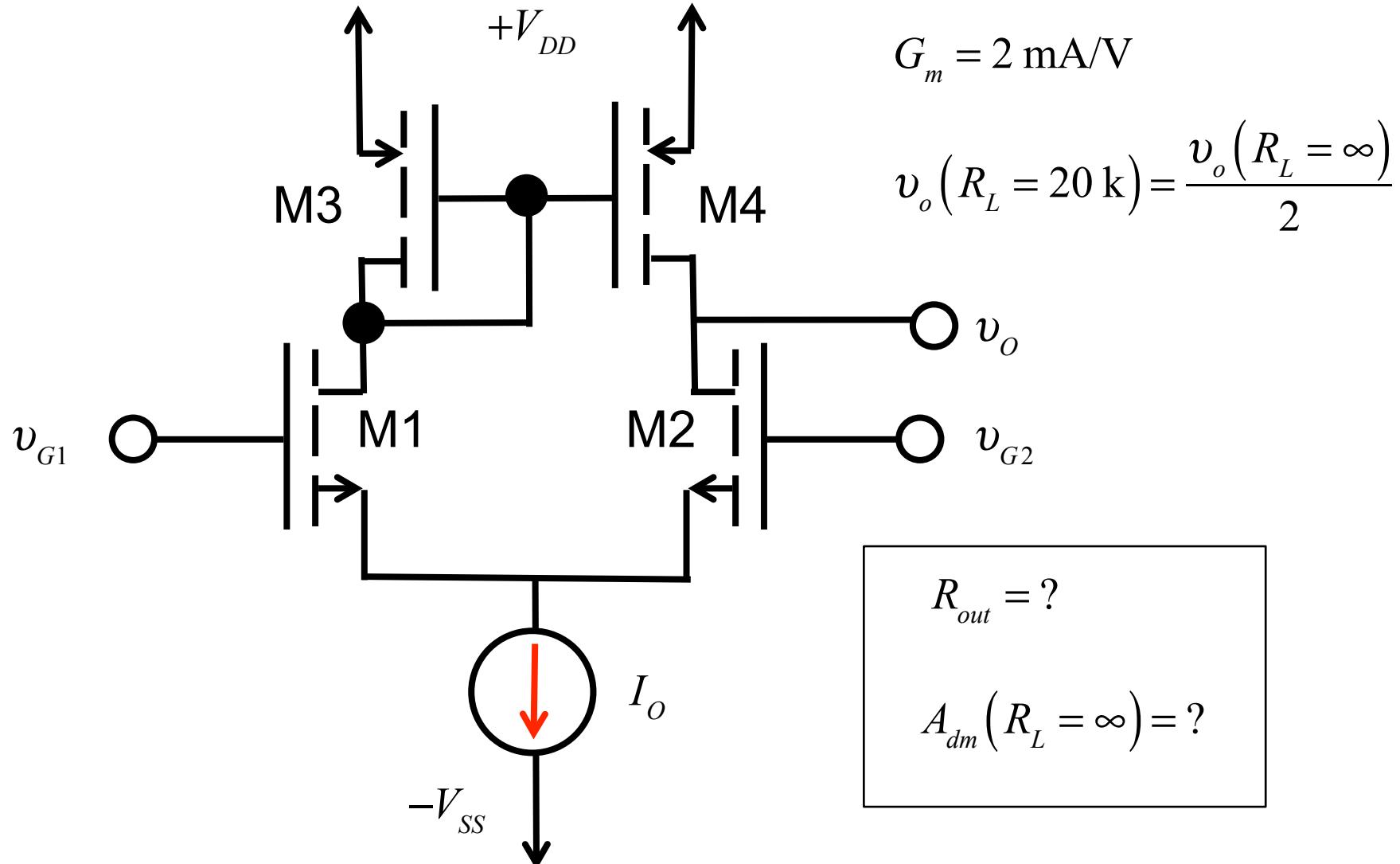


Problem 9.86

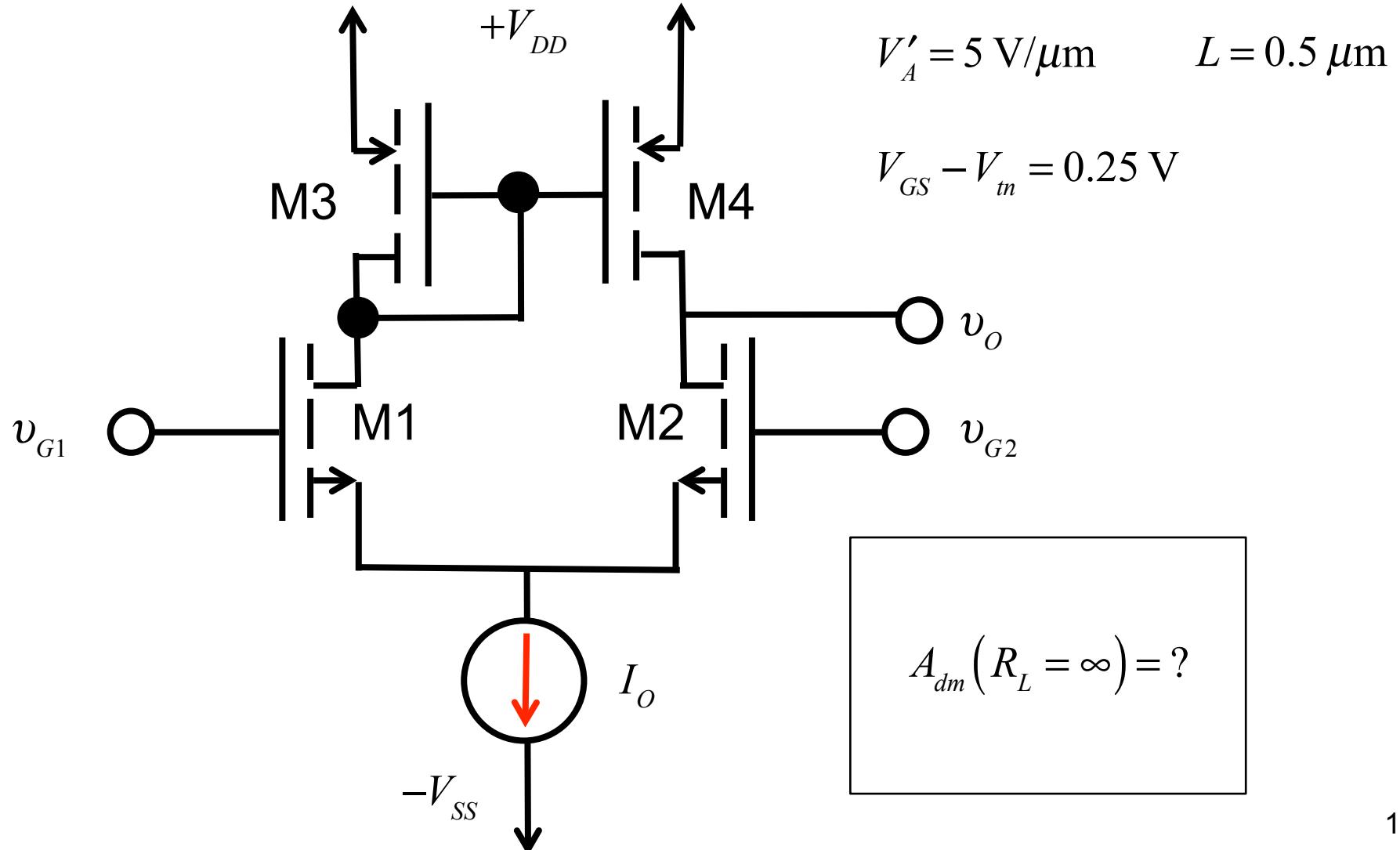

Problem 9.88

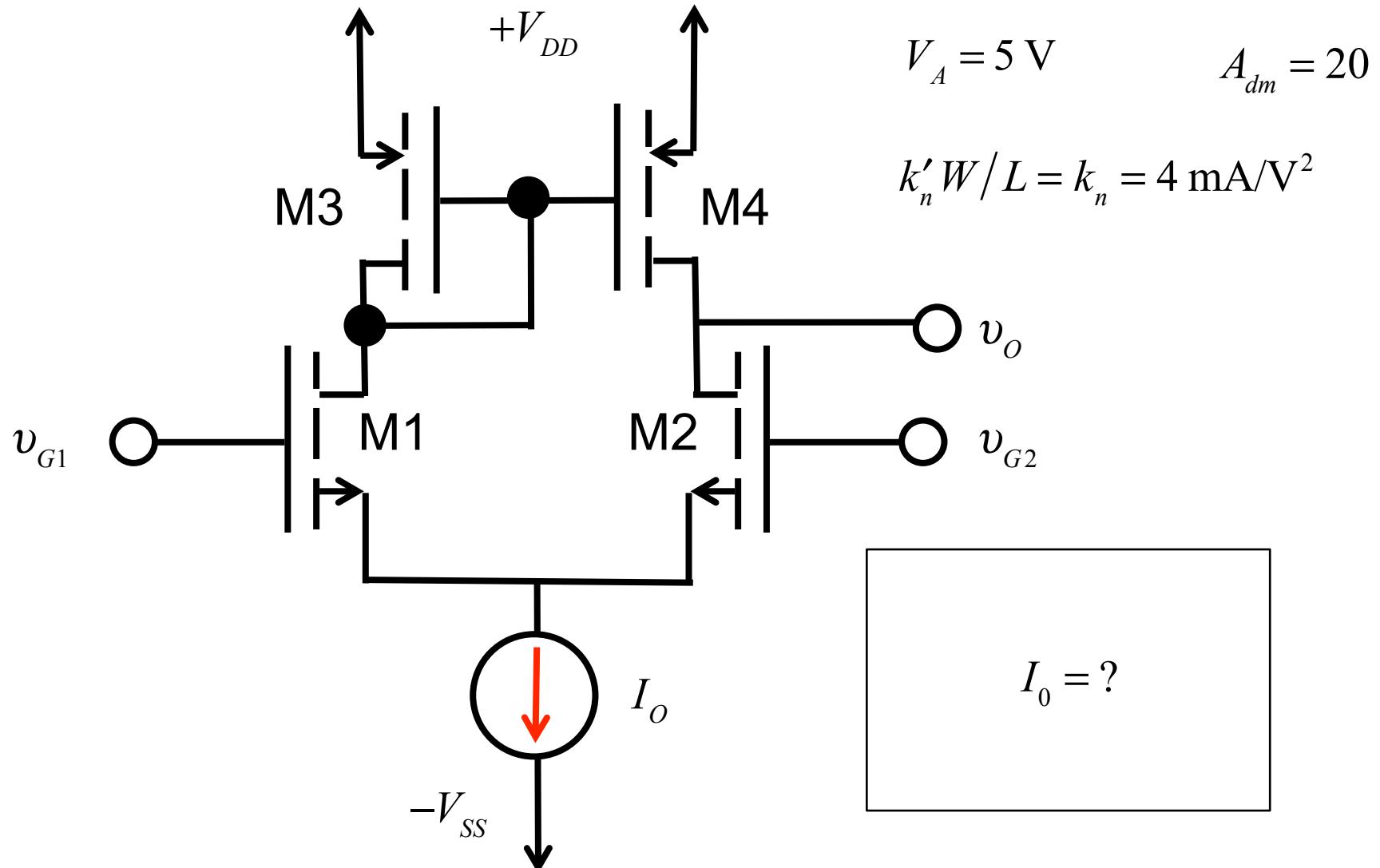

Common mode gain and CMRR

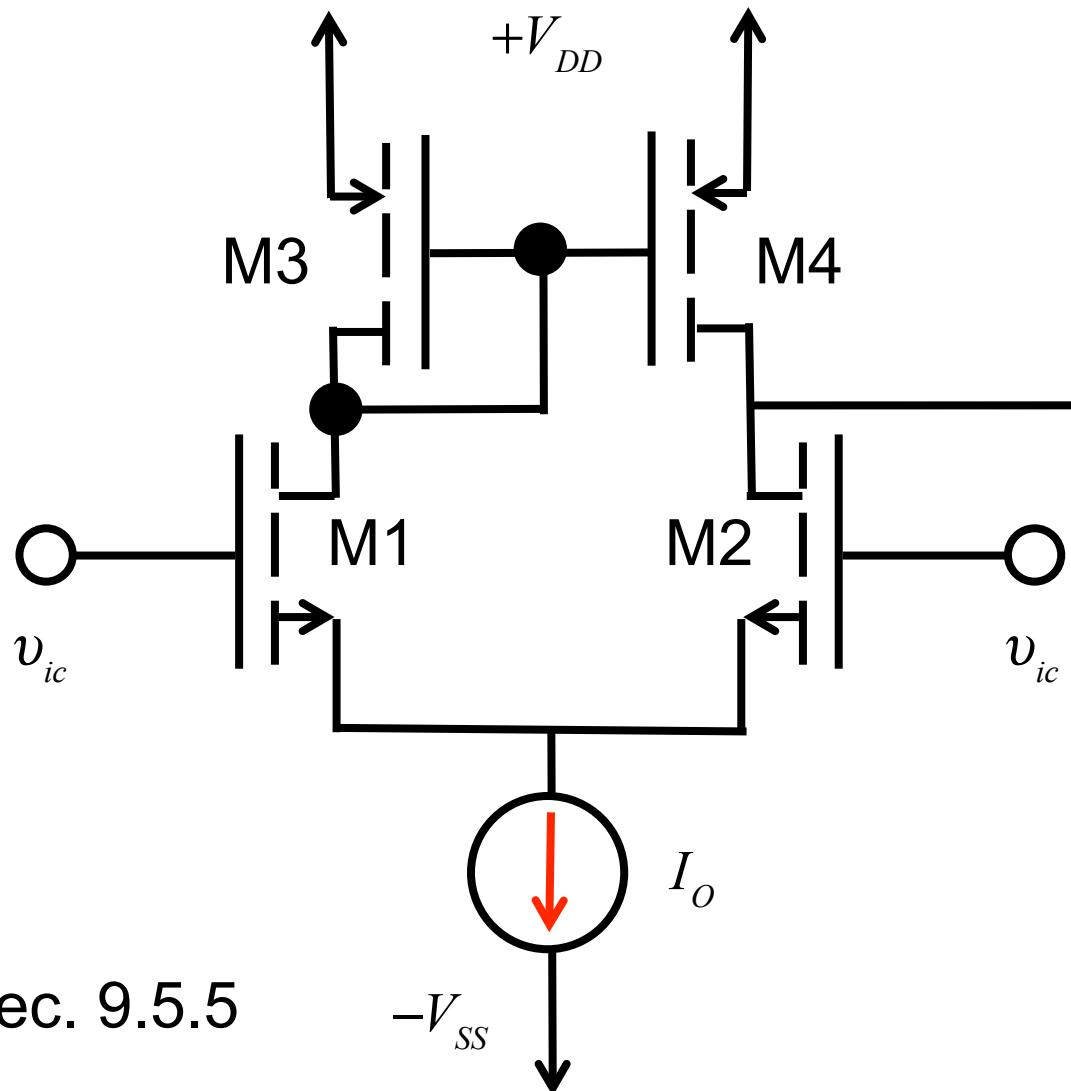

$$v_o = A_{cm} v_{ic}$$


$$A_{cm} \approx -\frac{1}{2g_m R_{SS}}$$

$$A_{dm} = g_m (r_{o2} \parallel r_{o4})$$

$$CMRR = |A_{dm}| / |A_{cm}|$$

Sec. 9.5.5

CM loaded differential pair

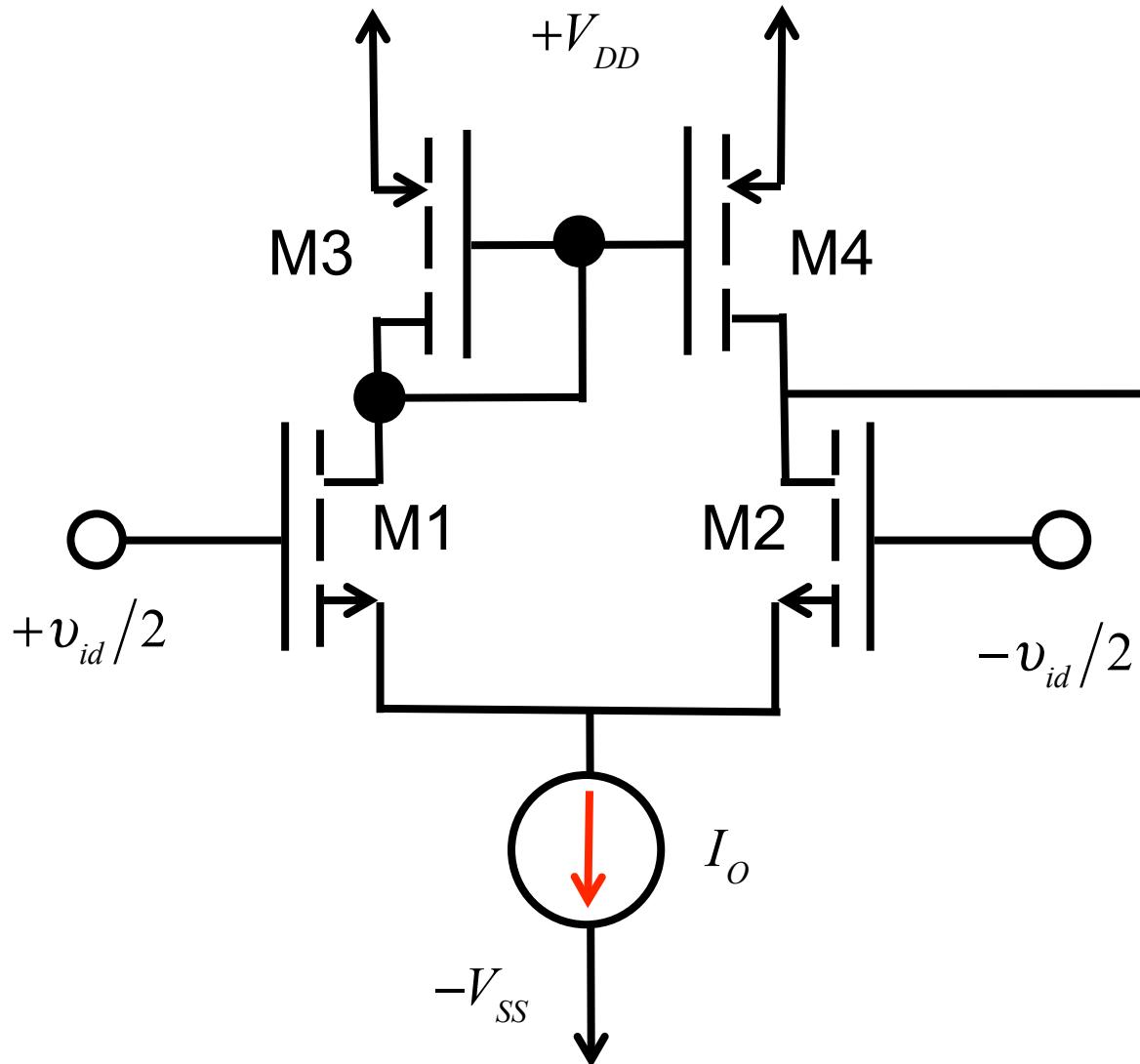

$$A_{dm} = g_m (r_{o2} \parallel r_{o4})$$

$$R_{out} = (r_{o2} \parallel r_{o4})$$


$$A_{cm} \approx -\frac{1}{2g_{m3}R_{SS}}$$

$$CMRR = |A_{dm}| / |A_{cm}|$$


Outline

- 1) Review
- 2) **PMOS input version**
- 3) Two-Stage Op Amps (PMOS input)

PMOS input differential pair

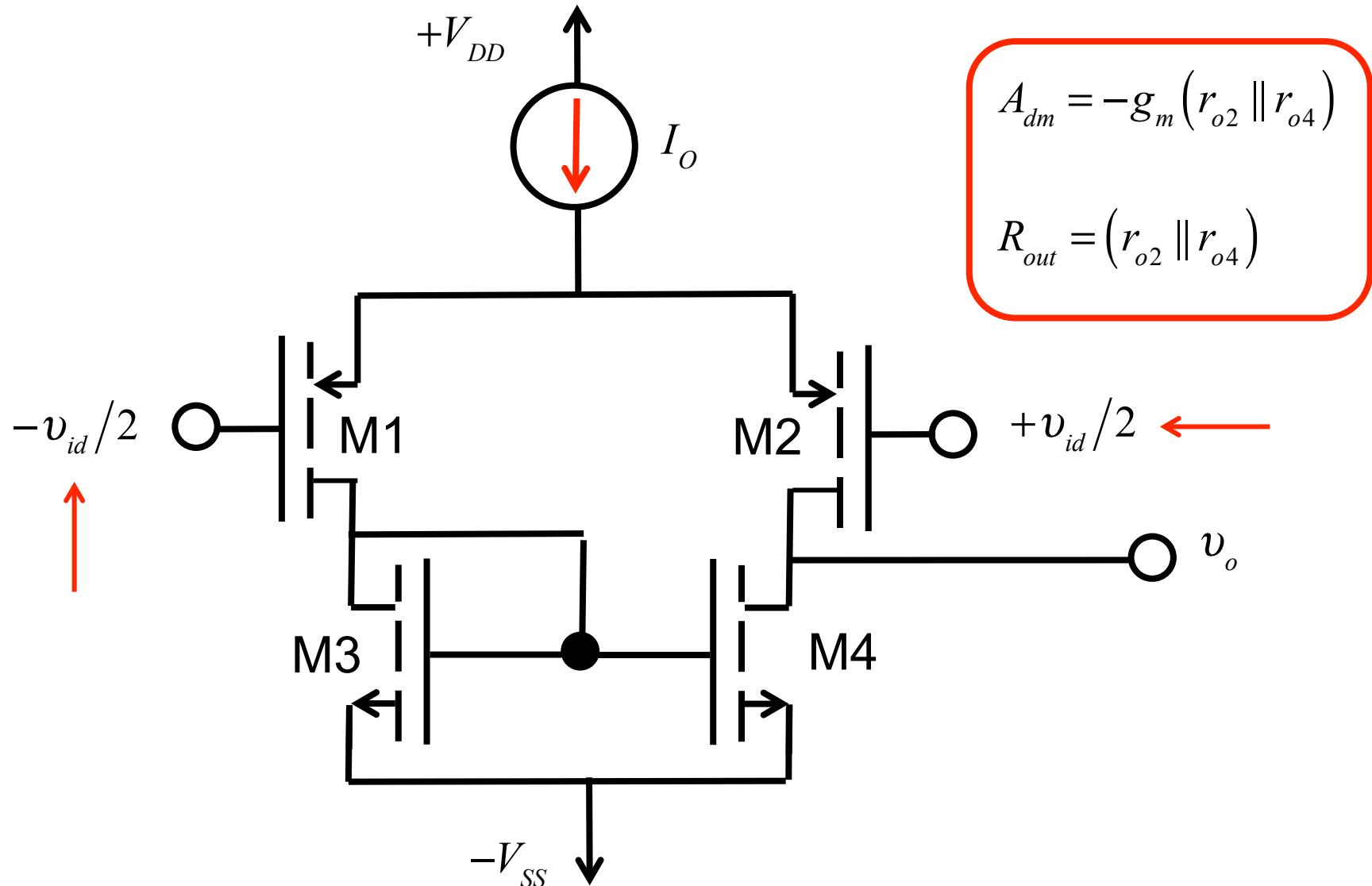

2-stage CMOS Op Amp

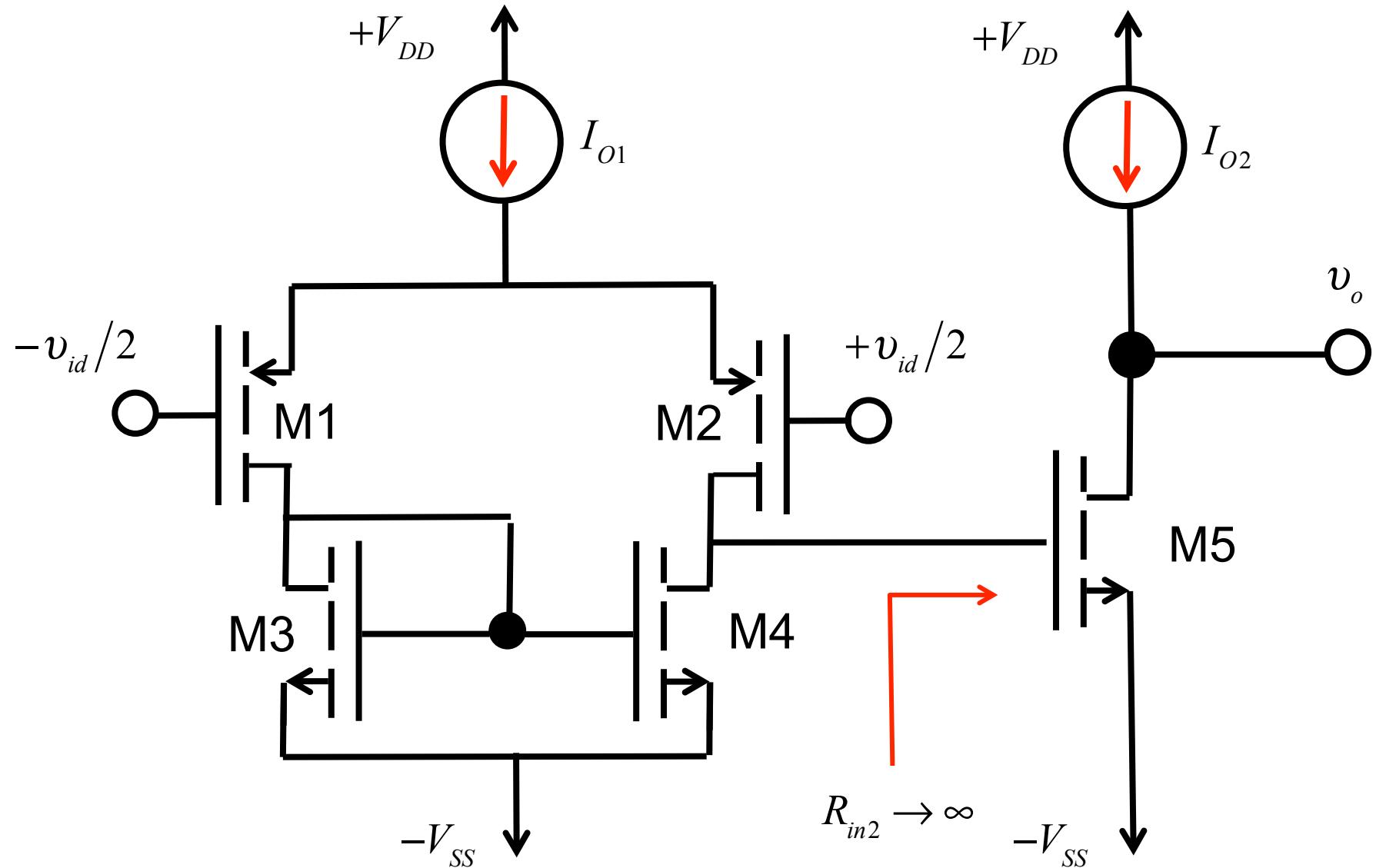

CMOS Op Amp

$$A_{dm} = A_{dm1} \times A_{CS}$$

$$A_{dm} = -g_m (r_{o2} \| r_{o4}) \times [-g_{m5} (r_{o5} \| R_{ocs})]$$

$$A_{cm} = A_{cm1} \times A_{CS}$$

$$A_{cm} \approx -\frac{1}{2g_{m3}R_{SS}} \times [-g_{m5} (r_{o5} \| R_{ocs})]$$

$$CMRR = \frac{|A_{dm}|}{|A_{cm}|}$$

Two-stage CMOS Op Amp


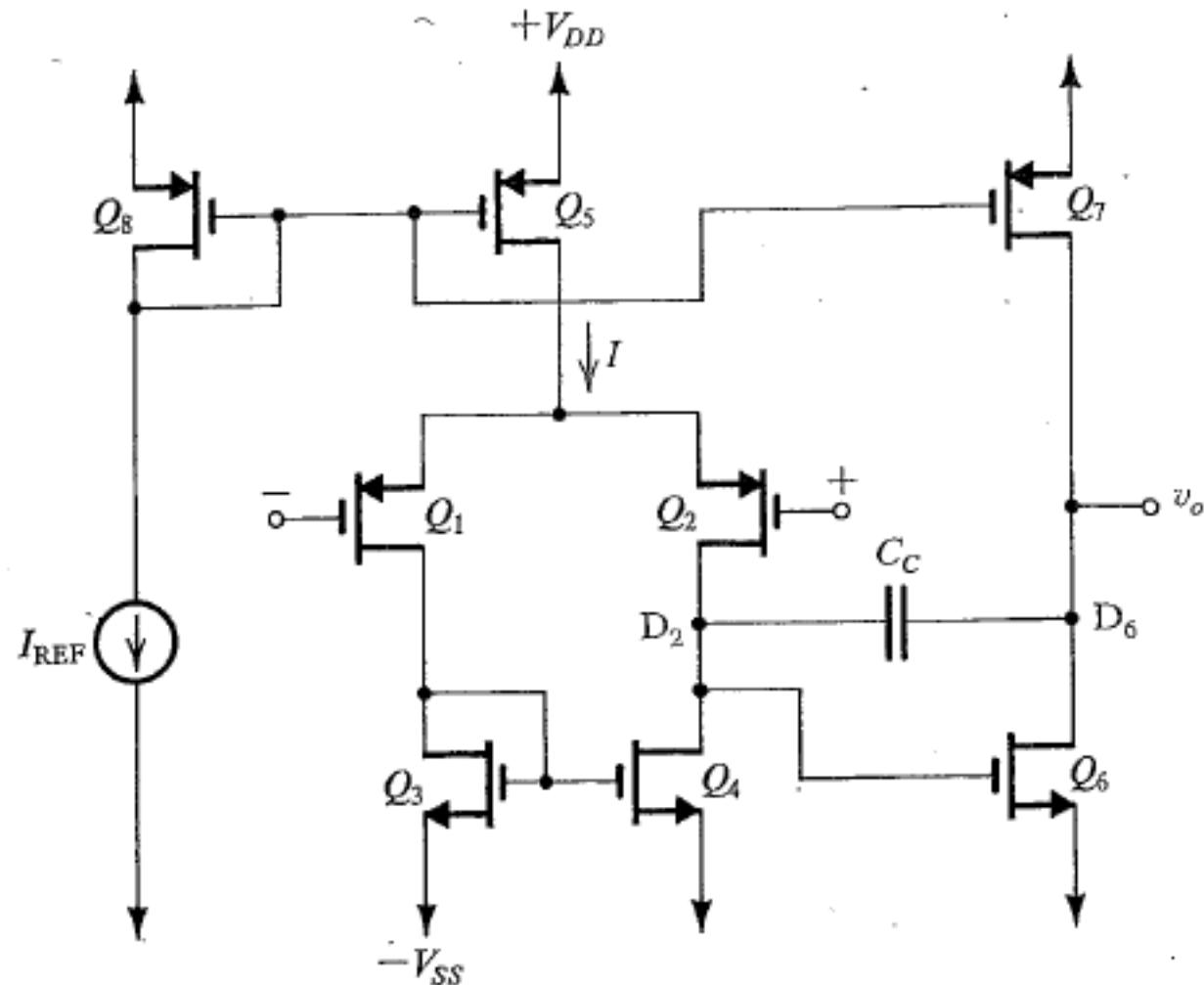


Fig. 9.40 Sedra and Smith 7th Ed.

Two-stage CMOS Op Amp

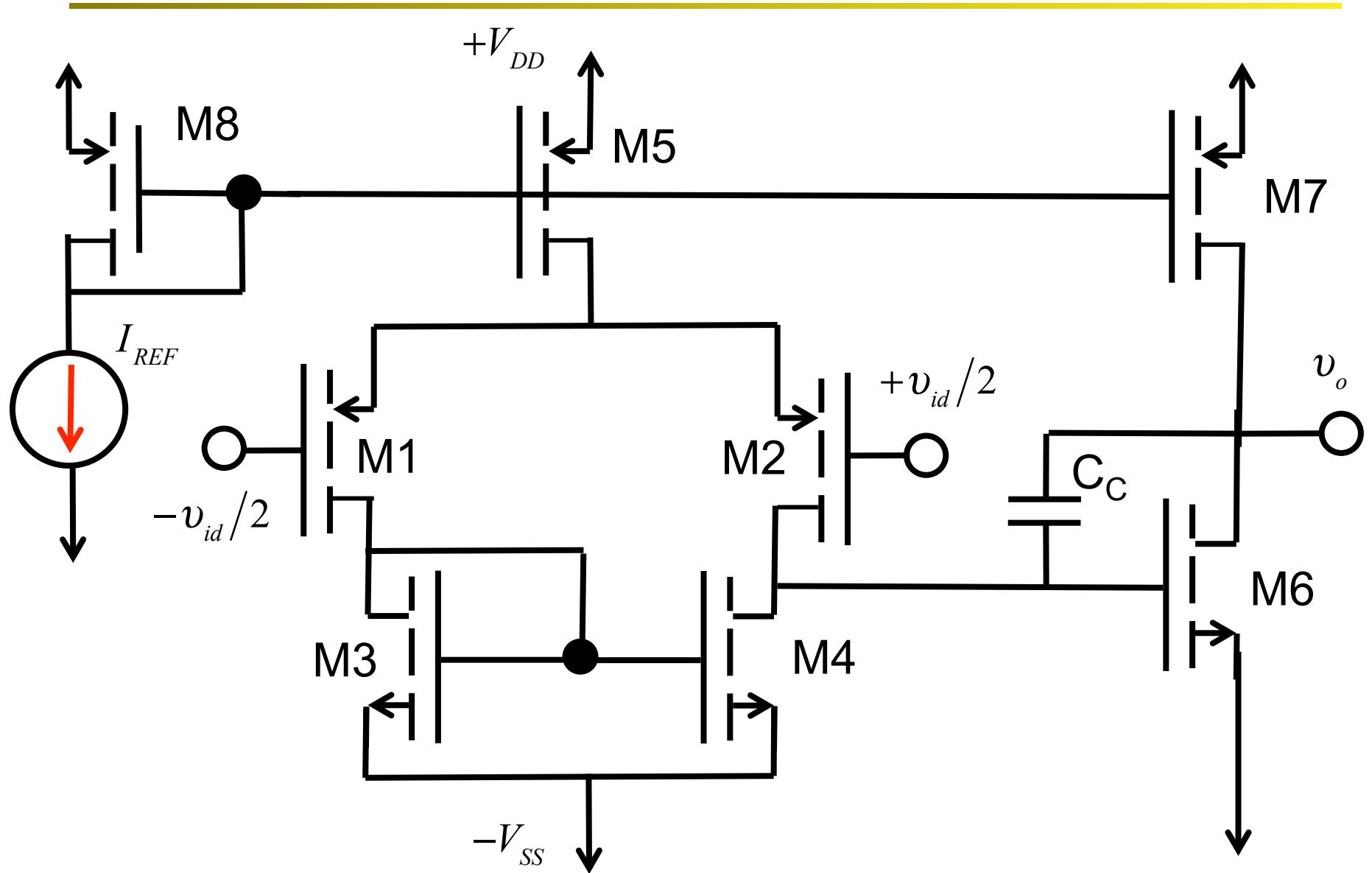

Two-stage CMOS Op Amp


$$A_{dm} = A_{dm1} \times A_{CS}$$

$$A_{dm} = -g_m (r_{o2} \| r_{o4}) \times [-g_{m6} (r_{o6} \| r_{o7})] = \left(\frac{g_m r_o}{2} \right)^2$$


$$A_{dm} = \left(\frac{g_m r_o}{2} \right)^2$$

$$R_{out} = \left(\frac{r_o}{2} \right)$$


Two-stage CMOS Op Amp: DC coupling

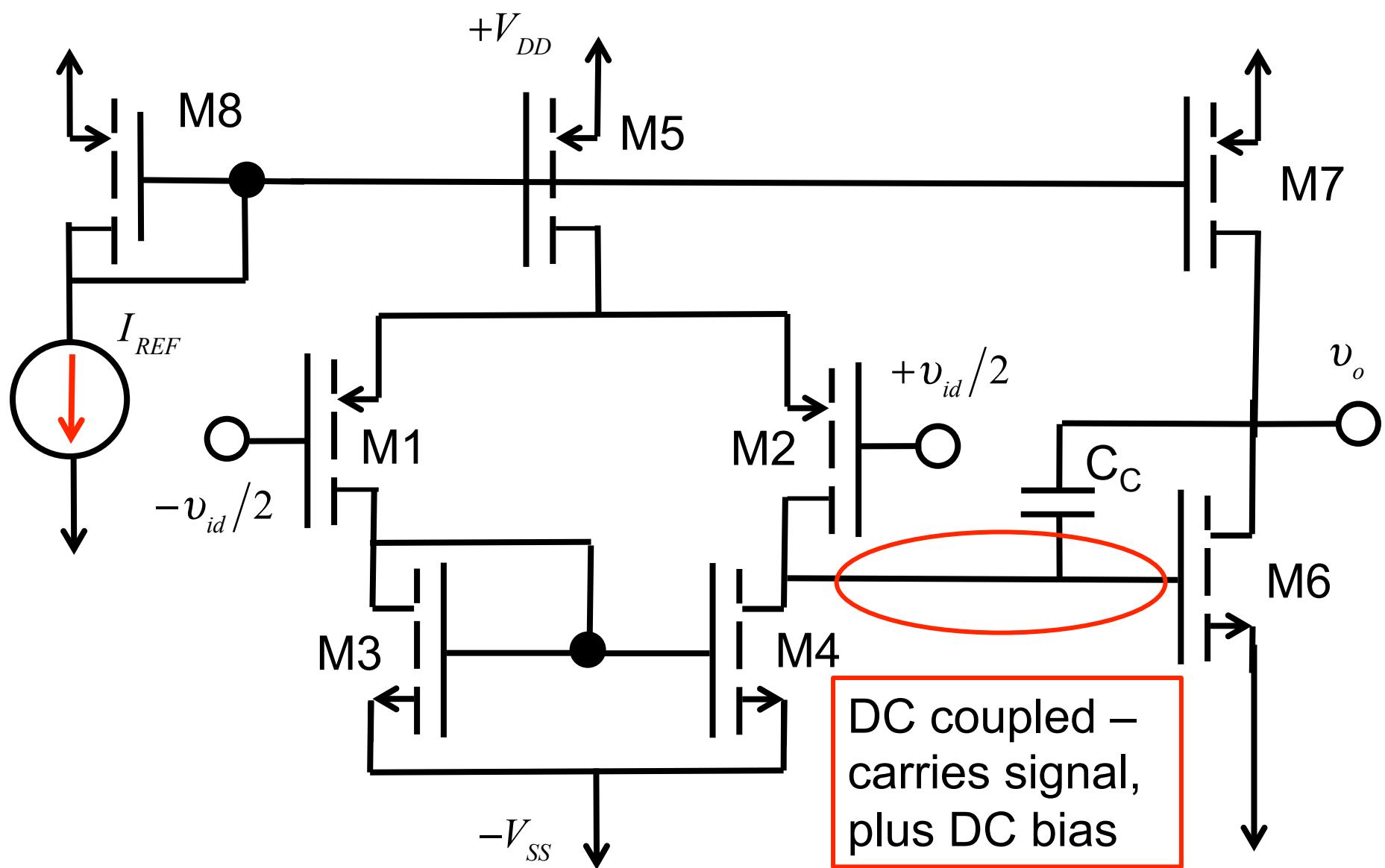

Input offset voltage

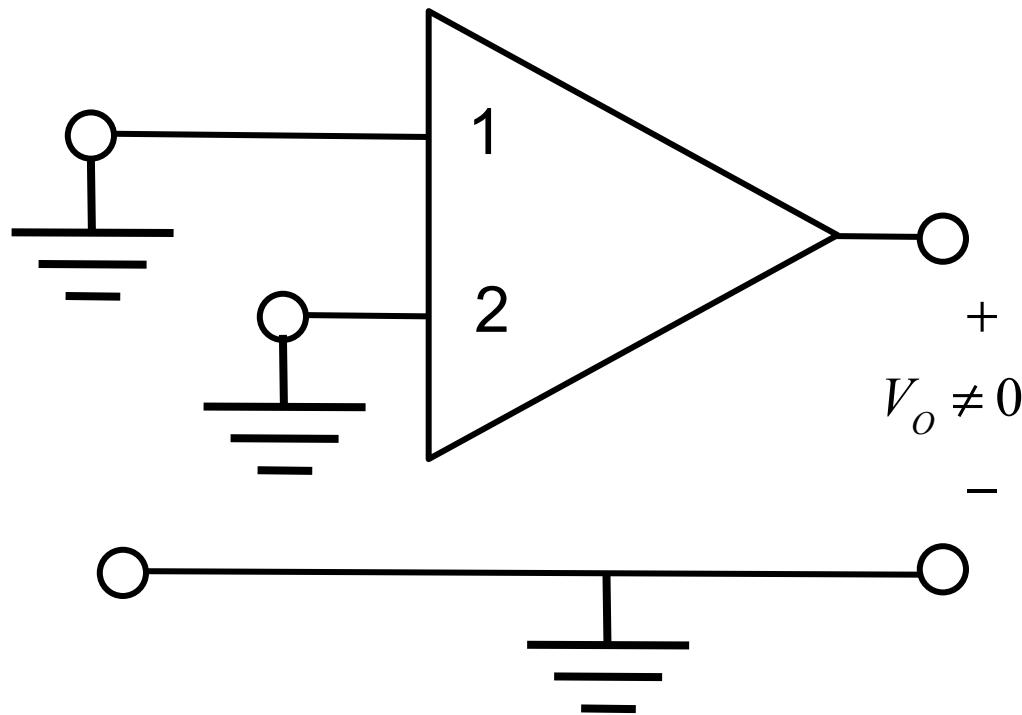


Input offset voltage

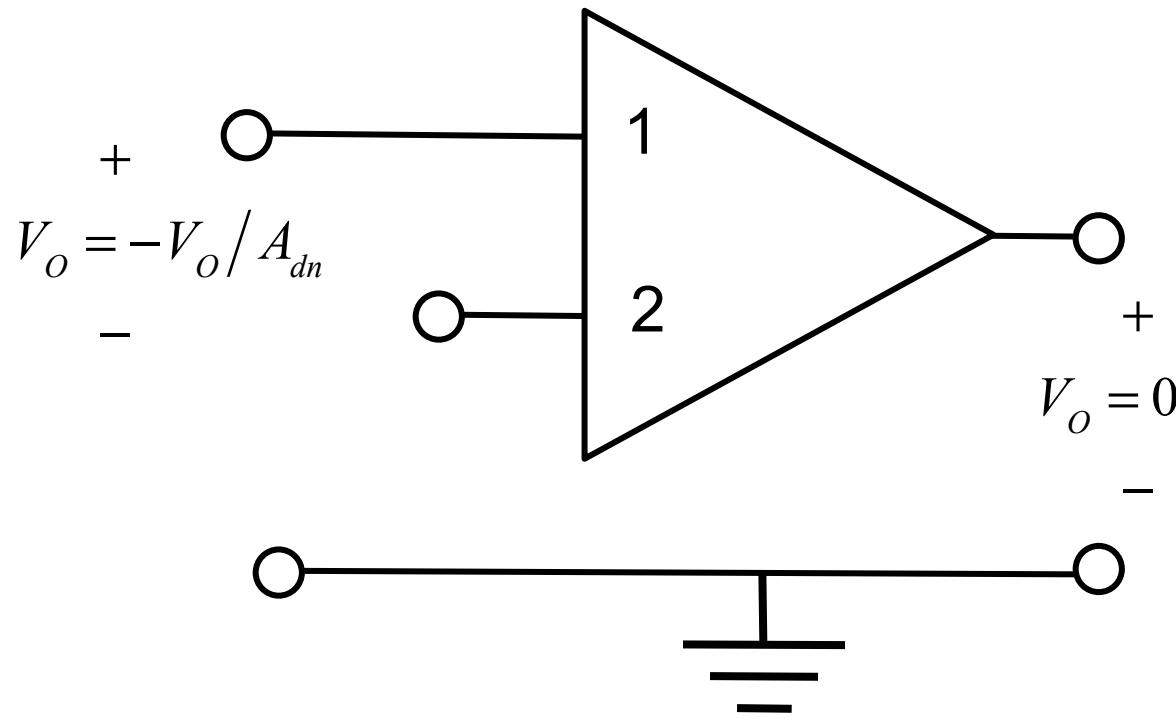


“random offset” and “systematic offset”

See Sec. 9.6.1 eqn. (9.172)


Two-stage CMOS Op Amp: DC coupling

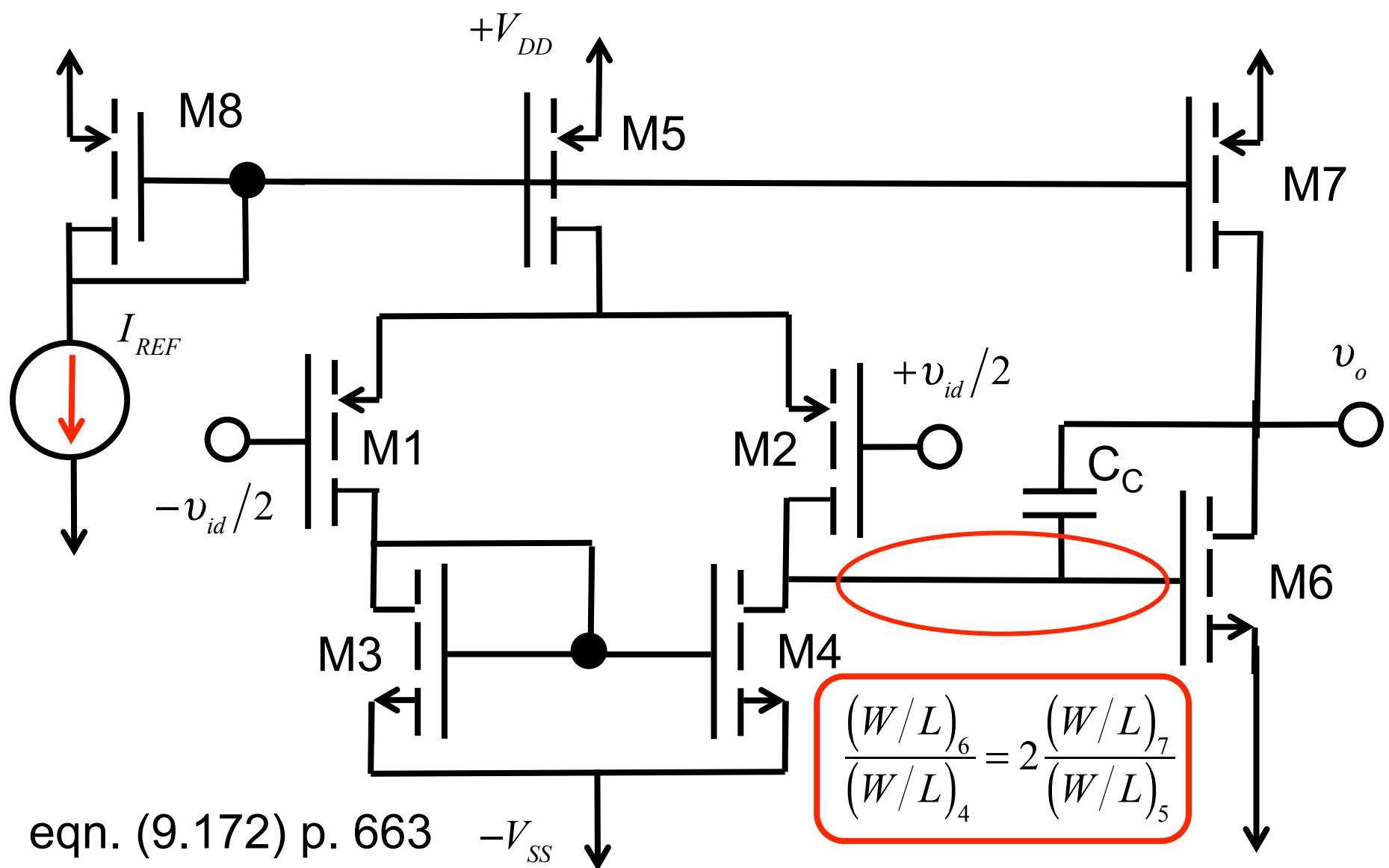

Two-stage CMOS Op Amp: Capacitor

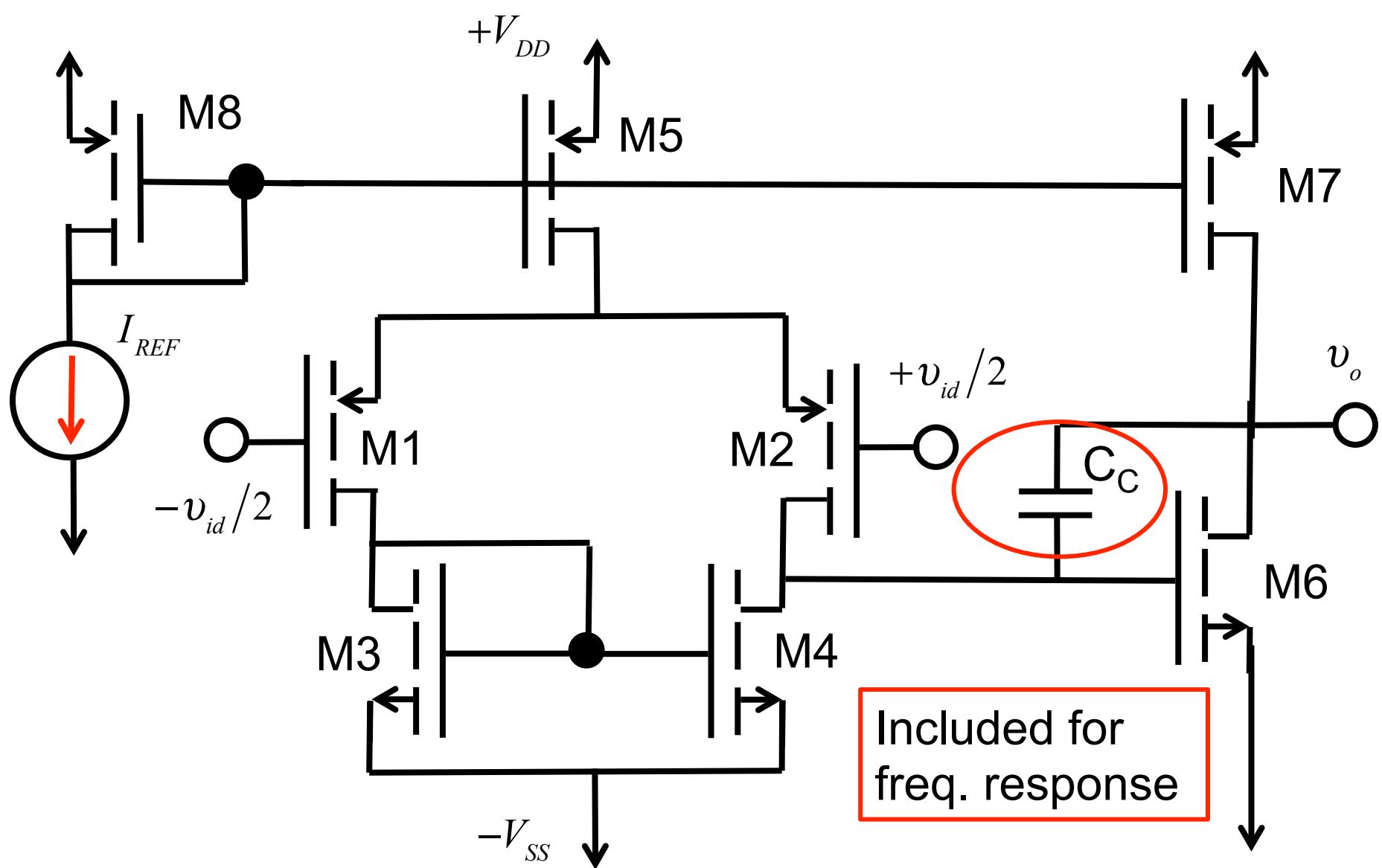

Two-stage CMOS Op Amp: Summary

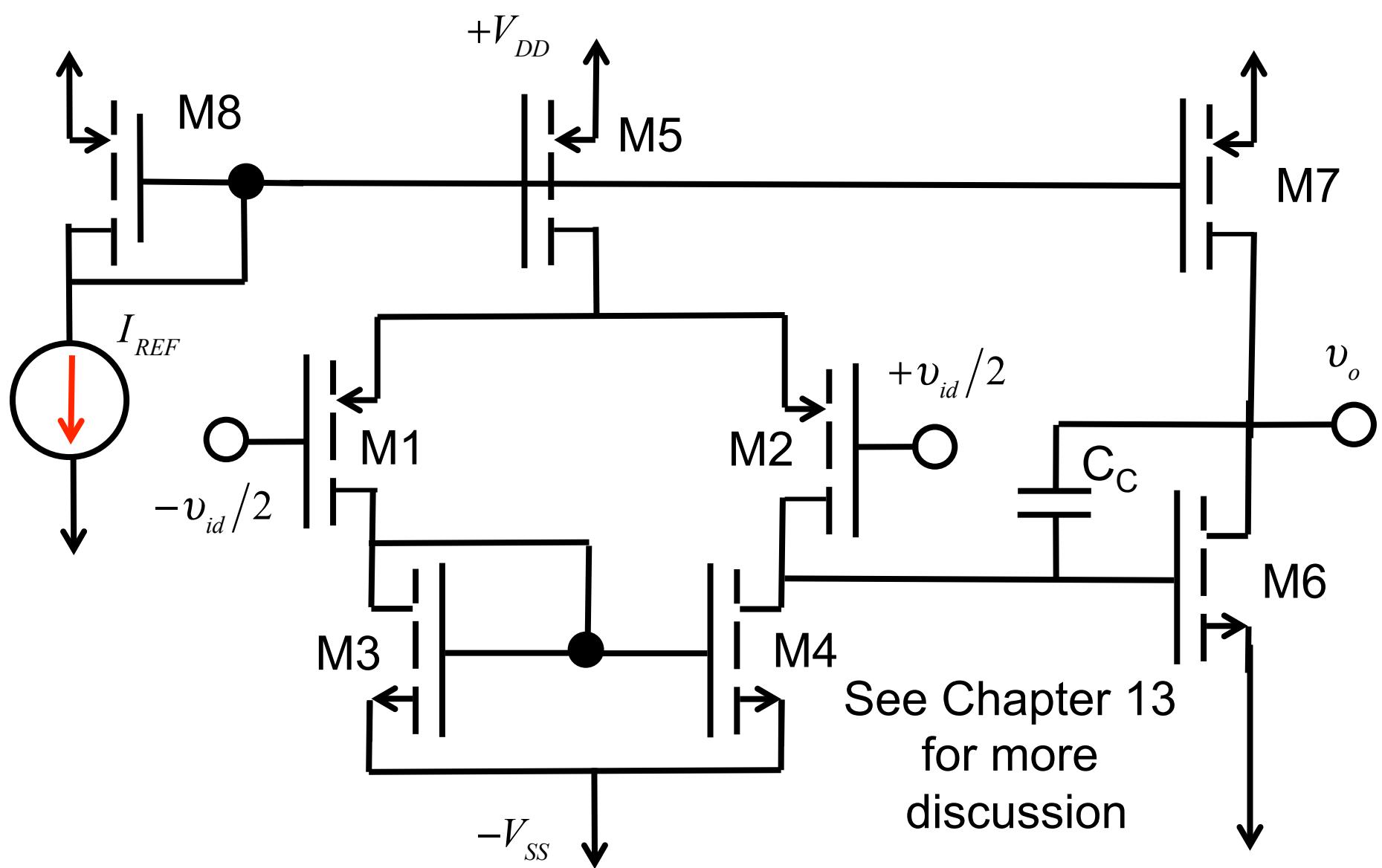

Two-stage CMOS Op Amp

You are encouraged to read through Example 9.6,
pp. 661, 662

Two-stage CMOS Op Amp: Summary


$$A_{dm} = \left(\frac{g_m r_o}{2} \right)^2 \quad 1000's \text{ but not millions}$$

$$R_{out} = \left(\frac{r_o}{2} \right) \quad \text{relatively large, suitable for driving MOS ckts.}$$

DC coupled – works all the way to DC

General purpose op amp requires more gain and a low output resistance.

741 Op Amp

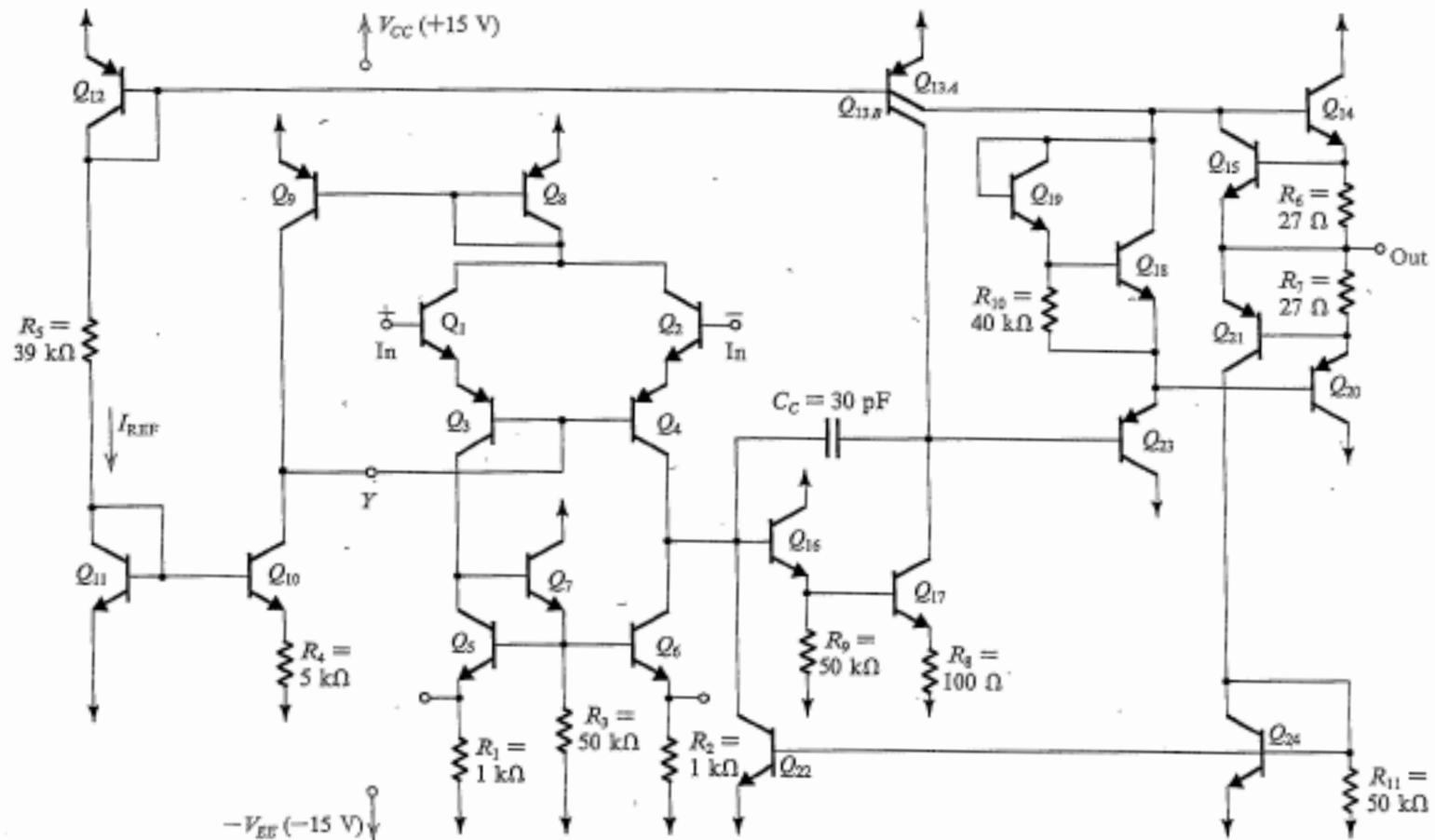

Sedra and Smith, Section 13.3, 7th Ed.

LTS spice Project 3

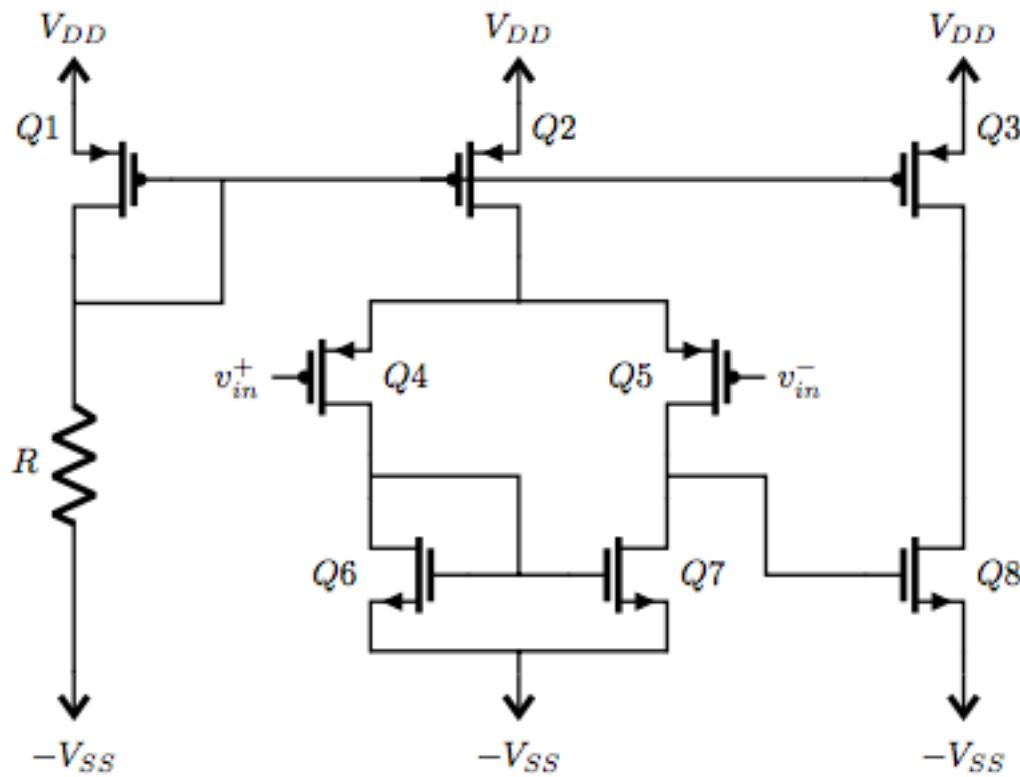


Fig.2 - Two-stage CMOS Amplifier