

Spring 2019 Purdue University

ECE 255: L32

Low Frequency Response

(Sedra and Smith, 7th Ed., Sec. 10.1)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA

Lundstrom: 2019

PURDUE
UNIVERSITY

Announcements


HW10 Due 5:00 PM Friday, April 19 in EE-209 dropbox

LTS spice Project III Due 5:00 PM Wed, April 17

Outline

- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix

Bode plot

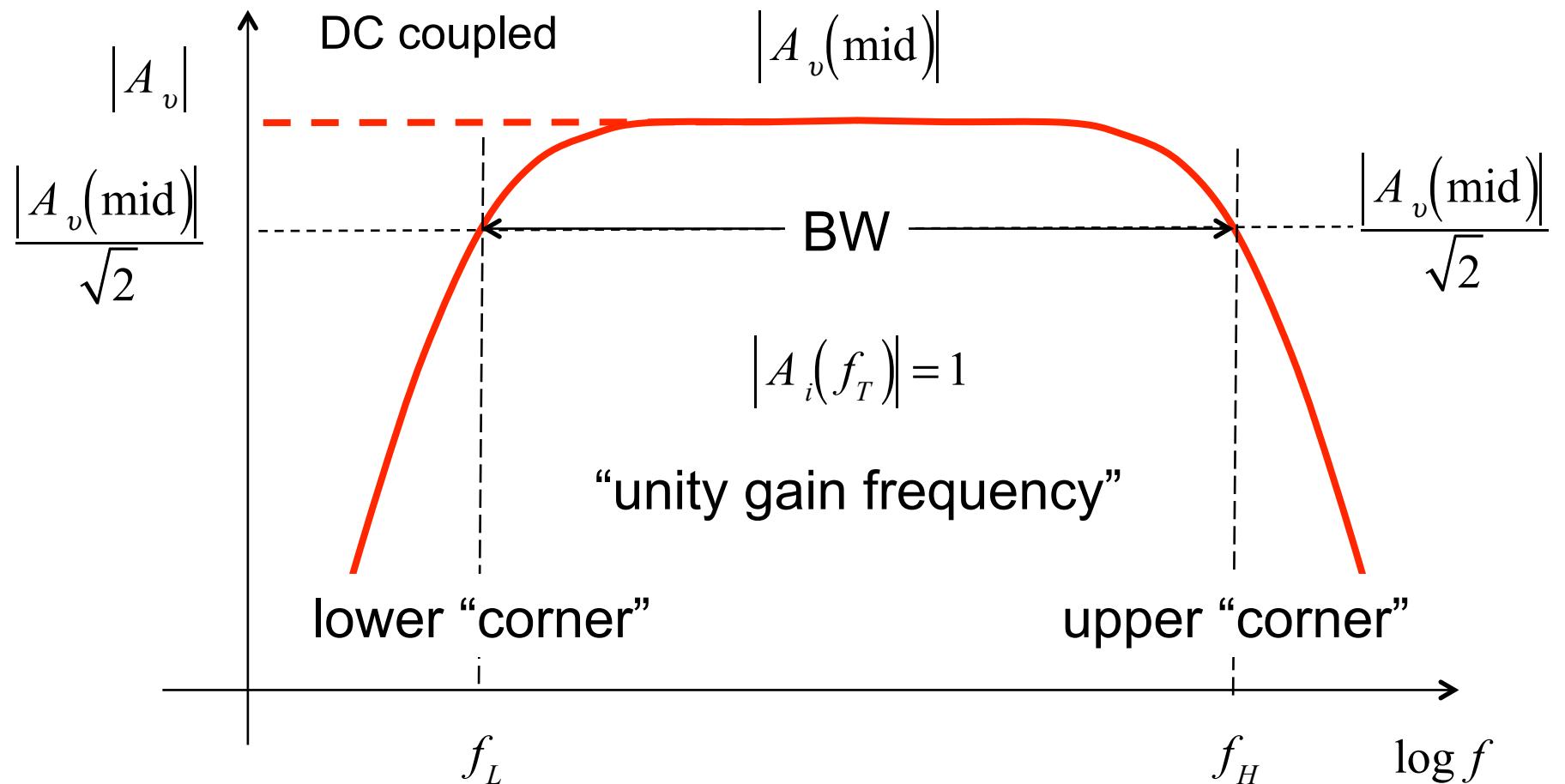

Decibels

Power

$$A_p = \frac{P_{out}}{P_{in}} = \frac{v_o i_o}{v_i i_i} = \frac{v_o v_o / R_L}{v_i v_i / R_{in}} = \left(\frac{v_o}{v_i} \right)^2 \frac{R_{in}}{R_L}$$

$$A_p|_{dB} = 10 \log_{10} \left(\frac{P_{out}}{P_{in}} \right)$$

Voltage

$$A_v = \frac{v_o}{v_i}$$


$$A_p|_{dB} = 20 \log_{10} \left(\frac{v_o}{v_i} \right)$$

Ap	Ap (dB)
0.01	-20 dB
0.1	-10 dB
0.5	-3 dB
1	0 dB
10	10 dB
100	20 dB

Lundstrom: 2019

Av	Av (dB)
0.01	-40 dB
0.1	-20 dB
1/sqrt(2)	-3 dB
1	0 dB
10	20 dB
100	40 dB

Bode plot

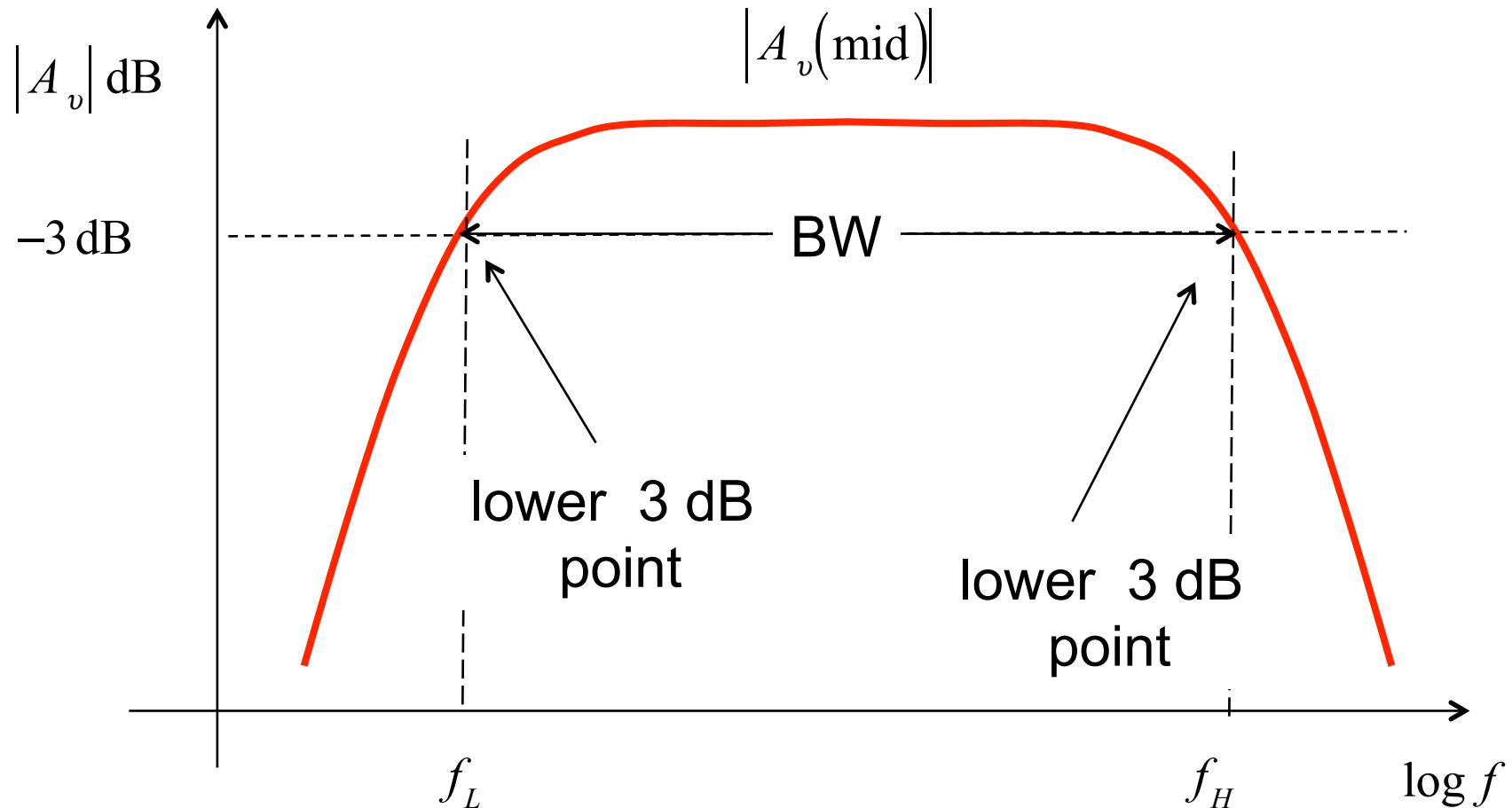


Outline

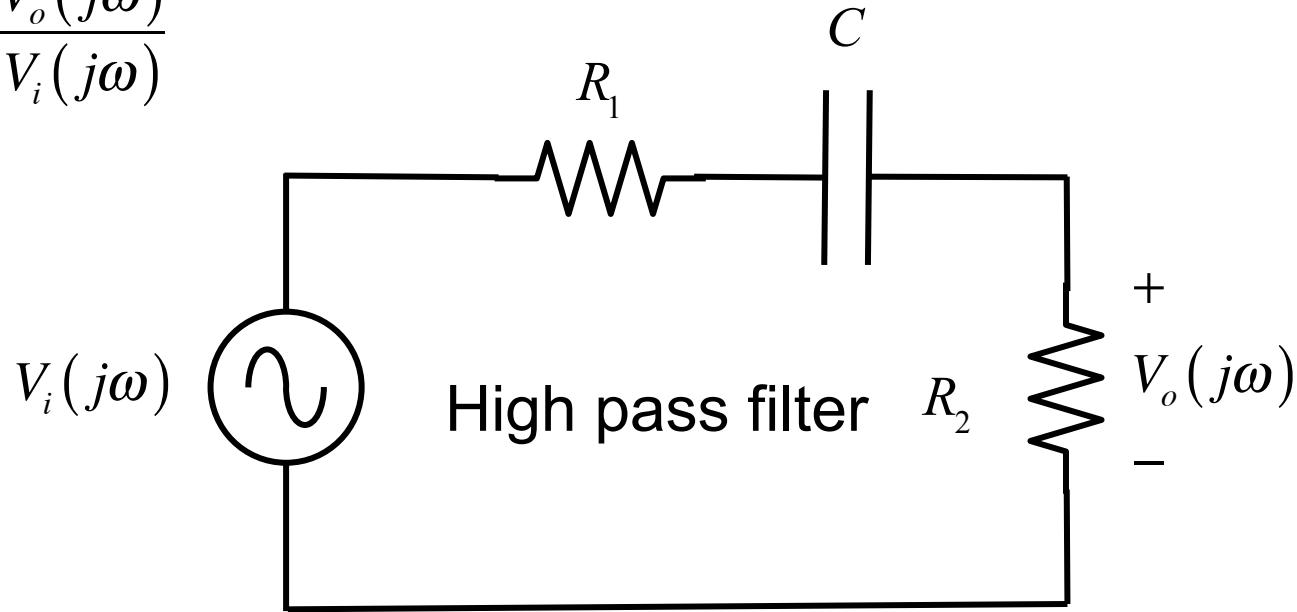- 1) Decibels
- 2) High pass filter / STC circuits**
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix

Single time constant (STC) circuit

$$T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$$



$$T(j\omega) = \frac{R_2}{R_1 + R_2 + 1/j\omega C}$$

$$T(j\omega) = \frac{R_2 / (R_1 + R_2)}{1 - j \frac{\omega C (R_1 + R_2)}{1}}$$

$$\omega_L = \frac{1}{(R_1 + R_2)C}$$

$$T(j\omega) = \frac{T_{mid}}{1 - j \omega_L / \omega}$$

(STC) circuit: Bode plot


$$T(j\omega) = \frac{T_{mid}}{1 - j\omega_L/\omega}$$

$$|T(j\omega)| = \frac{T_{mid}}{\sqrt{1 + \omega_L^2/\omega^2}}$$

$$\omega_L = \frac{1}{(R_1 + R_2)C}$$

$$\omega \gg \omega_L \quad |T(j\omega)| = T_{mid}$$

$$\omega \ll \omega_L \quad |T(j\omega)| = T_{mid} \frac{\omega}{\omega_L}$$

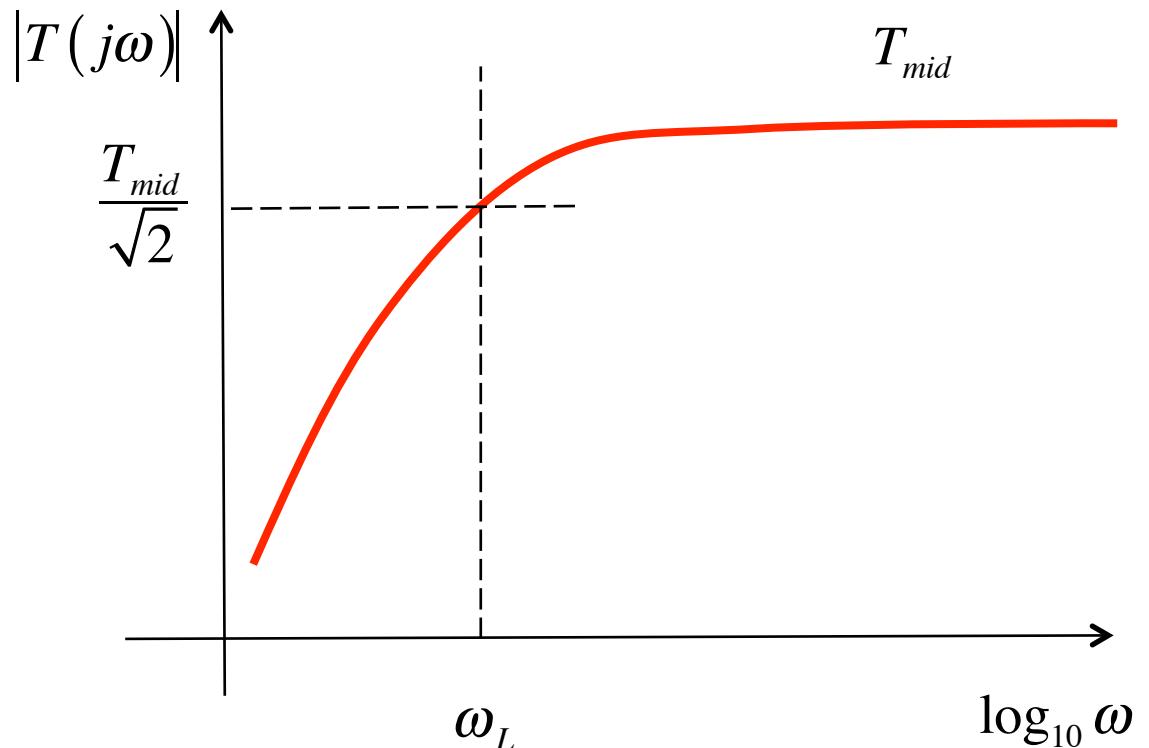

20 dB /decade or 6 dB per octave

Lundstrom: 2019

(STC) circuit: phase


$$T(j\omega) = \frac{T_{mid}}{1 - j\omega_L/\omega}$$

$$T(j\omega) = \frac{T_{mid}}{1 + \omega_L^2/\omega^2} (1 + j\omega_L/\omega)$$

$\omega \ll \omega_L$: phase = 90°

$\omega = \omega_L$: phase = 45°

$\omega \gg \omega_L$: phase = 0°

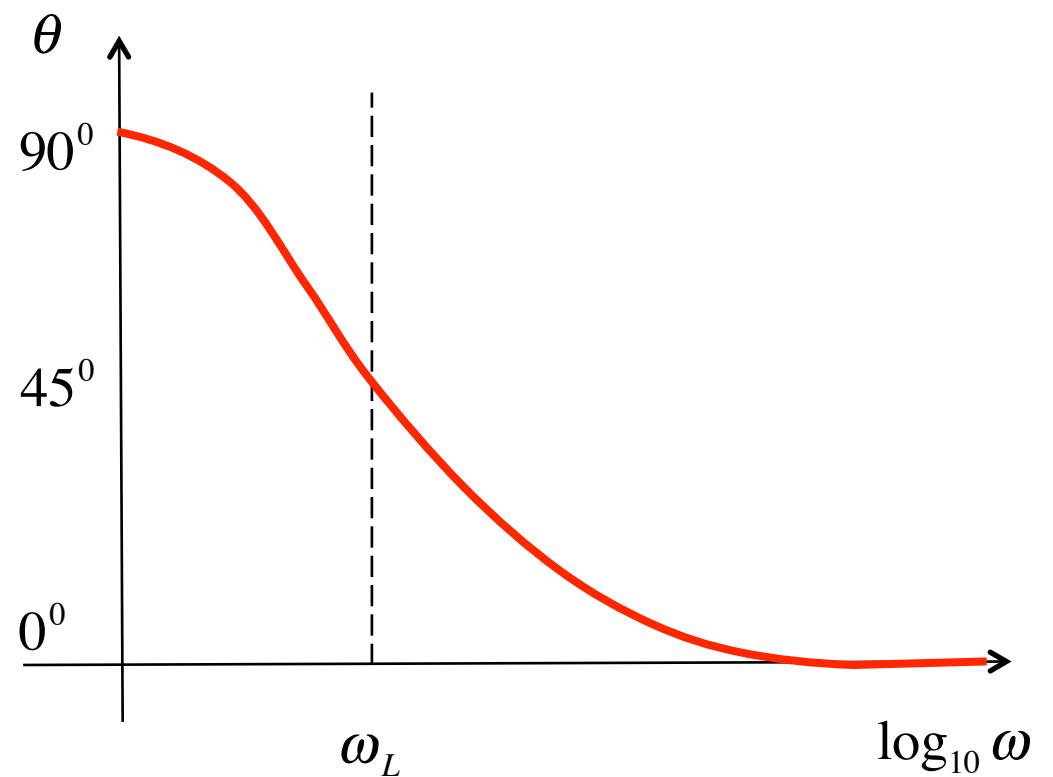

“Poles and zeros”

$$T(j\omega) = \frac{T_{mid}}{1 + \omega_L/j\omega}$$


$$s = j\omega$$

$$T(s) = \frac{T_{mid}}{1 + \omega_L/s}$$

$$T(s) = T_{mid} \times \frac{s}{s + \omega_L}$$

STC has one pole

Short cut


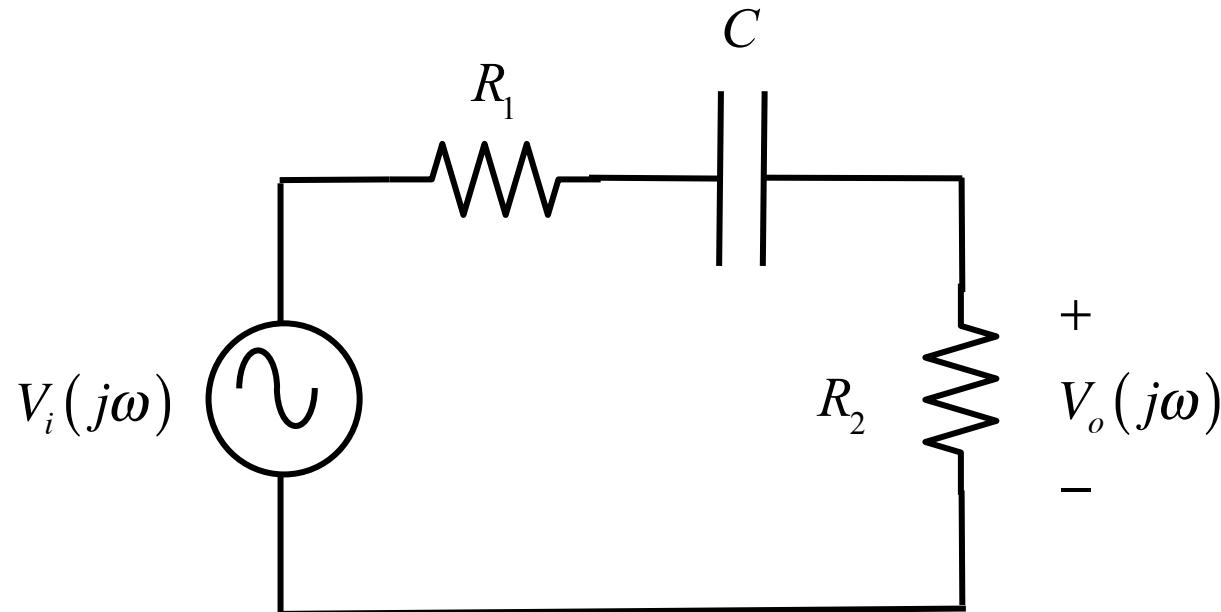


$$T(j\omega) = \frac{T_{mid}}{1 + \omega_L/j\omega}$$
$$\omega_L = \frac{1}{(R_1 + R_2)C}$$

The corner frequency (the pole) is one over a time constant – just find the RC time constant.

Kill the voltage source and find the Thevenin equivalent resistance that the capacitor sees.

Short cut

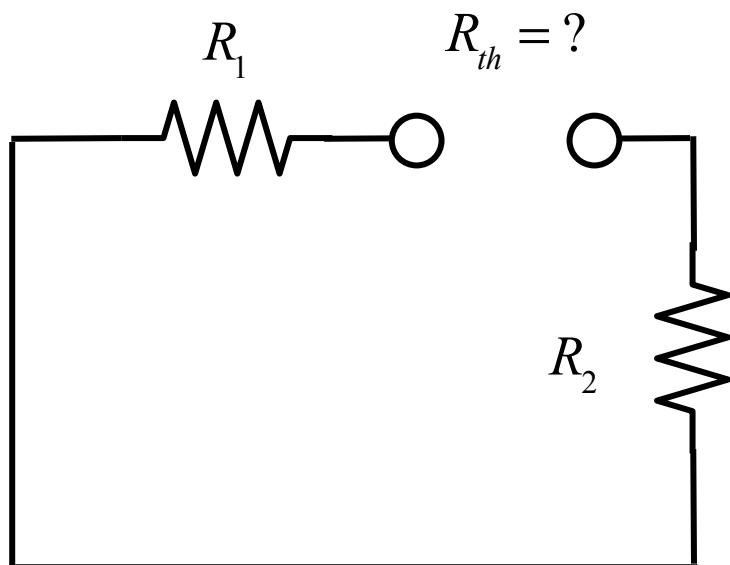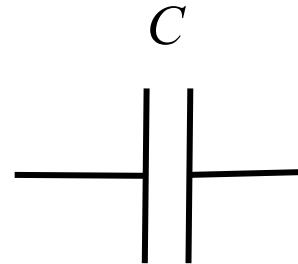

$$R_{th} = ?$$


$$R_{th} = R_1 + R_2$$

$$\omega_L = \frac{1}{R_{th} C} = \frac{1}{(R_1 + R_2) C}$$

Outline

- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of a **discrete** CS
- 4) Design Example
- 5) LF Response of CE
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix

Now analyze this circuit

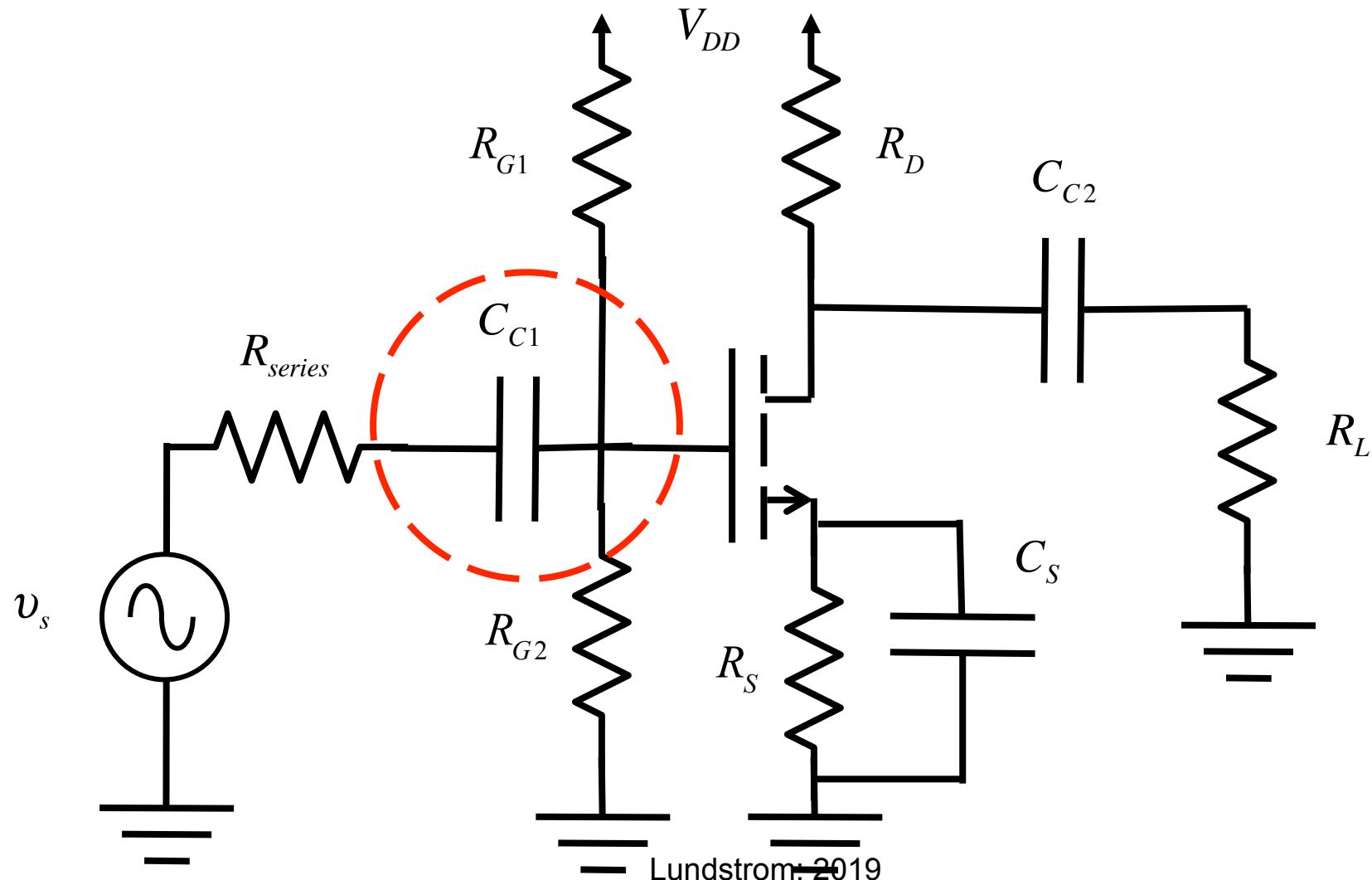


First corner frequency

$$\omega_{L1} = \frac{1}{C_{C1}(R_{series} + R_{G1} \parallel R_{G2})}$$

Expected be small (which is good)

Important: While we compute this corner frequency, we assume that the other C's are shorted – this produces a STC circuit.

Second coupling capacitor

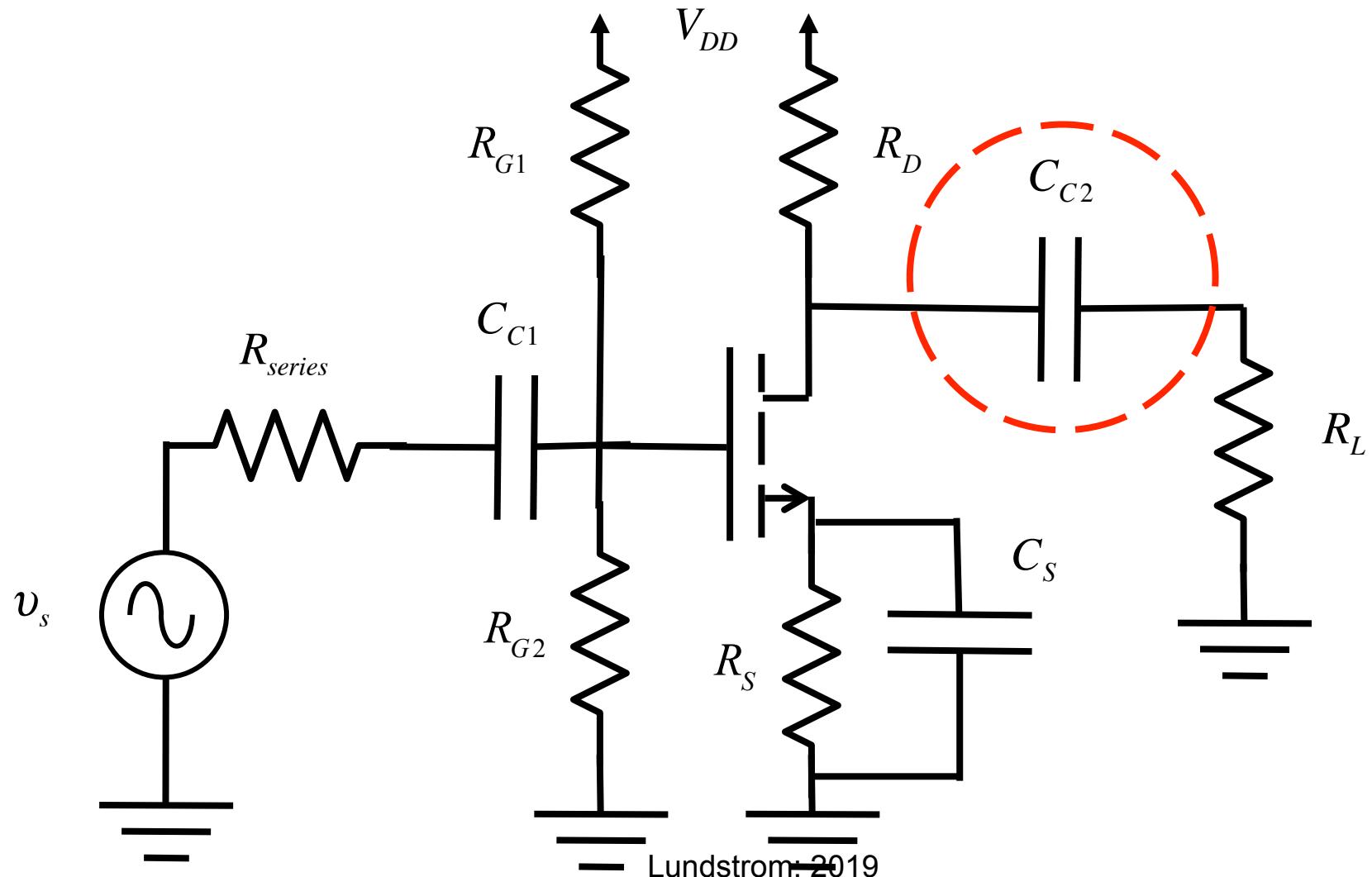


Second corner frequency

$$\omega_{L2} = \frac{1}{C_{C2}(R_D + R_L)}$$

Expected be reasonably small (which is also good)

Third coupling capacitor

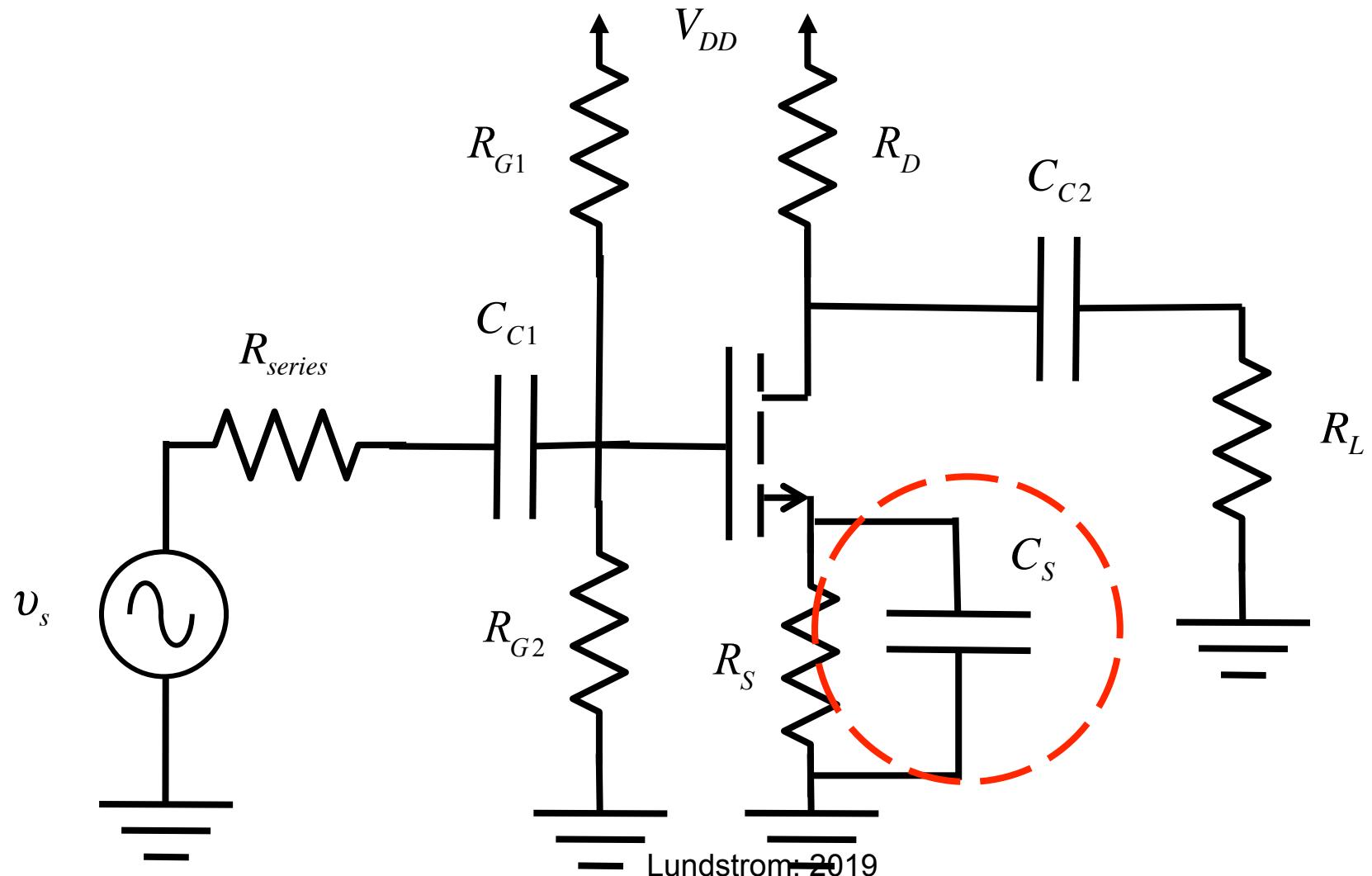


Third corner frequency

$$\omega_{LS} = \frac{1}{C_s(R_s \parallel (1/g_m))}$$

Expected be the **largest** of the three.


Result

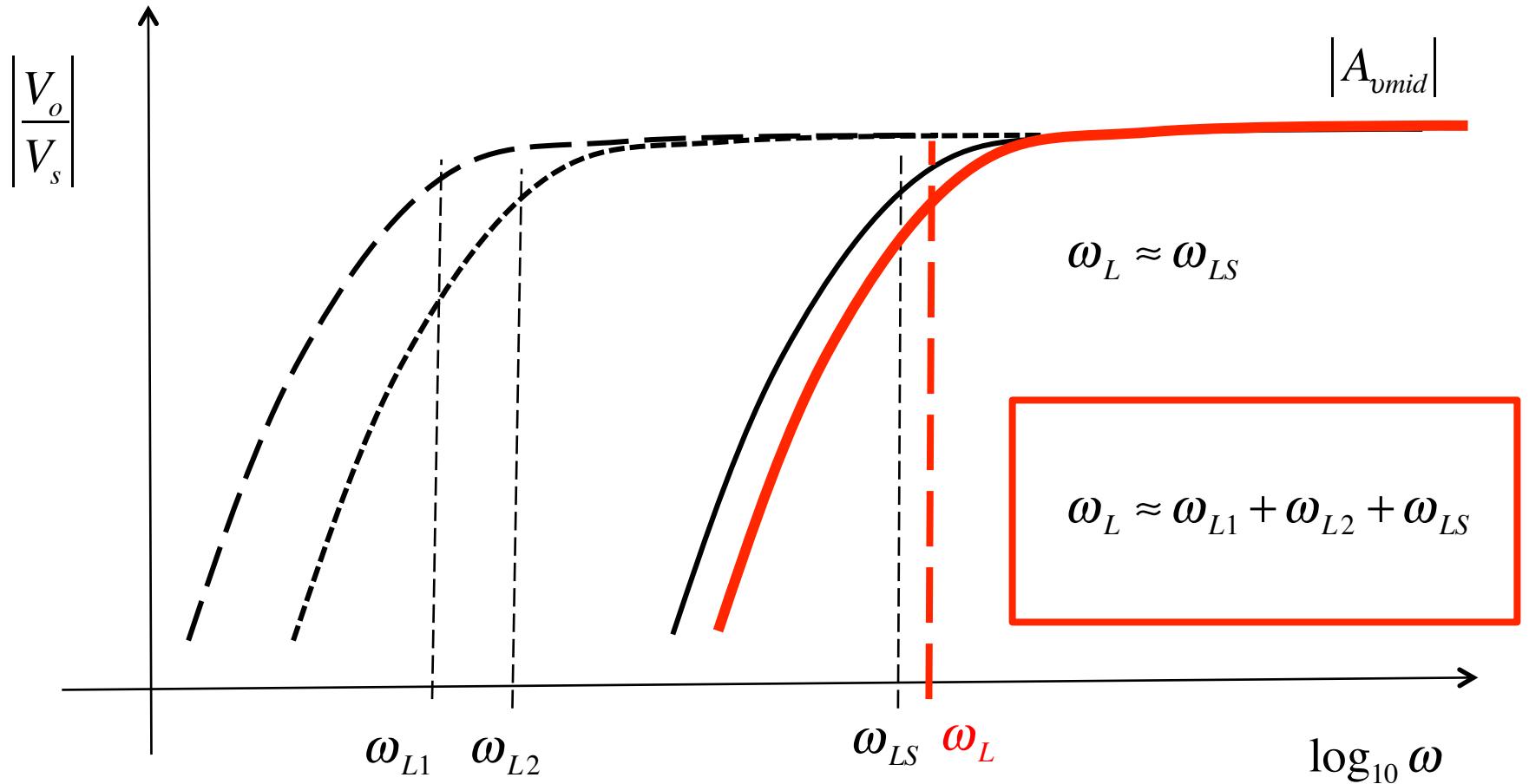


Outline

- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example**
- 5) LF Response of CE and CB:CC
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix


Select the capacitors to:

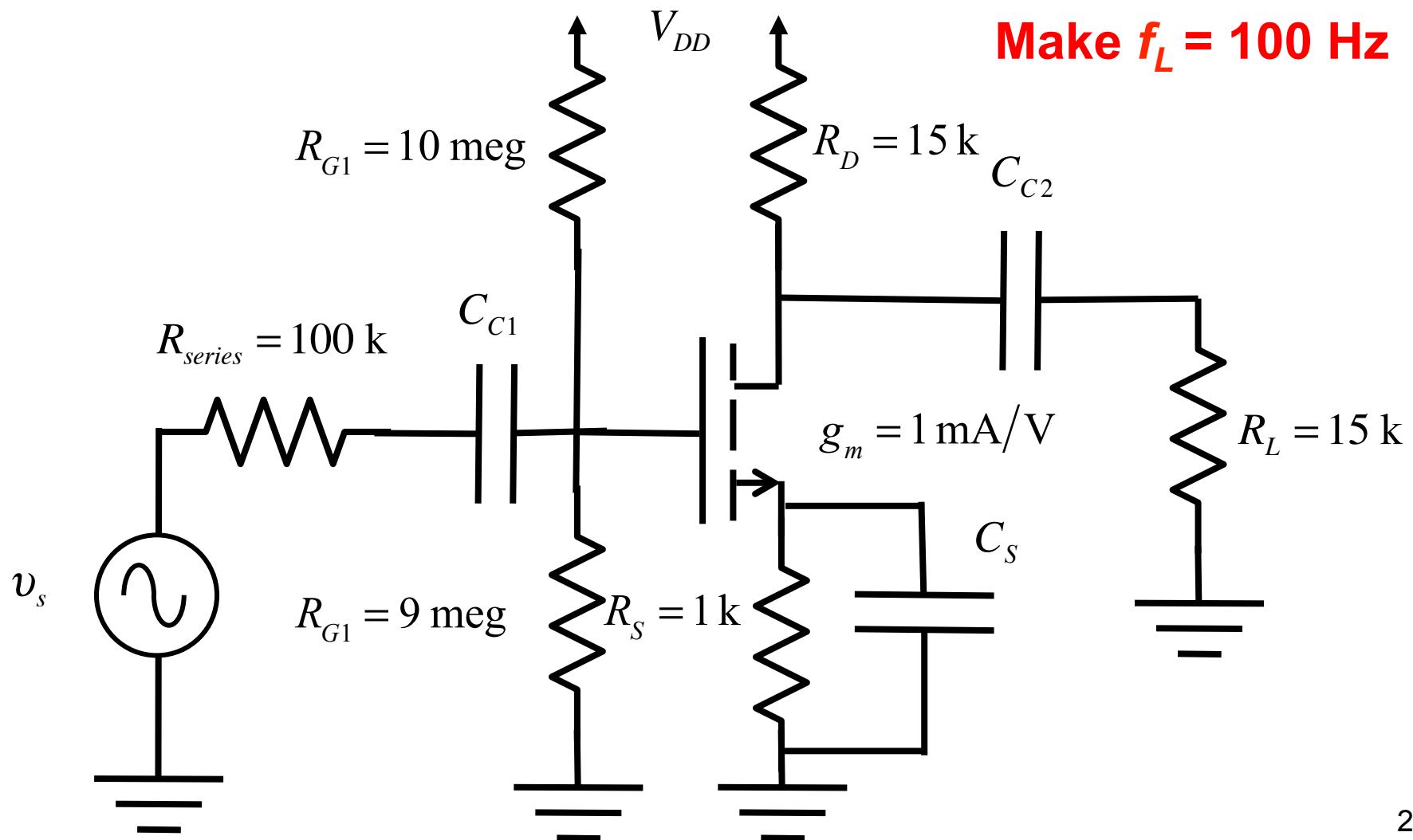

Bode plot

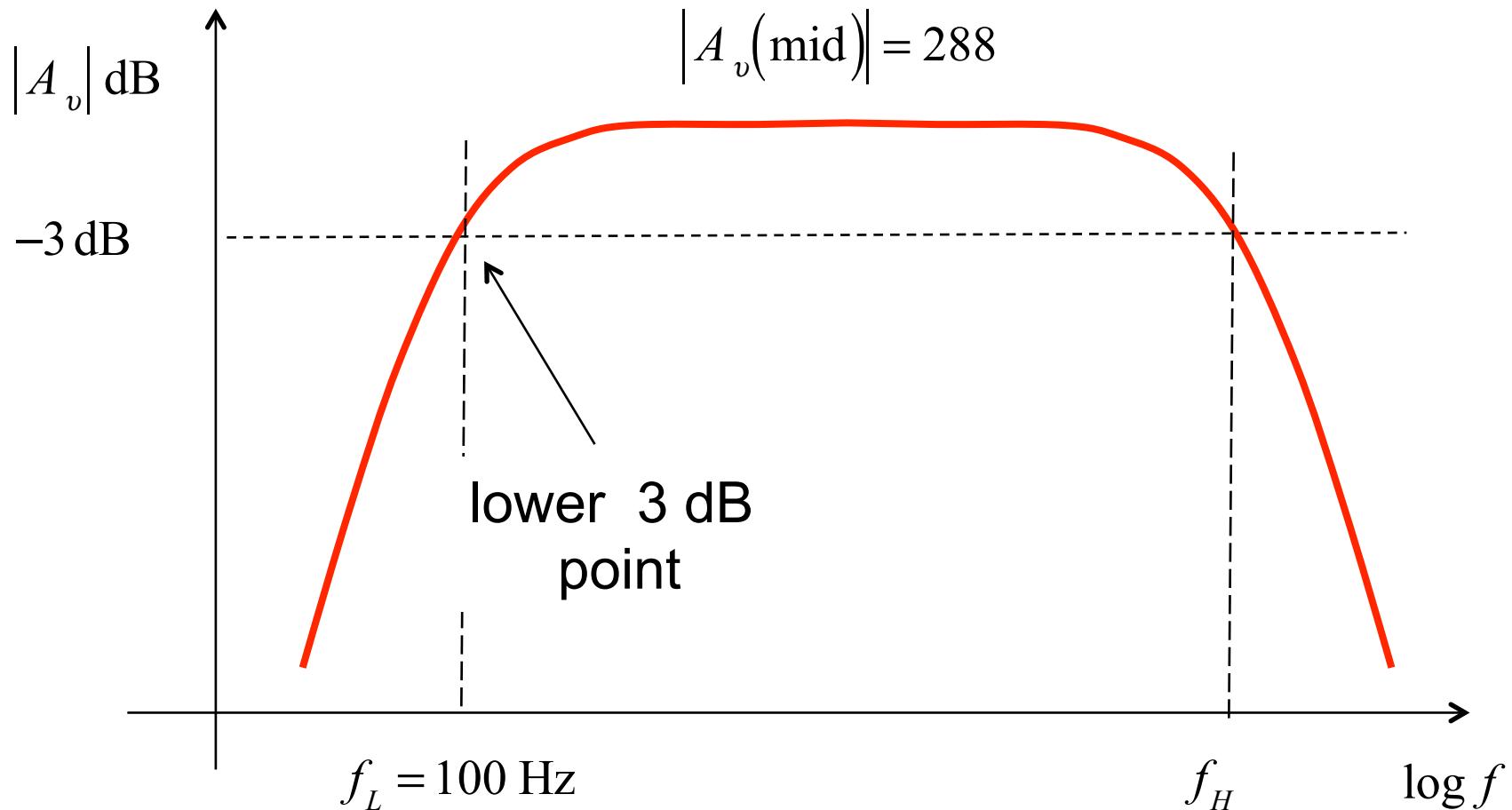

Select the first capacitor

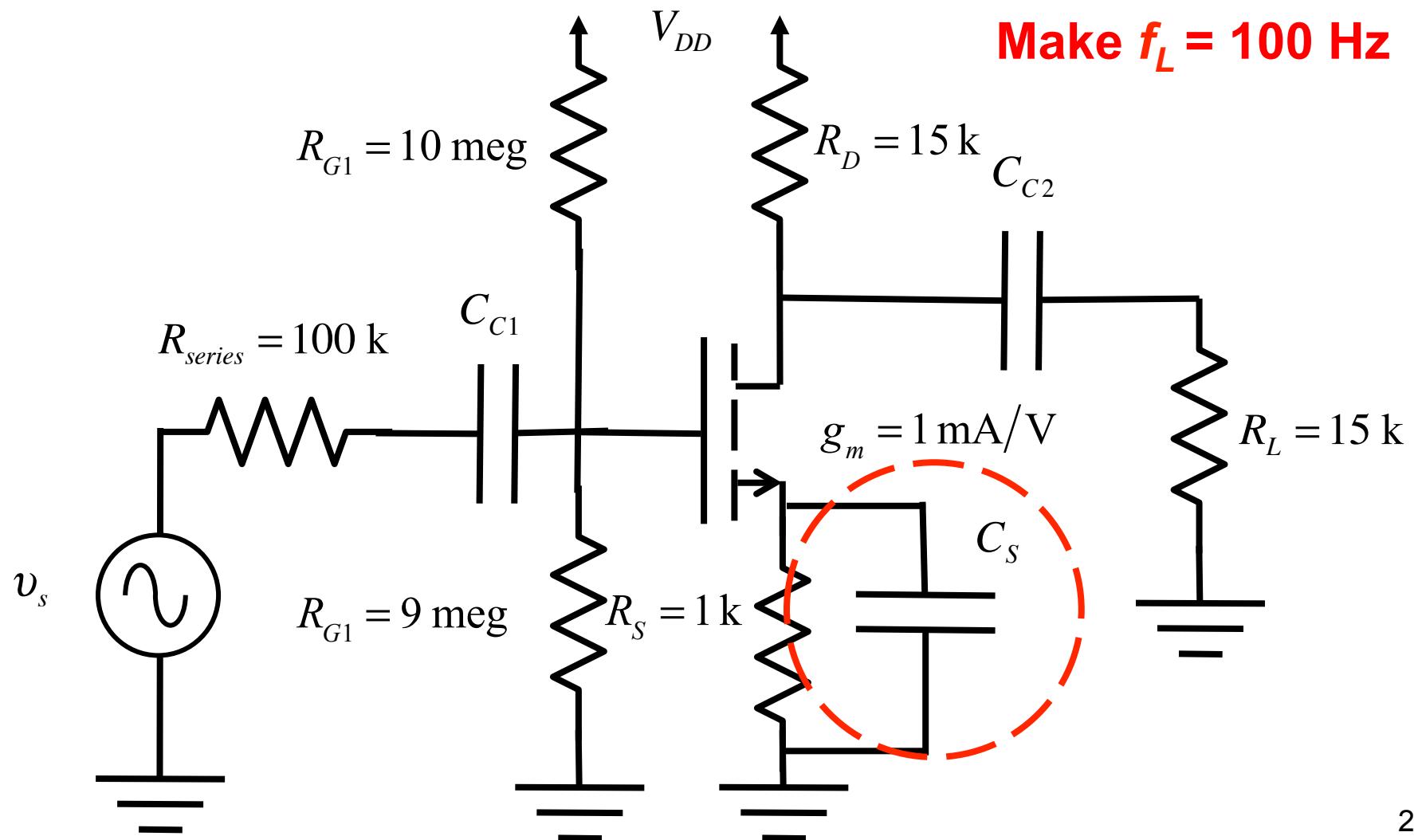

Source capacitance

C_S is expected be the largest of the three. It require the largest C to make the Corner Frequency spec.

$$\omega_{LS} = \frac{1}{C_S(R_S \parallel (1/g_m))} = 2\pi \times 100$$


$$1/g_m = 26 \Omega$$

$$\frac{1}{C_S} = 628 \times 26$$

$$C_S = 62 \times 10^{-6} \text{ F}$$

Now make the other two corner frequencies 5-10 X smaller.

Select the second capacitors

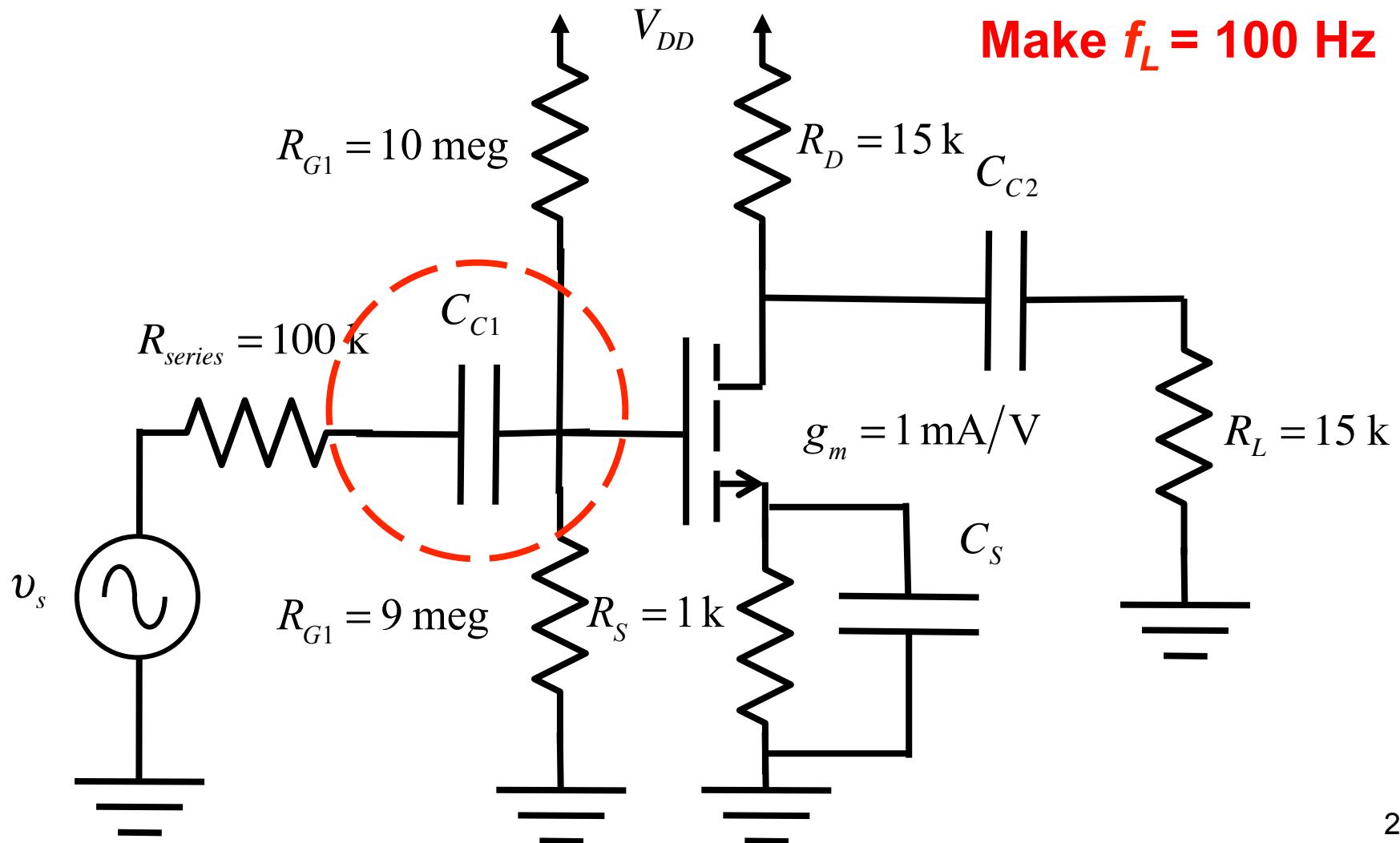


The second capacitor

$$\omega_{L1} = \frac{1}{C_{C1}(R_{series} + R_{G1} \parallel R_{G2})} = 2\pi \times 10 \quad 10 \times \text{smaller}$$

$$C_{C1} = \left[62.8 \times (100 \times 10^3 + 4.7 \times 10^6) \right]^{-1}$$

$$C_{C1} = 3.3 \times 10^{-9} \text{ F}$$

Select the third capacitor

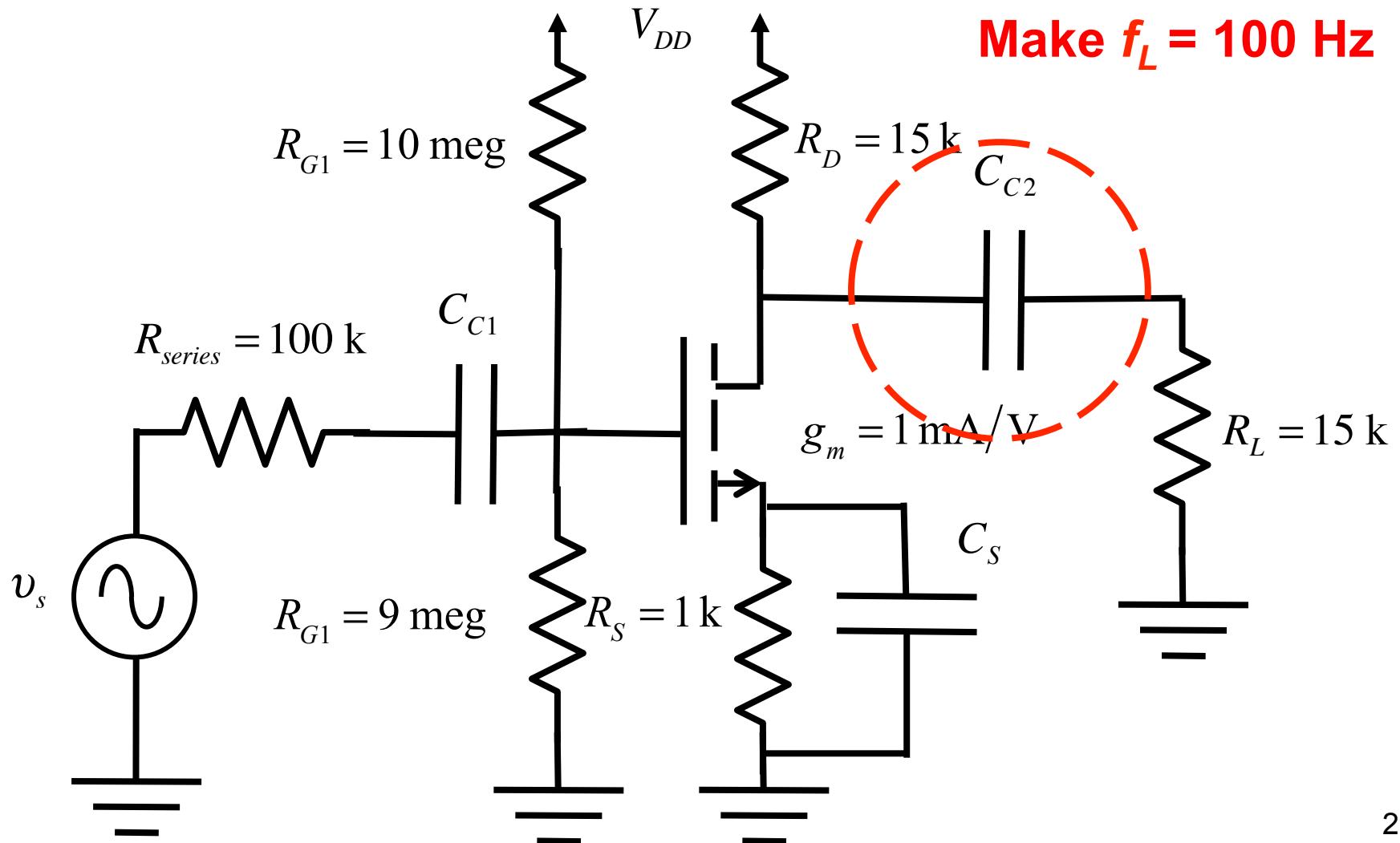

The third capacitor

$$\omega_{L_2} = \frac{1}{C_{C2}(R_D + R_D)} = 2\pi \times 10$$

10 X smaller


$$C_{C2} = (62.8 \times 30 \times 10^3)^{-1}$$

$$C_{C2} = 0.5 \times 10^{-6} \text{ F}$$

Outline


- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE and CB:CC**
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix

Now analyze this circuit

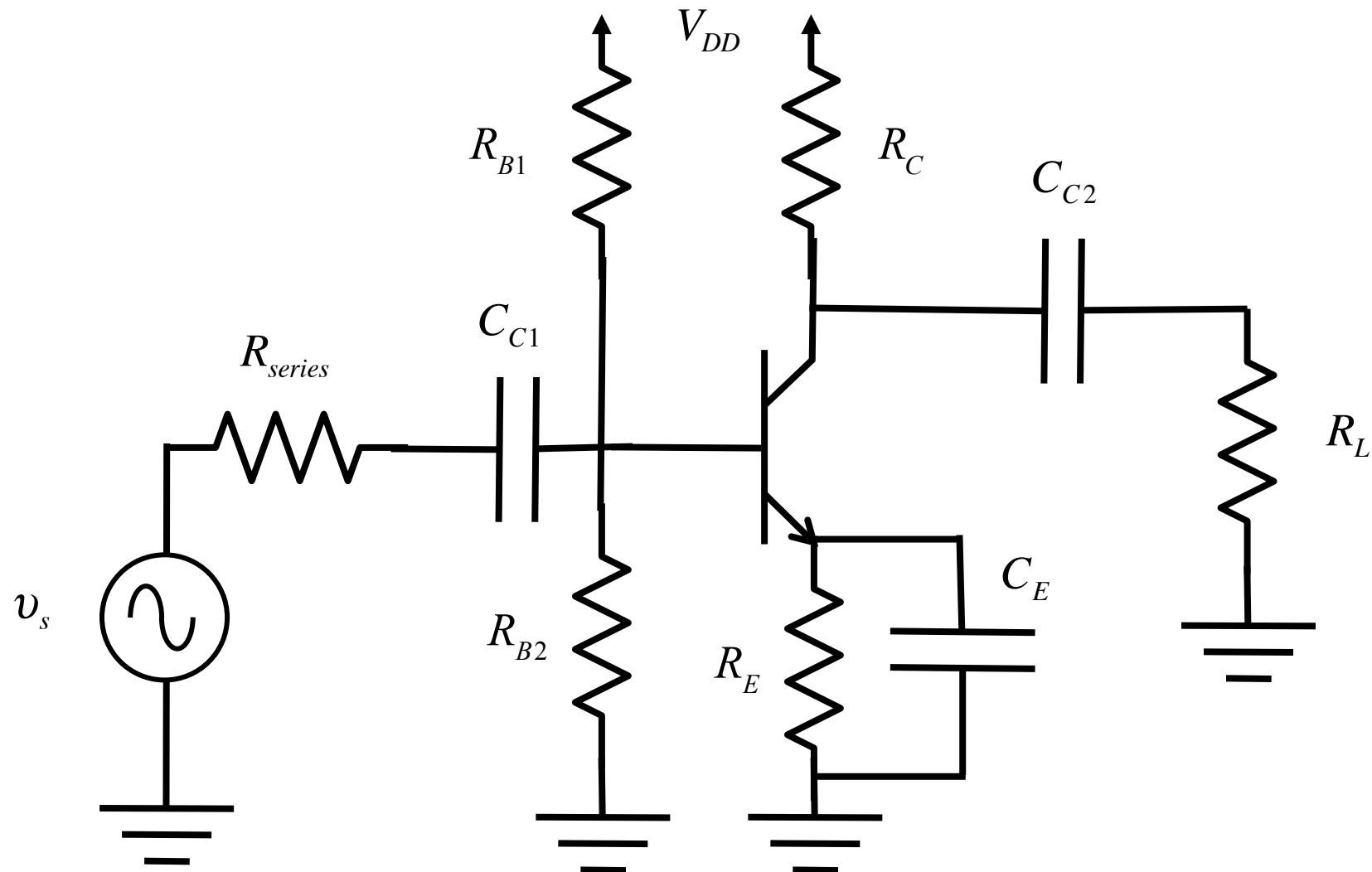


Answers can be written down by inspection

CB: CC Example

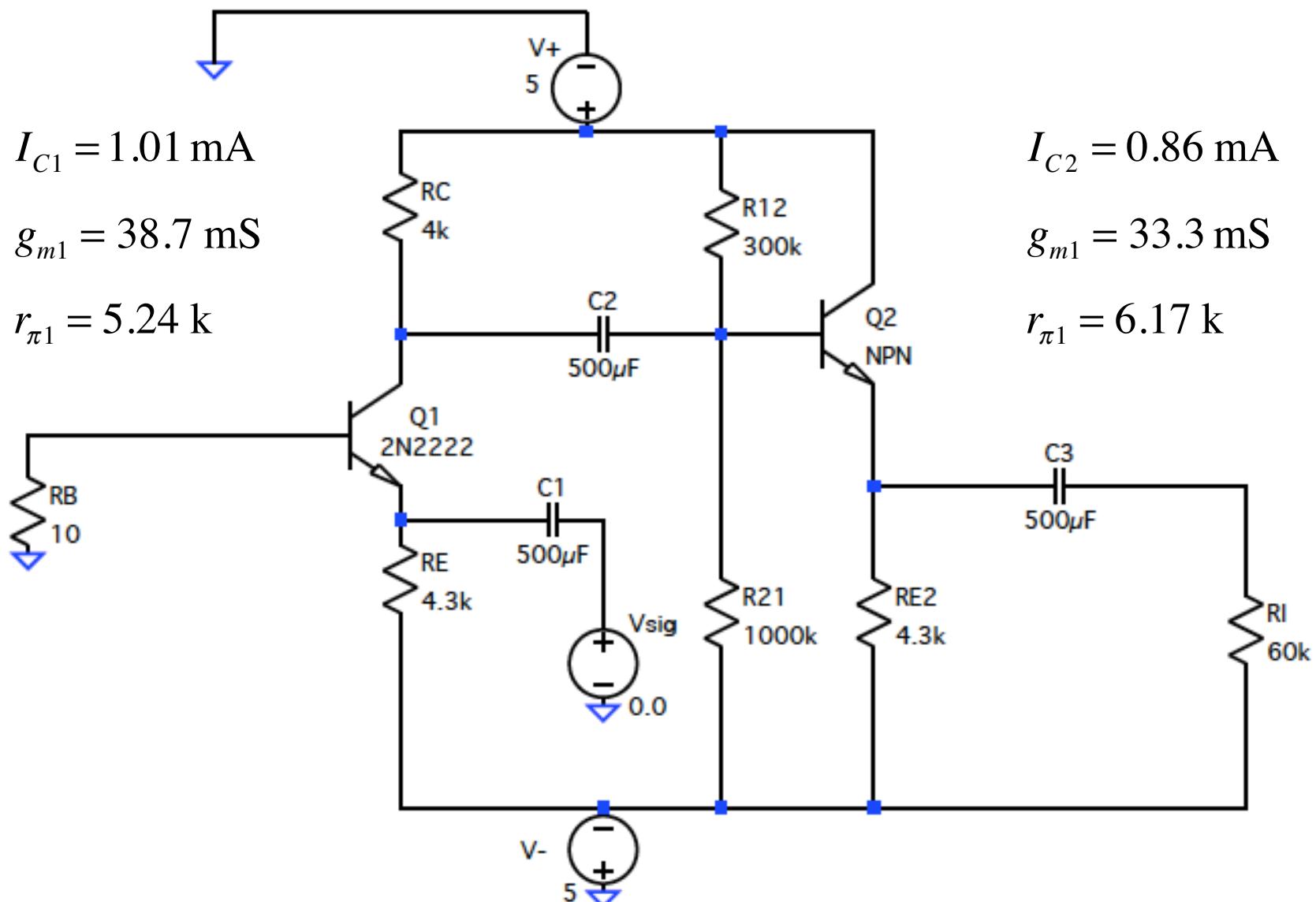


Example

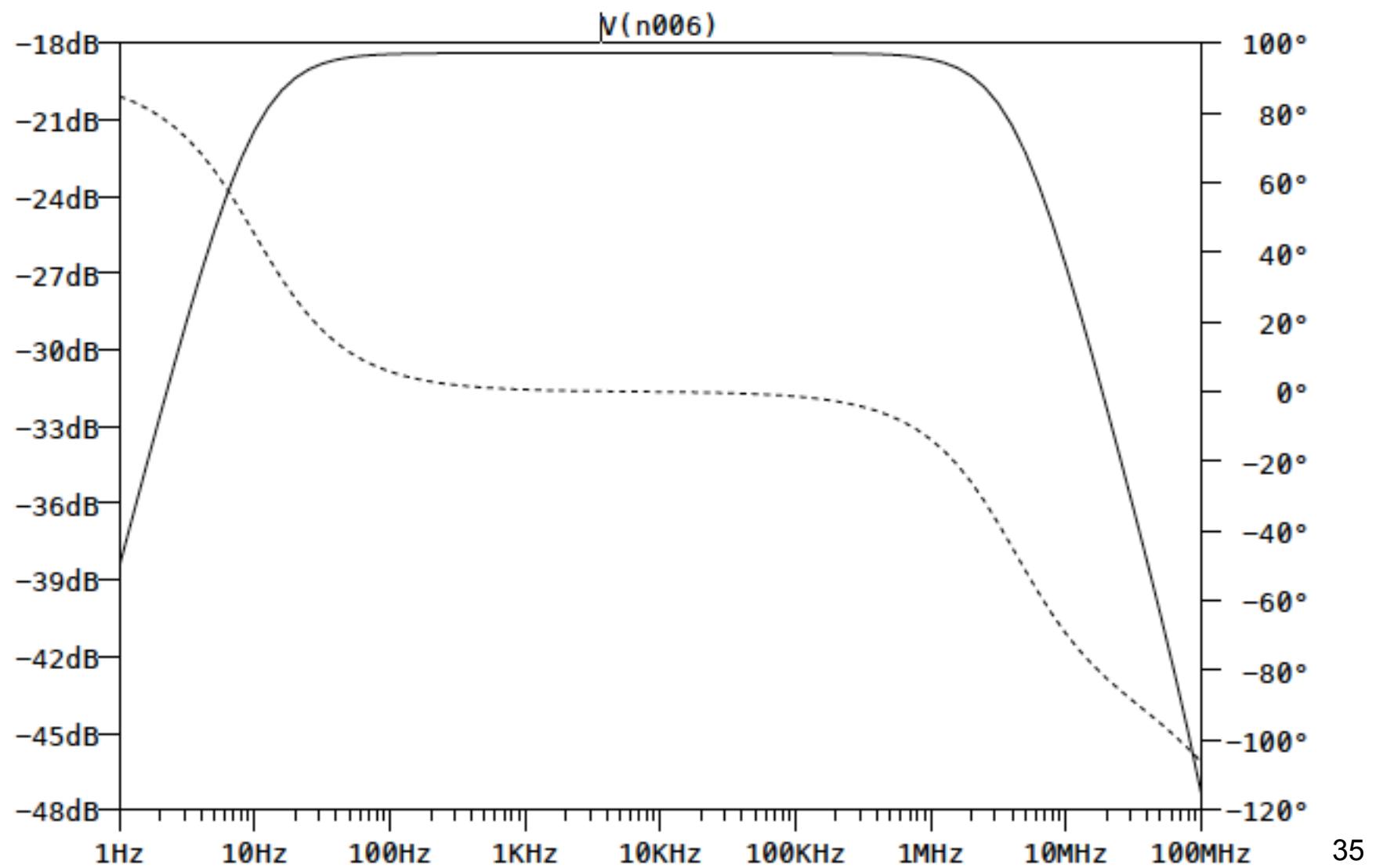

Outline

- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE and CB:CC
- 6) Exact CS analysis**
- 7) Summary
- 8) Appendix

Our CS circuit

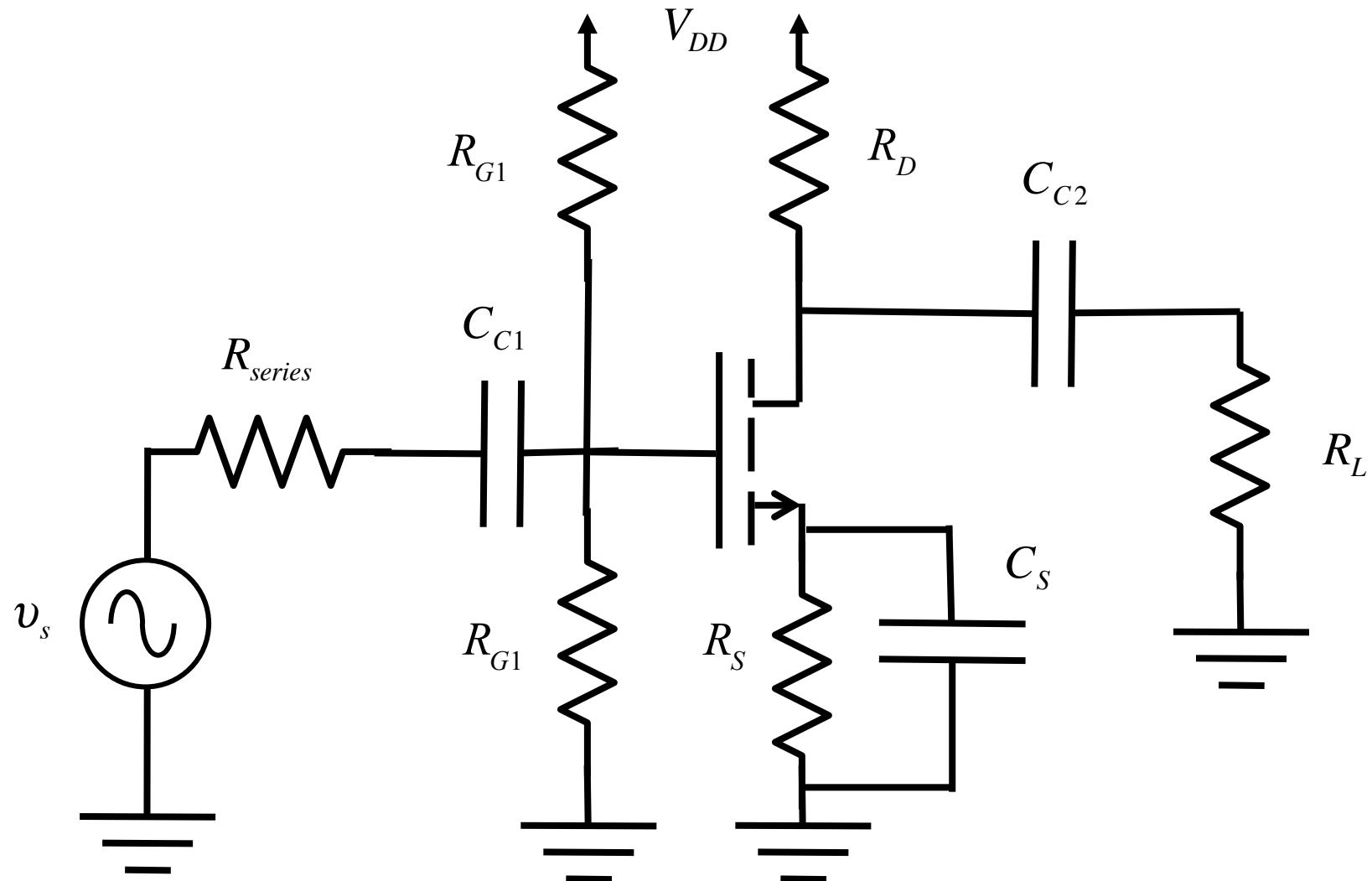

Our (simplified) approach

- 1) Short two of the capacitors (they are supposed to have essentially zero impedance at the frequencies of interest).
- 2) Evaluate the STC circuit:

$$\omega_{L1} = 1/(C_1 R_{th1})$$

- 3) Repeat for the other two capacitors.
- 4) Estimate the frequency response the amplifier as:

$$|A_v(\omega)| = \frac{A_v(\text{mid})}{\sqrt{1 + (\omega_L/\omega)^2}} \quad \omega_L = \omega_{L1} + \omega_{L2} + \omega_{L3}$$

Our (simplified) approach (ii)

This approach assume that the overall transfer function is the product of the three STC circuits:

$$A_v(\omega) = A_v(\text{mid}) \left(\frac{1}{1 + \omega_{L1}/j\omega} \right) \left(\frac{1}{1 + \omega_{L2}/j\omega} \right) \left(\frac{1}{1 + \omega_{L3}/j\omega} \right)$$

$$T(\omega) = T_1(\omega) \times T_2(\omega) \times T_3(\omega)$$

There is no guarantee that this will always work, but the procedure often gives us a good estimate for the corner frequency.

How would we solve the problem correctly?

Exact low frequency response of CS amplifier

$$A_{v_s}(\omega) = A_{v_s}(\text{mid}) \frac{1 + \frac{\omega_z}{j\omega}}{\left(1 + \frac{\omega_{C1}}{j\omega}\right)\left(1 + \frac{\omega_s}{j\omega}\right)\left(1 + \frac{\omega_{C2}}{j\omega}\right)}$$

(See Appendix)

Almost the product of 3 STC responses, but there is an additional zero.

$$\omega_z = \frac{1}{R_s C_s} \ll \omega_s = \frac{1}{(R_s \parallel 1/g_m) C_s}$$

So the zero is not important - it does not affect our conclusions about the LF corner frequency.

Outline

- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE and CB:CC
- 6) Exact CS analysis
- 7) Summary**
- 8) Appendix

Short-circuit time constant method

- 1) Short the other capacitors (they are supposed to have essentially zero impedance at the frequencies of interest).
- 2) Evaluate the STC circuit:

$$\omega_{L1} = 1/(C_1 R_{th1})$$


- 3) Repeat for the other capacitors.
- 4) Select the largest corner frequency and estimate the frequency response the amplifier as:

$$|A_v(\omega)| = \frac{A_v(\text{mid})}{\sqrt{1 + (\omega_L/\omega)^2}} \quad \omega_L = \omega_{L1} + \omega_{L2} + \omega_{L3}$$


Outline

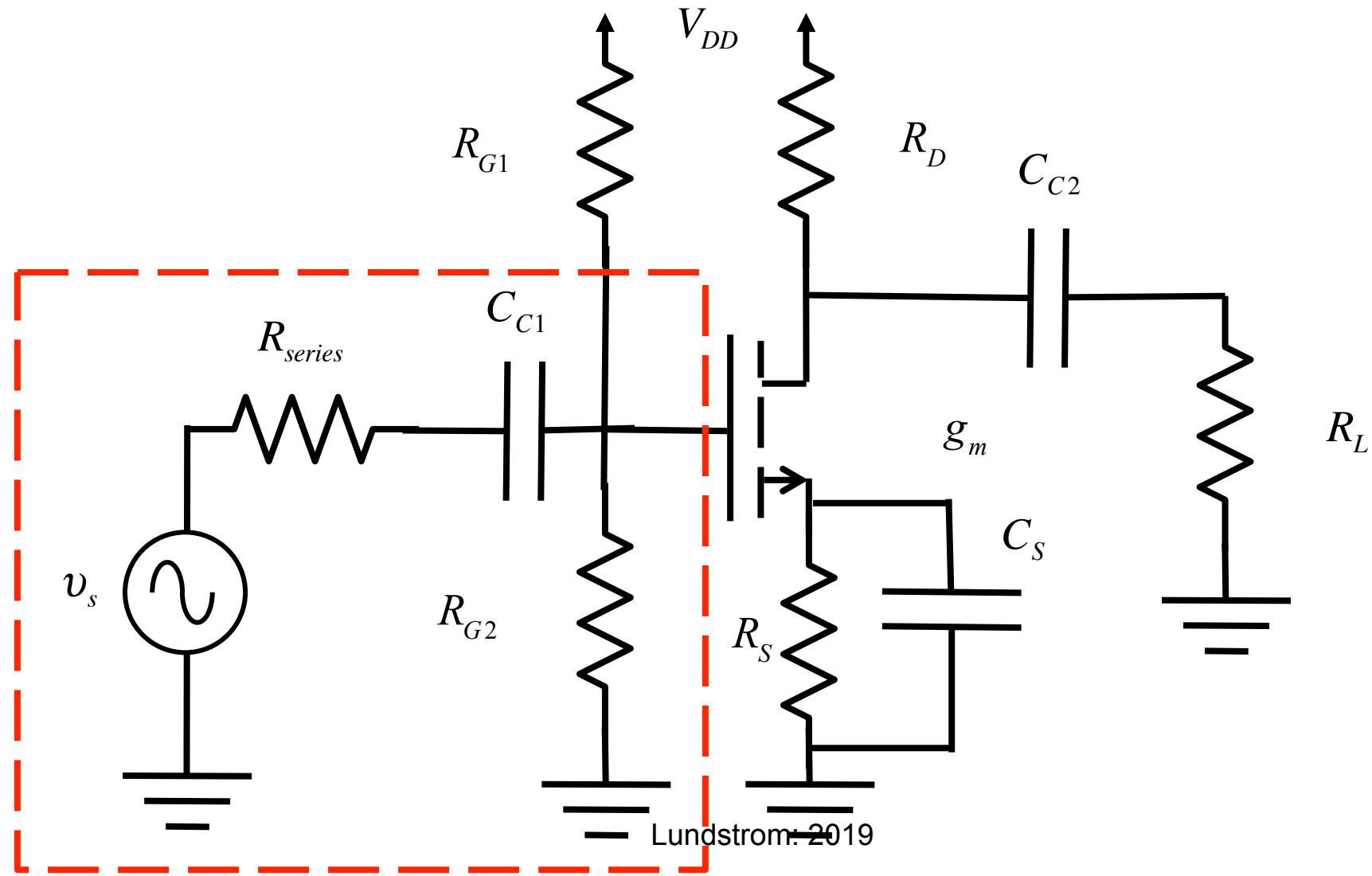- 1) Decibels
- 2) High pass filter / STC circuits
- 3) LF response of CS
- 4) Design Example
- 5) LF Response of CE and CB:CC
- 6) Exact CS analysis
- 7) Summary
- 8) Appendix

Exact low frequency response of CS amplifier



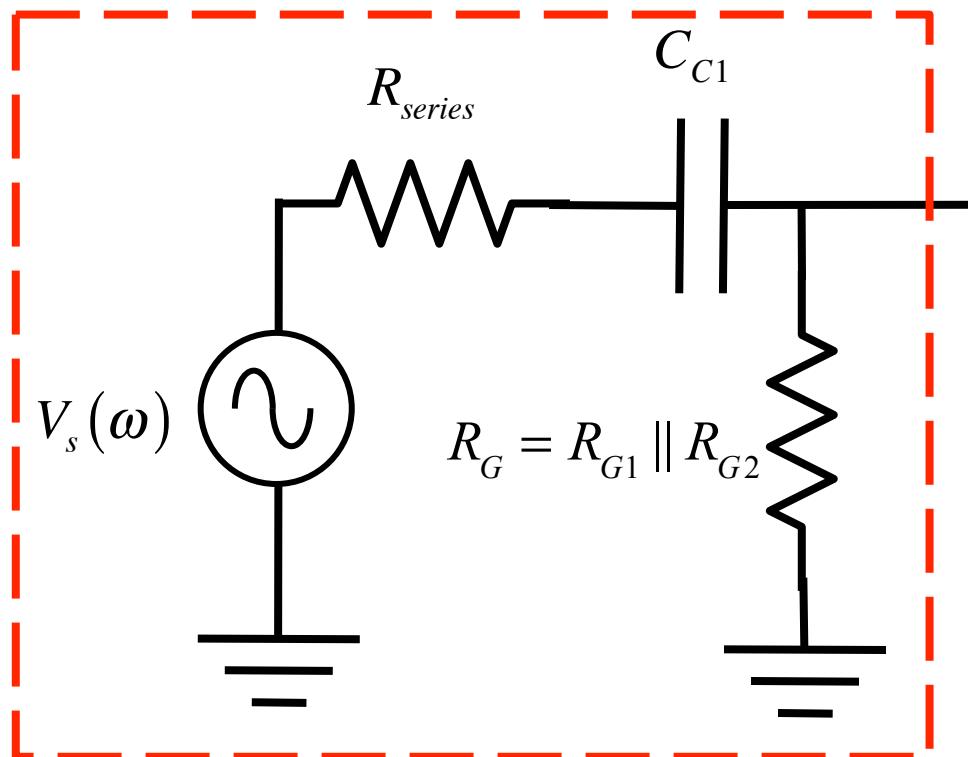Exact low frequency response of CS amplifier




$$V_i(\omega)$$

$$V_i(\omega) = \frac{R_G}{R_G + R_{series} + \frac{1}{j\omega C_{C1}}} V_s(\omega)$$



$$V_i(\omega) = \left(\frac{R_G}{R_G + R_{series}} \right) \frac{1}{1 + \frac{\omega_{C1}}{j\omega}} V_s(\omega)$$

$$\omega_{C1} = \frac{1}{(R_G + R_{series}) C_{C1}}$$

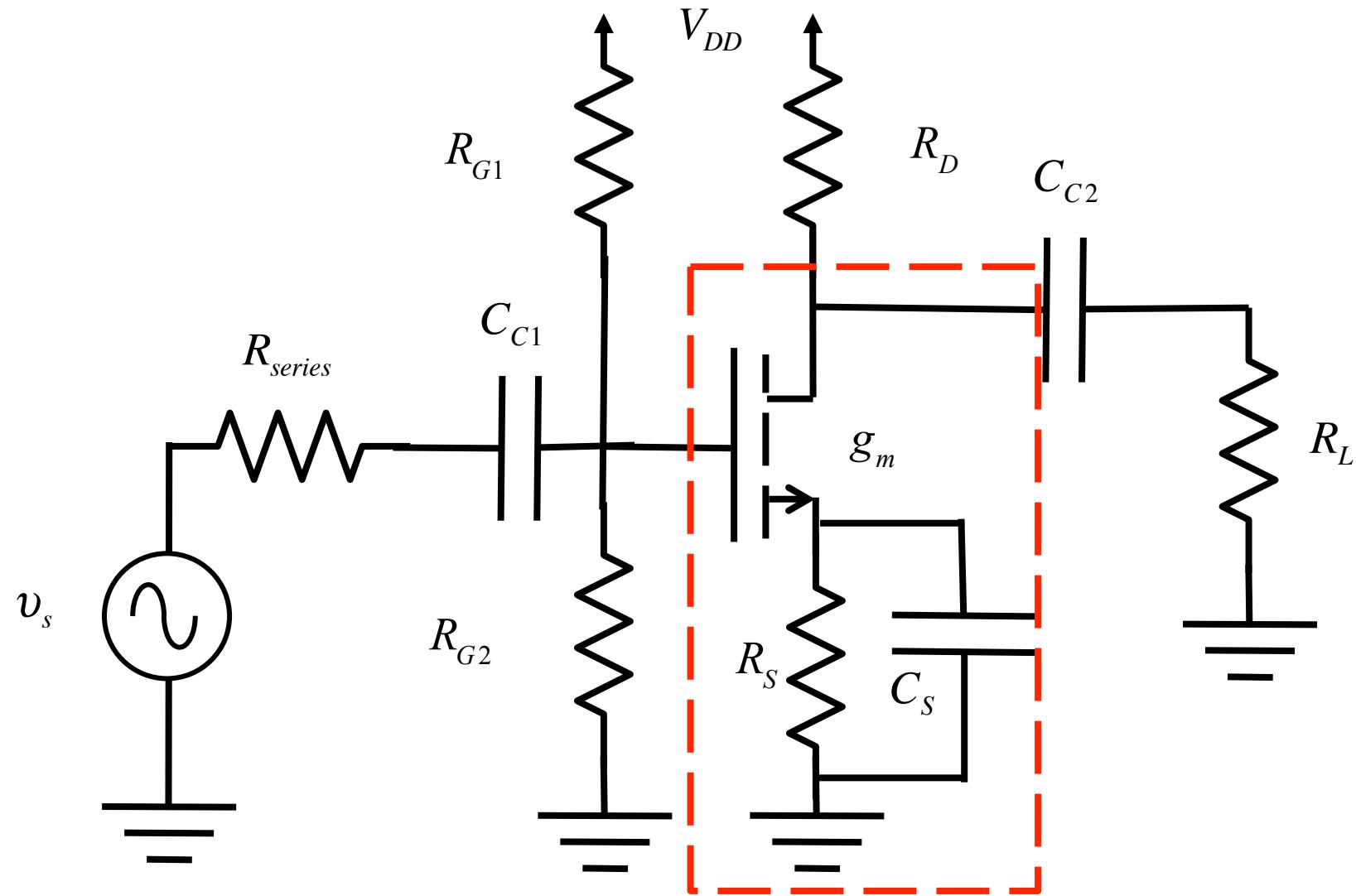Exact low frequency response of CS amplifier




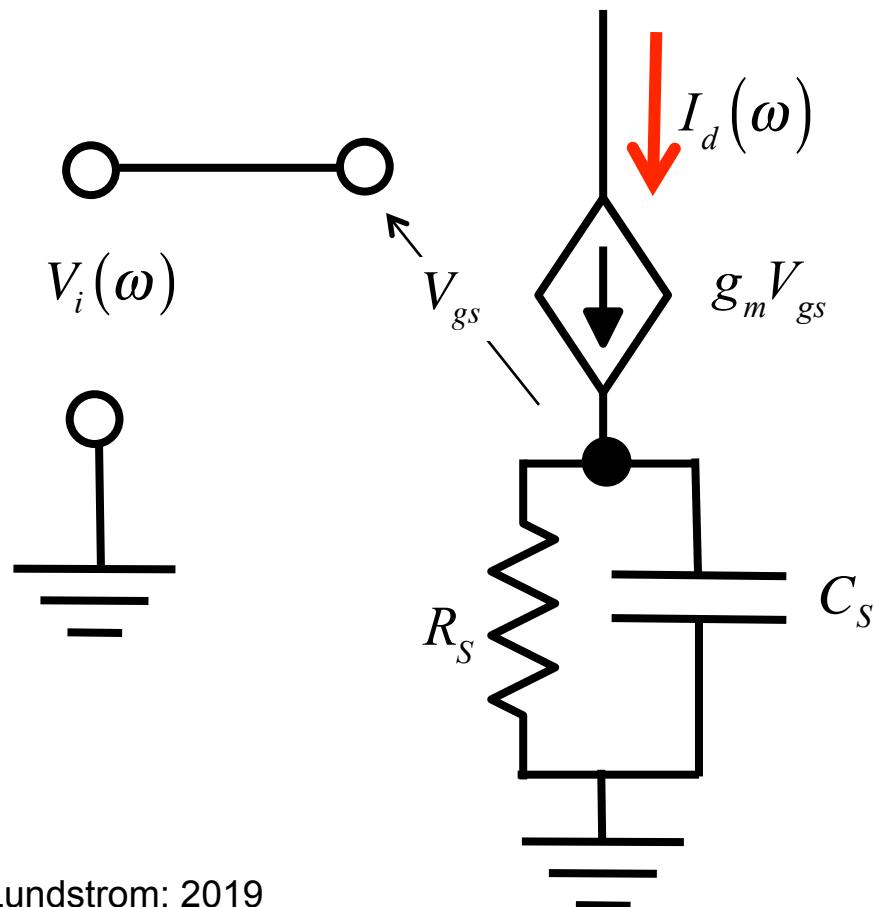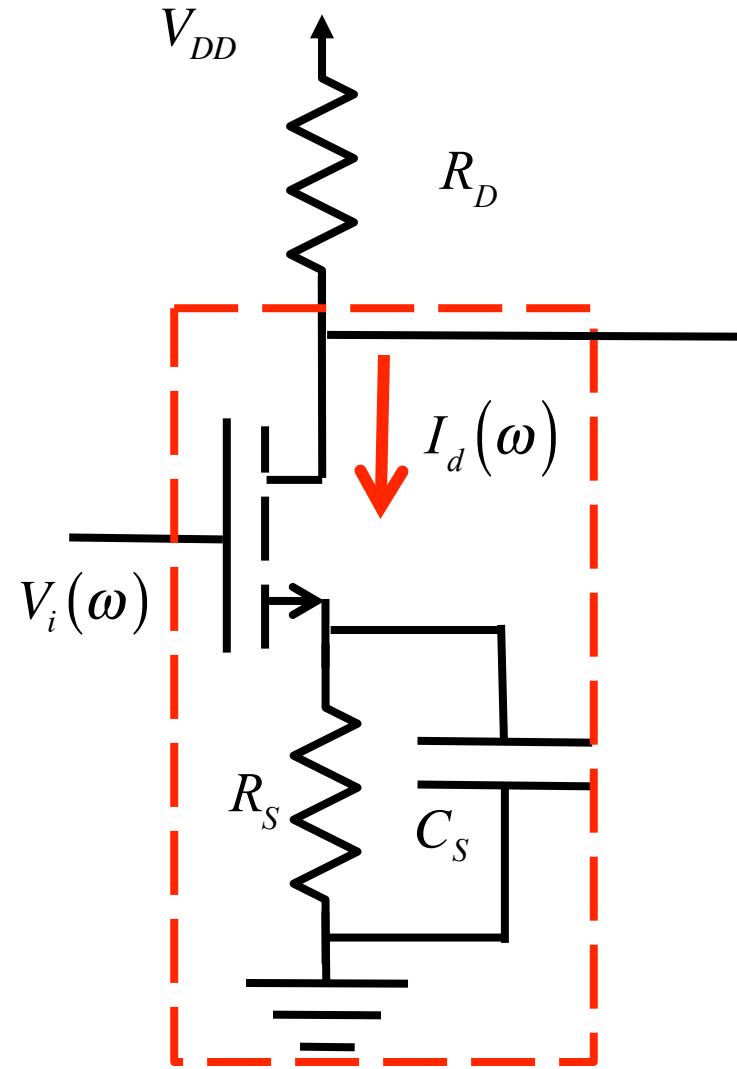Exact low frequency response of CS amplifier



Lundstrom: 2019

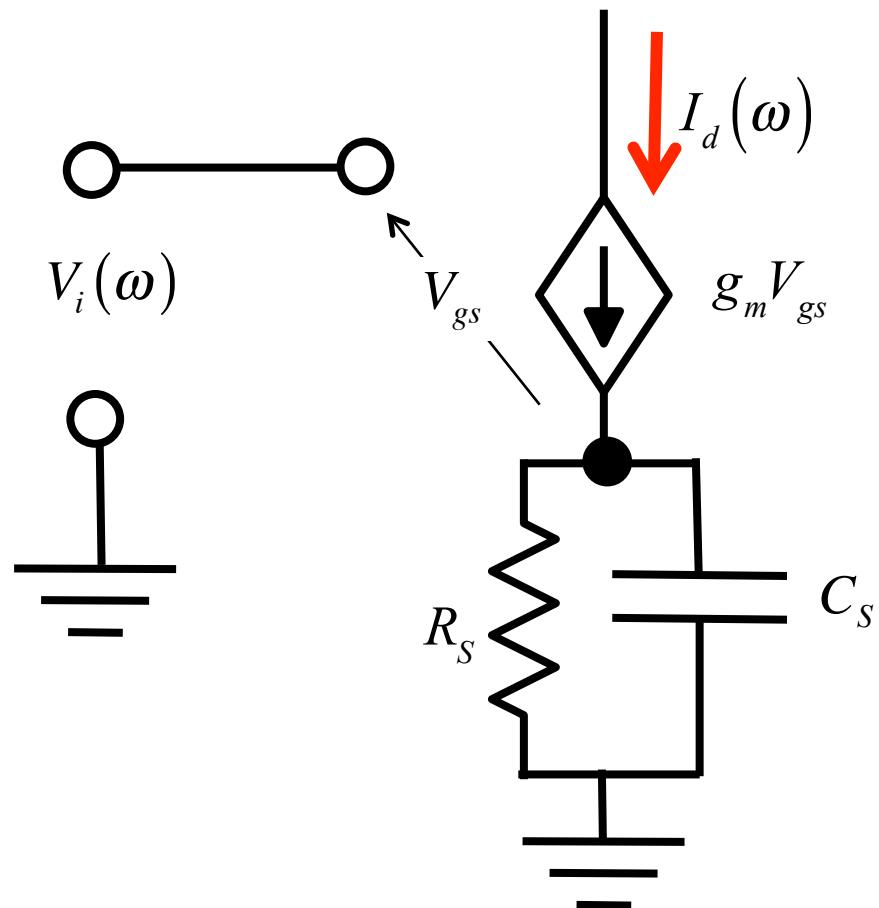Exact low frequency response of CS amplifier



$$I_d = g_m V_{gs}$$

$$V_{gs} = V_i - I_d Z_S$$

$$I_d = \frac{g_m V_i}{1 + g_m Z_S}$$

$$I_d = g_m V_i \frac{Y_S}{Y_S + g_m}$$

$$Y_S = \frac{1}{R_S} + j\omega C_S$$

Exact low frequency response of CS amplifier


$$I_d = g_m V_i \frac{Y_s}{Y_s + g_m} \quad Y_s = \frac{1}{R_s} + j\omega C_s$$

After some work, we find:


$$I_d = g_m V_i \frac{\frac{1 + \frac{\omega_z}{j\omega}}{1 + \frac{\omega_s}{j\omega}}}{\frac{1 + \frac{\omega_z}{j\omega}}{1 + \frac{\omega_s}{j\omega}}} \quad \omega_s = \frac{1}{(R_s \parallel 1/g_m) C_s} \quad \omega_z = \frac{1}{R_s C_s}$$

In addition to the expected pole, we find a zero.

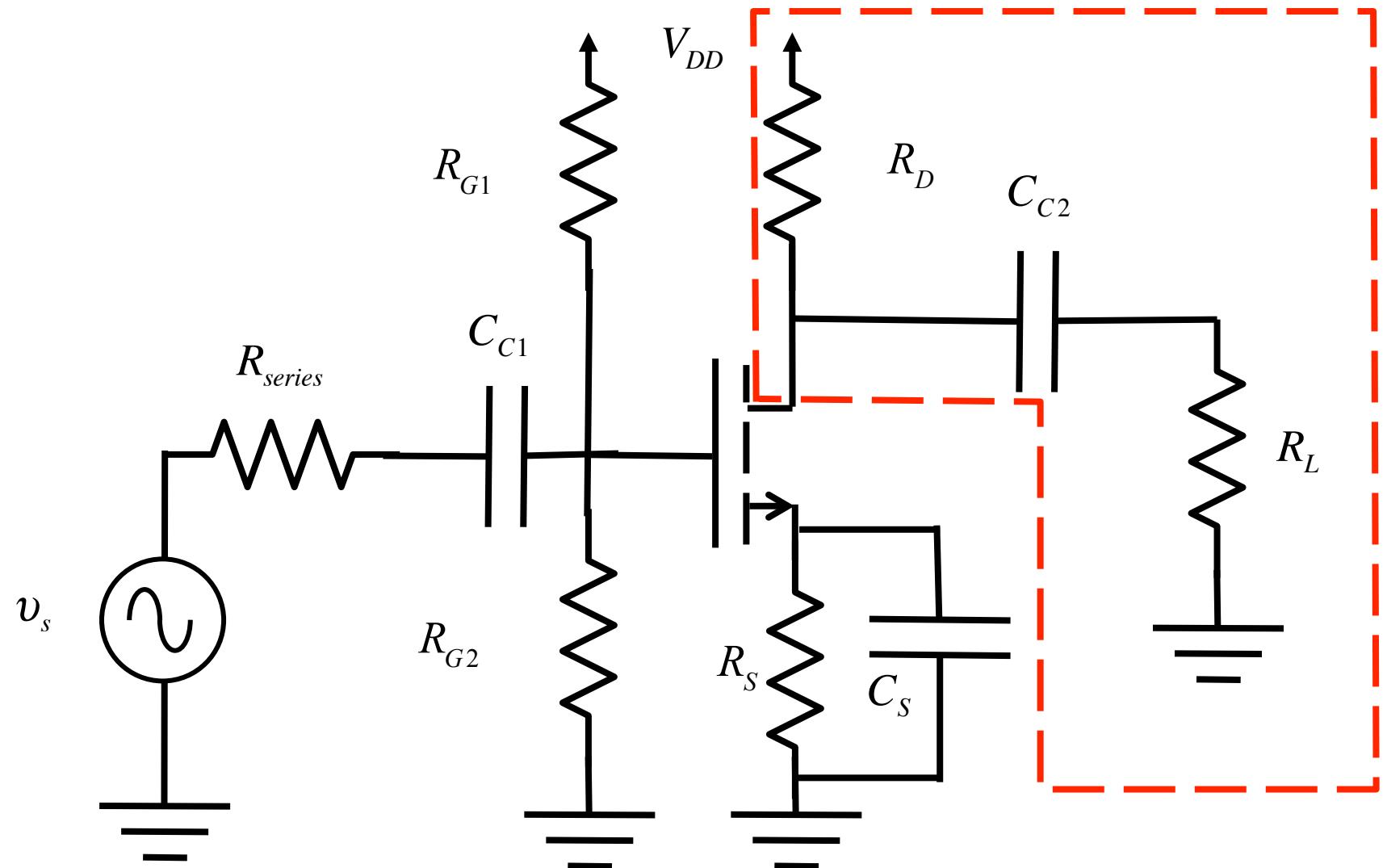Exact low frequency response of CS amplifier



Putting it all together

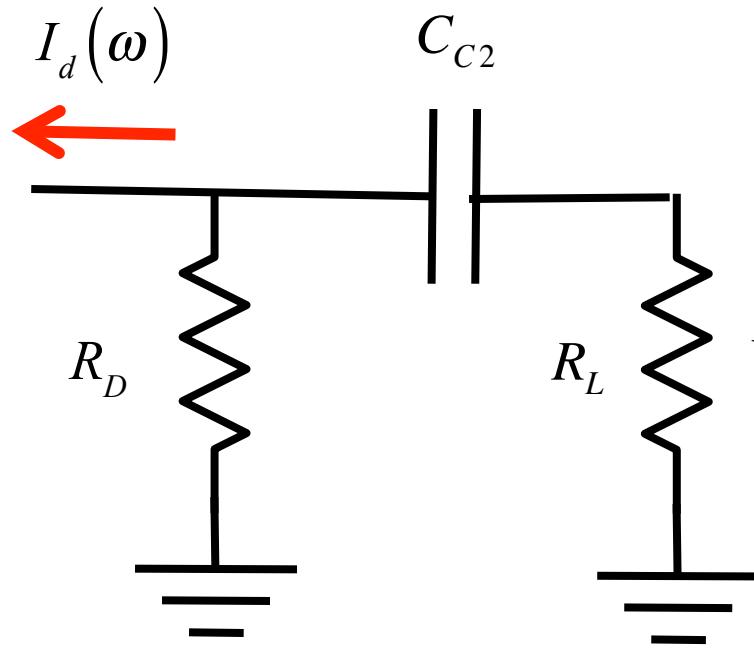

$$I_{R_L}(\omega) = I_d(\omega) \frac{R_D}{R_D + \left(R_L + \frac{1}{j\omega C_{C2}} \right)}$$

$$V_o(\omega) = I_{R_L}(\omega) R_L$$

$$V_o(\omega) = - (R_D \parallel R_L) \frac{1}{1 + \frac{\omega_{C2}}{j\omega}} I_d(\omega)$$

We find the expected pole.

Exact low frequency response of CS amplifier

$$V_o(\omega) = - (R_D \parallel R_L) \frac{1}{1 + \frac{\omega_{C2}}{j\omega}} I_d(\omega)$$

$$I_d(\omega) = g_m \frac{1 + \frac{\omega_z}{j\omega}}{1 + \frac{\omega_s}{j\omega}} V_i(\omega)$$

$$V_i(\omega) = \left(\frac{R_G}{R_G + R_{series}} \right) \frac{1}{1 + \frac{\omega_{C1}}{j\omega}} V_s(\omega)$$

$$\frac{V_o(\omega)}{V_i(\omega)} = A_{v_s}(\omega) = \left(\frac{R_G}{R_G + R_{series}} \right) g_m R_L \parallel R_D \times \frac{1 + \frac{\omega_z}{j\omega}}{\left(1 + \frac{\omega_{C1}}{j\omega} \right) \left(1 + \frac{\omega_s}{j\omega} \right) \left(1 + \frac{\omega_{C2}}{j\omega} \right)}$$

Exact low frequency response of CS amplifier

$$A_{v_s}(\omega) = A_{v_s}(\text{mid}) \frac{1 + \frac{\omega_z}{j\omega}}{\left(1 + \frac{\omega_{c1}}{j\omega}\right)\left(1 + \frac{\omega_s}{j\omega}\right)\left(1 + \frac{\omega_{c2}}{j\omega}\right)}$$

$$A_{v_s}(\text{mid}) = -\left(\frac{R_g}{R_g + R_{\text{series}}}\right) g_m(R_L \parallel R_D)$$

Almost the product of 3 STC responses, but there is an additional zero.

$$\omega_z = \frac{1}{R_s C_s} \ll \omega_s = \frac{1}{(R_s \parallel 1/g_m) C_s}$$

So the zero is not important - it does not affect our conclusions about the LF corner frequency.