

Spring 2019 Purdue University

ECE 255: L8

Modeling Diodes (Sedra and Smith, 4.3-4.4)

Mark Lundstrom
School of ECE
Purdue University
West Lafayette, IN USA

Lundstrom: 2019

PURDUE
UNIVERSITY


Announcements

Exam 1: Thursday, Feb. 7, 6:30 PM, LILY 1105.

(Weeks -1- 4 topics, semiconductors, diodes, BJTs. i.e.
HW1 – HW4.)

Remember: Do the assigned reading **before class!**

Quiz problem

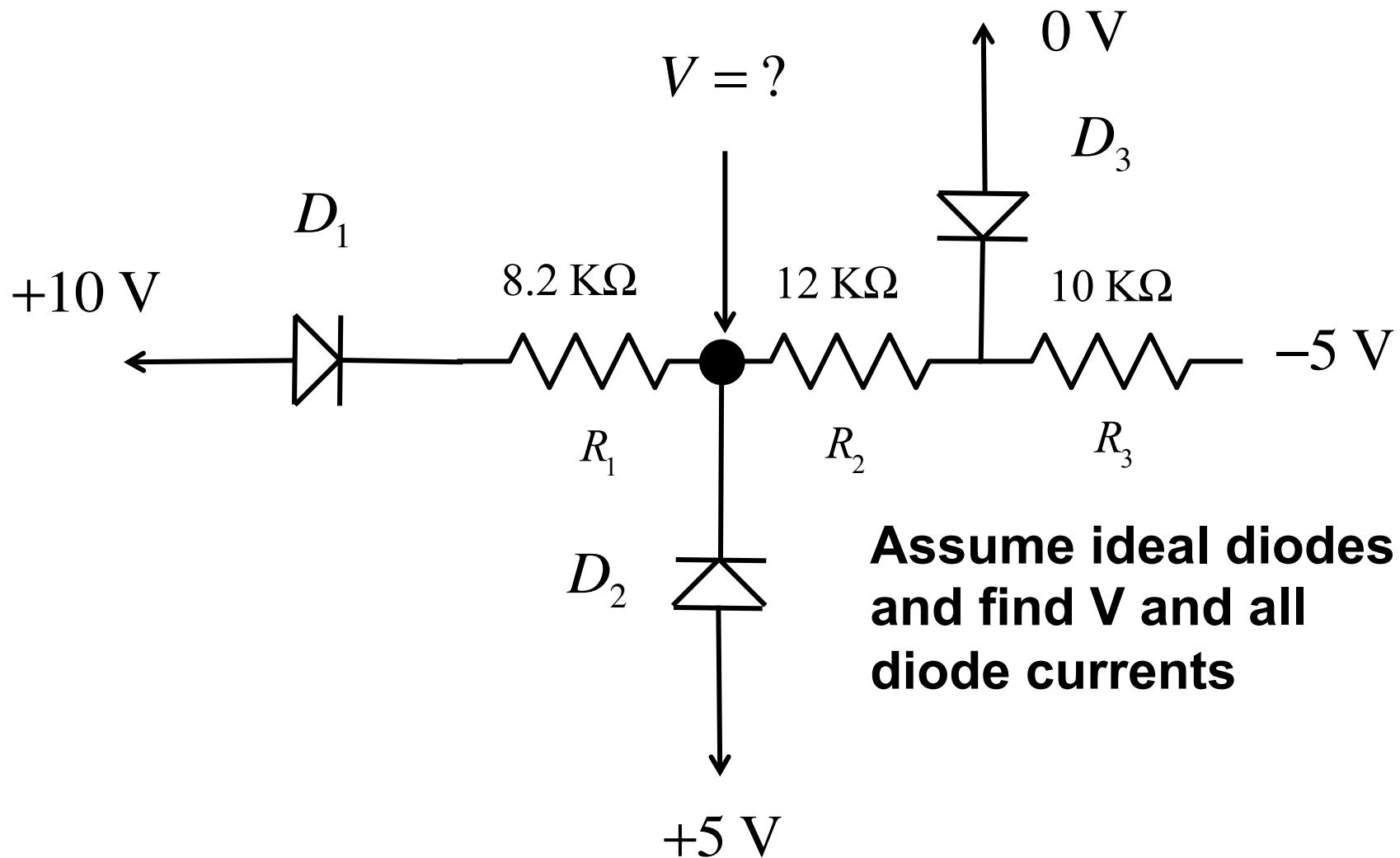

Quiz problem

Guess:

- D1 (FB) **Show why this does not work**
- D2 (FB)
- D3 (FB)

Quiz problem

Guess:

D1 (FB)

D2 (FB)

D3 (FB)

Show why this does not work

Find:

$$IR_1 = (10-5)/8.2K = 0.61 \text{ mA}$$

$$IR_2 = (5-0)/12K = 0.42 \text{ mA}$$

Implies

$$ID_2 < 0$$

D2 is NOT FB

Quiz problem

Guess:

D1 (FB)
D2 (RB)
D3 (FB)

Show that this does work.

Quiz problem

Guess:

D1 (FB)

D2 (RB)

D3 (FB)

Show that this does work.

Find:

$$IR_1 = (10 - 0) / 20.2 \text{ K} = 0.495 \text{ mA}$$

$$V = 10 - 0.495 \times 8.2 = 5.94$$

VD2 < 0 RB



$$IR_3 = (0 - (-5)) / 10 = 0.5 \text{ mA}$$

$$ID_3 = IR_3 - IR_1 - 0.005 \text{ mA}$$

Modeling diodes

- 1) Model parameters
- 2) Exponential model
- 3) Small signal model
- 4) Zener diode model
- 5) Zener diode applications

Three diode models

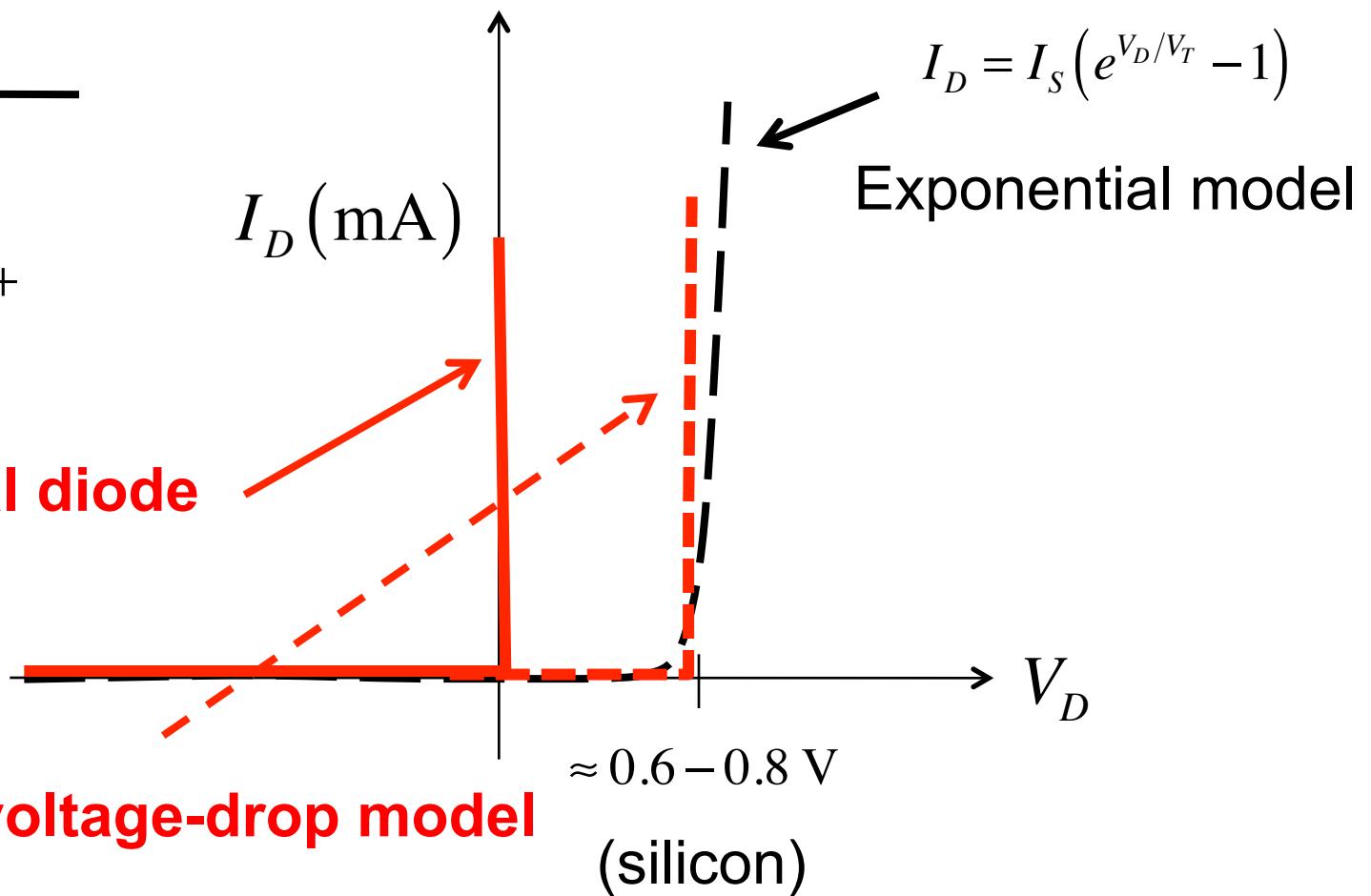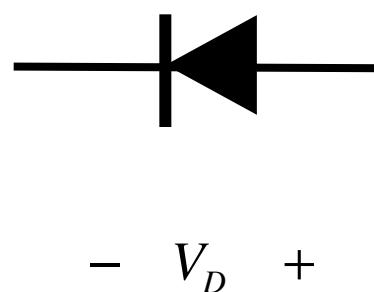

Constant-voltage-drop model
(silicon)

Big idea: Complicated devices can be “simply” modeled. ₉


Model parameters

1) Ideal diode model

No model parameters

2) Constant-voltage-drop
model

One model parameter

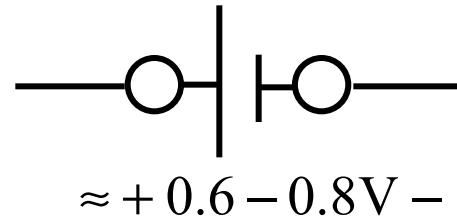

3) Exponential model

One model parameter

$$I_D = I_S \left(e^{V_D/V_T} - 1 \right)$$

Determining model parameters

Question: Given a diode for which we want to model with the exponential equation, how do we determine I_S ?

Answer: Do a measurement at 300 K:

e.g. $I_D(V_D = 0.7 \text{ V}) = 5 \text{ mA}$

What is I_S ?

Computing I_S

$$I_D = I_S (e^{V_D/V_T} - 1) \approx I_S e^{V_D/V_T}$$

$$I_S = I_D e^{-V_D/V_T}$$

$$V_T = k_B T / q = 0.0259 \text{ V}$$

$$I_S = 5 \times 10^{-3} e^{-0.7/0.026}$$

$$I_S = 9.15 \times 10^{-15} \text{ A}$$



But this would not be considered good engineering judgment. Why?

How could we do better?

Determining model parameters

Given a diode for which we want to model with the constant-voltage drop model, how do we determine V_D ?

First, estimate the current that will result in the circuit.

e.g. $I_D \approx 10 \mu\text{A}$

Then do a measurement, or compute V_D if we know I_S .

Determining model parameters

Given: $I_S = 9.15 \times 10^{-15} \text{ A}$

The expected current in the circuit is about 10 microamps.

Find V_D : $I_D = I_S (e^{V_D/V_T} - 1) \approx I_S e^{V_D/V_T}$

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$V_D = 0.026 \ln\left(\frac{10^{-5}}{9.15 \times 10^{-15}}\right) = 0.54 \text{ V} \quad \checkmark$$


Ideal and Real Diodes

- 1) Model parameters
- 2) Exponential model**
- 3) Small signal model
- 4) Zener diode model
- 5) Zener diode applications

A question

How much do we need to
increase V_D to **increase** the
current by 10X?

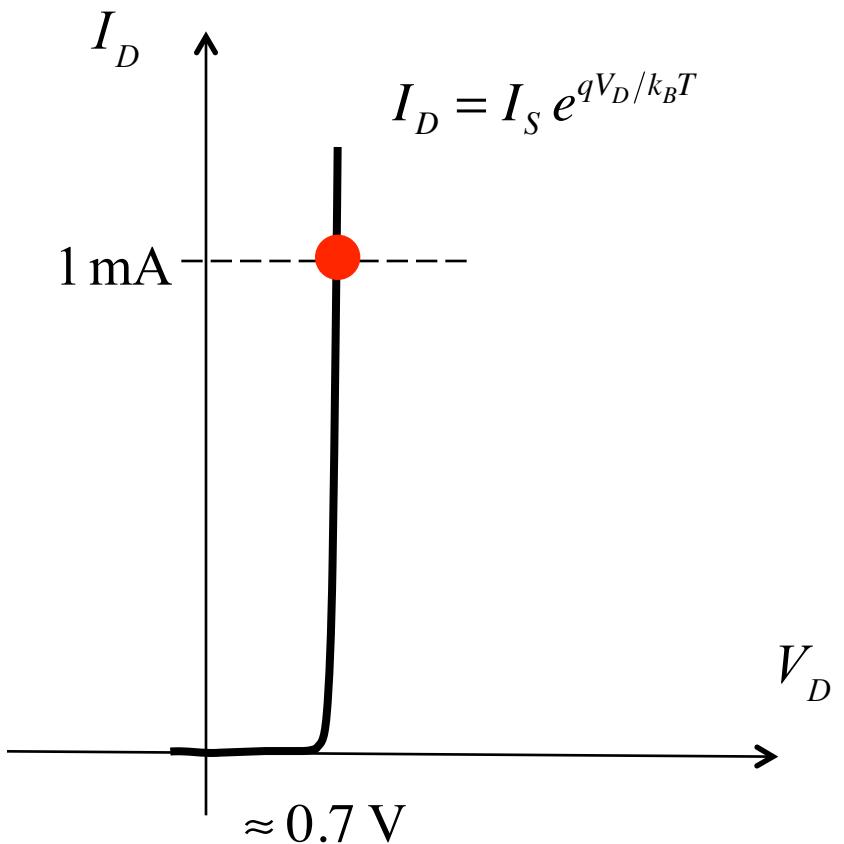How much do we need to
decrease V_D to **decrease** the
current by 10X?



The answer


$$I_{D1} = I_S e^{V_{D1}/V_T}$$

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$\frac{I_{D1}}{I_{D2}} = e^{(V_{D1}-V_{D2})/V_T}$$

$$\Delta V_D = V_T \ln(10)$$

$$\Delta V_D = 60 \text{ mV/decade}$$

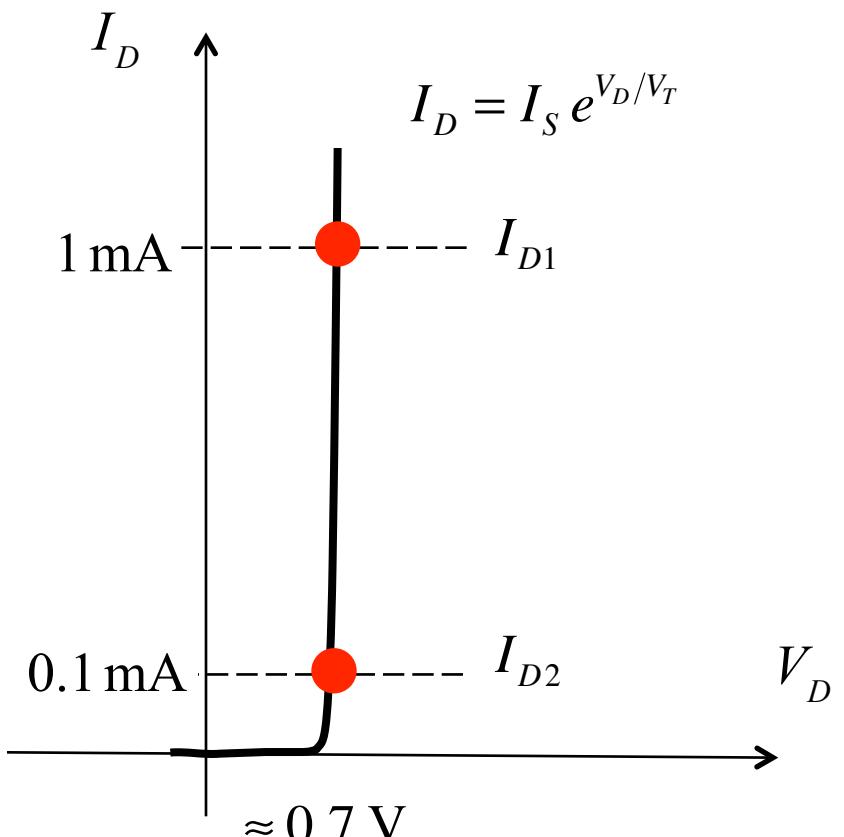


Temperature sensitivity

$$I_{D1} = I_S e^{V_{D1}/V_T}$$

$$I_S \propto n_i^2 \propto e^{-E_G/k_B T}$$

How much does the voltage need to change to keep the current constant if T increases by 1 deg C?


Answer: $\sim -2 \text{ mV/degC}$

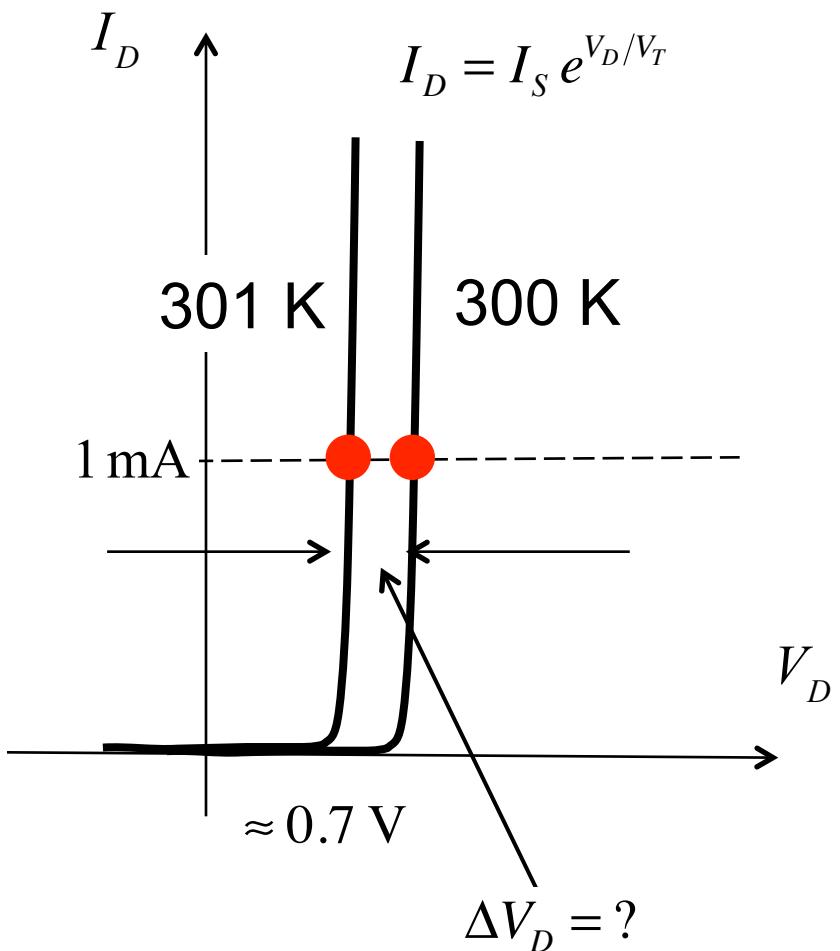

Modeling diodes

- 1) Model parameters
- 2) Exponential model
- 3) Small signal model**
- 4) Zener diode model
- 5) Zener diode applications

Small signal analysis

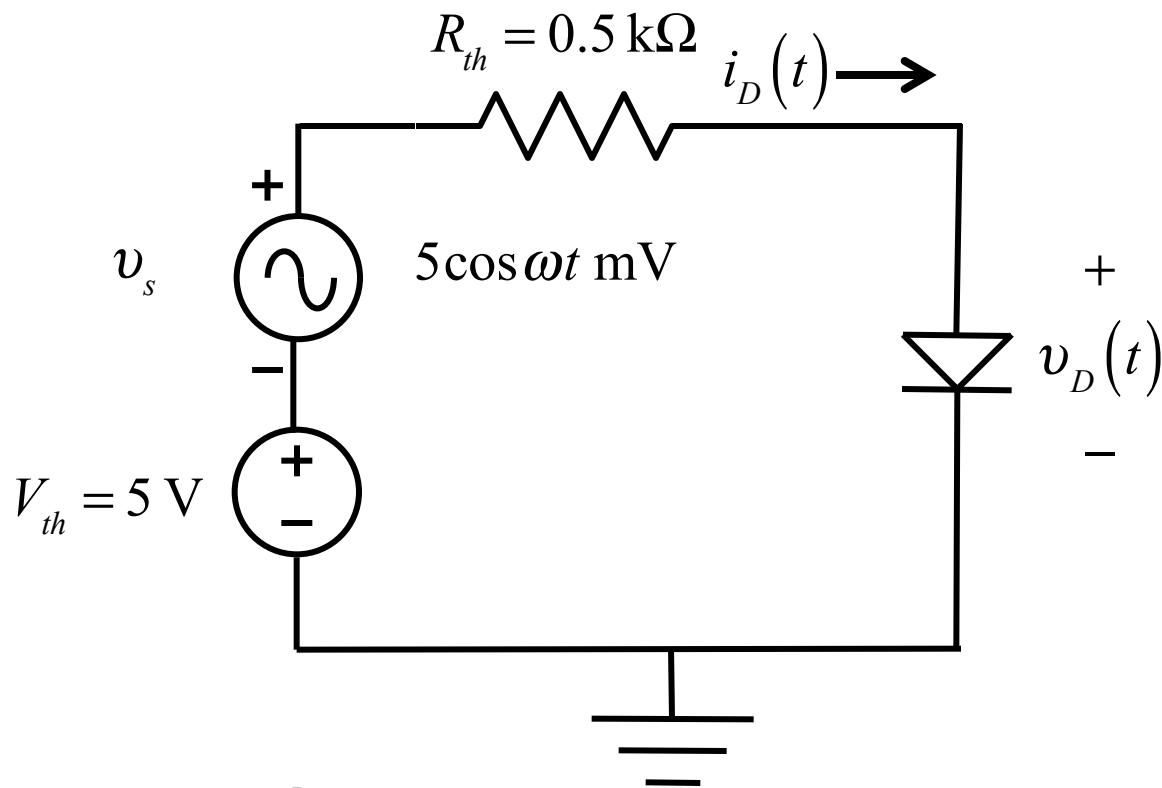

Large signal:


$$i_D(t) = I_S \left(e^{v_D(t)/V_T} - 1 \right) + \mathbf{C's}$$

Notation:

Small letter, capital subscript means the total time varying quantity.

Small signal:

Small signal analysis by equations

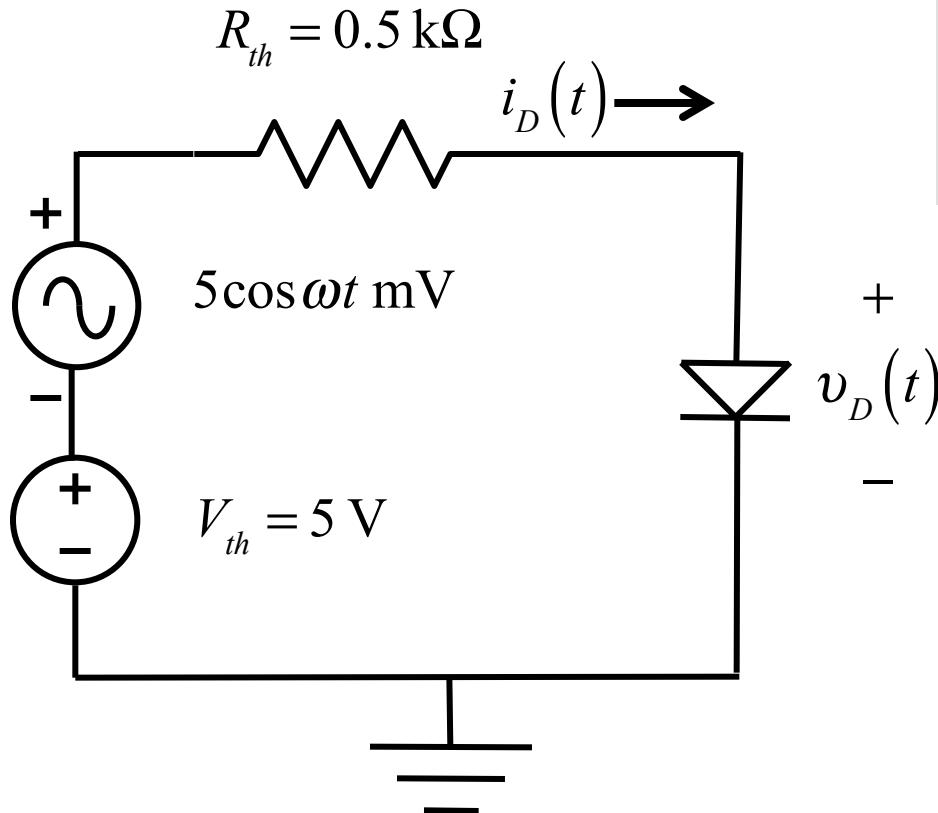

$$e^x \approx 1 + x \quad x \ll 1$$

$$I_D = I_S e^{qV_D/k_B T} = I_S e^{V_D/V_T}$$

$$V_T = k_B T / q = 0.026 \text{ V (300 K)}$$

$$i_D(t) = I_S e^{v_D(t)/V_T}$$

$$v_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_S e^{(V_D + v_d)/V_T}$$


$$= I_S e^{V_D/V_T} e^{v_d/V_T}$$

$$= I_D e^{v_d/V_T}$$

$$\approx I_D \left(1 + v_d/V_T \right)$$

$$v_d \ll V_T = 0.026$$

Small signal analysis by equations

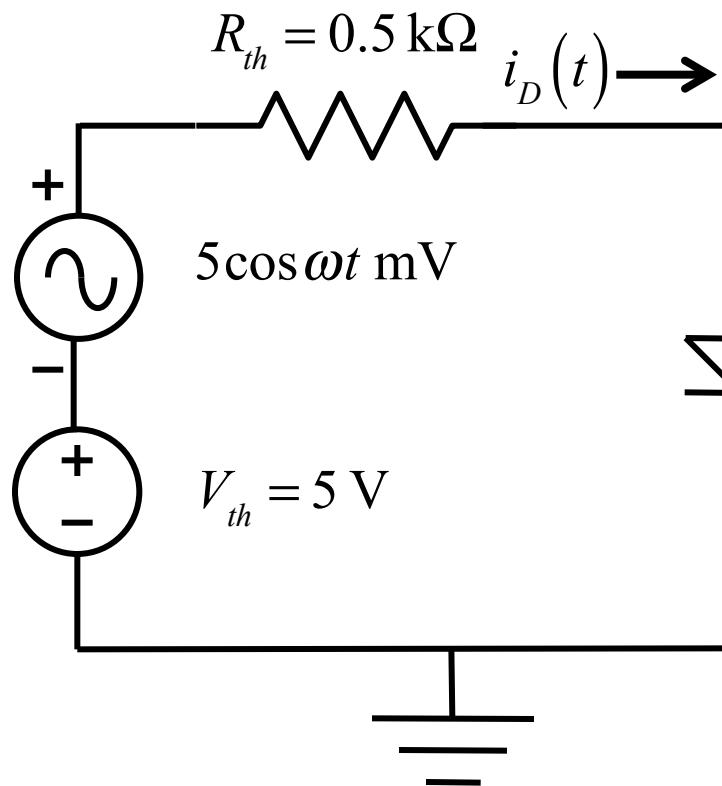

$$i_D(t) \approx I_D \left(1 + v_d / V_T \right)$$


$$i_D(t) \approx I_D + i_d(t)$$

$$i_d = \frac{v_d}{V_T / I_D} = \frac{v_d}{r_d}$$

For small signals, the diode behaves as a resistor. The value of the resistor is determined by the dc current.

$$r_d = V_T / I_D$$

Analysis procedure

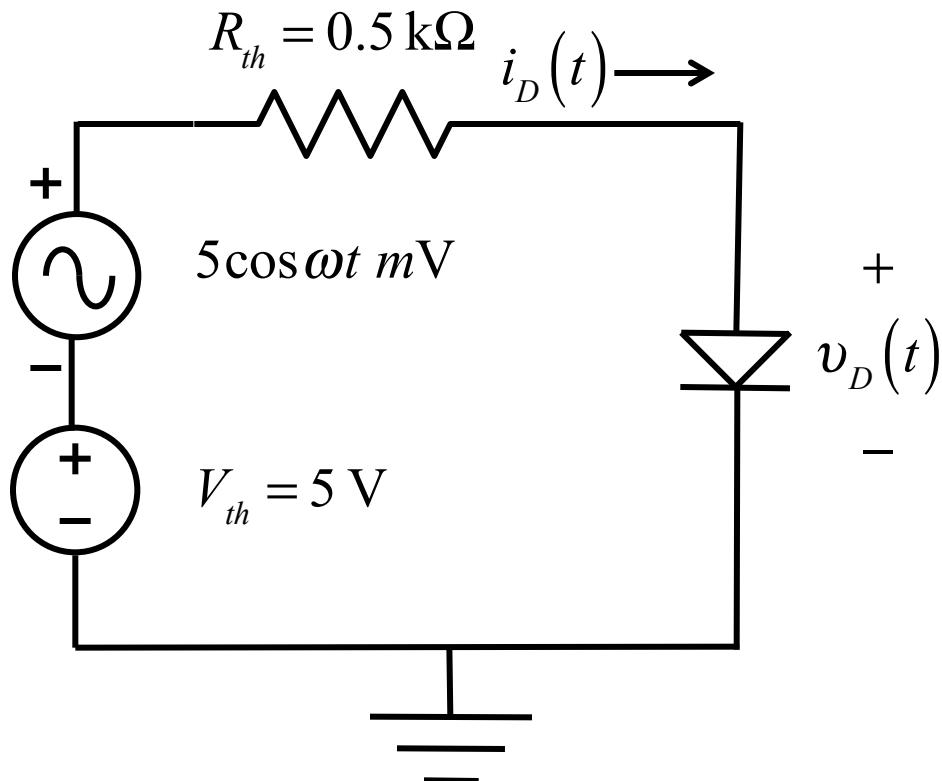

1) Kill the ac source, and analyze the circuit to determine the dc current.

Answer:


$$I_D = 8.61 \text{ mA} \quad V_D = 0.7145 \text{ V}$$

2) Determine the value of the small signal resistor.

$$r_d = V_T / I_D = 0.026 / 8.61 \times 10^{-3}$$

$$r_d = 3.02 \Omega$$

Analysis procedure

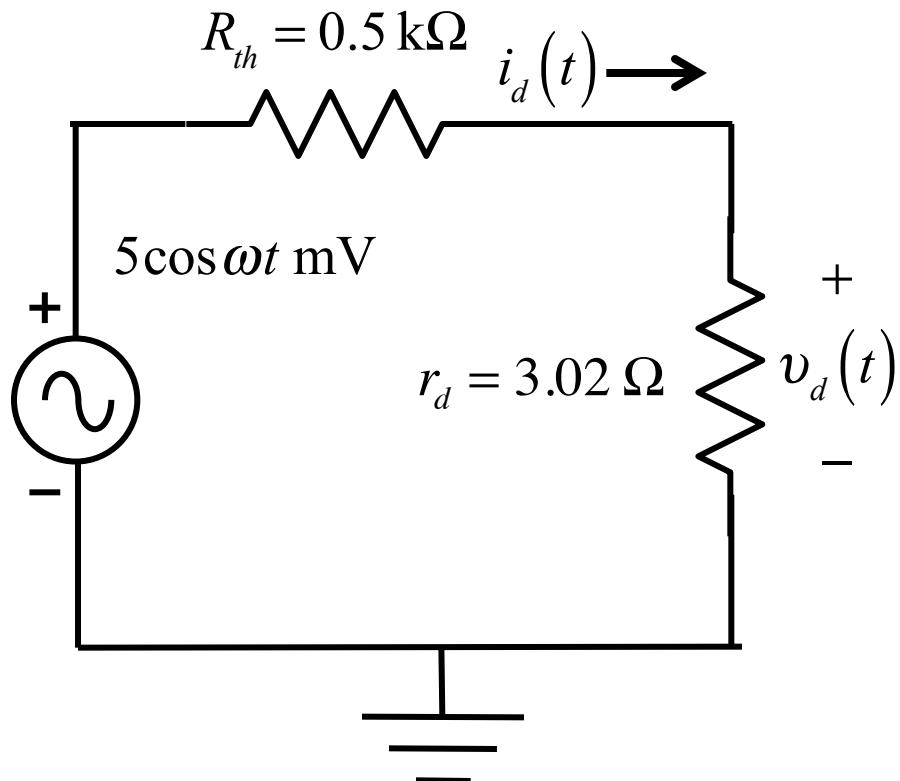

3) Kill the **dc** source, and replace the diode by its ac model (resistor).

4) Ac circuit analysis.


$$v_d = \left(\frac{r_d}{r_d + R_{th}} \right) 5\cos\omega t \text{ mV}$$

$$v_d = \left(\frac{3.02}{503} \right) 5\cos\omega t \text{ mV}$$

$$v_d = 0.03\cos\omega t \text{ mV}$$

$$v_d = 30\cos\omega t \mu\text{V}$$

Analysis procedure

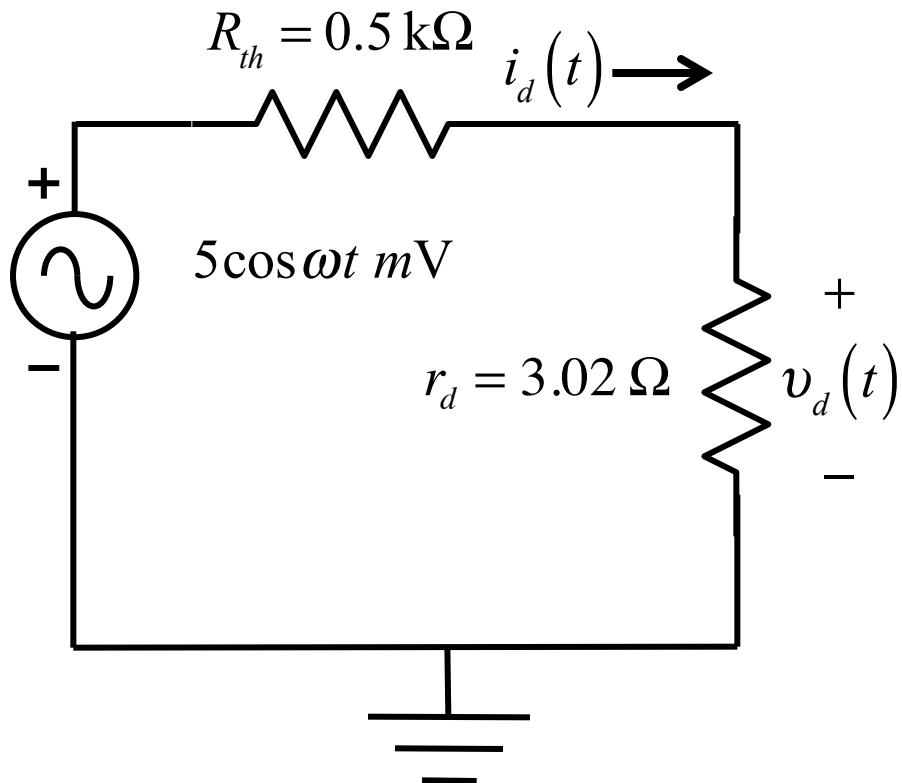


4) ac circuit analysis (cont.)

$$v_d = 30 \cos\omega t \mu\text{V}$$

$$i_d = \frac{v_d}{r_d} = \frac{30 \cos\omega t \mu\text{V}}{3.02 \Omega} = 10 \cos\omega t \mu\text{A}$$

Analysis procedure

5) Add dc and ac.

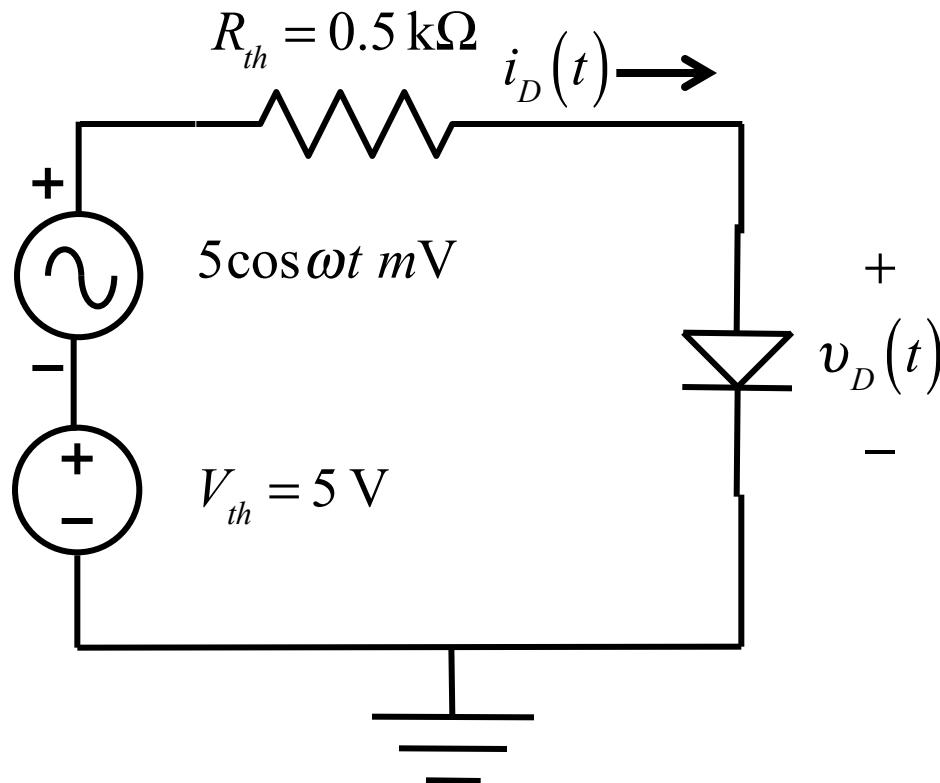


$$i_D(t) = I_D + i_d(t)$$

$$i_D(t) = 8.61 \text{ mA} + 10 \cos \omega t \mu\text{A}$$

$$v_D(t) = V_D + v_d(t)$$

$$v_D(t) = 0.7145 \text{ V} + 30 \cos \omega t \mu\text{V}$$

Graphical picture

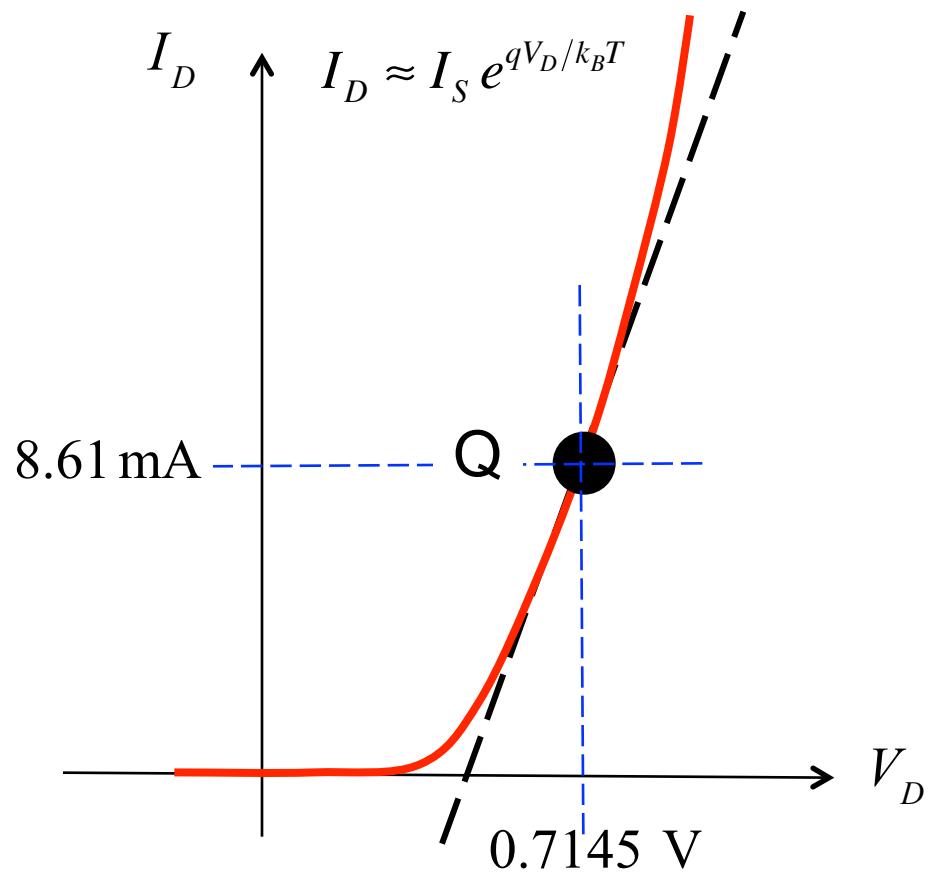

$$g_d = \left. \frac{dI_D}{dV_D} \right|_Q = \frac{\Delta I_D}{\Delta V_D} = \frac{i_d}{v_d} = \frac{1}{r_d}$$



$$r_d = \left(\left. \frac{dI_D}{dV_D} \right|_Q \right)^{-1} = 3.02 \Omega$$

**Set DC bias to get
the r_d needed.**


Modeling Diodes

- 1) Model parameters
- 2) Exponential model
- 3) Small signal model
- 4) Zener diode model**
- 5) Zener diode applications


Recall: ideal voltage source

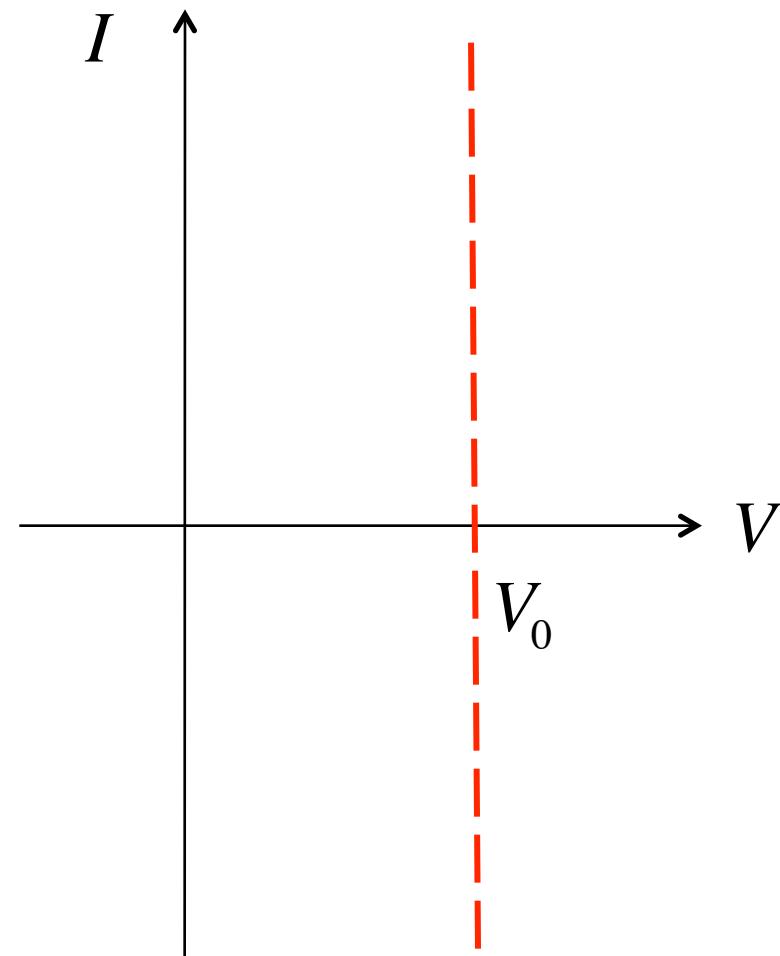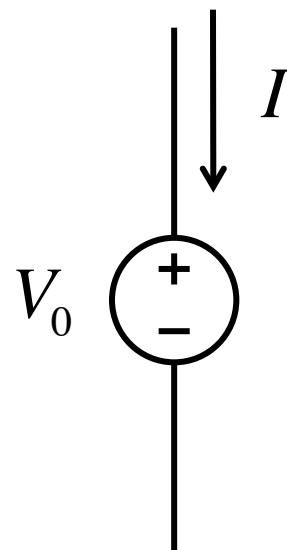


Recall: real voltage source

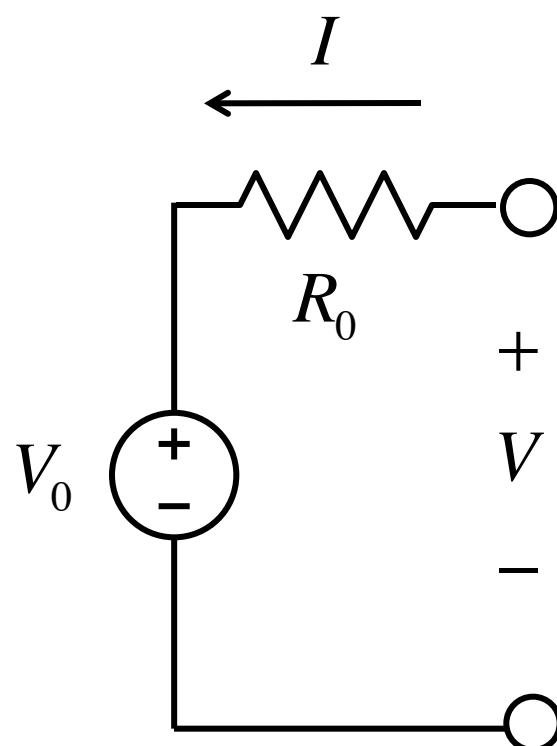


$$V = V_0 + IR_0$$

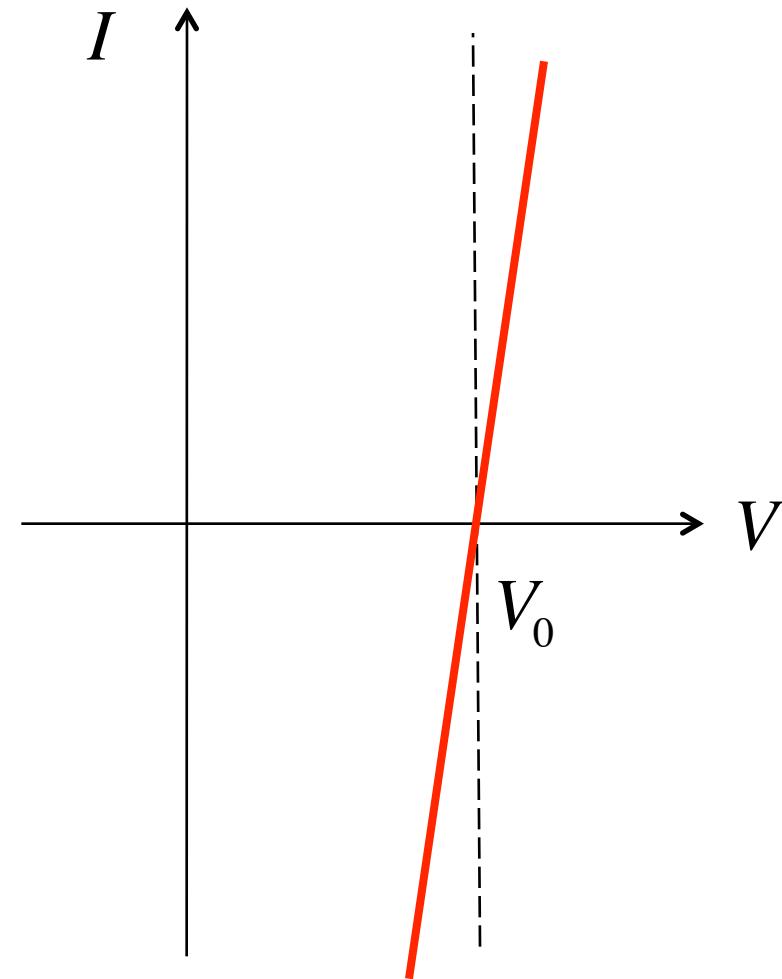


Diode IV: reverse breakdown

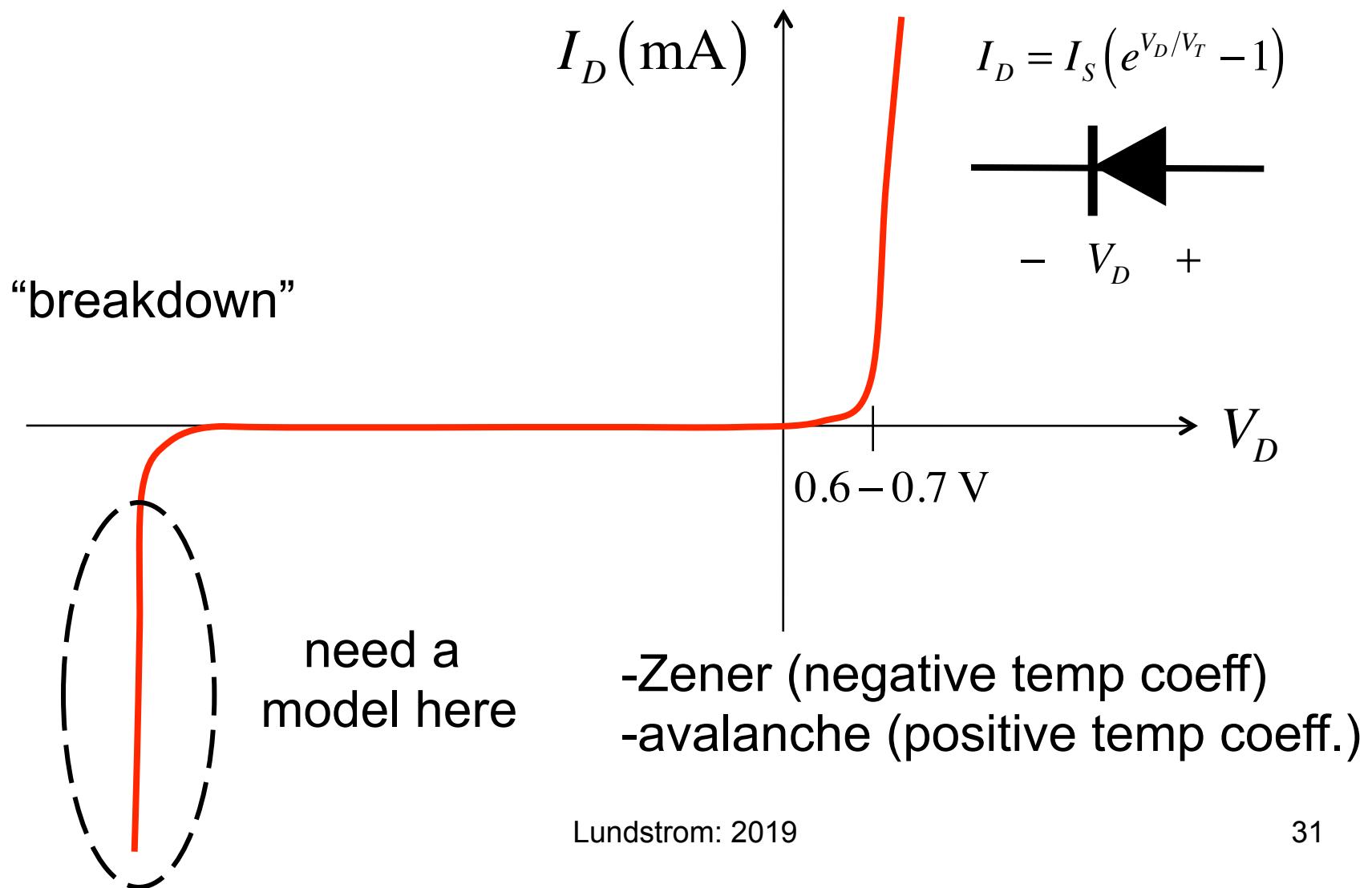

Diode IV: reverse breakdown

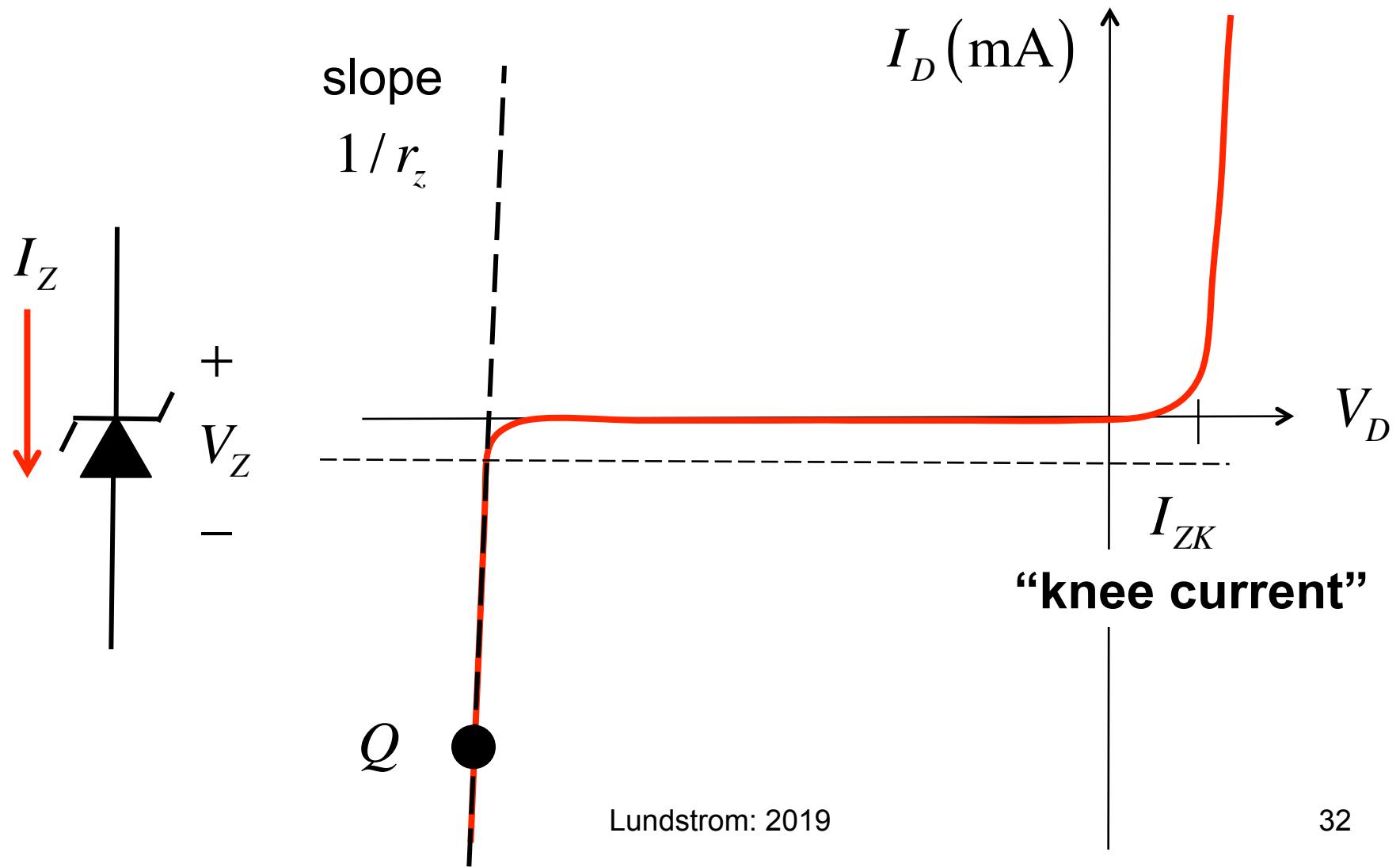

Modeling the Zener diode

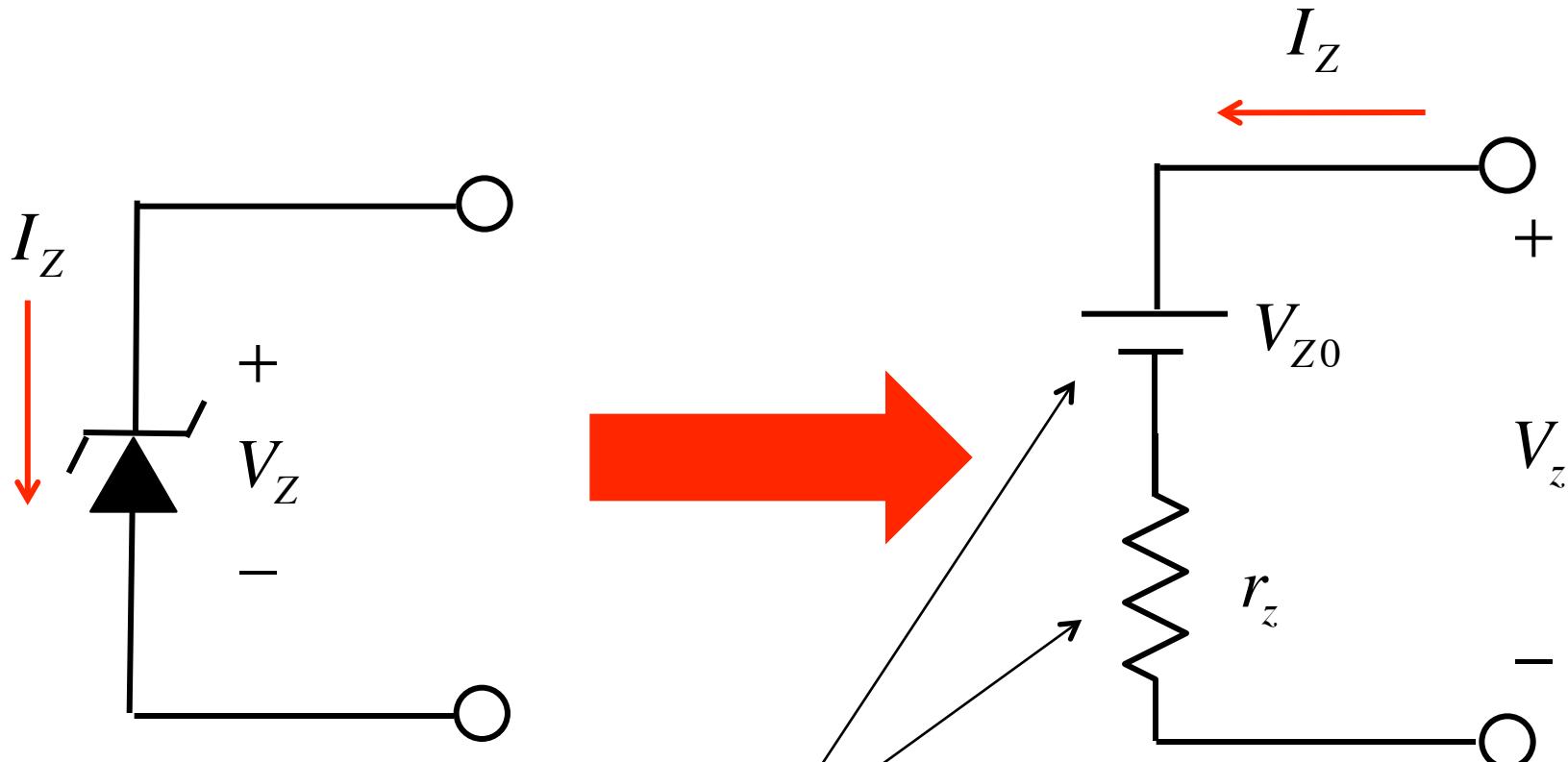

Model
parameters:



Lundstrom: 2019

$$\text{if } V_z > V_{ZK}$$
$$I_Z > I_{ZK}$$


Modeling diodes

- 1) Model parameters
- 2) Exponential model
- 3) Small signal model
- 4) Zener diode model**
- 5) Zener diode applications**

“battery regulator”

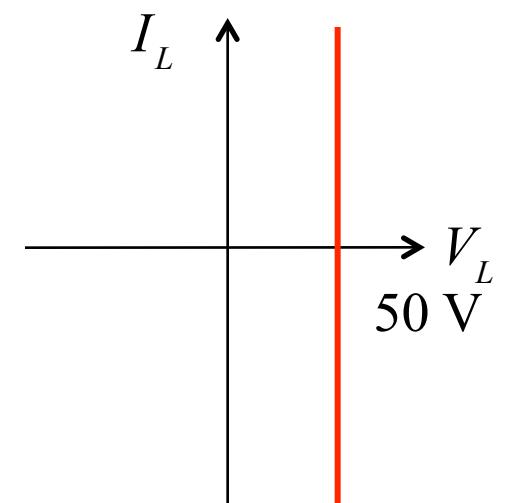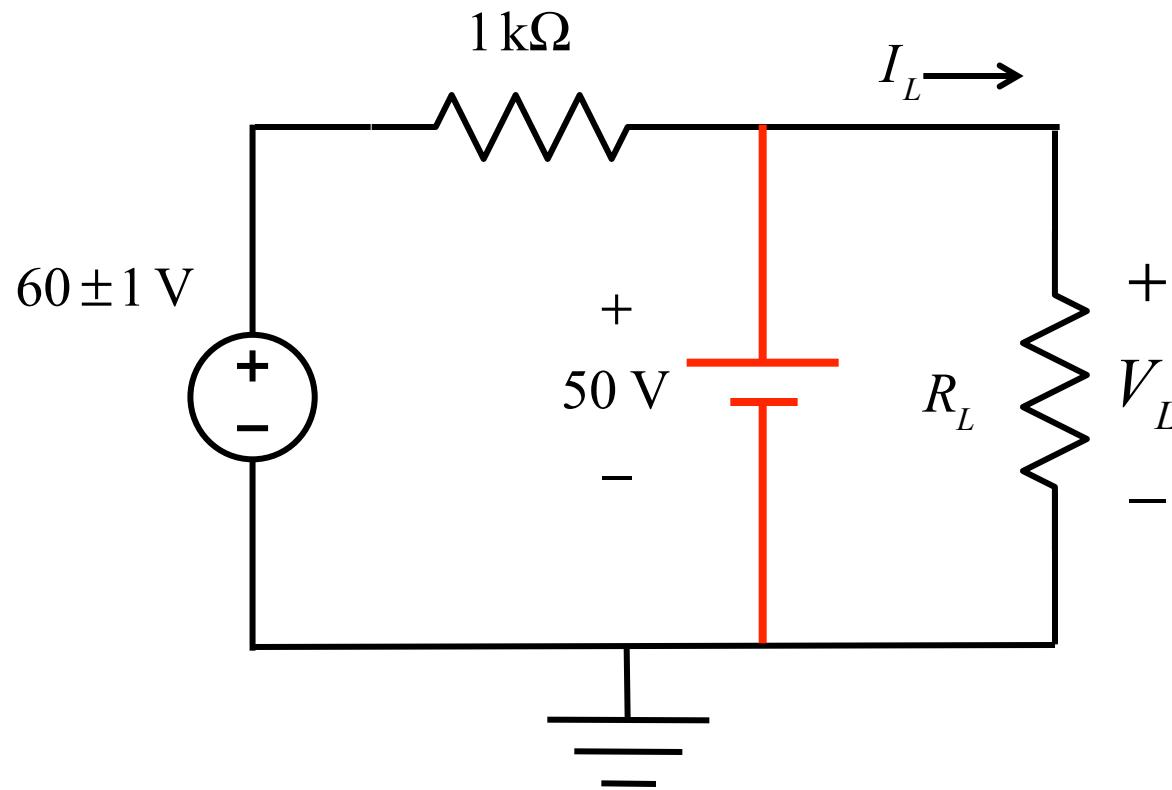

“Zener shunt regulator”

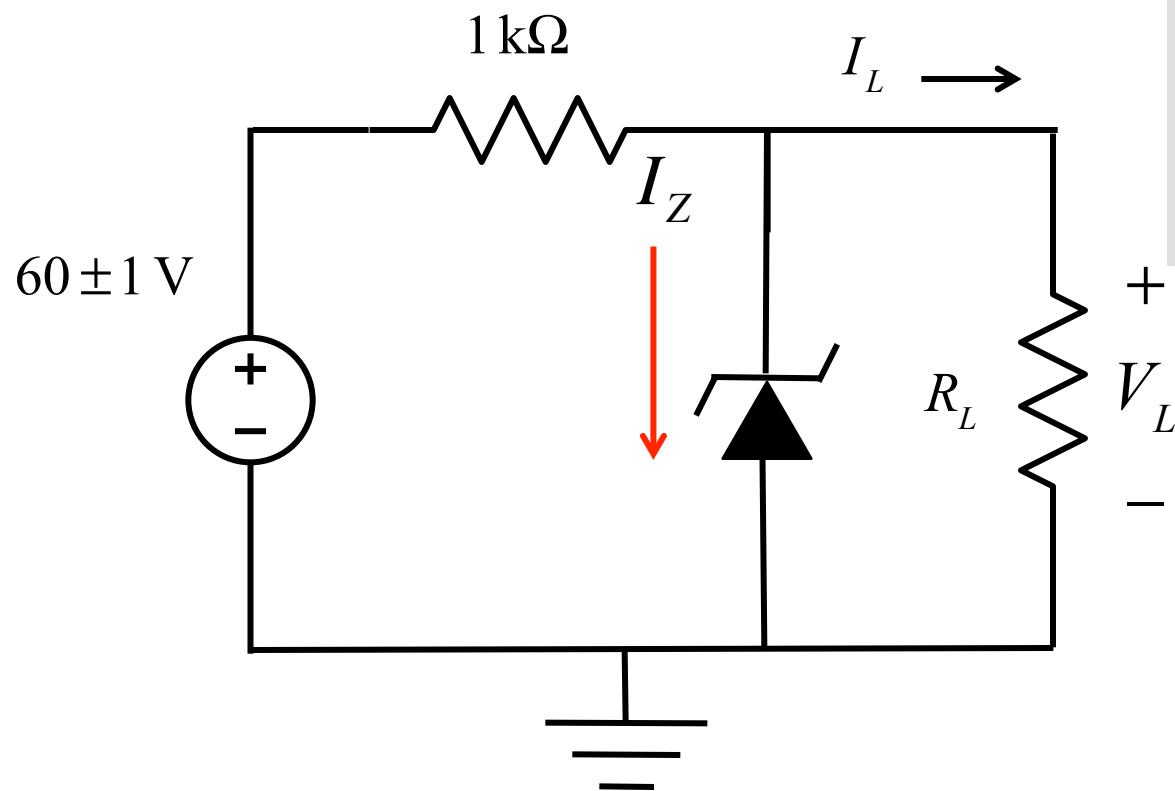


$$V_Z = 50 \text{ V at } I_Z = 50 \text{ mA}$$

$$r_z = 20 \Omega \quad V_{Z0} = ?$$

$$I_{ZK} = 0.3 \text{ mA}$$

At the nominal input voltage, what is V_L when I_L = 0?

Zener diode model

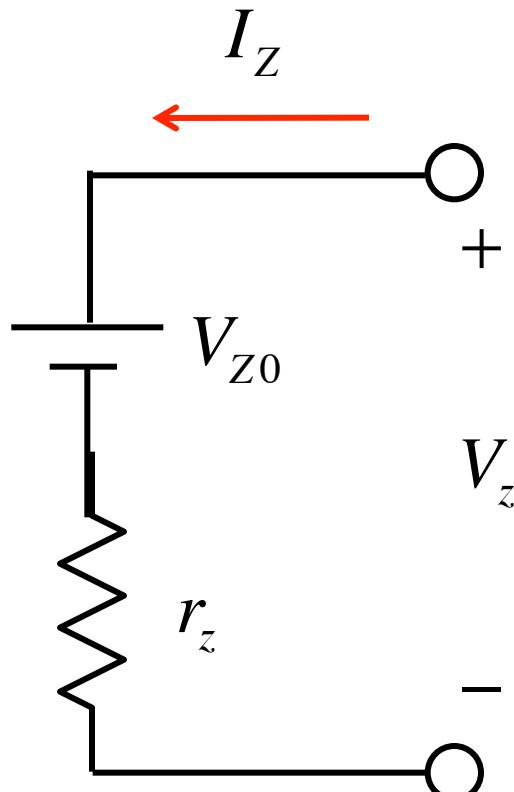

$$V_z = 50 \text{ V at } I_z = 50 \text{ mA}$$


$$r_z = 20 \Omega \quad I_{zK} = 0.3 \text{ mA}$$

$$V_z = V_{z0} + I_z r_z$$

$$\begin{aligned} 50 &= V_{z0} + 50 \text{ mA} \times 20 \Omega \\ &= V_{z0} + 1 \end{aligned}$$

$$V_{z0} = 49 \text{ V} \quad \checkmark$$

Zener shunt regulator

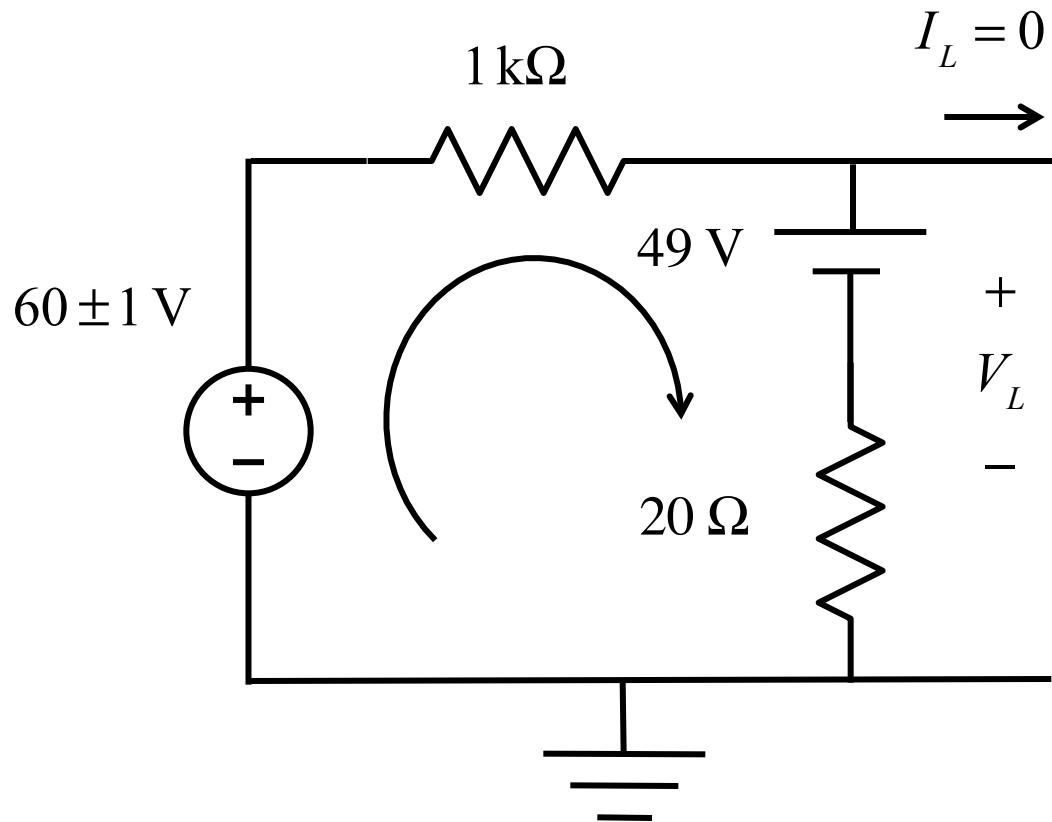


$$I_L = 0$$

$$I_z = \frac{60 - 49}{1 \text{ k} + 0.02 \text{ k}} \\ = 10.8 \text{ mA}$$

$$V_L = 49 + 10.8 \times 0.02 \\ = 49.2$$

At the nominal input voltage, what is V_L when $I_L = 0$?

Regulation

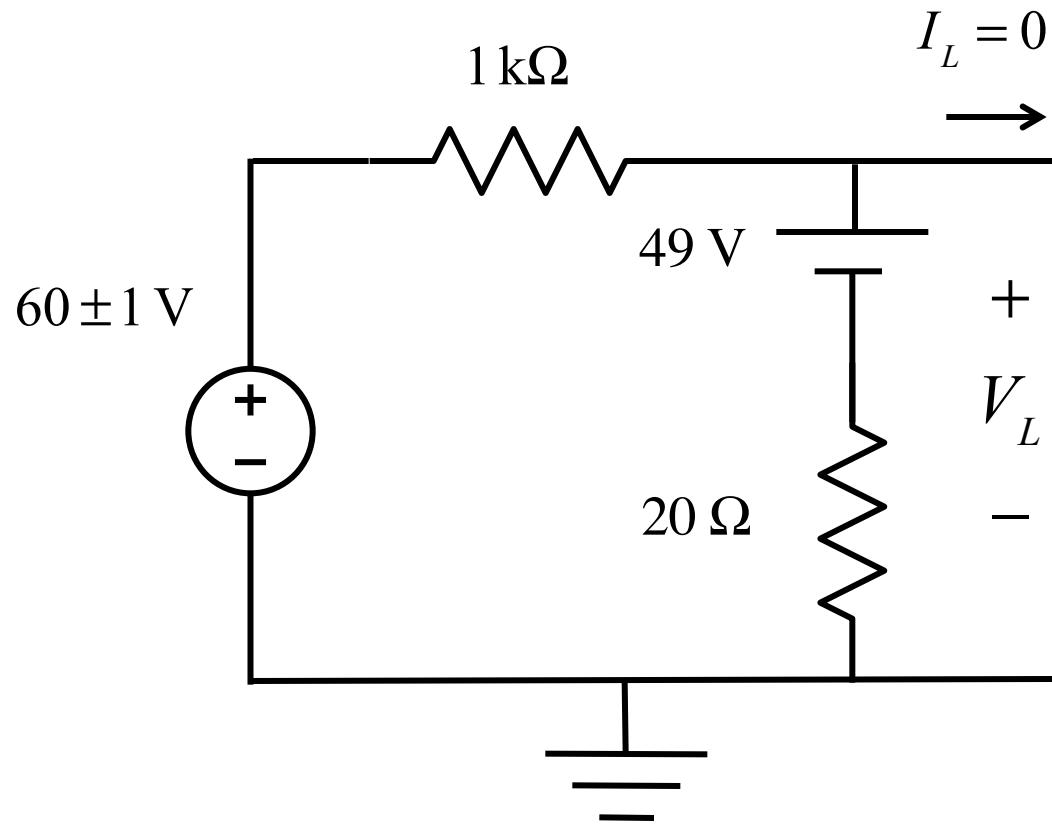

$$\Delta V_L = \Delta V \frac{r_z}{r_z + R}$$

$$\frac{\Delta V_L}{\Delta V} = \frac{r_z}{r_z + R}$$


“line regulation”

$$\frac{\Delta V_L}{\Delta V} = \frac{0.02}{1.02} = 0.02$$

line regulation = 20 mV/V

What is the change in output voltage for a $\pm 1 \text{ V}$ change in input voltage?

“Load regulation”

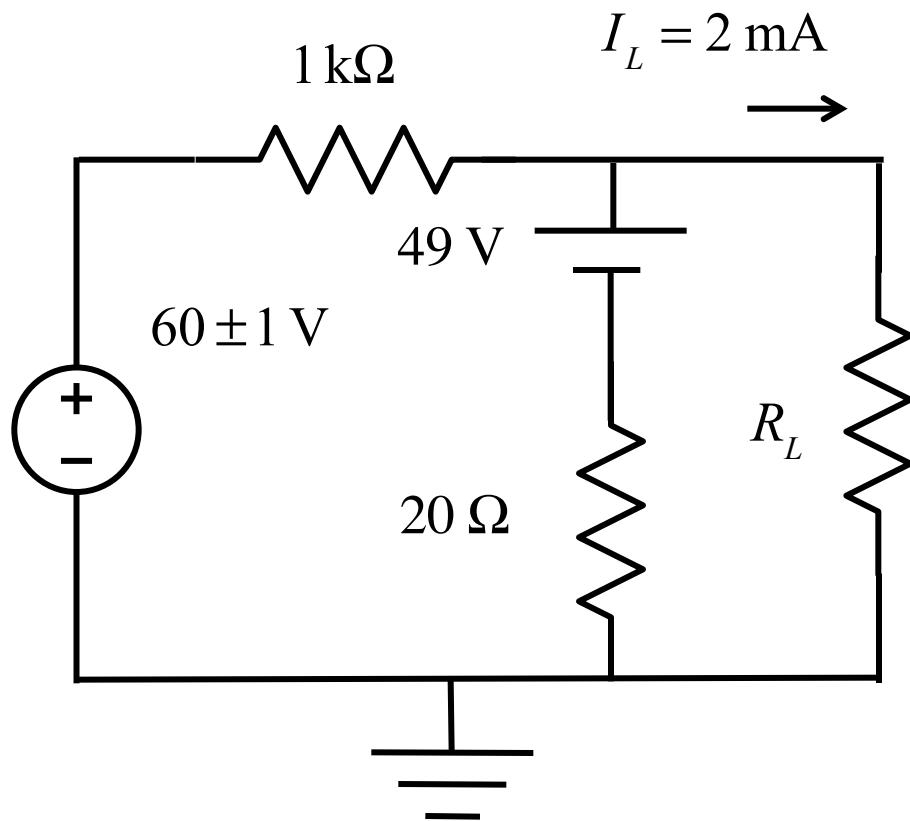


$$\Delta V_L = r_z \Delta I_z = 0.020 \times (-2) = -0.040$$

$$V_L = + \frac{\Delta V_L}{\Delta I_L} = -0.020 \frac{\text{V}}{\text{A}} = -20 \frac{\text{mV}}{\text{mA}}$$

“load regulation”


What is the change in output voltage if the load draws 2 mA of current?

Question

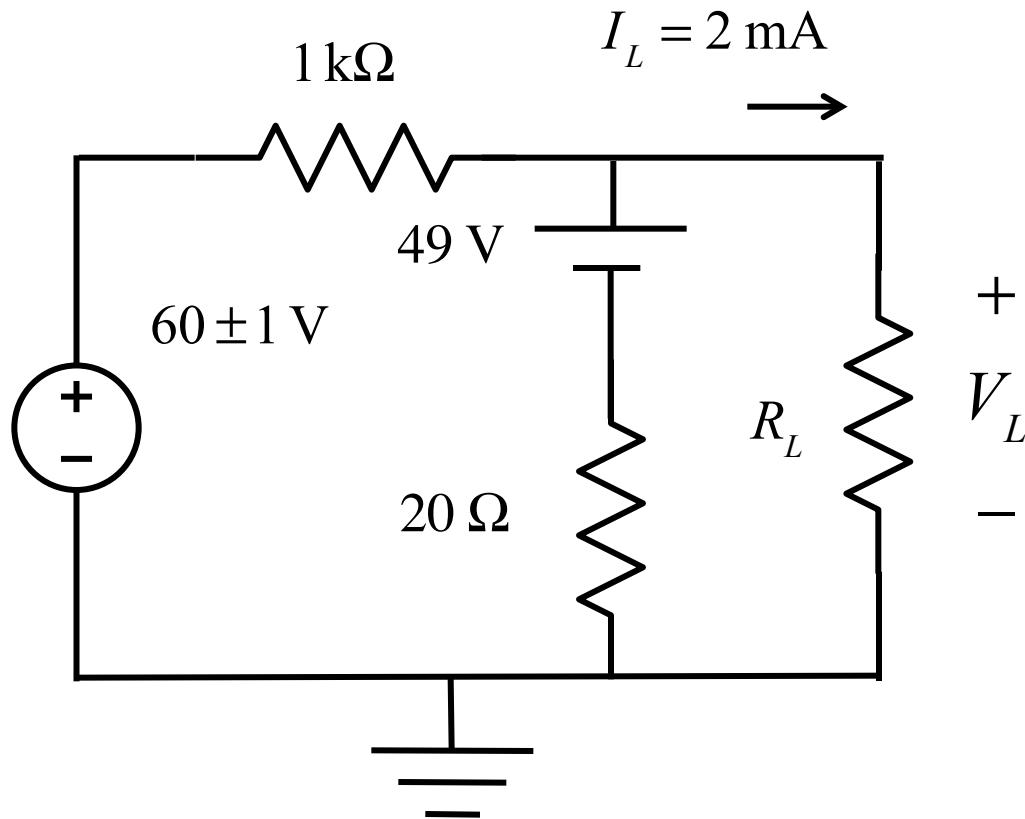

Question: What value of load resistor produces 2 mA of load current?

Maximum load current

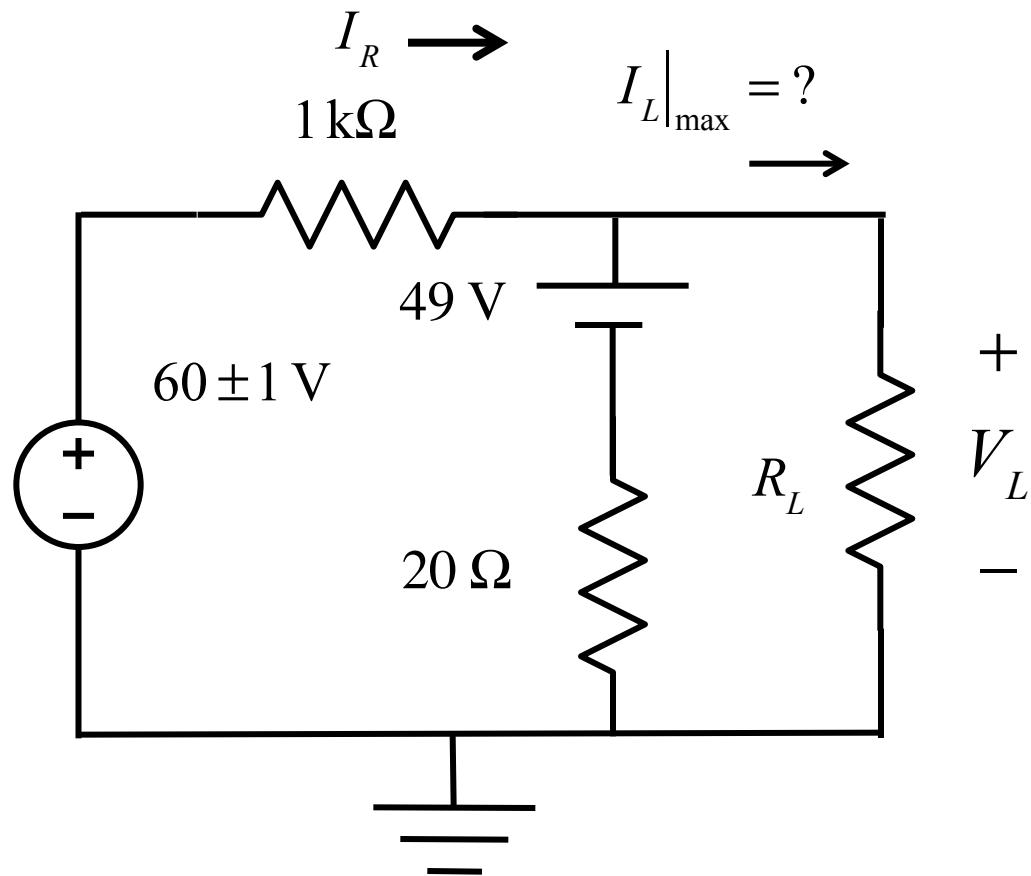

$$I_{ZK} = 0.3 \text{ mA}$$

$$V_L \approx 49 \text{ V}$$

$$I_R \approx \frac{60 - 49}{1 \text{ k}} = 11 \text{ mA}$$

$$I_L|_{\max} = I_R - I_{ZK} = 10.7 \text{ mA}$$

What maximum load current can be drawn if the regulator is to operate properly?

Summary

Model have **model parameters**. To get good results, we need a good model and accurate model parameters.

We discussed three types of diode models: i) ideal, ii) constant-voltage-drop, and iii) mathematical (exponential).

Small signal model parameters depend on the DC bias.

The small signal diode model is a resistor (+ junction and diffusion capacitances).

A good Zener diode in breakdown is like a good battery.

Modeling diodes

- 1) Model parameters
- 2) Exponential model
- 3) Small signal model
- 4) Zener diode model
- 5) Zener diode applications**

