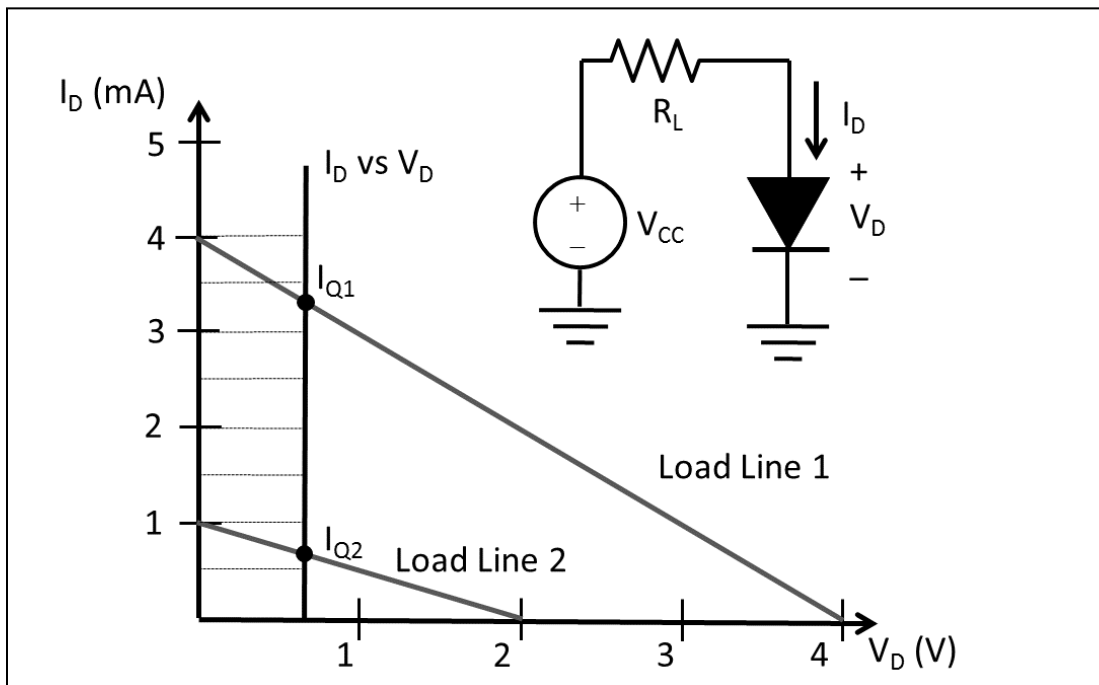


# ECE 255 Spring 2019


## Homework 3

Due 5:00 PM Monday, Jan 28 in MSEE 180 Dropbox


1. Consider a silicon diode that follows an “ideal diode” equation ( $I = I_0 (\exp(V/V_T) - 1)$ ), with  $I_0 = 1e-14$  A. Consider forward-biased operation at room temperature ( $V_T = 0.026$ V). (Note that this is the region that we typically approximate as  $V_D \sim 0.7$  in circuit analysis).
  - a. Determine the current range over which the diode voltage is between 0.65 and 0.75 V. Your solution should include a plot of the current-voltage relationship on a semilog scale ( $\log I$  versus linear V).
  - b. Determine the ratio between the largest and smallest current calculated in part a).
2. Consider the resistor/diode circuit shown below. The I-V plot shows: i) the diode current-voltage relationship (using the  $V_D \sim 0.7$  V approximation) and ii) load lines 1 and 2, representing different values of  $V_{CC}$  and  $R_L$ .
  - a. For load line 1, find the values of  $V_{CC}$  and  $R_L$ .
  - b. For load line 1, find  $I_D$  by reading it off the graph (to the nearest 0.1 mA)
  - c. For load line 1, find  $I_D$  by expressing the load line equation in the form  $y = ax + b$  and using the  $V_D \sim 0.7$  V approximation.
  - d. Repeats parts a) and b) for load line 2.



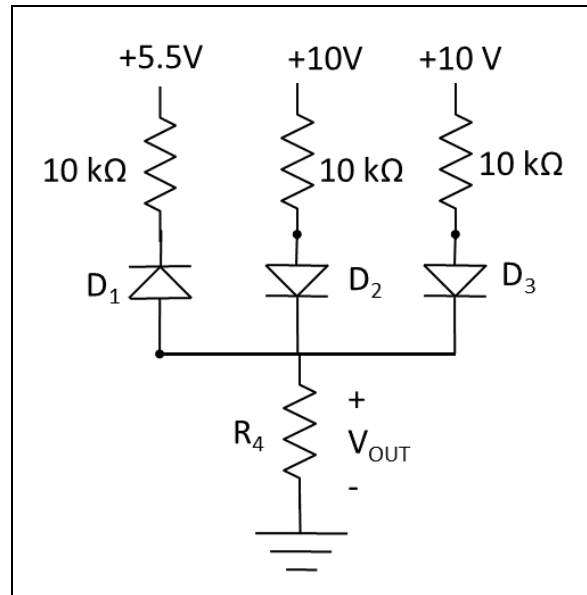3. Consider the circuit shown below. The diodes are all identical, and are general purpose diodes with reverse breakdown voltage  $V_Z > 10V$ . In forward bias, each diode can be modeled using a “constant voltage drop” approximation ( $V_D = 0.7V$ ).




- Consider the case in which  $R_4 = 5 \text{ k}\Omega$  and  $D_1$  is off. What is the value of the output voltage ( $V_{OUT}$ )?
  - Consider the same circuit as in part a), except for the value of  $R_4$ . What is the minimum value of  $R_4$  required in order for  $D_1$  to become forward biased (i.e. for  $V_{D1}$  to be  $0.7V$  or greater, in the polarity corresponding to forward bias)?
4. Consider the clipper circuit shown below, employing two Zener diodes. In forward bias, each diode can be modeled as a standard diode using a constant voltage drop model with  $V_D = 0.7V$ . The Zener voltages for the two diodes are  $V_{Z1} = 4.5V$  and  $V_{Z2} = 5.5V$ . You can assume that the series resistance in the Zener region is negligible.

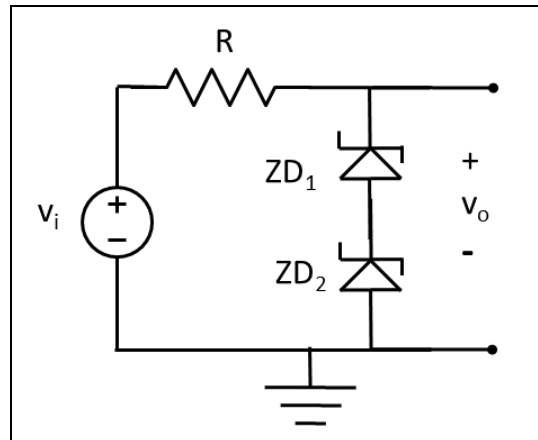

- Consider the case in which  $v_i$  is a DC bias voltage varying from  $-12V$  to  $+12V$ . Find and plot/sketch the output voltage ( $v_o$ ) versus input voltage ( $v_i$ ). You should state the minimum and maximum output voltages.
  - Next, consider the case in which  $v_i$  is a sinusoidal voltage  $v_i = 12V \sin(\omega t)$ . Plot/sketch the input and output ( $v_o$ ) waveforms versus time for two periods of the input sinusoid.
5. (Derived from S&S Problem 4.70). A half-wave rectifier circuit (see Fig. 4.23) with a  $1 \text{ k}\Omega$  load operates from a  $120\text{-V}$  (rms)  $60 \text{ Hz}$  household supply through a  $12\text{-to-}1$  step-down transformer. In forward bias, the silicon diode can be modeled using a  $0.7\text{-V}$  drop for any current.
- What is the peak voltage of the rectified output?
  - For what fraction of the cycle does the diode conduct?
  - What is the average output voltage?
  - What is the average current in the load?
  - Suppose that we place a capacitor ( $C_1$ ) in parallel with the resistor. What value of  $C_1$  is required in order to realize an RC time constant equal to twice the time

interval over which the diode is “off” (determined from your analysis in parts a)-d)). For “R”, you should use 1 k $\Omega$ .

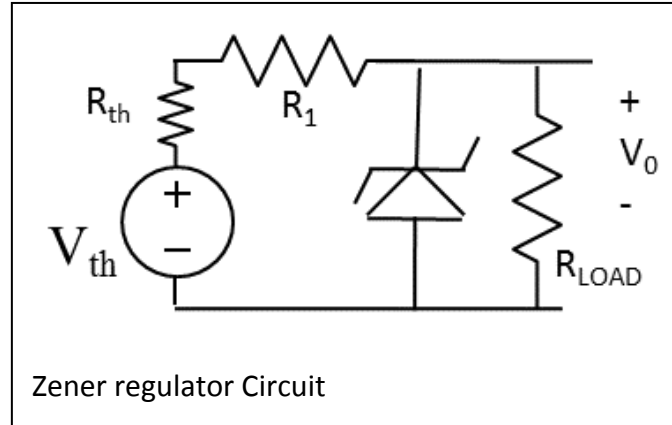6. Consider a Zener diode in a regulator circuit, as discussed in S&S Example 4.7. The Zener diode has  $V_{Z0} = 10\text{V}$  and  $r_z = 25\ \Omega$ .  $R_1 = 400\ \Omega$ . To be consistent with Ex. 4.7, an  $R_{LOAD}$  is shown, but  $R_{LOAD} = \infty$  throughout this problem. The source represents the output of a diode regulator circuit, with  $V_{th} = (16 \pm 1)\text{V}$ .



- a) First consider the case in which  $R_{th} = 0$ . Find the min and max values of  $V_O$  (corresponding to  $V_{th,min} = 15\text{V}$  and  $V_{th,max} = 17\text{V}$ , respectively).
- b) Next, consider the case in which  $R_{th}$  is not zero. What is the maximum value of  $R_{th}$  for which the Zener diode is operating with a current of at least 2 mA over the full range of  $V_{th}$ ? You may assume that the corresponding knee voltage is  $\sim V_{Z0}$ .
- c) The regulating action of the Zener diode can be illustrated using appropriate load lines. Plot/sketch the Zener diode current-voltage relationship in the reverse-bias region – since the diode is “upside down” in the circuit, you can plot this in the first quadrant (i.e. current and voltage are both positive quantities). Plot/sketch load lines corresponding to i) the  $V_{th,min}$  and  $V_{th,max}$  points from part a) and ii) the  $V_{th,min}$  point from part b).

