


ECE 255 Spring 2019

Homework 5

Due 5:00 PM **Monday**, Feb. 17 in EE-209 Dropbox

 1) Consider the BJT bias circuit shown in the figure. Our design goal is $I_C = 1.5 \text{ mA}$ and $V_{CE} = 4 \text{ V}$.

- For $\beta = 100$, what values of R_C and R_B do we need in order to achieve the design goal?
- What are the values of I_B and I_E for the circuit you designed?
- Suppose the value of β increases to 200. Using the values for R_C and R_B that you found in part a), find I_C , I_B , I_E and V_{CE} for this circuit.



2) Consider a modern MOSFET with a gate length of 10 nm and a gate width of 20 nm. Assume a gate insulator with an equivalent gate oxide thickness of 0.5 nm. (This means some insulator with a relative dielectric constant and thickness equivalent to 0.5 nm of SiO₂, which has $\kappa_{ox} = 4$. If the gate voltage is 1.0 V and $V_m = 0.2 \text{ V}$, how many electrons are there in the channel (i.e. how many electrons on one plate of the capacitor)?

3) Use dimensional analysis to show that the expression for drain current,

$$I_D = \frac{W}{L} \frac{\mu_n C_{ox}}{2} (V_{GS} - V_m)^2$$

gives the correct units for current.

HW 5 (continued)

- 4) The table below is for a square law NMOS transistor with $V_{tn} = 1.0$ V. The terminal voltages relative to ground are specified. Identify the region of operation for each case (Cut-off, triode, or saturation). If you encounter a case for which $V_{DS} < 0$, then interchange the source and drain terminals before answering the question. You can do this because MOSFETs are symmetric.

Case	Source	Gate	Drain	Region?
1	+1.0	+1.0	+2.0	
2	+1.0	+2.5	+2.0	
3	+1.0	+2.5	+1.25	
4	+1.0	+1.5	0	
5	0	+2.5	+1.0	

- 5) The table below is for a square law PMOS transistor with $V_{tp} = -1.0$ V. The terminal voltages relative to ground are specified. Identify the region of operation for each case (Cut-off, triode, or saturation). If you encounter a case for which $V_{DS} > 0$, then interchange the source and drain terminals before answering the question. You can do this because MOSFETs are symmetric.


Case	Source	Gate	Drain	Region?
1	+2.0	+2.0	0	
2	+2.5	+1.0	0	
3	+2.0	0	0	
4	+2.0	0	+1.0	
5	+2.0	0	+1.5	

HW 5 (continued)


- 6) An NMOS transistor has a drain current of 0.4 mA at $V_{GS} = V_{DS} = 1$ V and a drain current of 0.1 mA at $V_{GS} = V_{DS} = 0.8$ V. Assuming a square law device, what are the values of k_n and V_m for this transistor?

 - 7) Consider the NMOS circuit shown in the figure to the left. The symbol denotes an enhancement-mode device. Let $V_m = 0.5$ V, $k_n' = 0.1$ mA/V², $W_n = 4$ μ m, $L_n = 1$ μ m and $\lambda = 0$.

- For $R_D = 4$ k Ω , calculate I_D and V_{DS} .
- Calculate the value of R_D for which V_{DS} is at the boundary between the triode and saturation regions.
- Suppose that we increase R_D to 40 k Ω . Find I_D and V_{DS} . Note that you should be able to infer the operating regime by considering your answer to part b).



 - 8) Consider the NMOS circuit shown in the figure to the left. Let $V_m = 0.5$ V, $k_n' = 0.1$ mA/V², $W_n = 4$ μ m, $L_n = 1$ μ m and $\lambda = 0$. Specify the value of the three resistors so that $I_D = 0.2$ mA and $V_{DS} = 2.5$ V.



HW 5 (continued)

- 9) Consider the enhancement-model PMOS circuit shown in the figure to the left. Let $|V_{tp}| = 1.0 \text{ V}$, $k_p' = 0.05 \text{ mA/V}^2$, $W_p = 6 \mu\text{m}$, $L_p = 1 \mu\text{m}$ and $\lambda = 0$. Calculate I_D and V_{SD} for $R_D = 5 \text{ k}\Omega$.

