


ECE 255 Spring 2019

Homework 6


Due 5:00 PM **Monday**, Feb. 24 in EE-209 Dropbox

Note: Throughout this assignment, the use of upper and lower case characters in symbols for voltages and currents is consistent with the text and lecture convention.

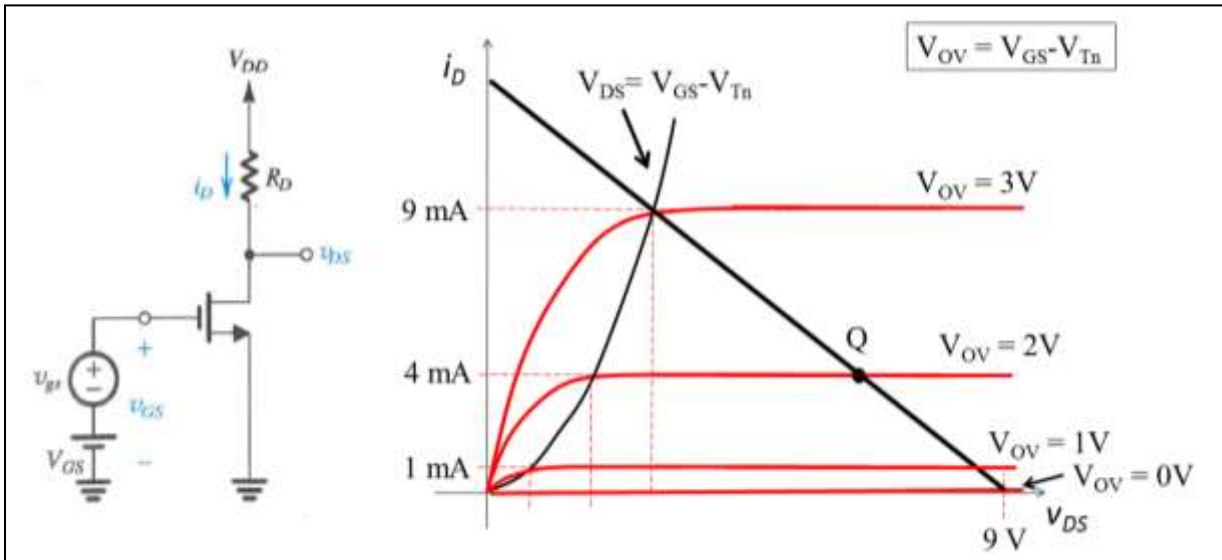- 1) Consider the MOSFET circuit shown below. The MOSFET has $k_n = 2 \text{ mA/V}^2$, $V_{Tn} = 1 \text{ V}$, and $\lambda = 0$. The I-V characteristics and load line corresponding to $R_D = 0.667 \text{ k}\Omega$ and $V_{DD} = 9 \text{ V}$ are shown. The point marked “Q” corresponds to $v_{gs} = 0$ (the “signal” component).



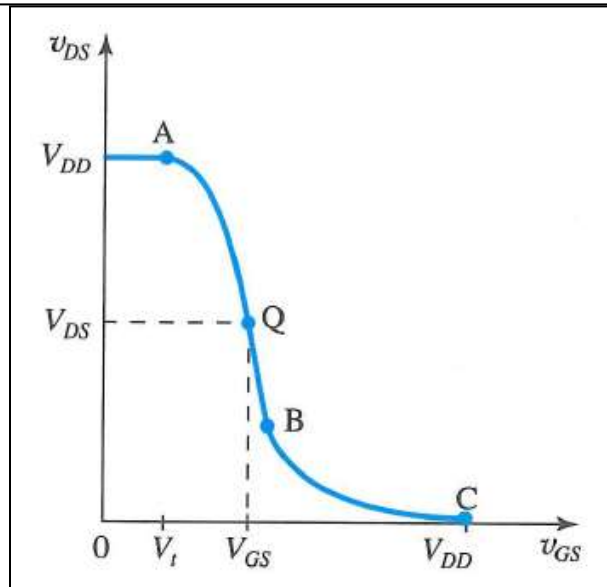- a) Find the gate and drain voltages (V_{GS} and V_{DS}) at the “Q” point.
- b) Calculate the change in value of v_{DS} for $v_{gs} = +0.1 \text{ V}$.
- c) What is the voltage gain ($\Delta v_{DS} / \Delta v_{GS}$) for this circuit?
- d) Consider the transfer curve shown to the right. What are the values of v_{GS} corresponding to points A and B?
- e) Suppose that we apply appropriate V_{GS} to bias the circuit at the Q point from part a), then apply $v_{gs} = v_{sig} \cos(\omega t)$.



What is the maximum value of v_{sig} for which the circuit will remain in the “high gain” region (i.e. between points A and B on transfer curve)?


HW 6 (continued)

2) Consider a NPN BJT with $\beta = 80$ and $V_A = 40V$. The transistor is biased at $I_C = 1 \text{ mA}$ and operates at room temperature in the (forward) active region at $V_{CE} = 2.5V$. For parts a)-d), you should consider the hybrid π model.

- Find the value of r_π .
- Find the value of g_m .
- Find the value of r_o .
- Find the value of r_e (for the T-model)

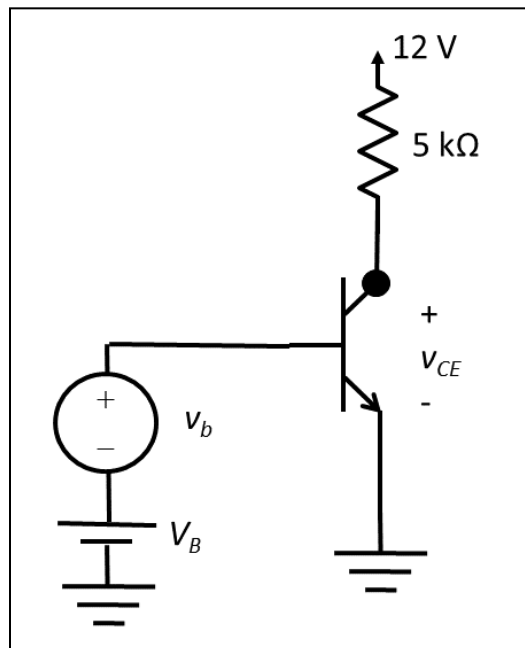3) Consider the BJT circuit shown in the figure below. The transistor has $\beta = 100$. The value of V_B is adjusted such that $I_B = 0.02 \text{ mA}$ and $V_{BE} \sim 0.7V$. For parts a)-d), $V_A = 0$.

- Find I_C and V_{CE} .
- What are the values of r_π and g_m ?
- Draw a small-signal equivalent circuit for the amplifier, showing v_b and v_{ce} .
- Find the voltage gain, v_{ce}/v_b .
- For this part, assume that $V_A = 30 \text{ V}$. Find the value of r_o and the voltage gain. You should assume that I_C and V_{CE} are unchanged.




4) The IV characteristics of an N- and P-MOSFET for the 14 nm technology node are shown on the next page. Note that the NMOS characteristics are shown in the $V_{DS} > 0$ region and PMOS characteristics in the $V_{DS} < 0$ region (with same magnitudes, but negative values, for V_{GS}). The current is normalized by device width, so your result will be expressed in “per micron.” Reading from the graphs as carefully as you can, estimate the average transconductance, g_m , for the two cases below:

- For the N-MOSFET at $V_{DS} = 0.7 \text{ V}$ and for V_{GS} between 0.6 and 0.7 V.
- The corresponding transconductance for the P-MOSFET.

HINT: Note that this is not a square law MOSFET.


HW 6 (continued)

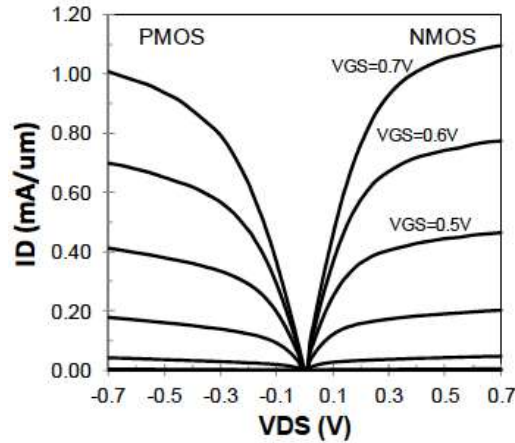

From: S. Natarajan, et al., “A 14nm Logic Technology Featuring 2nd-Generation FinFET Transistors, Air-Gapped Interconnects, Self-Aligned Double Patterning and a 0.0588 um² SRAM cell size,” pp. 70-72. Tech. Digest, Intern. Electron Dev. Mtg, Dec. 2014.

- 5) An enhancement-mode PMOS transistor operating in saturation has $m_p C_{ox} = 250 \text{ mA/V}^2$ and $V_{tp} = -0.5 \text{ V}$. The channel length is $L = 0.5 \text{ } \mu\text{m}$
- Find the value of W that produces $g_m = 2 \text{ mA/V}^2$ at $I_D = 0.5 \text{ mA}$.
 - Find the value of V_{SG} corresponding to this bias point.

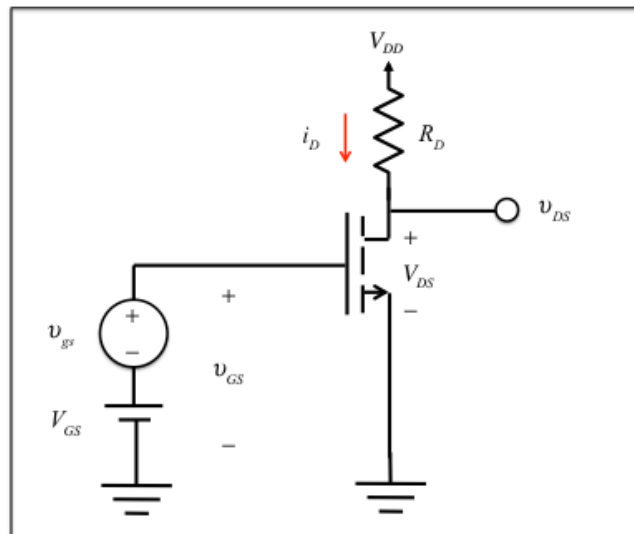- 6) Consider the MOSFET amplifier shown in the figure at the right. Assume a transistor with $k_n = 5 \text{ mA/V}^2$ and $V_{tn} = 0.4 \text{ V}$. Also assume that $V_{GS} = 0.6 \text{ V}$, $V_{DD} = 1.8 \text{ V}$, and $R_D = 10 \text{ kW}$. Answer the following questions.



- Compute I_D and V_{DS}
- Calculate g_m
- Calculate the voltage gain (v_{ds}/v_{gs})
- If $\beta = 0.1 \text{ V}^{-1}$, find r_o and the voltage gain.

HW 6 (continued)

7) Consider the amplifier shown below. All of the capacitors are large – you may assume that they are short circuits to the ac signals and open circuits for dc. The transistor has $k_n = 4 \text{ mA/V}^2$, $V_{in} = 1 \text{ V}$ and $V_A = 100 \text{ V}$. Also assume that $V_{DD} = 1.8 \text{ V}$, and $R_D = 10 \text{ kW}$. Answer the following questions.

- Show that $V_{GS} = 1.5 \text{ V}$, $I_D = 0.5 \text{ mA}$ and that $V_D = 7.0 \text{ V}$
- Find g_m and r_o
- Draw the complete small signal equivalent circuit assuming that all capacitors are short circuits at the signal frequency.
- Find R_{in} , u_{gs}/u_{sig} , u_o/u_{gs} , and u_o/u_{sig}

