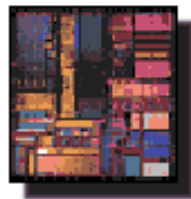




ECE 595Z

Digital Systems Design Automation

Module 2 (Lectures 3-5) : Advanced Boolean Algebra
Lecture 5



Anand Raghunathan
MSEE 348
raghunathan@purdue.edu

Terminology Checklist

- Boolean Algebra
- Boolean Function
- Cube
- Implicant (of a function)
- Minterm
- Cover (of a function)
- Tautology
- Satisfiable / Un-satisfiable
- Sum-of-products
- Minterm canonical representation
- Product-of-sums
- Conjunctive Normal Form
- Disjunctive Normal Form
- Binary Decision Tree
- Binary Decision Diagram
- Symbolic Simulation



Lecture #5 Outline


- Converting between representations - continued
- Co-factors and their applications

Conversion : Example #2

- How do you convert a general Boolean network (multi-level circuit) into a Boolean formula that is linear in the circuit size?
 - Size(formula) = $O(M)$ where M = no. of gates in circuit
 - SOP may be exponential in the worst case
 - Hints
 - Use variables to represent intermediate signals in the circuit
 - Compose the formula using a 1 : 1 mapping from each gate in the circuit into a piece of the formula

Converting a Boolean Circuit into a CNF Formula

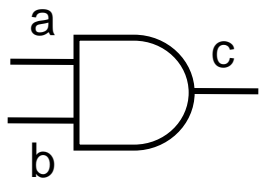- First, let us see how very simple circuits (single gates) can be expressed in CNF form



| | | | |
|---|----------|---|---|
| | | b | |
| | \wedge | 0 | 1 |
| a | 0 | 0 | 0 |
| | 1 | 0 | 1 |

$$c = ab$$

$$\downarrow$$

$$c \rightarrow ab, ab \rightarrow c$$

$$\downarrow$$

$$c \rightarrow a, c \rightarrow b, ab \rightarrow c$$

$$a = 0 \rightarrow c = 0$$

$$b = 0 \rightarrow c = 0$$

$$a = 1, b = 1 \rightarrow c = 1$$

$$\downarrow$$

$$a' \rightarrow c', b' \rightarrow c', ab \rightarrow c$$

$$(a+c')(b+c')(a'+b'+c)$$



Converting a Boolean Circuit into a CNF Formula

- Simple rules for converting various basic gates into CNF equivalent

| Gate Type | Function | CNF Formula |
|-----------|------------|-------------------------|
| NOT | $c = a'$ | $(a+c)(a'+c')$ |
| AND | $c=ab$ | $(a+c')(b+c')(a'+b'+c)$ |
| NAND | $c=a'+b'$ | $(a+c)(b+c)(a'+b'+c')$ |
| OR | $c=a+b$ | $(a'+c)(b'+c)(a+b+c')$ |
| NOR | $c = a'b'$ | $(a'+c')(b'+c')(a+b+c)$ |

Converting a Boolean Circuit into a CNF Formula

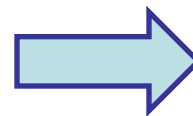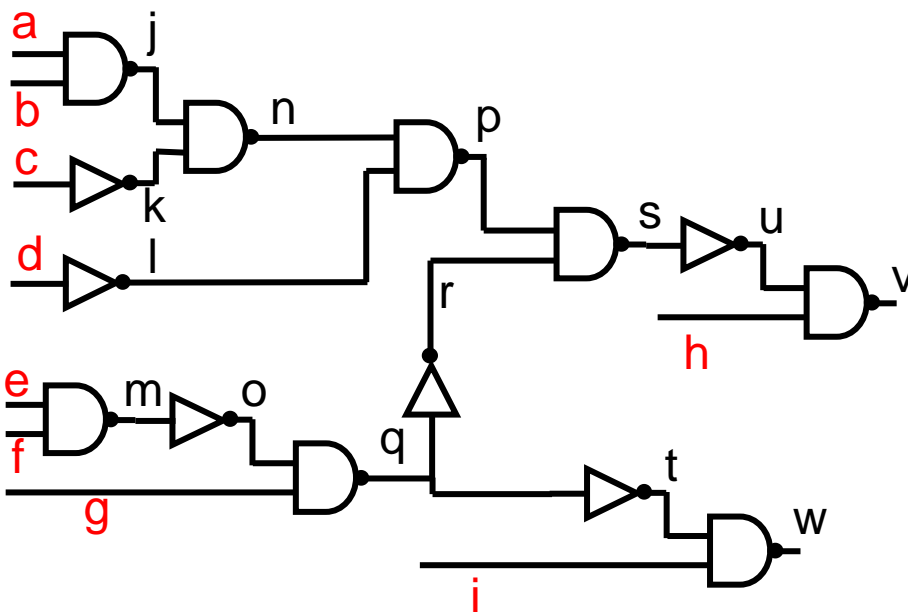- Now, we are ready to convert a multi-level circuit into a CNF formula
 - Simply concatenate formulae representing each of its gates



- $(a+j)(b+j)(a'+b'+j')$
- $(c+k)(c'+k')$
- $(d+l)(d'+l')$
- $(e+m)(f+m)(e'+f'+m')$
- $(m+o)(m'+o')$
- $(j+n)(k+n)(j'+k'+n')$
- $(n+p)(l+p)(n'+l'+p')$
- $(o+q)(g+q)(o'+g'+q')$
- $(q+r)(q'+r')$
- $(p+s)(r+s)(p'+r'+s')$
- $(s+u)(s'+u')$
- $(u+v)(h+v)(u'+h'+v')$
- $(q+t)(q'+t')$
- $(t+w)(i+w)(t'+l'+w')$

Known as the Tseitin Transformation

Co-factors

- A very useful operation on Boolean functions
- Applications of co-factors
 - Shannon's expansion
 - Boolean difference
 - Universal and Existential Quantification

Co-factors of Boolean Functions

- A co-factor of a function is derived by **fixing one of the variables to a constant** (0 or 1), resulting in a new function of $n-1$ variables

- Given a function $f(x_1 \dots x_n)$

- Positive co-factor w.r.t. x_i is defined as

$$f_{x_i} (x_1 \dots x_{i-1}, x_{i+1} \dots x_n) = f(x_1 \dots x_{i-1}, \mathbf{x_i = 1}, x_{i+1} \dots x_n)$$

- Negative co-factor w.r.t. x_i is defined as

$$f_{x_i'} (x_1 \dots x_{i-1}, x_{i+1} \dots x_n) = f(x_1 \dots x_{i-1}, \mathbf{x_i = 0}, x_{i+1} \dots x_n)$$

Examples:

$$f = ab + bc + ac$$

$$f_a = 1.b + bc + 1.c = b + c$$


$$f_{a'} =$$

$$f_b =$$

$$f_{b'} =$$

$$f_c =$$

$$f_{c'} =$$

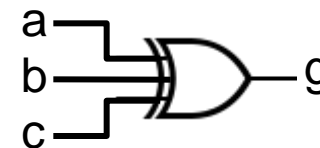

$$g_a =$$

$$g_{a'} =$$

$$g_b =$$

$$g_{b'} =$$

$$g_c =$$

$$g_{c'} =$$

Co-factors of Boolean Functions

- Also called
 - Shannon co-factors
 - Restriction of a function on a variable
- Can be applied on multiple variables
$$f_{x_i x_j'} = f(x_1 \dots x_i = 1 \dots x_j = 0 \dots x_n)$$
- Order does not matter
$$f_{x_i x_j} = (f_{x_i})_{x_j} = (f_{x_j})_{x_i}$$
- Co-factor w.r.t. a cube

Examples:


$$f = ab + bc + ac$$

$$f_{ab} =$$

$$f_{ab'} =$$

$$f_{a'b'c'} =$$

$$f_{ab'c} =$$

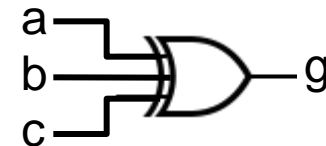

$$g_{ab} =$$

$$g_{a'b} =$$

$$g_{b'c'} =$$

$$g_{abc'} =$$

OK, so why do we need Co-factors?

- Many applications... for example
- Recall **Taylor series** from high-school math?


- A representation of a (real or complex) function as a sum of polynomial terms ($1, x, x^2, x^3, x^4, \dots$)

- $e^x = 1 + x + x^2/2! + x^3/3! + \dots$

- General form:

$$f =$$

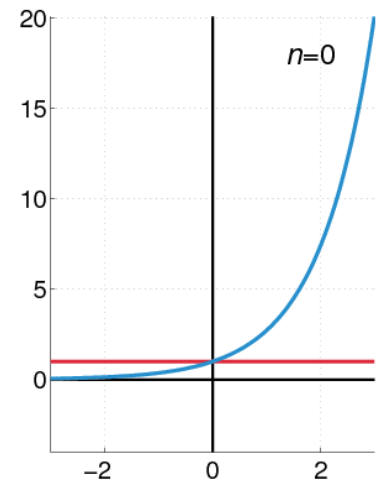- Question: Is there a similar concept for Boolean functions?




Animation of Taylor series for e^x
(Source: Wikipedia)

Shannon's Expansion Theorem

- Given a Boolean function $f(x_1 \dots x_n)$ and any variable x_i


$$f = x_i f_{x_i} + x_i' f_{x_i'}$$

Structural view of
Shannon Expansion

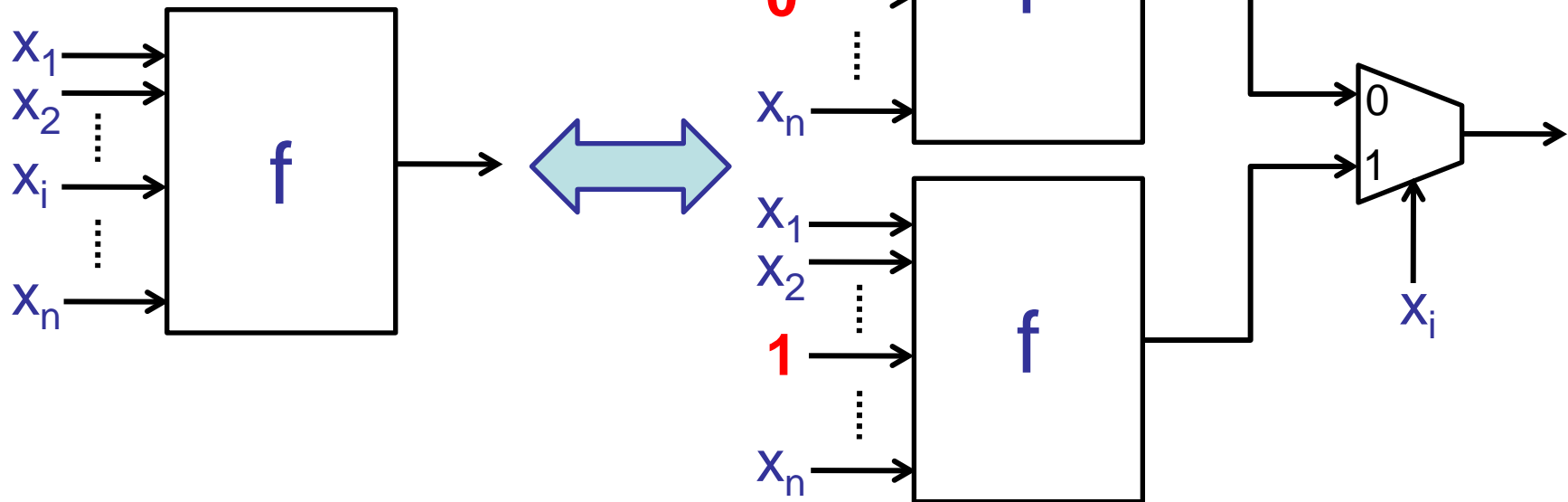

Shannon Expansion

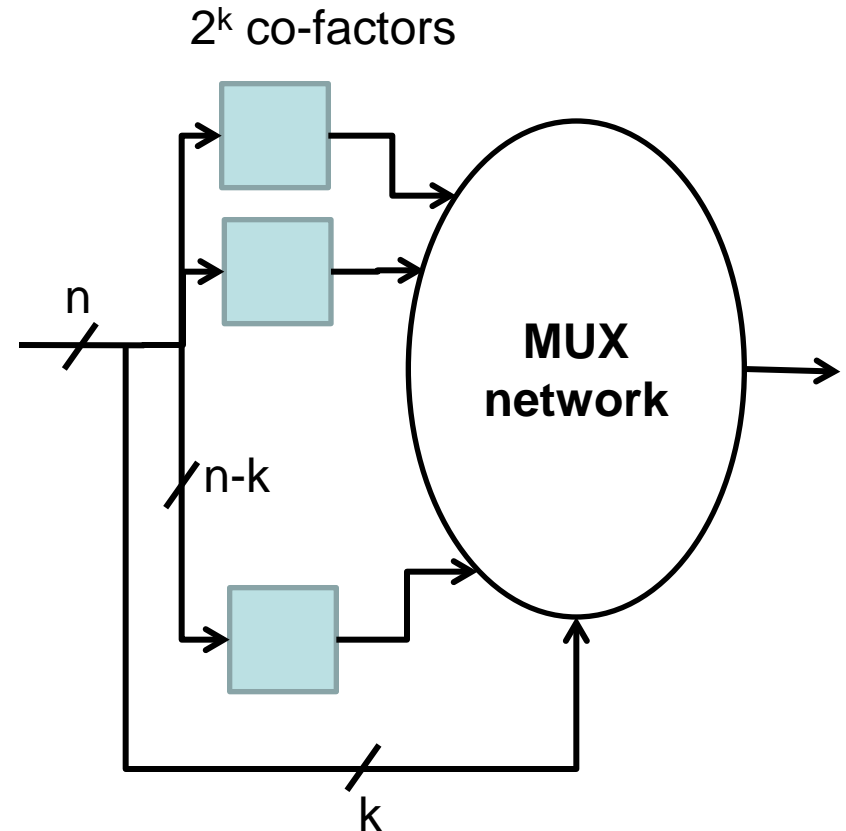- Also called **Shannon Decomposition**
- Can be applied recursively to “decompose” a function into its co-factors
 - In the extreme case, just a network of multiplexers



For an interesting application to variation-tolerant synthesis, see: Swaroop Ghosh, Swarup Bhunia and Kaushik Roy, “CRISTA: A new paradigm for low-power and robust circuit synthesis under parameter variations using critical path isolation”, IEEE Trans. Computer Aided Design, Nov 2007.

Shannon Expansion

- Example

$$f = xy + zw' + x'w'$$

Properties of Co-factors

- Given two functions $f(x)$ and $g(x)$
- How can we compute co-factors of a function h that is derived from f and g ?

| Function | Co-factors | |
|---------------------------------|---|--|
| $h(x) = f'(x)$ | $h_{x_i} = (f_{x_i})'$ $h_{x_i'} = (f_{x_i'})'$ | Co-factor of complement is complement of co-factor |
| $h(x) = f(x) \text{ AND } g(x)$ | $h_{x_i} = f_{x_i} \text{ AND } g_{x_i}$ $h_{x_i'} = f_{x_i'} \text{ AND } g_{x_i'}$ | Co-factor of AND is AND of co-factors |
| $h(x) = f(x) \text{ OR } g(x)$ | $h_{x_i} = f_{x_i} \text{ OR } g_{x_i}$ $h_{x_i'} = f_{x_i'} \text{ OR } g_{x_i'}$ | Co-factor of OR is OR of co-factors |
| $h(x) = f(x) \text{ XOR } g(x)$ | $h_{x_i} = f_{x_i} \text{ XOR } g_{x_i}$ $h_{x_i'} = f_{x_i'} \text{ XOR } g_{x_i'}$ | Co-factor of XOR is XOR of co-factors |

The co-factor operation distributes over any binary operator

Combinations of Co-factors

- Combining f_x and $f_{x'}$ in different ways leads to useful new functions


$$- f_x \oplus f_{x'} = ?$$

$$- f_x \cdot f_{x'} = ?$$

$$- f_x + f_{x'} = ?$$

Another analogy to the "real" world

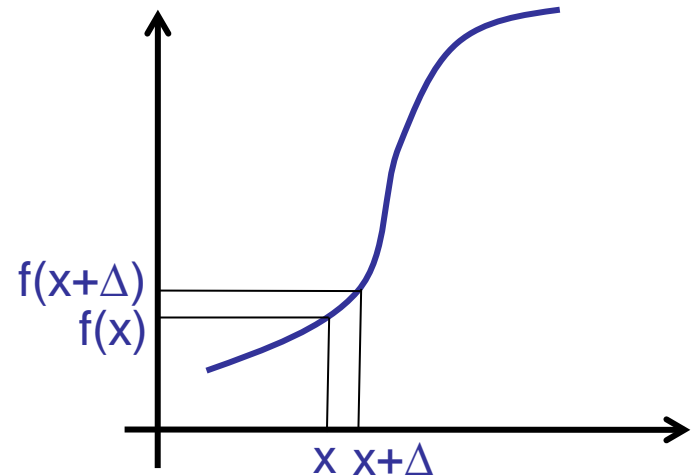- The derivative of a function measures how much it changes when its input changes
- Let us think of the analogy in the case of Boolean functions (which only take values 0 and 1)



$$f'(x) = \lim_{\Delta \rightarrow 0} \frac{f(x + \Delta) - f(x)}{\Delta}$$

Boolean Difference

- Boolean difference of a function w.r.t. a variable is the exclusive-OR of the Shannon co-factors w.r.t. the variable
- Interpretation: $\frac{\partial f}{\partial x} = 1 \rightarrow f$ is sensitive to the value of x
- A new function that does not depend on x

$$\frac{\partial f}{\partial x} = f_x \oplus f_{x'}$$

Example:

$$f = xy + zw' + x'w'$$

$$f_x =$$

$$f_{x'} =$$

$$\frac{\partial f}{\partial x} =$$


Boolean Difference

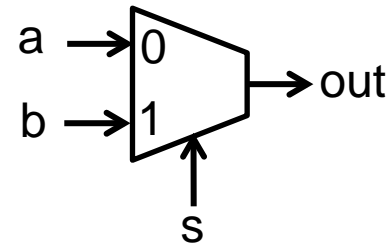- Examples:



$$\frac{\partial s}{\partial a} =$$

$$\frac{\partial c_{out}}{\partial c_{in}} =$$




$$\frac{\partial out}{\partial a} =$$

$$\frac{\partial out}{\partial s} =$$

Application of Boolean Difference

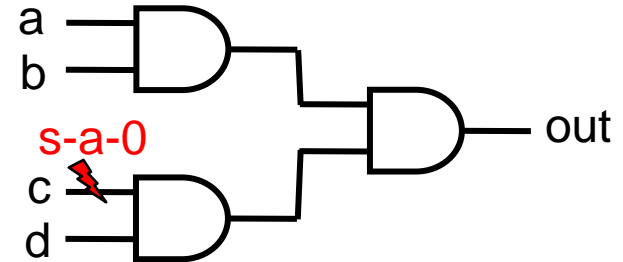- Manufacturing test
 - Apply test vectors to ensure that each fabricated instance of an IC behaves correctly
 - Cannot apply exhaustive test set (too big!)
- Fault model :
Abstraction of physical defects that could impact the IC
 - Commonly used: “stuck-at” fault model
 - Signals in the circuit are stuck-at-0, stuck-at-1



How do you derive a test vector to detect the fault c s-a-0?

- Set $c = 1$
- Set other inputs such that output of good and faulty circuits are different

Looks familiar?

Co-factors: Re-cap

- A very useful operation on Boolean functions
 - Derived by fixing one of the variables to a constant (0 or 1)
- Applications of co-factors
 - Shannon's expansion – a way to recursively simplify or divide Boolean functions
 - Boolean difference ($f_x \oplus f_{x'}$)
 - Universal and Existential Quantification

Quantification

- Two more functions of Shannon cofactors
 - $f_{x_i} \cdot f_{x_i'} = 1$ specifies when $f = 1$ independent of the value of x_i
 - $f(x_1 \dots x_{i-1}, \mathbf{x_i=1}, x_{i+1} \dots x_n) = 1$ AND
 - $f(x_1 \dots x_{i-1}, \mathbf{x_i=0}, x_{i+1} \dots x_n) = 1$
 - Called **Universal quantification** or **Consensus**

$$\forall x(f) = f_x \cdot f_{x'}$$

$$C_a(f)$$