









ECE 595Z Digital VLSI Design Automation

Module 6 (Lectures 21-24): Timing Analysis and Optimization
Lecture 22



Anand Raghunathan
MSEE 318
raghunathan@purdue.edu

Lecture 21 - Recap

- Timing constraints on combinational logic are imposed by requirements for correct operation in sequential circuits
 - Setup and hold condition
- Various delay models for gates / cells
 - Unit, constant, pin-to-pin, load/slew-rate dependent, state dependent, PVT-corners, statistical
- Given a delay model, how to analyze combinational logic for timing?

Approaches to Timing Analysis


Simulation

- Very accurate (can use complex delay models)
- Very slow (need to try all input vectors unless we are given the "worst case" input)


Static Timing Analysis

- Topological
 - Fast (single traversal of circuit)
 - Conservative (can lead to pessimistic estimate)
 - Best suited for repeated use in synthesis
- Functional
 - Reduce pessimism of topological analysis
 - Account for false paths
 - Slower (involves solution to a search problem)
- Combination of both approaches may be used in practice

 - Timing graph
 - Representation of combinational logic circuit as a directed acyclic graph (DAG)
 - Add dummy source and sink vertices
 - Do not care about the function of each gate, only it's delay
 - Annotate delays on edges of timing graph
 - Flexible: Pin-to-pin delays, multiple delays for different transitions, delays based on load and slew rate



 - Latest arrival time: Latest time a which a gate's output becomes *stable*
 - Longest path from primary inputs to the gate output
- Earliest arrival time:
 Earliest time at which a
 gate's output can become
 unstable
 - Shortest path from primary inputs to the gate output



Timing analysis = Finding longest/shortest paths through the timing graph


 Procedure for computing the (longest) topological delay of a circuit

```
    Construct timing graph
    Sort nodes in topological order
    For each node in sorted order
        Compute (latest) arrival time AT(v<sub>i</sub>) as max<sub>v<sub>j</sub> ∈ inputs(v<sub>i</sub>)</sub> {AT(v<sub>j</sub>) + D(v<sub>j</sub>,v<sub>i</sub>)}
```

NOTE: Above pseudo-code assumes pin-to-pin delay model. If using load and slew rate dependent model, also need to propagate slew rates and use them along with loads to compute delay of each gate.

For transition-dependent delay model, propagate separate rising and falling arrival times

• Example:

 

Topological order:

a, b, c, d, e, f, g, h, g1, g2, g4, g7, g3, g8, g5, g9, g6, g10, g11, g12

Latest Arrival Times:

a: 0, b: 0, c: 0, d: 0, e: 0, f: 0, g: 0, h: 0

g1: 2, g2: 1, g4: 1, g7: 2

g3: 4, g8: 3

g5: 6, g9: 5, g6: 7

g10: 9, g11: 10, g12: 12

Computing Earliest and Latest Arrival Times Using min-max Delays

- A single traversal of the timing graph can be used to compute both earliest and latest arrival times
 - Similar algorithm as before, except
 - Gate delays are specified as min-max ranges
 - Propagate earliest and latest arrival times

```
    Construct timing graph
    Sort nodes in topological order
    For each node in sorted order


            Compute latest arrival time AT<sub>L</sub>(v<sub>i</sub>) as max<sub>v<sub>j</sub> ∈ inputs(v<sub>i</sub>)</sub> {AT<sub>L</sub> (v<sub>j</sub>) + D<sub>max</sub>(v<sub>j</sub>, v<sub>i</sub>)}
            Compute earliest arrival time AT<sub>E</sub>(v<sub>i</sub>) as min<sub>v<sub>j</sub> ∈ inputs(v<sub>i</sub>)</sub> {AT<sub>E</sub>(v<sub>j</sub>) + D<sub>min</sub>(v<sub>j</sub>, v<sub>i</sub>)}
```

Usage of Timing Analysis

- **Answer the question**: Will a circuit operate correctly at the intended clock frequency
 - Yes/No
 - Check whether earliest and latest arrival times at the primary outputs satisfy the setup/hold conditions
- **Help in answering the question**: What can I do to improve the timing of the circuit?
 - Diagnostic information (why not?)
 - Identify targets for improvement (where should I focus re-design effort?)
 - Guide synthesis towards better implementations

Required Times

- Given a circuit and a timing constraint on it's primary outputs
 - Latest required time:
 Latest time at which the output of a gate may become stable without causing violation of a timing constraint
 - Longest path from the gate output to the primary outputs
 - Earliest required time:
 Earliest time at which the output of a gate may become unstable without causing violation of a timing constraint
 - Shortest path from the gate output to the primary outputs

 

Computing Required Times


• Similar to ATs, except propagate backwards from the primary outputs

```
    Construct timing graph
    Sort nodes in topological order
    Set RTs at primary outputs
    For each node in reverse sorted order

            Compute latest required time RT<sub>L</sub>(v<sub>i</sub>) as min<sub>vj ∈ fanouts(v<sub>i</sub>)</sub> {RT<sub>L</sub>(v<sub>j</sub>) - D<sub>max</sub>(v<sub>i</sub>,v<sub>j</sub>)}
            Compute earliest required time RT<sub>E</sub>(v<sub>i</sub>) as max<sub>vj ∈ fanouts(v<sub>i</sub>)</sub> {RT<sub>E</sub>(v<sub>j</sub>) - D<sub>min</sub>(v<sub>i</sub>,v<sub>j</sub>)}
```

Required Times: Example

• Example:

 

Topological order:

a, b, c, d, e, f, g, h, g1, g2, g4, g7, g3, g8, g5, g9, g6, g10, g11, g12

Latest Required Times:

g12: 10

g11: 8, g10: 7

g6: 5, g9: 5, g5: 4,


g8: 3, g3: 2, g7: 2, g4: 2, g2: 0, g1: 0, h: 8, g: 3, f: 0, e: 0, d: 1, c: -1, a: -2, b: -2

Timing Slack

- Slack at a node is equal to the Required Time – Arrival Time
- Reflects the timing margin available before the node becomes "critical"
- Negative slack means that a timing constraint is not satisfied

Timing Critical Nodes

 - A **critical node** is a node in the network that has the lowest slack
 - Not unique



Delay(NAND2) = 2

RT(O1) = RT(O2) = 5

Topological order:

Arrival times:

Required times:

Slacks:

Critical nodes:

Timing Critical Paths

- Interesting Property: The set of timing critical nodes forms a connected network consisting of paths from PIs to POs
 - Called critical paths

Algorithm to find critical paths

- 1. Construct timing graph
- 2. Sort nodes in topological order
- 3. Compute AT, RT, and Slack at each node
- 4. Slack_{min} = min_{all nodes vi}(Slack(v_i))
- 5. Trace path(s) through the network where each node has Slack = Slack_{min}

ε-critical Network

- In practice, we may be interested in paths that are critical or "close-to-critical"
 - Close-to-critical paths could become critical when we optimize the critical paths
 - Uncertainty / margin of error in delay models
- ε-critical node: A node v_i is ε-critical if Slack(v_i) ≤ Slack_{min} + ε
- Interesting Property: The set of ε-critical nodes forms a connected network consisting of paths from PIs to Pos
 - Called the ε-critical network


Summary: Topological Timing Analysis

- Computation of Arrival Times and Required Times
- Slack represents the timing margin at a node
- Critical paths: Paths with minimum slack

The False Path Problem

- Problem: Topological timing analysis may be pessimistic!
 - Ignores functionality of the nodes in the circuit
- Some paths can never be responsible for determining the delay of a circuit
 - Called "false" paths
- A path is false if no sequence of input vectors can result in an event propagating along it


False Path Examples

 

Delay(NAND2) = 2, Delay(INV)= 1, Delay(MUX) = 2

Longest Path:

False?

 

Delay(AND) = 2, Delay(INV)= 1, Delay(OR) = 2

Longest Path:

False?

False Path: Real Example

• 2-bit carry-bypass adder

