 


ECE 595Z

Digital VLSI Design Automation

Module 5 (Lectures 14-20): Multi-level Synthesis




Anand Raghunathan

MSEE 348

raghunathan@purdue.edu


Structure of a Logic Circuit

 - Combinational logic, memory elements (FFs, latches), I/O
- Combinational logic synthesis focuses on optimizing the combinational logic
 - Two-level synthesis is one form of combinational logic synthesis




Why Multi-level?

- Two-level implementation is impractical (too large) for many functions
 - N-bit adder has $O(2^N)$ product terms in minimum cover
- Specification by designers (Verilog, VHDL) is often naturally in multi-level form
- Multiple metrics of interest (a specific point in the tradeoff space between area vs. delay, delay vs. power, *etc.* is not enough)
 - Two-level implementations represent only a small part of this space

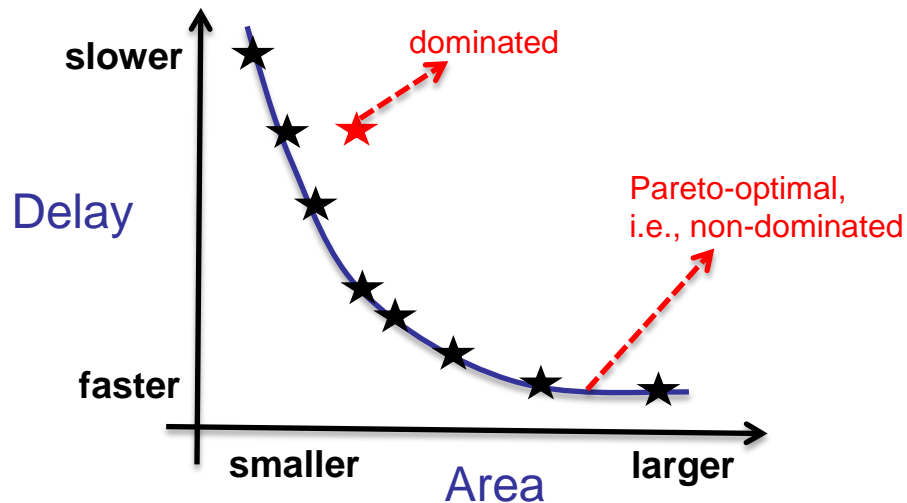


Multi-level Logic Implementation

 - Logic depth in modern microprocessors: 10-25



11 "levels" of logic

Typical Synthesis Flow

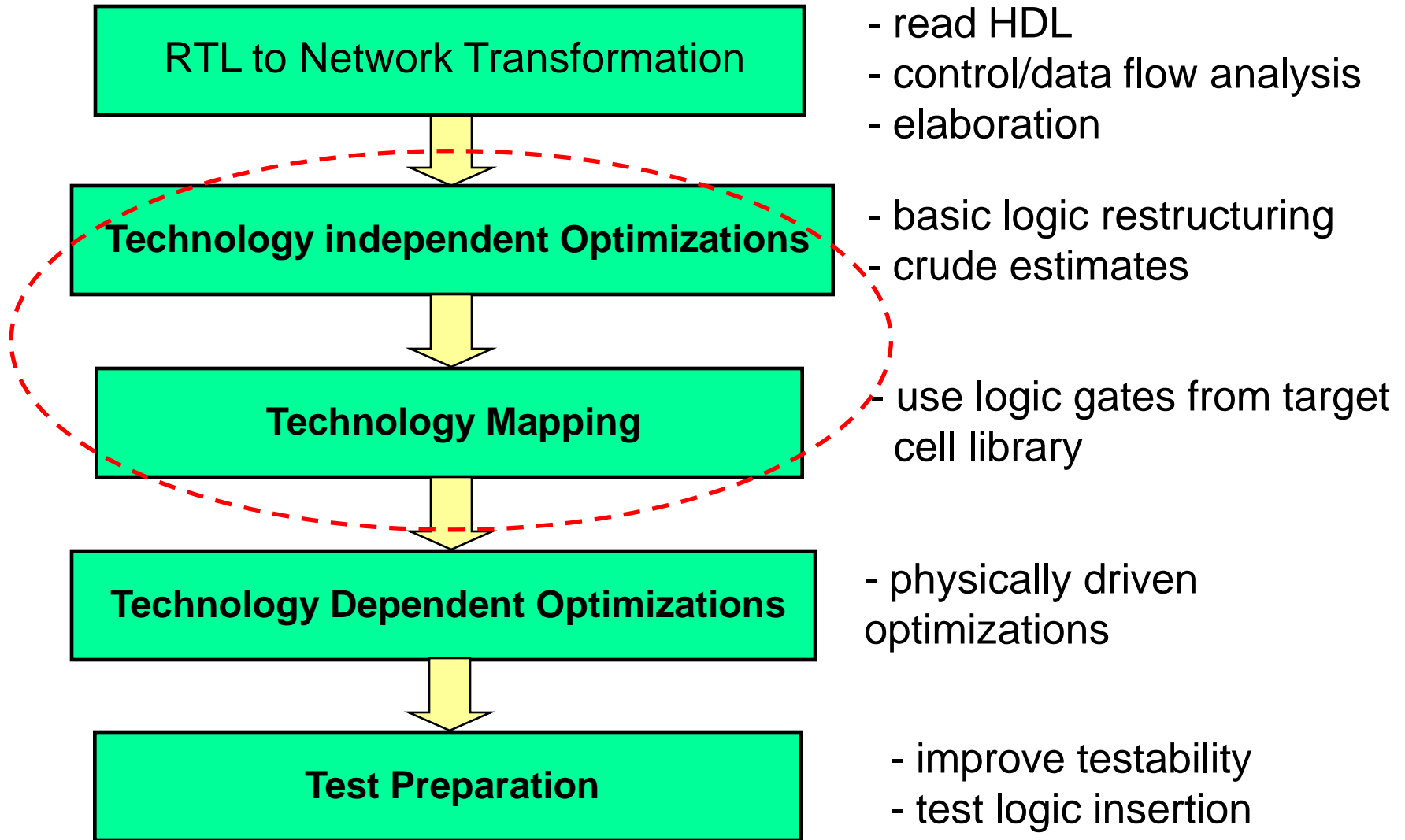

Steps in Multi-level Synthesis that we will Discuss


- Technology independent optimization
 - Optimize the network independent of a specific fabrication process (cell library)
 - Approximate metrics for area (literals), delay (levels in circuit), ...
- Technology Mapping
 - Map the network to a specific cell library
 - More accurate estimation of metrics

Reading

- Introduction to multi-level synthesis
 - De Micheli, Chapters 8.1-8.2
 - Hachtel & Somenzi, Chapters 10.1-10.2


Representation : Boolean Network

 - Abstraction of multi-level circuits
- Directed Acyclic Graph (DAG)
 - Nodes represent primary inputs, primary outputs, and internal functions
 - Edges : indicate input-output relationships between nodes




Representation : Boolean Network

 - What is inside each node?
- A Boolean function!
 - Simple gate
 - SOP expression in terms of primary inputs and outputs of other nodes
 - Arbitrary logic expression



Boolean Network

 - Directed Acyclic Graph
- Nodes
 - Primary Inputs
 - Primary Outputs
 - Intermediate nodes
- Edges : Connectivity between nodes
- Fan-in, transitive fan-in
- Fan-out, transitive fan-out



$$y_1 = f_1(x_2, x_3) = x_2' + x_3'$$


$$y_2 = f_2(x_4, x_5) = x_4' + x_5'$$

$$y_3 = f_3(x_4, y_1) = x_4' y_1'$$

$$y_4 = f_4(x_1, y_3) = x_1 + y_3'$$

$$y_5 = f_5(x_6, y_2, y_3) = x_6 y_2 + x_6' y_3'$$


Boolean Network : Example

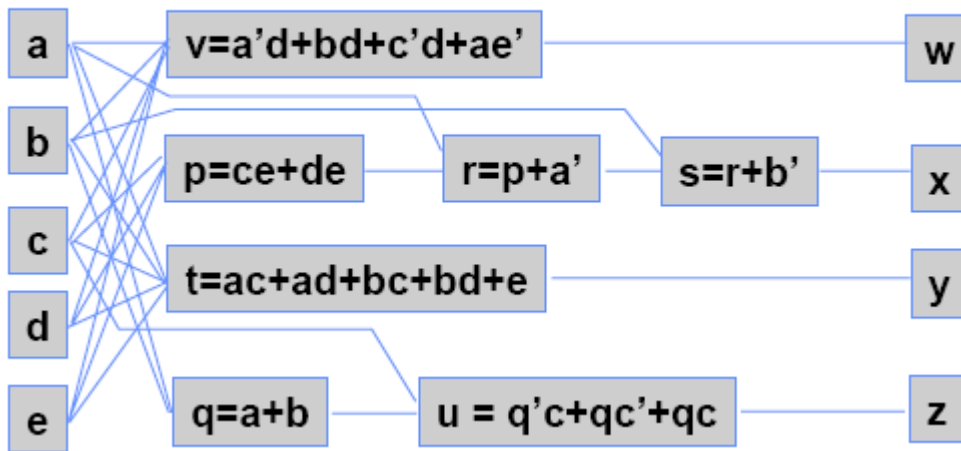

$$\begin{aligned} p &= ce + de \\ q &= a + b \\ r &= p + a' \\ s &= r + b' \\ t &= ac + ad + bc + bd + e \\ u &= q'c + qc' + qc \\ v &= a'd + bd + c'd + ae' \\ w &= v \\ x &= s \\ y &= t \\ z &= u \end{aligned}$$

Boolean Network : Example

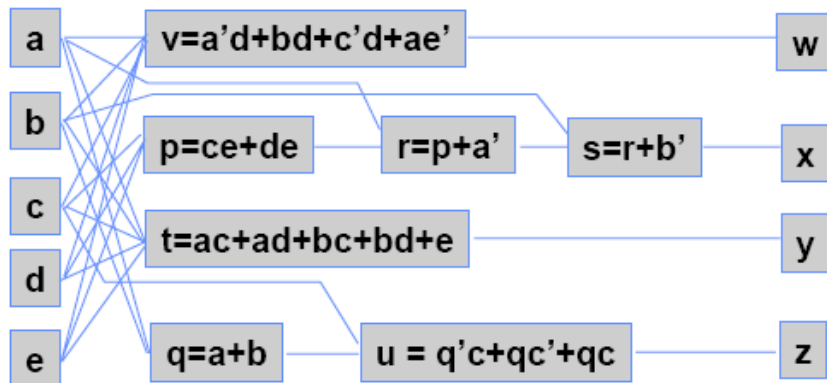- How do we measure the complexity of a network?
 - How many gates?
 - How many literals?



General Approach to Multi-level Synthesis

- **Much** more complex than two-level minimization
 - Give up any hope of optimality
- Iterative Improvement Approach
 - Similar to ESPRESSO
 - Apply transformations to improve the network as long as there is improvement
- User-driven
 - “Scripts” that specify sequences of optimization steps to perform


Transformations on Boolean Networks

- Scope
 - Global
 - Any optimization across nodes
 - Re-structuring of entire network
 - Local
 - Optimizations within a node
- Effect
 - Reducing # of nodes
 - Elimination, Substitution
 - Adding new nodes
 - Extraction, Factoring
 - Simplifying nodes
 - Directly apply what we learnt in two-level minimization

Transformation Example: Elimination

- Reducing the # of nodes in the network
 - Requires collapsing of the function performed by the node into the other nodes that it feeds

Example:

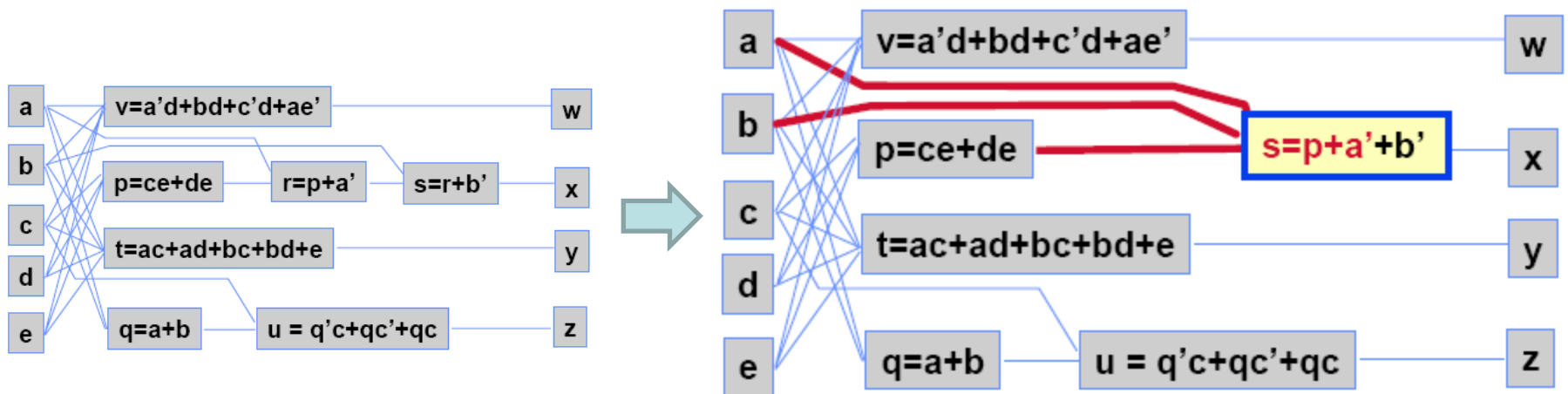


Question : What effect could this have on area (literals) and delay?

Transformation Example: Extraction

- Increases the # of nodes in the network
 - Creates a new node that implements a common sub-expression of two or more nodes in the original network
 - Aggressively substitute the output of the new node in other nodes

Example:

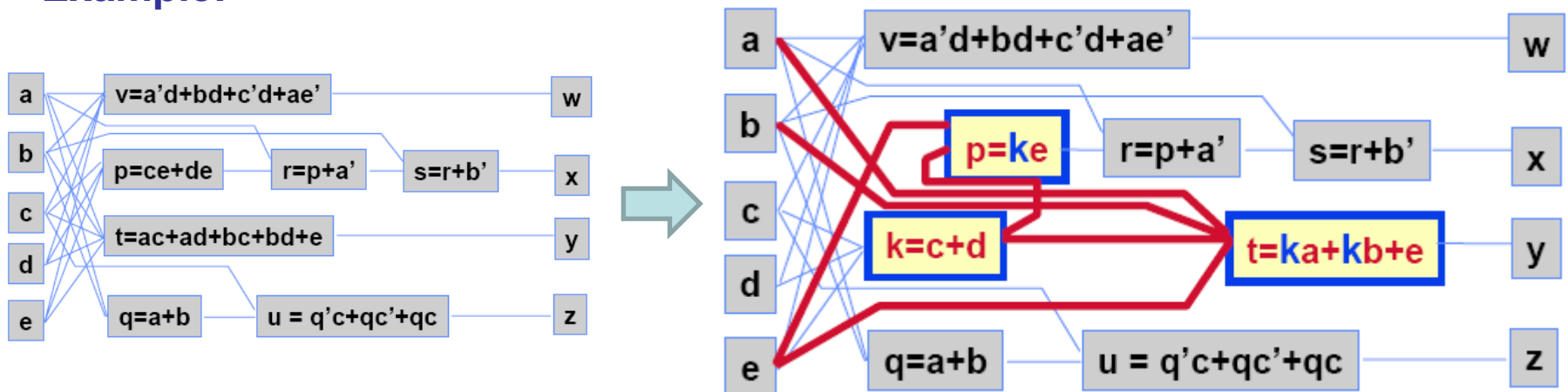


Question : What effect could this have on area (literals) and delay?

Transformation Example: Simplification

- Simplify the internal logic expression for a node
 - Direct application of ESPRESSO if the node functions are represented in SOP form!
 - Usually a local change (exception : eliminating a variable)

Example:

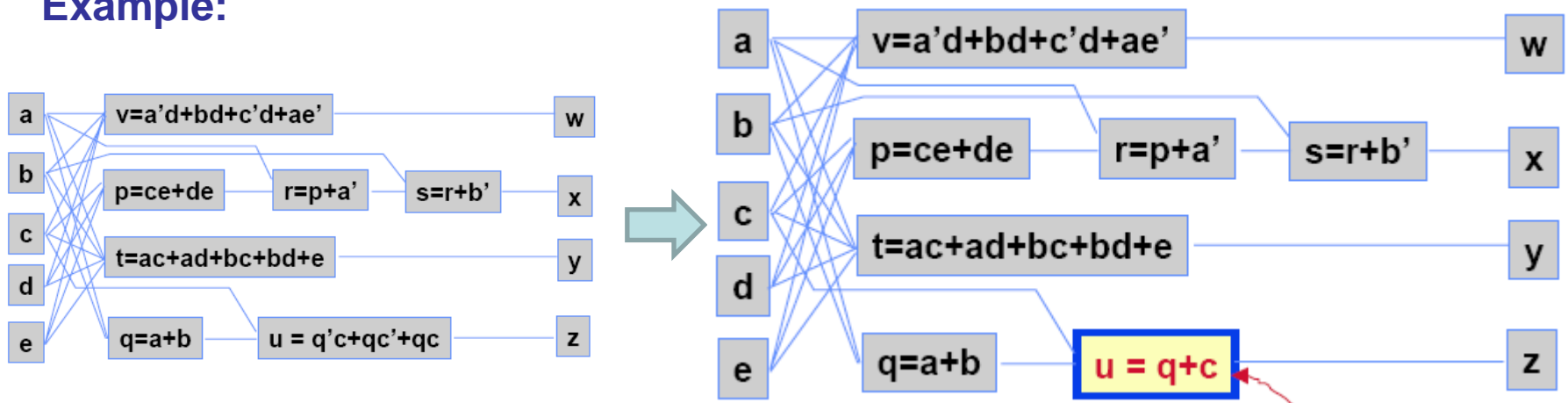

Question : What effect could this have on area (literals) and delay?

Multi-level synthesis operations: Summary

- Global
 - Extraction
 - Find common **factors** for two or more nodes
 - Elimination / Collapsing
 - Collapse a node into its fan-outs
 - Re-substitution
 - Re-substitute node into other nodes in the network through **factoring**
- Local
 - Decomposition
 - Decompose a node through **factoring**
 - Simplification
 - Use ESPRESSO to simplify the expression inside a node