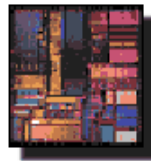




# Digital Systems Design Automation

## Unit 2: Advanced Boolean Algebra

### Lecture 2.4: Conversion of Boolean Function Representations



Anand Raghunathan


raghunathan@purdue.edu

## Outline

- 2.1 Boolean algebra: Quick review
- 2.2 Boolean spaces and functions
- 2.3 Boolean function representations
- 2.4 Conversion of Boolean function representations
- 2.5 Co-factors of Boolean functions
- 2.6 Boolean difference and Quantification
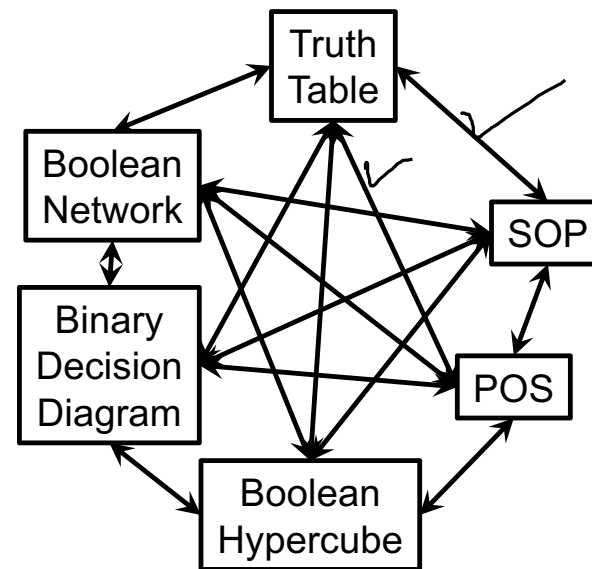
# Converting Between Boolean Function Representations

- All of the previously described representations are functionally equivalent...
- But vary in their complexity (size), and ease of performing various operations
  - No single “best” representation
- Need to convert between representations



## Conversion: Example #1


- How do you convert a general Boolean network (multi-level circuit) into SOP form?
  - Quick-and-dirty (exhaustive) algorithm

```
For each input vector  $v \in \{00\dots0 \text{ to } 11\dots1\}$  {  
  Simulate the circuit for input  $v$ ;  
  If (output == 1) {  
    encode input vector as a minterm;  
  }  
}
```

- Works, but *guaranteed to be exponential* in the number of inputs
- There should be a better algorithm!
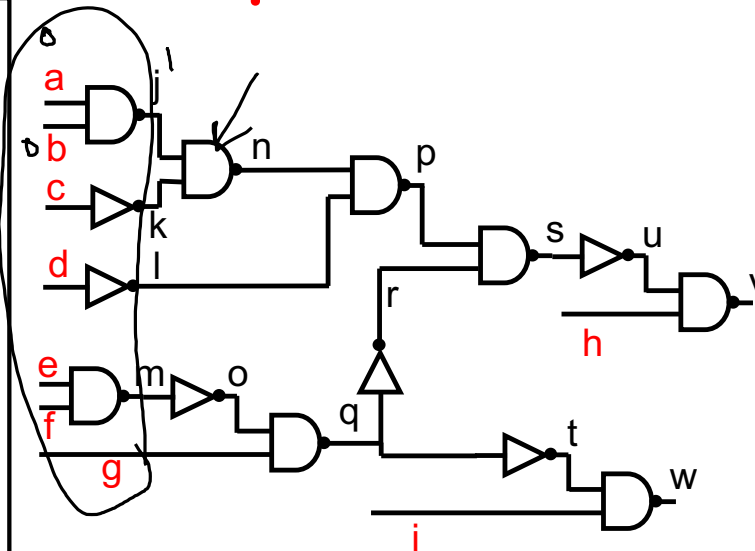
## Conversion: Example #1

- $j = (ab)' = a' + b'$
- $k = c'$
- $l = d'$
- $m = e' + f'$  ✓ ↓
- $n = j' + k' = (a'+b')' + (c')' = ab + c$
- $o = m' = ef$
- $p = n' + l' = (ab+c)' + d = a'c' + b'c' + d$
- $q = o' + g' = e' + f' + g'$
- $r = q' = efg$
- $s = p' + r' = (a+c)(b+c)d' + e' + f' + g' = abd' + cd' + e' + f' + g'$
- $t = q' = efg$
- $u = s' = (a'+b'+d)(c'+d)efg = a'c'efg + b'c'efg + defg$
- $v = u' + h' = abd' + cd' + e' + f' + g' + h'$
- $w = t' + i' = e' + f' + g' + i'$





Notice the similarity to circuit simulation?  
 Only difference is, we are propagating Boolean expressions, not 0/1 values.  
 This is called **Symbolic Simulation**

## Conversion: Example #2

- How do you convert a general Boolean network (multi-level circuit) into a Boolean formula that is linear in the circuit size?
  - Size(formula) =  $O(M)$  where  $M$  = no. of gates in the circuit
  - SOP may be exponential in the worst case
  - Hints
    - Use variables to represent intermediate signals in the circuit
    - Compose the formula using a 1 : 1 mapping from each gate in the circuit into a piece of the formula
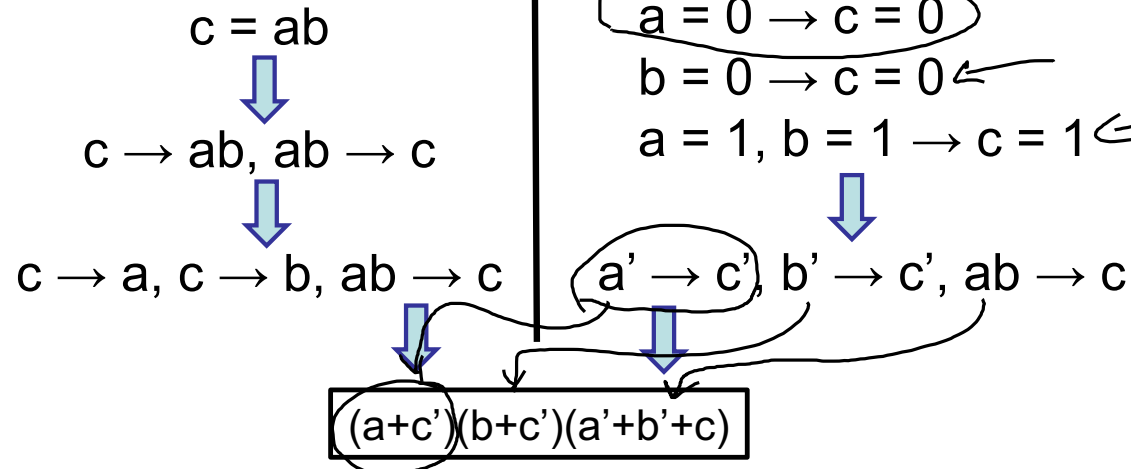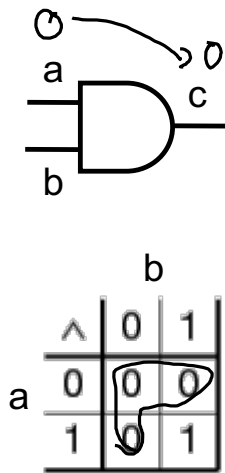
# Converting a Boolean Circuit into a CNF Formula

- First, let us see how very simple circuits (single gates) can be expressed as a Boolean formula (in CNF form)



## Converting a Boolean Circuit into a CNF Formula


- Rules for converting various basic gates into CNF equivalent

Gate Type	Function	CNF Formula
NOT	$c = a'$	$(a+c)(a'+c')$
AND	$c=ab$	$(a+c')(b+c')(a'+b'+c)$
NAND	$c=a'+b'$	$(a+c)(b+c)(a'+b'+c')$
OR	$c=a+b$	$(a'+c)(b'+c)(a+b+c')$
NOR	$c = a'b'$	$(a'+c')(b'+c')(a+b+c)$


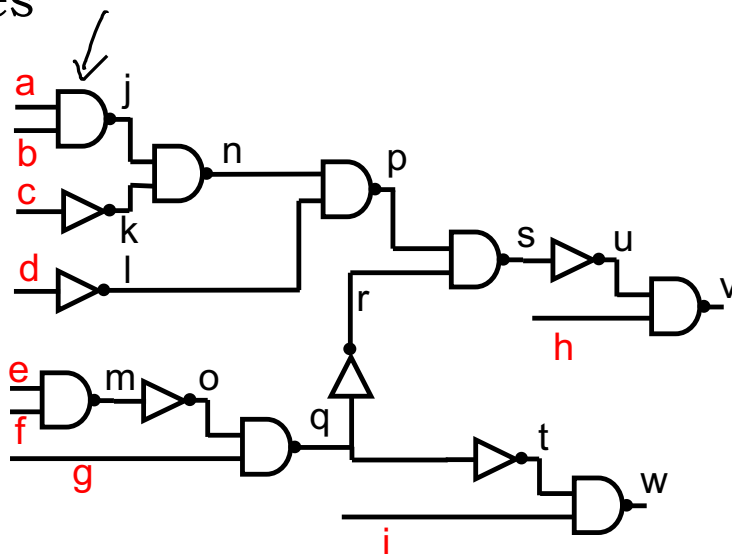
## Converting a Boolean Circuit into a CNF Formula

- Now, we are ready to convert a multi-level circuit into a CNF formula
  - Conjunction (AND) of formulae representing each of its gates



Known as the Tseitin Transformation

$$\begin{aligned}
 &(a+j)(b+j)(a'+b'+j') \quad \leftarrow \\
 &(c+k)(c'+k') \\
 &(d+l)(d'+l') \\
 &(e+m)(f+m)(e'+f'+m') \\
 &(m+o)(m'+o') \\
 &(j+n)(k+n)(j'+k'+n') \\
 &(n+p)(l+p)(n'+l'+p') \\
 &(o+q)(g+q)(o'+g'+q') \\
 &(q+r)(q'+r') \\
 &(p+s)(r+s)(p'+r'+s') \\
 &(s+u)(s'+u') \\
 &(u+v)(h+v)(u'+h'+v') \\
 &(q+t)(q'+t') \\
 &(t+w)(i+w)(t'+l'+w')
 \end{aligned}$$

# Terminology Checklist

- Boolean Algebra
- Boolean Function
- Tautology
- Satisfiable / Un-satisfiable
- Cube
- Implicant (of a function)
- Minterm
- Cover (of a function)
- Sum-of-products
- Minterm canonical representation
- Product-of-sums
- Conjunctive Normal Form
- Disjunctive Normal Form
- Binary Decision Tree
- Binary Decision Diagram
- Symbolic Simulation
- Tseitin Transformation

