BAND PASS FILTER

The Band Pass filter allows passage only to a certain band of frequencies. All other frequencies are attenuated (removed or blocked).

R - Resistance
C - Capacitance
L - Inductance

$$Transfer\,Function : H(jw) = \frac{(R/L)jw}{(jw)^2 + (R/L)jw + (1/LC)}$$