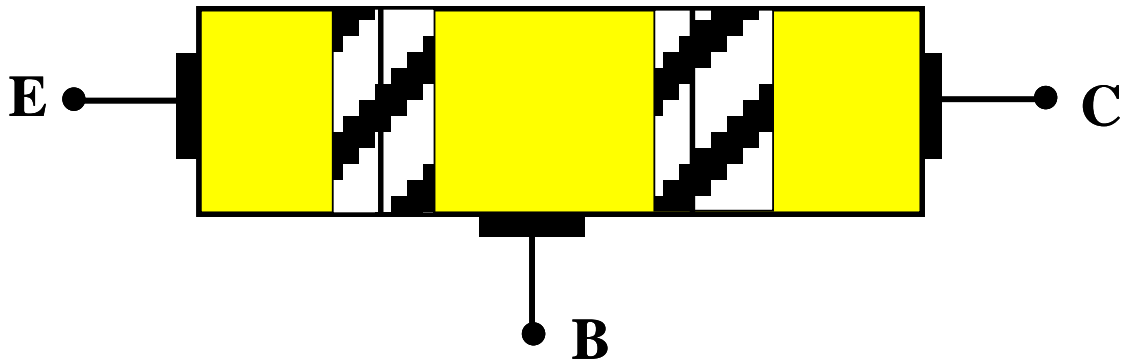


BJT Lab: Theoretical Exercises


Dragica Vasileska (ASU) and Gerhard Klimeck (Purdue)

1. Show diagrammatically and with analytical expressions (the simple ones) the current components in reverse active mode and in the cut-off mode.

(a) reverse active mode:



(b) cut-off mode

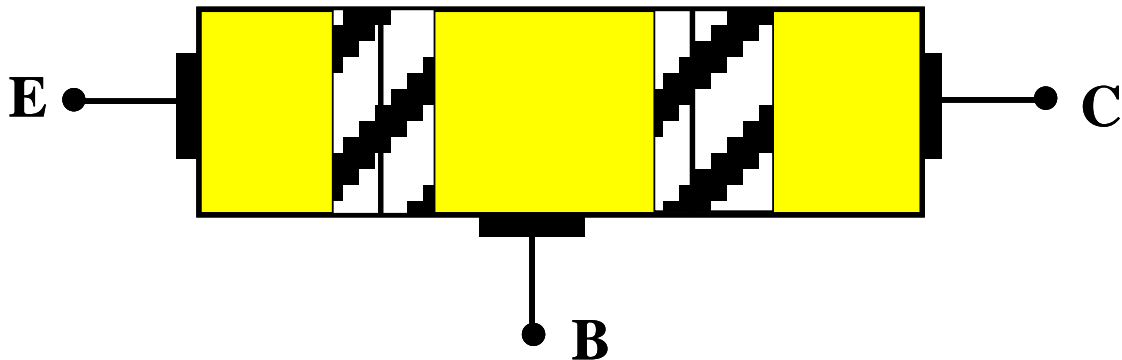

2. On the figure below are given the output characteristics of a BJT in a common-emitter configuration:

- (a) What is the small signal current gain for $V_{CE} = 10$ V.
- (b) What is the output conductance of this device.
- (c) Estimate the Early voltage of the transistor. What is the reason for the Early effect?

