

Section 25

Bipolar Junction Transistor - Design

Gerhard Klimeck


gekco@purdue.edu



School of Electrical and
Computer Engineering

Section 25

Bipolar Junction Transistor - Design


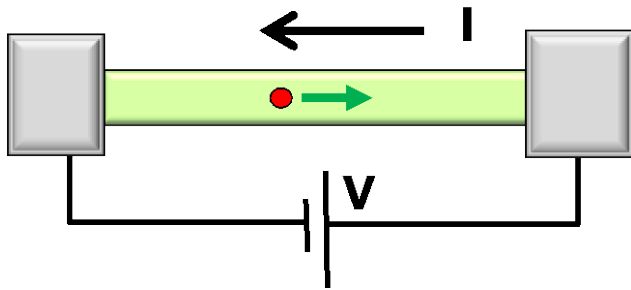


$$I = G \times V$$

$$= q \times n \times v \times A$$


↑ charge density
 ↑ velocity
 area

- 24.1 Introduction
- 24.2 Band Diagram in Equilibrium
- 24.3 Currents in BJTs
- 24.4 Ebers Moll Model
- 25 BJT Design
- 26 BJT High Frequency Response
- 27 HBT – Heterojunction Bipolar Transistor

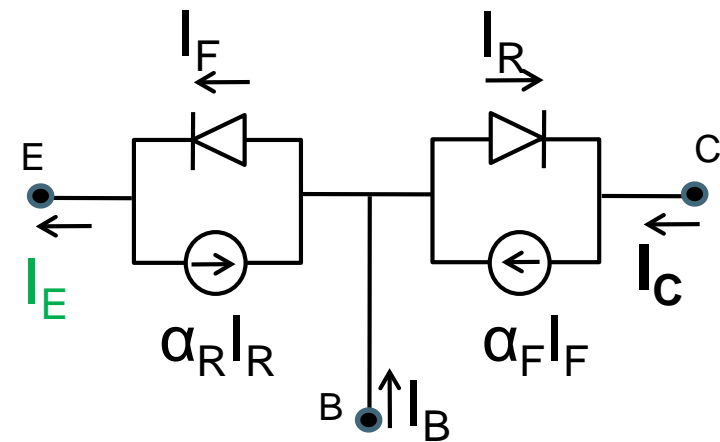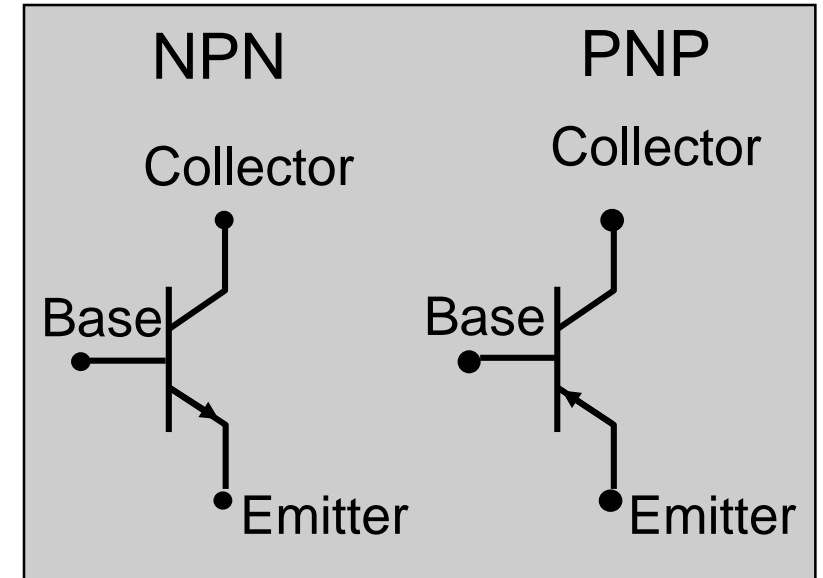

Section 25


Bipolar Junction Transistor - Design

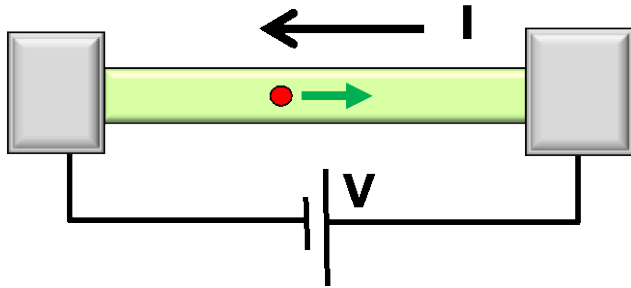

$$I = G \times V$$



$$= q \times n \times v \times A$$

↑ charge density
 ↑ velocity
 area

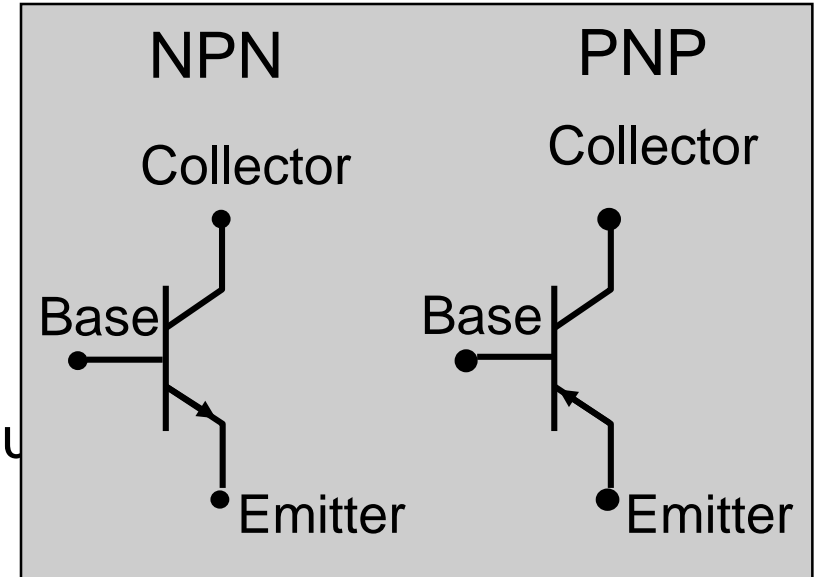



- >
- >
- >
- >
- >
- >

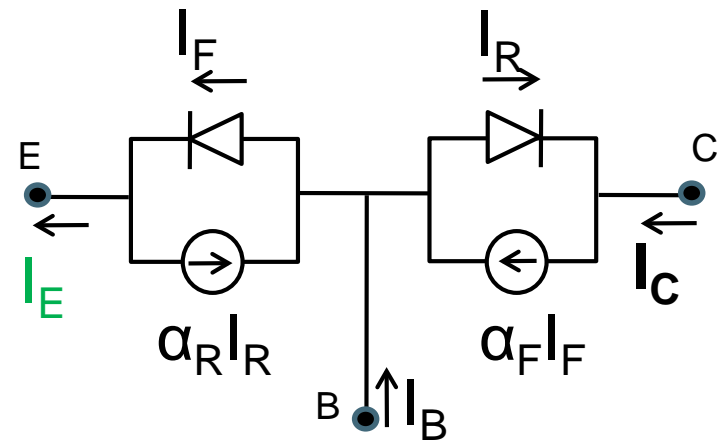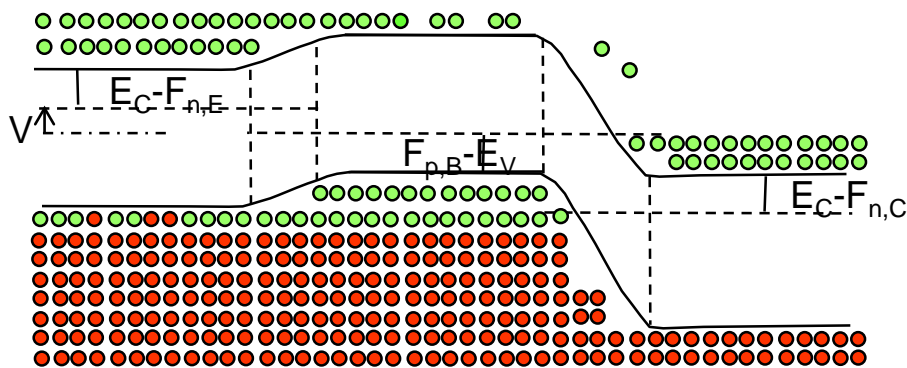- 25.1 Current gain in BJTs
- 25.2 Base Doping Design
- 25.3 Collector Doping Design (Kirk Effect, Base Pushout)
- 25.4 Emitter Doping Design
- 25.5 Poly-Si emitter
- 25.6 Short base transport






Current flow with Bias

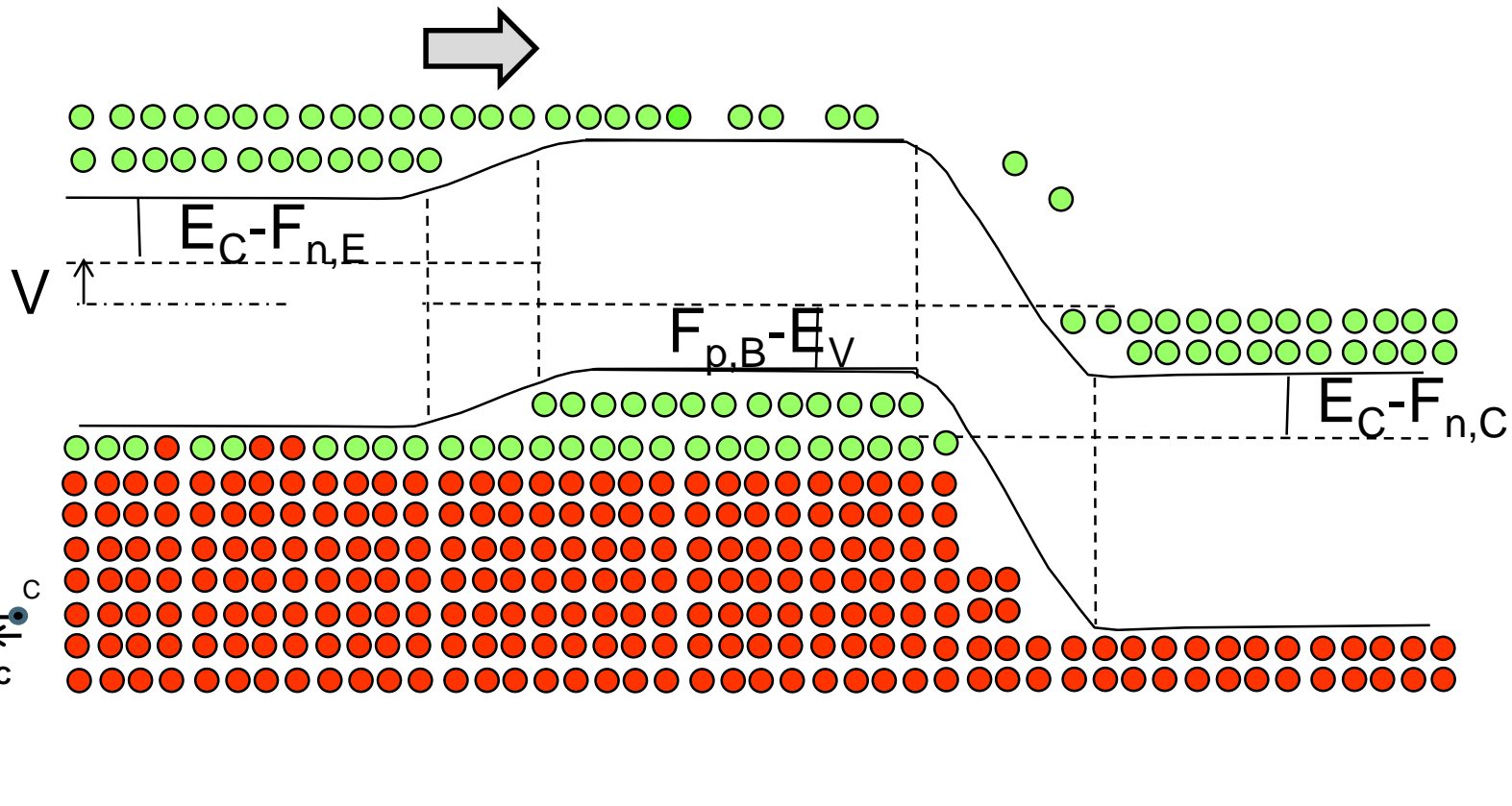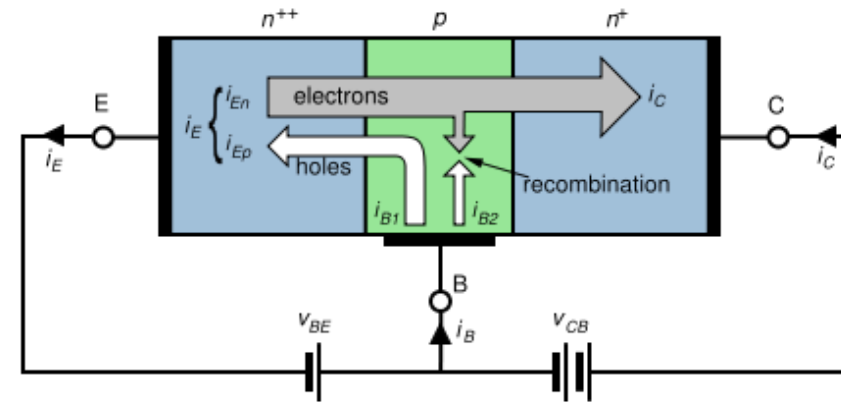Input small amount of holes results in large amount of electron output








Current flow with Bias

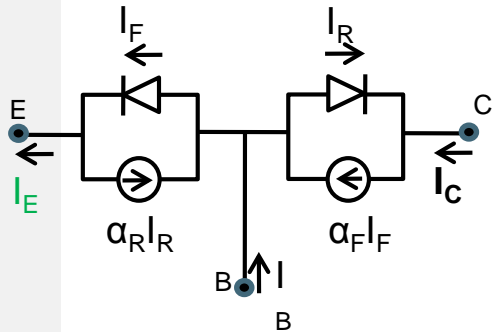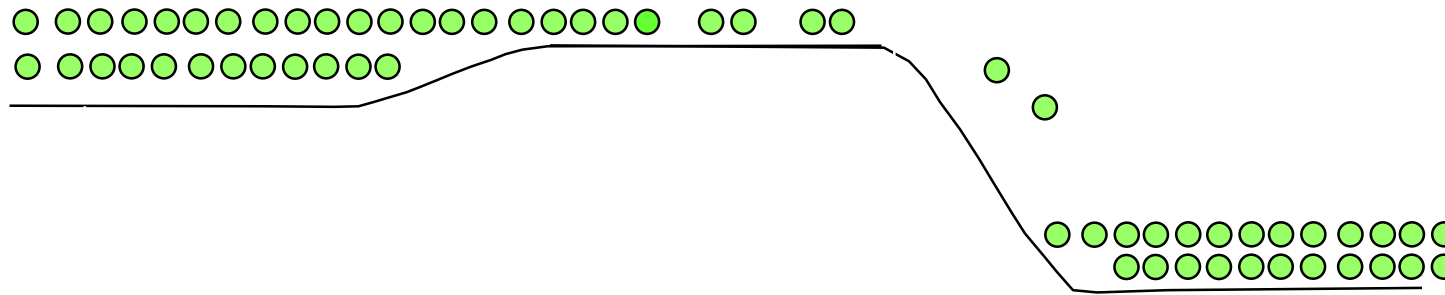
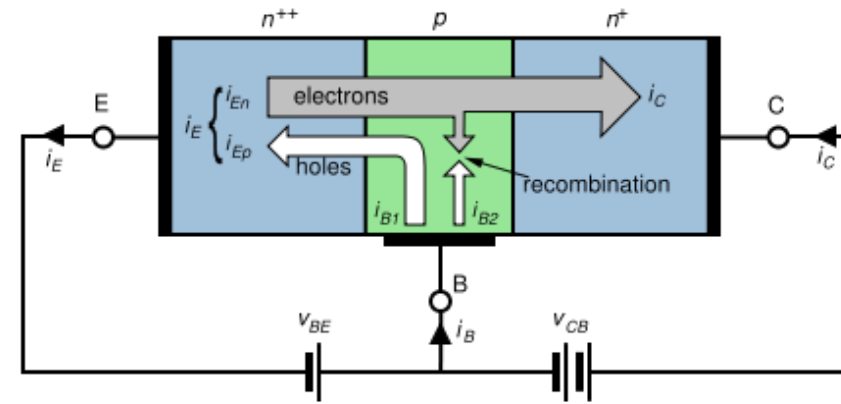
Input small amount of holes results in large amount of electron output



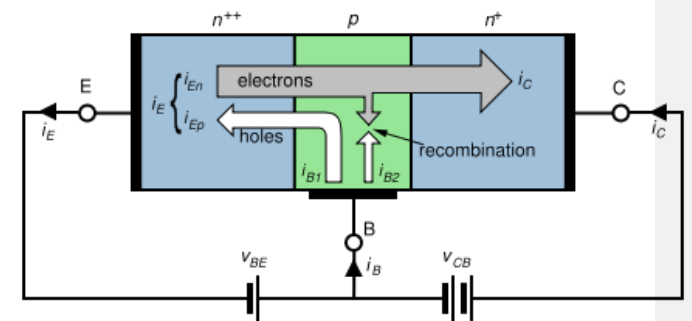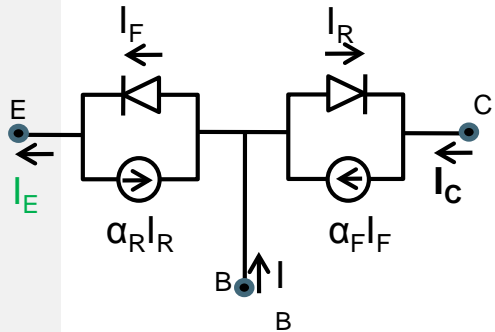
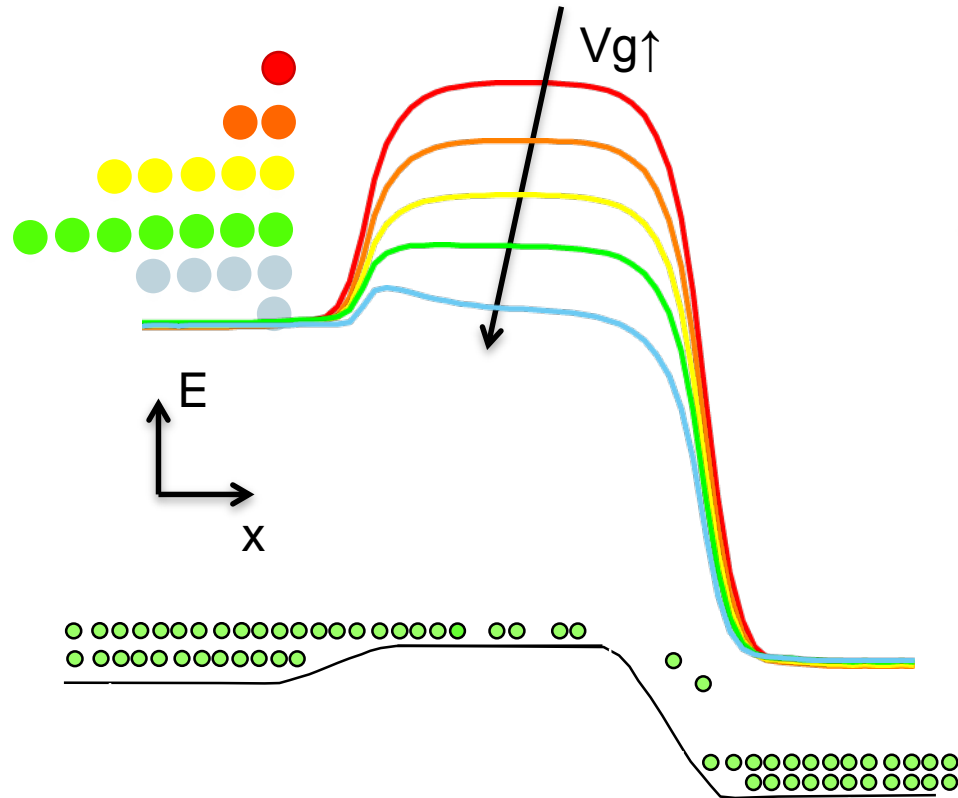
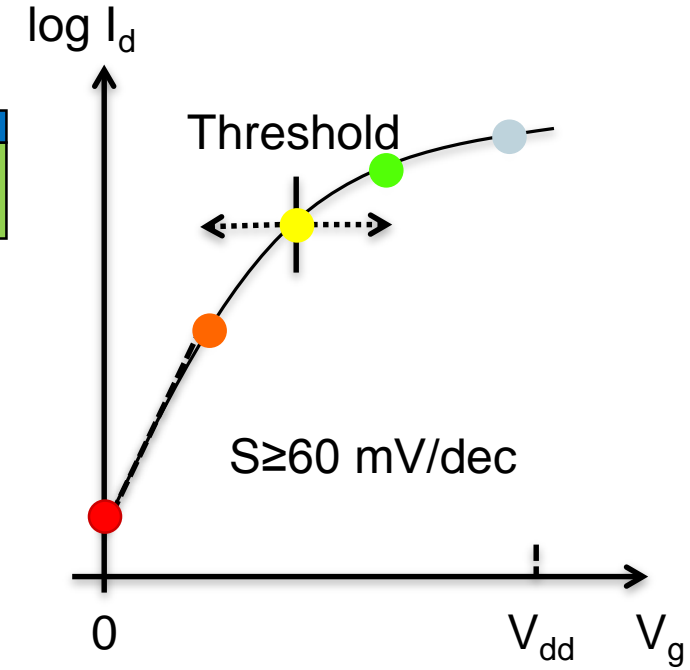
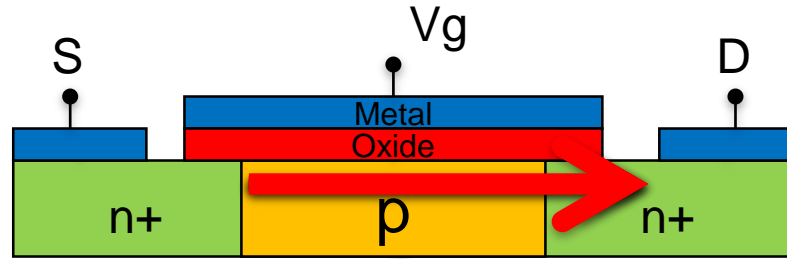
Modern MOSFET - "Fundamental" Limit looks similar to BJT



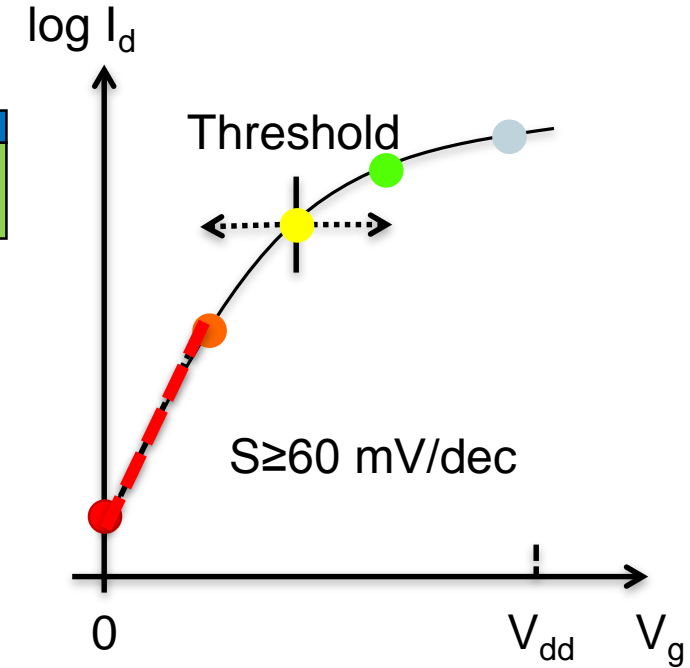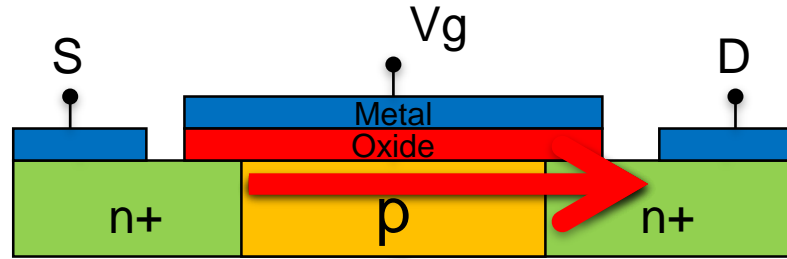Modern MOSFET - "Fundamental" Limit looks similar to BJT



DOS(E), $\log f(E)$

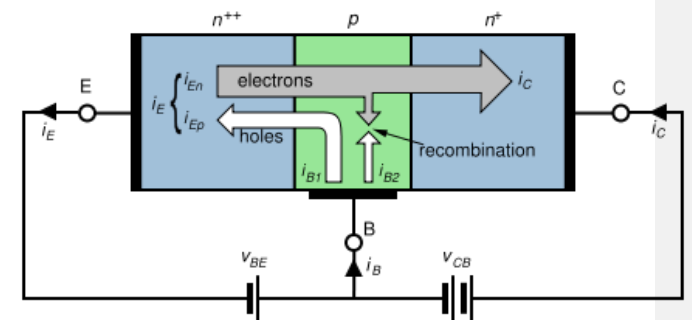
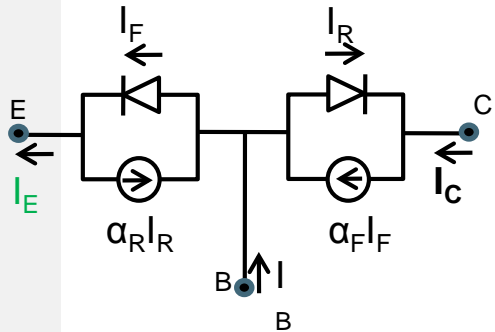
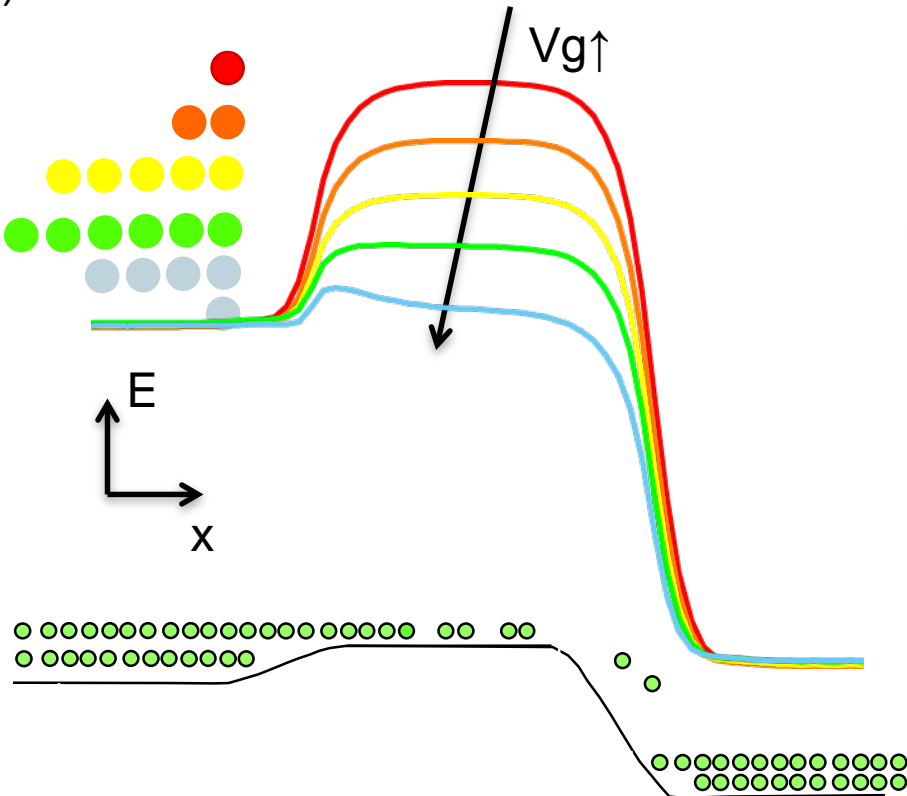
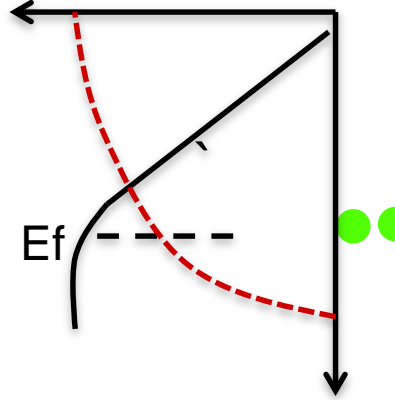


Ebers Moll Model

$$I_C = -A \frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1) + A \left[\frac{qD_n n_{i,B}^2}{W_B N_B} + \frac{qD_p n_{i,C}^2}{W_C N_C} \right] (e^{qV_{BC}\beta} - 1)$$

$$I_B = A \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1) + A \frac{qD_p n_{i,C}^2}{W_C N_C} (e^{qV_{BC}\beta} - 1)$$

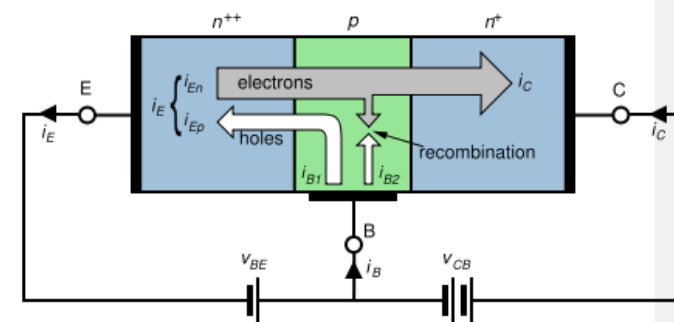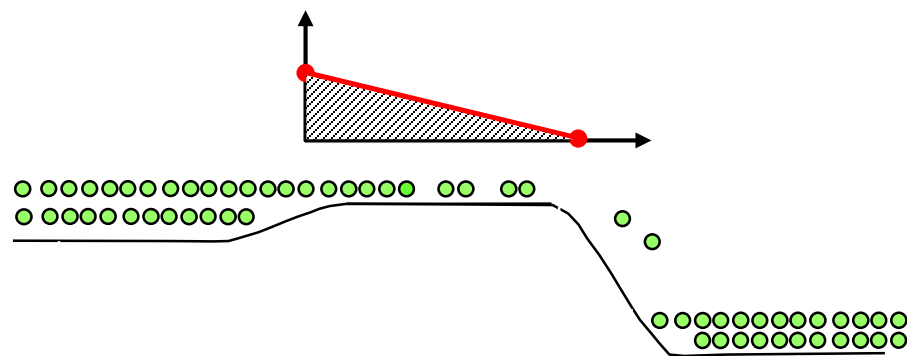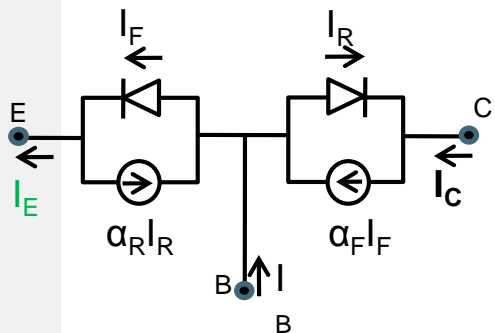
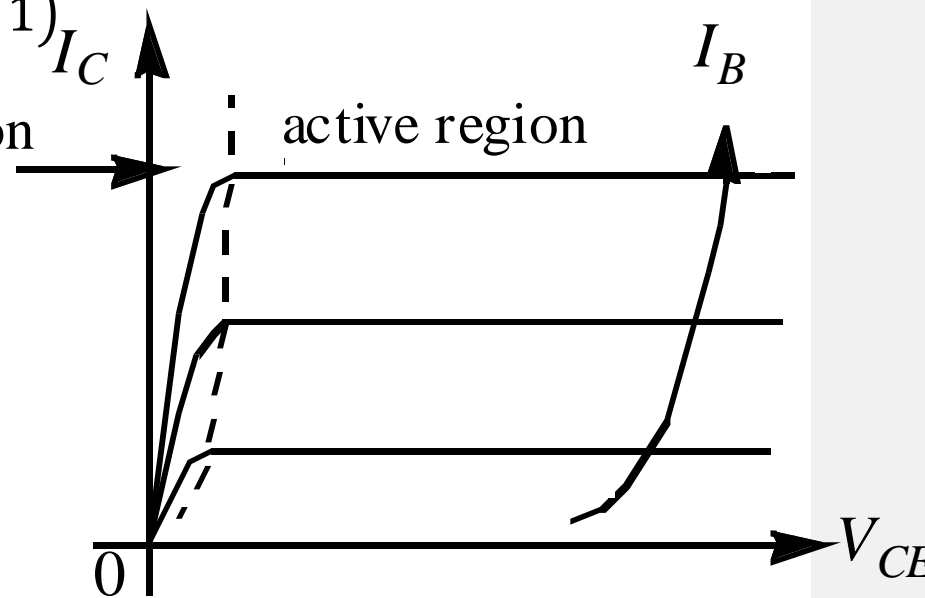
The Ebers-Moll model describes both the active and the saturation regions of BJT operation.





Ebers Moll Model

$$I_C = -A \frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1) + A \left[\frac{qD_n n_{i,B}^2}{W_B N_B} + \frac{qD_p n_{i,C}^2}{W_C N_C} \right] (e^{qV_{BC}\beta} - 1) \quad \frac{I_C}{A} \approx -\frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1)$$
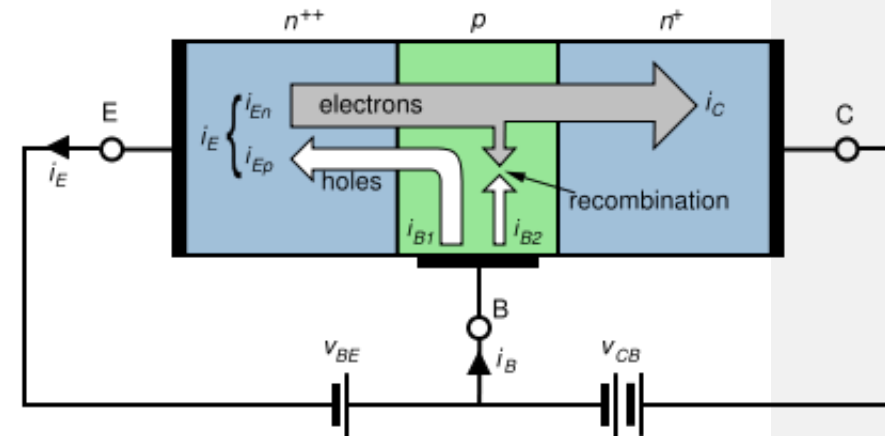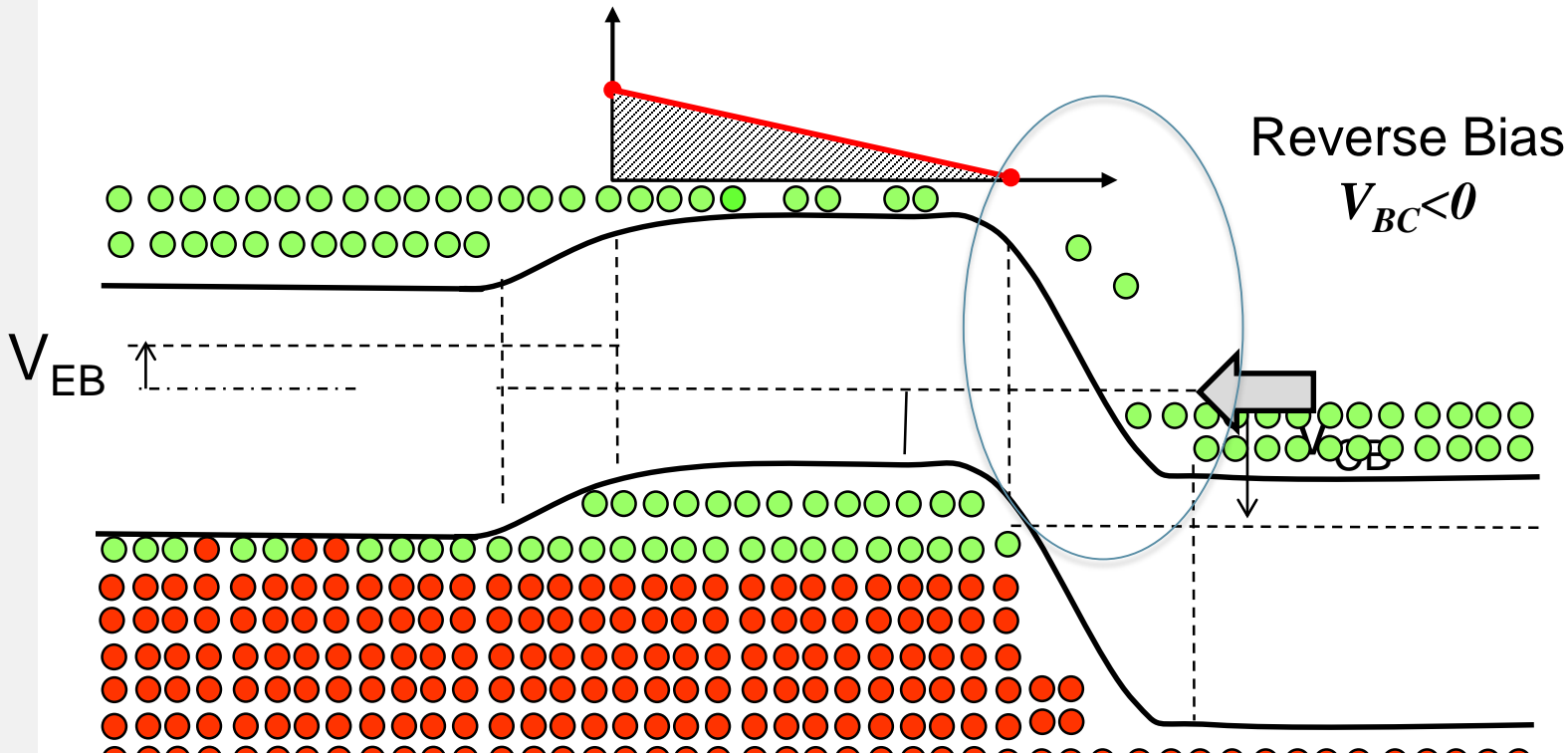
$$I_B = A \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1) + A \frac{qD_p n_{i,C}^2}{W_C N_C} (e^{qV_{BC}\beta} - 1) \quad \frac{I_B}{A} \approx \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1)$$



Gummel Plot

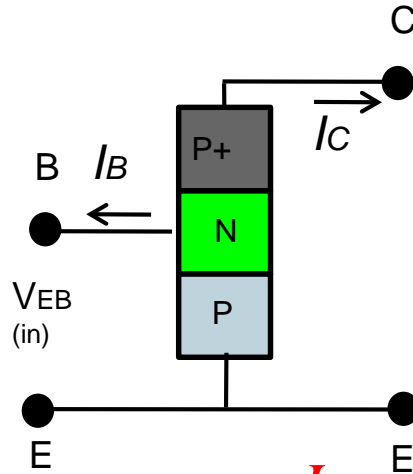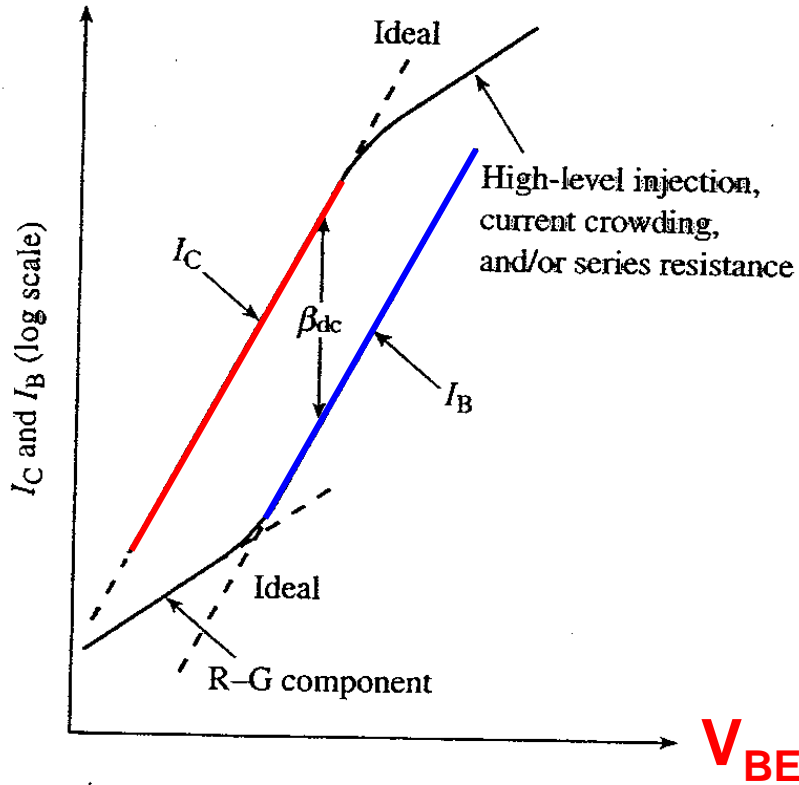

$$\beta_{DC} = \frac{I_C}{I_B}$$

Common emitter
Current Gain

$$\alpha_{DC} = \frac{I_C}{I_E}$$

DC transfer gain


$$\frac{I_C}{A} \approx -\frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1)$$

$$\frac{I_B}{A} \approx \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1)$$


$$\beta_{DC} \approx \frac{D_n W_E n_{i,B}^2 N_E}{W_B D_p n_{i,E}^2 N_B}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{I_C}{I_E - I_C} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$$

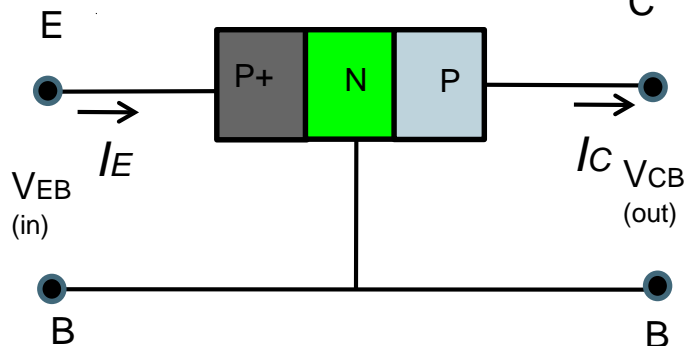Properties are related – (transistor did not change)



Gummel Plot

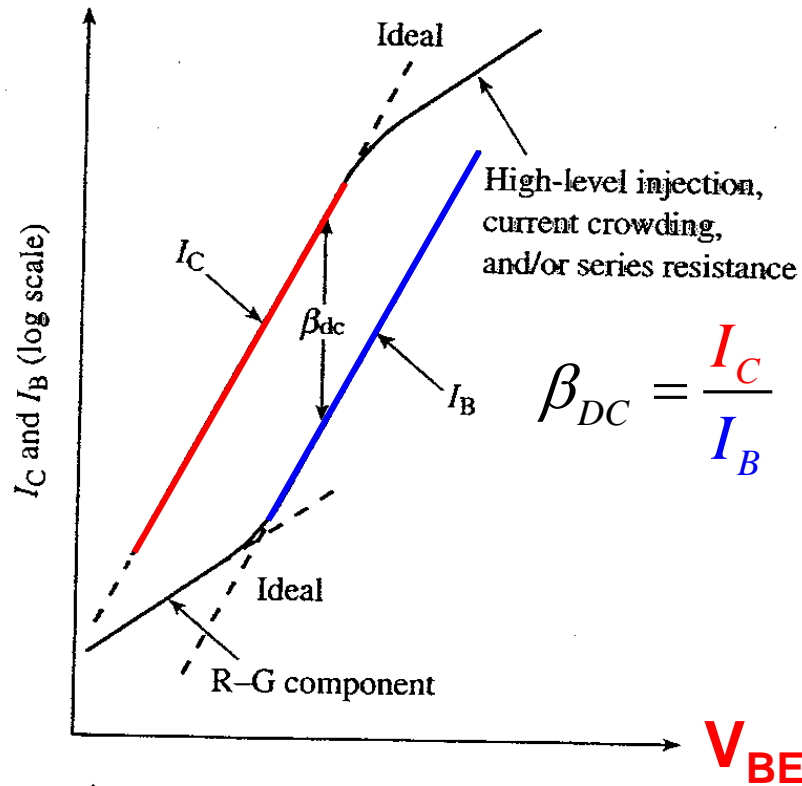



$$\frac{I_C}{A} \approx - \frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1)$$

$$\frac{I_B}{A} \approx \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1)$$

$$\beta_{DC} \approx \frac{D_n W_E n_{i,B}^2 N_E}{W_B D_p n_{i,E}^2 N_B}$$

- Gummel Plot: I_C and I_B on semi-log plot
 => device characterization
 => quality of the emitter-base junction with constant base-collector bias
 => DC gain β , base and collector ideality factors, series resistances and leakage currents.

Gummel Plot and Current Gain

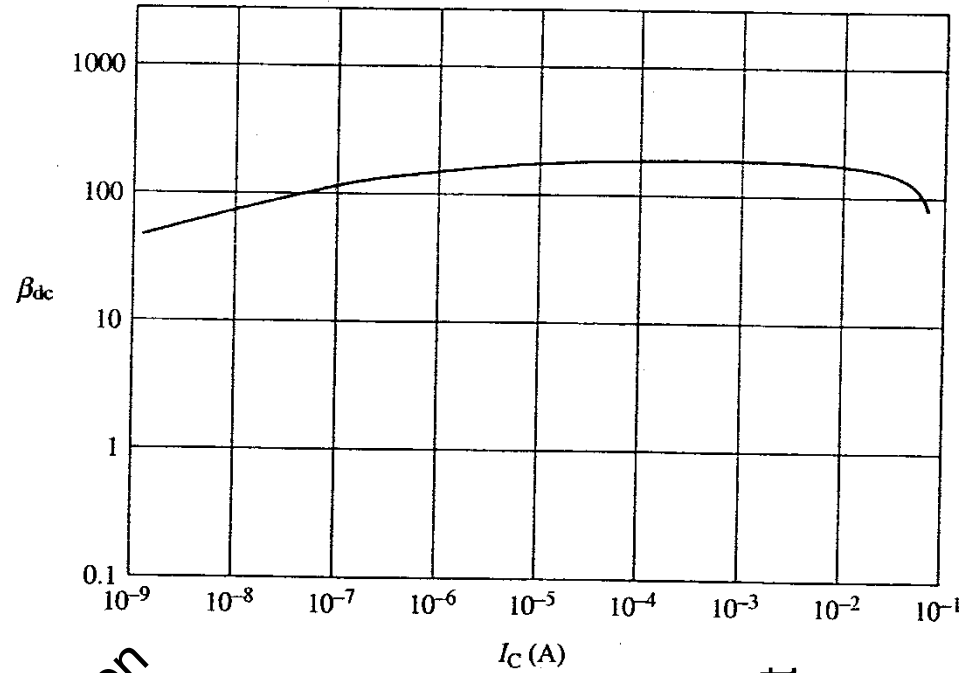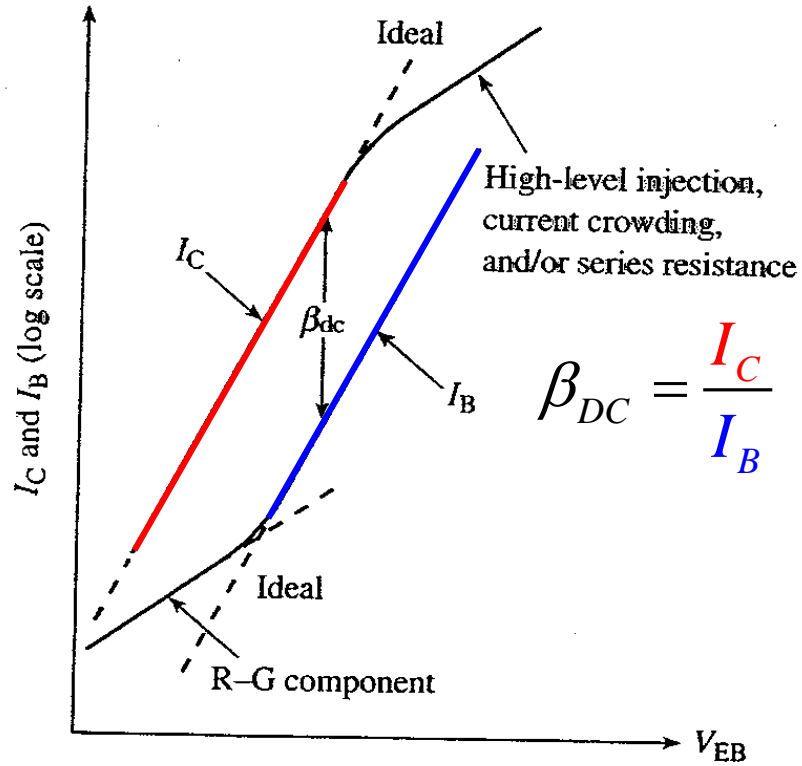

Base recombination
 \Rightarrow roll-off


High injection
 collector current
 \Rightarrow roll-off
 Base current
 does not roll off

$$\frac{I_C}{A} \approx -\frac{qD_n n_{i,B}^2}{W_B N_B} (e^{qV_{BE}\beta} - 1)$$

$$\frac{I_B}{A} \approx \frac{qD_p n_{i,E}^2}{W_E N_E} (e^{qV_{BE}\beta} - 1)$$


$$\beta_{DC} \approx \frac{D_n}{W_B} \frac{W_E}{D_p} \frac{n_{i,B}^2}{n_{i,E}^2} \frac{N_E}{N_B}$$

Gummel Plot & Output Characteristic

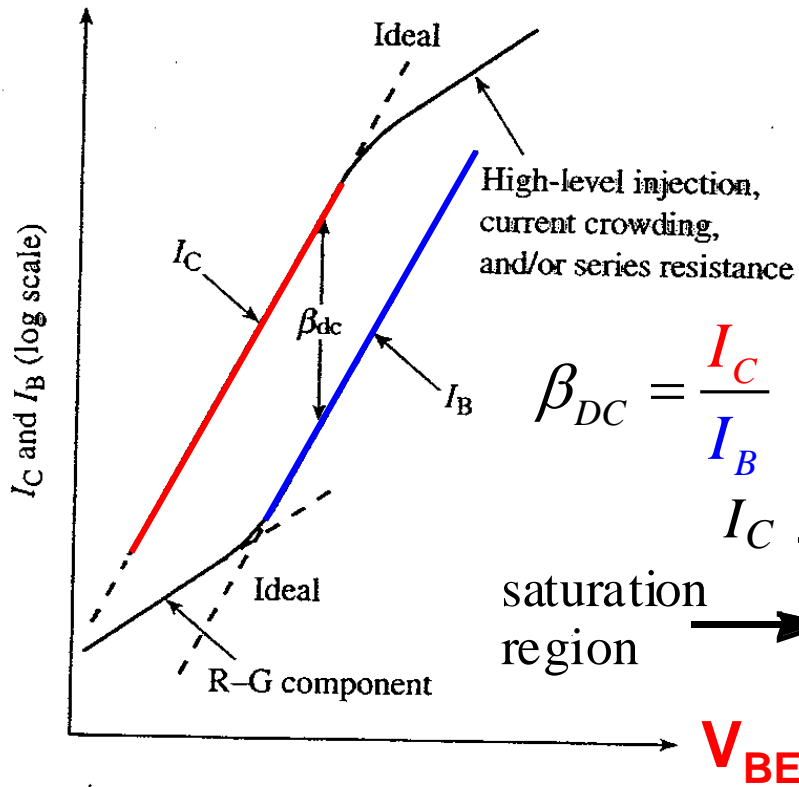

$$\frac{I_C}{A} \approx - \frac{q D_n n_{i,B}^2}{W_B N_B} (e^{q V_{BE} \beta} - 1)$$
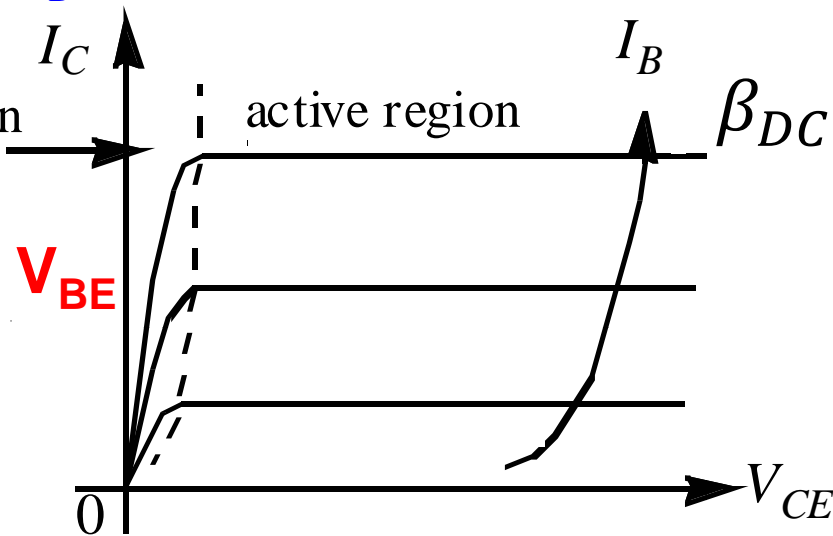
$$\frac{I_B}{A} \approx \frac{q D_p n_{i,E}^2}{W_E N_E} (e^{q V_{BE} \beta} - 1)$$



$$\beta_{DC} \approx \frac{D_n W_E n_{i,B}^2 N_E}{W_B D_p n_{i,E}^2 N_B}$$

How to make a Good Silicon Transistor?

For a given Emitter length

$$\beta_{DC} \approx \frac{D_n W_E}{W_B D_p} \frac{n_{i,B}^2 N_E}{n_{i,E}^2 N_B}$$

~1, same material
primarily determined
by bandgap



Make-Base short ...
(few mm in 1950s, 200 Å now)
Want high gradient of carrier density

Emitter doping higher
than Base doping

Base doping hard to control
Emitter doping easier


Doping for Gain ...

$$\beta_{DC} \approx \frac{D_n}{W_B} \frac{W_E}{D_p} \frac{\cancel{n_{i,B}^2}}{\cancel{n_{i,E}^2}} \frac{N_E}{N_B}$$

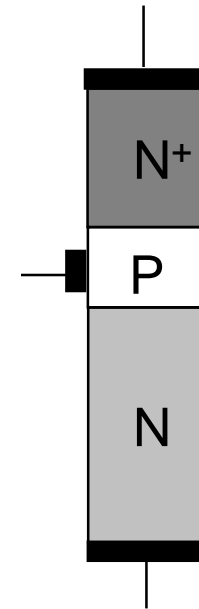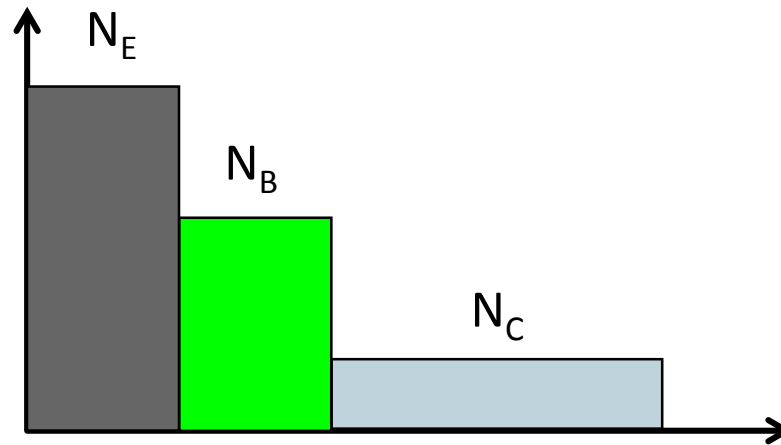

Section 25


Bipolar Junction Transistor - Design

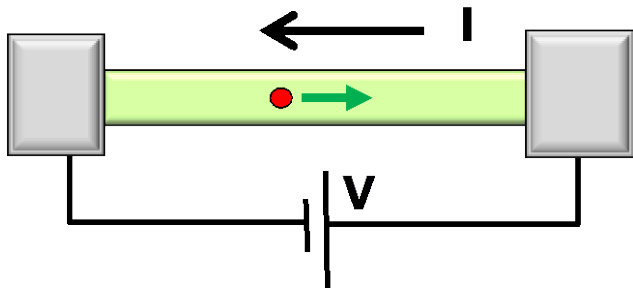

$$I = G \times V$$

$$= q \times n \times v \times A$$



↑ charge density ↑ velocity area

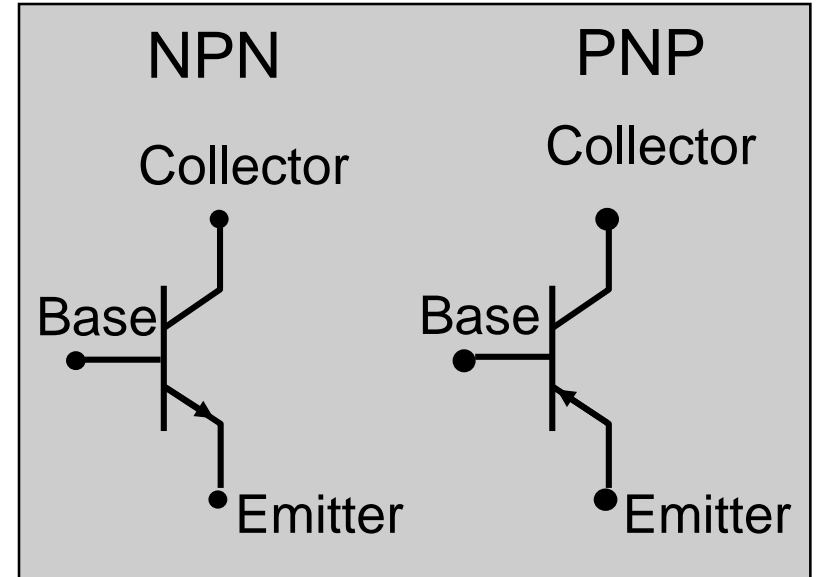

- > • 25.1 Current gain in BJTs
- 25.2




- > • 25.3
- > • 25.4
- > • 25.5
- > • 25.6

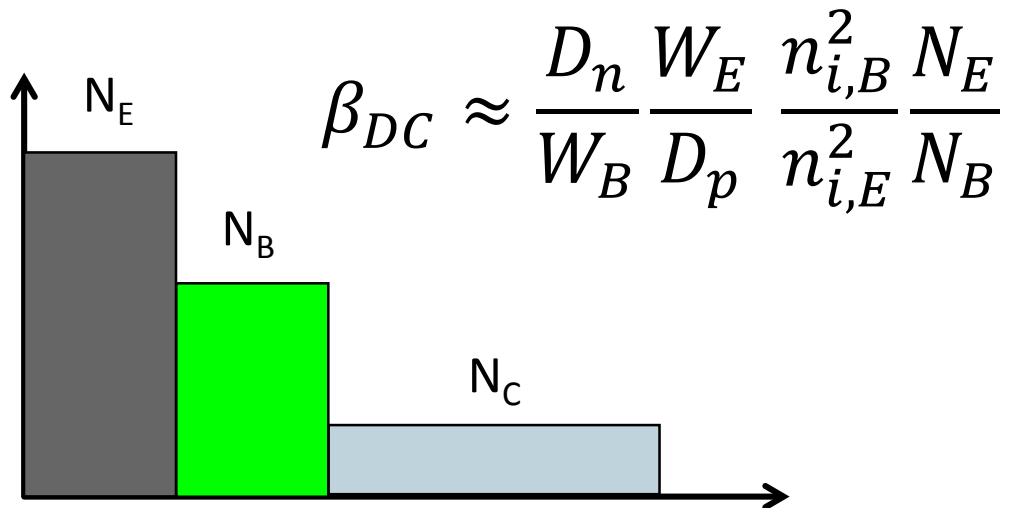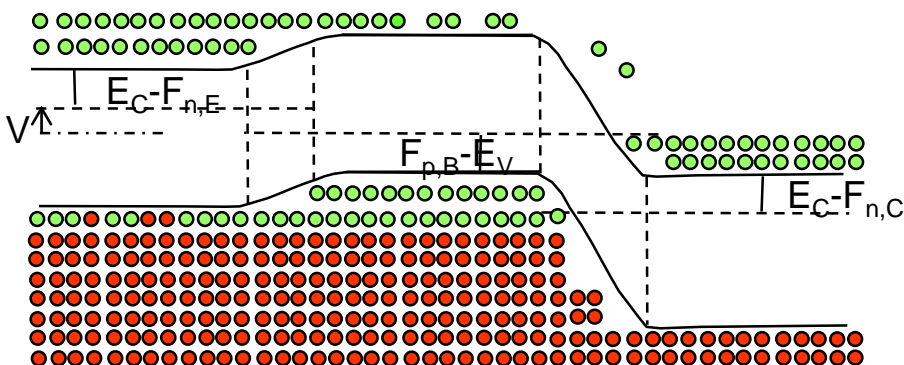

Section 25


Bipolar Junction Transistor - Design

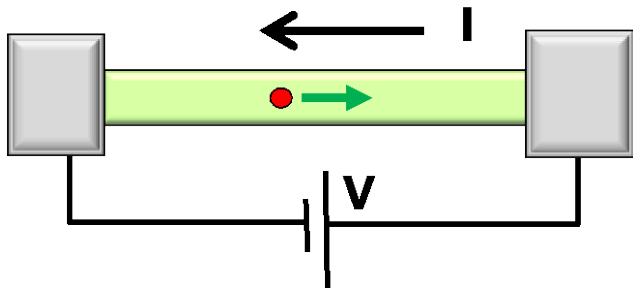

$$I = G \times V$$



$$= q \times n \times v \times A$$

↑ charge density
 ↑ velocity
 area

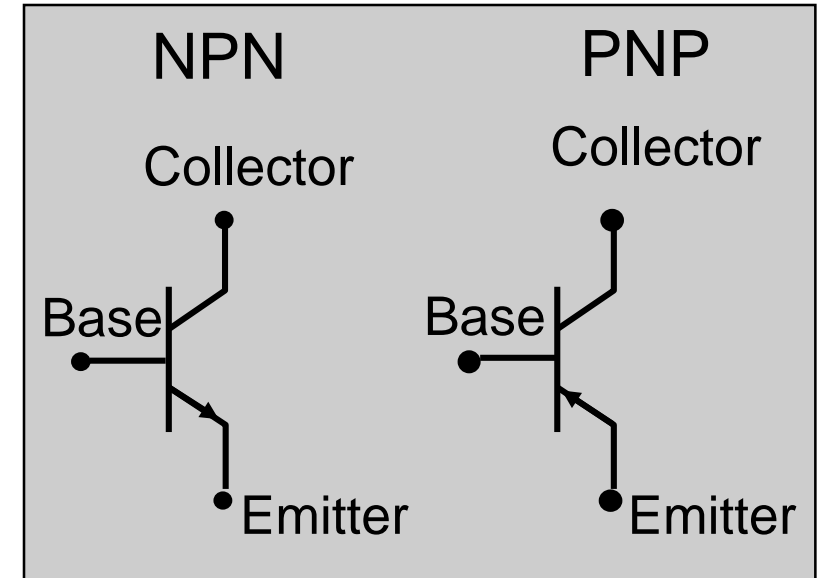

What's wrong with the recipe?
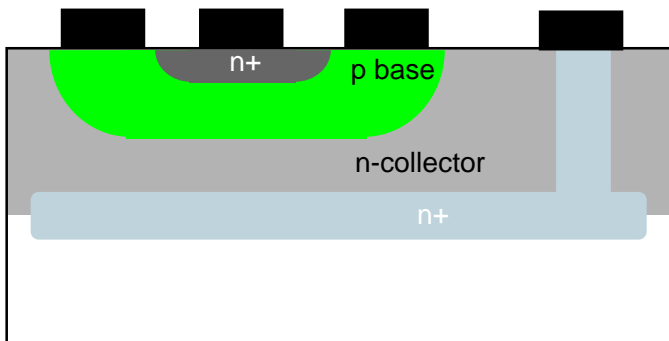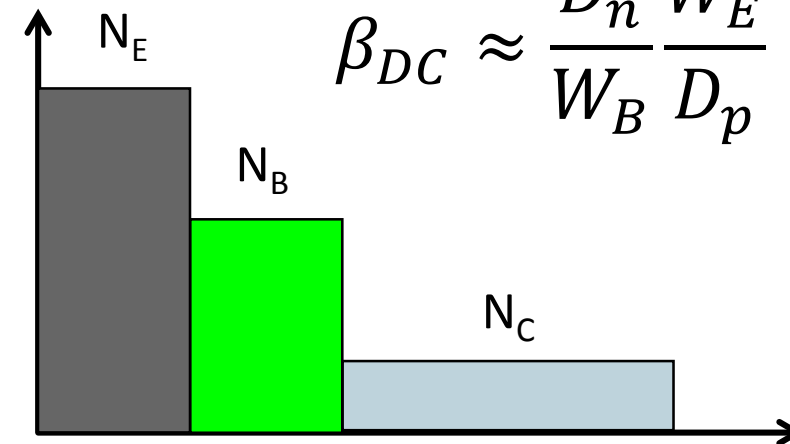
$$\beta_{DC} \approx \frac{D_n}{W_B} \frac{W_E}{D_p} \frac{n_{i,B}^2}{n_{i,E}^2} \frac{N_E}{N_B}$$



- 25.1 Current gain in BJTs
- 25.2 Base Doping Design
 - » Current Crowding – Non-Uniform Turn-On
 - » Punch-through
 - » Base Width Modulation

- 25.3
- 25.4
- 25.5
- 25.6

>

>

>

>

>

>